
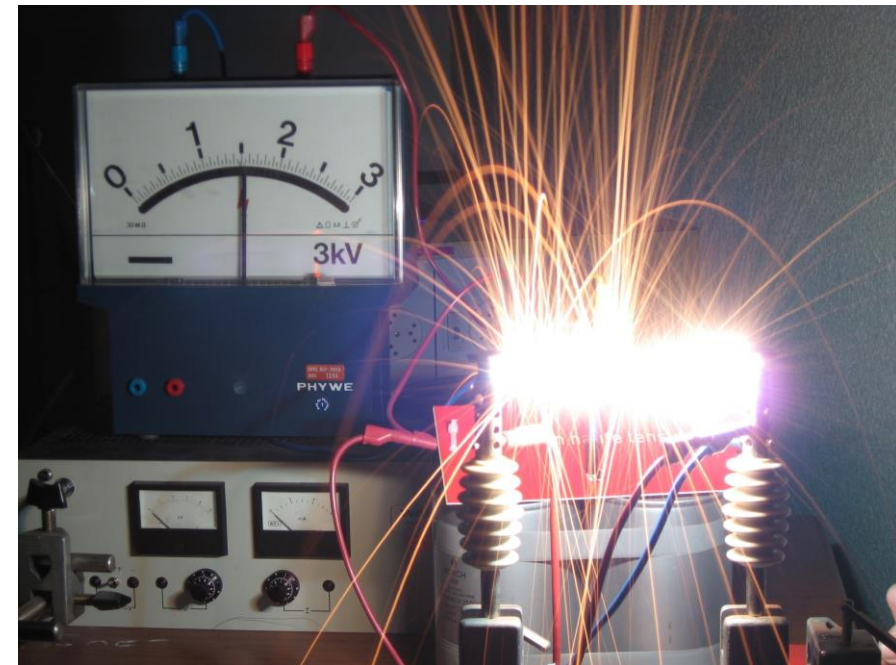


Week 6:

Current, Resistance, RC Circuit

Energy of a capacitor (copper wire)

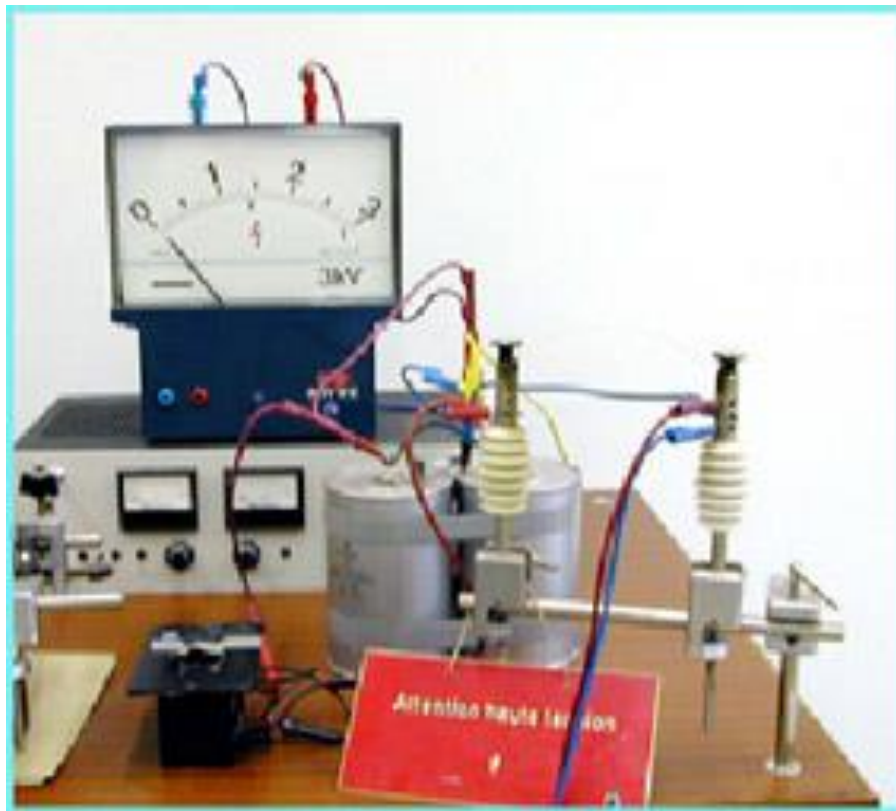The purpose of this experiment is to illustrate the **internal resistance** of an object (here a copper wire) by vaporizing it by Joule effect using a capacitor. The capacitor will pass a lot of electrical energy through the copper wire in a very short time, which will have the effect of increasing its temperature very quickly to the point of vaporizing this cable almost instantaneously.



<https://auditoires-physique.epfl.ch/experiment/422/energie-dun-condensateur-fil-de-cuivre>


Electric Current

Electric field in conductors and resistivity:

- E inside of conductors is 0 only in static (no current)
- Electrons in a conductor move like molecules in a gas
- Upon applying potential difference electrons in addition drift toward +
- Their motion is hindered by scattering on atoms (also on impurities) – this causes electric resistivity.
- The higher is T, the higher is chaotic thermal motion – larger resistance.

Electric current: Charge flux per unit time through a surface A

Let's consider the total charge crossing a conductor cross-section each unit of time

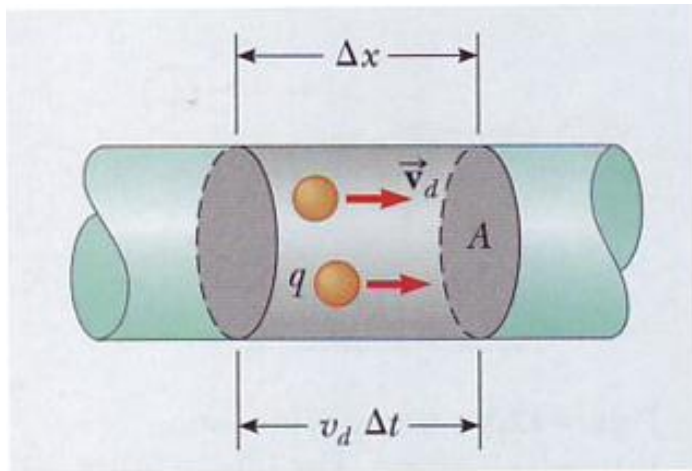

Note 1: 1 A = 1 C/s

Electron charge: $e \cong 1.6 \times 10^{-19}$ C

⇒ a current of 1 A consists of 6×10^{18} electrons/s through the surface A

$$I \triangleq \frac{dQ}{dt} = \frac{\Delta Q}{\Delta t} = \frac{\rho A \Delta x}{\Delta t} = (nq v_d) A = JA$$

Charge density: $\rho = nq$ [C/m³]

Density of charged particles: n [1/m³]

Current density: $\mathbf{J} = nq\mathbf{v}_d = \rho\mathbf{v}_d$ [A/m²]

Current: $I = JA$ [A]

Charge "drift" Speed: $\mathbf{v}_d$ [m/s]

typical currents:

- 100 W light bulb: roughly 1A
- car starter motor: roughly 200A
- TV, computer, phone: nA to mA

current is a scalar (not a vector)

- has a **sign** associated with it
- **conventional** current is flow of **positive** charge

Electric Current density


- current density J is **current per area** or, equivalently,

charge per area and time

unit of J : A/m^2


directions are important ...

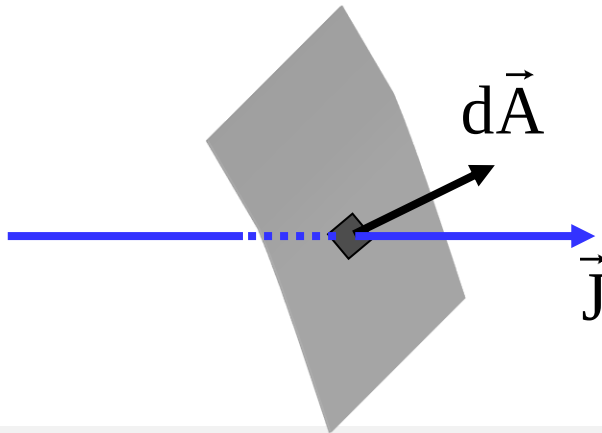- current density is a **vector**
(direction is direction of velocity of positive charge carriers)



- current density $\vec{j}$ flowing through infinitesimal area $d\vec{A}$ produces infinitesimal current $dI = \vec{j} \cdot d\vec{A}$
- total current passing through A is
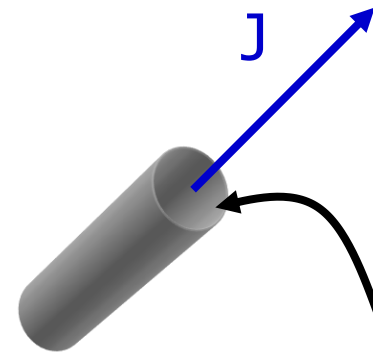
$$I = \int_{\text{surface}} \vec{j} \cdot d\vec{A}$$



cross section A of wire


- if $\vec{j}$ is uniform and parallel to $d\vec{A}$:

$$I = \int_{\text{surface}} \vec{j} \cdot d\vec{A} = J \int_{\text{surface}} dA = JA \Rightarrow \boxed{J = \frac{I}{A}}$$

Currents in Materials

Metals are conductors because they have “free” electrons, which are not bound to metal atoms.

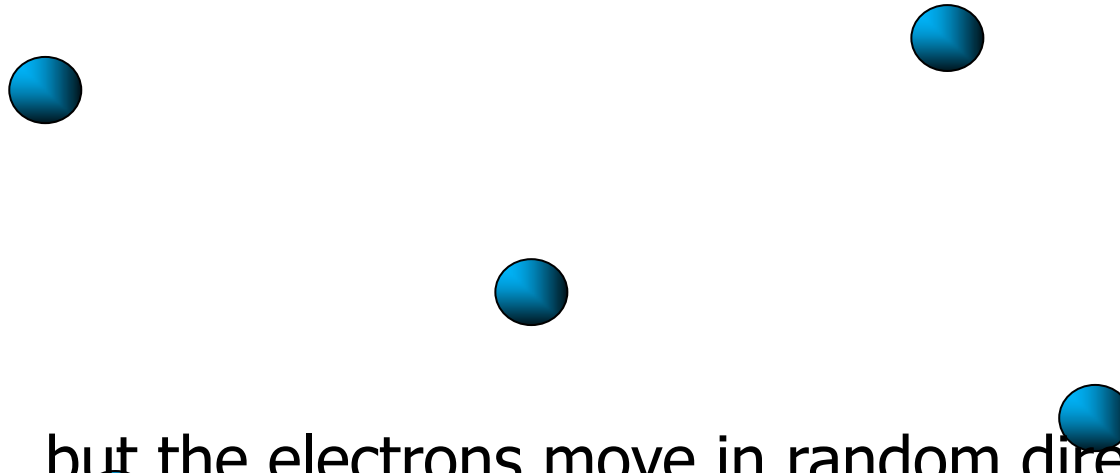
In a cubic meter of a typical conductor there roughly 10^{28} free electrons, moving with typical speeds of 1,000,000 m/s...




...but the electrons move in random directions, and there is no net flow of charge, until you apply an electric field.

Ohm's Law
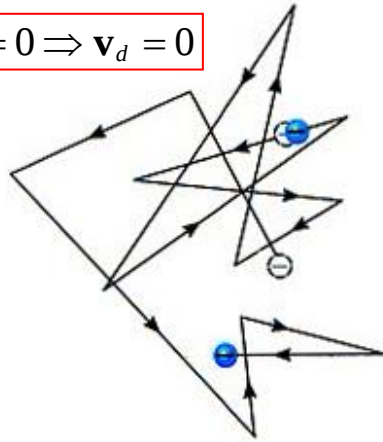
$$\mathbf{E} = 0 \Rightarrow \mathbf{v}_d = 0$$


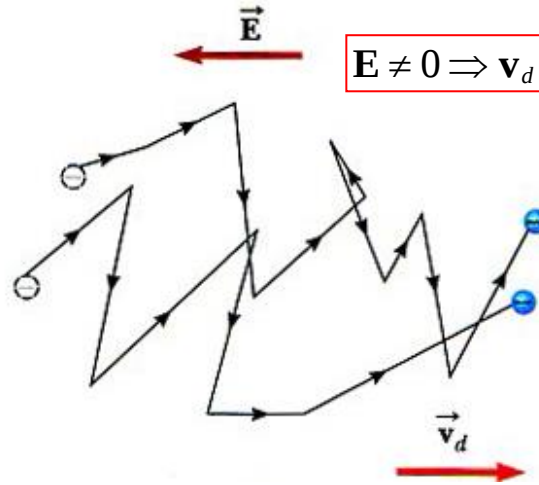
$$\mathbf{E} \neq 0 \Rightarrow \mathbf{v}_d \neq 0$$



Due to collisions with fixed ions, the speed of free electrons in a solid reaches a limiting value v_d («drift» velocity) proportional to the electric field.
($\approx$ viscous friction)

For many materials (including most metals), the ratio of the current density to the electric field is a constant σ that is independent of the electric field producing the current.

Drude Model:

$$\mathbf{F} = q\mathbf{E} \Rightarrow \mathbf{a} = \frac{q}{m_e}\mathbf{E} \Rightarrow$$

For a single charge between two collisions:

$$\mathbf{v}(t) = \mathbf{v}(0) + \frac{q}{m_e}\mathbf{E}t$$


For a large number of charges:

$$\langle \mathbf{v}(0) \rangle = 0 \Rightarrow$$

$$\langle \mathbf{v} \rangle \triangleq \mathbf{v}_d = \langle \mathbf{v}(0) \rangle + \frac{q\mathbf{E}}{m_e} \langle t \rangle \cong \frac{q}{m_e} E \tau$$

τ : average time between two collisions

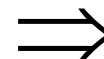$\mathbf{v}_d$: "drift" velocity (effective average speed in the direction of the field $\mathbf{E}$)



$$\mathbf{v}_d = \frac{q}{m_e}\mathbf{E}\tau$$

$\Rightarrow$

$$\mathbf{J} \equiv nq\mathbf{v}_d = \frac{nq^2\mathbf{E}}{m_e}\tau = \sigma\mathbf{E}$$

$\Rightarrow$


$$\mathbf{J} = \sigma\mathbf{E} \quad \text{Ohm's law "local"}$$

Electrical conductivity [$1/\Omega\text{m} = \text{S/m}$]:

$$\sigma \equiv \frac{nq^2}{m_e}\tau$$

Electrical Resistivity [Ωm]: $\rho \equiv \frac{m_e}{nq^2\tau}$

Electric Current and Resistance

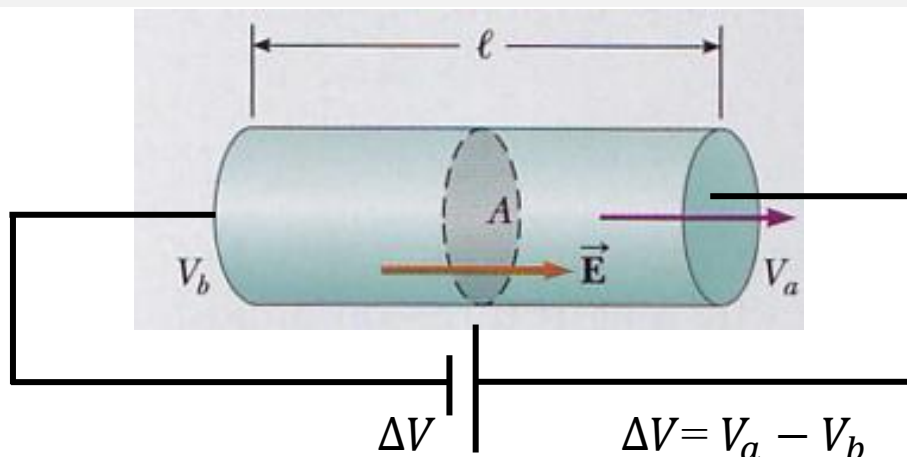

$\Delta V = V_a - V_b$
(generated,
for instance,
by a battery)

$$\mathbf{E} = -\nabla V \quad \text{stationary condition}$$

$\Rightarrow$

$$\mathbf{E}(\mathbf{x}) = E_0 \hat{\mathbf{x}} = \text{const}$$

$\Rightarrow$

$$\int_0^l \mathbf{E} \cdot d\mathbf{l} = \Delta V \quad \int_0^l \mathbf{E} \cdot d\mathbf{l} = E_0 l$$

$\Rightarrow$

$$E_0 = \frac{\Delta V}{l}$$

$\mathbf{E}$ is not zero in the conductor.
(stationary current but not static charges...
therefore the condition is not "electrostatic")

conductor	ρ [$\Omega \cdot \text{m}$]
Copper	$1.7 \cdot 10^{-8}$
Iron	10^{-7}
Glass	10^{+12}

If the ends of the conducting wire are connected to a battery, all points on the loop are not at the same potential. **The battery sets up a potential difference between the ends of the loop, creating an electric field within the wire.** The electric field exerts forces on the electrons in the wire, causing them to move in the wire and therefore **creating a current**

In some materials, the current density is proportional to the electric field

$$\mathbf{J} = \frac{I}{A} = \sigma \mathbf{E} = \sigma \frac{\Delta V}{l}$$

$\Rightarrow$

$$\Delta V = \frac{l}{\sigma} \mathbf{J} = \left(\frac{l}{\sigma A}\right) I = \mathbf{R} I$$

$\Rightarrow$

$$\Delta V = R I$$

$$R \triangleq \left(\frac{l}{\sigma A}\right) = \rho \frac{l}{A}$$

Ohm's law "global"

ρ is called resistivity


Unit of Resistance $\mathbf{R}$: $1 \Omega = 1\text{V} / 1\text{A}$

Unit of resistivity ρ : $\Omega \cdot \text{m}$

Resistance of a wire

current in a wire:

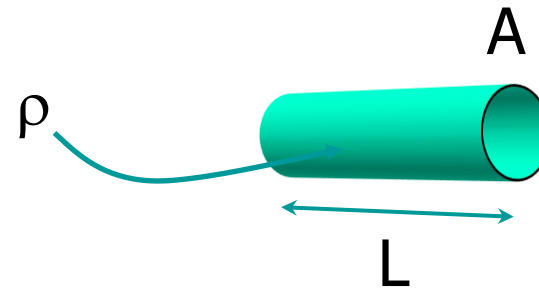- length L , cross section A
- material of resistivity ρ



start from $E = \rho J$

$$V = EL = \rho J L = \rho \frac{I}{A} L = IR$$

$$R = \frac{\rho L}{A}$$

Ohm' law (device version)

$$V = IR$$

resistance of the wire,

unit $\frac{V}{A} = \Omega$ (Ohm)

- resistance of wire (or other device) measures how easily charge flows through it
- the longer a wire, the harder it is to push electrons through it
- the greater the cross-sectional area, the “easier” it is to push electrons through it
- the greater the resistivity, the “harder” it is for the electrons to move in the material

Distinguish:



Resistivity = material's property

Resistance = device property

$$\Delta V = RI$$

$$R \triangleq \left(\frac{l}{\sigma A} \right) = \rho \frac{l}{A}$$

Ohm's law "global"

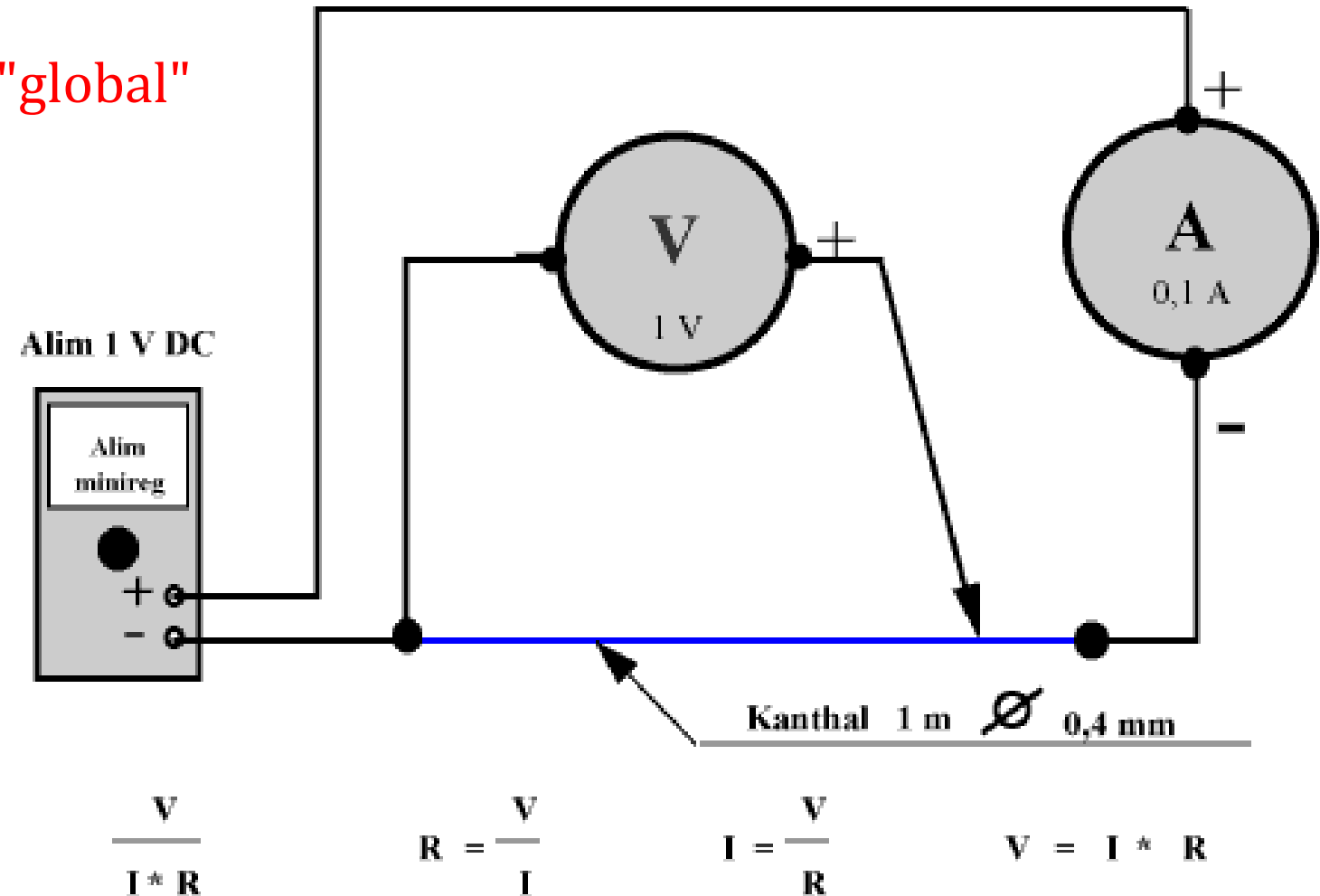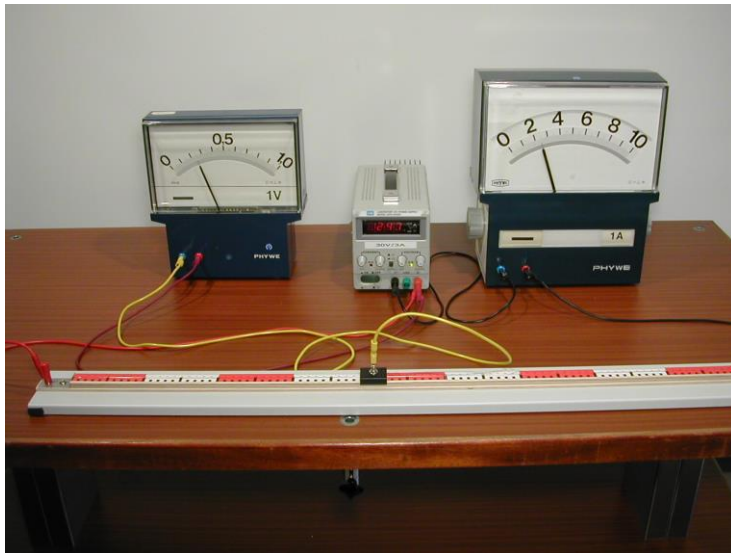

<https://auditoires-physique.epfl.ch/experiment/526/loi-dohm-sur-un-fil>

Notes:

1. Problem of the notation

Beware of confusion between: ρ (resistivity) and ρ (charge density in a volume),
 σ (conductivity) and σ (surface charge density)

2. Speed of thermal agitation and mean time between two collisions:

$\langle \mathbf{v}(0) \rangle = 0$ but $\langle v(0) \rangle \neq 0$ (thermal agitation of electrons)

$$\langle v(0) \rangle \cong v_{th} = \sqrt{\frac{3kT}{m_e}} \cong 10^5 \text{ m/s} \quad (!!) \quad \text{for } T \cong 300 \text{ K}$$

The Mean Free Path λ is a little larger than the distance between the atoms d_{atoms} .

So, the time between collisions is: $\tau \sim \frac{\lambda}{v_{th}} \sim \frac{10d_{atoms}}{v_{th}} \sim \frac{10^{-9} \text{ m}}{10^5 \text{ m/s}} \sim 10^{-14} \text{ s}$

3. Drift velocity:

For a copper wire ($n \cong 8.5 \times 10^{28}$ électrons/m³)

with section $A=1 \text{ mm}^2$ with a current $I=10 \text{ A} \Rightarrow$

$$J = env_d = \frac{I}{A} = 10^7 \text{ A/m}^2 \quad \Rightarrow v_d = \frac{J}{en} \cong 1 \text{ mm/s} \quad (!!) \quad \Rightarrow v_d \ll v_{th} \quad (!!)$$

4. Field $\mathbf{E} = 0$ or $\mathbf{E} \neq 0$ in a conductor?

$\mathbf{E} = 0$ for a conductor in electrostatic conditions (static charges, so for $\mathbf{J}=0$).

For a Perfect Conductor (with $\sigma = \infty$), $\mathbf{E} = \frac{\mathbf{J}}{\sigma} = 0$ also for $\mathbf{J} \neq 0$.

For a real conductor $\mathbf{E} = 0$ in electrostatic conditions ("static charges") but $\mathbf{E} \neq 0$ for $\mathbf{J} \neq 0$.

5. Phenomenologically, the current density in many systems obeys Ohm's law. But Ohm's law is not a "mathematical" consequence of Maxwell's equations.

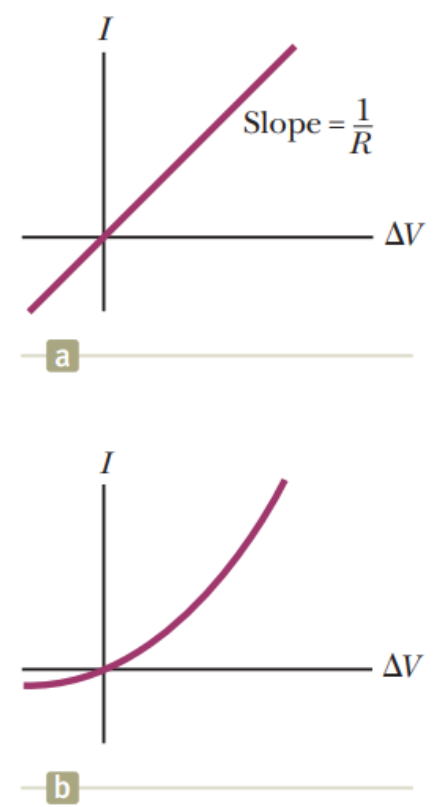


Figure 27.7 (a) The current–potential difference curve for an ohmic material. The curve is linear, and the slope is equal to the inverse of the resistance of the conductor. (b) A nonlinear current–potential difference curve for a junction diode. This device does not obey Ohm's law.

Table 27.2 Resistivities and Temperature Coefficients of Resistivity for Various Materials

Material	Resistivity ^a ($\Omega \cdot \text{m}$)	Temperature Coefficient ^b α [$(^\circ\text{C})^{-1}$]
Silver	1.59×10^{-8}	3.8×10^{-3}
Copper	1.7×10^{-8}	3.9×10^{-3}
Gold	2.44×10^{-8}	3.4×10^{-3}
Aluminum	2.82×10^{-8}	3.9×10^{-3}
Tungsten	5.6×10^{-8}	4.5×10^{-3}
Iron	10×10^{-8}	5.0×10^{-3}
Platinum	11×10^{-8}	3.92×10^{-3}
Lead	22×10^{-8}	3.9×10^{-3}
Nichrome ^c	1.00×10^{-6}	0.4×10^{-3}
Carbon	3.5×10^{-5}	-0.5×10^{-3}
Germanium	0.46	-48×10^{-3}
Silicon ^d	2.3×10^3	-75×10^{-3}
Glass	10^{10} to 10^{14}	
Hard rubber	$\sim 10^{13}$	
Sulfur	10^{15}	
Quartz (fused)	75×10^{16}	

^a All values at 20°C . All elements in this table are assumed to be free of impurities.



^b See Section 27.4.

^c A nickel–chromium alloy commonly used in heating elements. The resistivity of Nichrome varies with composition and ranges between 1.00×10^{-6} and $1.50 \times 10^{-6} \Omega \cdot \text{m}$.

^d The resistivity of silicon is very sensitive to purity. The value can be changed by several orders of magnitude when it is doped with other atoms.

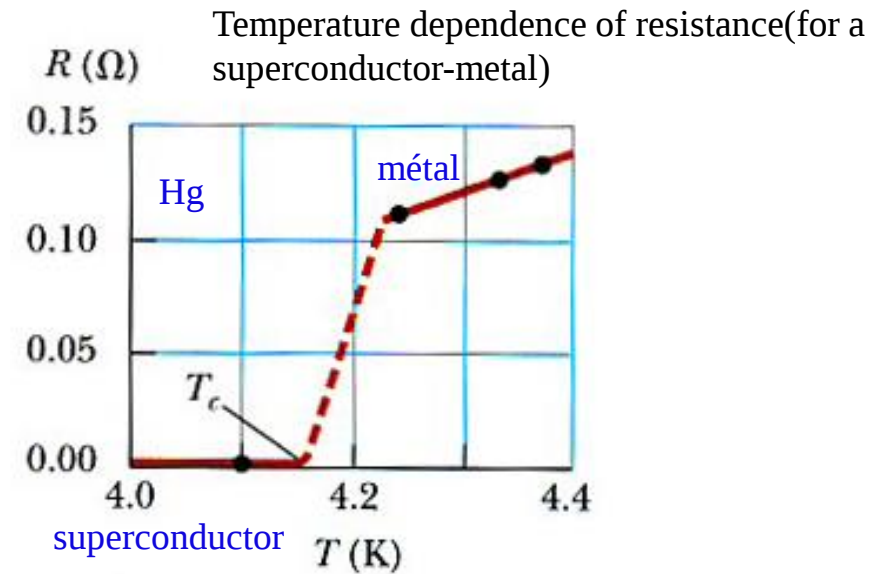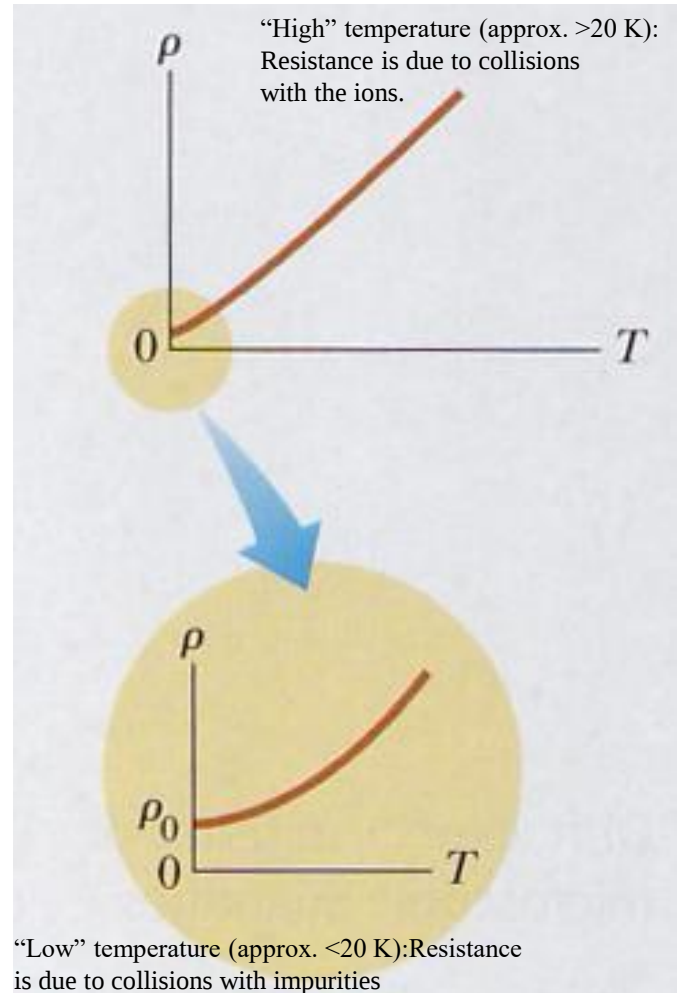6. Resistance and Resistivity for Metals and Other Materials.


Temperature dependence of resistivity (for a metal)



One truly remarkable feature of superconductors is that once a current is set up in them, it persists without any applied potential difference (because $R = 0$). Steady currents have been observed to persist in superconducting loops for several years with no apparent decay!

Ideal Direct Current (DC) Circuits

$$I = \frac{V}{R}$$

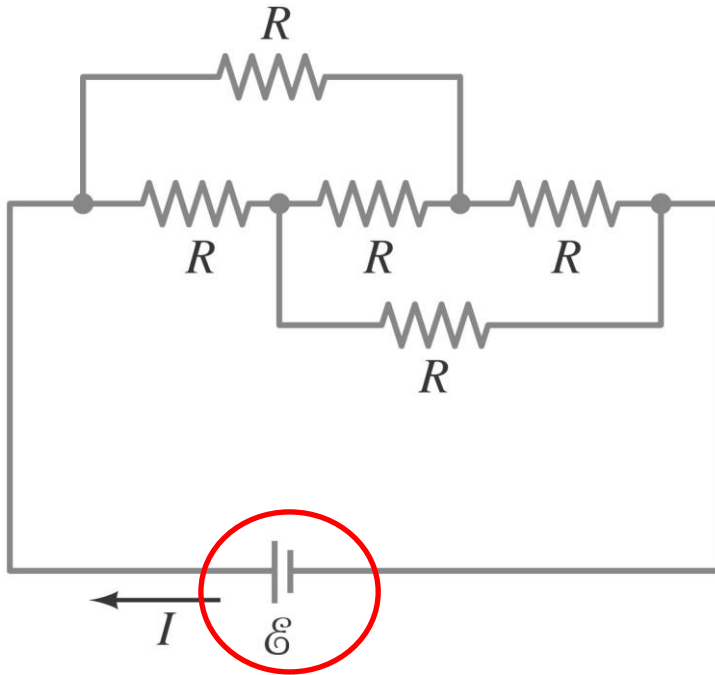

Idealization (convention):

- Connecting **wires** have **no resistance** (or **inductance** or **capacity**).
- All resistance is in special elements labeled **R** .
- All capacity is in elements labeled **C** .


Properties of battery ?

Ideal versus real voltage sources

- **ideal** battery (or other voltage source):
voltage does **not** depend on the current flowing
- **real** battery: voltage does depend on current,
typically voltage **decreases** with increasing current (load)

How to model a real battery?

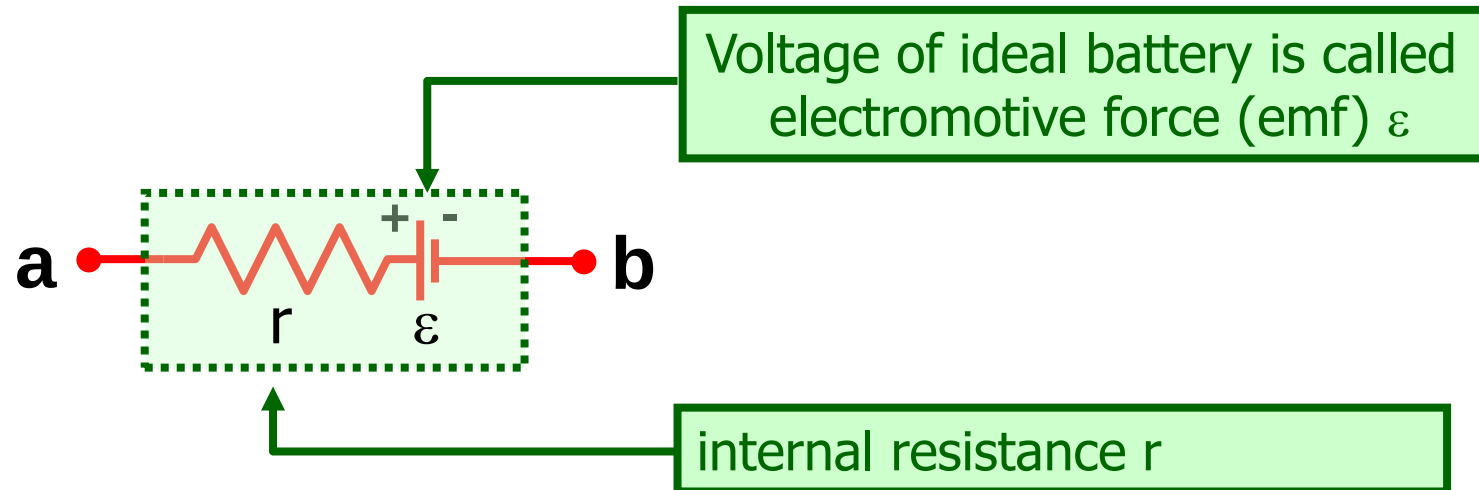- real battery consists of ideal battery + internal resistance



EMF and terminal voltage


The electromotive force (emf) of a voltage source is the potential difference it produces when no current is flowing.

Can the emf be measured?

- hook up a voltmeter:
- as soon as you connect the voltmeter, current flows
- you can only measure **terminal voltage** V_{ab} , but not emf ε

An ideal voltmeter would be able to measure ε .

emf is not a force!

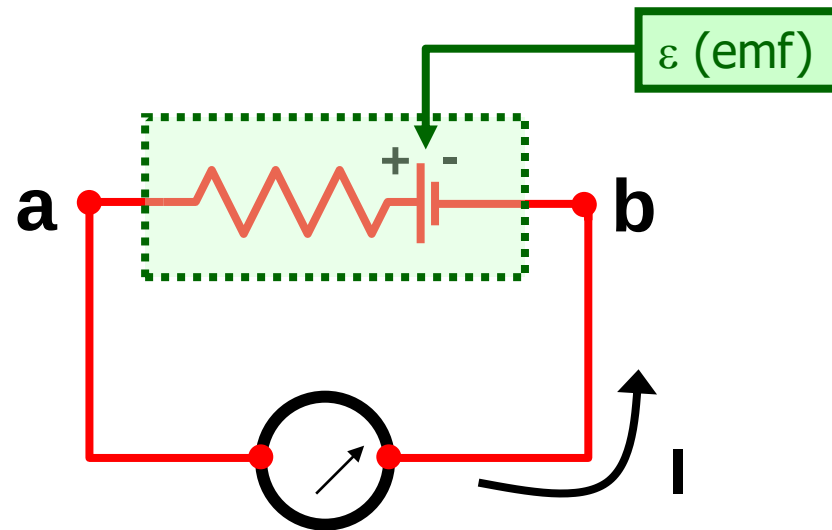


The "battery" is everything inside the green box.

EMF and Terminal Voltage

We will generally use a **battery** as a **source of energy** for circuits in our discussion.

battery

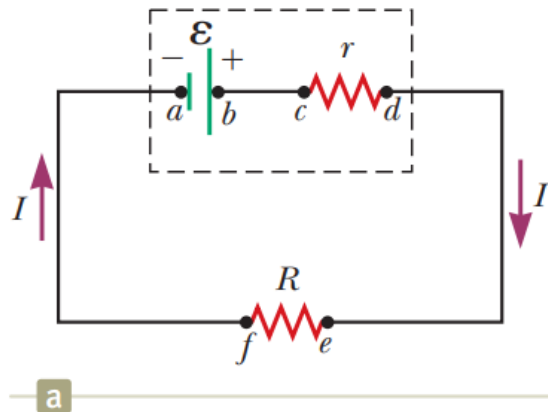

Electric circuit needs battery or voltage generator to produce current – these are called, in general, sources of **electromotive force** (emf, $\mathcal{E}$).

Real battery does have a small **internal resistance** r , such that:



$$V_{ad} = \mathcal{E} - Ir$$

This resistance behaves as though it were in series with the emf.

The actual voltage V_{ad} applied to an external resistor R drops upon increase of the current

$$I_{\max} < \mathcal{E}/r$$

$$(R \gg r)$$

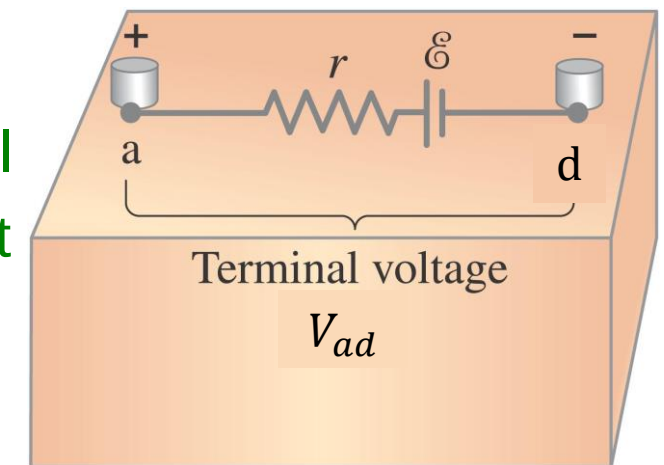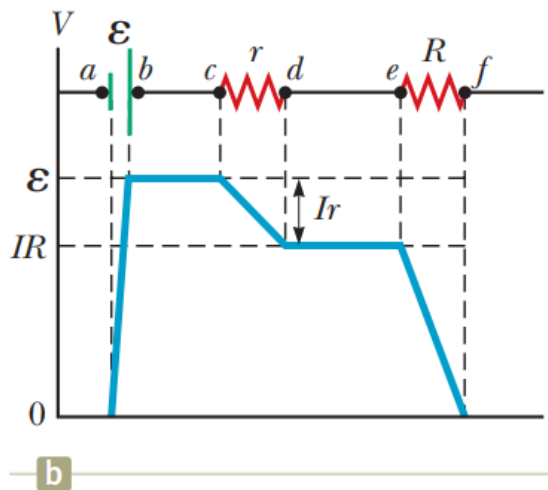

Electric Power

Consider an electric circuit with an ideal battery and a resistor :

- *The battery keeps $\Delta V = \text{constant}$*
- *Current is from + to -*

The energy spent by battery to transfer a charge Q through the resistor:

$$W = \Delta V \cdot Q$$

- *This energy is released in the resistor as heat (Joule effect)*


The **rate** at which the electric potential energy of the system decreases as the charge Q passes through the resistor:

$$P = \frac{dW}{dt} = \frac{d}{dt}(\Delta V \cdot Q) = \Delta V \cdot \frac{dQ}{dt} = \Delta V \cdot I$$

**POWER
DISSIPATED
through R**

$$P = VI = V^2/R = I^2R$$

$$(I = V/R)$$

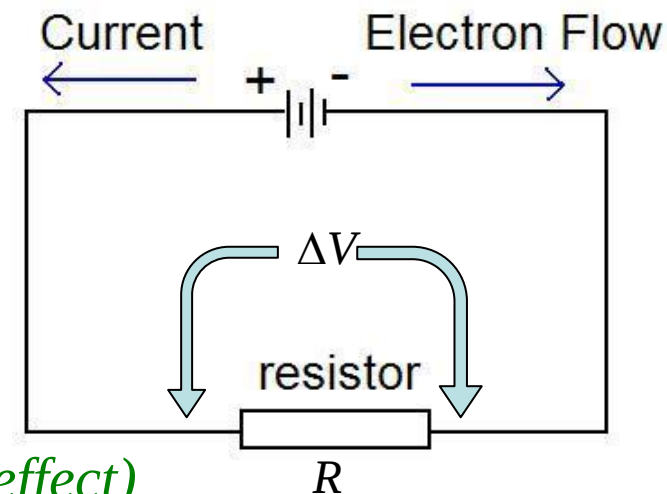

Unless noted otherwise, we shall assume the resistance of the wires is small compared with the resistance of the circuit element so that the energy delivered to the wires is negligible


$$[P] = \text{Watt} = \text{VA}$$

Simple examples for Electric Power

Example I

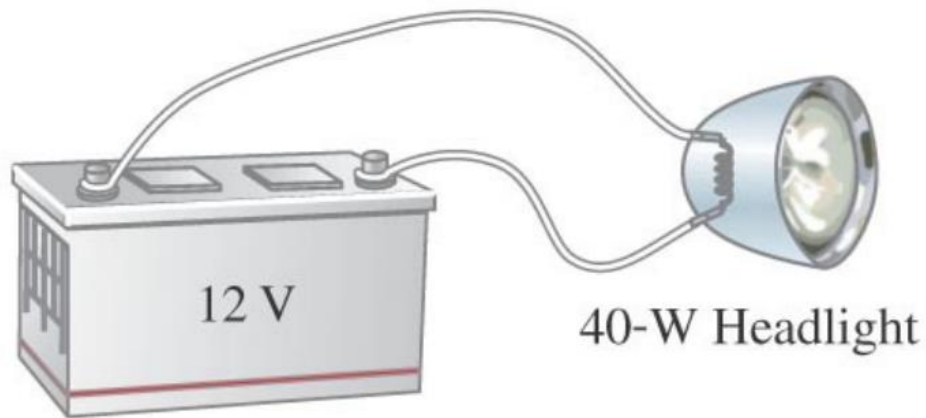Example: Headlights.

Calculate the resistance of a 40-W automobile headlight designed for 12 V.



$$P = V^2 / R, \Rightarrow R = V^2 / P = 144 / 40 = 3.6 \, \Omega$$

Example II

What you pay for on your electric bill is not power, but energy – the power consumption multiplied by the time.


We have been measuring energy in joules, but the electric company measures it in kilowatt-hours, kWh:

$$1 \text{ kWh} = (1000 \text{ W})(3600 \text{ s}) = 3.60 \times 10^6 \text{ J.}$$


$$W = P \cdot t = V \cdot I \cdot t = V \cdot Q$$

Resistors in Series and in Parallel

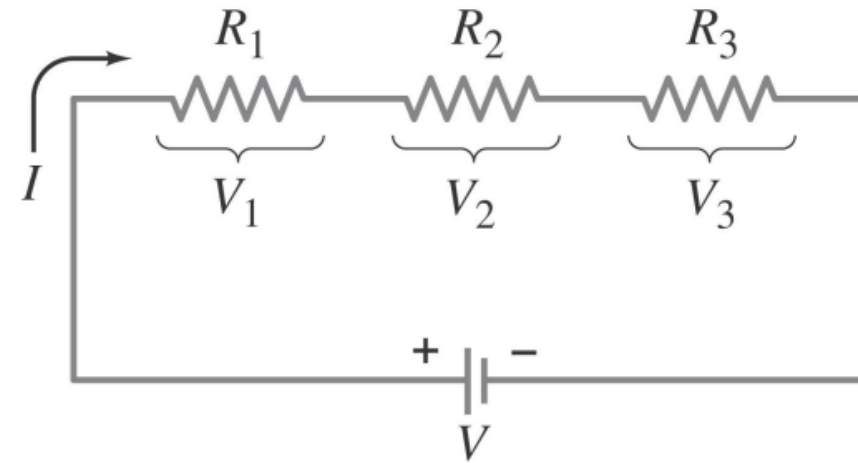Series: a single path from the battery, through each circuit element in turn, then back to the battery.



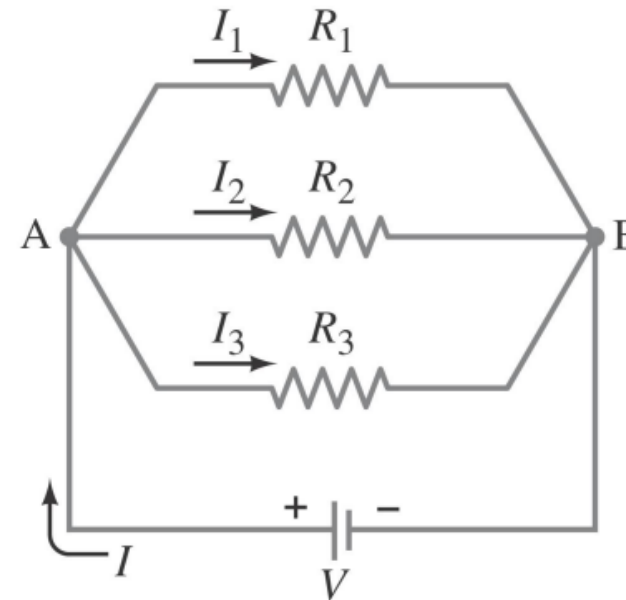Parallel: the current is split; the voltage across each resistor is the same.



Q: What is the **equivalent** resistance?

The equivalent resistance has the same effect on the circuit as the series/parallel combination of resistors; that is, the equivalent resistance draws the same current I from the battery.


Resistors in Series and in Parallel

Series: single circuit; the same current.

$$V = V_1 + V_2 + V_3 = IR_1 + IR_2 + IR_3$$

$$V = IR_{\text{series}} = IR_1 + IR_2 + IR_3$$

$$R_{\text{series}} = R_1 + R_2 + R_3$$

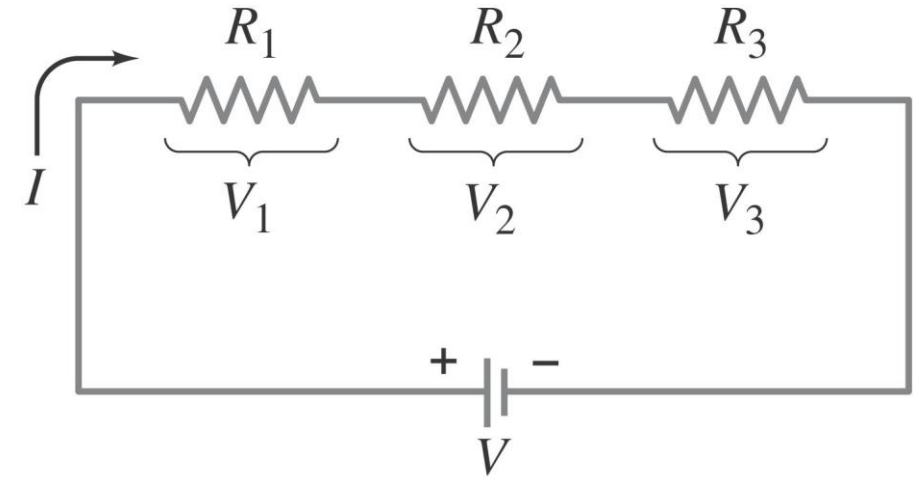


What is the **equivalent** resistance?

Parallel: the current is split; the voltage across each resistor is the same.

$$I = I_1 + I_2 + I_3 = \frac{V}{R_{\text{parallel}}} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} \rightarrow$$

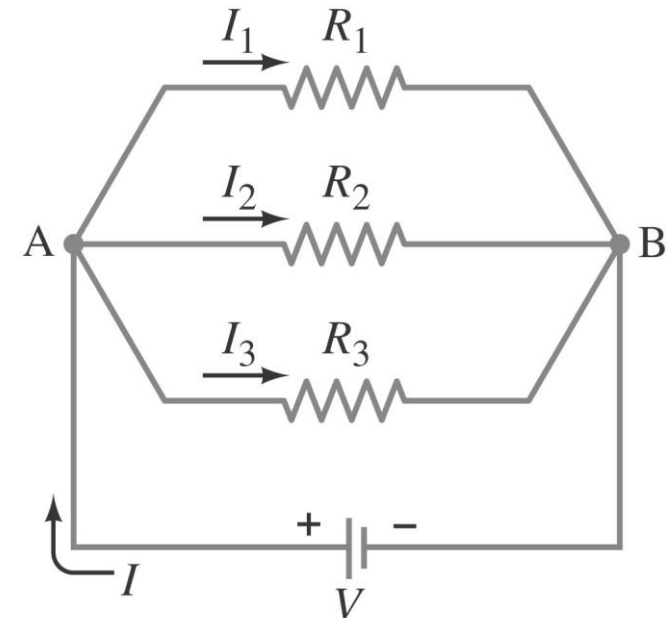
$$\frac{1}{R_{\text{parallel}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



Electric Power at home

$$I = \frac{V}{R_k + r_{\text{wire}}}; \quad P_k = I^2 R_k; \quad P_{\text{wire}} = I^2 r_{\text{wire}} \Rightarrow \eta = \frac{P_k}{P_k + P_{\text{wire}}} = \frac{R_k}{R_k + r_{\text{wire}}}$$

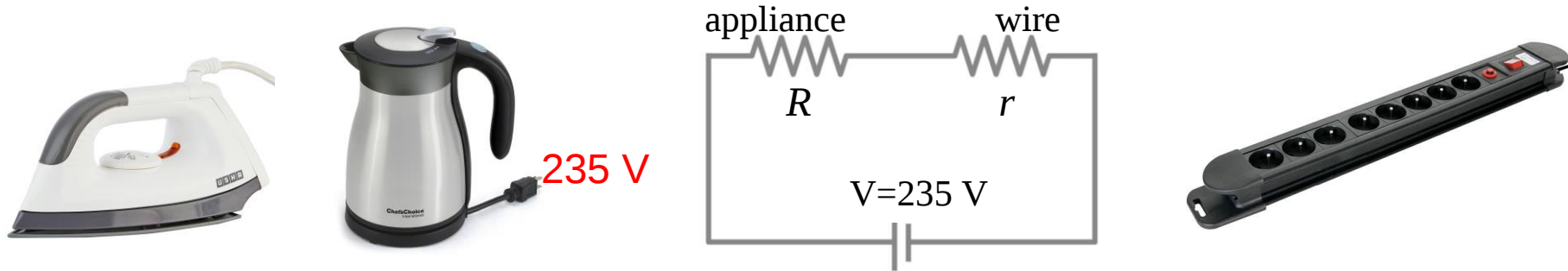$R_k \gg r_{\text{wire}}$ (otherwise loss of energy in the wires = heating of the wires)



Power strip (n -sockets): parallel connection:

$$R_n = \frac{R_k}{n} \Rightarrow I = \frac{V}{R_k/n + r_{\text{wire}}}; \quad \eta = \frac{R_k}{R_k + nr_{\text{wire}}}$$

burns out


switches off



Too high current through a wire can heat it up and inflame (make wires short and thick; respect max current through).


Resistors in Series and in Parallel

Example: Big circuit.

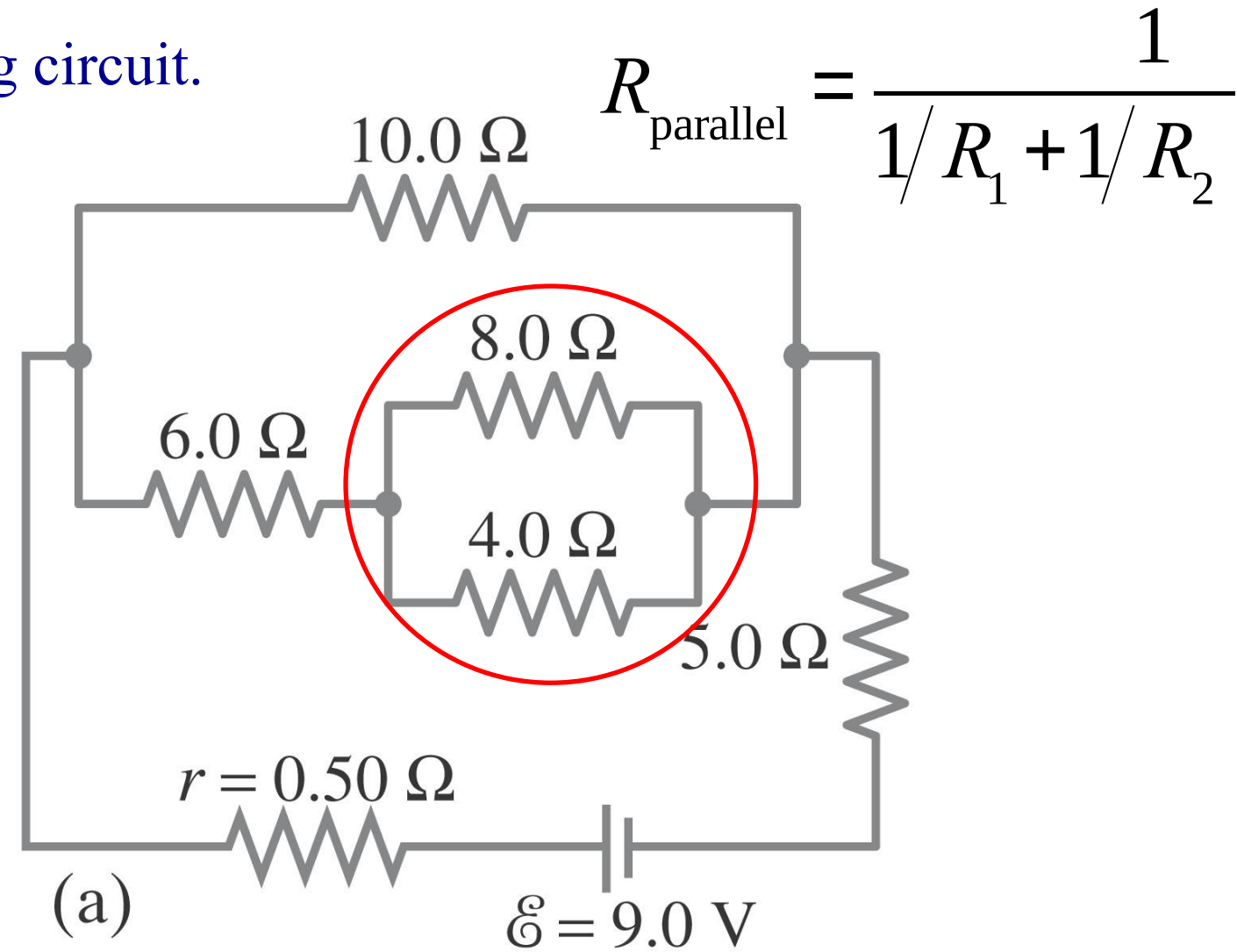


Resistors in Series and in Parallel

Example: Big circuit.

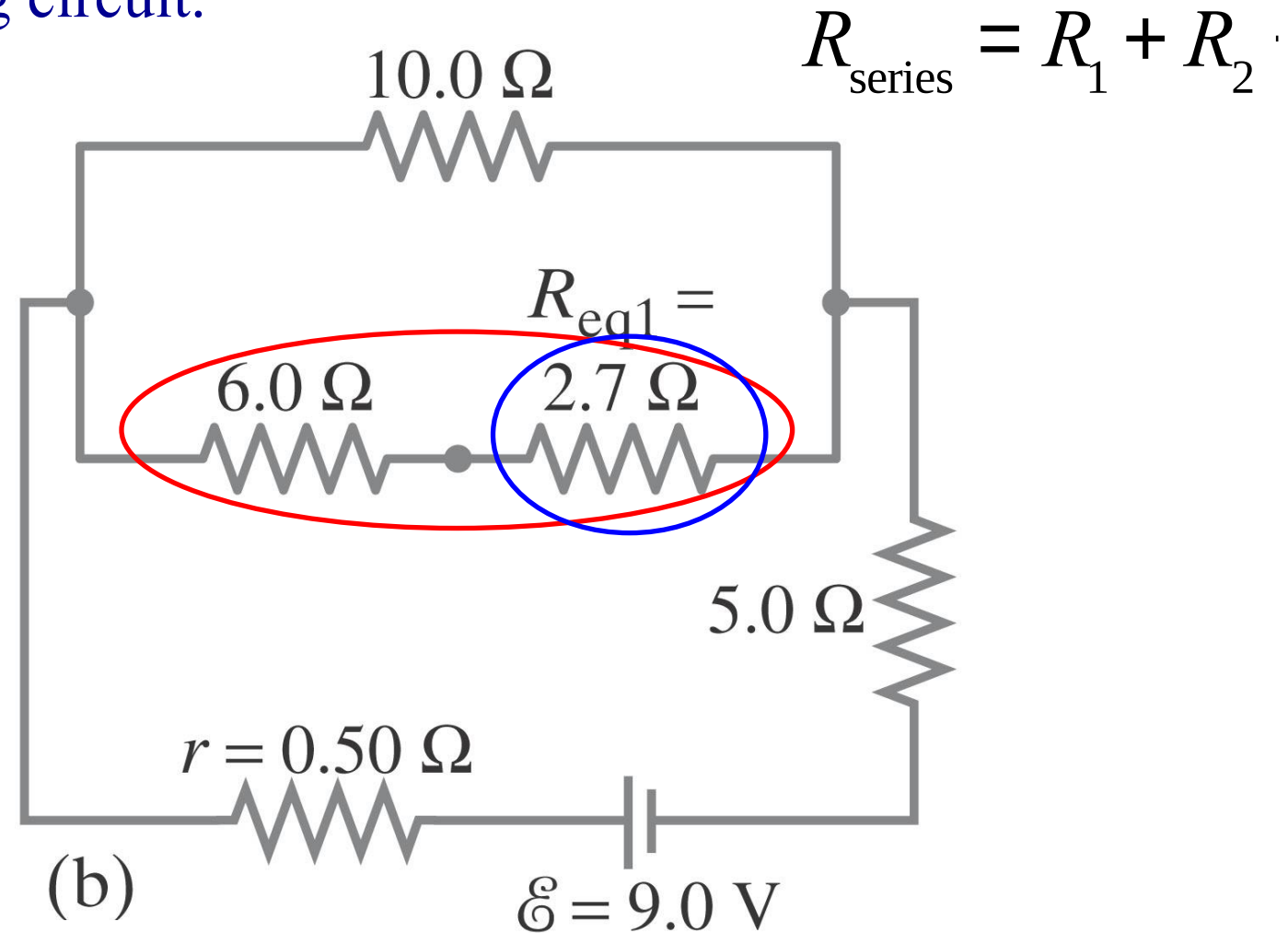


Resistors in Series and in Parallel

Example: Big circuit.

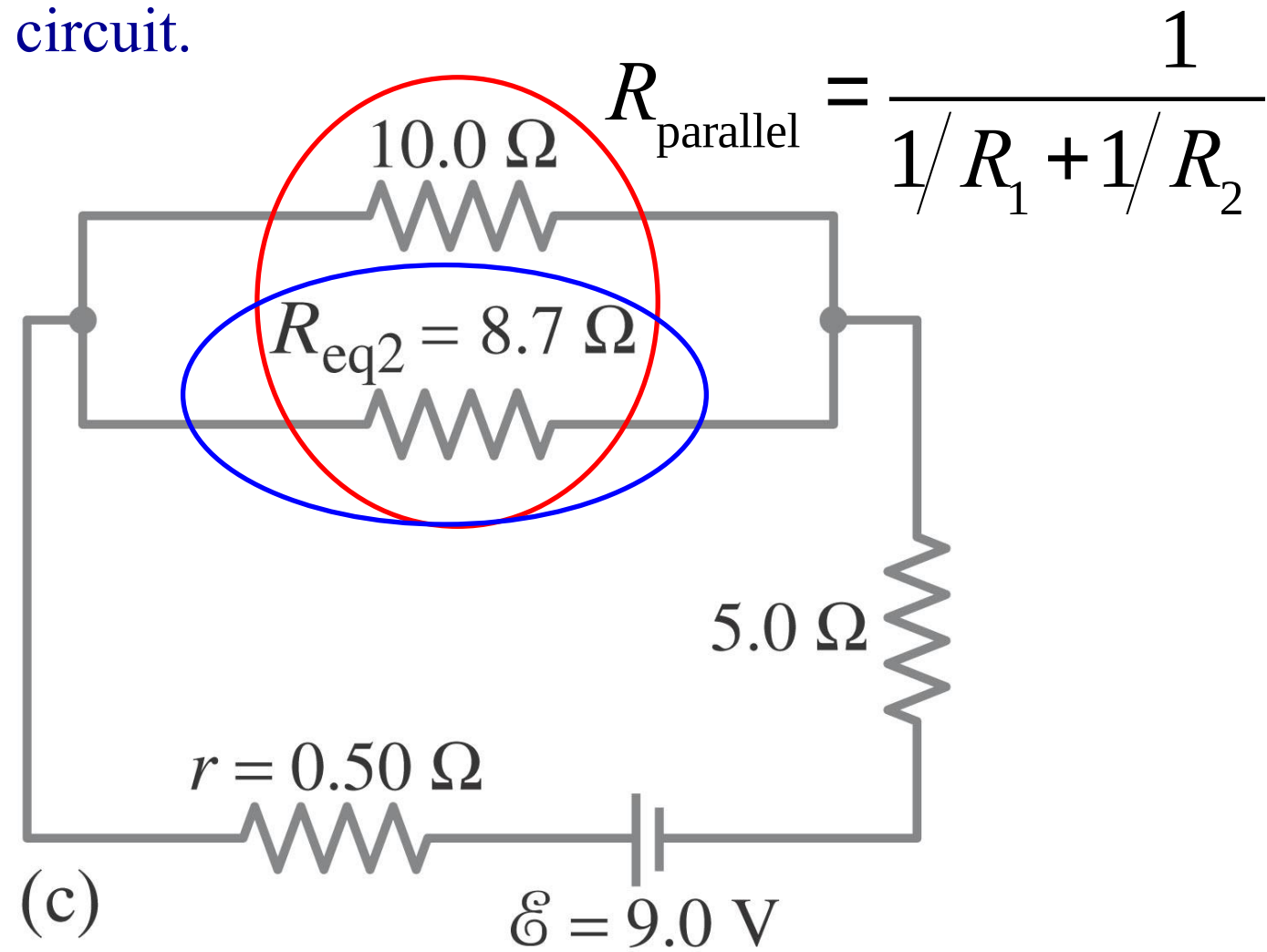

Resistors in Series and in Parallel


$$R_{\text{series}} = R_1 + R_2 + R_3$$

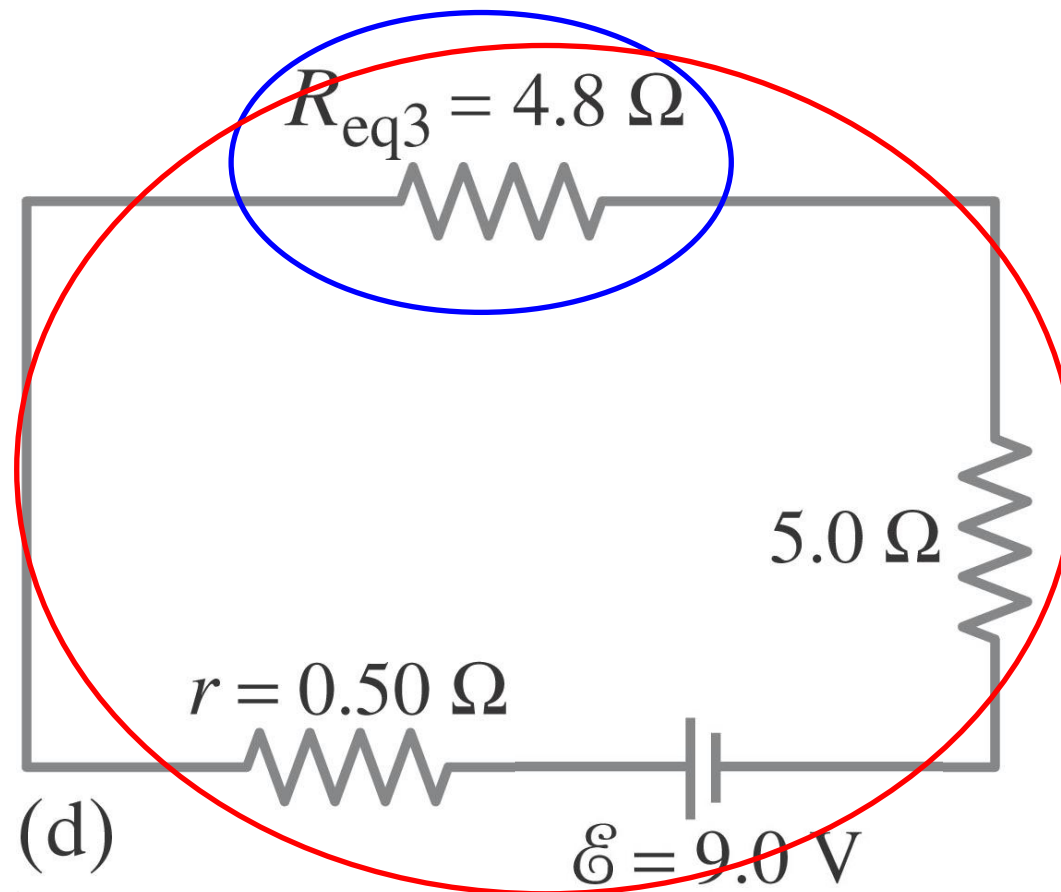

Resistors in Series and in Parallel


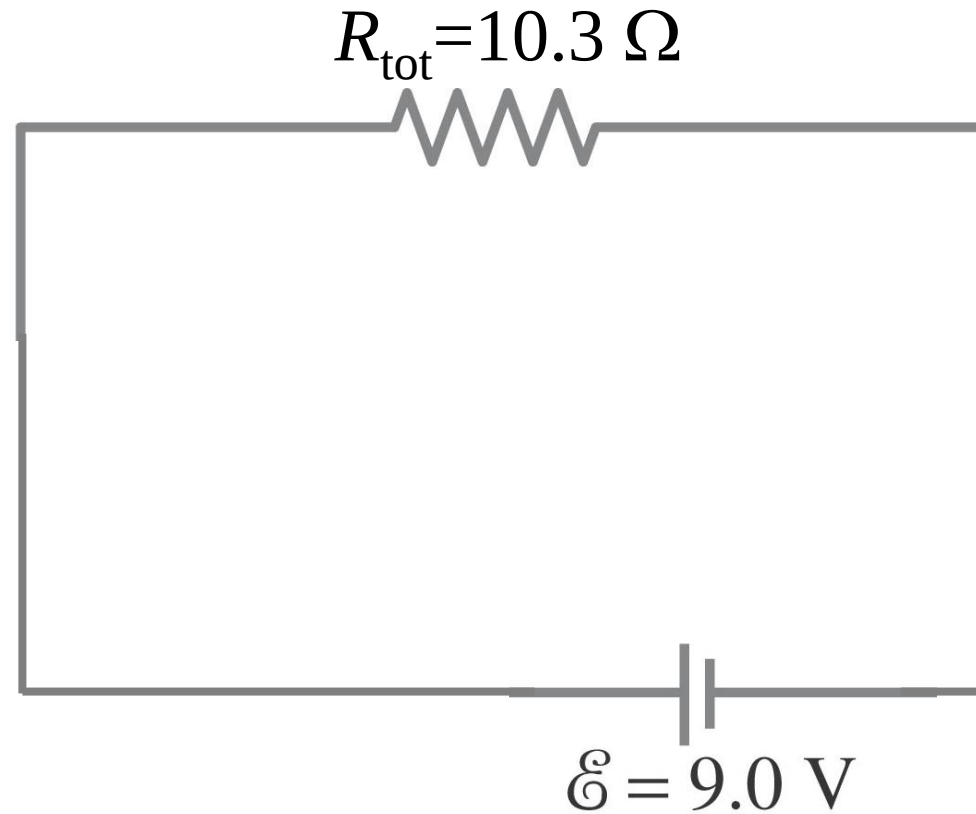
Example: Big circuit.

$$I = \frac{\mathcal{E}}{R_{tot}} = 0.873 \text{ A}$$



Lamp Brightness 1

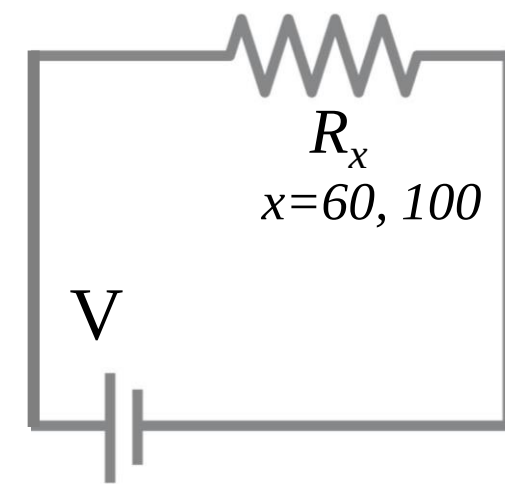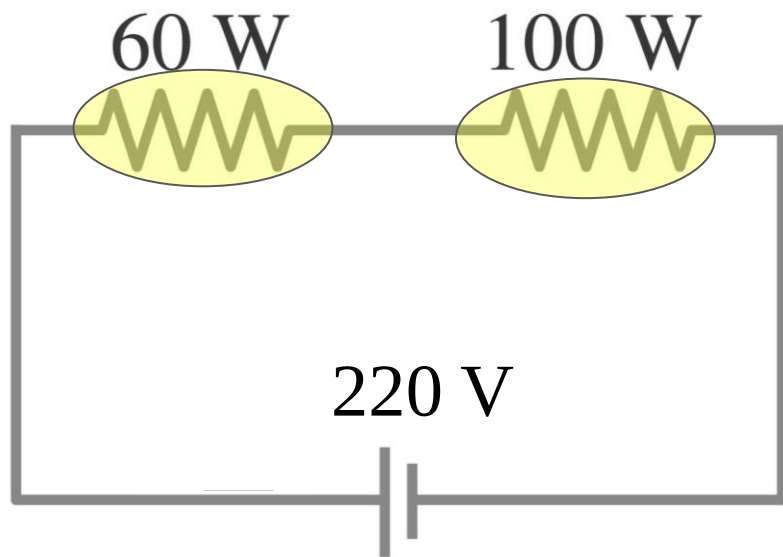Two different 220-V light bulbs are connected to 220 V power supply as shown. Which bulb is brighter? Ignore change of filament resistance with current (and temperature).




$$P_{1x} = \frac{V^2}{R_x} \Rightarrow R_x = \frac{V^2}{P_{1x}} \Rightarrow R_{100\text{ W}} < R_{60\text{ W}}$$

$$P_{2x} = I^2 R_x \Rightarrow I = \text{const} \Rightarrow P_{100\text{ W}} < P_{60\text{ W}}$$

- Brightness is proportional to resistance

Lamp Brightness 2

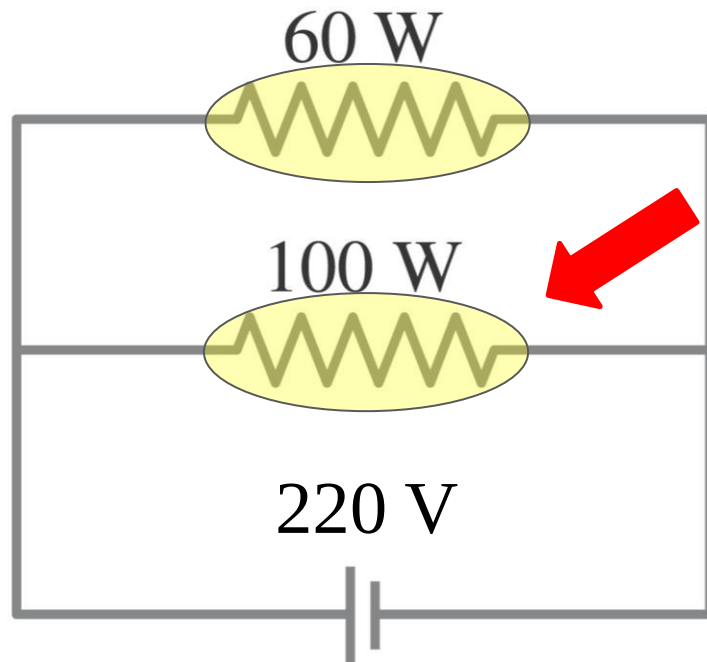What is the brightest light bulb in the circuit?



The same voltage is applied to both, therefore the power of each bulb is nominal

$$P = \frac{V^2}{R}$$

$$R_{100} < R_{60}$$

Example

Three resistors are connected in parallel as shown in Figure 28.11a. A potential difference of 18.0 V is maintained between points a and b.

(A) Calculate the equivalent resistance of the circuit.

Because the three resistors are connected in parallel, we can use the rule for resistors in parallel, to evaluate the equivalent resistance.

$$\frac{1}{R_{\text{eq}}} = \frac{1}{3.00 \, \Omega} + \frac{1}{6.00 \, \Omega} + \frac{1}{9.00 \, \Omega} = \frac{11}{18.0 \, \Omega}$$

$$R_{\text{eq}} = \frac{18.0 \, \Omega}{11} = 1.64 \, \Omega$$


(B) Find the current in each resistor

The potential difference across each resistor is 18.0 V. Apply the relationship $\Delta V = IR$ to find the currents:

$$I_1 = \frac{\Delta V}{R_1} = \frac{18.0 \, \text{V}}{3.00 \, \Omega} = 6.00 \, \text{A}$$

$$I_2 = \frac{\Delta V}{R_2} = \frac{18.0 \, \text{V}}{6.00 \, \Omega} = 3.00 \, \text{A}$$
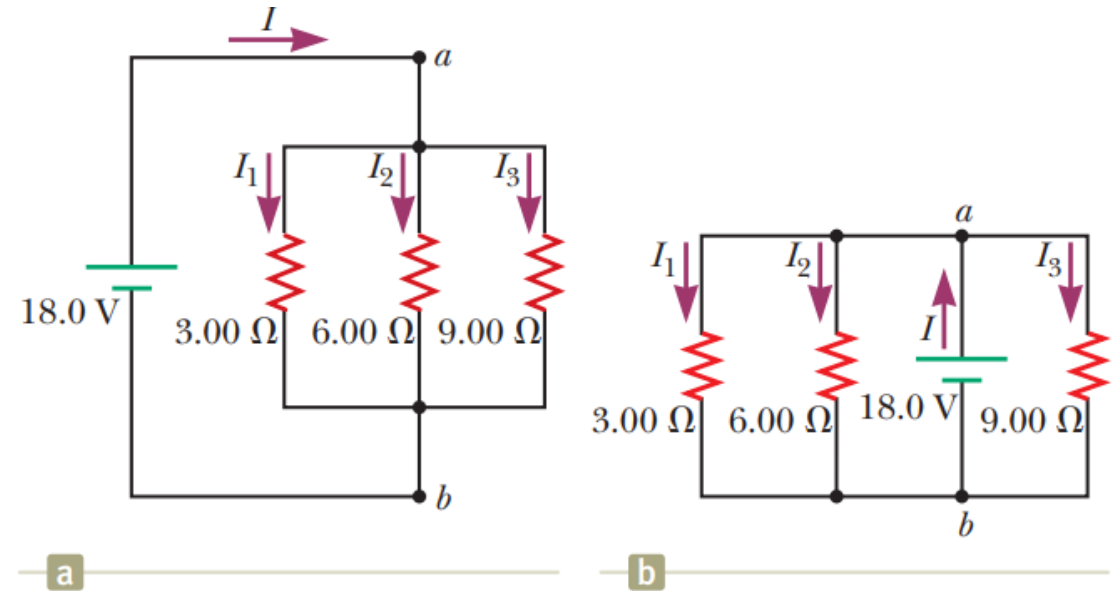
$$I_3 = \frac{\Delta V}{R_3} = \frac{18.0 \, \text{V}}{9.00 \, \Omega} = 2.00 \, \text{A}$$



(C) Calculate the power delivered to each resistor and the total power delivered to the combination of resistors

$$3.00\text{-}\Omega: P_1 = I_1^2 R_1 = (6.00 \, \text{A})^2 (3.00 \, \Omega) = 108 \, \text{W}$$

$$6.00\text{-}\Omega: P_2 = I_2^2 R_2 = (3.00 \, \text{A})^2 (6.00 \, \Omega) = 54 \, \text{W}$$

$$9.00\text{-}\Omega: P_3 = I_3^2 R_3 = (2.00 \, \text{A})^2 (9.00 \, \Omega) = 36 \, \text{W}$$

Summing the three quantities gives a total power of 198 W


$$P = (\Delta V)^2 / R_{\text{eq}} = (18.0 \, \text{V})^2 / 1.64 \, \Omega = 198 \, \text{W}.$$

Kirchhoff's Rules

Some circuits cannot be broken down into series and parallel connections (i.e. not reducible).


There is no way to reduce the three resistors to one effective resistance or to combine the two voltage sources to one voltage source.

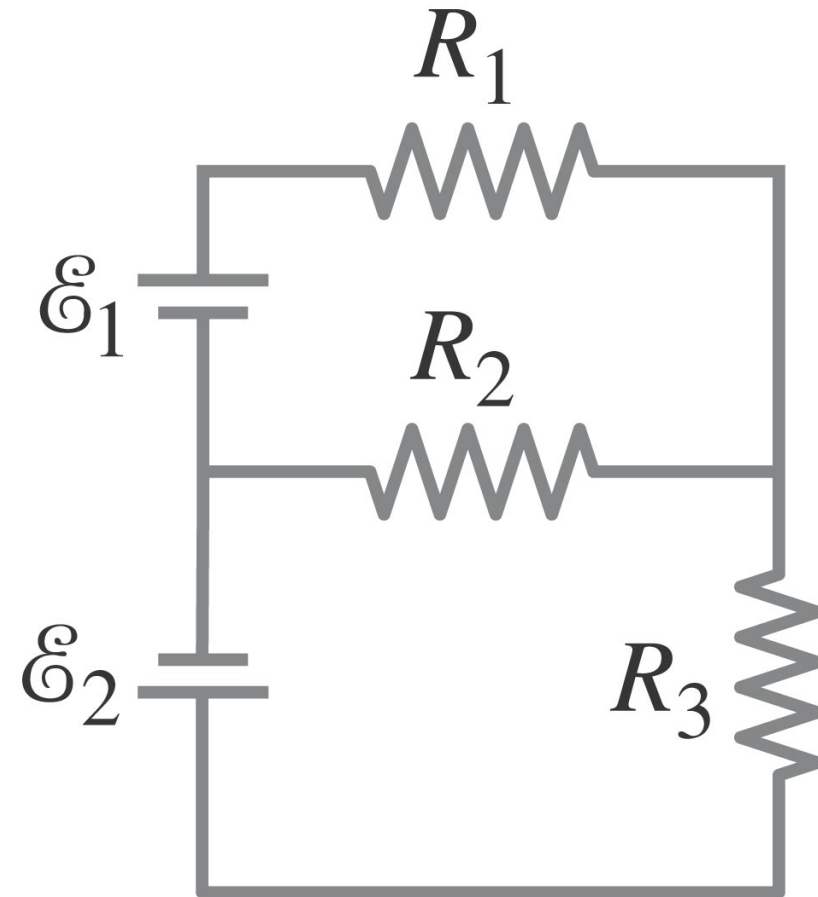For such circuits we use **Kirchhoff's rules**.




Kirchhoff's Rules

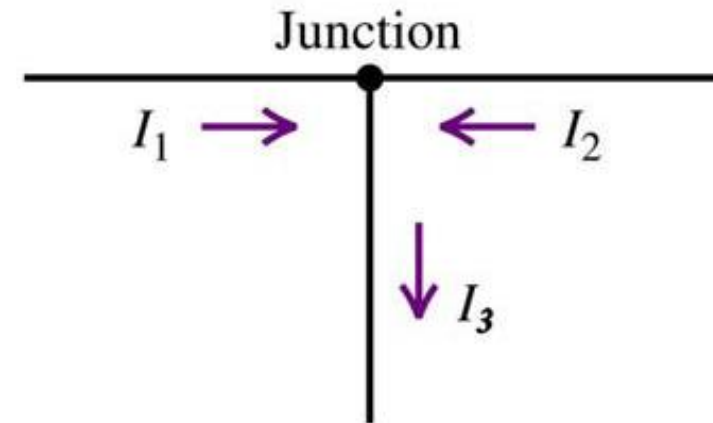A **junction**, also called a **node** or **branch point**, is a point where three or more conductors meet.



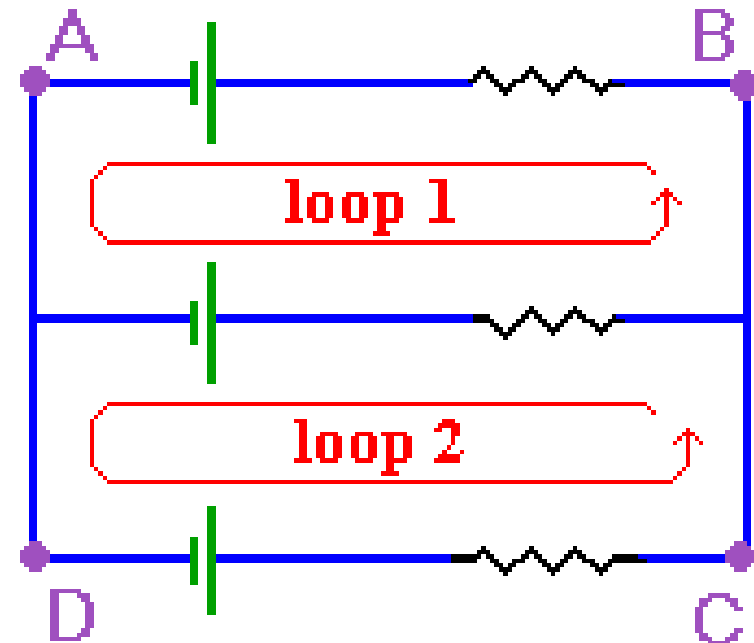
A **loop** is any closed conducting path.



Kirchhoff's Rules

Junction rule: The sum of the currents entering a junction is equal to the sum of leaving currents.

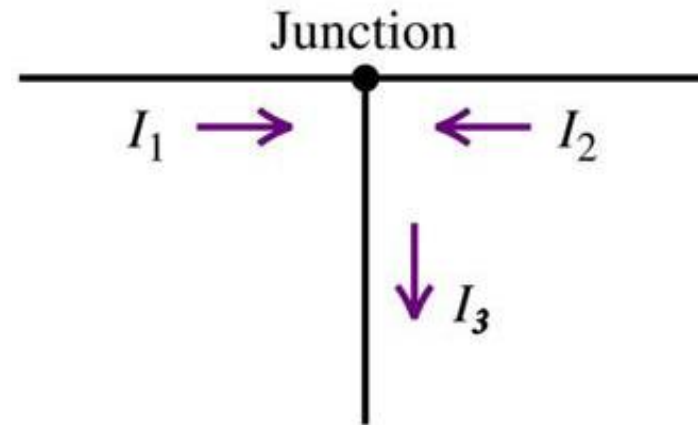Kirchhoff's first rule is a statement of conservation of electric charge. All charges that enter a given point in a circuit must leave that point because charge cannot build up or disappear at a point.



$$I_1 + I_2 = I_3$$

$$\sum I_{in} = \sum I_{out}$$



Kirchhoff's Rules

Loop rule: The algebraic sum of the emfs (batteries) in a loop *is equal* to the sum of potentials drops on all other (inactive) elements in the loop.

Kirchhoff's second rule follows from the law of conservation of energy for an isolated system. Let's imagine moving a charge around a closed loop of a circuit. When the charge returns to the starting point, the charge–circuit system must have the same total energy as it had before the charge was moved.





$$\sum_{\text{batteries}} \mathcal{E}_k = \sum_{R,C,L} V_{ij}$$
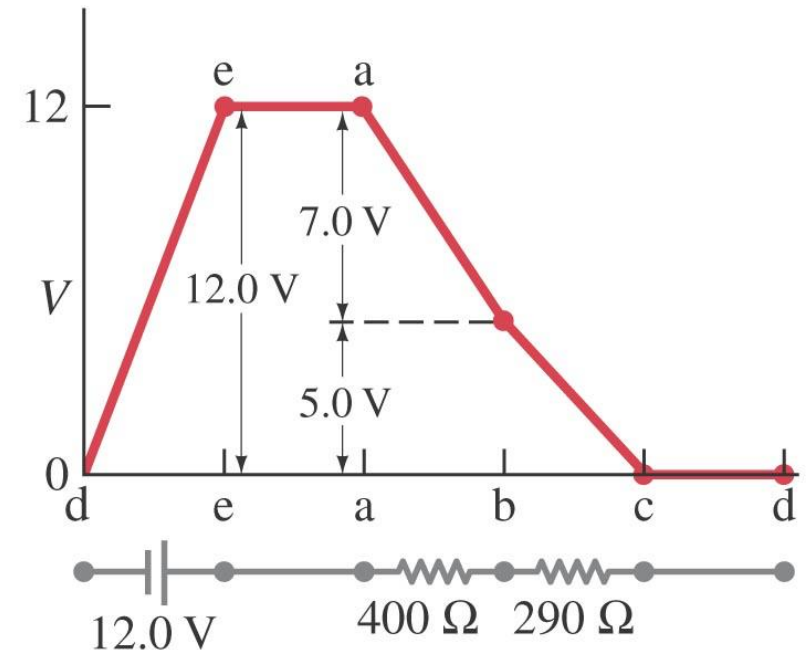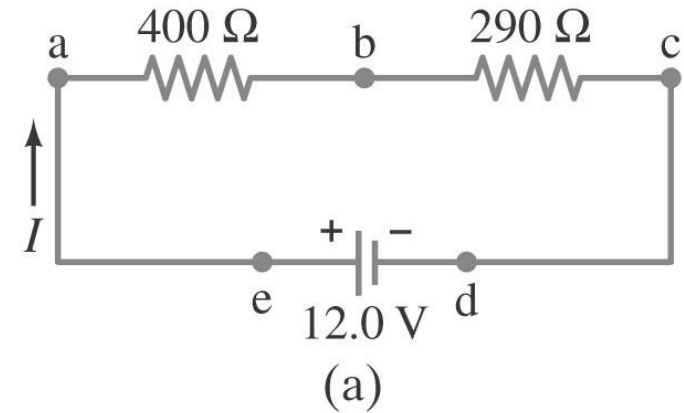
$$V_{ac} = V_{ab} + V_{bc} = V_{ae} + V_{ed} + V_{dc}$$




Kirchhoff's Rules

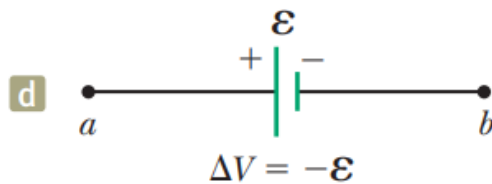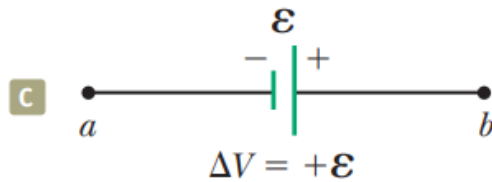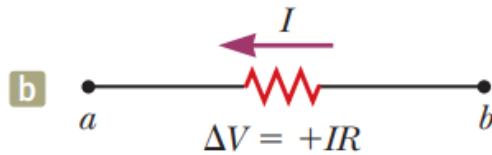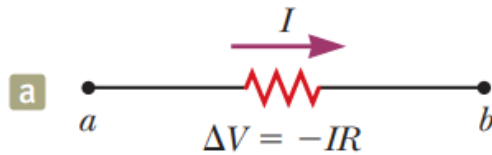
In each diagram, $\Delta V = V_b - V_a$
and the circuit element is
traversed from a to b , left to right.



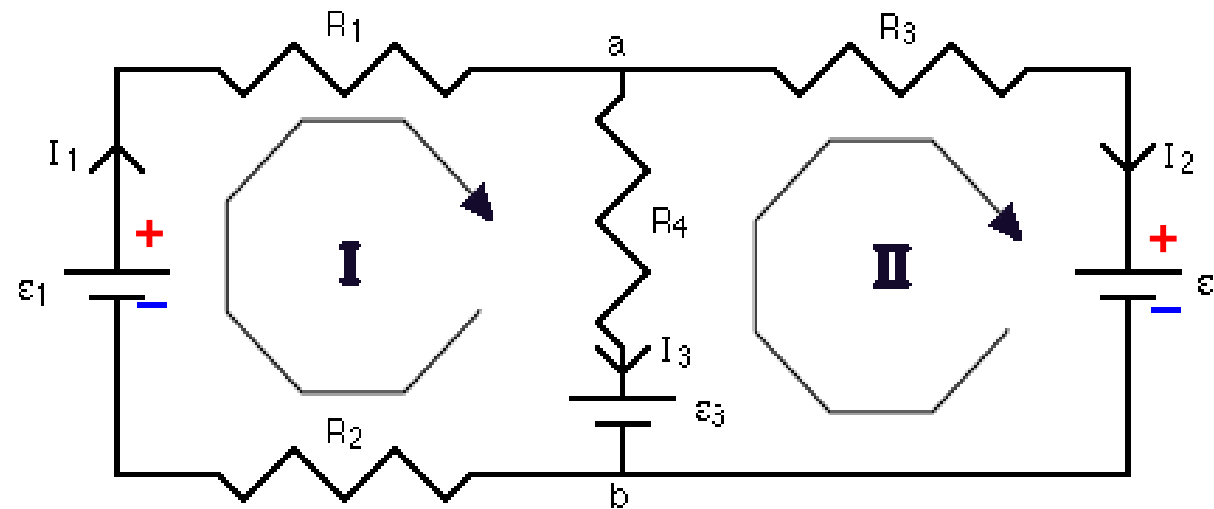- Choose the loops and the directions of currents.
- A $\Delta V = \text{emf}$ term is considered to be **positive** if we go in the direction $-$ to $+$, otherwise it is **negative**.
- A $\Delta V = IR$ term is **positive** if we cross R in the same sense as the current that is going through it, otherwise it is **negative**.



Kirchhoff's Rules

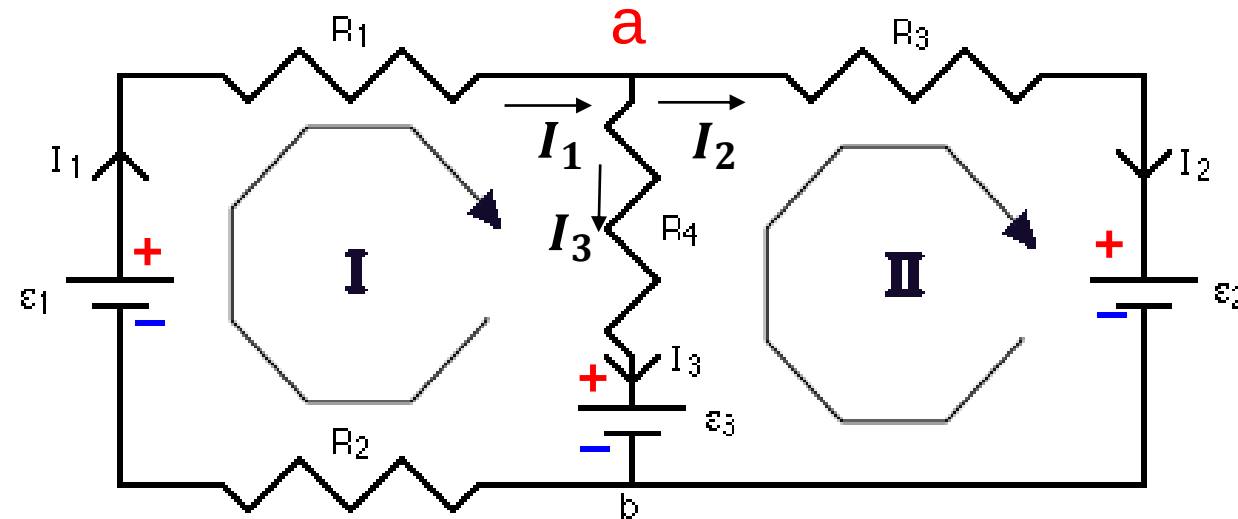

For loop **I** we have $\mathcal{E}_1 - \mathcal{E}_3 = I_1 R_1 + I_3 R_4 + I_1 R_2$



For loop **II** we have $\mathcal{E}_3 - \mathcal{E}_2 = I_2 R_3 - I_3 R_4$

Junction equation at **a** gives us $I_1 = I_2 + I_3$

We now have three equations for the three unknown currents.

Loi de Kirchhoff

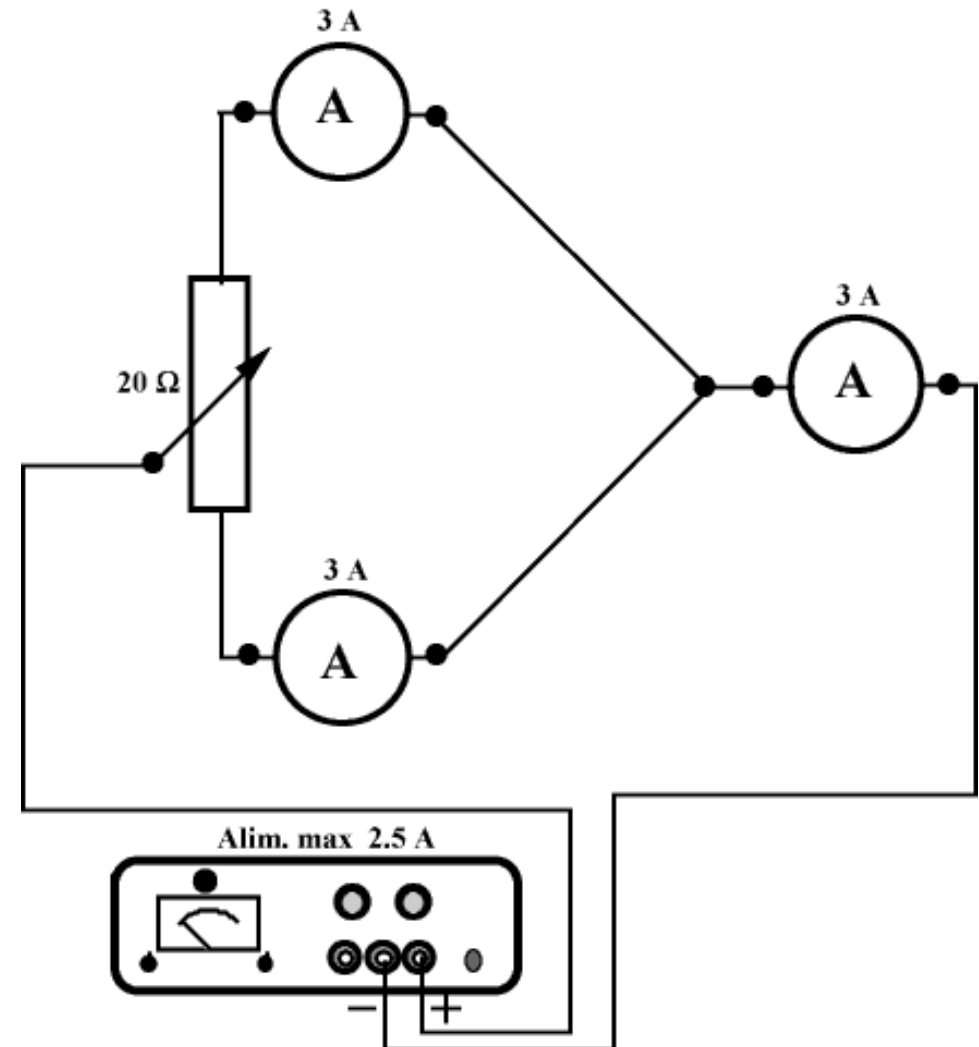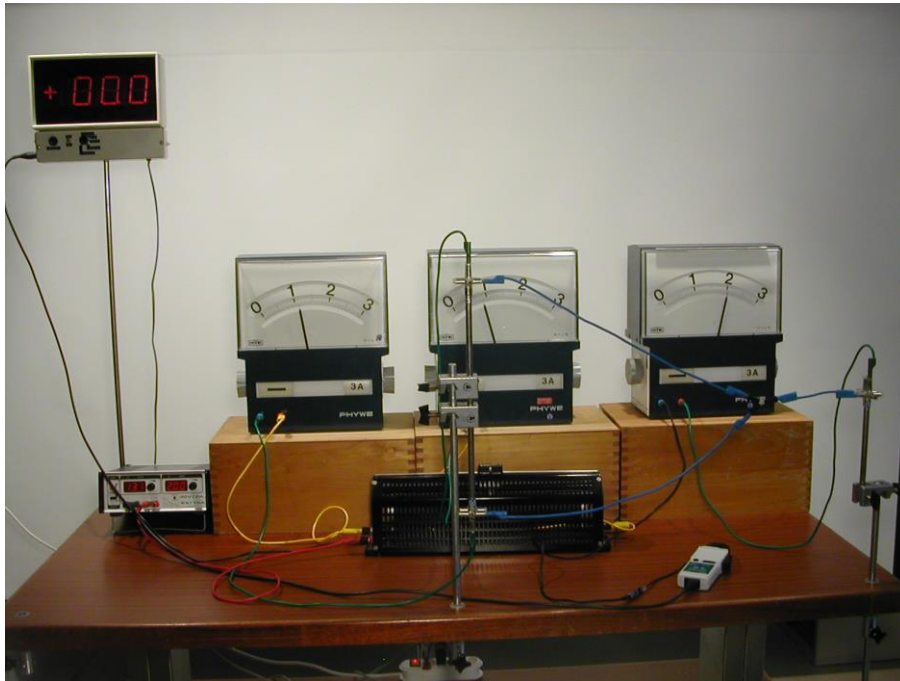In this experiment, a generator, three ammeters and a resistor are placed according to the electrical diagram below




<https://auditoires-physique.epfl.ch/experiment/460/loi-de-kirchhoff>

Circuits Containing Resistor and Capacitor (RC Circuits)

When the switch is closed, the capacitor will begin to charge. As it does, the voltage across it increases, and the current through the resistor decreases.

- Empty capacitor behaves like $R=0$
- Charged capacitor is like $R= \infty$
- The $\Delta V(t)$ at the extremities of a capacitor is $Q(t)/C$

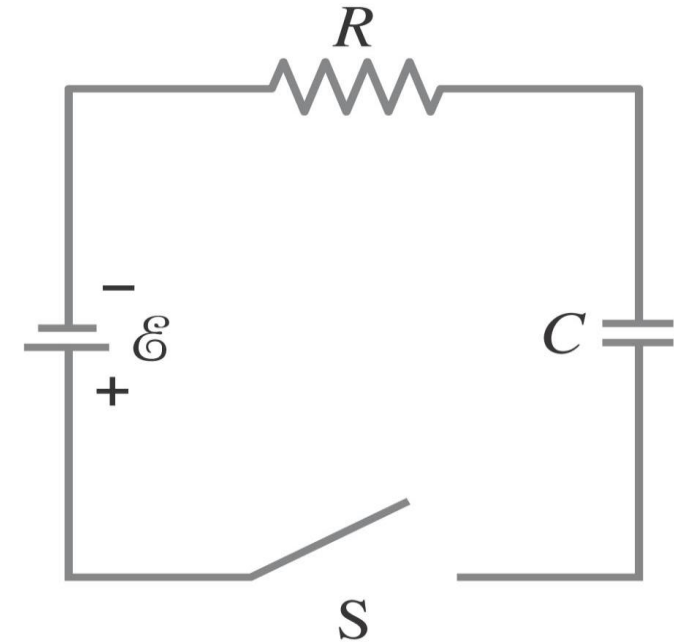How the charge, potential and current depend on time ?



Circuits Containing Resistor and Capacitor (RC Circuits)

Kirchhoff' equation for the voltage around the loop:


$$\mathcal{E} = IR + \frac{Q}{C} \quad \bullet \quad \text{This equation is valid at any time } t$$

$$\mathcal{E} = I(t)R + \frac{Q(t)}{C} \quad \text{Recall: } I = \partial Q / \partial t \quad \longrightarrow$$

Time-dependent equation:

$$\mathcal{E} = \frac{\partial Q(t)}{\partial t} R + \frac{Q(t)}{C}$$


Let's solve it !

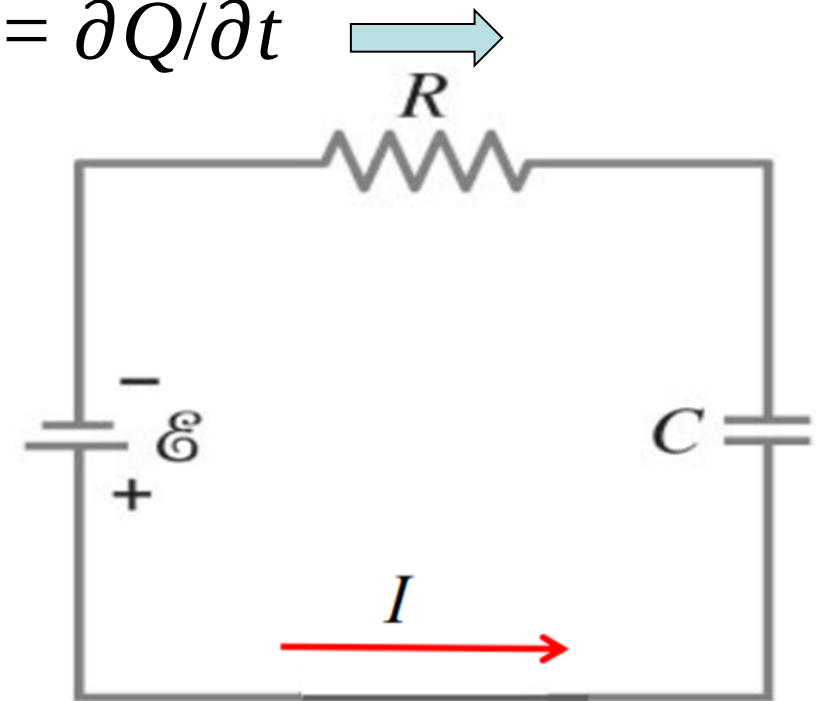

$$\varepsilon = \frac{\partial Q(t)}{\partial t} R + \frac{Q(t)}{C}$$

Initial conditions:

at $t = 0$ no charge ($Q = 0$) on C

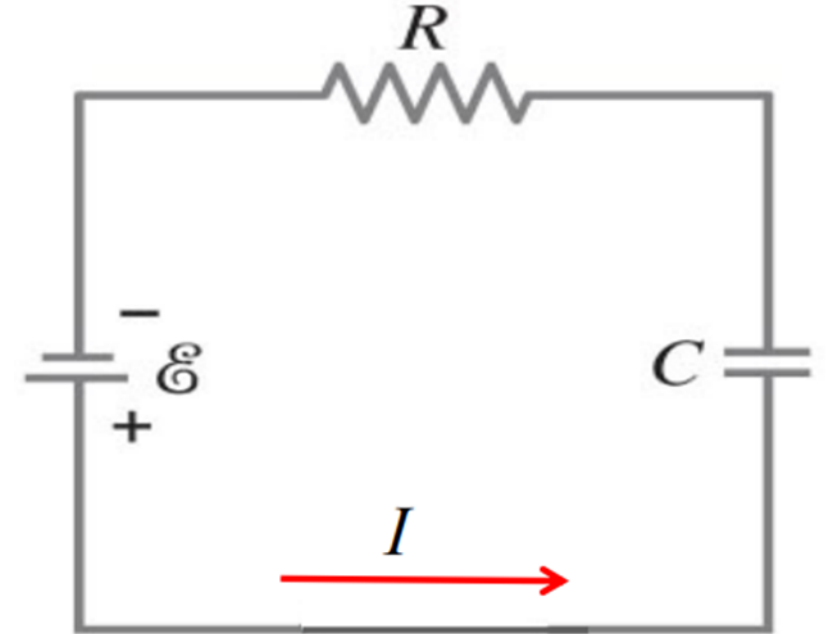

We can easily find the initial current I_i in the circuit
and the maximum charge Q_{max} on the capacitor (for $t = \infty$)

$$I_i = \frac{\varepsilon}{R} \text{ (current at } t=0\text{)}$$
$$Q(t=0) = 0$$

$$Q_{max} = C\varepsilon \text{ (maximum charge)}$$
$$I(t = \infty) = 0$$

RC Circuits

$$\varepsilon = \frac{\partial Q}{\partial t} R + \frac{Q}{C}$$

multiply by C and rearrange:

differentiate:

$$\frac{\partial Q}{\partial t} RC = \varepsilon C - Q$$

$$y = \varepsilon C - Q \Rightarrow \partial y = \partial(\varepsilon C - Q) = -\partial Q$$

Integrate (separation of variable)

$$-\frac{\partial y}{\partial t} = y \frac{Q}{RC} \Rightarrow \frac{\partial y}{y} = -\frac{\partial t}{RC} \Rightarrow \ln(y) = -\frac{t}{RC} + \text{const}$$

Put to exp to both sides: $y = A \exp\left(-\frac{t}{RC}\right)$

Replace y back: $\varepsilon C - Q = A \exp\left(-\frac{t}{RC}\right)$

Initial conditions: $\text{for } t = 0$
 $Q = 0 \iff A = \varepsilon C$

$$Q = \varepsilon C \left[1 - \exp\left(-\frac{t}{RC}\right)\right]$$

RC Circuits: CHARGE

$$Q = \mathcal{E}C \cdot (1 - \exp(-\frac{t}{RC}))$$

$$Q_f = \lim_{t \rightarrow \infty} Q = \lim_{t \rightarrow \infty} C\mathcal{E} \left(1 - e^{-t/RC}\right) = C\mathcal{E}$$

$$Q = Q_f \cdot (1 - \exp(-\frac{t}{RC}))$$


The quantity RC that appears in the exponent is called the **time constant** of the circuit:

$$t = RC.$$

- After this time $Q = (1 - 1/e) = 63\%$ of its final value

$$[\tau] = [RC] = \left[\left(\frac{\Delta V}{I} \right) \left(\frac{Q}{\Delta V} \right) \right] = \left[\frac{Q}{Q/\Delta t} \right] = [\Delta t] = T$$

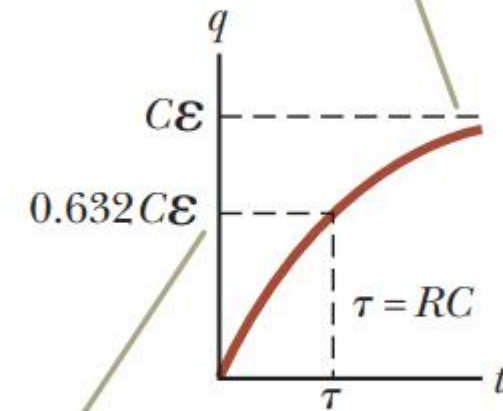The charge approaches its maximum value $C\mathcal{E}$ as t approaches infinity.



After a time interval equal to one time constant τ has passed, the charge is 63.2% of the maximum value $C\mathcal{E}$.



RC Circuits: VOLTAGE

$$Q = \mathcal{E}C \cdot (1 - \exp(-\frac{t}{RC}))$$

The voltage across the capacitor is $V_C = Q/C$:

$$V_C = \mathcal{E} \left(1 - e^{-t/RC} \right)$$

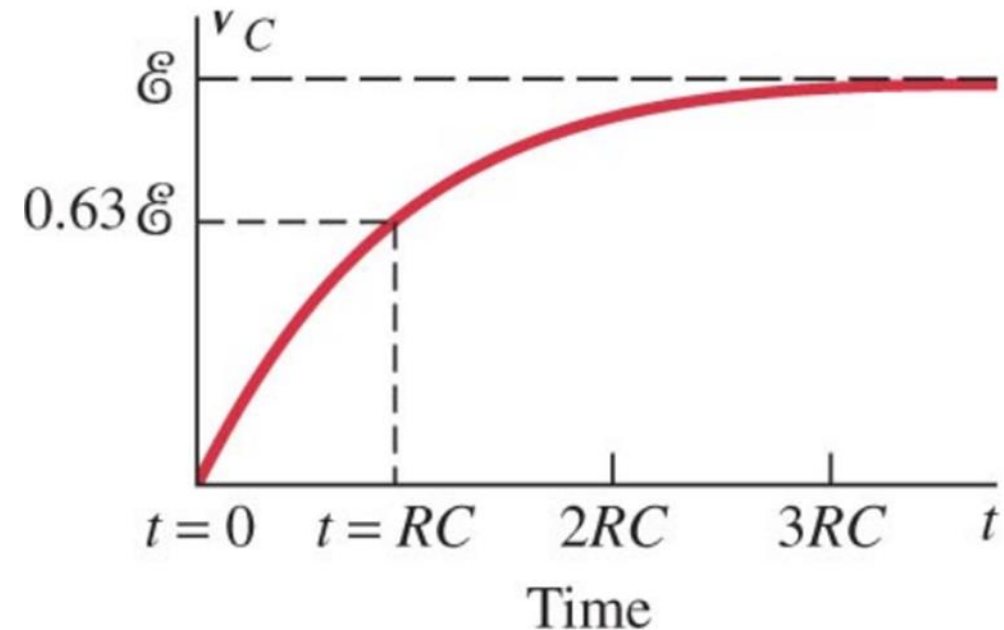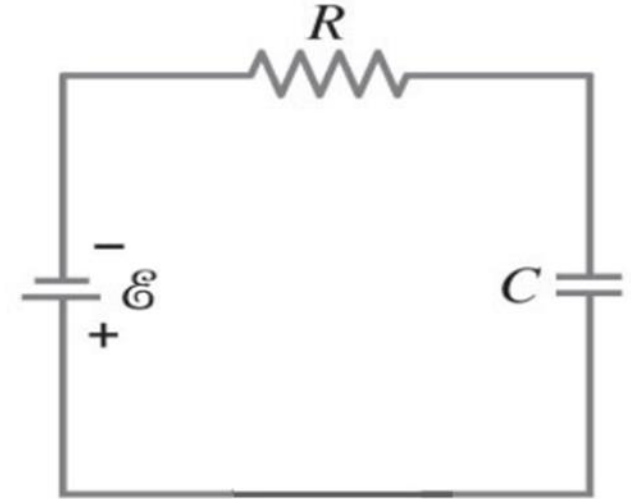- Voltage on capacitor follows the charge



RC Circuits: CURRENT

$$Q = \epsilon C \cdot (1 - \exp(-\frac{t}{RC}))$$


Differentiate the charge:

$$I = \frac{dQ}{dt} = \frac{1}{RC} \frac{dQ}{d(-t/RC)}$$

$$y = -\frac{t}{RC}$$

$$I = \frac{dQ}{dt} = \frac{d[\epsilon C (1 - \exp(y))]}{dy} * \frac{dy}{dt}$$
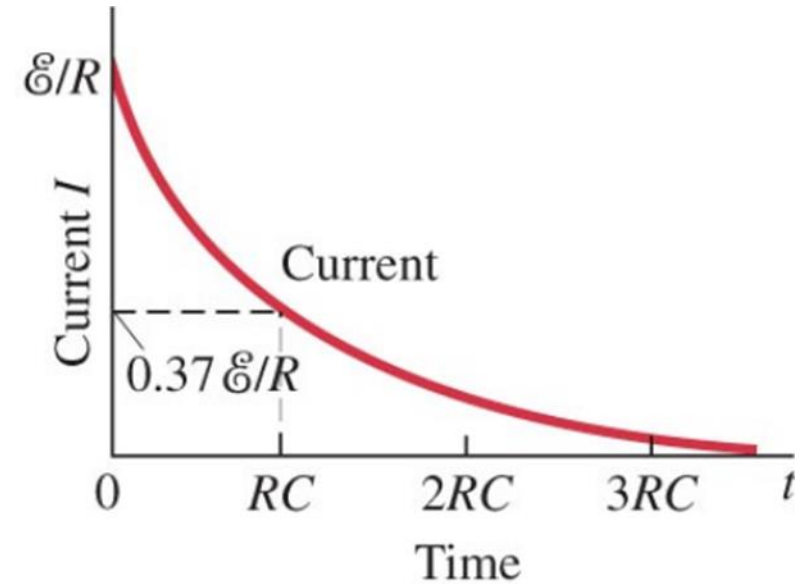
$$I = \frac{dQ}{dt} = -\epsilon C \exp(y) * (-\frac{1}{RC})$$



Current decays with
time constant RC


$$I = \frac{\epsilon}{R} e^{-t/RC}$$

RC Circuits: discharging

Circuit: charged capacitor in series with a resistor and an open switch (starting condition).

The capacitor will now act as a source of emf (but not constant in time, as for a battery).

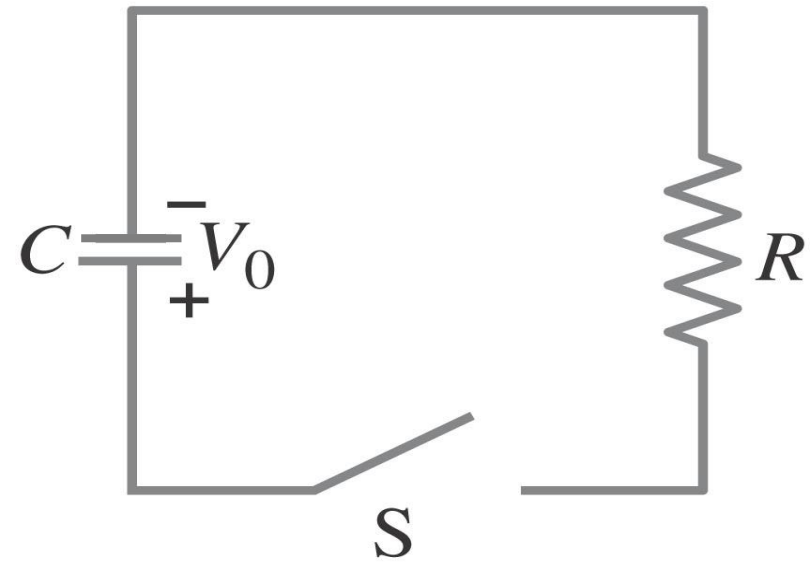The capacitor will discharge and its voltage and emf will decrease in time.



Let's solve it !

RC Circuits: discharging

Kirchhoff's 2nd rule gives us

$$\frac{Q}{C} = IR.$$



As the capacitor discharges

$$I = - \frac{dQ}{dt}.$$

Therefore,

$$\frac{Q}{C} = - \frac{dQ}{dt} R \rightarrow Q = Q_0 e^{-t/RC}.$$

- 1/e of Q_0 will be left at $t = RC$

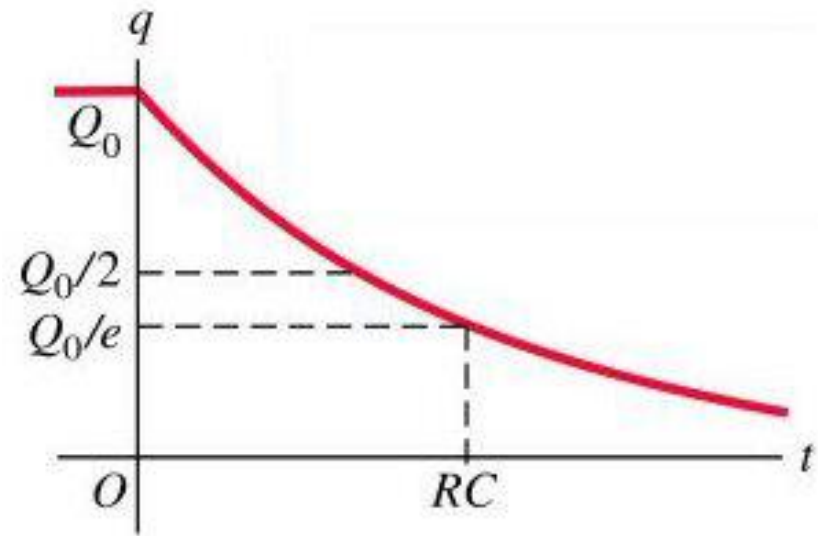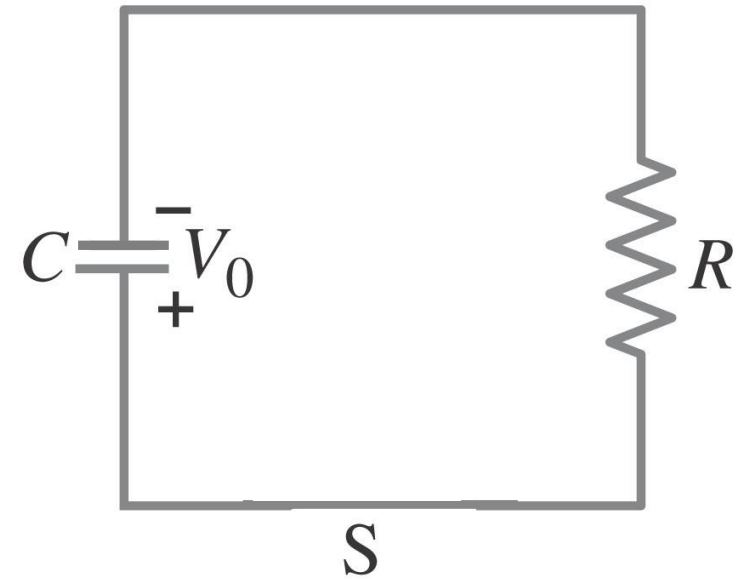

RC Circuits: discharging

$$Q = Q_0 e^{-t/RC}.$$

Once again, the voltage and current as a function of time can be found from the charge:

$$V_C = \frac{Q}{C} = \frac{Q_0}{C} e^{-t/RC} = V_0 e^{-t/RC}$$


and

$$I = -\frac{dQ}{dt} \rightarrow I = \frac{Q_0}{RC} e^{-t/RC} = I_0 e^{-t/RC}.$$


- Q , V_C and I_C decay with time constant $\tau = RC$
- For a small R the discharge can be short but with high current !

Electrostatics and Microtechnology

Touchscreen

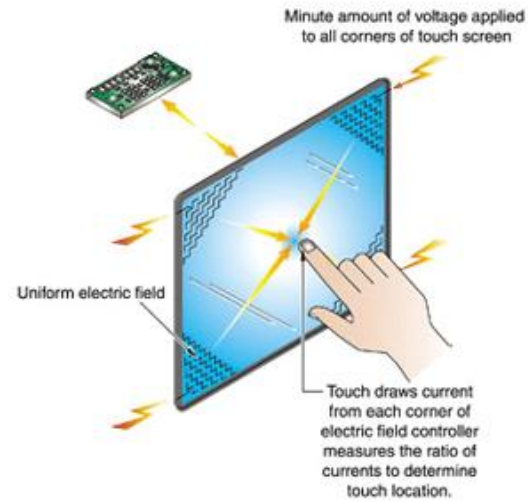

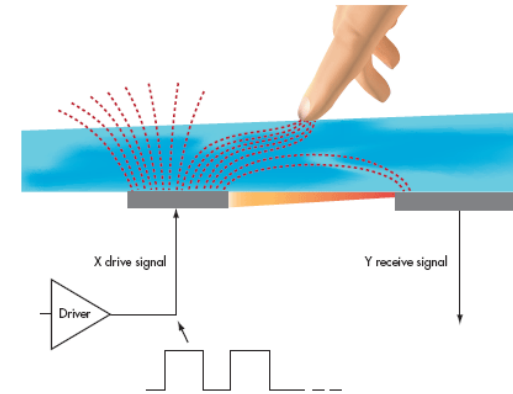3. One projected touchscreen technology involves sensing along both the X- and Y-axis using clearly etched ITO patterns.



Piezoelectric “motors” for micro/nanometric positioning (with capacitive position sensors)


1-axis





2-axis




3-axis

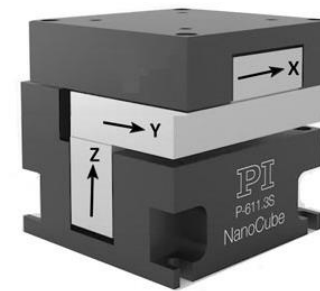




Fingerprint sensor

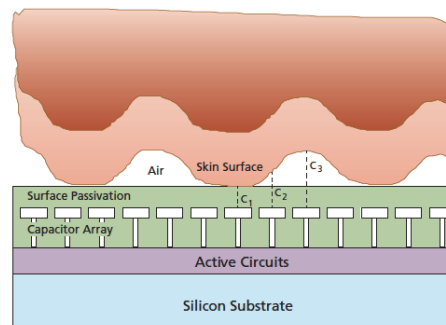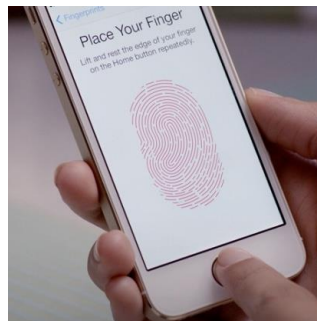

Accelerometer and Gyrometer

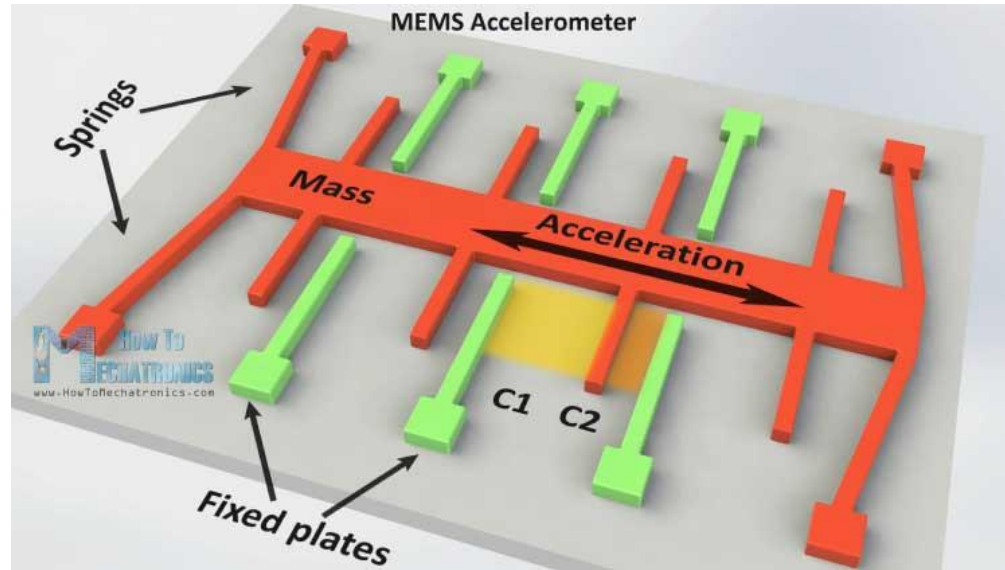

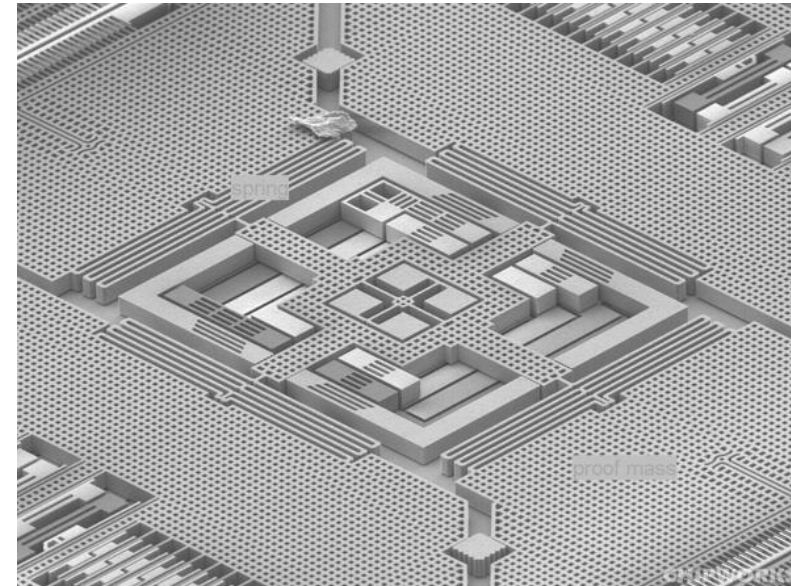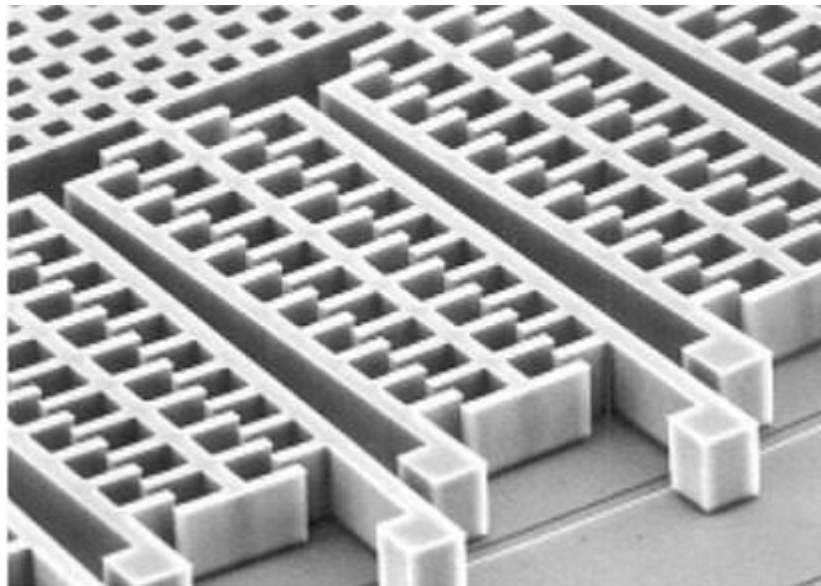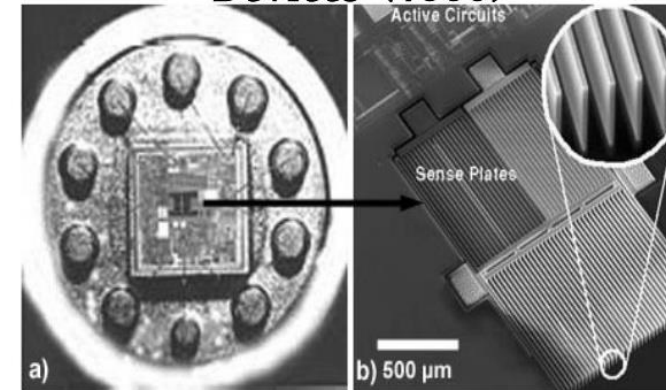The first commercial accelerometer from Analog Devices (1990)



Summary of electrostatics

