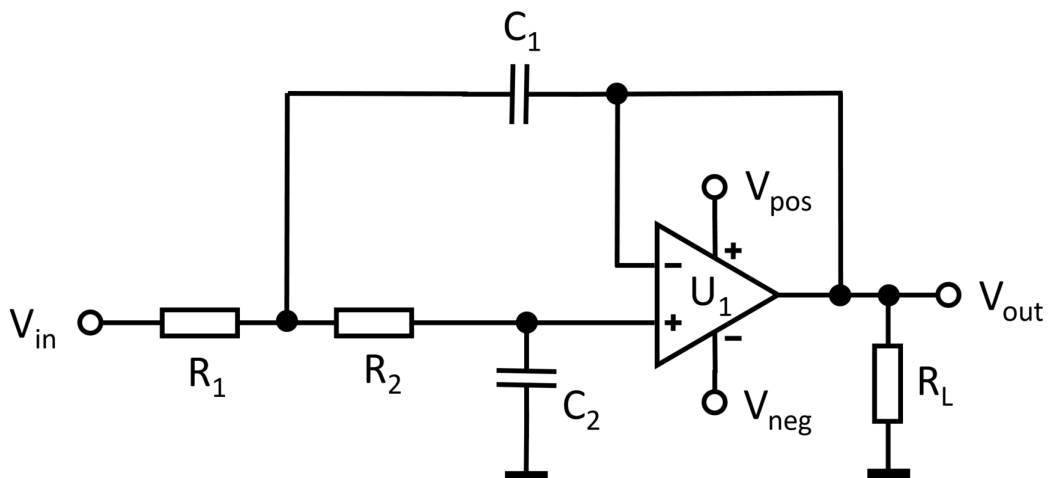


Exercise set

Exercise 1:

We want to analyze the following circuit using *LTspice*:



- a) Draw the circuit and use the following values for the components:

R_1	$15\text{ k}\Omega$
R_2	$15\text{ k}\Omega$
R_L	$50\text{ }\Omega$
C_1	225 pF
C_2	115 pF
$U1$	<i>UniversalOpamp2</i>
V_{pos}	5 V
V_{neg}	-5 V

b) Simulate the circuit and plot V_{out} as a function of time, when V_{in} is a sinusoidal signal with an amplitude of 1 V , a DC offset of 0 V and frequency $f = 10\text{ kHz}$.

c) Repeat the simulation for $f = 5\text{ kHz}$, $f = 50\text{ kHz}$, $f = 100\text{ kHz}$ and $f = 500\text{ kHz}$. What does the circuit do?

d) Find f_C for which the amplitude of V_{out} is 3 dB lower than V_{in} .

e) Repeat d) for $C_2 = 65\text{ pF}$, $C_2 = 200\text{ pF}$ and $C_2 = 250\text{ pF}$.

f) Find a value for C_2 such that $f_C = 30\text{ kHz}$.

g) Simulate the circuit and plot V_{out} as a function of time, when V_{in} is a rectangular signal with an amplitude of 1 V , a DC offset of 0 V and frequency $f = 20\text{ kHz}$. What do you observe?

h) Plot the spectrum of V_{out} .