

CS-472: Design Technologies for Integrated Systems

Exercise Problem Set 8

Date: 04/12/2025

Topics: Boolean methods (cf. slide set 12), timing analysis & retiming (cf. slide sets 13 & 14)

Problem 1

Consider the logic network where inputs are $\{a, b, c, d\}$ and output is $\{f\}$ defined as:

$$k = ad$$

$$n = c + k$$

$$m = \overline{ab}$$

$$f = m + n$$

Assuming $CDC_{in} = ab$, compute CDC_{out} .

Problem 2

Consider the logic network from Problem 1. Compute the ODC sets for all internal and input vertices assuming that the output is fully observable.

Problem 3

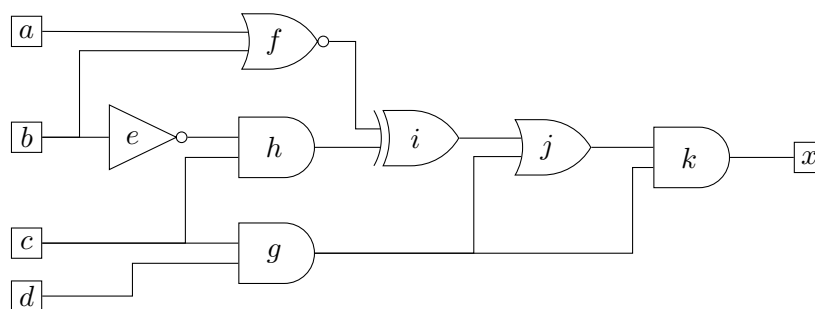


Figure 1: Combinational logic network.

Consider the network in Fig. 1: The inputs are $\{a, b, c, d\}$ and the output is x . The data ready time for all the inputs is 0, and the inputs are stable after time 0. Assume the following delays for logic gates:

INV gate: $t_d = 1$ ns;

AND gate: $t_d = 1$ ns;

OR/NOR/XOR gate: $t_d = 2$ ns.

- (a) The data required time for the output x is 7 ns. Find all the topological critical paths.
- (b) Is the path (b, e, h, i, j, k, x) a true critical path?

Problem 4

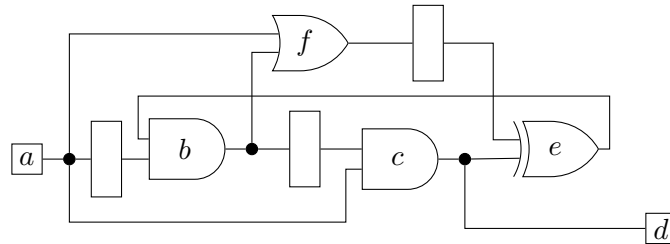


Figure 2: Sequential logic network.

Consider the network in Fig. 2, where the rectangles are registers. Assume the following delays for logic gates:

AND gate: $t_d = 3$ ns;

OR gate: $t_d = 4$ ns;

XOR gate: $t_d = 5$ ns.

- (a) Draw the synchronous network graph, where weights of vertices are the combinational delays of the logic gates, and weights of the edges are the numbers of registers between two vertices.
- (b) What is the minimum cycle time currently (before retiming)?
- (c) Draw the constraint graph modeling to search for a legal retiming with a cycle time of 12 ns.
- (d) To find a retiming solution, apply the Bellman-Ford Algorithm on the constraint graph using r_a as the source (compute the longest distance from r_a to each vertex).
- (e) Redraw the retimed synchronous network graph using the retiming vector \vec{r} obtained in (d). Verify that the targeted cycle time 12 ns is met.