 


Fusion Compiler Project

- Project to understand and optimize a design with Fusion Compiler (FC)
- Reference design a MAC unit which does:
 - $a*b + c$
 - $a, b,$ and c are three signed 32b integers
 - result is a signed 32b output
 - yes, it can overflow and for the purpose of this exercise we are ok with it
- Final project requires a PDF answerings the questions that will follow
- Get the project folder at:



/education/classes/2025-2026/CS472/FC_Labs/FC_Labs/labs/project



Q1


Given the RTL and the script which contains a 33x33 floorplan

Run the first script:

make run_1

Questions:

 - a. **What is the critical path in each compilation step?**
- b. **Write the chain of cells of the critical path:**
 - i. **How long it is?**
- c. **What is the utilization?**






Q2

Look at the modified RTL `mac_unit_2.sv` to see how we break the path from the multiplier to the adder as in the Figure. Complete the 2nd script to have a floorplan 36x36 and answers the questions below:

make run_2

 Questions:

- What is the critical path in each compilation step?**
- Write the chain of cells of the critical path:
 - How long it is?**
- What is the utilization?**





Q3 & Q4

Optimize the floorplan of the **design1** (mac_unit) in project3 and **design2** (mac_unit_2) in project4 to be as small as possible (yet placeable with utilization <100%). Re-run the synthesis of the two design and report a pareto curve graph and table with AREA and LATENCY (where latency is number of cycles to get the valid result * minimum period)

Careful: if you select a too small floorplan, compile_fusion will raise an error

DESIGN	AREA (WxH) [um ²]	LATENCY [ns]
design1		
design2		




Q5

Optimize the floorplan of the design1 (mac_unit) in project5 a to be as fast as 1.5ns (yet placeable with utilization <100%). Re-run the synthesis of the design and compare its LATENCY-AREA against the previous designs.

Questions:

 - a. **What is the critical path in each compilation step?**
- b. **Write the chain of cells of the critical path:**
 - i. **How long it is?**
- c. **What is the utilization?**
- d. **What is the throughput?**
- e. **What is the latency?**





Q6

Modify the floorplan to be as little as possible and and synthesized the `mac_unit_3.sv` which uses 16b datapath Complete the 3rd script and answers the questions below:

Questions:

- What is the critical path in each compilation step?
- Write the chain of cells of the critical path:
 - How long it is?
- What is the utilization?
- What is the throughput?
- What is the latency?
- Explain the different architectures with PROs and CONS
- Draw the dataflow graph

$$\begin{aligned}
 &A_{32} * B_{32} = \\
 &uAL_{16} * uBL_{16} + \\
 &sAH_{16} * uBL_{16} \ll 16 + \\
 &sBH_{16} * uAL_{16} \ll 16 + \\
 &sAH_{16} * sBH_{16} \lll 32
 \end{aligned}$$

Where s or u means signed or unsigned and 32 and 16 means data width and H or L means higher (31:16) or lower part (15:0)

Report

- Complete and understand the previous scripts
- Write a **PDF report** answering the previous questions:
 - **Max 2 pages**
 - **Each question is worth one point**
 - **Deadline Thursday 6th 23:59**
 - **Submission through Moodle**

