

EE-334


Digital System Design

Custom Digital Circuits
Field Programmable Gate Arrays
(FPGAs)

Andreas Burg

Implementation Options for Digital Circuits

 
- Digital **systems** often **require** different **digital functions** which are **not** readily **available** as **standard** commercial off-the-shelf (COTS) **integrated circuits**.
- Options to realize those functions:



<https://hackaday.com/2019/06/23/a-ttl-cpu-minimising-its-chip-count/>

Composition of discrete Components

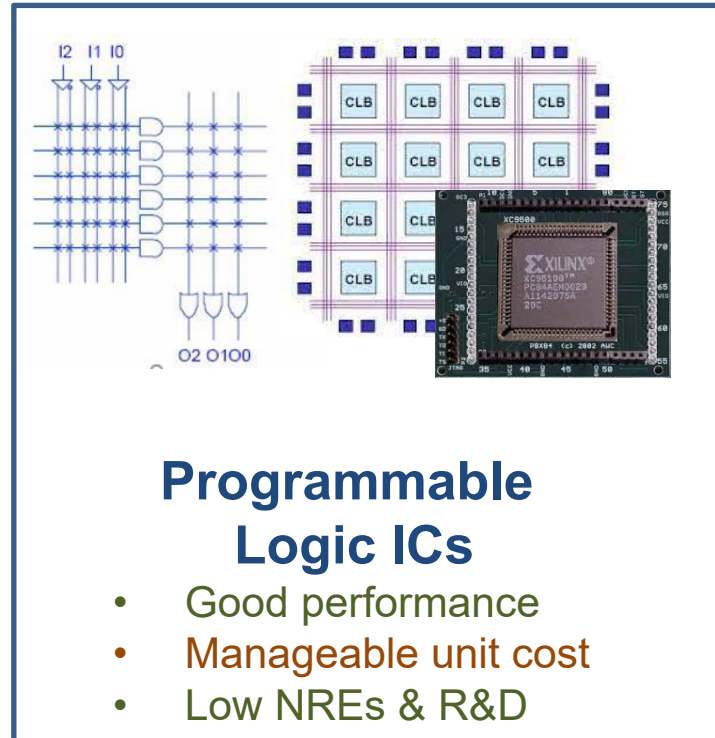
- **Poor performance**
- **High unit cost**
- **Manageable NREs & R&D**



Programmable Logic ICs

- **Good performance**
- **Manageable unit cost**
- **Low NREs & R&D**

Option of choice for medium volume

 

Application specific integrated circuit


- **Great performance**
- **Very low unit cost**
- **Very high NREs & R&D**

Basic Idea of Programmable Logic

- **Objectives:**
 - **avoid high NREs** of a dedicated ASIC
 - **speed up** the **development process** for each application
 - provide **flexibility to update a system** in the field
- **Programmable logic device:** a **fixed** application specific IC (**ASIC**) that
 - **Integrates** all the **basic building blocks (logic & memory)** to **realize** different **digital circuits**
 - **Allows to change connections** between components after manufacturing (**at run time**)
- **After programming**, the **chip behaves** similar to a dedicated ASIC **as custom digital logic**, ideally with no visible difference


Programmable Logic Application

- **Development** of custom digital logic based on same principles as for an ASIC
 - **Synchronous RTL design**
 - **Similar** design tools to those for **semicustom ASIC design**
 - Device limitations impose **additional restrictions on complexity and abstraction**
- **Programming configures the device**
 - **from a PC** or from a separate **non-volatile memory** (EEPROM or FLASH)
 - **Some devices can store the configuration in on-chip non-volatile memory**
 - Dedicated interface (parallel or serial) or through JTAG (standardized test-access port)
 - **In-system programming**: programming while the chip is already integrated
 - **Run-time reconfiguration**: reconfigure parts of the FPGA during operation

 



Principle of Programmable Logic

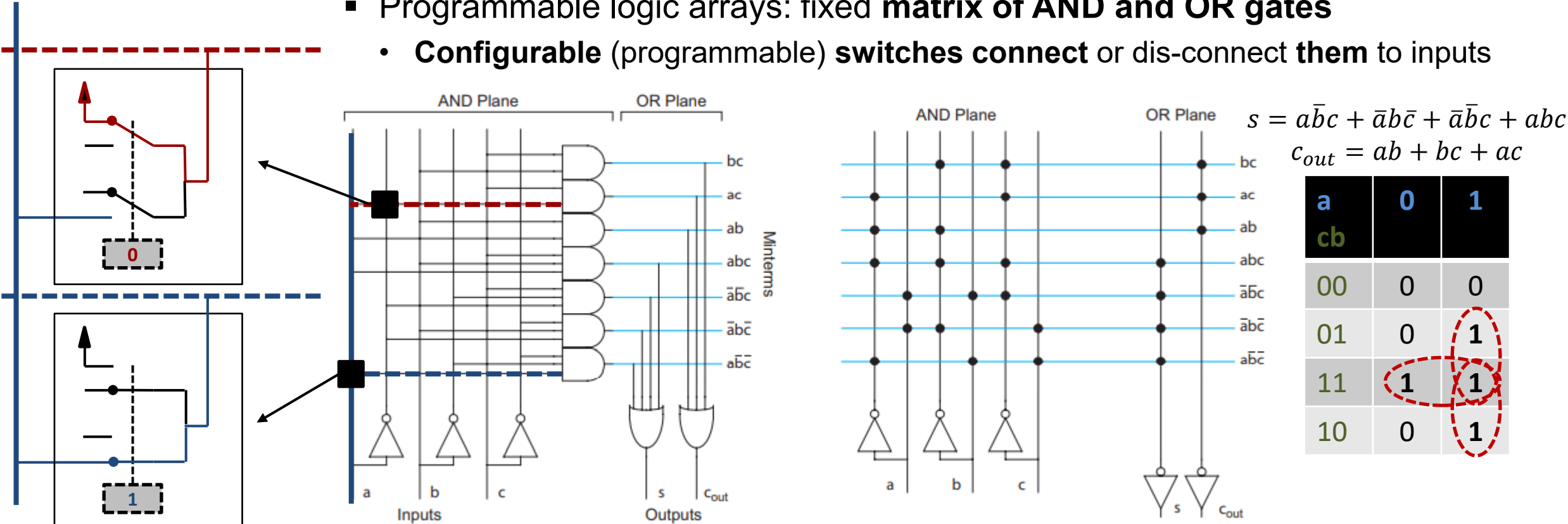- Remember: **any logic function can be realized** with 2 logic stages as
 - Sum-of-products:** 2-stage AND-OR function of inputs and inverted inputs
 - Product-of-sums: 2-stage OR-AND function
 - Programmable logic arrays: fixed **matrix of AND and OR gates**
 - Configurable** (programmable) **switches connect or dis-connect them** to inputs



Early Complex Programmable Logic

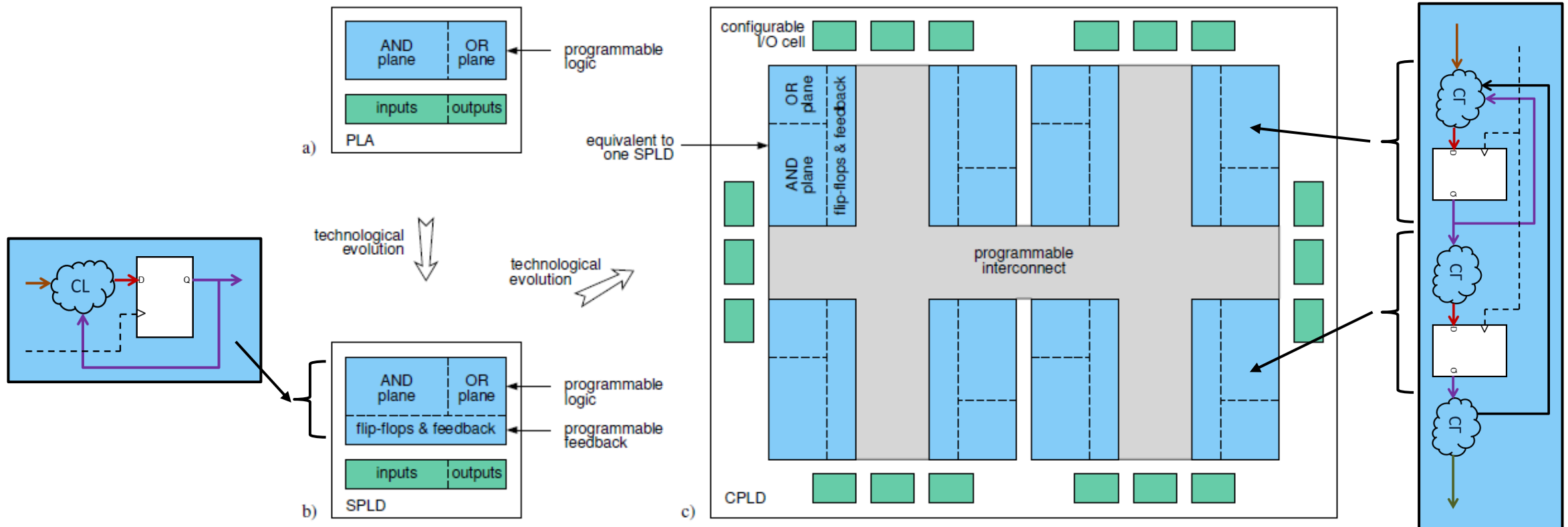 - **Complex Programmable Logic Devices (CPLDs):**
multiple stages of logic and registers in a single device
- **Some programmable interconnect between large logic stages**




Issues of AND-OR Based Programmable Logic

- The **AND-OR** based **2-stage logic style** of PLAs/CPLDs **has several disadvantages**
 - From an **application perspective**
 - 2-stage logic **limits the fan-in** (maximum number of inputs per output)
 - 2-stage logic also **limits resource/logic sharing** between multiple outputs
 - Modern synthesis tools, developed for ASIC design, rely on multi-stage logic
 - From a **device design perspective**
 - PLAs, especially with larger fan-in have a **high power consumption**
 - Area-**efficient implementation** of PLA circuit **is** sometimes **tricky**
 - **Not well suited** for the highly efficient **CMOS** logic style
(**favours** more tricky logic styles such as **dynamic logic** or **pseudo-nMOS logic**)
 - Few large **interconnects** between complex logic stages **involve large overhead**

Field Programmable Gate Arrays (FPGAs)



- **FPGAs**: Similar idea to CPLDs, but **built for multi-stage logic** (with logic sharing)
 - Collection of **many small** programmable **logic/register blocks**
 - Focus on **massive, but highly modular interconnect** between logic blocks
- **Configurable logic blocks (CLBs)**:
 - Registers
 - Programmable logic with 4-6 inputs
- **Interconnect wires** and **switch matrices**:
 - 2D grid of short and long wires
 - Local **switch matrices** to connect
 - Wires to wires
 - Wires to logic blocks
- Programmable IOs (pads)

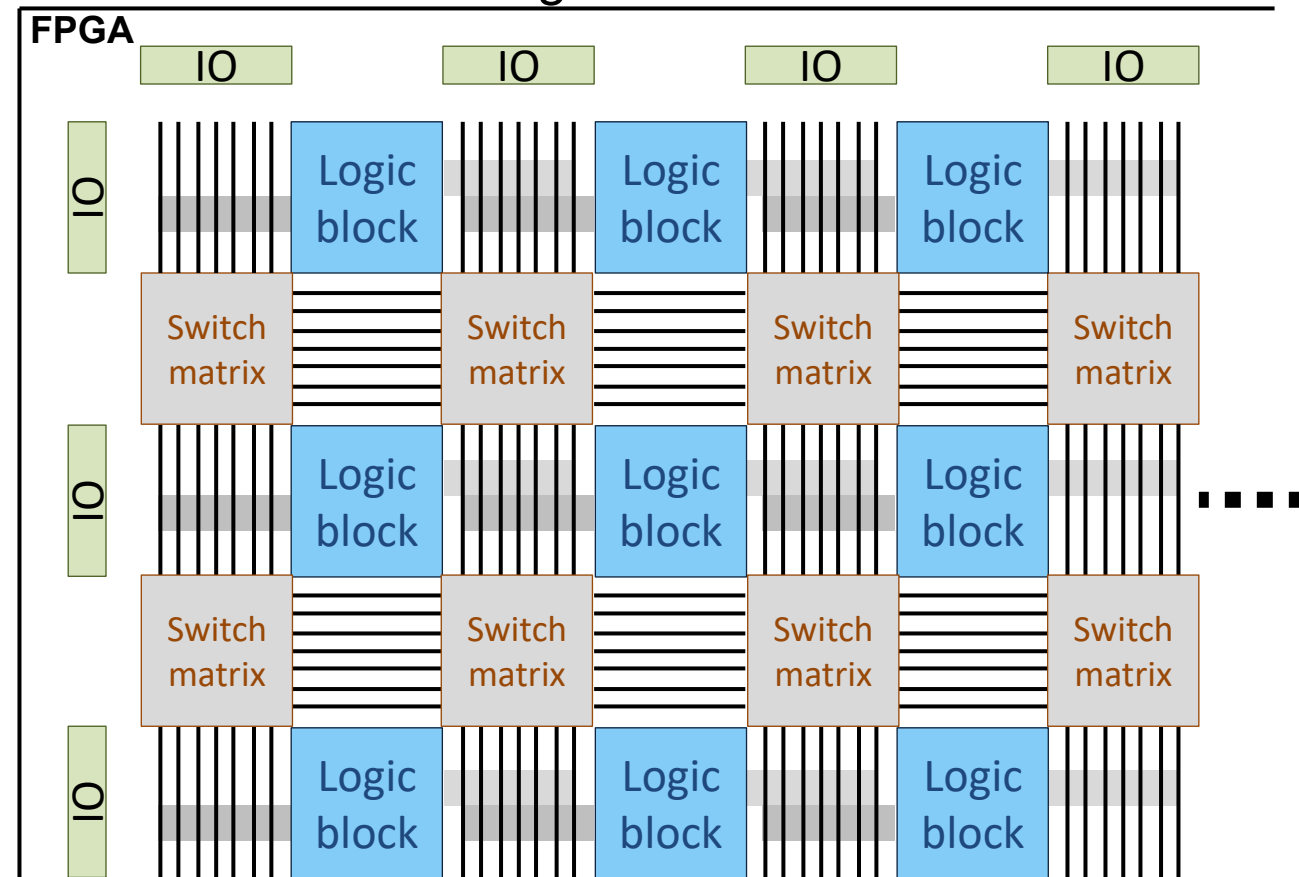

Implementation of Logic Operations in FPGAs

- Logic is implemented based on programmable **look-up tables**
- **Basic principle:** start from truth table representation
 - **Programming:**
 - Registers connected as a shift-register
 - **Truth table** content (logic result) **shifted into the LUT configuration registers** during programming
 - **Operation (after programming):**
 - **Truth table** content stored in **configuration registers**
 - A **multiplexer** chooses the **output** from the registers **based on the logic input**
- **Note:** LUT is basically a memory that is pre-loaded during configuration

ABC	Z
000	0
001	1
010	0
011	0
100	1
101	1
110	0
111	1

  

Implementation of Logic Operations in FPGAs

- **Logic is implemented based on programmable look-up tables**

- **Functional registers** (with bypass) added to LUT outputs

- **Basic principle:** start from truth table representation

- **Programming:**



- Registers connected as a shift-register
- **Truth table** content (logic result) **shifted into the LUT configuration registers** during programming

- **Operation (after programming):**

- **Truth table** content stored in **configuration registers**
- A **multiplexer** chooses the **output** from the registers **based on the logic input**

- **Note:** LUT is basically a memory that is pre-loaded during configuration



ABC	Z
000	0
001	1
010	0
011	0
100	1
101	1
110	0
111	1

  

Logic Blocks in Modern FPGAs



- Modern FPGAs all build on the LUT concept
- **Trend: cluster more logic/registers into each configurable logic block to minimize use of the slow global interconnect**
 - **Additional logic** (e.g., MUXes after LUTs or dedicated connections) **supports** important and frequent **high fan-in logic** operations
 - **Implement larger LUTs** with multiple outputs
 - XILINX Virtex-7: supports either 5-input-1-output OR 6-input-2-output
 - Advanced **LUTs can be re-purposed for special functions**, e.g., memory or shift registers

Example: XILINX Virtex-5 Slice

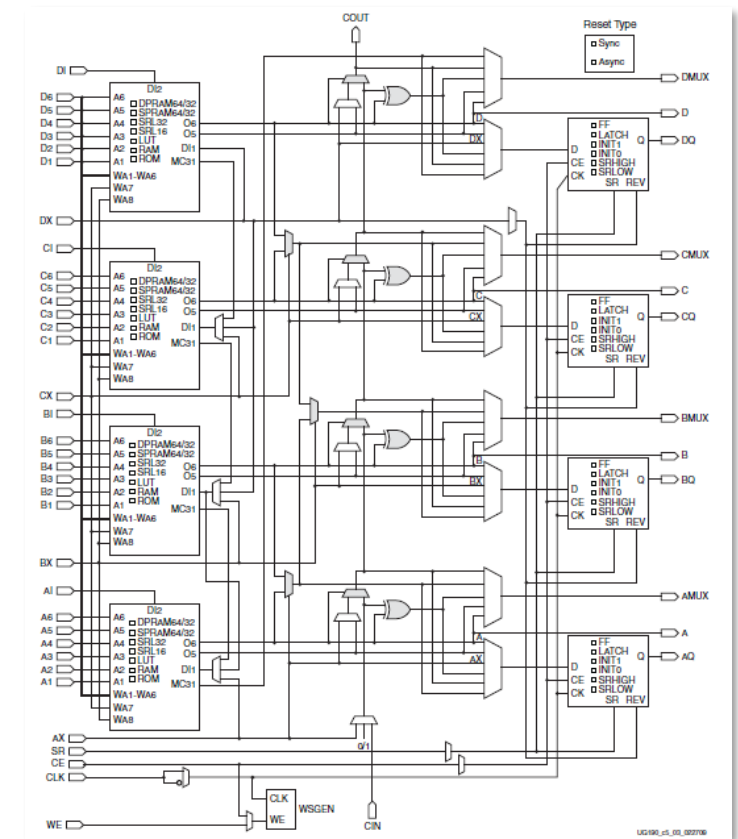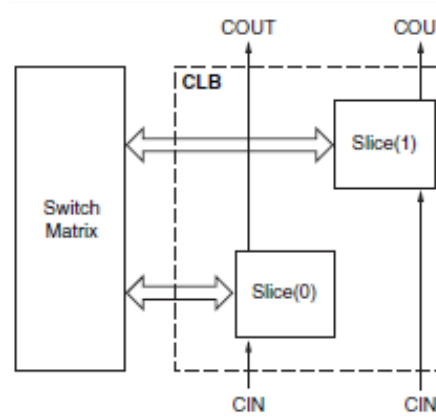

Connecting CLBs with Configurable Global Routing

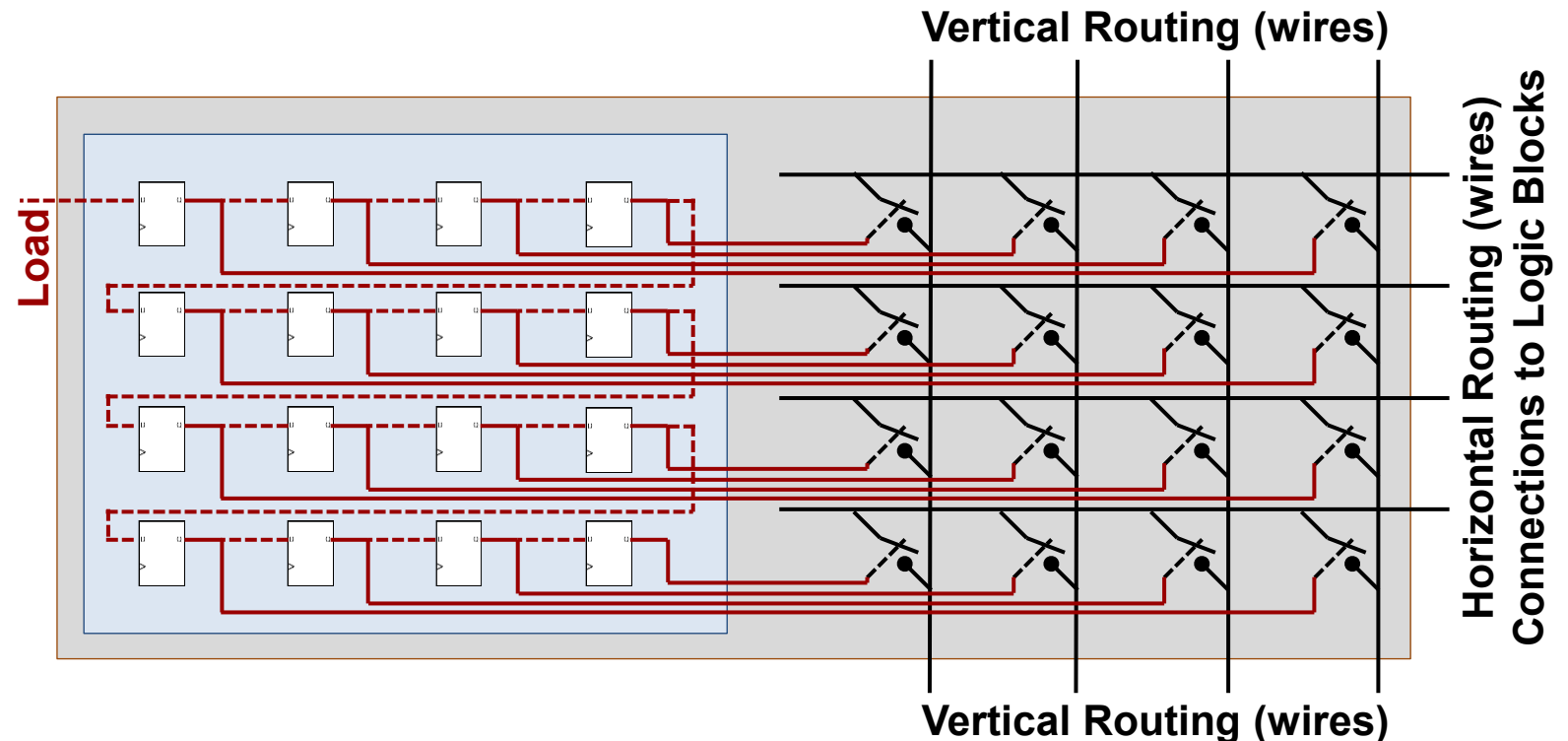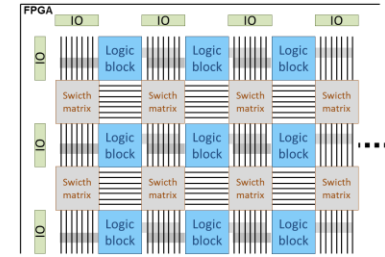
- **Routing resources** on the **FPGA devices** comprise
 - **Wires** (short (local) and long (global)) **that run both horizontally and vertically**
 - **Switch boxes** to connect
 - wires to logic blocks and
 - horizontal and vertical wires
 - Configuration in registers
 - **Programming:** through shift register configuration



Programming FPGAs


- **Programming loads the configuration registers & LUTs** of the FPGA logic and the programmable routing (switch boxes).

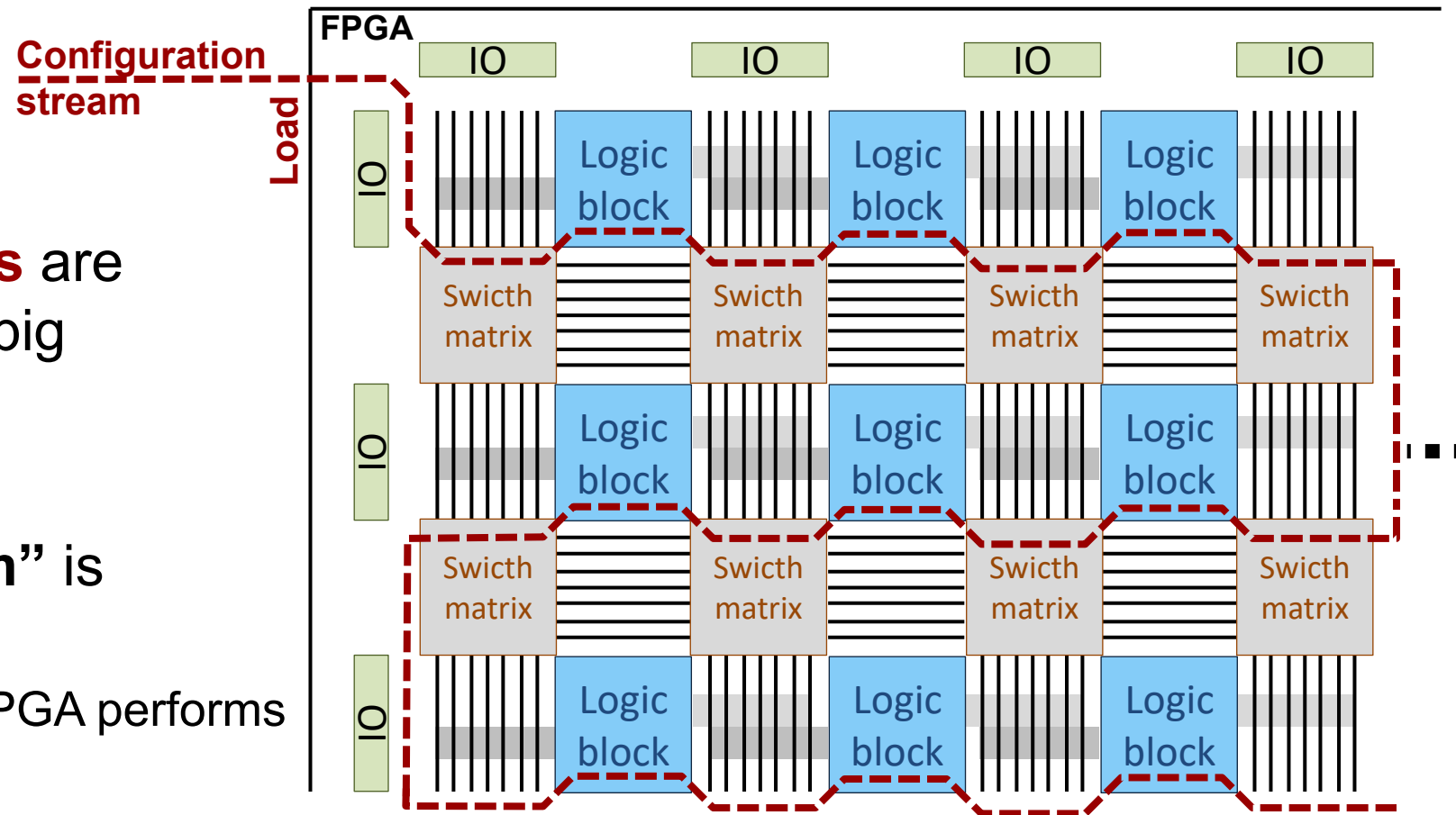- All **configuration registers** are **daisy chained** in a single big shift register
- **Configuration “bit-stream”** is shifted in bit-by bit
 - After this configuration, the FPGA performs the configured function



Modern FPGAs also Include Complex Macros

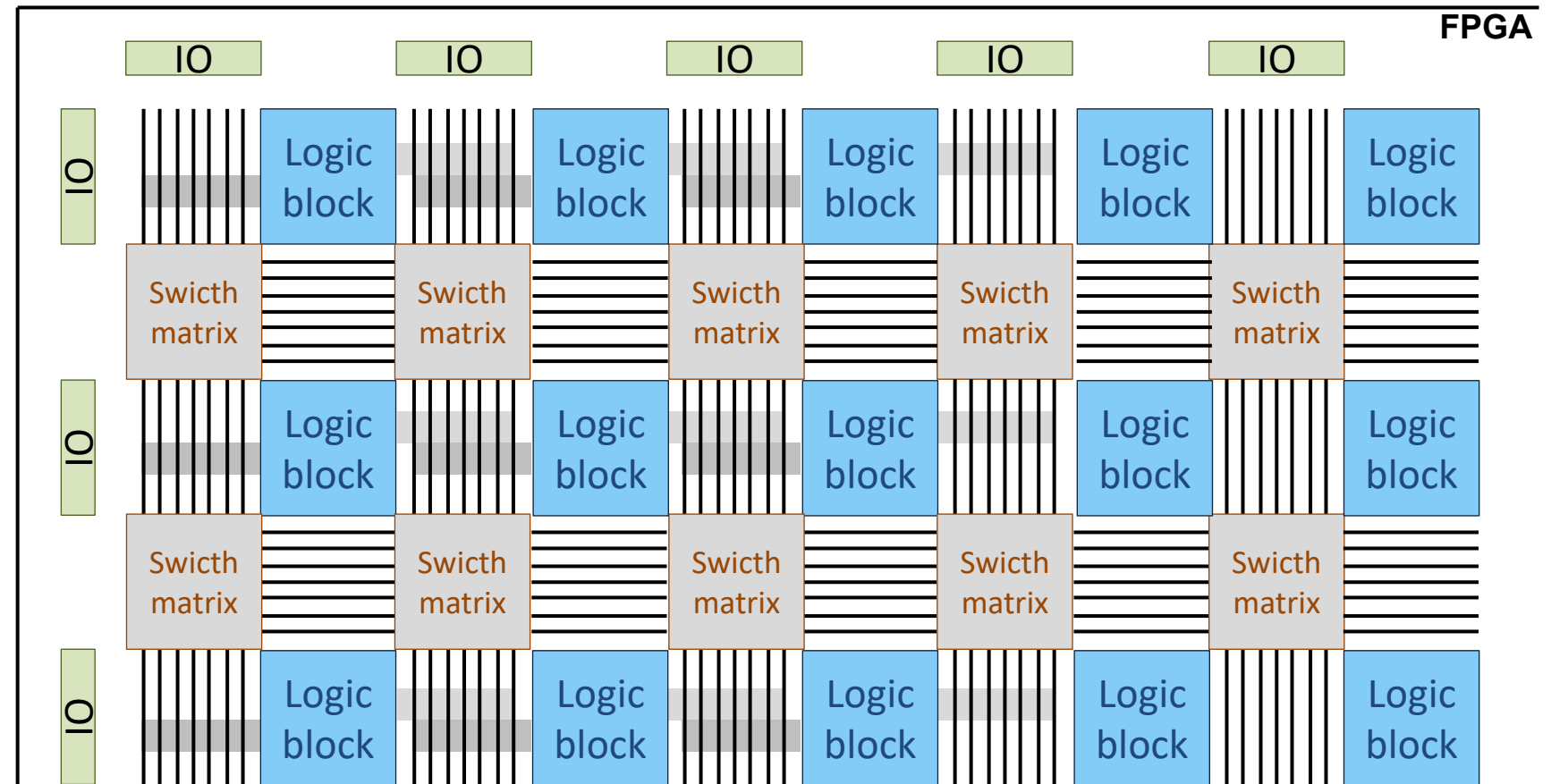- **Some common functions** (e.g., arithmetic, memory) **are costly** and slow **when realized with** general purpose **configurable logic** blocks




Modern FPGAs also Include Complex Macros

- **Some common functions** (e.g., arithmetic, memory) **are costly** and slow **when realized with** general purpose **configurable logic** blocks

- **Solution:** integrate **common complex functions as fixed, optimized macros**

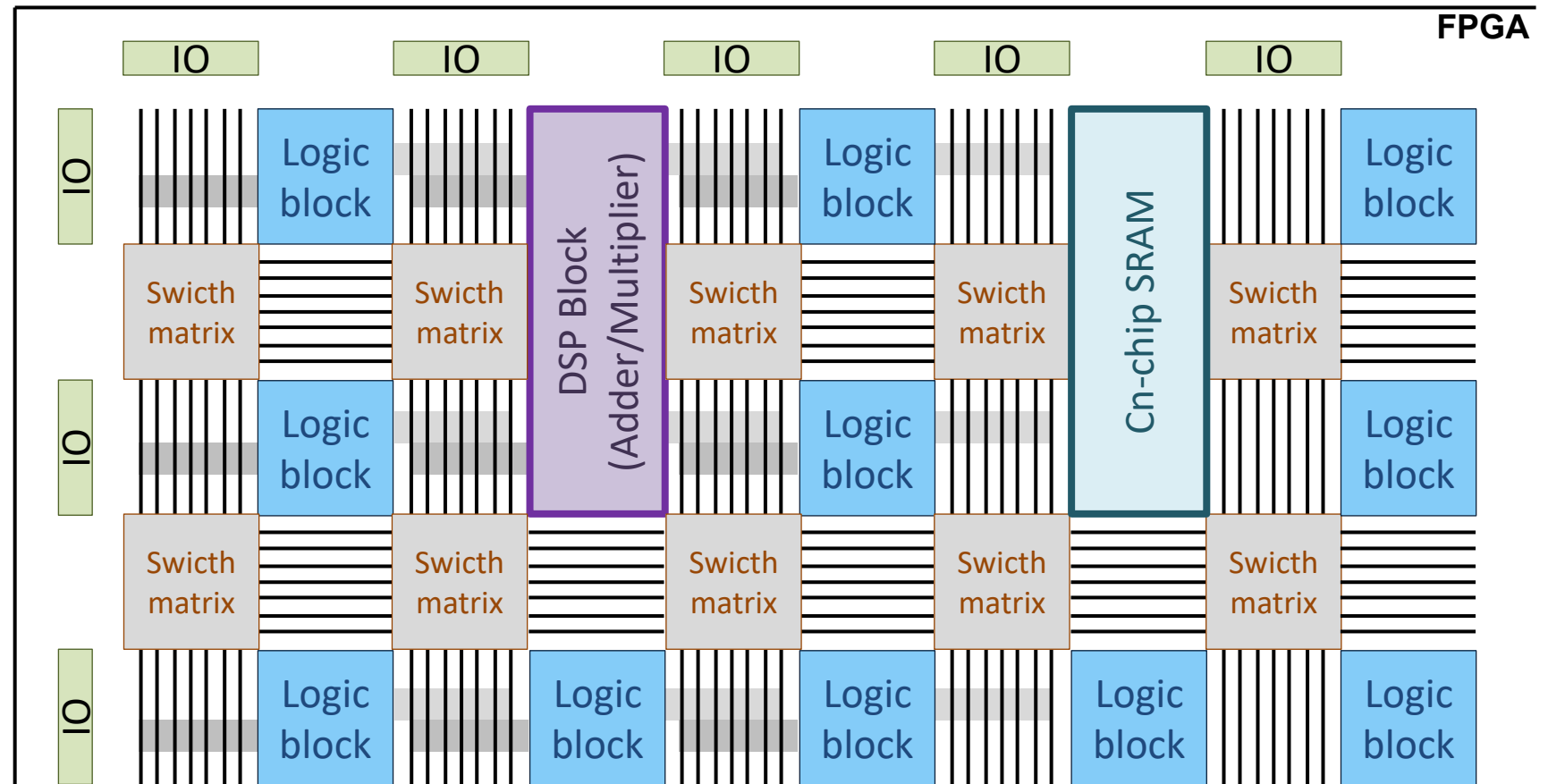
- Examples:
 - **DSP blocks**
 - **On-chip SRAM**



Modern FPGAs as SoC Platform

- Complex **systems often include microprocessors** and high-speed interfaces
 - Microprocessor sub-systems are generic and can be very efficient in dedicated logic
 - High-speed interfaces require dedicated analog circuits (can not map to CLBs)

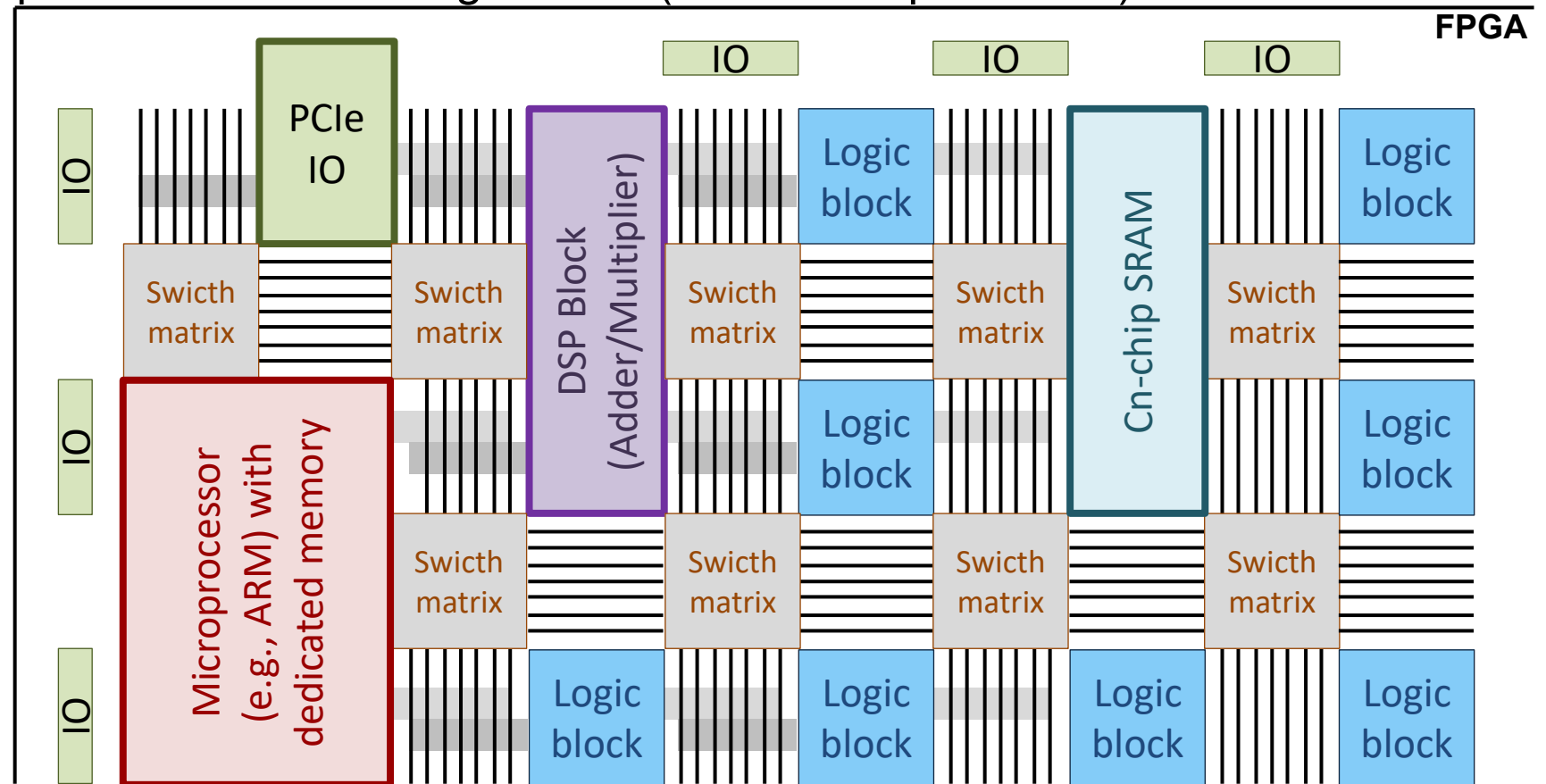- **FPGA SoCs include Micro-processors** that have access to the programmable logic (e.g., for accelerators)
- **High-speed IOs** are added for common standards (e.g., PCIe)



The FPGA Implementation Flow

- **FPGA design** typically **starts from HDLs**
- **Synthesis produces a netlist** of logic gates
- The **netlist is partitioned** into groups of gates that are **mapped into** individual **LUTs**
- **Place**: assign LUTs to logic blocks
- **Route**: determine switch box configuration
- **Bitfile generation**: write out the configuration bits to be loaded into the FPGA
- Load bit stream into FPGA

