

# EE-334

# Digital System Design


## Custom Digital Circuits

### Timing Analysis and Constraints in Synchronous Circuits

Andreas Burg
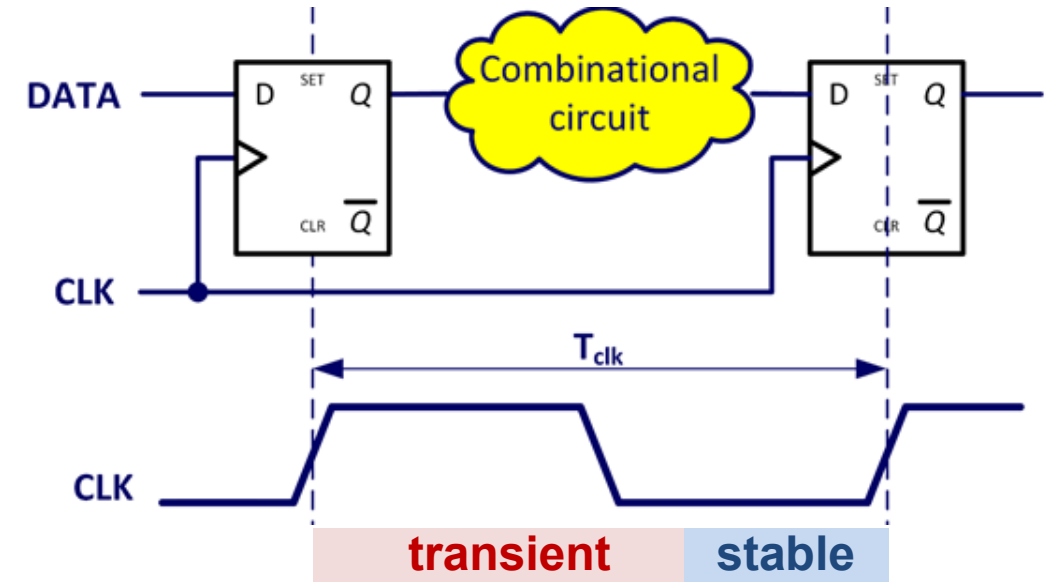
# Reminder: Principle of Synchronous RTL Design



- Synchronous circuits are composed of
  - Registers that store the current state and
  - Combinational logic that defines the next state
- A **single global clock signal triggers all registers** at the same time
  - **Registers capture all outputs** of the combinational logic at the same time **when they are stable**
  - Inputs of all combinational circuits change at the same time
- **After the positive clock edge**
  - **the circuit enters a transient state** and
  - **stabilizes again after some time**, ready for the next clock edge



How can we verify that data is always captured safely?

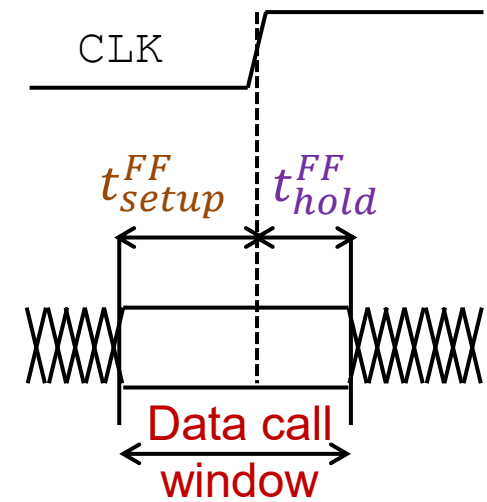
 
# Register Timing Requirements

- Requirements for safely capturing the next state/data are set by the registers
- Input must be **stable during the data call window** around the active clock edge
- Formal register **timing requirements**:
  - Setup time  $t_{setup}^{FF}$ : time the data must be stable before the active clock edge
  - Hold time  $t_{hold}^{FF}$ : time the data must remain stable after the active clock edge


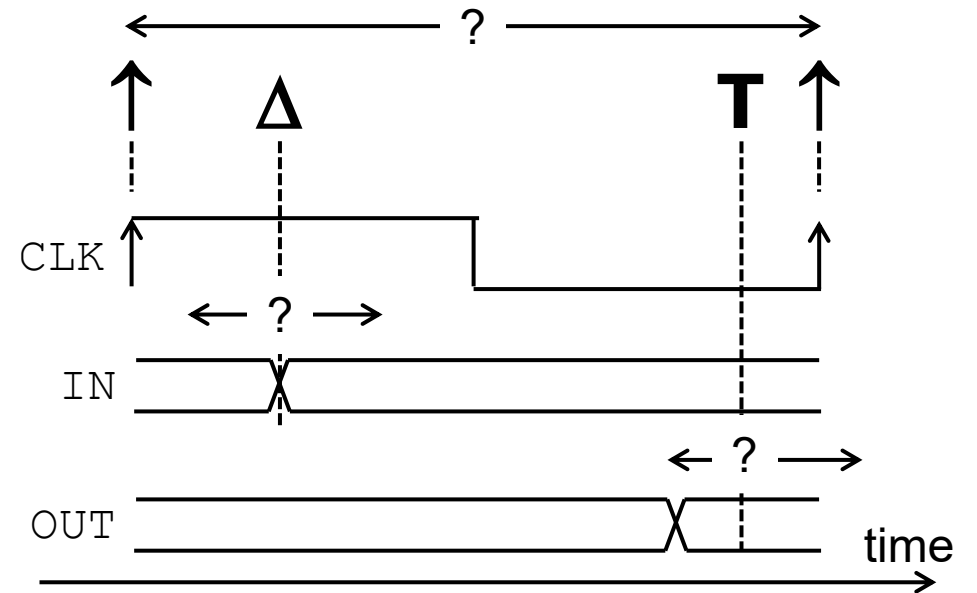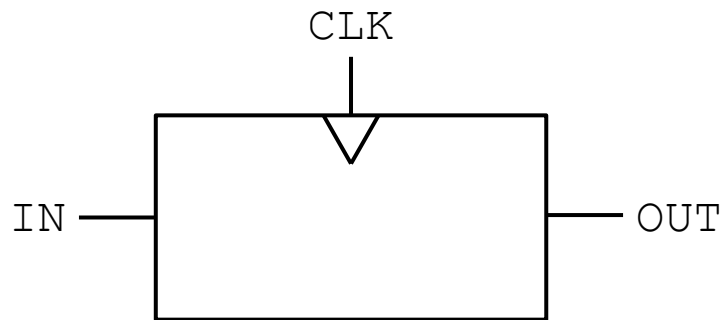
# Static Timing Analysis (STA)

- **Static Timing Analysis** characterizes a digital circuit in terms of its timing parameters and **verifies the timing requirements** of a circuit and its registers
- Questions answered by static timing analysis
  - **How fast can we clock a circuit?**
  - **What is the time window in which we can safely**
    - **apply signals** to the input? (stimuli application)
    - **sample the output** of a circuit? (response acquisition)



**Δ . . . Stimuli application**



**T . . . Response acquisition**

**↑ . . . Active clock edge**



# Modelling the Delay of Combinational Circuits

- Combinational Circuits are composed of combinational logic gates

- Logic gates have a propagation delay**

  



- Delays of subsequent gates add up**

  

- To abstract transient effects it is convenient to **define a minimum and a maximum delay**


- Contamination delay (min):  $t_{cd}$**

- Propagation delay (max):  $t_{pd}$**

  
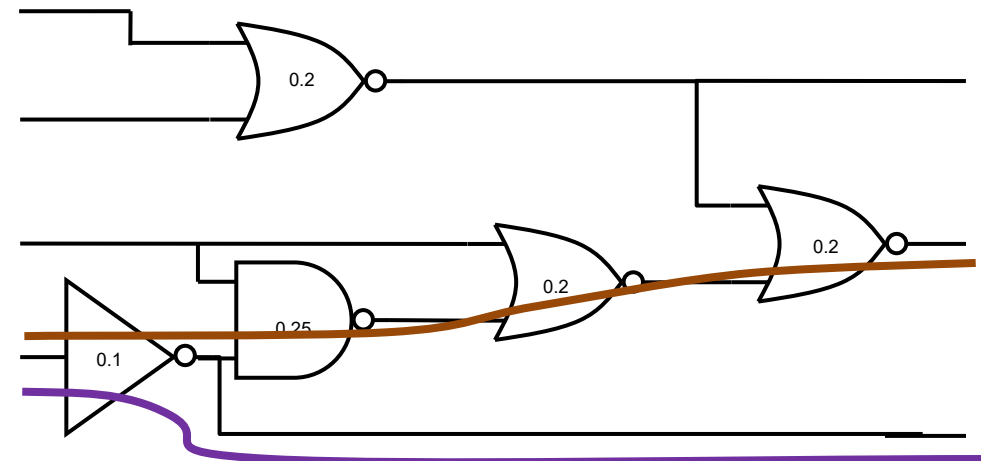
# Characterizing the Delay of Combinational Circuits


- **Combinational circuits have multiple inputs and multiple outputs**
  - Different inputs may cause changes in the same output
  - The same input may cause changes in different outputs
- **Consider all paths from all inputs to all outputs and define**
  - **Contamination delay:** shortest path  $t_{cd}$ 
    - Based on contamination delays of the gates
    - Earliest change of an output after a change on any input
  - **Propagation delay:** longest path  $t_{pd}$ 
    - Based on propagation delays of the gates
    - Latest change of an output after a change on any input




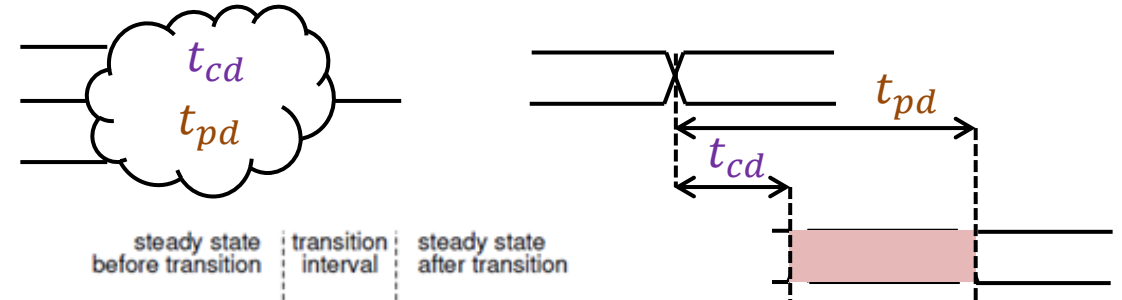
# Delays of Complex Gates and Sub-Circuits

- **Contamination delay and propagation delay determine the time when the output of a combinational circuit is guaranteed to be stable**

- **Transition window** (transient time between contamination and propagation delay):
  - **Outputs do not match Boolean equations**
  - **Must assume outputs are unknown**




- **Example**

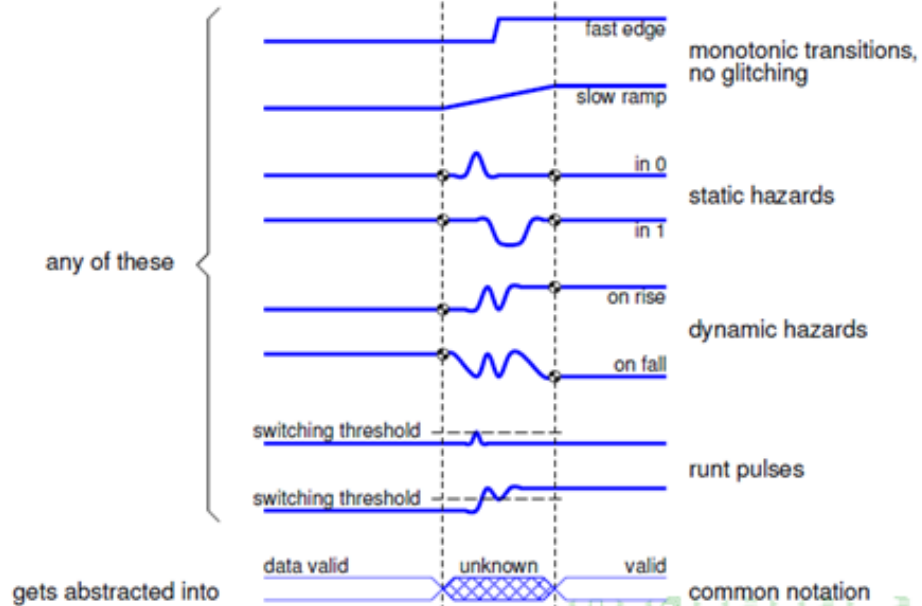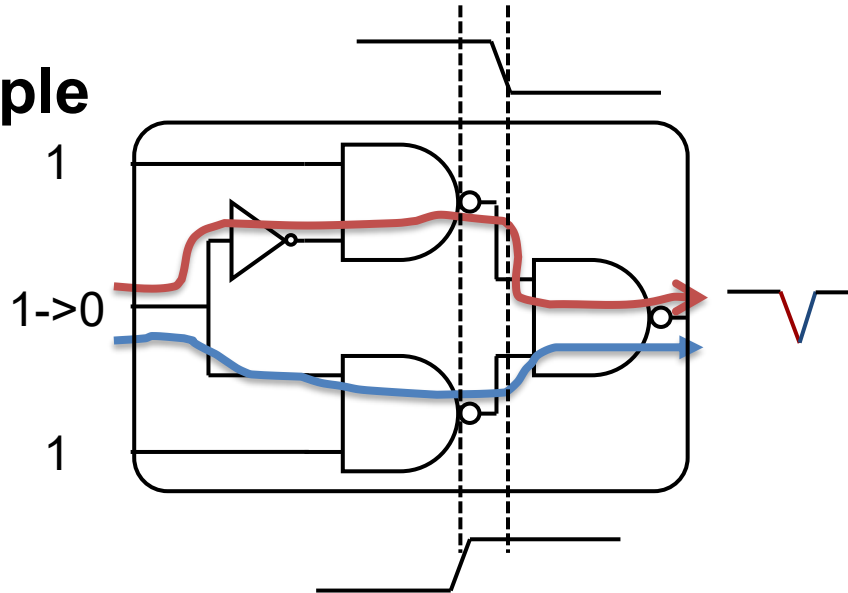
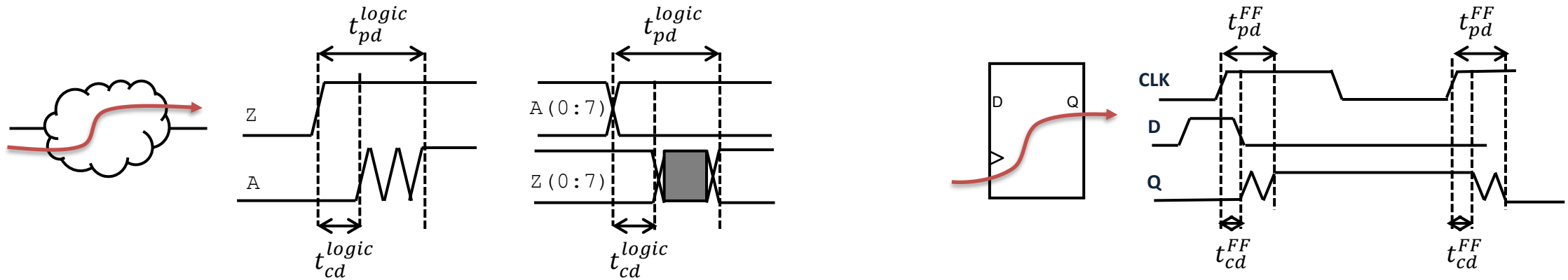
# Static Timing Analysis

- STA is based on **delays of combinational logic and sequential elements**



## Combinational logic


- Timing arc from input to output
  - Propagation delay  $t_{pd}^{logic}$
  - Contamination delay  $t_{cd}^{logic}$
  - Entire circuit (multiple paths)
  - Critical path  $t_{crit}^{logic} = \max(t_{pd}^{logic})$

## Sequential elements

- Timing arc **from clock to output** (between clock and data)
  - Propagation delay  $t_{pd}^{FF}$
  - Contamination delay  $t_{cd}^{FF}$
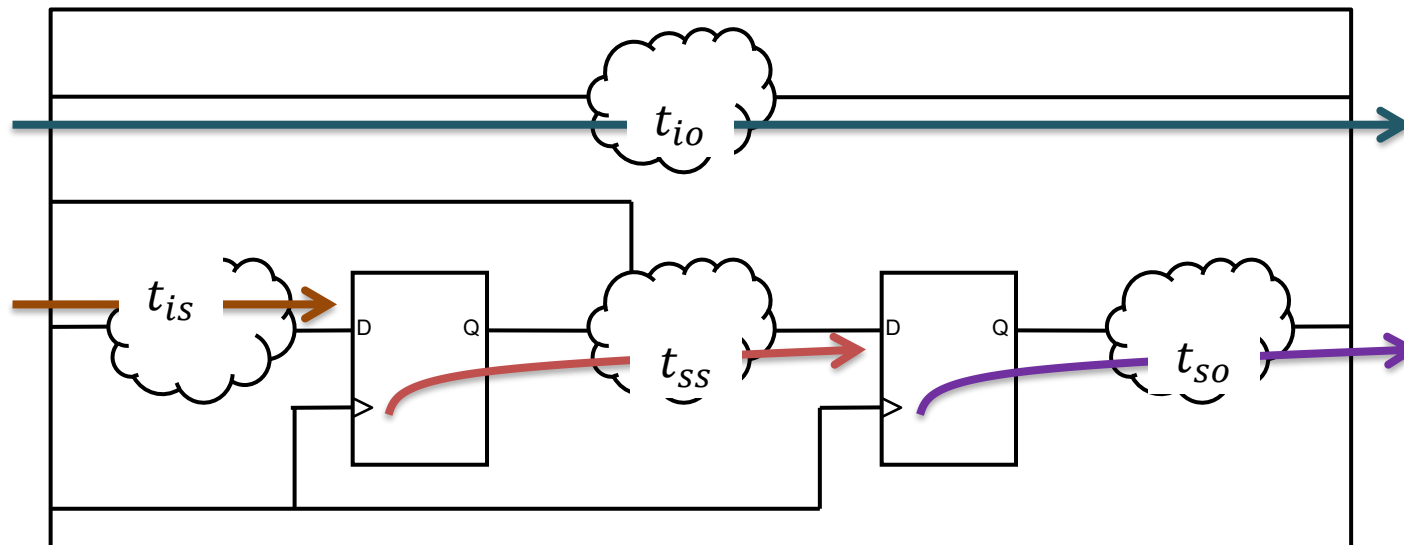
# Static Timing Analysis: Path Groups

- STA considers **four path groups**, defined by the type of start- and end-points
  - **Input-to-Register** ( $t_{is}$ ): from a primary input to a register data input
  - **Register-to-Register** ( $t_{ss}$ ): from **clock input** of a register to the **data input** of a register
  - **Register-to-Output** ( $t_{so}$ ): from clock input of a register to a primary output
  - **Input-to-Output** ( $t_{io}$ ): direct path from a primary input to a primary output



# STA: Checking Timing Conditions

- **Timing requirements for all register-to-register paths**
  - Path starts from the clock pin of a register and ends on the data pin of a register


- **Setup condition:** latest arrival

$$\underbrace{t_{pd}^{FF} + t_{pd}^{logic}}_{t_{ss}^{max}} < t_{clk} - t_{setup}^{FF}$$

Determines  
maximum  
frequency

- Hold condition: earliest arrival
 
$$\underbrace{t_{cd}^{FF} + t_{cd}^{logic}}_{t_{ss}^{min}} > t_{hold}^{FF}$$




# Critical Path

- The **critical path** is the path within a circuit that **limits its clock frequency**
- The critical path contains
  - For reg->reg: the Clk->Q delay delay of the register from which it starts
  - The delay of the subsequent logic
- The critical path does not include:
  - For in->reg: the stimuli application delay (if known, otherwise 0)
  - For reg->out: the output sampling time (if known, otherwise 0)
  - The setup time of the register at the end
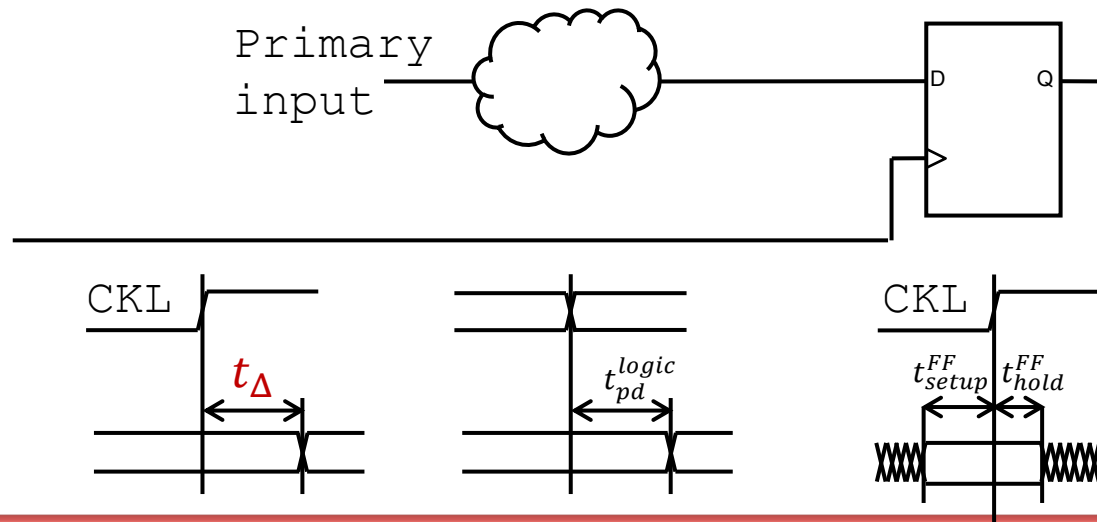
# STA: Checking Timing Conditions

- **Timing requirements** for all **input-to-register** paths
  - Path starts from **primary input** and ends on the **data pin** of a register
  - **Setup condition**: latest arrival  
 $t_{\Delta} + t_{pd}^{logic} < t_{clk} - t_{setup}^{FF}$
  - **Hold condition**: earliest arrival  
 $t_{\Delta} + t_{cd}^{logic} > t_{hold}^{FF}$

Determine  
setup window  
for primary  
inputs



# STA: Checking Timing Conditions

- **Timing requirements** for all **register-to-output** paths

- Path starts from data pin of a register and ends on the sampling of the output


- **Setup condition:** earliest (ideal) sampling

$$t_{pd}^{FF} + t_{pd}^{logic} < t_T$$

- **Hold condition:** latest (ideal) sampling


$$t_{cd}^{FF} + t_{cd}^{logic} > t_T$$

 **Determine the sampling window for primary outputs**



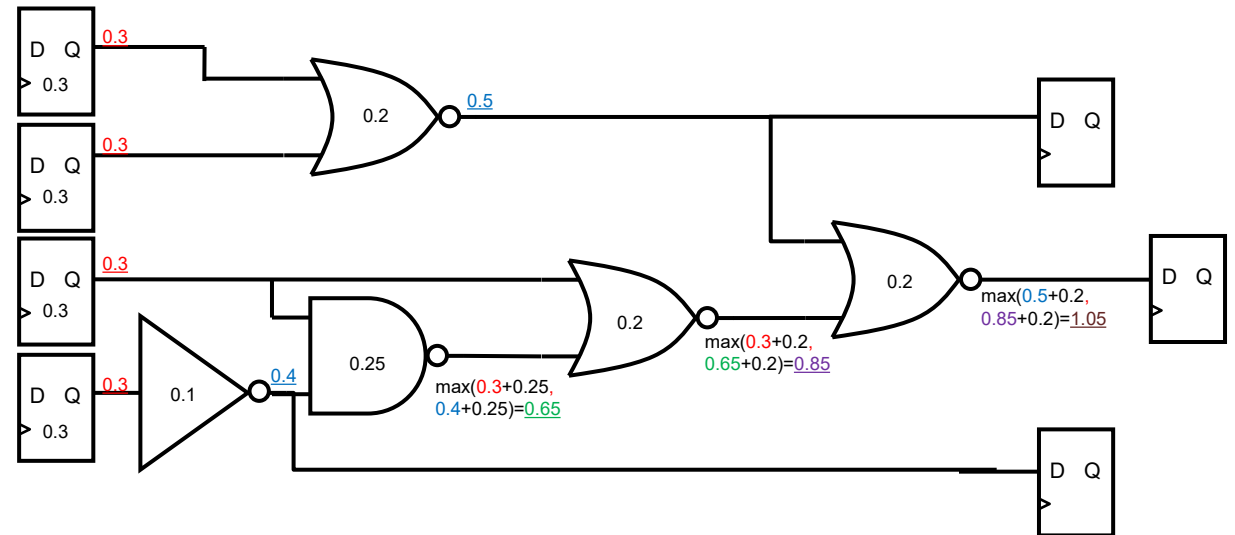
# Static Timing Analysis on Gate Level

- The STA procedure identifies
  - the critical (longest) path  $t_{pd}^{logic}$  to verify setup
  - the shortest path  $t_{cd}^{logic}$  to verify hold
- Identify the shortest and the longest path for the data-input of each Flip-Flop
  - Annotate the circuit with the worst-case arrival times (delay) of the signal
  - Start from the clock input of the FFs
  - Keep only the longest (shortest) path (Add-Compare-Select)




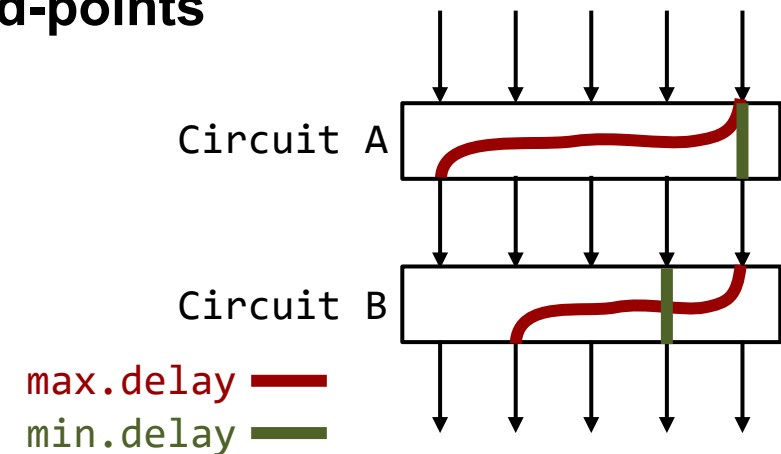
# Static Timing Analysis of Datapath Components

- STA of gate level circuits is tedious and therefore carried out by automatic tools
- Designers often want to **have a quick estimate of complex circuits composed of arithmetic components** or other well-studied combinational circuits
- Combinational sub-circuits have multiple inputs and multiple outputs
  - **Critical paths** of sub-circuits **have different start and end-points**
    - Critical end-point in one sub-circuit is often NOT the critical starting point in the next sub-circuit
- **Accurate timing analysis is difficult**
  - Needs to be done at the gate level or with complex models of the individual sub-circuits.


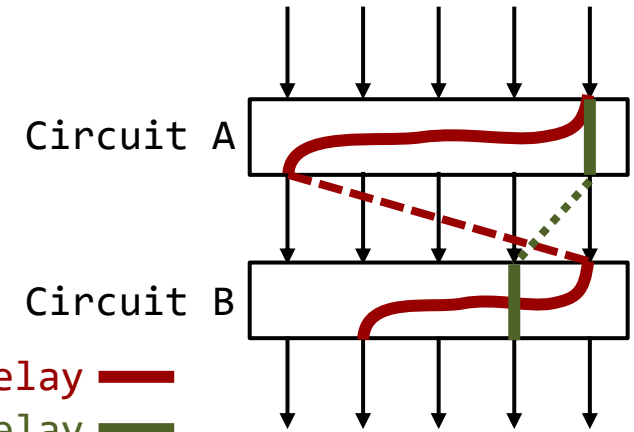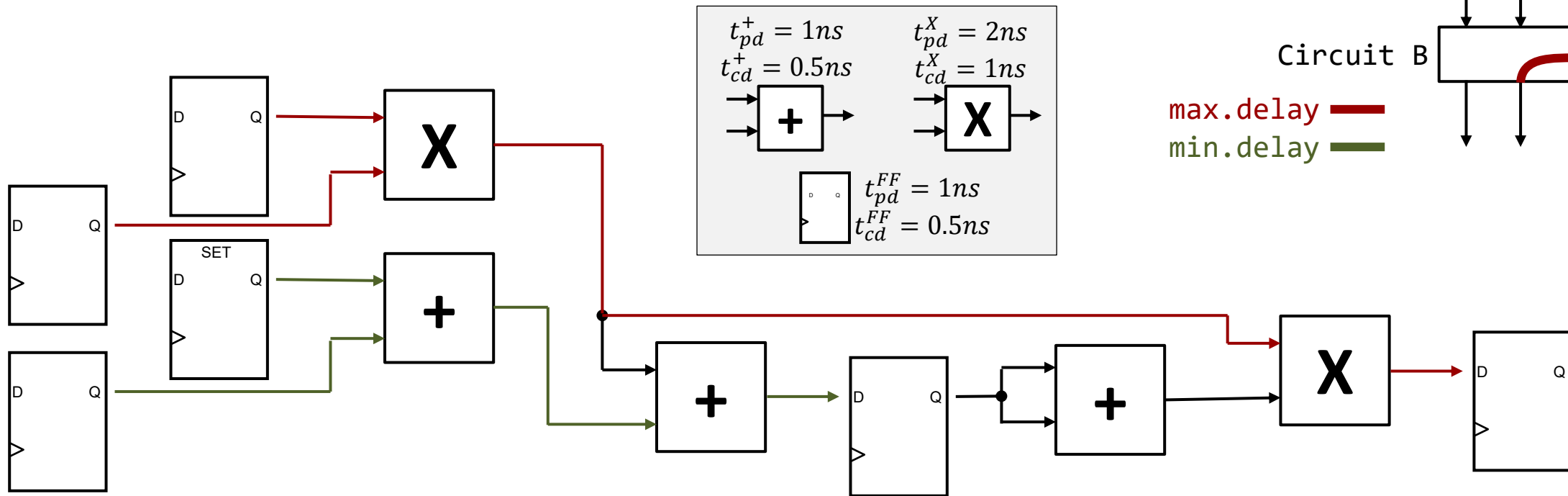
# Static Timing Analysis of Datapath Components

- In practice, we are often only **interested in a quick worst-case estimate**
  - Model** timing of **each** (combinational) **component** with its **min. and max delay** only
  - Worst case estimate** obtained by
    - Approximating the **longest path from the sum of the maximum delays**
    - Approximating the **shortest path from the sum of the minimum delays**




# Timing in Hierarchical Designs

- Concatenate two blocks A and B (design entities or chips)
  - Register-to-output path of block A and the input-to-register path of block B merge into a new register-to-register path




$$t_{so}^{max}(A) + t_{is}^{max}(B) < t_{clk} - t_{setup}^{FF}$$
 
$$t_{so}^{min}(A) + t_{is}^{min}(B) > t_{hold}^{FF}$$


  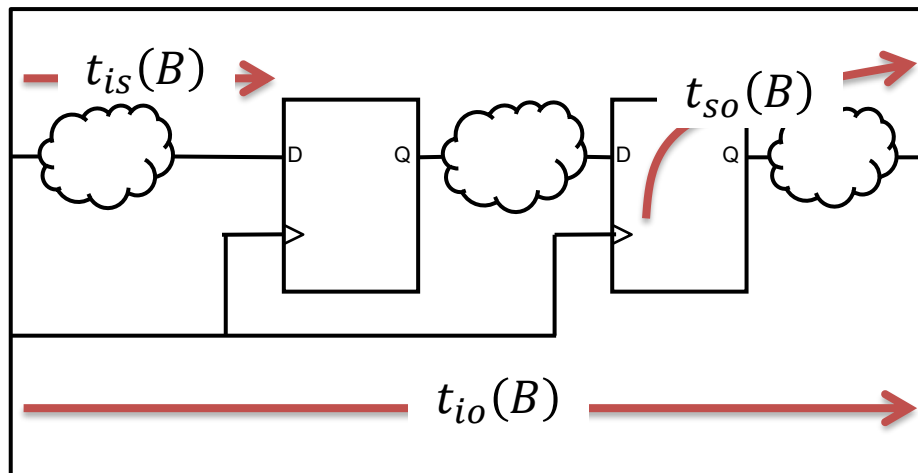
# Timing in Hierarchical Designs

- Timing of individual blocks can be abstracted using clk-Q, setup-, and hold-concepts
  - Interpret the clocked block as a single flip-flop:
    - Input delays translate into setup-  $t_{su}^A$  and hold-delays  $t_{ho}^A$
    - Output delays translate into clk-Q delays:  $t_{CQ}^A$
  - Input-to-output delays remain and are modelled like combinatorial logic gate



$$t_{su}^B = t_{is}(B) + t_{setup}^{FF}$$

$$t_{ho}^B = t_{ho}^{FF} - t_{is}(B)$$

$$t_{CQ}^B = t_{pd}^{FF} + t_{so}(B)$$

$$t_{io}^B$$