

# EE-334



# Digital System Design

**Custom Digital Circuits**  
VHDL for Synthesis –  
Basic Constructs and Correspondences


Andreas Burg
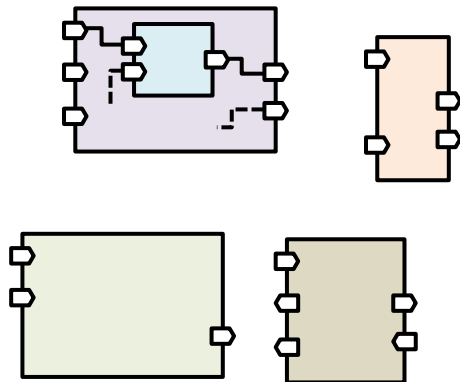 
# Hierarchy and Instantiation

- **Hierarchy is required** for modularity, abstraction, and **to deal with complexity**
- **Blocks used later** in a hierarchy **are** called **COMPONENTS**
  - **Components can themselves be hierarchical** (include instances of other components)
  - **Signals** declared in a component are **only visible within the component**
  - The interface of a component is defined by its ENTITY
- Each “**appearance/use**” of a component is called an **INSTANCE**
  - There can be **multiple instances of the same component**
  - **Instances are connected through** the ports of their components





all  
separate  
VHDL files

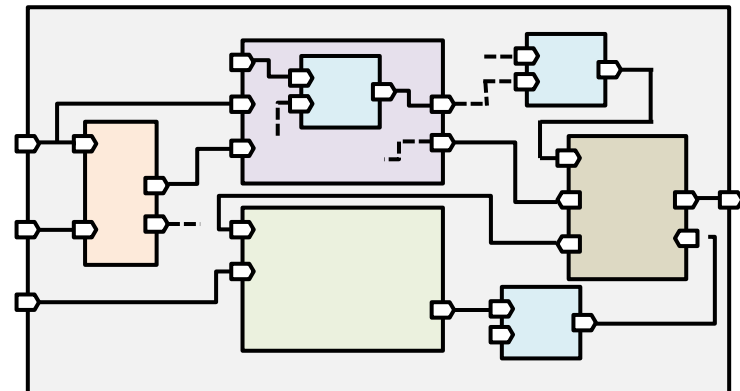

# Components vs. Functions

- Only **distant analogy** to functions in programming: **similar purpose** (reuse), **BUT very different physical presence**

## Hardware (VHDL)

  

Co-exist  
in parallel

## Software (C)

```
Int my_fct(int a, int b)
{
    return a+b;
}

Main() {
    ...
    x = my_fct(a, b);
    y = my_fct(c, d);
    z = my_fct(x, y);
}
```

Function definition

Function calls

Sequential execution

# Instantiating Components in VHDL (1/2)

- **Components need to be declared** before instantiating/using them in the architecture of another component
  - **Declaration in the preamble of the architecture** in which they are used
  - Alternative: declaration in a package (not discussed here)
- **Component declaration & name must match the corresponding entity name**

Entity declaration of a component in a file,  
e.g., entity\_name.vhd

```
ENTITY entity_name IS
    GENERIC (
        generic_1_name : generic_1_type;
        generic_2_name : generic_2_type
    );
    PORT (
        port_1_name : port_1_dir port_1_type;
        port_2_name : port_2_dir port_2_type
    );
END entity_name;
```

```
ARCHITECTURE architecture_name OF other_entity_name IS

    -- component declaration
    COMPONENT component_name IS
        GENERIC (
            generic_1_name : generic_1_type;
            generic_2_name : generic_2_type
        );
        PORT (
            port_1_name : port_1_dir port_1_type;
            port_2_name : port_2_dir port_2_type
        );
    END COMPONENT;

BEGIN
    -- VHDL statements
END architecture_name;
```

# Instantiating Components in VHDL (2/2)

- Declared **components can be instantiated in the architecture body**
- **Instantiation(s)**
  - defines the **instance name**
  - **connects ports** of an instance of the components **to signals**
  - **Defines the generics** (parameters) based on expressions that can be evaluated at compile-time

```
ARCHITECTURE architecture_name OF other_entity_name IS
    -- signal declarations
    SIGNAL port_1_1_signal, port_2_1_signal : port_1_type;
    SIGNAL port_1_2_signal, port_2_2_signal : port_2_type;
    -- component declaration
    COMPONENT component_name IS
        GENERIC ( ... );
        PORT ( ... );
    END COMPONENT;
BEGIN
    -- Component instantiation
    instance_1_name : component_name
        GENERIC MAP (
            generic_1_name => CONSTANT_EXP_1_1,
            generic_2_name => CONSTANT_EXP_1_2
        )
        PORT MAP (
            port_1_name => port_1_1_signal,
            port_2_name => port_1_2_signal
        );
    instance_2_name : component_name
        GENERIC MAP ( CONSTANT_EXP_2_1, CONSTANT_EXP_2_2
    )
        PORT MAP ( port_2_1_signal, port_2_2_signal );
END architecture_name;
```

# Array Types

- To describe **hardware** we often need **BUSSES** (groups of signals or constants)
- **Arrays are** defined by declaring a **custom type**
- **Custom types are declared in the architecture preamble**
  - Elements from left-to-right can be counted “**from-low-to-high**” or “**from-high-downto-low**”
  - **Array types**, once declared, can again serve as basis for new arrays to build 2+D arrays

```
ARCHITECTURE architecture_name OF other_entity_name IS
  -- type declarations
  TYPE array_type_name_1_1D IS ARRAY (low TO high) of base_type;
  TYPE array_type_name_2_1D IS ARRAY (high DOWNTO low) of base_type;
  TYPE array_type_name_3_2D IS ARRAY (INTEGER RANGE <>) of array_type_name_2;

  -- signal declaration
  SIGNAL signal_1_name : array_type_name_1;
  SIGNAL signal_2_name : array_type_name_3(low TO high);
BEGIN
  -- VHDL statements
END architecture_name;
```

Counting high-to-low

Range defined here

- **Array size declaration can be deferred until type is used**

# STD\_LOGIC\_VECTOR with DOWNTO Index

- **STD\_LOGIC\_VECTOR**: heavily used in hardware modelling
  - Array type that comes with STD\_LOGIC type
  - **Defined in IEEE.STD\_LOGIC\_1164 package**
- **STD\_LOGIC\_VECTORS** for binary numbers are **typically declared “from-high-downto-low”**

- Correlates better to the established weighted number representation
  - MSB on the left (low index)
  - LSB on the right (high index)

“0 1 0 0 0” = 8’dec

Bit idx. 4 3 2 1 0  
(4 downto 0)

- **Ideally, use only DOWNTO**

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.all;

ENTITY entity_name IS
    ...
END entity_name;

ARCHITECTURE architecture_name OF other_entity_name IS
    -- signal declaration
    SIGNAL signal_bus_name : STD_LOGIC_VECTOR(low TO high);
    SIGNAL bin_signal_name : STD_LOGIC_VECTOR(high DOWNTO low);
BEGIN
    -- VHDL statements
END architecture_name;
```

# Operations on Array Types

- **Accessing from** and **assigning to** array elements or ranges

```
target_array_object(index) <= base_type_object
```

```
target_base_type_object <= target_base_type_array(index)
```

```
target_array_object(index_range) <= from_array_object(index_range)
```

```
index_range = low TO high | high DOWNTO low
```

- **Assigning array aggregates** (collections of elements) to an array

- Multiple options exist to “fill” an array (assign multiple elements together)

```
target_array_object <= (value_1, value_2, ...);
```

```
target_array_object <= (idx_1=>value_1, idx_2=>value_2, ...);
```

```
target_array_object <= (idx_1=>value_1, idx_2|idx_3=>value_2, ...);
```

# Operations on Array Types

- **Filling an array:** **OTHERS** refers to all still unassigned elements in the aggregator

```
target_array_object <= (idx_1=>value_1, OTHERS=>value_2); -- fill all remaining
target_array_object <= (OTHERS=>value_1);                -- fill all elements
```
- **Assignments to arrays with character elements**
  - **Array literal values** can be placed **in double quotes**

```
target_array_object(index_range) <= “...” -- e.g., “0100-1”
```
  - **STD\_LOGIC\_VECTOR** is based on STD\_LOGIC which is a character type, i.e., ‘0’, ‘1’, ‘X’, ‘-’, ...

```
target_array_object(index_range) <= “010-10-”
```
- **Concatenation of arrays and array elements**

```
target_array_object(index_range) <= base_type_object_1 & base_type_object_1
```

# Example Operations on STD\_LOGIC\_VECTOR

- Signal declarations of STD\_LOGIC\_VECTOR

```
-- signal declaration of std_logic_vectors  
SIGNAL AxD, BxD, CxD, DxD, ExD : STD_LOGIC_VECTOR(8-1 DOWNT0 0);  
SIGNAL QxS : STD_LOGIC;
```

- Assignments

```
QxS <= '1';  
AxD <= "10010101";  
BxD <= "-0-001-1";  
CxD <= (OTHERS => '0');
```

- Concatenation and indexing

```
BxD <= AxD(7-1 downto 0) & '0';           -- SHIFT LEFT  
CxD <= '0' & AxD(8-1 downto 1);          -- SHIFT RIGHT  
DxD <= AxD(7-1 downto 0) & AxD(8-1);    -- ROTATE LEFT  
ExD <= QxS & QxS & '1' & "00001";
```

# Types for Arithmetic: UNSIGNED/SIGNED

- Built-in type **INTEGER** supports basic arithmetic operations, **BUT** the integer type is not sufficiently generic for optimized hardware
  - INTEGER type has a fixed width of 32 bit (often too large or sometimes too small)
  - INTEGER represents only signed numbers having half the range
  - Any overflow or underflow will trigger an ERROR in the simulation rather than a wrap-around
- **Need for a more flexible type** with variable length for signed and unsigned
- **IEEE numeric\_std** package: define integer as array of std\_logic
- **Two new data types: UNSIGNED, SIGNED**
- The array interpreted as an unsigned or signed binary numbers
  - **UNSIGNED** are represented as standard binary
  - **SIGNED** vectors are represented using two's complement
  - Array elements can be accessed and assigned as in a std\_logic\_vector

# UNSIGNED/SIGNED Data Types (Best practice)

- SIGNED and UNSIGNED data types represent numbers. Therefore
  - Corresponding **signals** best **carry the suffix xD** to indicate the numeric type of data

**<Signal Name>xD**

MyInputAxDI, MySIGNALxD, AccuREGxDN, AccuREGxDP

- SIGNED and UNSIGNED use weighted binary digits, counted from right to left
  - **Use DOWNT0** bit order to place the LSB (bit-0) on the right and the MSB (bin-N) on the left

**SIGNAL <Signal Name>xD : UNSIGNED(8-1 DOWNT0 0);**

**SIGNAL ExSIGNALxD : SIGNED(8-1 DOWNT0 0);**

- When declaring a signal, it is often useful to immediately see the number of bits
  - Since bits are counted from zero (0), it is often more clear to write

**SIGNAL <Signal Name>xD : UNSIGNED(#BITS-1 DOWNT0 0);**

# Arithmetic Operations on SIGNED and UNSIGNED

- **IEEE numeric\_std** defines many **common operators**

overloaded operator	description	data type of operand a	data type of operand b	data type of result
<code>abs a</code> <code>- a</code>	absolute value negation	signed		signed
<code>a * b</code> <code>a / b</code> <code>a mod b</code> <code>a rem b</code>	arithmetic operation	unsigned unsigned, natural signed	unsigned, natural unsigned signed, integer	unsigned unsigned signed
<code>a + b</code> <code>a - b</code>		signed, integer	signed	signed
<code>a = b</code> <code>a /= b</code> <code>a &lt; b</code> <code>a &lt;= b</code> <code>a &gt; b</code> <code>a &gt;= b</code>	relational operation	unsigned unsigned, natural signed signed, integer	unsigned, natural unsigned signed, integer signed	boolean boolean boolean boolean

# Arithmetic Operations on SIGNED and UNSIGNED

- **IEEE numeric\_std** defines many common operators and **type conversions**

function	description	data type of operand a	data type of operand b	data type of result
shift_left(a,b)	shift left	unsigned, signed	natural	same as a
shift_right(a,b)	shift right			
rotate_left(a,b)	rotate left			
rotate_right(a,b)	rotate right			
resize(a,b)	resize array	unsigned, signed	natural	same as a
std_match(a,b)	compare '-'	unsigned, signed std_logic_vector, std_logic	same as a	boolean
to_integer(a)	data type	unsigned, signed		integer
to_unsigned(a,b)	conversion	natural	natural	unsigned
to_signed(a,b)		integer	natural	signed

# Type Conversions to/from SIGNED and UNSIGNED

- STD\_LOGIC\_VECTOR, UNSIGNED, and SIGNED are defined as arrays of std\_logic
- **However**, they are **considered as different types**

- **Type conversion functions needed** between these types
  - Second “length” argument required for source types without explicit length (INTEGER)
- **Type conversion requires NO hardware resources**

From	To	Cast/Function
std_logic_vector	unsigned	unsigned(std_logic_vector)
std_logic_vector	signed	signed(std_logic_vector)
unsigned	std_logic_vector	std_logic_vector(unsigned)
unsigned	signed	singed(unsigned)
signed	std_logic_vector	std_logic_vector(signed)
signed	unsigned	unsigned(signed)
unsigned	integer	to_integer(unsigned)
signed	integer	to_integer(signed)
integer	unsigned	to_unsigned(integer, no_of_bits)
integer	signed	to_signed(integer, no_of_bits)

# Arithmetic Operations Example

- Basic Arithmetic Operations: ENTITY ports are std\_logic\_vector

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.all;


ENTITY adder IS
    PORT (AxDI,BxDI          : IN  std_logic_vector(8-1 downto 0);
          CxD0              : OUT std_logic_vector(8-1 downto 0));
END adder;

ARCHITECTURE rtl OF adder IS
    -- signal declaration
    SIGNAL SgnAxD, SgnBxD, SgnCxD : signed(8-1 DOWNT0 0);
BEGIN
    -- Type conversion
    SgnAxD <= signed(AxDI);
    SgnBxD <= signed(BxDI);
    -- Arithmetic
    SgnCxD <= SgnAxD + SgnBxD;
    -- Convert back to std_logic_vector for output port
    CxD0 <= std_logic_vector(SgnCxD);
END rtl;
```

No  
hardware  
resources
 
# The Problem of Describing Logic Efficiently

- **Combinational** logic is the work-horse of any digital circuit as it **performs the data manipulation** (algorithm/operations)
- **Truth/look-up tables are the most generic way to describe Boolean logic, but also the most tedious one:** difficult to formulate and to read/interpret
- Some more efficient means exist to describe specific types of logic:
  - Sometimes operations are naturally described in Boolean equations, but these quickly become difficult to create or understand
  - Arithmetic operations describe a frequently used specific subset of operations and we know how to map these to Boolean logic (from many early research works)



Truth Table

Inputs			Outputs	
A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


**Need an efficient way to describe Boolean logic**

# The Problem of Describing Logic Efficiently

- **Combinational** logic is the work-horse of any digital circuit as it **performs the data manipulation** (algorithm/operations)
- **Truth/look-up tables (LUTs) are the most generic way to describe Boolean logic**
  - **Any** fully arbitrary **logic function** can always **be described by a truth/look-up table**
  - Inputs are the index into the LUT
  - LUT can have one or multiple outputs
- **Synthesis turns LUTs into Boolean functions (netlist of logic gates) that implement the corresponding logic**

*Truth Table*

Inputs			Outputs	
A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

# LUT Realization of a Boolean Function (Logic)


- **Full adder** with three-inputs and two outputs, **realized as two LUTs**
  - **1-D LUTs defined as array constants** (`std_logic_vector`)
  - **LUT input used as index into the LUT**
    - Concatenate multiple inputs to a vector and convert to an integer-type to index into the LUT

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.all;

ENTITY FullAdder IS
    PORT (AxDI,BxDI, CINxDI      : IN  std_logic;
          SxSO, COUTxD0         : OUT std_logic);
END FullAdder;

ARCHITECTURE rtl OF FullAdder IS
    CONSTANT S      : std_logic_vector(0 to 7) := "01101001";
    CONSTANT COUT   : std_logic_vector(0 to 7) := "00010111";
BEGIN
    SxDO    <= S(to_integer(AxDI & BxDI & CINxDI));
    COUTxD0 <= COUT(to_integer(AxDI & BxDI & CINxDI));
END rtl;
```

Inputs			Outputs	
A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

# The Problem of Describing Logic Efficiently

- Some more efficient means exist to describe specific types of logic:
  - Sometimes operations are naturally described in Boolean equations
  - Arithmetic operations describe a frequently used specific subset of operations and we know how to map these to Boolean logic (from many early research works)
- However, **in most cases, LUTs are difficult to formulate and to read or interpret**

**Need an efficient way to describe Boolean logic**

# Efficiently Describing Logic as Decision Trees

- Need a more systematic way to define a Boolean function based on “operational requirements”
- Completely **arbitrary functions are rare** in practice
  - Some inputs or combinations of some inputs render the output independent of all other inputs
  - In Karnaugh maps, we refer to this as “combining minterms”
- Such truth tables can be expressed efficiently and interpreted as decision diagrams
  - Interpretation as decision trees
  - Formulation based on if-then-elsif-elsif-...-else


	00	01	11	10
00	1	0	0	1
01	0	0	1	0
11	0	0	0	0
10	0	0	0	0

# Designing Logic “with/as Multiplexers” (1/2)

- Besides boolean and arithmetic operations, the **CONDITIONAL ASSIGNMENT** is a fundamental building block for HDL-based hardware design
- The **simplest conditional assignment** corresponds to a **2-input MUX**
  - natural way to combine 2 pieces of logic into one
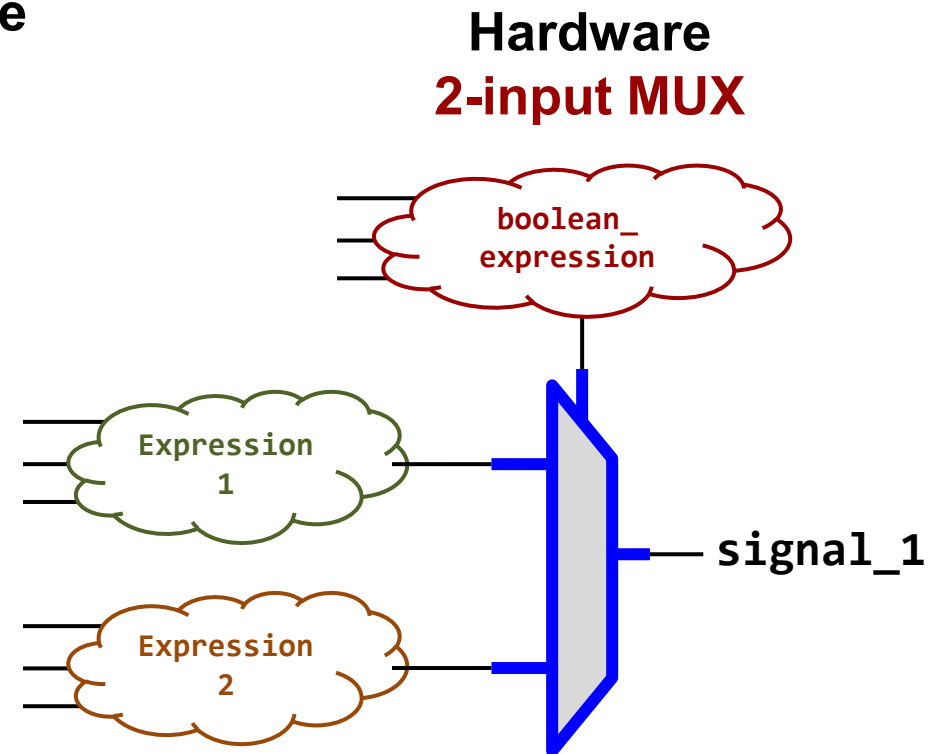
## HDL Pseudo-Code Conditional Assignment

```
If boolean_expression then  
    signal_1 <= expression_1  
Else  
    signal_1 <= expression_2  
End
```



# Designing Logic “with/as Multiplexers” (2/2)

- How to describe the **combination of multiple expressions?**

- **Nested IF statements:** VHDL version described later


HDL Pseudo-Code

```
If boolean_expression_1 then
    signal_1 <= expression_1
Else
    If boolean_expression_2 then
        signal_1 <= expression_2
    Else
        signal_1 <= expression_3
    End
End
```

End → Nesting level

- **Nesting level**

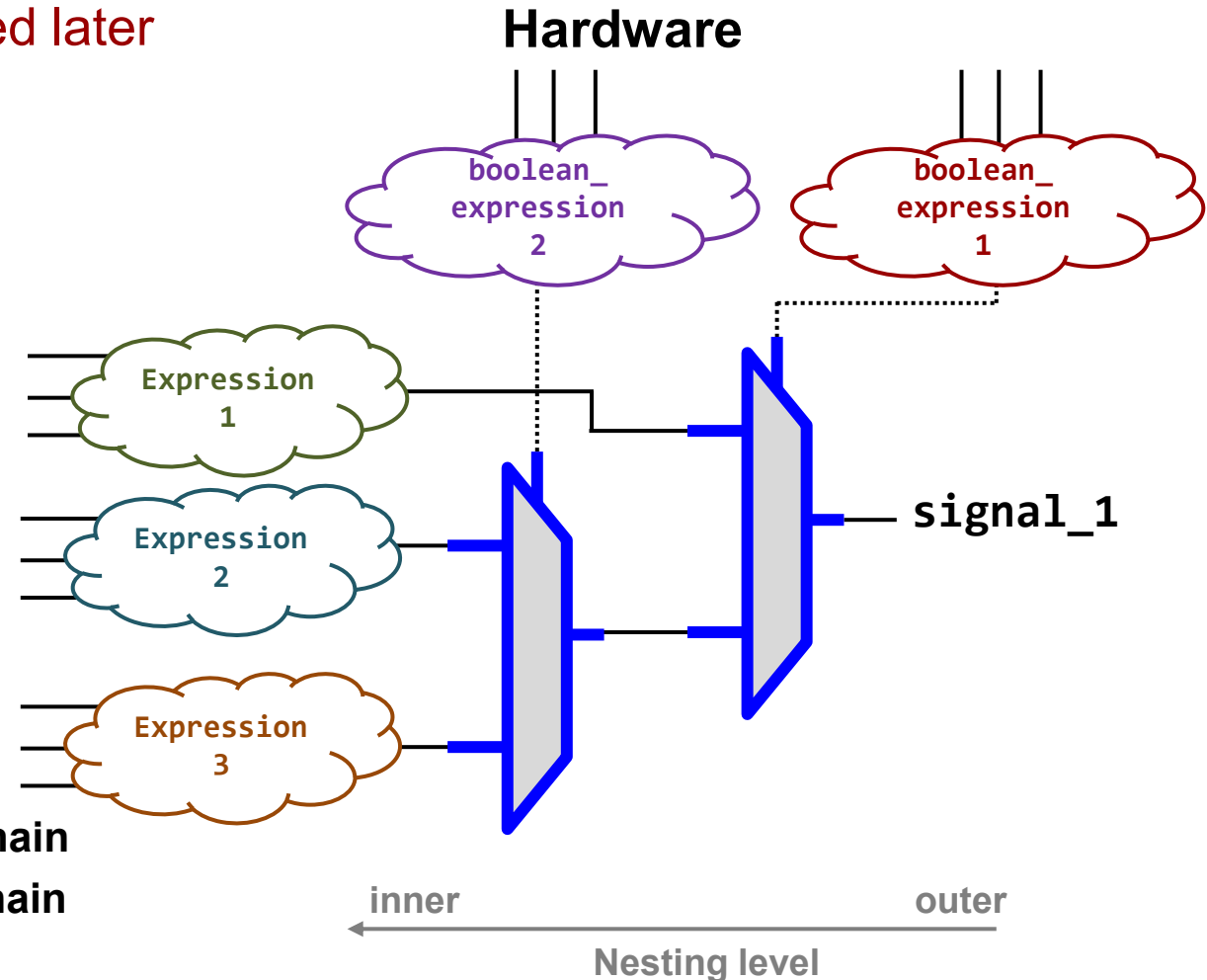- **encodes priority in the HDL description**
- **defines the level of the MUX in the HW**
  - Outer-most IF corresponds to last MUX in the chain
  - Inner-most IF corresponds to first MUX in the chain



# Designing Logic “with/as Multiplexers” (2/2)


- How to describe the **combination of multiple expressions?**

- Combined IF, ELSIF, ELSIF, ... , ELSE statements:

HDL Pseudo-Code

```
If boolean_expression_1 then
    signal_1 <= expression_1
Elsif boolean_expression_2 then
    signal_1 <= expression_2
Else
    signal_1 <= expression_3
End
```

Order

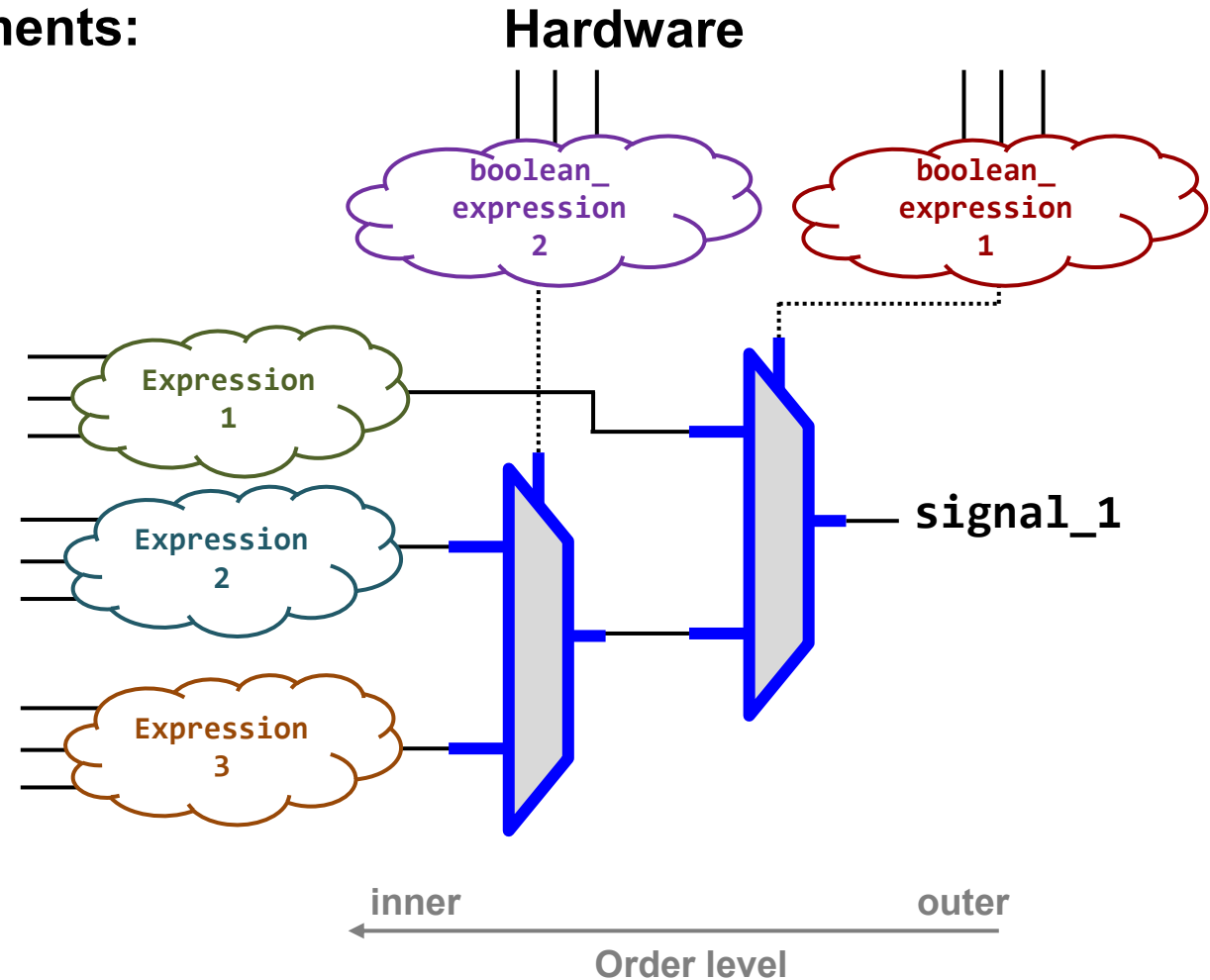

- **Order**

- **encodes priority in the HDL description**
- **defines the level of the MUX in the HW**
  - First IF corresponds to last MUX in the chain
  - Last IF corresponds to first MUX in the chain

# Conditional Assignments (MUXes) in VHDL (1/2)


- Due to their importance and power to describe logic in an intuitive manner, **VHDL provides many options for conditional assignments**

- **WHEN-ELSE** statement for multiple different binary conditions (IF, ELSIF, ELSIF, ... ELSE)

```
target_signal <= expression_1 WHEN boolean_expression_1 ELSE  
                expression_2 WHEN boolean_expression_2 ELSE  
                ...  
                expression_N;  
                ELSE
```

Order=  
Priority

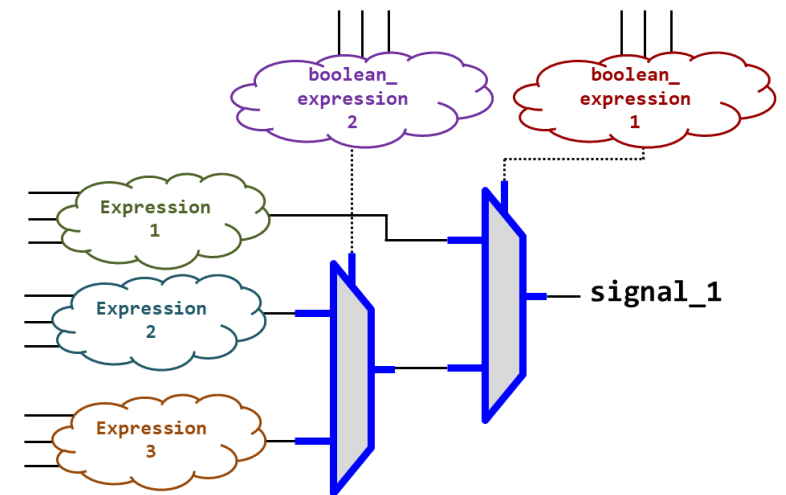- **Multiple conditions may be true at the same time**
  - **Order encodes the priority:** only first one is relevant
- **Note:** often `expression_x` is simply a *signal*



# Conditional Assignments (MUXes) in VHDL (2/2)


- Due to their importance and power to describe logic in an intuitive manner, **VHDL provides many options for conditional assignments**

- **WITH-SELECT** statement for a single multi-valued (non-binary) condition

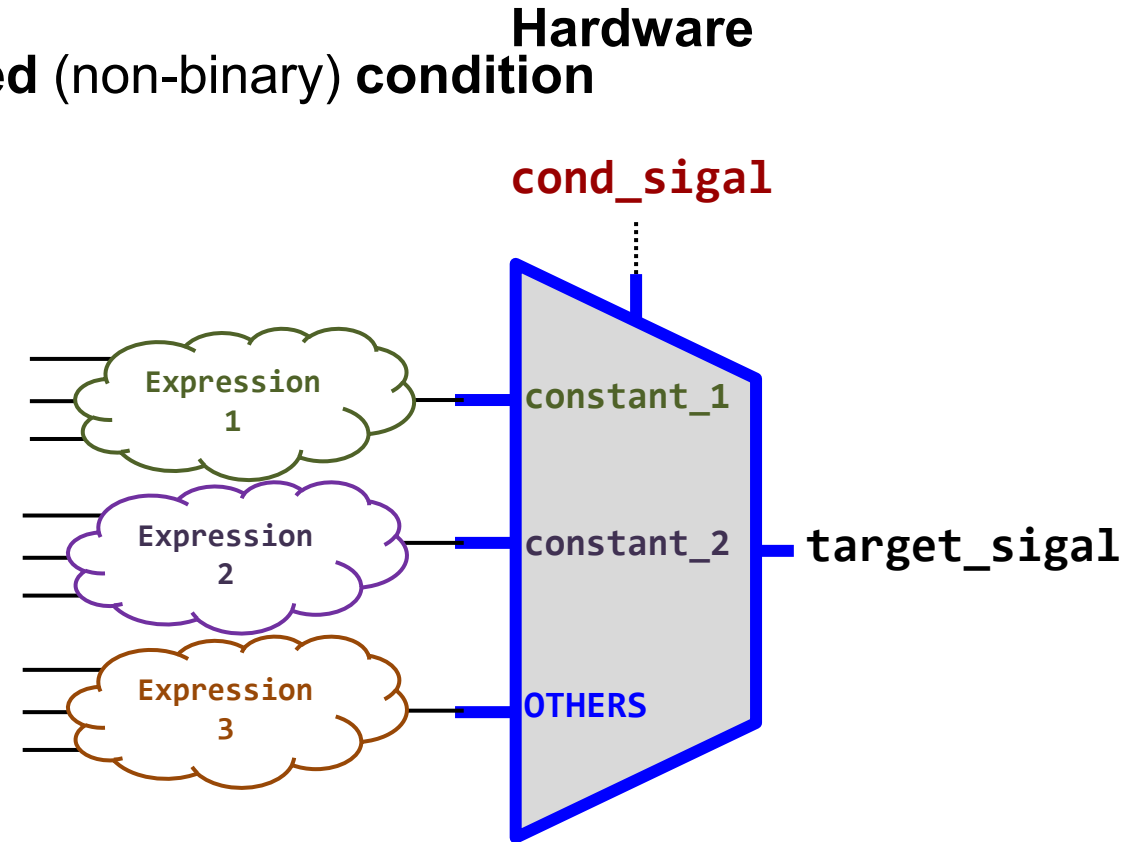**WITH** `cond_signal` **SELECT**

```
target_signal <=  
expression_1 WHEN constant_1,  
expression_2 WHEN constant_2,  
...  
expression_N WHEN OTHERS;  
                ELSE
```

- **Only one condition is true at the same time**
- **Note:** often `expression_x` is simply a *signal*




# An Important Remark on Conditional Assignments

- Consider the pseudo-code below, which is common practice in Software

```
If boolean_expression_1 then
    signal_1 <= expression_1
Elsif boolean_expression_2 then
    signal_1 <= expression_2
End
```

- NOTE: If none of the conditions is met, no assignment is made to signal\_1**

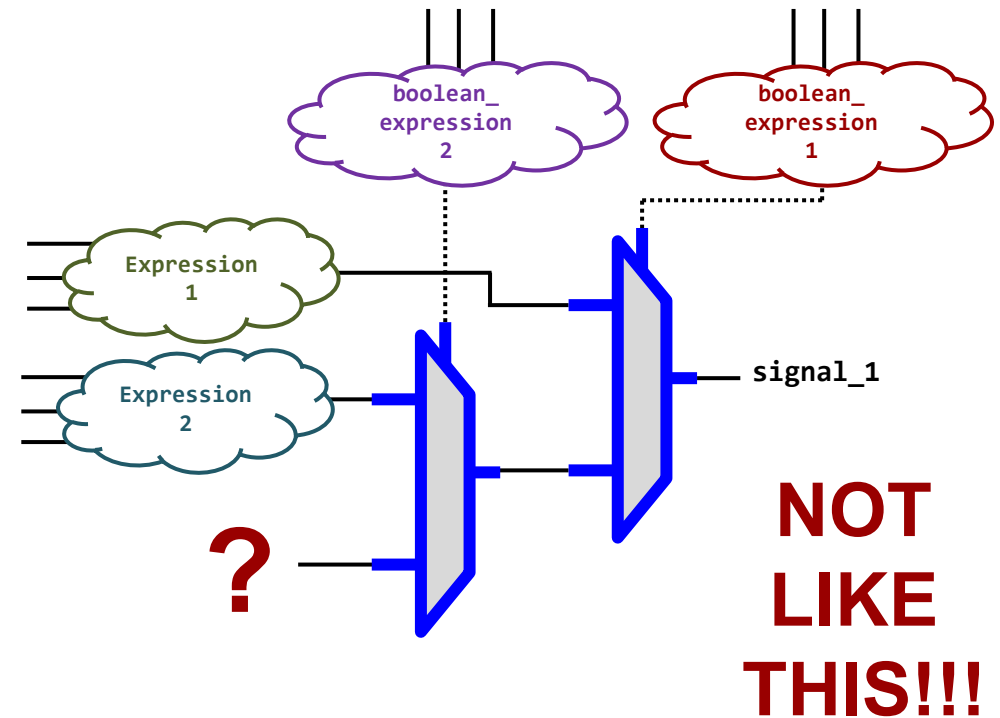- HOWEVER, a **physical wire can never be “not assigned”** any value at all




# An Important Remark on Conditional Assignments

- Consider the pseudo-code below, which is common practice in Software

```
If boolean_expression_1 then
    signal_1 <= expression_1
Elsif boolean_expression_2 then
    signal_1 <= expression_2
End
```

- NOTE: If none of the conditions is met, no assignment is made to signal\_1**

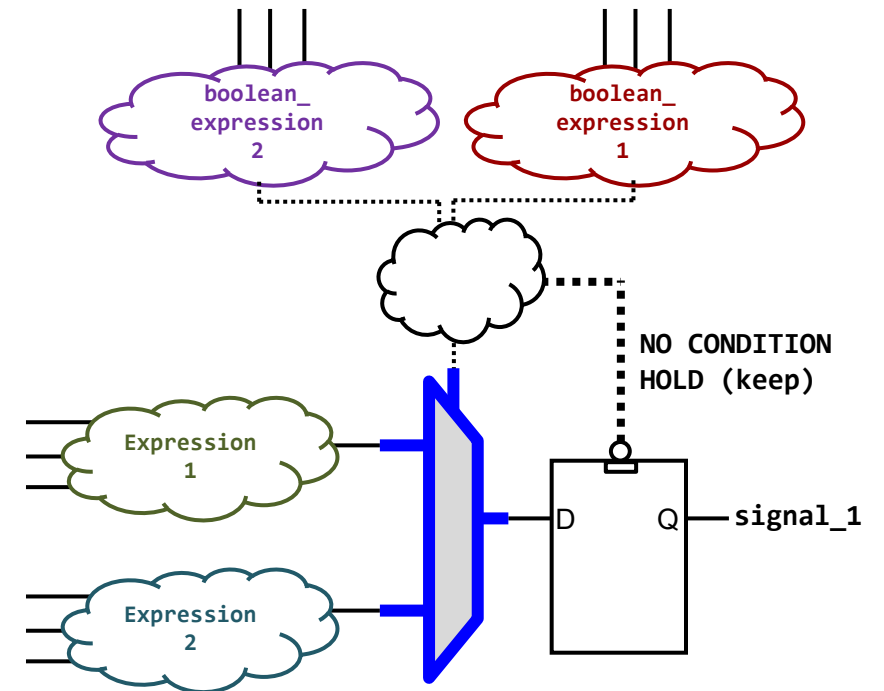- HOWEVER, a **physical wire can never be “not assigned”** any value at all
- In VHDL, **signals preserve their state if no value is assigned**
  - Works perfectly in simulation, BUT
    - Is often not the desired behaviour
    - Is NOT COMPATIBLE with the rules of synchronous design => issues later in the design**



**RULE: every combinational conditional assignment must be complete**

# Example: A Simple ALU

- **Specification:** 8-bit ALU
  - Three operations: +, -, AND
  - Specified by CMDxSI (2-bit command)
  - For CMDxDI="11", the output DOES NOT MATTER

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.all
ENTITY my_first_counter IS
  PORT (
    AxDI    : IN  std_logic_vector(8-1 DOWNT0 0);
    BxDI    : IN  std_logic_vector(8-1 DOWNT0 0);
    CMDxSI  : IN  std_logic_vector(2-1 DOWNT0 0);

    CxDO    : OUT std_logic_vector(8-1 DOWNT0 0)
  );
END my_first_counter;
...
```


```
...
ARCHITECTURE rtl OF my_first_counter IS
  -- signal declaration
  SIGNAL SgnCxD      : SIGNED(8-1 DOWNT0 0);

BEGIN

  WITH CMDxSI SELECT
    SgnCxD <=
      SIGNED(AxDI) + SIGNED(BxDI) WHEN "00",
      SIGNED(AxDI) - SIGNED(BxDI) WHEN "01",
      SIGNED(AxDI AND BxDI)      WHEN "10",
      "-----" WHEN OTHERS;

  -- Output assignment with type conversion
  CxDO <= std_logic_vector(SgnCxD);

END rtl;
```

 

# How to Implement Registers in a Clean Way?


- **Synchronous designs requires the notion of a state**
  - In VHDL, signals preserve their state (have a state) when nothing is assigned to them
  - This **preservation of states can be exploited to describe registers, but it must be done with care**
- **Objective: stick to the rules of synchronous design**
  - **ONLY the clock triggers a state transition**
  - **Use ONLY positive edge triggered FlipFLops (no latches)**
  - **→ Incomplete combinational conditional assignments are not the solution to create registers**
- **Clean solution:**

**Describe registers EXPLICITLY with a well controlled template**
 
# Describing Edge Triggered Registers in VHDL

- Two ingredients:
  - A conditional statement that is TRUE when an edge (transition) occurs: `clock_signal'event`
    - Positive edge: `clock_signal'event AND clock_signal = '1'`
  - A special process template that is well understood and clean

- **Assign input signal** of a FlipFlop (`next_state_signal`) to the FlipFlop output signal (`present_state_signal`)
- Conditional **assignment** is incomplete and only **triggers on rising edge of the clock**




```
ARCHITECTURE architecture_name OF other_entity_name IS
  -- signal declaration
  SIGNAL next_state_signal_1,next_state_signal_2:state_signal_type;
  SIGNAL present_state_signal_1 : state_signal_type;
  SIGNAL present_state_signal_2 : state_signal_type;
BEGIN

  -- Clocked Process, generating a FlipFlop behavior
  p_seq: PROCESS (clock_signal) IS
  BEGIN -- process name: p_seq
    IF clock_signal'EVENT AND clock_signal = '1' THEN
      present_state_signal_1 <= next_state_signal_1
        | expression;
      present_state_signal_2 <= next_state_signal_2
        | expression;
    END IF;
  END PROCESS p_seq;
END architecture_name;
```

**TWO registers**
 
# Describing Registers with Asynchronous Reset

- An **asynchronous reset** triggers also a **state transition**, independent of clock
  - The **asynchronous reset** typically **takes precedence** over the clock
    - **Asynchronous reset (async\_reset\_signal)** assigns a **constant** to the FlipFlop output signal (**present\_state\_signal**)
    - Conditional **assignment** is still incomplete and **now triggers on rising edge of the clock and on the reset signal**
    - Reset can be low- or high-active



```
ARCHITECTURE architecture_name OF other_entity_name IS
    -- signal declaration
    SIGNAL next_state_signal      : state_signal_type;
    SIGNAL present_state_signal   : state_signal_type;
BEGIN

    -- Clocked Process, generating a FlipFlop behavior
    p_seq: PROCESS (clock_signal, async_reset_signal) IS
    BEGIN -- process name: p_seq
        IF async_reset_signal = '0|1' THEN
            present_state_signal <= constant;
        ELSIF clock_signal'EVENT AND clock_signal = '1' THEN
            present_state_signal <= next_state_signal
                | expression;
        END IF;
    END PROCESS p_seq;
END architecture_name;
```

# Example: A Simple Counter (Overflowing)

- **Specification:** 8-bit counter, overflowing (wrap-around)

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.all
ENTITY my_first_counter IS
  PORT (
    CLKxCI : IN std_logic;
    RSTxRBI : IN std_logic;
    CNTxD0 : OUT std_logic_vector(8-1 DOWNT0 0)
  );
END my_first_counter;
...
```

```
...
ARCHITECTURE rtl OF my_first_counter IS
  -- signal declaration
  SIGNAL CNTxDN : UNSIGNED(8-1 DOWNT0 0);
  SIGNAL CNTxDP : UNSIGNED(8-1 DOWNT0 0);
BEGIN
  -- Counting/incrementing (Combinational Logic)
  CNTxDN <= CNTxDP + 1;

  -- Clocked Process, generating a FlipFlop behavior
  p_seq: PROCESS (CLKxCI, RSTxRBI) IS
  BEGIN -- process name: p_seq
    IF RSTxRBI = '0' THEN
      CNTxDP <= (OTHERS => '0');
    ELSIF CLKxCI'EVENT AND CLKxCI = '1' THEN
      CNTxDP <= CNTxDN;
    END IF;
  END PROCESS p_seq;

  -- Output assignment with type conversion
  CNTxD0 <= std_logic_vector(CNTxDP);
END rtl;
```