

# Fundamentals of Analog & Mixed Signal VLSI Design

## Single-ended Differential Amplifiers Part 3

Christian Enz


*Integrated Circuits Lab (ICLAB), Institute of Electrical and Micro-Engineering (IEM), School of Engineering (STI)  
Swiss Federal Institute of Technology, Lausanne (EPFL), Switzerland*

The logo of the Swiss Federal Institute of Technology (EPFL) in Lausanne, Switzerland. It consists of the letters 'EPFL' in a bold, red, sans-serif font. The 'E' is stylized with a vertical bar on its left side, and the 'F' has a vertical bar on its right side.

# Outline


- **The CMOS inverter OTA**
- Improved slew-rate OTAs
- Appendices

# The CMOS Inverter as an Amplifier

 

- The CMOS inverter can be used as a very efficient amplifier thanks to the current sharing between the nMOS and pMOS transistors
- The overall transconductance is the sum of the nMOS and pMOS transconductances
- In WI, the CMOS inverter can operate at very low-voltage thanks to the minimum saturation voltage achieved in WI
 
# The CMOS Inverter – Small-signal and Noise Analysis



- The overall OTA  $G_m$  is the sum of the nMOS and pMOS  $G_m$

$$G_m = G_{m1} + G_{m2} \cong 2G_{m1} = 2 \frac{I_b}{nU_T}$$


- which in WI is twice that of a single transistor since both transistors share the same bias current
- The DC gain is given by

$$A_{dc} = -\frac{G_m}{G_o} = -\frac{G_{m1} + G_{m2}}{G_{ds1} + G_{ds2}}$$

- and the noise is half that of a single transistor for the same bias current

$$R_n = \frac{G_{n1} + G_{n2}}{(G_{m1} + G_{m2})^2} = \frac{2 \gamma_{n1} \cdot G_{m1}}{4 G_{m1}^2} = \frac{\gamma_{n1}}{2G_{m1}} = \frac{R_{n1}}{2}$$
 
# Large-signal Transfer Characteristic in WI



- Assuming that  $n_1 = n_2 = n$  the output current  $I_{out} = I_p - I_n$  is given by

$$i_{out} \triangleq \frac{I_{out}}{I_b} = -2 \sinh\left(\frac{V_{in} - V_b}{nU_T}\right)$$



- $V_b$  and  $I_b$  correspond to the quiescent gate and bias current for  $I_{out} = 0$

$$I_b = I_{D01} \cdot e^{\frac{V_b}{nU_T}} = I_{D02} \cdot e^{\frac{V_{DD} - V_b}{nU_T}}$$

- where  $I_{D01} = I_{spec1} \cdot e^{\frac{-V_{T0n}}{nU_T}}$  and  $I_{D02} = I_{spec2} \cdot e^{\frac{-V_{T0p}}{nU_T}}$


- with  $I_{spec1} = I_{specn\Box} \cdot \frac{W_1}{L_1}$  and  $I_{spec2} = I_{specp\Box} \cdot \frac{W_2}{L_2}$

# Class AB Transfer Characteristic

  



- The current is not limited by a bias current but by the supply voltage
- The class AB transfer characteristic is shown above for the case  $V_b = V_{DD}/2$
- The use of inverters was proposed by Krummenacher already in 1981 for designing micropower SC filters
 
# Large-signal Transfer Characteristic in WI



- Assuming  $n_1 = n_2 = n$ ,  $I_{D01} = I_{D02}$  and neglecting SCE (DIBL and CLM)
- Can operate at very low supply voltage still providing some voltage gain

# Voltage Gain

 
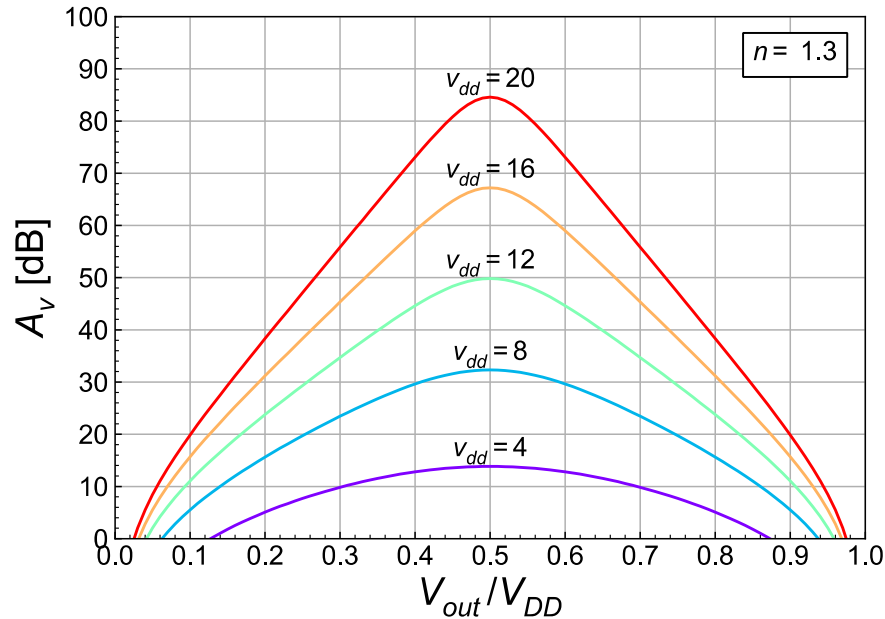


- Large DC gain can be obtained at very low-voltage, provided
  - ▶ low, controlled threshold voltages are available
  - ▶ adequate bias scheme is implemented
- Of course the large voltage gain shown above can be significantly lower because of SCE such as DIBL

# The CMOS Inverter in Weak Inversion

- The CMOS inverter has many great features particularly when it is biased in WI, including:
  - ▶ Maximum transconductance at given current  $I_b$   
(global  $G_m$  is doubled for the same bias current since in WI  $G_m \propto I_b$ )
  - ▶ Maximum DC gain
  - ▶ Minimum input-referred white noise at given current  $I_b$
  - ▶ Intrinsically class AB
  - ▶ Very low-voltage operation
- However it suffers from a major drawback, namely
  - ▶ Poor intrinsic PSRR (6 dB)!
- The later can be circumvented by adding a voltage regulator
- In SI and saturation, for long-channel transistors with for  $\beta_1/n_1 = \beta_2/n_2$ , the OTA operates as a linear transconductor

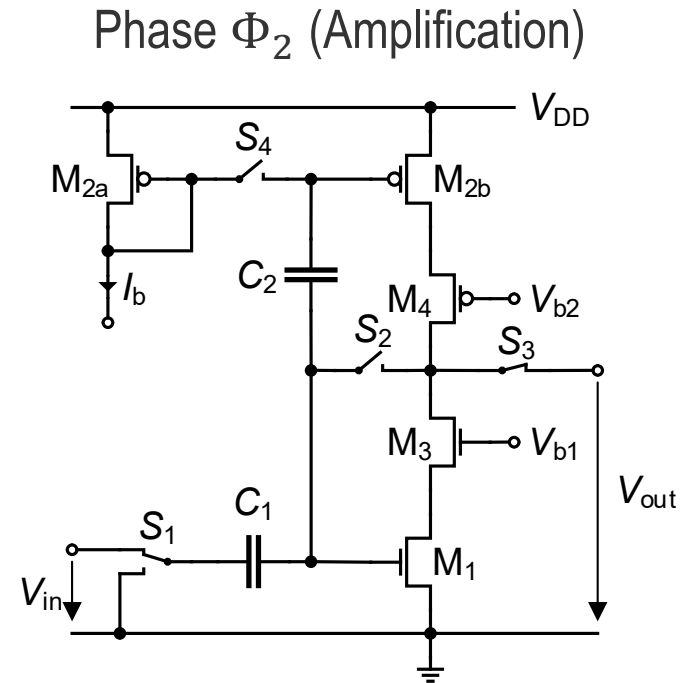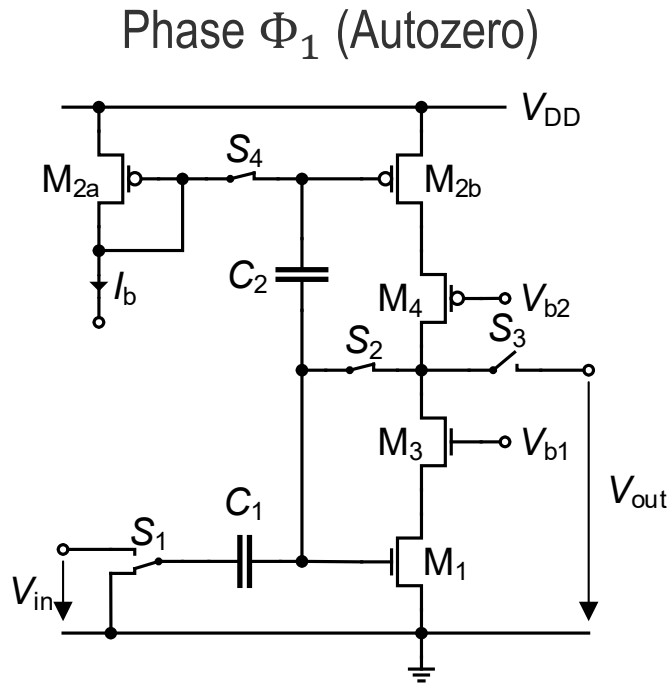
# Dynamically Biased Inverter Amplifier (1/2)



- Two non-overlapping phases operation
- During phase  $\Phi_1$ , the amplifier is disconnected from the input and the bias current is imposed in the inverter
- At the end of phase  $\Phi_1$ , the bias voltages are sampled on  $C_1$  and  $C_2$  ideally maintaining the bias current  $I_b$  in the inverter during the amplification phase  $\Phi_2$


 
# Differential Dynamically Biased Inverter Amplifier




- The above circuit provides a differential input
- In most SC circuits, the positive input is set to a certain common-mode voltage
- The above circuit samples the bias voltage during phase  $\Phi_1$  referenced to the common-mode voltage imposed on the positive input
- The bias voltage sampled on  $C_1$  and  $C_2$  are then applied to  $M_1$  and  $M_{2b}$  during the amplification phase  $\Phi_2$



# Outline

- The CMOS inverter OTA
- **Improved slew-rate OTAs**
- Appendices
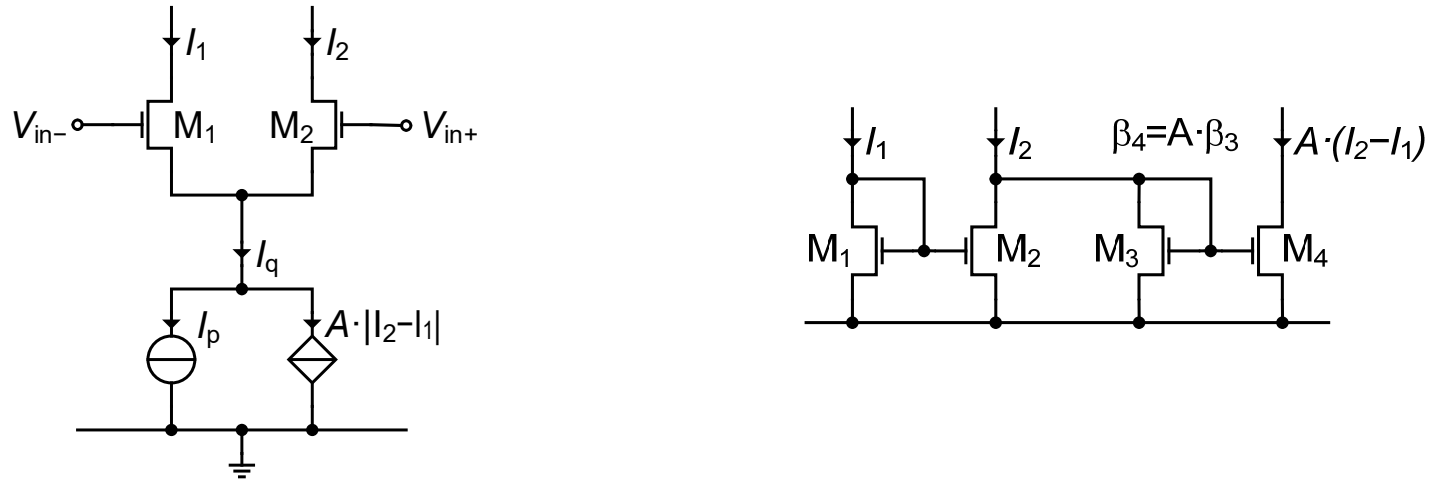
# Differential Feedback Amplifier – Principle



- **Settling time** of simple OTAs having their input differential pair biased in WI is set by the **slew-rate**
- Limited slew rate due to small currents can be circumvented by using **adaptive biasing**
- Principle: increase the differential pair bias current for large differential input signals

$$I_q = I_p + A \cdot |I_2 - I_1| \text{ with } I_q = I_1 + I_2$$

# Differential Feedback Amplifier – Output Current

- It can be shown that currents  $I_1$  and  $I_2$  depend on  $V_{in} \triangleq V_{in+} - V_{in-}$  according to

$$i_1 \triangleq \frac{I_1}{I_p} = \frac{1}{1+A+(1-A)e^{v_{in}}} \text{ and } i_2 \triangleq \frac{I_2}{I_p} = \frac{e^{v_{in}}}{1+A+(1-A)e^{v_{in}}} \text{ with } v_{in} \triangleq \frac{V_{in}}{nU_T}$$

- Resulting in the output current  $I_{out} = I_2 - I_1$  given by

$$i_{out} \triangleq \frac{I_{out}}{I_p} = i_2 - i_1 = \frac{\tanh\left(\frac{v_{in}}{2}\right)}{1 - A \tanh\left(\frac{v_{in}}{2}\right)}$$

- In the particular case where there is no feedback ( $A = 0$ ) we recover the differential pair transfer characteristic

$$i_{out} = \tanh\left(\frac{v_{in}}{2}\right)$$

- For  $0 < A < 1$ , the output current is limited to  $I_p/(1 - A)$
- For  $A \geq 1$ , the output current is no longer limited to the bias current  $I_p$
- The output current tends to infinity for a critical value of the input voltage given by

$$V_{in,crit} = nU_T \cdot \ln\left(\frac{A + 1}{A - 1}\right)$$



- For  $A = 1$ , one of the two branches remains at  $I_p/2$  i.e.  $\min(I_1, I_2) = \frac{I_p}{2}$  and the output current becomes

$$i_{out} = \frac{1}{2}(e^{v_{in}} - 1)$$


# Differential Feedback Amplifier – Output Current

$$I_{out} = I_2 - I_1$$

$$V_{in} = V_{in+} - V_{in-}$$

  
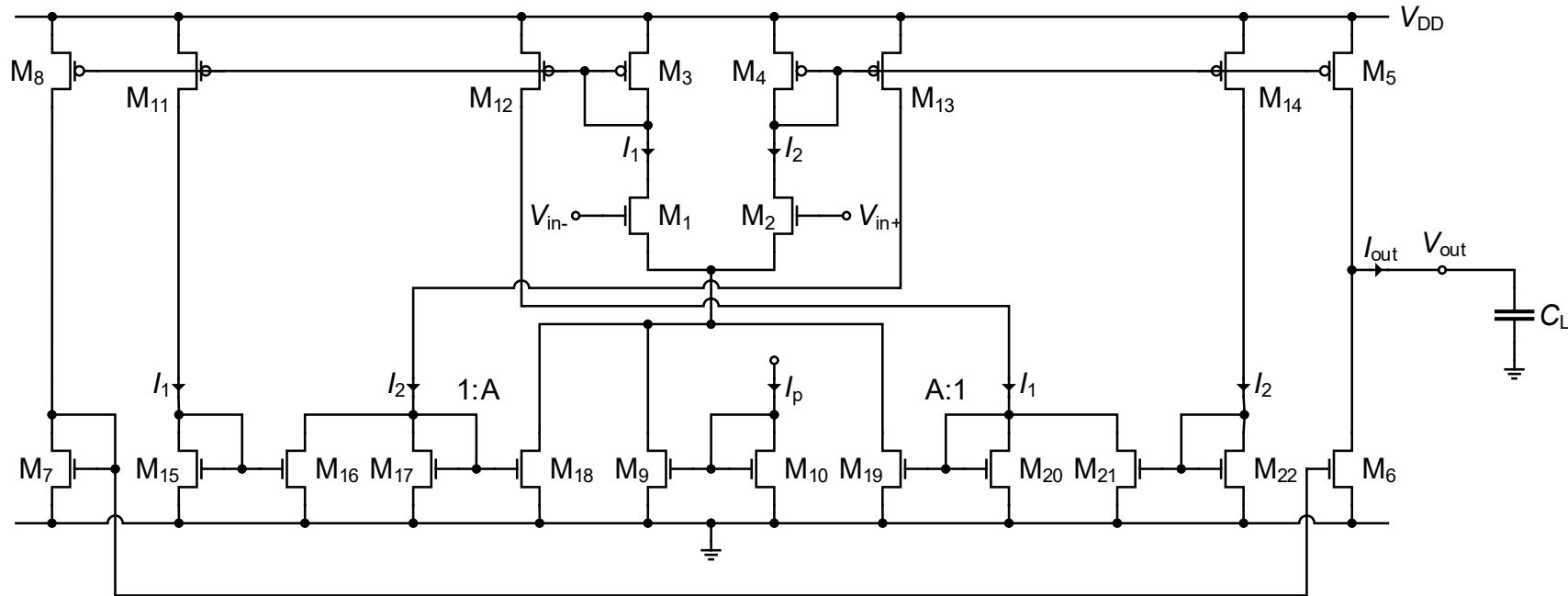
# Differential Feedback Amplifier – Differential OTA



- Transistors  $M_1$  to  $M_{10}$  implement the symmetrical OTA, whereas transistors  $M_{11}$  to  $M_{22}$  implement the two feedback networks

# Differential Feedback Amplifier – Experimental Validation

 


Fig. 8. Measured output current for  $I_p = 0$ .


 


Fig. 9. Supply current as a function of the input signal.

# Direct Feedback Amplifier – Principle

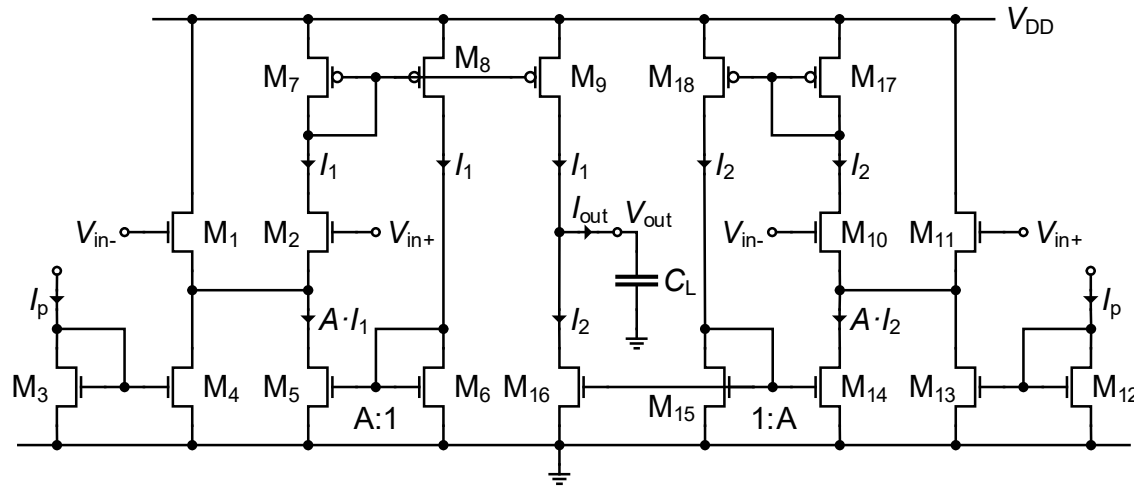

- When the differential input voltage  $V_{in} = V_{in+} - V_{in-}$  equals zero, the quiescent currents  $I_1$  and  $I_2$  are equal and given by

$$I_{1(2)} = \frac{1}{2} \cdot (I_p + A \cdot I_{1(2)})$$

- Which can be solved for  $I_1$  and  $I_2$  resulting in

$$I_1 = I_2 = I_0 = \frac{I_p}{2 - A}$$

- Stability is then insured for a current gain  $A < 2$

## Direct Feedback Amplifier – Output Current

- It can be shown that currents  $I_1$  and  $I_2$  depend on  $V_{in}$  according to

$$i_1 \triangleq \frac{I_1}{I_p} = \frac{1}{1-A+e^{-v_{in}}} \text{ and } i_2 \triangleq \frac{I_2}{I_p} = \frac{1}{1-A+e^{+v_{in}}} \text{ with } v_{in} \triangleq \frac{V_{in}}{nU_T}$$

- Resulting in the output current  $I_{out} = I_1 - I_2$  is given by

$$i_{out} \triangleq \frac{I_{out}}{I_p} = i_1 - i_2 = \frac{2 \sinh(v_{in})}{1 + (1 - A)^2 + 2(1 - A) \cosh(v_{in})}$$

- In the particular case where there is no feedback ( $A = 0$ ) we recover the differential pair transfer characteristic


$$i_{out} = \tanh\left(\frac{v_{in}}{2}\right)$$

- For  $A < 1$ , the output current is limited to  $I_p/(1 - A)$
- For  $A = 1$ , the currents become exponential and the output current is no more limited and becomes

$$i_{out} = 2 \sinh(v_{in})$$

- For  $A > 1$ , the current tends to infinity for  $v_{in} = \cosh^{-1}\left(\frac{A^2 - 2A + 2}{2(A - 1)}\right)$
 
# Direct Feedback Amplifier – Output Current



- As shown in the next slide, the output current will be limited by the maximum current that can be provided by the supply

# Direct Feedback Amplifier – Experimental Validation

$$A = 1.4$$

