

# **Fundamentals of Analog VLSI Design**

## **Exercise 3 - Solution**

**Design and Optimization of the Common-source Gain Stage**

Christian Enz (christian.enz@epfl.ch)

01.10.2025

# Table of contents

<b>Introduction</b>	<b>3</b>
<b>1 Problem 1: Imposing the gain-bandwidth product (unity gain frequency)</b>	<b>5</b>
1.1 Analysis . . . . .	5
1.2 Specifications . . . . .	5
1.3 Long-channel case . . . . .	6
1.3.1 Design . . . . .	6
1.3.2 Simulations . . . . .	6
1.4 Short-channel case (including velocity saturation) . . . . .	9
1.4.1 Design . . . . .	9
1.4.2 Simulations . . . . .	10
<b>2 Problem 2: Imposing the power consumption</b>	<b>13</b>
2.1 Specifications . . . . .	13
2.2 Long-channel case . . . . .	13
2.2.1 Design . . . . .	13
2.2.2 Simulations . . . . .	13
2.3 Short-channel case (including velocity saturation) . . . . .	14
2.3.1 Design . . . . .	14
2.3.2 Simulations . . . . .	15
<b>3 Problem 3: Imposing the gain bandwidth product and the current budget</b>	<b>17</b>
3.1 Specifications . . . . .	17
3.2 Design . . . . .	17
3.3 Simulations . . . . .	17
<b>4 Problem 4: Imposing the input-referred noise</b>	<b>19</b>
4.1 Specifications . . . . .	19
4.2 Design . . . . .	19
4.3 Simulations . . . . .	20
<b>5 Problem 5: Minimum current for a given gain-bandwidth product with self-loading</b>	<b>22</b>
5.1 Specifications . . . . .	23
5.2 Design . . . . .	23
5.3 Simulations . . . . .	24
<b>6 Problem 6: Minimum current for a given DC gain and gain-bandwidth product with self-loading</b>	<b>28</b>
6.1 Specifications . . . . .	29
6.2 Design . . . . .	29
6.3 Simulations . . . . .	30
<b>7 Conclusion</b>	<b>32</b>
<b>References</b>	<b>33</b>

# Introduction

 


Figure 1: Common-source (CS) gain stage.

In this exercise we want to apply the  $G_m/I_D$  design methodology using the inversion coefficient  $IC$  to the simple common source (CS) amplifier shown in Figure 1 for various specifications. For the design we assume a generic 180 nm bulk CMOS process. The physical parameters are given in Table 1, the global process parameters in Table 2 and finally the MOSFET parameters in Table 3.

## ! Important

For this process, the transistor dimensions are rounded to 10nm.

Table 1: Physical parameters

Parameter	Value	Unit
$T$	300	$K$
$U_T$	25.875	$mV$

Table 2: Global process parameters

Parameter	Value	Unit
$V_{DD}$	1.8	$V$
$C_{ox}$	8.443	$\frac{fF}{\mu m^2}$
$H_{dif}$	200	$nm$
$W_{min}$	200	$nm$
$L_{min}$	180	$nm$

Table 3: Transistor process parameters

Parameter	NMOS	PMOS	Unit
sEKV parameters			
$n$	1.27	1.31	-
$I_{spec\Box}$	715	173	$nA$
$V_{T0}$	0.455	0.445	$V$
$L_{sat}$	26	36	$nm$
$\lambda$	15	20	$\frac{V}{\mu m}$

Table 3: Transistor process parameters

Parameter	NMOS	PMOS	Unit
Overlap capacitances parameters			
$C_{GD0}$	0.366	0.329	$\frac{fF}{\mu m}$
$C_{GS0}$	0.366	0.329	$\frac{fF}{\mu m}$
$C_{GB0}$	0	0	$\frac{fF}{\mu m}$
Junction capacitances parameters			
$C_J$	1	1.121	$\frac{fF}{\mu m^2}$
$C_{JSW}$	0.2	0.248	$\frac{fF}{\mu m}$
Flicker noise parameters			
$K_F$	8.1e-24	6.8e-23	$J$
$AF$	1	1	-
$\rho$	0.05794	0.4828	$\frac{V \cdot m^2}{A \cdot s}$
Matching parameters			
$A_{VT}$	5	5	$mV \cdot \mu m$
$A_\beta$	1	1	$\% \cdot \mu m$
Source and drain sheet resistance parameter			
$R_{sh}$	600	2386	$\frac{\Omega}{\mu m}$
Width and length parameters			
$\Delta W$	39	54	$nm$
$\Delta L$	-76	-72	$nm$

# 1 Problem 1: Imposing the gain-bandwidth product (unity gain frequency)

In this first example we will design the CS gain stage shown in Figure 1 for the specifications at room temperature given in Table 1.1 by imposing the inversion coefficient and the load capacitance.

## 1.1 Analysis

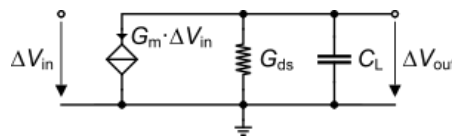


Figure 1.1: Small-signal schematic of the common-source (CS).

The small-signal schematic of the CS amplifier is shown in Figure 1.1. The transfer function is given by

$$H(s) \triangleq \frac{\Delta V_{out}}{\Delta V_{in}} = \frac{A_{dc}}{1 + \frac{s}{\omega_c}}, \quad (1.1)$$

where  $A_{dc} = -G_m/G_{ds}$  is the dc gain and  $\omega_c = G_{ds}/C_L$  the cut-off frequency.

The magnitude of the frequency response is then given by

$$|H(\omega)| = \frac{|A_{dc}|}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}} \simeq \frac{\omega_u}{\omega} \quad (1.2)$$

for  $\omega_c \ll \omega$  where

$$\omega_u = |A_{dc}| \cdot \omega_c = \frac{G_m}{C_L} \quad (1.3)$$

is the unity-gain frequency or gain-bandwidth product.

## 1.2 Specifications

The specifications for Problem 1 are given in Table 1.1.

Table 1.1: Specifications for problem 1.

Specification	Symbol	Value	Unit
Gain-bandwidth product	$GBW$	10	$MHz$
Inversion coefficient	$IC$	1	-
Load capacitance	$C_L$	1	$pF$

## 1.3 Long-channel case

### 1.3.1 Design

For the long-channel case, we take  $L = 1 \mu\text{m}$  which corresponds to an effective length  $L_{eff} = 924 \text{ nm}$ .

The gain-bandwidth product  $GBW$  and the load capacitance  $C_L$  set the required transconductance as  $G_m = 62.832 \mu\text{A}/\text{V}$ . Assuming a long-channel transistor we can neglect the effect of velocity saturation and calculate the current efficiency for the chosen inversion coefficient as  $G_m nU_T/I_D = 0.618$ , from which we get  $I_b = 3.344 \mu\text{A}$ . From the bias current and the inversion coefficient we get the specific current as  $I_{spec} = 3.344 \mu\text{A}$  and the aspect ratio  $W/L = 4.677$ . Knowing the length, we get the effective width  $W_{eff} = 4.319 \mu\text{m}$  and drawn width  $W = 4.28 \mu\text{m}$ .

We can check what is the resulting dc gain by estimating the output conductance  $G_{ds} = I_b/(\lambda_n L) = 0.241 \mu\text{A}/\text{V}$ . The resulting DC gain is then  $A_{dc} = G_m/G_{ds} = -260.391$  or 48.313 dB.

We also calculate the area and perimeter of the drain to estimate the junction capacitance and overlap capacitance in order to correct  $C_L$  to get the correct  $GBW$ . This results in  $C_{DBJ} = 3.6 \text{ fF}$ ,  $C_{GD} = 1.6 \text{ fF}$ ,  $C_D = 5.2 \text{ fF}$ . To account for the parasitic capacitance at the drain  $C_D = 5.2 \text{ fF}$ , we need to reduce the load capacitance. The effective load capacitance that needs to be added is then  $C_{L0} = 0.995 \text{ pF}$  instead of  $C_L = 1.000 \text{ pF}$ .

### 1.3.2 Simulations

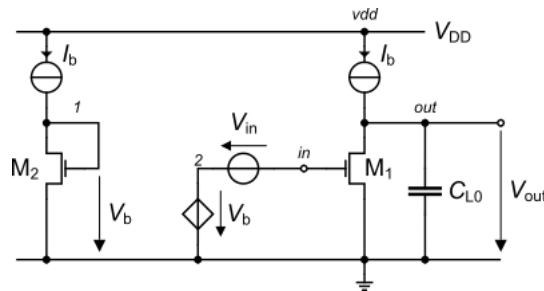


Figure 1.2: Schematic of the common-source (CS) gain stage used for simulation.

We can now check whether we get the correct  $GBW$  and DC gain using ngspice simulations with the schematic shown in Figure 1.2, where transistor  $M_2$  is used to correctly bias the gate of the CS transistor  $M_1$  so that it draws the desired bias current  $I_b$ .

The simulations will be performed with the following parameters:

```
.param VDD=1.8 Ib=3.344u
.param CL=994.80f W=4.28u L=1.00u AD=1.73e-12 PD=9.44e-06
```

Before running the AC simulation, we first need to check the quiescent voltages and currents and the operating point by running an .OP simulation. The node voltages are extracted from the .ic file and presented in Table 1.2.

Table 1.2: Operating point information.

Node	Voltage
vdd	1.8
in	0.508564

Table 1.2: Operating point information.

Node	Voltage
out	0.508564
1	0.508564
2	0.508564

The operating information for each transistor can be extracted and are given in Table 1.3 and Table 1.4.

Table 1.3: Operating point information extracted from ngspice .op file for each transistor.

Transistor	$I_D$ [ $\mu A$ ]	$I_{spec}$ [ $\mu A$ ]	$IC$	$n$	$V_{Dsat}$ [ $mV$ ]
M1	3.344	3.277	1.023	1.27	156
M2	3.344	3.277	1.023	1.27	156

Table 1.4: Small-signal operating point information extracted from ngspice .op file for each transistor.

Transistor	$n$	$G_{ms}$ [ $\mu A/V$ ]	$G_m$ [ $\mu A/V$ ]	$G_{mb}$ [ $\mu A/V$ ]	$G_{ds}$ [ $\mu A/V$ ]
M1	1.27	78.616	61.163	17.292	0.160
M2	1.27	78.616	61.163	17.292	0.160

We see that the simulated transconductance of  $M_1$   $G_m = 61.163 \mu A/V$  is slightly lower than the theoretical estimation  $G_m = 62.832 \mu A/V$ .

We can now proceed with the simulation of the transfer function which is shown in Figure 1.3.

From Figure 1.3, we see that the gain-bandwidth product  $GBW = 9.7 MHz$  is slightly lower than the specifications  $GBW = 10 MHz$  despite we have accounted for the junction capacitance at the output. This comes from the fact that the simulated transconductance  $G_m = 61.163 \mu A/V$  is slightly lower than the theoretical estimation  $G_m = 62.832 \mu A/V$ .

We also see that there is some discrepancy of the phase at high frequency (above the  $GBW$ ). This coming from the gate-to-drain capacitance (the overla capacitance  $C_{GD0}$ ) which introduces a positive zero. We can add this zero in the theoretical transfer leading to the transfer function magnitude and phase are plotted in Figure 1.4. We now see that we have a better fit at high frequency (dashed blue line). The gate-to-drain capacitance seems to be larger.

If we want to meet the specifications we can slightly increase the bias current to  $I_b = 3.5 \mu A$ . The transfer function is now given in Figure 1.5. We see that we are now right on spec.

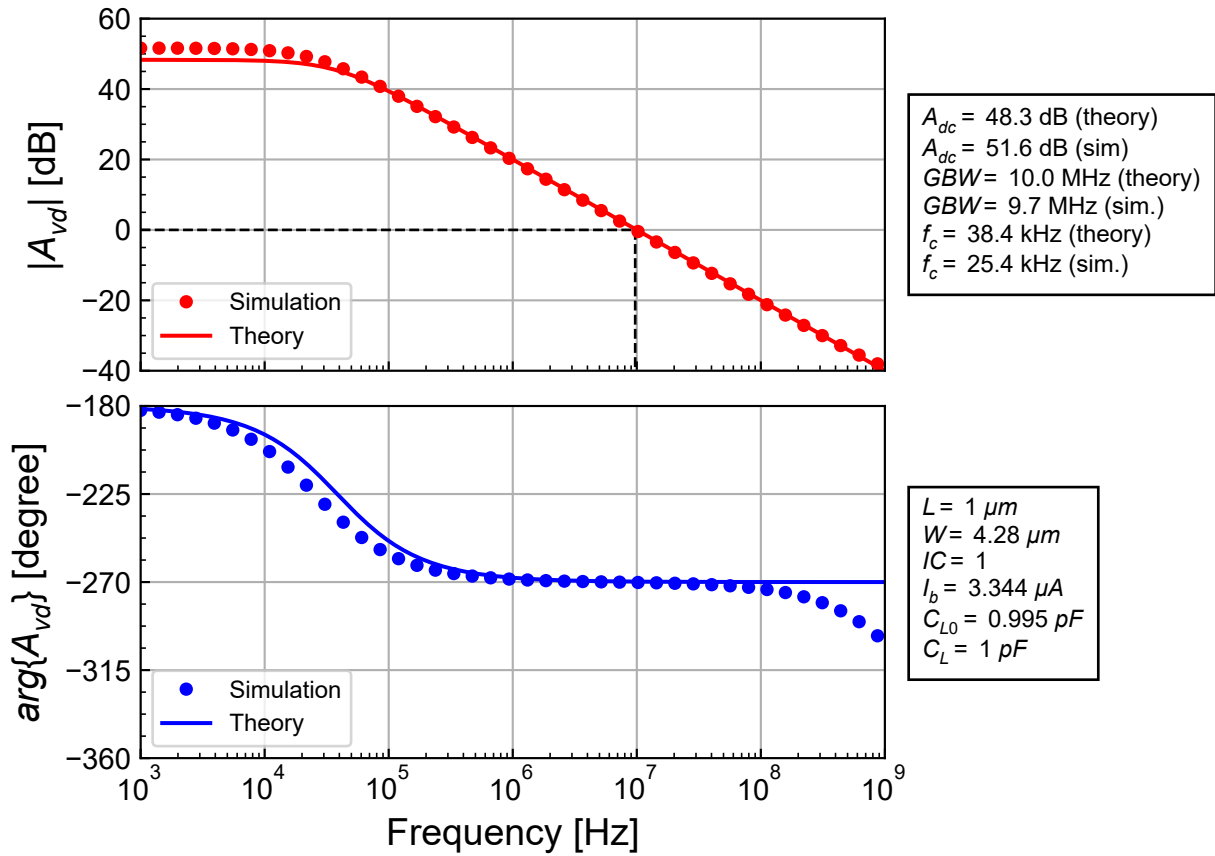


Figure 1.3: Simulated gain response compared to theoretical estimation for the long-channel case.

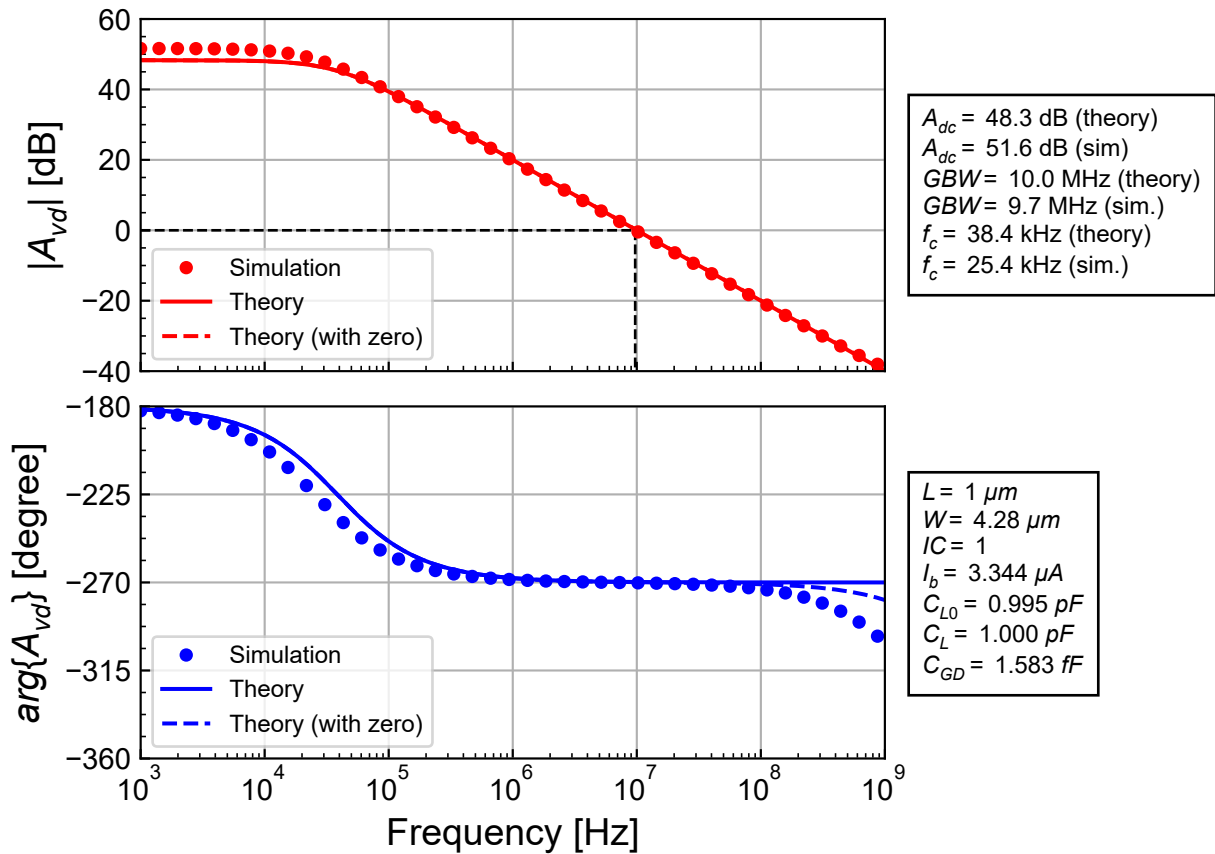


Figure 1.4: Simulated gain response compared to theoretical estimation for the long-channel case.

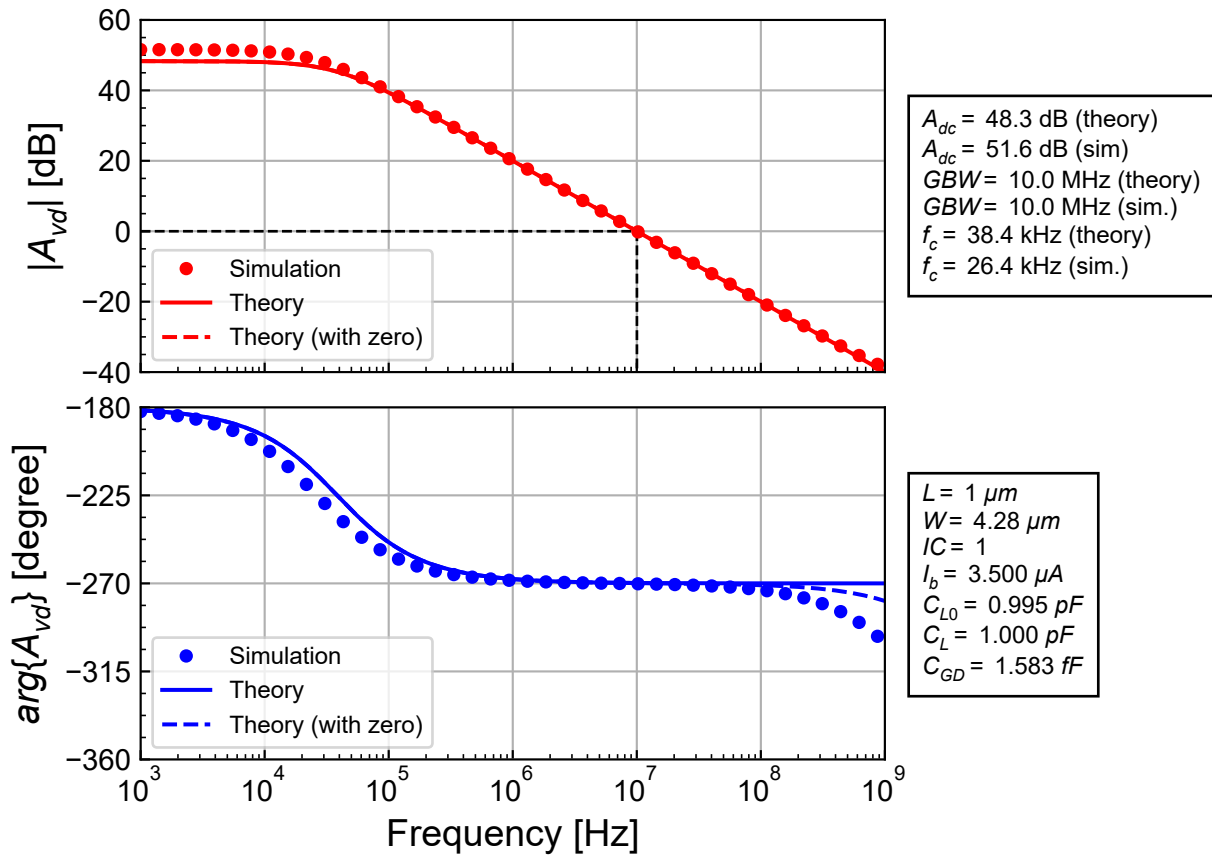


Figure 1.5: Simulated gain response compared to theoretical estimation for the long-channel case.

## 1.4 Short-channel case (including velocity saturation)

### 1.4.1 Design

The required transconductance hasn't changed because it is set by the desired gain-bandwidth product and load capacitance  $G_m = 62.832 \mu A/V$ .

For the short-channel case we will use the shortest channel length for this technology, namely  $L = 0.18 \mu m$  corresponding to an effective length  $L_{eff} = 104 nm$ . The velocity parameter for the chosen length is then given by  $\lambda_c = L_{satn}/L_{eff} = 0.250$ . The procedure is then the same: we first get the bias current from the current efficiency but including the effect of velocity saturation  $G_m nU_T/I_D = 0.606$ . We see that the current efficiency  $G_m nU_T/I_D$  is only slightly smaller than for the long-channel case due to velocity saturation. The bias current is then given by  $I_b = 3.410 \mu A$ . Despite we use a shorter channel-length, the required bias current is about the same than the one from the long-channel case. This is simply due to the fact the effect of velocity saturation is small in moderate and hence has little effect on the current efficiency.

From the bias current and the inversion coefficient we get the specific current as  $I_{spec} = 3.410 \mu A$  and the aspect ratio  $W_{eff}/L_{eff} = 4.770$ . For the chosen length we get the effective width  $W_{eff} = 0.499 \mu m$  and drawn width  $W = 0.46 \mu m$ .

We can check what is the resulting dc gain by estimating the output conductance  $G_{ds} = I_b/(\lambda_n L_{eff}) = 2.186 \mu A/V$ . The DC gain is now  $A_{dc} = -28.740$  or  $29.170 dB$ , which, as expected, is significantly lower than for the long-channel case.

We also calculate the area and perimeter of the drain to estimate the junction capacitance and overlap capacitance in order to correct  $C_L$  to get the correct  $GBW$ . This results in  $C_{DBJ} = 1 fF$ ,  $C_{GD} =$

0.183  $fF$ ,  $C_D = 1 fF$ . The effective load capacitance that needs to be added is then  $C_{L0} = 0.999 pF$ .

### 1.4.2 Simulations

We can check whether we get the correct GBW and dc gain using simulations with the following values of the parameters:

Before running the AC simulation, we first need to check the quiescent voltages and currents and the operating point by running an .OP simulation. The node voltages are extracted from the .ic file and presented in Table 1.5.

Table 1.5: Operating point information.

Node	Voltage
vdd	1.8
in	0.511076
out	0.511076
1	0.511076
2	0.511076

The operating information for each transistor can be extracted and are given in Table 1.6 and Table 1.7.

Table 1.6: Operating point information extracted from ngspice .op file for each transistor.

Transistor	$I_D [\mu A]$	$I_{spec} [\mu A]$	$IC$	$n$	$V_{Dsat} [mV]$
M1	3.500	3.273	1.072	1.27	157
M2	3.500	3.273	1.072	1.27	157

Table 1.7: Small-signal operating point information extracted from ngspice .op file for each transistor.

Transistor	$n$	$G_{ms} [\mu A/V]$	$G_m [\mu A/V]$	$G_{mb} [\mu A/V]$	$G_{ds} [\mu A/V]$
M1	1.27	81.190	63.169	17.855	0.167
M2	1.27	81.190	63.169	17.855	0.167

We see that the simulated transconductance of M<sub>1</sub>  $G_m = 63.169 \mu A/V$  is slightly larger than the theoretical estimation  $G_m = 62.832 \mu A/V$ .

```
.param VDD=1.8 Ib=3.410u
.param CL=999f W=0.46u L=0.18u AD=2.00e-13 PD=1.80e-06
```

The transfer function magnitude and phase are plotted in Figure 1.6, which shows a reasonable fit between the simulation and the theoretical estimation. The simulated gain-bandwidth product  $GBW$  is slightly lower than target and the simulated DC gain is slightly larger than the theoretical estimation.

From Figure 1.6, we see that the simulated DC gain is slightly larger than the theoretical estimation. We also see that the gain-bandwidth product specs is not met. If we want to meet the specifications we can slightly increase the bias current to  $I_b = 4.0 \mu A$ . The transfer function is now given in Figure 1.7. We see that we are now right on spec.

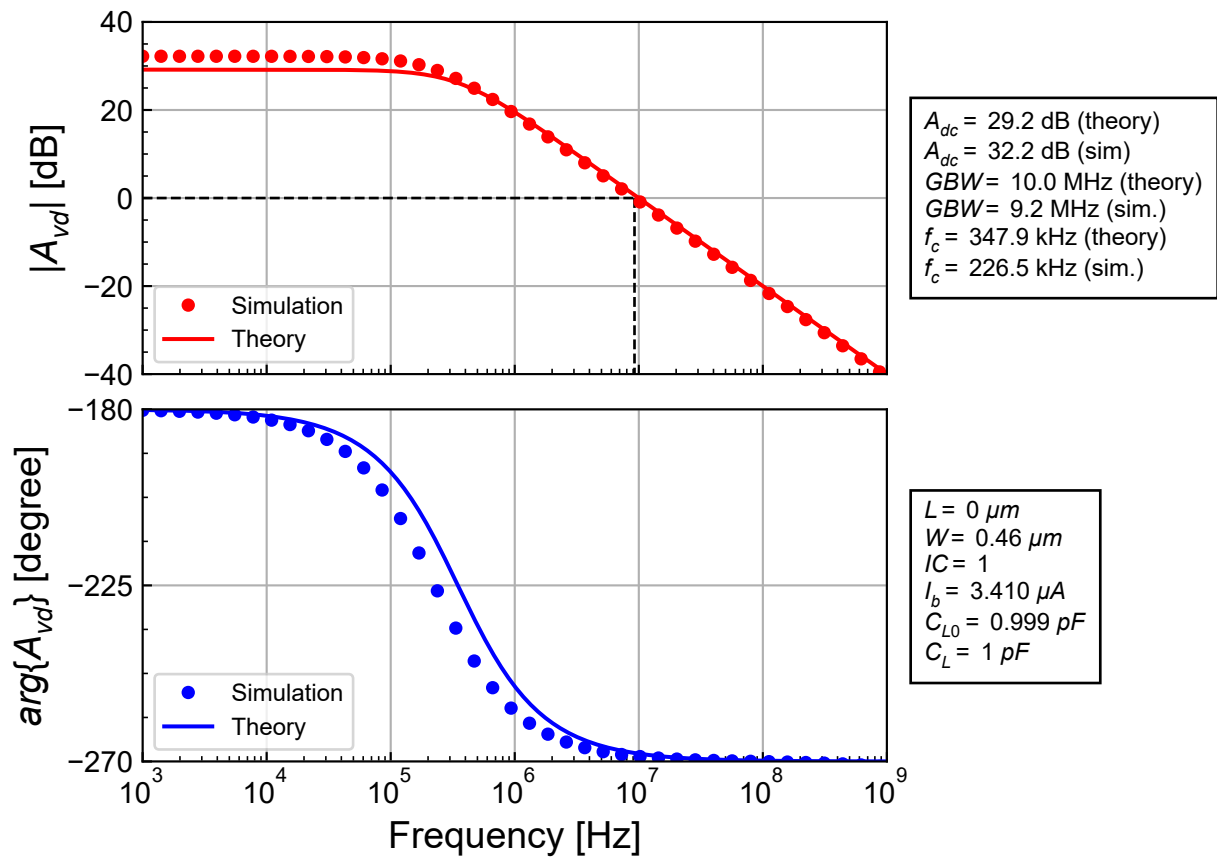


Figure 1.6: Simulated gain response compared to theoretical estimation for the short-channel case.

#### **i** Note

We also see that for the short-channel case, we don't see the zero which has moved to much higher frequency. This is due to the much smaller transistor width which significantly reduces the gate-to-drain capacitance.

 


Figure 1.7: Simulated gain response compared to theoretical estimation for the short-channel case.

## 2 Problem 2: Imposing the power consumption

### 2.1 Specifications

We now impose the power consumption, the inversion coefficient and the load capacitance according to the specifications given in Table 2.1.

Table 2.1: Specifications for problem 2.

Specification	Symbol	Value	Unit
Power consumption	$P$	20	$\mu W$
Inversion coefficient	$IC$	1	-
Load capacitance	$C_L$	1	$pF$

### 2.2 Long-channel case

#### 2.2.1 Design

For the long-channel case, we choose  $L = 1 \mu m$  which corresponds to an effective width  $L_{eff} = 0.924 \mu m$ . The maximum available current is directly given by  $I_b = P/V_{DD} = 11.111 \mu A$ . Since the inversion coefficient is chosen as  $IC = 1$ , we get the specific current as  $I_{spec} = 11.111 \mu A$ . The normalized transconductance is the given by the chosen inversion coefficient as  $g_{ms} = G_{ms}/G_{spec} = 0.618$ , from which we derive the transconductance  $G_m = 208.747 \mu A/V$  and the gain-bandwidth product for the given load capacitance  $GBW = G_m/C_L = 33.223 MHz$ . The aspect ratio is then given by  $W_{eff}/L_{eff} = 15.540$ . The effective width  $W_{eff} = 14.359 \mu m$  and drawn width  $W = 14.32 \mu m$ .

We can calculate the dc gain by first estimating the output conductance  $G_{ds} = I_b/(\lambda_n L_{eff}) = 0.802 \mu A/V$ . The dc gain is then given by  $A_{dc} = G_m/G_{ds} = -260.391$  or  $48.313 dB$ .

We also calculate the area and perimeter of the drain to estimate the junction capacitance and overlap capacitance in order to correct  $C_L$  to get the correct  $GBW$ . This results in  $C_{DBJ} = 12 fF$ ,  $C_{GD} = 5.248 fF$ ,  $C_D = 17 fF$ . The effective load capacitance that needs to be added is then  $C_{L0} = 0.983 pF$ .

#### 2.2.2 Simulations

We can now check whether we get the correct  $GBW$  and  $DC$  gain using ngspice simulations with the schematic shown in Figure 1.2. The simulations will be performed with the following parameters:

```
.param VDD=1.8 Ib=11.111u
.param CL=983.10f W=14.32u L=1.00u AD=5.74e-12 PD=2.95e-05
```

Before running the AC simulation, we first need to check the quiescent voltages and currents and the operating point by running an .OP simulation. The node voltages are extracted from the .ic file and presented in Table 1.2.

Table 2.2: Operating point information.

Node	Voltage
vdd	1.8
in	0.508531
out	0.508531
1	0.508531
2	0.508531

The operating information for each transistor can be extracted and are given in Table 1.3 and Table 1.4.

Table 2.3: Operating point information extracted from ngspice .op file for each transistor.

Transistor	$I_D$ [ $\mu A$ ]	$I_{spec}$ [ $\mu A$ ]	$IC$	$n$	$V_{Dsat}$ [ $mV$ ]
M1	11.111	10.895	1.022	1.27	156
M2	11.111	10.895	1.022	1.27	156

Table 2.4: Small-signal operating point information extracted from ngspice .op file for each transistor.

Transistor	$n$	$G_{ms}$ [ $\mu A/V$ ]	$G_m$ [ $\mu A/V$ ]	$G_{mb}$ [ $\mu A/V$ ]	$G_{ds}$ [ $\mu A/V$ ]
M1	1.27	261.256	203.257	57.466	0.533
M2	1.27	261.256	203.257	57.466	0.533

We see that the simulated transconductance of M<sub>1</sub>  $G_m = 203.257 \mu A/V$  is slightly lower than the theoretical estimation  $G_m = 208.747 \mu A/V$ .

The transfer function magnitude and phase are plotted in Figure 1.4, which shows a good fit between the simulation and the theoretical estimation.

## 2.3 Short-channel case (including velocity saturation)

### 2.3.1 Design

For the short-channel case we will use the shortest channel length for this technology, namely  $L = 180 \text{ nm}$ . The velocity parameter for the chosen length is then given by  $\lambda_c = L_{satn}/L = 0.250$ . The procedure is basically the same except that we now need to account for velocity saturation in the estimation of the transconductance. Since the inversion coefficient is chosen as  $IC = 1$ , we get the specific current as  $I_{spec} = 11.111 \mu A$ . The normalized transconductance is the given by the chosen inversion coefficient as  $g_{ms} = G_{ms}/G_{spec} = 0.606$ , from which we derive the transconductance  $G_m = 0.205 \text{ mA/V}$  and the gain-bandwidth product for the given load capacitance  $GBW = G_m/C_L = 32.580 \text{ MHz}$ . The aspect ratio is then given by  $W_{eff}/L_{eff} = 15.540$ . The effective width  $W_{eff} = 1.619 \mu m$  and drawn width  $W = 1.58 \mu m$ .

We can calculate the dc gain by first estimating the output conductance  $G_{ds} = I_b/(\lambda_n L_{eff}) = 7.123 \mu A/V$ . The dc gain is then given by  $A_{dc} = G_m/G_{ds} = -28.740$  or  $29.170 \text{ dB}$ .

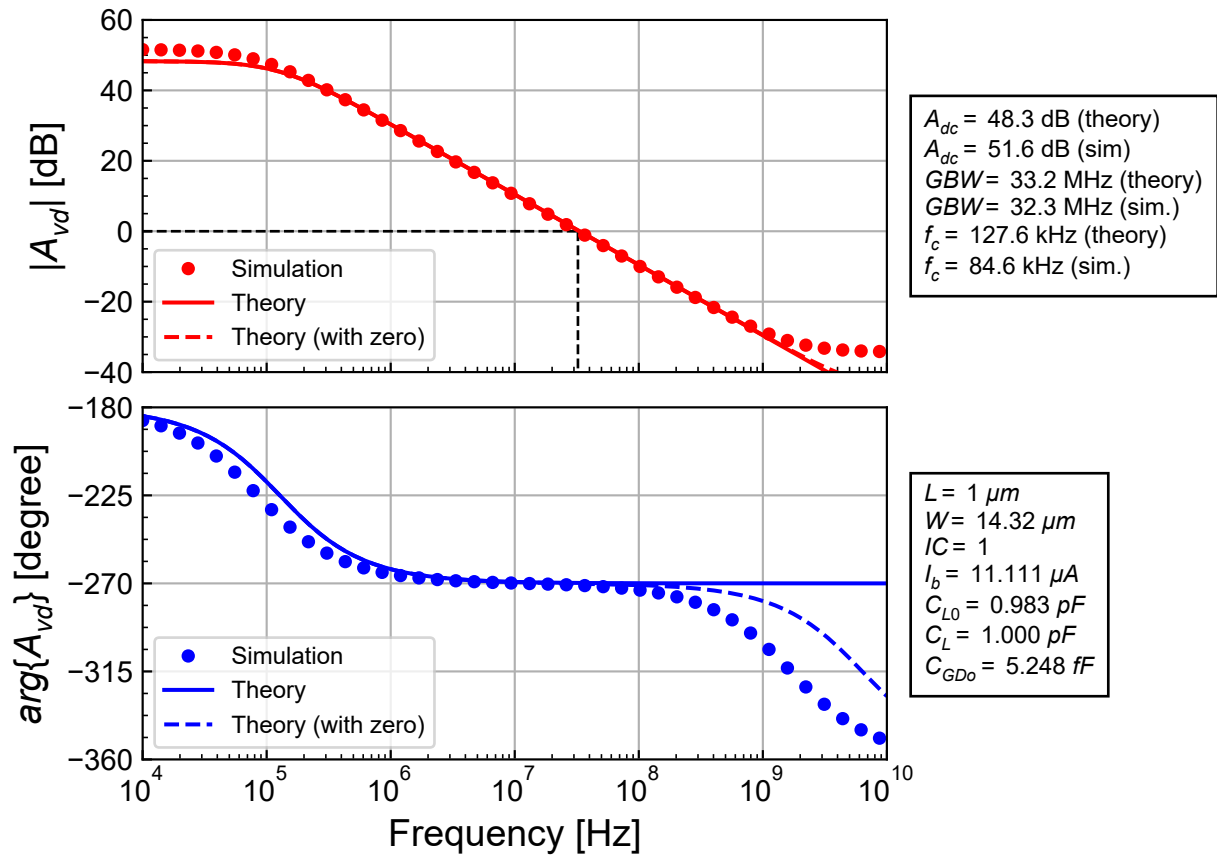


Figure 2.1: Simulated gain response compared to theoretical estimation for the long-channel case.

We also calculate the area and perimeter of the drain to estimate the junction capacitance and overlap capacitance in order to correct  $C_L$  to get the correct  $GBW$ . This results in  $C_{DBJ} = 1.5 \text{ fF}$ ,  $C_{GD} = 0.579 \text{ fF}$ ,  $C_D = 2.0 \text{ fF}$ . The effective load capacitance that needs to be added is then  $C_{L0} = 0.998 \text{ pF}$ .

### 2.3.2 Simulations

We can check whether we get the correct  $GBW$  and dc gain using simulations with the following values of the parameters:

```
.param VDD=1.8 Ib=11.111u
.param CL=997.97f W=1.58u L=0.18u AD=6.48e-13 PD=4.04e-06
```

The transfer function magnitude and phase are plotted in Figure 2.2, which shows a reasonable fit between the simulation and the theoretical estimation.

 


Figure 2.2: Simulated gain response compared to theoretical estimation for the short-channel case.

## 3 Problem 3: Imposing the gain bandwidth product and the current budget

### 3.1 Specifications

We now don't impose the inversion coefficient but the gain bandwidth product and the current budget. We keep the same load capacitance and consider a long channel. The specifications are now given in Table 3.1.

Table 3.1: Specifications for problem 3.

Specification	Symbol	Value	Unit
Gain-bandwidth product	$GBW$	1	$MHz$
Bias current	$I_b$	400	$nA$
Load capacitance	$C_L$	1	$pF$
Transistor length	$L$	1	$\mu m$

### 3.2 Design

We first get the transconductance required to achieve the target gain-bandwidth product as  $G_m = 6.283 \mu A/V$ . Knowing the bias current and the transconductance we can calculate the current efficiency as  $G_m nU_T/I_D = 0.517$ , from which we can derive the corresponding inversion coefficient  $IC = 1.810$ . We see that we are in the moderate inversion region. The specific current is then given by  $I_{spec} = 221 nA$ , the aspect ratio by  $W_{eff}/L_{eff} = 0.309$ , the effective width by  $W_{eff} = 289 nm$  and finally the drawn width  $W = 250 nm$ .

We can calculate the dc gain by first estimating the output conductance  $G_{ds} = I_b/(\lambda_n L_{eff}) = 28.860 nA/V$ . The dc gain is then given by  $A_{dc} = G_m/G_{ds} = -217.712$  or  $46.758 dB$ .

We also calculate the area and perimeter of the drain to estimate the junction capacitance and overlap capacitance in order to correct  $C_L$  to get the correct  $GBW$ . This results in  $C_{DBJ} = 391.2 aF$ ,  $C_{GD} = 105.918 aF$ ,  $C_D = 497.1 aF$ . The effective load capacitance that needs to be added is then  $C_{L0} = 999.503 fF$ . We observe that the parasitic capacitance at the drain are negligible compared to the load capacitance.

### 3.3 Simulations

We can now check whether we get the correct GBW and DC gain using ngspice simulations with the schematic shown in Figure 1.2. The simulations will be performed with the following parameters:

```
.param VDD=1.8 Ib=0.400u
.param CL=999.50f W=0.25u L=1.00u AD=1.16e-13 PD=1.38e-06
```

The transfer function magnitude and phase are plotted in Figure 1.4, which shows a good fit between the simulation and the theoretical estimation.

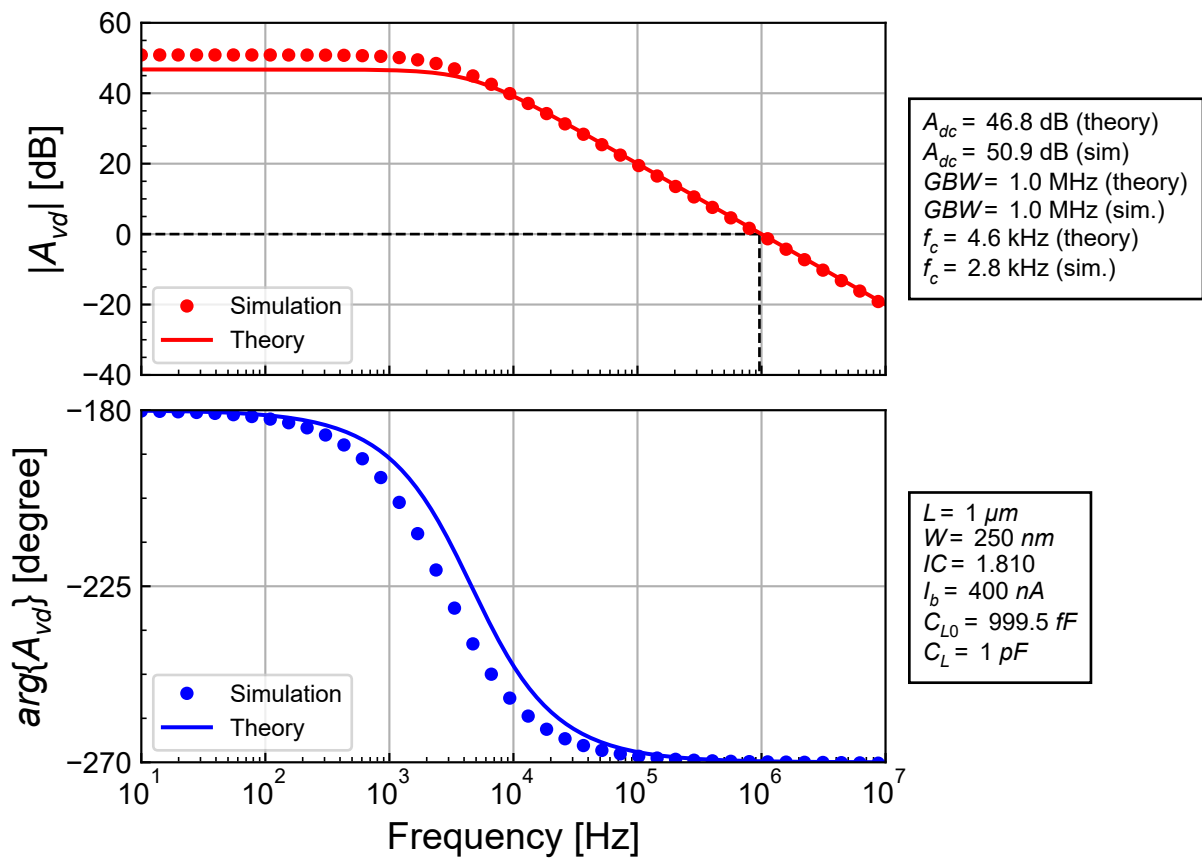


Figure 3.1: Simulated gain response compared to theoretical estimation for the long-channel case.

## 4 Problem 4: Imposing the input-referred noise

### 4.1 Specifications

In this example, we impose the input-referred noise by setting the white noise and the corner frequency. The specifications are given in Table 4.1.

Table 4.1: Specifications for problem 4.

Specification	Symbol	Value	Unit
Corner frequency	$f_k$	100	$kHz$
Input referred white PSD	$\sqrt{S_{n,th}}$	30	$\frac{nV}{\sqrt{Hz}}$
	$10 \log(S_{n,th})$	-150.46	$\frac{dBV}{\sqrt{Hz}}$
Inversion coefficient	$IC$	1	-
Load capacitance	$C_L$	1	$pF$

### 4.2 Design

We need the flicker noise parameter  $K_f = 8.100e-24 J$  and the oxide capacitance per unit area  $C_{ox} = 8.443 fF/\mu m^2$ .

Before the transconductance is derived from the thermal noise specification, we need to know the thermal noise excess factor  $\gamma_n$  for the given  $IC$  (we assume long-channel case) which is  $\gamma_n = 0.717$ . The transconductance is then given by  $G_m = 4kT\gamma_n/S_{nin,th} = 13.186 \mu A/V$ , where  $S_{nin,th} = V_{nin,th}^2$ . Once we have the transconductance, the procedure is similar to the previous one.

Having imposed the inversion coefficient  $IC = 1$ , we can deduce the current efficiency as  $G_m nU_T/I_D = 0.618$ . By definition of the current efficiency we can get the corresponding bias current  $I_b = 702 nA$ . The specific current and aspect ratio are then given by  $I_{spec} = 702 nA$  and  $W_{eff}/L_{eff} = 0.982$ .

The corner frequency will actually set the flicker noise which is inversely proportional to the gate area. We can therefore calculate the gate area from the flicker noise remembering that the corner frequency is the frequency at which the flicker noise becomes equal to the white noise. The gate area is obtained as  $W_{eff} L_{eff} = 10.660 \mu m^2$ . Knowing the  $W/L$  ratio we can calculate the effective width and length as  $W_{eff} = 3.235 \mu m$  and  $L_{eff} = 3.295 \mu m$ . The drawn width and length follow as  $W = 3.20 \mu m$  and  $L = 3.37 \mu m$ .

The gain-bandwidth product is given by  $GBW = 2.099 MHz$ .

We can calculate the dc gain by first estimating the output conductance  $G_{ds} = I_b/(\lambda_n L_{eff}) = 0.014 \mu A/V$ . The dc gain is then given by  $A_{dc} = G_m/G_{ds} = -928.687$  or  $59.357 dB$ .

We also calculate the area and perimeter of the drain to estimate the junction capacitance and overlap capacitance in order to correct  $C_L$  to get the correct  $GBW$ . This results in  $C_{DBJ} = 2.7 fF$ ,  $C_{GD} = 1.186 fF$ ,  $C_D = 3.9 fF$ . The effective load capacitance that needs to be added is then  $C_{L0} = 0.996 pF$ .

### 4.3 Simulations

We can now check whether we get the correct GBW and DC gain using ngspice simulations with the schematic shown in Figure 1.2. The simulations will be performed with the following parameters:

```
.param VDD=1.8 Ib=702n
.param CL=996.07f W=3.20u L=3.37u AD=1.29e-12 PD=7.27e-06
```

The transfer function magnitude and phase are plotted in Figure 4.2, which shows a good fit between the simulation and the theoretical estimation.

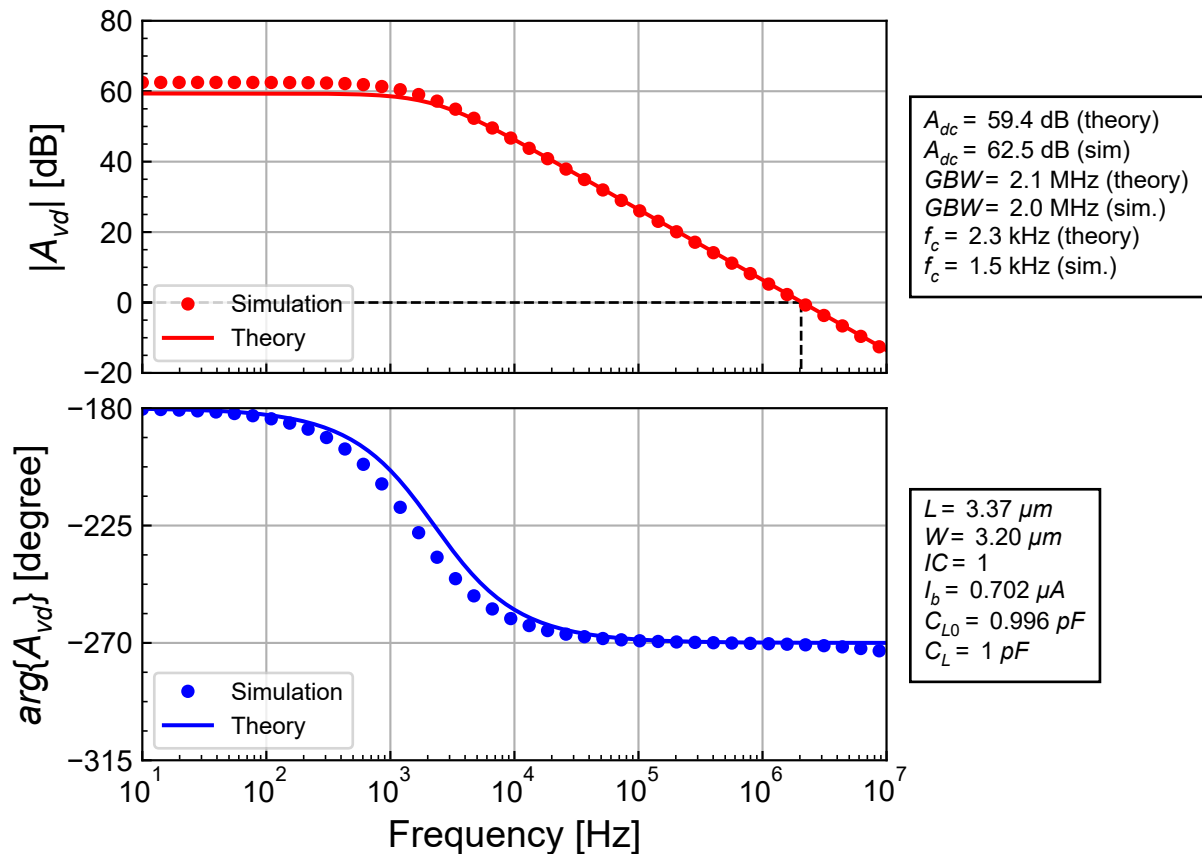


Figure 4.1: Simulated gain response compared to theoretical estimation for the long-channel case.

We can now check the input-referred noise PSD which is plotted in Figure 4.2. We can see that simulation perfectly matches the theoretical estimation.

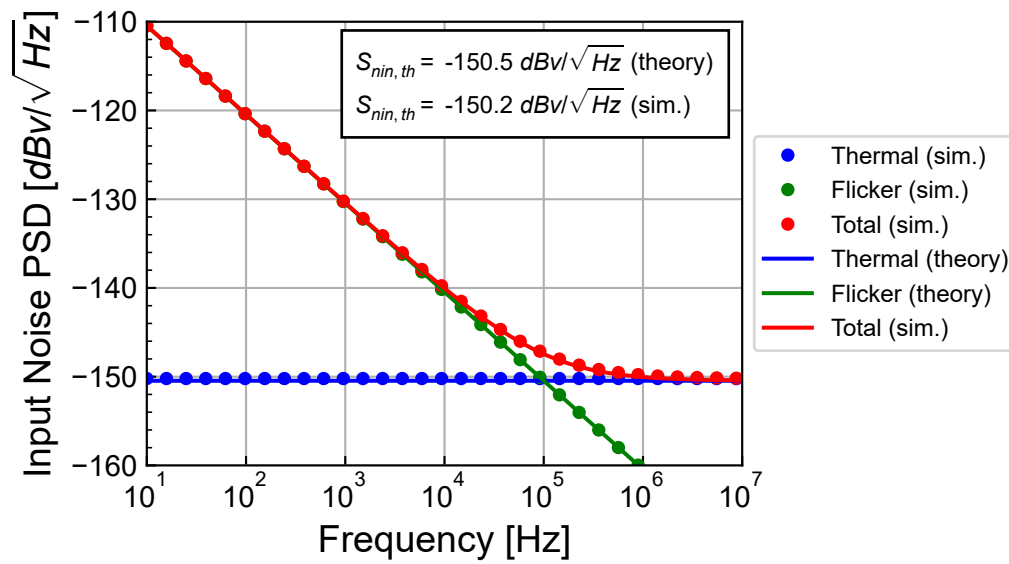


Figure 4.2: Simulated input-referred noise PSD compared to theoretical estimation.

## 5 Problem 5: Minimum current for a given gain-bandwidth product with self-loading

 


Figure 5.1: Schematic of the common-source (CS) illustrating the self-loading effect.

In this problem we want to find the minimum current required to achieve a given gain-bandwidth product accounting for the effect of self-loading as illustrated in Figure 5.1.

The total transistor parasitic capacitance at the drain can be written as

$$C_D = C_{D0} + C_{DW} \cdot W. \quad (5.1)$$

with

$$C_{D0} = 4H_{dif} \cdot C_{JSW}, \quad (5.2)$$

$$C_{DW} = 2(H_{dif} \cdot C_J + C_{JSW}) + C_{GDe}, \quad (5.3)$$

where  $C_{GDe}$  is the extrinsic capacitance per unit width which is made of the overlap capacitance  $C_{GD0}$ . In more advanced technologies we also need to add the fringing-field capacitance  $C_{GDf}$ . In this 180nm technology the fringing-field capacitance can be neglected so that  $C_{GDe} \cong C_{GD0}$ .

The part  $C_{D0}$  of the total parasitic capacitance at the drain  $C_D$  that doesn't scale with  $W$  needs to be added to  $C_{L0}$  so that the total load capacitance that does not scale with  $W$  is given by

$$C_L = C_{L0} + C_{D0}. \quad (5.4)$$

It can be shown [1] that when accounting for the self-loading effect, there is a minimum current for achieving a given gain-bandwidth product. The optimum value of the inversion coefficient  $IC_{opt}$  corresponding to this minimum bias current is given by

$$IC_{opt} = \left( \sqrt{\Theta \cdot (1 + \Theta)} + \Theta + \frac{1}{2} \right)^2 - \frac{1}{4} = 2\Theta \cdot (1 + \Theta) + (1 + 2\Theta) \cdot \sqrt{\Theta \cdot (1 + \Theta)}, \quad (5.5)$$

where

$$\Theta \triangleq \frac{\omega_u}{\omega_W}, \quad (5.6)$$

with

$$\omega_u \triangleq 2\pi GBW, \quad (5.7)$$

$$\omega_W \triangleq \frac{I_{spec\Box}}{nU_T \cdot C_{DW} \cdot L}. \quad (5.8)$$

The parameter  $\Theta$  is usually  $\Theta \ll 1$  and therefore (5.5) reduces to

$$IC_{opt} \cong 2\Theta + \sqrt{\Theta}. \quad (5.9)$$

We can define a normalized current and aspect ratio as

$$i_b \triangleq \frac{I_b}{I_{pec\Box} \cdot \Omega}, \quad (5.10)$$

$$AR \triangleq \frac{W/L}{\Omega}, \quad (5.11)$$

where

$$\Omega \triangleq \frac{\omega_u}{\omega_L}, \quad (5.12)$$

$$\omega_L \triangleq \frac{I_{spec\Box}}{nU_T \cdot C_L}. \quad (5.13)$$

The minimum normalized current  $i_{bopt}$  and aspect ratio  $AR_{opt}$  only depend on  $\Theta$  according to

$$i_{bopt} \triangleq i_b(IC_{opt}) = \sqrt{4IC_{opt} + 1} = 1 + 2\Theta + 2\sqrt{\Theta \cdot (1 + \Theta)}, \quad (5.14)$$

$$AR_{opt} \triangleq AR(IC_{opt}) = \frac{\sqrt{4IC_{opt} + 1}}{IC_{opt}} = \frac{1}{\sqrt{\Theta \cdot (1 + \Theta)}}. \quad (5.15)$$

## 5.1 Specifications

The specifications for Problem 5 are given in Table 5.1.

Table 5.1: Specifications for problem 5.

Specification	Symbol	Value	Unit
Gain-bandwidth product	$GBW$	25	$MHz$
Load capacitance	$C_{L0}$	20	$fF$
Transistor length	$L$	1	$\mu m$

## 5.2 Design

For accounting for the self-loading effect we need the capacitance per width  $C_{DW} = 1.167 fF/\mu m$ . All the parameters are given in Table 5.2.

Table 5.2: Parameters for problem 5.

Parameter	Value	Unit
$C_{DW}$	1.167	$fF/\mu m$
$C_{D0}$	0.16	$fF$
$C_{L0}$	20	$fF$
$C_L$	20.16	$fF$
$f_L$	171.589	$MHz$
$f_W$	2.965	$GHz$
$\Omega$	0.146	-
$\Theta$	0.00843	-

Table 5.2: Parameters for problem 5.

Parameter	Value	Unit
$IC_{opt}$	0.111	-
$i_{b,opt}$	1.201	-
$AR_{opt}$	10.846	-
$(W/L)_{opt}$	1.58	-
$I_{b,opt}$	125	$nA$
$W_{opt}$	1.46	$\mu m$
$G_{m,opt}$	3.456	$\mu A/V$
$C_{D,opt}$	1.703	$fF$
$AD$	0.58	$\mu m^2$
$PD$	3.72	$\mu m$
$C_{DBJ}$	1.328	$fF$
$C_F$	0.535	$fF$
$C_{out}$	21.863	$fF$
$GBW$ (check)	25	$MHz$
$f_z$	1.028	$GHz$
$A_{dc}$	52.346	$dB$

### 5.3 Simulations

We can now check whether we get the correct GBW and DC gain using ngspice simulations with the schematic shown in Figure 1.2. The simulations will be performed with the following parameters:

```
.param VDD=1.8 Ib=125n
.param CL=20.00f W=1.42u L=1.00u AD=5.84e-13 PD=3.72e-06
```

Before running the AC simulation, we first need to check the quiescent voltages and currents and the operating point by running an .OP simulation. The node voltages are extracted from the .ic file and presented in Table 5.3.

Table 5.3: Operating point information.

Node	Voltage
vdd	1.8
in	0.412978
out	0.412978
1	0.412978
2	0.412978

The operating information for each transistor can be extracted and are given in Table 5.4 and Table 5.5.

Table 5.4: Operating point information extracted from ngspice .op file for each transistor.

Transistor	$I_D$ [ $\mu A$ ]	$I_{spec}$ [ $\mu A$ ]	$IC$	$n$	$V_{Dsat}$ [ $mV$ ]
M1	0.125	1.147	0.109	1.27	121
M2	0.125	1.147	0.109	1.27	121

Table 5.5: Small-signal operating point information extracted from ngspice .op file for each transistor.

Transistor	$n$	$G_{ms}$ [ $\mu A/V$ ]	$G_m$ [ $\mu A/V$ ]	$G_{mb}$ [ $\mu A/V$ ]	$G_{ds}$ [ $\mu A/V$ ]
M1	1.27	4.385	3.395	0.981	0.008
M2	1.27	4.385	3.395	0.981	0.008

We see that the simulated transconductance of  $M_1$   $G_m = 3.395 \mu A/V$  is close to the theoretical estimation  $G_m = 3.456 \mu A/V$ .

The transfer function magnitude and phase are plotted in Figure 5.2, which shows a good fit between the simulation and the theoretical estimation. The gain-bandwidth product  $GBW$  is right on target. However, the simulated DC gain is slightly larger than the theoretical estimation. We also see some discrepancy at higher frequency. This is due to the zero introduced by the gate-to-drain capacitance  $C_{GD}$ .

 


Figure 5.2: Simulated gain response compared to theoretical estimation for the long-channel case.

From Figure 5.2 we see that accounting for the gate-to-drain capacitance which corresponds actually to the overlap capacitance  $C_{GD0}$ , still underestimates the location of the zero. This is due to a larger feedback capacitance. This is actually coming from the fact that we have ignored the transcapacitance  $C_m$  in the small-signal analysis. In the quasi-static (QS) circuit of the MOS transistor, the transconductance needs to be replaced by the a transadmittance  $Y_m$  given by

$$Y_m = G_m + s C_m \quad (5.16)$$

where  $C_m$  is the gate transcapacitance given by

$$C_m = C_{OX} \cdot c_m \quad (5.17)$$

where  $C_{OX} \triangleq W L C_{ox}$  and  $c_m$  is the normalized gate transcapacitance given by [2]

$$c_m = \frac{q_s - q_d}{15} \frac{4q_s^2 + 4q_d^2 + 12q_s q_d + 10q_s + 10q_d + 5}{(q_s + q_d + q)^3}, \quad (5.18)$$

which in saturation ( $q_d = 0$ ) reduces to

$$c_{m_{sat}} \cong \frac{4q_s^2 + 10q_s + 5}{(q_s + 1)^3}. \quad (5.19)$$

For a long-channel transistor,  $q_s$  is simply given by

$$q_s = \frac{\sqrt{4IC + 1} - 1}{2}. \quad (5.20)$$

The corresponding transfer function including the effect of the gate transcapacitance  $C_m$  is then given by

$$A(s) \triangleq \frac{\Delta V_{out}}{\Delta V_{in}} = A_{dc} \cdot \frac{1 - s/\omega_z}{1 + s/\omega_p} \quad (5.21)$$

where

$$A_{dc} = -G_m \cdot R_{ds}, \quad (5.22)$$

$$\omega_z = \frac{G_m}{C_F + C_m}, \quad (5.23)$$

$$\omega_p = \frac{1}{R_{ds} C_{out}}, \quad (5.24)$$

with  $C_{out} = C_L + C_F$  the total load capacitance. We see that the transcapacitance  $C_m$  directly adds to the feedback capacitance  $C_F$ , but does not add to the load capacitance  $C_{out}$ . Therefore, the expression of the pole remains unchanged. The DC gain and the gain-bandwidth hence also remain unaffected by the transcapacitance.

The theoretical transfer function including the effect of the gate transcapacitance is shown in Figure 5.3. We now see that the theoretical estimation perfectly matches the simulation including at high frequency.

 


Figure 5.3: Simulated gain response compared to theoretical estimation for the long-channel case.

## 6 Problem 6: Minimum current for a given DC gain and gain-bandwidth product with self-loading

In this problem we want to find the minimum current required to achieve a given gain-bandwidth product and a given dc gain accounting for the effect of self-loading. We can actually use the additional degree of freedom, namely the transistor length  $L$  (which has been arbitrarily set in the previous example), to set the DC gain. To this purpose we can use the simple output conductance model given by

$$G_{ds} \cong \frac{I_D}{\lambda \cdot L}. \quad (6.1)$$

It can be shown that there is also an optimum value of the inversion coefficient for which the bias current becomes minimum [1]

$$IC_{opt} = \frac{\sqrt{\xi}}{(1 - \sqrt{\xi})^2}, \quad (6.2)$$

where parameter  $\xi$  brings together the technology parameters and the specs according to

$$\xi \triangleq \underbrace{A_{dc} \cdot \omega_u}_{\text{specifications}} \cdot \underbrace{\frac{C_{DW} \cdot (nU_T)^2}{I_{spec\Box} \cdot \lambda}}_{\text{technology parameters}}. \quad (6.3)$$

It can be shown that parameter  $\xi$  needs to satisfy the following inequality

$$\xi \triangleq A_{dc} \cdot \omega_u \cdot \frac{C_{DW} \cdot (nU_T)^2}{I_{spec\Box} \cdot \lambda} < 1.$$

This means that we can check whether the specifications on  $A_{dc}$  and  $\omega_u$  can be achieved for a given technology (i.e. for a set of  $I_{spec\Box}$ ,  $\lambda$  and  $C_{DW}$ ). The closer  $\xi$  gets to 1, the larger the required current and size.

We can define the normalized bias current  $i_b$ , transistor width  $w$  and length  $\ell$  according to

$$i_b \triangleq \frac{I_b}{I_{norm}} = \frac{g_{ms} \cdot IC}{g_{ms}^2 - \xi \cdot IC} = \frac{g_{ms}/IC}{(g_{ms}/IC)^2 - \xi/IC}, \quad (6.4)$$

$$w \triangleq \frac{W}{W_{norm}} = \frac{IC}{g_{ms}^2 - \xi \cdot IC}, \quad (6.5)$$

$$\ell \triangleq \frac{L}{L_{norm}} = \frac{IC}{g_{ms}}, \quad (6.6)$$

where

$$I_{norm} \triangleq nU_T \cdot C_{L0} \cdot \omega_u, \quad (6.7)$$

$$W_{norm} \triangleq \frac{C_{L0} \cdot (nU_T)^2}{I_{spec\Box} \cdot \lambda} \cdot A_{dc} \cdot \omega_u, \quad (6.8)$$

$$L_{norm} \triangleq \frac{nU_T}{\lambda} \cdot A_{dc}. \quad (6.9)$$

The minimum normalized current is then given by

$$i_{b,opt} \triangleq i_b(IC_{opt}) = \frac{1}{(1 - \sqrt{\xi})^2} = \frac{1 + 2IC_{opt} + \sqrt{4IC_{opt} + 1}}{2}. \quad (6.10)$$

The optimum normalized width, length and transconductance are given by

$$w_{opt} \triangleq w(IC_{opt}) = \frac{1}{\sqrt{\xi} (1 - \sqrt{\xi})} = \frac{1 + 3IC_{opt} + (1 + IC_{opt}) \sqrt{4IC_{opt} + 1}}{2IC_{opt}}, \quad (6.11)$$

$$\ell_{opt} \triangleq \ell(IC_{opt}) = \frac{1}{1 - \sqrt{\xi}} = \frac{1 + \sqrt{4IC_{opt} + 1}}{2}, \quad (6.12)$$

$$g_{m,opt} \triangleq g_m(IC_{opt}) = \frac{1}{1 - \sqrt{\xi}} = \frac{1 + \sqrt{4IC_{opt} + 1}}{2}. \quad (6.13)$$

Note that the optimum current, width, length and transconductance only depend on  $\xi$ .

## 6.1 Specifications

The specifications for Problem 5 are given in Table 6.1.

Table 6.1: Specifications for problem 6.

Specification	Symbol	Value	Unit
DC gain	$A_{dc}$	50	$dB$
Gain-bandwidth product	$GBW$	25	$MHz$
Load capacitance	$C_{L0}$	20	$fF$

## 6.2 Design

We can start by checking that the specifications in Table 6.1 are feasible for the given 180nm technology. For this we can check that

$$\xi \triangleq A_{dc} \cdot \omega_u \cdot \frac{C_{DW} \cdot (nU_T)^2}{I_{spec} \cdot \lambda} < 1.$$

For the specifications in Table 6.1 and the chosen 180nm technology we have  $\xi = 0.006$  which is smaller than 1.

Table 6.2: Parameters or problem 6.

Parameter	Value	Unit
$C_{DW}$	1.167	$fF/\mu m$
$C_{D0}$	0.16	$fF$
$C_{L0}$	20	$fF$
$C_L$	20.16	$fF$
$\xi$	0.006	-
$IC_{opt}$	0.09	-
$i_{b,opt}$	1.172	-
$w_{opt}$	14.161	-
$\ell_{opt}$	1.083	-
$g_{m,opt}$	1.083	-

Table 6.2: Parameters or problem 6.

Parameter	Value	Unit
$I_{b,opt}$	122	$nA$
$(W/L)_{opt}$	1.58	-
$I_{norm}$	104	$nA$
$W_{norm}$	101	$nm$
$L_{norm}$	694	$nm$
$G_{m,norm}$	3.167	$\mu A/V$
$I_{b,opt}$	122.138	$nA$
$W_{opt}$	1.43	$\mu m$
$L_{opt}$	750.94	$nm$
$G_{m,opt}$	3.429	$\mu A/V$
$C_{D,opt}$	1.669	$fF$
$AD$	0.57	$\mu m^2$
$PD$	3.662	$\mu m$
$C_{DBJ}$	1.305	$fF$
$C_F$	0.524	$fF$
$C_{out}$	21.829	$fF$
$GBW$ (check)	25	$MHz$
$f_z$	1.028	$GHz$
$A_{dc}$	50	$dB$

### 6.3 Simulations

We can now check whether we get the correct GBW and DC gain using ngspice simulations with the schematic shown in Figure 1.2. The simulations will be performed with the following parameters:

```
.param VDD=1.8 Ib=122n
.param CL=20.00f W=1.43u L=0.75u AD=5.72e-13 PD=3.66e-06
```

Before running the AC simulation, we first need to check the quiescent voltages and currents and the operating point by running an .OP simulation. The node voltages are extracted from the .ic file and presented in Table 6.3.

Table 6.3: Operating point information.

Node	Voltage
vdd	1.8
in	0.4076
out	0.4076
1	0.4076
2	0.4076

The operating information for each transistor can be extracted and are given in Table 6.4 and Table 6.5.

Table 6.4: Operating point information extracted from ngspice .op file for each transistor.

Transistor	$I_D$ [ $\mu A$ ]	$I_{spec}$ [ $\mu A$ ]	$IC$	$n$	$V_{Dsat}$ [mV]
M1	0.122	1.597	0.076	1.27	118
M2	0.122	1.597	0.076	1.27	118

Table 6.5: Small-signal operating point information extracted from ngspice .op file for each transistor.

Transistor	$n$	$G_{ms}$ [ $\mu A/V$ ]	$G_m$ [ $\mu A/V$ ]	$G_{mb}$ [ $\mu A/V$ ]	$G_{ds}$ [ $\mu A/V$ ]
M1	1.27	4.390	3.400	0.980	0.010
M2	1.27	4.390	3.400	0.980	0.010

We see that the simulated transconductance of  $M_1$   $G_m = 3.400 \mu A/V$  is close to the theoretical estimation  $G_m = 3.429 \mu A/V$ .

The transfer function magnitude and phase are plotted in Figure 6.1, which shows an almost perfect fit between the simulation and the theoretical estimation. The DC gain and gain-bandwidth product are right on target. Even the high frequency behavior is well captured because of the good estimation of the total gate-to-drain capacitance including the contribution of the gate transcapacitance.

 


Figure 6.1: Simulated gain response compared to theoretical estimation for the long-channel case.

## 7 Conclusion

This exercise has shown various ways to design a single transistor setting its bias current and choosing its width and length for reaching different specifications. It has also illustrated the role of parasitic capacitances and how to estimate them. All the designs have been successfully checked with simulations using ngspice and the EKV 2.6 compact model.

## References

- [1] C. Enz, “Common-source Open-loop Optimization.” [https://github.com/chrisenz/Analog-Circuit-Design/blob/main/Amplifiers/Basic/CS%20OL%20Optimization/CS\\_OL\\_optimization.pdf](https://github.com/chrisenz/Analog-Circuit-Design/blob/main/Amplifiers/Basic/CS%20OL%20Optimization/CS_OL_optimization.pdf), 2025.
- [2] C. C. Enz and E. A. Vittoz, *Charge-Based MOS Transistor Modeling - The EKV Model for Low-Power and RF IC Design*, 1st ed. John Wiley, 2006.