

# **Fundamentals of Analog VLSI Design**

## **Exercise 5 - Solution**

**The Cascode Gain Stage**

Christian Enz (christian.enz@epfl.ch)

15.10.2025

# Table of contents

<b>1</b>	<b>Cascode stage</b>	<b>3</b>
1.1	Analysis . . . . .	3
1.1.1	Small-signal analysis . . . . .	3
1.1.2	Noise analysis . . . . .	5
1.2	Design . . . . .	7
1.3	Simulations . . . . .	10
1.3.1	Transfer function . . . . .	11
1.3.2	Input-referred noise . . . . .	11
<b>2</b>	<b>Regulated cascode</b>	<b>13</b>
2.1	Small-signal analysis . . . . .	13
2.2	Noise analysis . . . . .	14

# 1 Cascode stage

 


Figure 1.1: Schematic of the cascode gain stage.

## 1.1 Analysis

### 1.1.1 Small-signal analysis

 


Figure 1.2: Small-signal schematic of the cascode stage of Figure 1.1 for the calculation of the equivalent transconductance.

The small-signal schematic corresponding to Figure 1.1 for the derivation of the equivalent transconductance is shown in Figure 1.2. Note that the output is short-circuited to ground for calculating the short-circuit output current and the corresponding transconductance. The equivalent transconductance is then given by

$$G_{meq} \triangleq \left. \frac{\Delta I_{out}}{\Delta V_{in}} \right|_{\Delta V_{out}=0} = G_{m1} \cdot \frac{G_{ms2} + G_{ds2}}{G_{ms2} + G_{ds1} + G_{ds2}} \cong G_{m1}, \quad (1.1)$$

which shows that assuming  $G_{ms2} \gg G_{ds1}, G_{ds2}$ , the equivalent transconductance of the cascode stage is equal to the transconductance of the driver transistor  $M_1$ . This result is expected since the cascode transistor is a common gate stage which has a unity current gain so that the current coming from the driver transistor  $M_1$  is directly directed to the output.

The small-signal schematic for the calculation of the output conductance is shown in Figure 1.3. The output conductance is given by

$$G_{out} \triangleq \frac{\Delta I_{out}}{\Delta V_{out}} = \frac{G_{ds1} G_{ds2}}{G_{ms2} + G_{ds1} + G_{ds2}} \cong \frac{G_{ds1}}{G_{ms2}/G_{ds2}}, \quad (1.2)$$

which is equal to the output conductance of  $M_1$ ,  $G_{ds1}$ , divided by the voltage gain of the cascode  $G_{ms2}/G_{ds2}$ . This means that, at low-frequency, the output conductance of a single transistor can be reduced by adding a cascode stage at the cost of some voltage headroom to maintain  $M_2$  in saturation.

 


Figure 1.3: Small-signal schematic of the cascode stage of Figure 1.1 for the calculation of the output conductance.

 


Figure 1.4: Small-signal schematic of the cascode stage of Figure 1.1 for the calculation of the output admittance including the parasitic capacitance  $C_{p1}$ .

 


Figure 1.5: Effect of the parasitic capacitance  $C_{p1}$  on the output admittance  $Y_{out}$ .

The impact of the parasitic capacitance at node 1 on the output admittance can be investigated by adding the capacitance as shown in Figure 1.4. The output admittance then becomes

$$Y_{out} = G_{out} \cdot \frac{1 + s/\omega_z}{1 + s/\omega_p}, \quad (1.3)$$

where

$$G_{out} \cong \frac{G_{ds1}G_{ds2}}{G_{ms2}}, \quad (1.4)$$

$$\omega_z \triangleq \frac{G_{ds1}}{C_{p1}}, \quad (1.5)$$

$$\omega_p \triangleq \frac{G_{ms2}}{C_{p1}}. \quad (1.6)$$

The magnitude of  $Y_{out}$  versus frequency is sketched in Figure 1.5. At low-frequency, i.e. for  $\omega \ll \omega_z \ll \omega_p$ , the output admittance is equal to the output conductance  $Y_{out} \cong G_{out}$ . However for  $\omega_z \ll \omega_p \ll \omega$ , the output admittance increases to the output conductance of  $M_2$   $Y_{out} \cong G_{ds2}$ . We see that the cascode effect is lost. This can easily be understood since for  $\omega_p \ll \omega$ , the cascode node 1 is shortened to the ac ground and the voltage controlling the source of  $M_2$  is zero leaving the output conductance of  $M_2$  only in the small-signal schematic of Figure 1.4.

### 1.1.2 Noise analysis

 


Figure 1.6: Small-signal schematic of the cascode stage of Figure 1.1 for the noise calculation.

To calculate the output noise PSD we can use the schematic shown in Figure 1.6. The output noise current is then given by

$$I_{nout} = \frac{G_{ms2} + G_{ds2}}{G_{ms2} + G_{ds1} + G_{ds2}} \cdot I_{n1} + \frac{G_{ds1}}{G_{ms2} + G_{ds1} + G_{ds2}} \cdot I_{n2} \cong I_{n1} + \frac{I_{n2}}{G_{ms2}/G_{ds1}}, \quad (1.7)$$

for  $G_{ms2} \gg G_{ds1}, G_{ds2}$ . We see that the contribution to the output noise current of the cascode stage  $I_{n2}$  is actually divided by  $G_{ms2}/G_{ds1}$ . Provided that this gain can be made sufficiently large and that both transistors have the same noise, the noise of the cascode stage can be made negligible compared to the noise due to  $M_1$ . Ultimately if  $G_{ds1} = 0$ , the noise current  $I_{n2}$  circulates in the cascode transistor  $M_2$  ( $G_{ms2}$  in the small-signal schematic of Figure 1.6) and hence does not reach the output.

The output noise conductance  $G_{nout}$  is then given by

$$G_{nout}(f) \cong G_{n1}(f) + \left( \frac{G_{ds1}}{G_{ms2}} \right)^2 G_{n2}(f) \quad (1.8)$$

where the noise conductances are given by

$$G_{ni}(f) = \gamma_{ni} \cdot G_{mi} + \frac{\rho_n}{f W_i L_i} \cdot G_{mi}^2 \quad \text{for } i = 1, 2. \quad (1.9)$$

The input-referred noise is obtained by dividing  $G_{nout}$  by  $G_{meq}^2$ , resulting in

$$R_{nin} = \frac{G_{nout}(f)}{G_{meq}^2} \cong \frac{G_{nout}(f)}{G_{m1}^2} \cong \frac{G_{n1}(f)}{G_{m1}^2} + \left( \frac{G_{ds1}}{G_{m1} G_{ms2}} \right)^2 G_{n2}(f). \quad (1.10)$$

It can be decomposed into the thermal and flicker noise components according to

$$R_{nin} = R_{nt} + R_{nf}(f) \quad (1.11)$$

where  $R_{nt}$  is the total input-referred thermal noise given by

$$R_{nt} \cong \frac{\gamma_{n1}}{G_{m1}} + \left( \frac{G_{ds1}}{G_{m1}} \right)^2 \frac{\gamma_{n2}}{n_2 G_{ms2}} = \frac{\gamma_{n1}}{G_{m1}} \cdot (1 + \eta_{th}), \quad (1.12)$$

where  $\eta_{th}$ , given by

$$\eta_{th} \cong \frac{\gamma_{n2}}{n_2 \gamma_{n1}} \cdot \frac{G_{ds1}^2}{G_{m1} G_{ms2}}, \quad (1.13)$$

represents the contribution of the cascode transistor  $M_2$  to the input-referred thermal noise relative to that of  $M_1$ . Since  $\gamma_{n1}$  and  $\gamma_{n2}$  are of the same order of magnitude and  $G_{m1}, G_{ms2} \gg G_{ds1}$ , this results in  $\eta_{th} \ll 1$ , meaning that the contribution of  $M_2$  is negligible compared to that of  $M_1$  (at low frequency).

The noise excess factor of the cascode gain stage is given by

$$\gamma_{cas} \triangleq G_{meq} \cdot R_{nt} \cong G_{m1} \cdot R_{nt} = \gamma_{n1} \cdot (1 + \eta_{th}) \cong \gamma_{n1}. \quad (1.14)$$

The thermal noise excess factor of the cascode gain stage is about equal to the thermal noise excess factor of the driver transistor  $M_1$ .

The input-referred flicker noise  $R_{nf}(f)$  is given by

$$R_{nf}(f) \cong \frac{\rho_n}{f W_1 L_1} + \left( \frac{G_{ds1}}{G_{m1}} \right)^2 \frac{\rho_n}{n_2^2 f W_2 L_2} = \frac{\rho_n}{f W_1 L_1} \cdot (1 + \eta_{fl}). \quad (1.15)$$

where  $\eta_{fl}$ , given by

$$\eta_{fl} = \left( \frac{G_{ds1}}{n_2 G_{m1}} \right)^2 \frac{W_1 L_1}{W_2 L_2} \quad (1.16)$$

Assuming  $M_1$  and  $M_2$  have the same area and  $G_{m1}/G_{ds1} \gg 1$ , the contribution of  $M_2$  to the input-referred flicker noise is negligible compared to that of  $M_1$  and (1.15) simplifies to

$$R_{nf}(f) \cong \frac{\rho_n}{f W_1 L_1}, \quad (1.17)$$

which corresponds to the contribution of  $M_1$  only.

 


Figure 1.7: Small-signal schematic of the cascode stage of Figure 1.1 for the calculation of the noise including the effect of the parasitic capacitance  $C_{p1}$ .

Similarly, the impact of the parasitic capacitance on the noise can be calculated from Figure 1.7. The output noise conductance is then given by

$$G_{nout} = |H_{n1}(\omega)|^2 \cdot G_{n1} + |H_{n2}(\omega)|^2 \cdot G_{n2}, \quad (1.18)$$

where

$$H_{n1}(s) = \frac{1}{1 + s/\omega_p} \tag{1.19}$$

$$H_{n2}(s) = \frac{G_{ds1}}{G_{ms2}} \cdot \frac{1 + s/\omega_z}{1 + s/\omega_p}. \tag{1.20}$$

 


Figure 1.8: Magnitude of the noise transfer functions  $H_{n1}$  and  $H_{n2}$  versus frequency.

The magnitude of  $H_{n1}$  and  $H_{n2}$  versus frequency are sketched in Figure 1.8. For  $\omega \ll \omega_z \ll \omega_p$ ,  $H_{n1} \cong 1$  and  $H_{n2} \cong G_{ds1}/G_{ms2}$  which is the result obtained above. However, for  $\omega_z \ll \omega_p \ll \omega$ ,  $H_{n1} \cong \omega_p/s$  and  $H_{n2} \cong 1$ . We see that the cascode effect is lost since the noise of  $M_2$  is no more divided by the cascode gain  $G_{ms2}/G_{ds1}$  but is entirely transferred to the output.

As a conclusion, adding a cascode stage reduces the output conductance without penalty on the noise, but at the cost of a slight voltage overhead for maintaining  $M_2$  in saturation. This is only true for  $\omega < \omega_z = G_{ds1}/C_{p1}$ . For frequencies  $\omega \gg \omega_p = G_{ms2}/C_{p1}$  the cascode effect is lost. Note that in order to maximize  $G_{ms2}$  at a given current and minimize its saturation voltage,  $M_2$  should be biased in weak inversion.

## 1.2 Design

We want to size the circuit of Figure 1.1 for the specifications given in Table 1.1. We need to find the minimum current and size the transistor to achieve these specs. We will design the amplifier for a generic 180nm bulk CMOS process. The physical parameters are given in Table 1.2, the global process parameters in Table 1.3 and finally the MOSFET parameters in Table 1.4.

Table 1.1: Specifications for the differential pair with resistive loads.

Specification	Symbol	Value	Unit
DC gain	$A_{dc}$	80	$dB$
DC gain	$A_{dc}$	10000	-
Gain-bandwidth product	$GBW$	10	$MHz$
Load capacitance	$C_L$	1	$pF$

Table 1.2: Physical parameters

Parameter	Value	Unit
$T$	300	$K$
$U_T$	25.875	$mV$

Table 1.3: Global process parameters

Parameter	Value	Unit
$V_{DD}$	1.8	$V$
$C_{ox}$	8.443	$\frac{fF}{\mu m^2}$
$W_{min}$	200	$nm$
$L_{min}$	180	$nm$

Table 1.4: Transistor process parameters

Parameter	NMOS	PMOS	Unit
sEKV parameters			
$n$	1.27	1.31	-
$I_{spec\Box}$	715	173	$nA$
$V_{T0}$	0.455	0.445	$V$
$L_{sat}$	26	36	$nm$
$\lambda$	13	20	$\frac{V}{\mu m}$
Overlap capacitances parameters			
$C_{GDo}$	0.366	0.329	$\frac{fF}{\mu m}$
$C_{GSo}$	0.366	0.329	$\frac{fF}{\mu m}$
$C_{GBo}$	0	0	$\frac{fF}{\mu m}$
Junction capacitances parameters			
$C_J$	1	1.121	$\frac{fF}{\mu m^2}$
$C_{JSW}$	0.2	0.248	$\frac{fF}{\mu m}$
Flicker noise parameters			
$K_F$	8.1e-24	6.8e-23	$J$
$AF$	1	1	-
$\rho$	0.05794	0.4828	$\frac{V \cdot m^2}{A \cdot s}$
Matching parameters			
$A_{VT}$	5	5	$mV \cdot \mu m$
$A_\beta$	1	1	$\% \cdot \mu m$
Source and drain sheet resistance parameter			
$R_{sh}$	600	2386	$\frac{\Omega}{\mu m}$
Width and length parameters			
$\Delta W$	39	54	$nm$
$\Delta L$	-76	-72	$nm$

The gain-bandwidth product directly sets the transconductance of  $M_1$  as  $G_{m1} = 62.832 \mu A/V$ . Imposing an inversion coefficient  $IC_1 = 1$  allows to derive the required bias current as  $I_b = G_{m1} n U_T / g_{msid}(IC_1) = 3.344 \mu A$ . We then can find the specific current  $I_{spec1} = 3.344 \mu A$  and aspect ratio  $W_1/L_1 = 4.677$ .

The DC gain then sets the output conductance as  $G_{out} = 6.283 nA/V$ . To minimize the voltage headroom needed for  $M_2$  and maximize its current efficiency, we will bias  $M_2$  in weak inversion setting its inversion coefficient to  $IC_2 = 0.1$ . Knowing  $IC_2$  and  $I_b$  we can deduce its source transconductance as  $G_{ms2} = 118.405 \mu A/V$ . If we split the overall voltage gain equally between  $M_1$  and  $M_2$  we get  $G_{m1}/G_{ds1} = G_{ms2}/G_{ds2} = \sqrt{A_{dc}} = 100$ . We now can deduce  $G_{ds1} = 0.628 \mu A/V$  and  $G_{ds2} = 1.184 \mu A/V$ . This leads to  $L_1 = 0.49 \mu m$  and  $L_2 = 0.29 \mu m$ .

It turns out that the length of  $M_1$  and  $M_2$  are actually independent of their transconductances  $G_{m1}$

and  $G_{ms2}$ . Indeed, from the output conductance we get the transistor length as

$$L_1 = \frac{I_b}{\lambda_n G_{ds1}} \quad (1.21)$$

The output conductance  $G_{ds1}$  is set by the required DC gain as

$$G_{ds1} = \frac{G_{m1}}{\sqrt{A_{dc}}} = \frac{2\pi GBW C_L}{\sqrt{A_{dc}}} \quad (1.22)$$

Now the bias current is given by

$$I_b = G_{m1} \frac{n_1 U_T}{gmsid(IC_1)} \quad (1.23)$$

Replacing (1.23) and (1.22) in (1.21) results in

$$L_1 = \frac{n_1 U_T \sqrt{A_{dc}}}{\lambda_n gmsid(IC_1)}, \quad (1.24)$$

which is independent of the transconductance  $G_{m1}$ .

Similarly for  $M_2$  we get

$$L_2 = \frac{U_T \sqrt{A_{dc}}}{\lambda_n gmsid(IC_2)}, \quad (1.25)$$

which is independent of the source transconductance  $G_{ms2}$  of  $M_2$ .

We now get the transistor width as  $W_1 = 1.88 \mu m$  and  $W_2 = 10.12 \mu m$ .

We still need to set the bias voltage for the cascode transistor. We want to bias  $M_1$  at the onset of saturation  $V_{DSsat1}$ . The  $V_{GS2}$  voltage of  $M_2$  can be approximated by  $V_{T0n}$ . The bias voltage is then given by

$$V_{b2} = V_{GS2} + V_{DSsat1} \quad (1.26)$$

which is 0.571 V. We will set it to  $V_{b2} = 0.650 V$  so we have some margin.

Table 1.5: Transistor size and bias information.

Transistor	$W$ [ $\mu m$ ]	$L$ [ $\mu m$ ]	$I_D$ [ $\mu A$ ]	$I_{spec}$ [ $\mu A$ ]	$IC$	$V_G - V_{T0}$ [ $mV$ ]	$V_{DSsat}$ [ $mV$ ]
M1	1.88	0.49	3.344	2.763	1.2	22	118
M2	10.12	0.29	3.344	24.682	0.1	-38	105
M3	1.88	0.49	3.344	2.763	1.2	22	118
M4	10.12	0.29	3.344	24.682	0.1	-38	105

Table 1.6: Transistor small-signal and thermal noise parameters.

Transistor	$G_{spec}$ [ $\mu A/V$ ]	$G_{ms}$ [ $\mu A/V$ ]	$G_m$ [ $\mu A/V$ ]	$G_{ds}$ [ $nA/V$ ]	$\gamma_n$
M1	106.796	75.656	59.508	529.950	0.724
M2	953.893	115.312	90.700	877.208	0.659
M3	106.796	75.656	59.508	529.950	0.724
M4	953.893	115.312	90.700	877.208	0.659

 


Figure 1.9: Schematic used for the simulation of the transfer function.

### 1.3 Simulations

We can now check the design by simulation using the circuit shown in Figure 1.9. The purpose of  $M_3$  and  $M_4$  is to set the DC gate voltage of  $M_1$  such that its current is equal to the bias current. Of course  $M_3$  is identical to  $M_1$  and  $M_4$  is identical to  $M_2$ .

We first will check the operating point. The node voltages are given in Table 1.7. We can check that all transistors are biased in saturation. The transistor operating point information are given in Table 1.8 and Table 1.9. We see that the simulated transconductances are very close to the theoretical values given in Table 1.6.

Table 1.7: OTA node voltages with the OTA in open-loop without offset correction.

Node	Voltage
vdd	1.8
in	0.527778
out	0.527778
vb2	0.65
1	0.176378
2	0.176378
3	0.527778

Table 1.8: Large-signal operating point information extracted from ngspice .op file for each transistor.

Transistor	$I_D$ [nA]	$I_{spec}$ [nA]	$IC$ [-]	$n$ [-]	$V_{DSsat}$ [mV]
M1	3.344	3.182	1.060	1.27	157
M2	3.344	33.928	0.099	1.27	120
M3	3.344	3.182	1.060	1.27	157
M4	3.344	33.928	0.099	1.27	120

Table 1.9: Small-signal operating point information extracted from ngspice .op file for each transistor.

Transistor	$G_m$ [ $\mu A/V$ ]	$G_{ms}$ [ $\mu A/V$ ]	$G_{ds}$ [nA/V]
M1	60.093	77.541	878.705
M2	93.586	117.423	992.781
M3	60.093	77.541	878.705
M4	93.586	117.423	992.781

### 1.3.1 Transfer function

We now can simulate the transfer function which is plotted in Figure 1.10. We see that the simulation results are close to the theoretical values. The  $GBW$  is slightly lower than specs despite the simulated transconductance  $G_{m1}$  is larger. This is coming from the self-loading. Indeed, since  $M_2$  is biased in weak inversion, it is a fairly large transistor and therefore its parasitic capacitance at the drain adds to the load capacitance. We could estimate this parasitic capacitance and add it to the load capacitance.

 


Figure 1.10: Simulated gain response compared to theoretical estimation.

### 1.3.2 Input-referred noise

We can compare the theoretical input-referred noise to that obtained from simulations. The simulation results are presented in Figure 1.11.

The simulation confirms that, below the gain-bandwidth product  $GBW = 10$  MHz, the square root of the input-referred flicker noise of  $M_2$  is about 40 dB lower than that of  $M_1$ .

 


Figure 1.11: Simulated input-referred noise PSD compared to theoretical estimation.

## 2 Regulated cascode

 


Figure 2.1: Schematic of the regulated cascode.

The schematic of Figure 2.1 corresponds to the regulated cascode, where an additional CS gain stage  $M_3$  is added.

### 2.1 Small-signal analysis

 


Figure 2.2: Small-signal schematic of the regulated cascode.

The small-signal equivalent schematic of the regulated cascode of Figure 2.1 is presented in Figure 2.2.

Solving the KCL equations accounting for all the output conductances leads to the full expression of the equivalent transconductance given by

$$G_{meq} = G_{m1} \cdot \frac{G_{m2} G_{m3} + G_{ds3} (G_{ms2} + G_{ds2})}{G_{m2} G_{m3} + G_{ds3} (G_{ms2} + G_{ds2} + G_{ds1})} \quad (2.1)$$

which for  $G_{ms2} \gg G_{ds2}, G_{ds1}$  reduces to

$$G_{meq} \cong G_{m1}. \quad (2.2)$$

This is the same result as the cascode stage.

The output conductance accounting for all transistor's output conductances is given by

$$G_{out} = \frac{G_{ds1} G_{ds2} G_{ds3}}{G_{m2} G_{m3} + G_{ds3} (G_{ms2} + G_{ds2} + G_{ds1})}, \quad (2.3)$$

which for  $G_{ms2} \gg G_{ds2}, G_{ds1}$  reduces to

$$G_{out} \cong G_{ds1} \cdot \frac{G_{ds2}}{G_{m2}} \cdot \frac{G_{ds3}}{G_{m3}}. \quad (2.4)$$

Equation (2.4) shows that the output conductance of the regulated cascode is equal to the output conductance of  $M_1$  divided by the square of a transistor self-gain, i.e.  $(G_m/G_{ds})^2$ , this is  $G_m/G_{ds}$  smaller than that of the simple cascode.

The voltage gain is given by

$$A_v \triangleq \frac{\Delta V_{out}}{\Delta V_{in}} = -\frac{G_{meq}}{G_{out}} = -G_{m1} \cdot \frac{G_{m2} G_{m3} + G_{ds3} (G_{ms2} + G_{ds2})}{G_{ds1} G_{ds2} G_{ds3}}, \quad (2.5)$$

which for  $G_{ms2} \gg G_{ds2}, G_{ds1}$  and reduces to

$$A_v \cong -\frac{G_{m1}}{G_{ds1}} \cdot \frac{G_{m2}}{G_{ds2}} \cdot \frac{G_{m3}}{G_{ds3}}. \quad (2.6)$$

Equation (2.6) shows that the voltage gain of the regulated cascode is equivalent of that of a cascade of three stages, i.e.  $(G_m/G_{ds})^3$ . However, this gain is achieved at lower current since the driver transistor  $M_1$  and the cascode transistor  $M_2$  share the same current (current reuse).

## 2.2 Noise analysis

 


Figure 2.3: Small-signal schematic of the regulated cascode including the noise sources.

The equivalent small-signal circuit of the regulated cascode including all the noise current sources for the calculation of the noise is shown in Figure 2.3. The output noise current is given by

$$I_{nout} = H_{n1} \cdot I_{n1} + H_{n2} \cdot I_{n2} + H_{n3} \cdot I_{n3}. \quad (2.7)$$

where

$$H_{n1} = \frac{G_{m2} G_{m3} + G_{ds3} (G_{ms2} + G_{ds2})}{G_{m2} G_{m3} + G_{ds3} (G_{ms2} + G_{ds1} + G_{ds2})} \cong 1, \quad (2.8)$$

$$H_{n2} = \frac{G_{ds1} G_{ds3}}{G_{m2} G_{m3} + G_{ds3} (G_{ms2} + G_{ds1} + G_{ds2})} \cong \frac{G_{ds1} G_{ds3}}{G_{m2} G_{m3}}, \quad (2.9)$$

$$H_{n3} = -\frac{G_{m2} G_{ds1}}{G_{m2} G_{m3} + G_{ds3} (G_{ms2} + G_{ds1} + G_{ds2})} \cong -\frac{G_{ds1}}{G_{m3}}. \quad (2.10)$$

Equation (2.8) shows that the noise of  $M_1$  is transferred directly to the output. Equation (2.9) shows that the noise of  $M_2$  is divided by the square of a transistor self-gain, i.e. divided by  $(G_m/G_{ds})^2$ . Finally, the noise coming from  $M_3$  is divided by  $G_m/G_{ds}$ . This means that the noise coming from  $M_2$  and  $M_3$  are much smaller than the noise coming from  $M_1$  and can usually be neglected. We still will derive the output and input-referred noise accounting for all contributions.

The output noise conductance is given by

$$G_{nout} = |H_{n1}|^2 \cdot G_{n1} + |H_{n2}|^2 \cdot G_{n2} + |H_{n3}|^2 \cdot G_{n3} \quad (2.11)$$

where  $G_{ni}$  is given by (1.9).

The input-referred noise is obtained by dividing  $G_{nout}$  by  $G_{meq}^2$ , resulting in

$$R_{nin} = \frac{G_{nout}(f)}{G_{meq}^2}. \quad (2.12)$$

It can be decomposed into a thermal and flicker noise component according to

$$R_{nin} = R_{nt} + R_{nf}(f) \quad (2.13)$$

$R_{nt}$  is the total input-referred thermal noise resistance which can be written as

$$R_{nt} = \frac{\gamma_{n1}}{G_{m1}} \cdot (1 + \eta_{th}), \quad (2.14)$$

where  $\eta_{th}$  represents the contributions of  $M_2$  and  $M_3$  to  $R_{nt}$  relative to that of  $M_1$

$$\eta_{th} \cong \frac{\gamma_{n2}}{\gamma_{n1}} \cdot \frac{G_{ds1}^2 G_{ds3}^2}{G_{m1} G_{m2} G_{m3}^2} + \frac{\gamma_{n3}}{\gamma_{n1}} \cdot \frac{G_{ds1}^2}{G_{m1} G_{m3}}. \quad (2.15)$$

$\eta_{th}$  allows to compare the contributions of  $M_2$  and  $M_3$  to that of  $M_1$ . It confirms what we already have mentioned above, namely that the contribution of  $M_2$  (first term in (2.15)) is completely negligible since it is inversely proportional to  $(G_m/G_{ds})^4$ . The contribution of  $M_3$  (second term in (2.15)) is also very small since it is inversely proportional to  $(G_m/G_{ds})^2$ .

The input-referred flicker noise resistance is given by

$$R_{nf} = \frac{\rho_n}{f W_1 L_1} \cdot (1 + \eta_{fl}), \quad (2.16)$$

where  $\eta_{fl}$  represents the contributions of  $M_2$  and  $M_3$  to  $R_{nf}$  relative to the that of  $M_1$

$$\eta_{fl} \cong \left( \frac{G_{ds1}}{G_{m1}} \cdot \frac{G_{ds3}}{G_{m3}} \right)^2 \cdot \frac{W_1 L_1}{W_2 L_2} + \left( \frac{G_{ds1}}{G_{m1}} \right)^2 \cdot \frac{W_1 L_1}{W_3 L_3}. \quad (2.17)$$

Similarly to the thermal noise, assuming that  $M_1$ ,  $M_2$  and  $M_3$  have all about the same gate area, (2.17) shows that the contribution of  $M_2$  (first term in (2.17)) is completely negligible since it is inversely proportional to  $(G_m/G_{ds})^4$ . The contribution of  $M_3$  (second term in (2.17)) is also very small since it is inversely proportional to  $(G_m/G_{ds})^2$ .

The equivalent noise excess factor of the regulated cascode can then be written as

$$\gamma_{neq} \triangleq G_{meq} \cdot R_{nt} \cong \gamma_{n1} \cdot (1 + \eta_{th}) \cong \gamma_{n1}. \quad (2.18)$$

This shows that, similarly to the cascode gain stage, the noise of the regulated cascode is dominated by the contribution of the driver transistor  $M_1$ .