

EE-429

Fundamentals of VLSI Design

Alternative Logic Styles

Andreas Burg

Different Logic Styles


- **Static CMOS is the most popular logic style due to its**
 - Robustness against noise (good noise margins)
 - Robust against variations in transistor parameters (un-ratioed logic)
 - Almost-zero static power consumption
 - Ability to easily cascade multiple logic stages of any type of gates
 - Ease of use and very good suitability for abstracting delay models (good for EDA)
- **Other styles have been proposed to improve some short-comings of CMOS**
 - Limited fanin (number of inputs to a single-stage gate)
 - Inability to describe certain Boolean functions in a single logic stage
 - Notable area overhead due to the need for complementary PMOS and NMOS
 - Imbalance between PMOS and NMOS stage (differences in mobility)

Pass-Transistor Logic

- **CMOS always drives gate-output from the rails**
 - Good for output noise margins
 - Less obvious when outputs are trivial functions of the inputs (e.g., MUX) or for some basic non-unate gates such as XORs
- **Solution: drive output from one of the inputs using switches made from NMOS or PMOS transistors**

- **Systematic construction from Boolean equations using Shannon expansion**

 
- Start from Boolean expression: $f(x_1, x_2, \dots, x_n)$ and re-write as $f(x_1, x_2, \dots, x_n) = x_1 \cdot f(1, x_2, \dots, x_n) + \bar{x}_1 \cdot f(0, x_2, \dots, x_n)$




$$\begin{aligned} f(x, y) &= \bar{x} + x \cdot y = \\ &= x \cdot (0 + 1 \cdot y) + \bar{x} \cdot (1 + 0 \cdot y) = \\ &= x \cdot (y) + \bar{x} \cdot (1) \end{aligned}$$

Pass-Transistor Logic

 - **Problem: VT drop as NMOS and PMOS lack the ability to drive a strong '1' and a strong '0' respectively**




 - **Solution: drive output from one of the inputs** using switches made from **Transmission gates** instead of **NMOS or PMOS transistors**



 - **Example 2-input MUX**

- Doubles the number of transistors
- Adds PMOS to an otherwise NMOS-only circuit
- Need for inverted inputs



Pass-Transistor Logic


- **Systematic construction** from Boolean equations using **Shannon expansion**

- **Many disadvantages:** with various solutions

- Logic output can depend directly on the input: **drive strength degrades** gradually across multiple logic stage
Solution **CMOSTG**: regularly buffer outputs with CMOS inverters


- Typically **requires** inputs and **also inverted inputs**
Solution (**DPL**): generate both outputs and inverted outputs

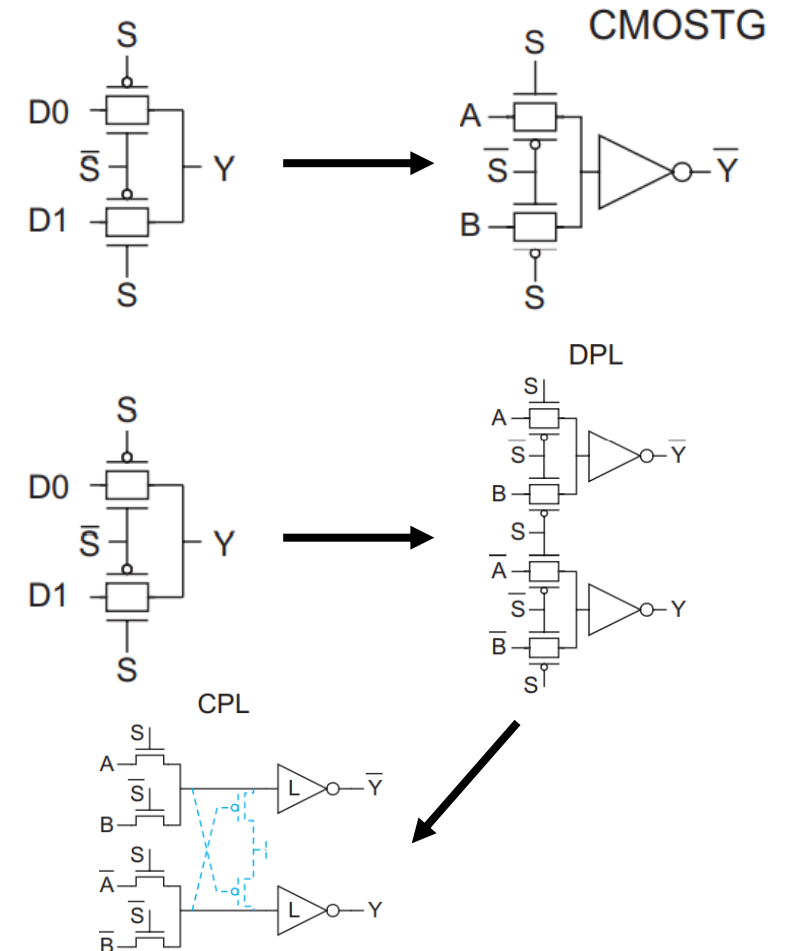- Large **overhead from transmission gates**
Solution (**CPL**): accept a V_T drop in one branch of the differential (complementary) output



Ratioed Logic Gates

- **CMOS gates “waste” 50% of the transistors** to cut one of the supplies when the other supply rail is connected to the output
- **Solution: replace pull-up or pull-down switch** with constant “resistance” that is
 - Sufficiently strong to **pull** the output **when it is not pulled actively to the other side**
 - Sufficiently weak to **marginally impact** the output **when it is actively pulled to the other side**
- **Especially attractive to remove the larger PMOS**




 


Pseudo NMOS Logic

- **Replaces PMOS network with an always weakly-on biased PMOS**



- Constant power consumption due to short-circuit when output is low
- Fall time determined by sizing of the NMOS network
- Rise time determined by sizing of the always-on PMOS
 - Determines static power consumption
 - Strong PMOS (short rise time) degrades output low-level noise margin

- **Example: inverter**

    

Dynamic Logic


- **Drawback of Ratioed Logic: short-circuit current** (for one of the outputs)
 - **Limits the drive strength** of the always-on (pull-up or pull-down) device
- **Solution: operation in two phases separates pull-up from pull-down**
 - **Phase 1** pre-charge (pre-discharge): always pull-up (pull-down) (optional footer prevents short-circuit during precharge)
 - **Phase 2** evaluate output: conditionally pull-down (pull-up) depending on inputs

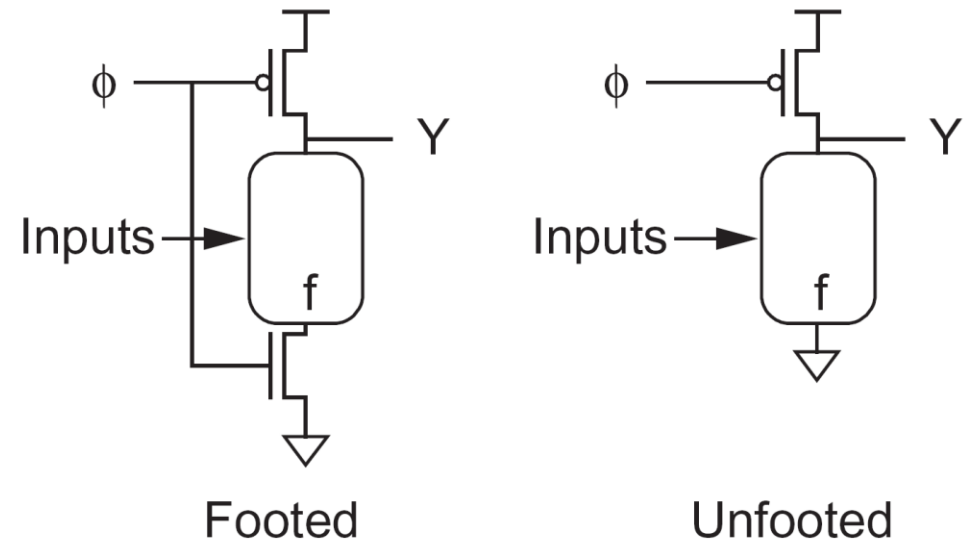 


Dynamic Logic Examples

Unfooted


Inverter

 

NAND2

 

NOR2

 

Footed

