


Noise Part 1: Time and Frequency Analysis
Noise Part 2: Transistor-level analysis

Analog ICs
Adil KOUKAB


Chap2-Outline1 : Noise in Devices

- MOSFET Channel Thermal Noise
- MOSFET Flicker Noise
- Circuit-Noise Analysis and Modeling
 - Example: Noise and SNR in CS Amplifier
- Input-Referred Noise
 - Effect of source impedance
- Examples: Noise analyses in classical single-stage amplifiers (CS, CG, and CS).

Channel Thermal Noise

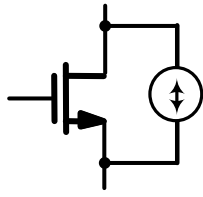
$$\overline{i_n^2} = 4kT\gamma g_m \text{ [A}^2\text{/ Hz]} \\ \text{(in saturation)}$$

Channel current thermal noise

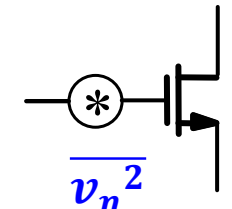
$$\overline{v_n^2} \\ = 4kT\gamma \frac{1}{g_m} \text{ [V}^2\text{/ Hz]}$$


Input Voltage representation

- With $\gamma \approx 2/3$ for long channel MOSFETs ($\rightarrow 1$ for modern technologies)
- nMOS has a **larger** g_m ($\mu_e > \mu_h$) and so **larger channel current thermal noise**



Should we minimize or maximize g_m ?


Flicker Noise

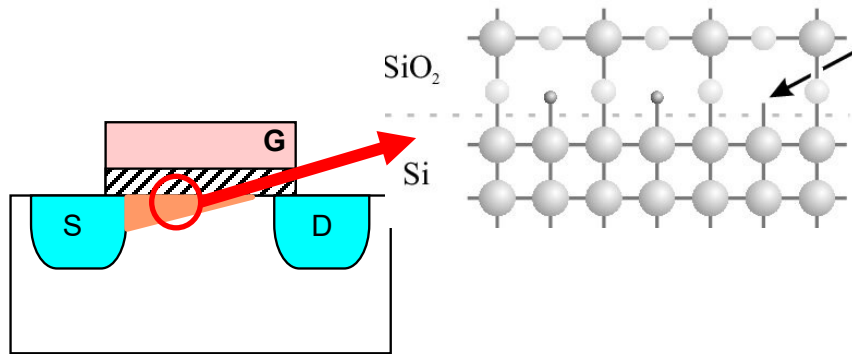

Dangling Bonds

→ Trapping and de-trapping mobile carriers


→ Flicker noise

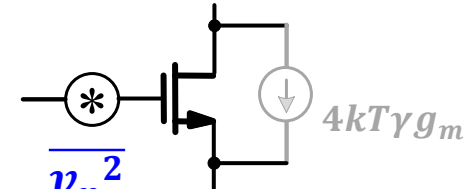


$$= \frac{K}{C_{ox}LW} \cdot \frac{1}{f} \quad [\text{V}^2/\text{Hz}]$$

- K is a constant empirically determined
- Big transistors have less flicker noise
- K is generally lower for PMOS
- Ex: The total noise power from f_1 to f_2 [V²]:
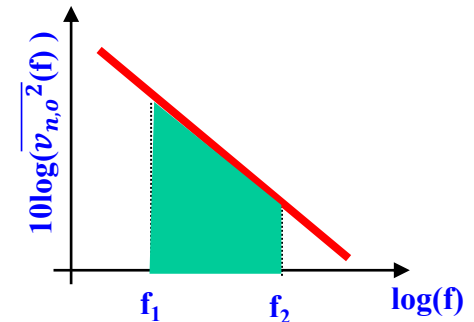
$$\overline{v_n^2} = \int_{f_1}^{f_2} \frac{K}{C_{ox}LW} \cdot \frac{1}{f} df = \frac{K}{C_{ox}LW} \cdot \text{Ln} \left(\frac{f_2}{f_1} \right) \quad [\text{V}^2]$$



Total Noise in MOSFETs

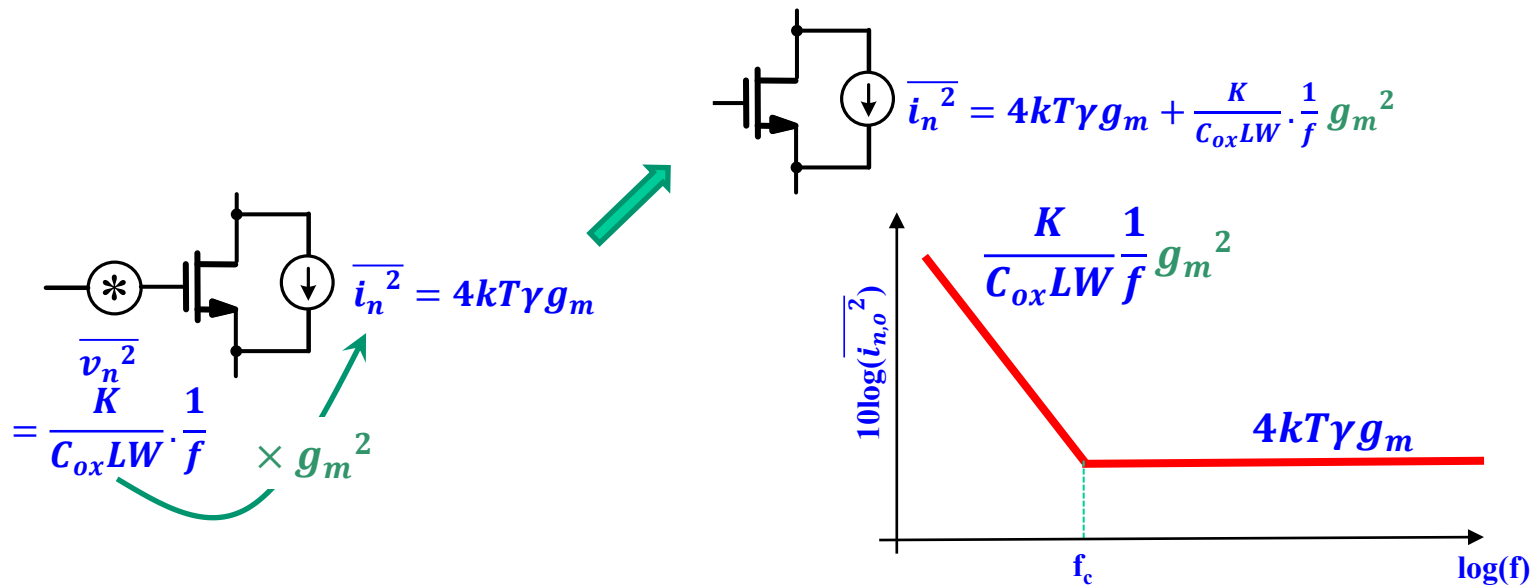


f_c : Flicker noise “corner frequency”

$$f_c = \frac{K}{C_{ox}WL} g_m \frac{3}{8kT} \quad (\text{usually between 500 kHz, 1 MHz})$$

- Flicker noise is detrimental for low-frequency circuits
- Or if it is upconverted the signal Band.


nMOS vs pMOS

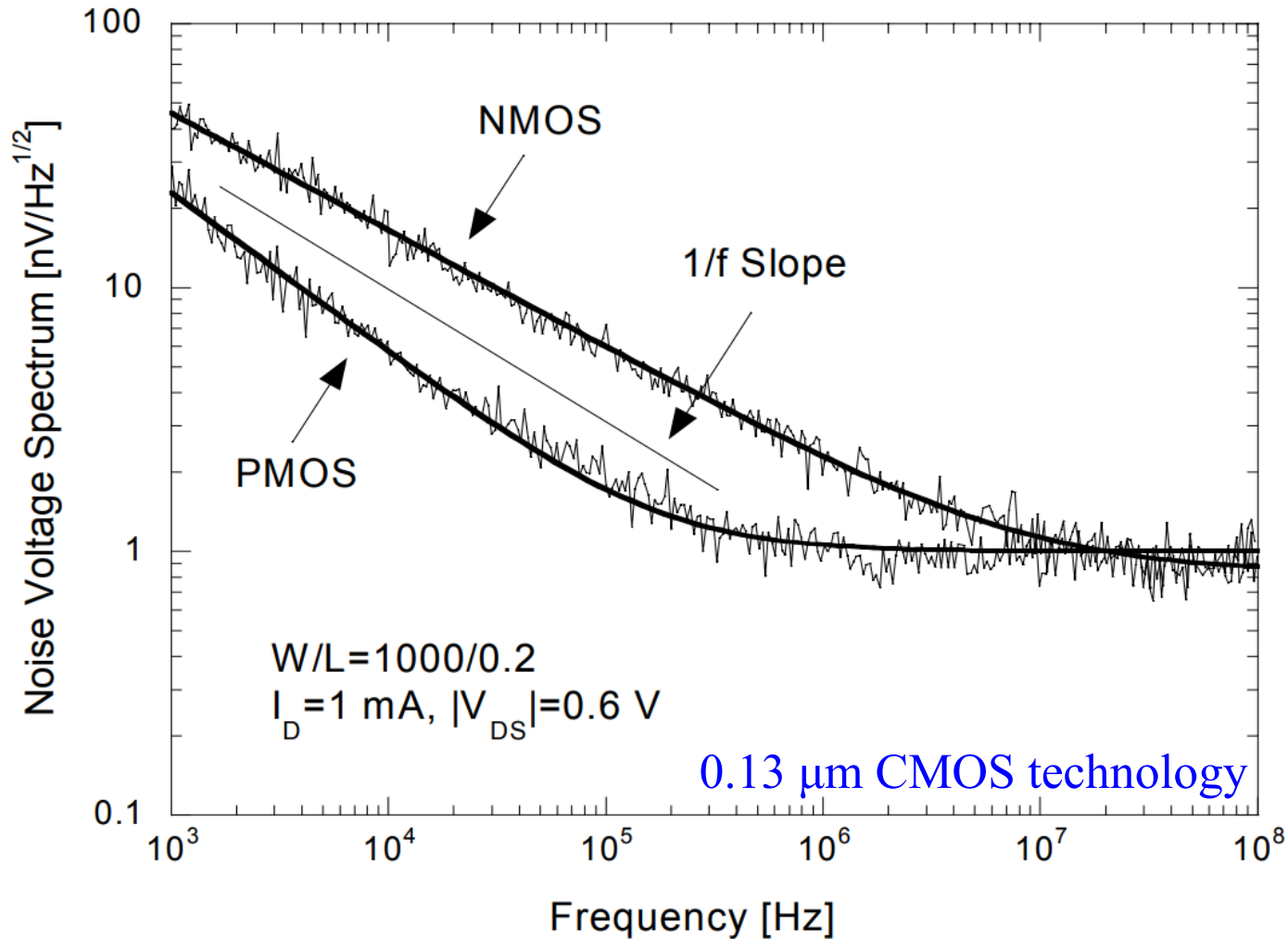

Chap2-Outline1 : Noise in Devices

- MOSFET Channel Thermal Noise
- MOSFET Flicker Noise
- Circuit-Noise Analysis and Modeling
 - Example: Noise and SNR in CS Amplifier
- Input-Referred Noise
 - Effect of source impedance
- Examples: Noise analyses in classical single-stage amplifiers (CS, CG, and CS).

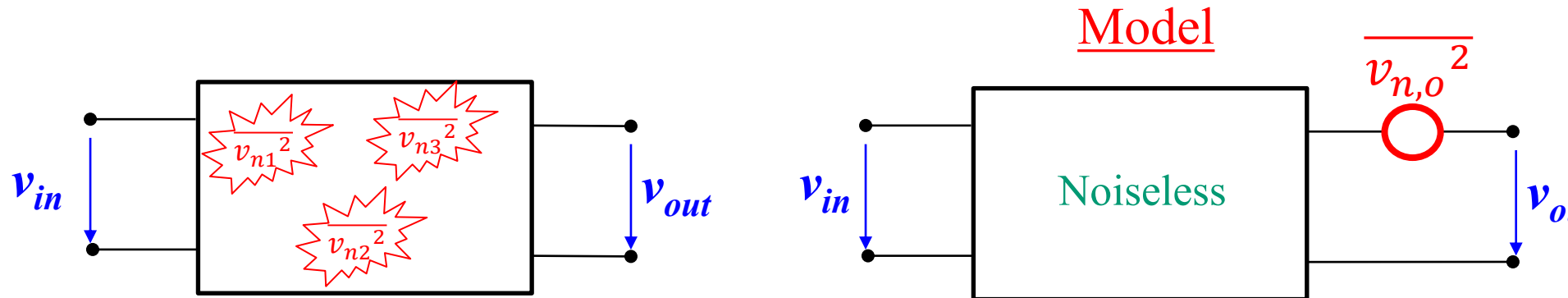Circuit-Noise Analysis and Modeling Procedure




- Identify noise sources.
- Determine ($H_i(s)$) from v_{ni}^2 to the output.
- Add all of the contributions to the output

The diagram shows the mathematical combination of noise sources. Three noise sources $v_{n,1}^2(f)$, $v_{n,2}^2(f)$, and $v_{n,3}^2(f)$ are each multiplied by their respective transfer function magnitudes $|H_1|^2$, $|H_2|^2$, and $|H_3|^2$. These contributions are then summed at a junction (represented by a circle with a plus sign) to produce the total output noise power spectral density:

$$\overline{v_{n,o}^2}(f) = \sum_{j=1}^3 \overline{v_{n,j}^2}(f) |H_j(f)|^2$$

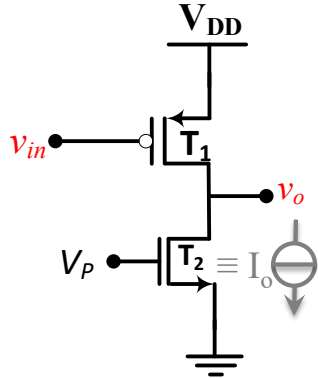Example 1: Noise in CS Amplifier

- Determine the output thermal noise voltage of a common source amplifier and deduce the impact of g_{m1} and g_{m2} on noise performance.




$$\overline{i_{n1,2}^2} = 4kT\gamma g_{m1,2} \text{ [A}^2/\text{ Hz]}$$

$$\overline{v_{n,o}^2} = 4kT\gamma (g_{m1} + g_{m2})(r_{o1} // r_{o2})^2 \text{ [V}^2/\text{ Hz]}$$

Output Noise \searrow if $g_{m1} \searrow$ and $g_{m2} \searrow$

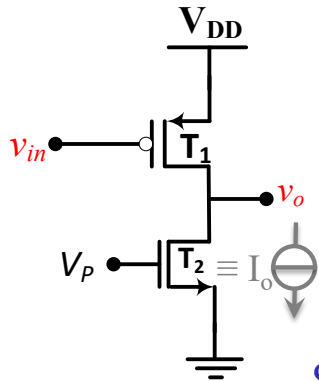Example 2: SNR of a CS Amplifier

- Reevaluate the noise performance using the signal-to-noise ratio (SNR).



$$|A_v| = g_{m1} r_{o1} // r_{o2}$$

$$\overline{v_{n,o}^2} = 4kT\gamma(g_{m1} + g_{m2})(r_{o1} // r_{o2})^2 \text{ [V}^2/\text{Hz]}$$

$$SNR = \frac{\overline{v_o^2}}{\overline{v_{n,o}^2}} = \frac{|A_v|^2 \overline{v_i^2}}{\overline{v_{n,o}^2}} = \frac{g_{m1}^2}{4kT\gamma(g_{m1} + g_{m2})\Delta f} \overline{v_i^2} = \frac{1}{\Delta f} \frac{g_{m1}}{4kT\gamma\left(1 + \frac{g_{m2}}{g_{m1}}\right)} \overline{v_i^2}$$


$SNR \nearrow$ if $g_{m1} \nearrow$ and $g_{m2} \searrow$

Conclusion: improve noise performances \rightarrow maximize g_m of active transistor and minimize g_m of load (current source)

Chap2-Outline1 : Noise in Devices

- MOSFET Channel Thermal Noise
- MOSFET Flicker Noise
- Circuit-Noise Analysis and Modeling
 - Example: Noise and SNR in CS Amplifier
- Input-Referred Noise
 - Effect of source impedance
- Examples: Noise analyses in classical single-stage amplifiers (CS, CG, and CS).

Input-Referred Noise

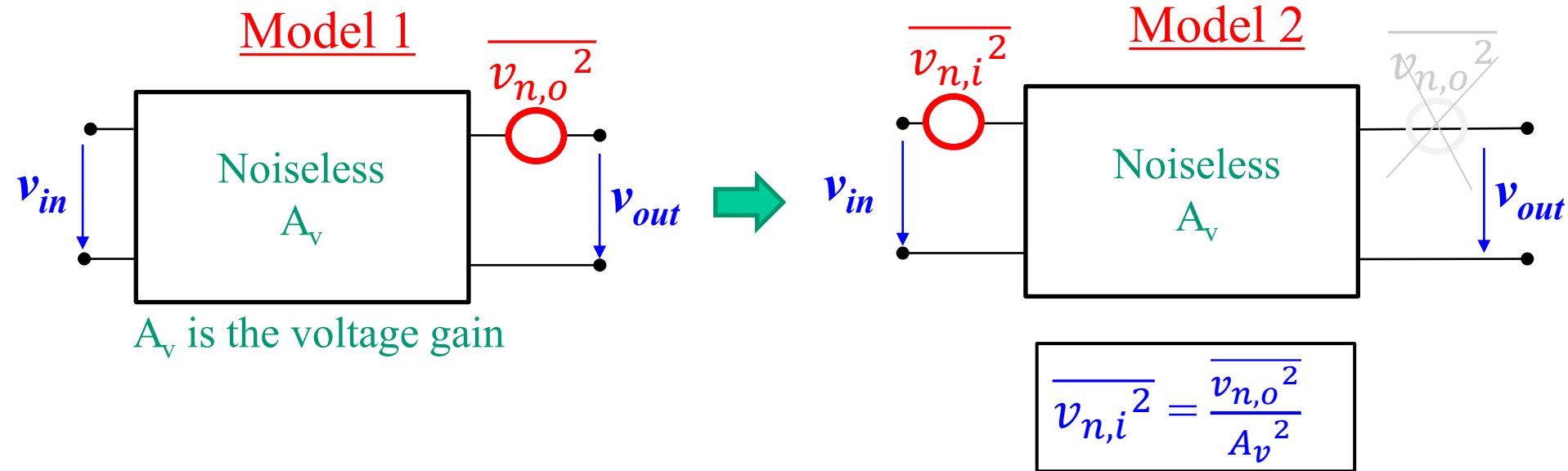


- Why is $\overline{v_{n,i}^2}$ important?:

- Optimizing $\overline{v_{n,o}^2}$ can degrade the gain (A_v) and so the desired signal

→ Better optimize $\overline{v_{n,i}^2}$ (just like SNR)

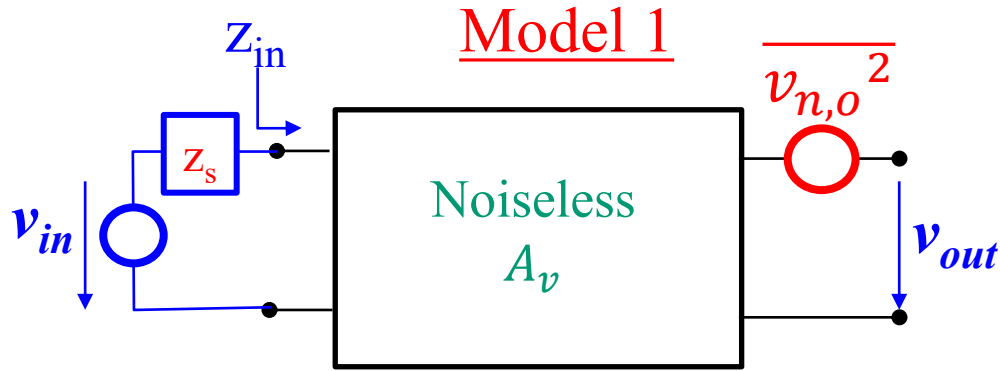
Effect of source Impedance on Input-Referred Noise



$$\overline{v_{n,i}^2} = \frac{\overline{v_{n,o}^2}}{\left(A_v \frac{z_{in}}{z_{in} + z_s}\right)^2}$$



Model 2

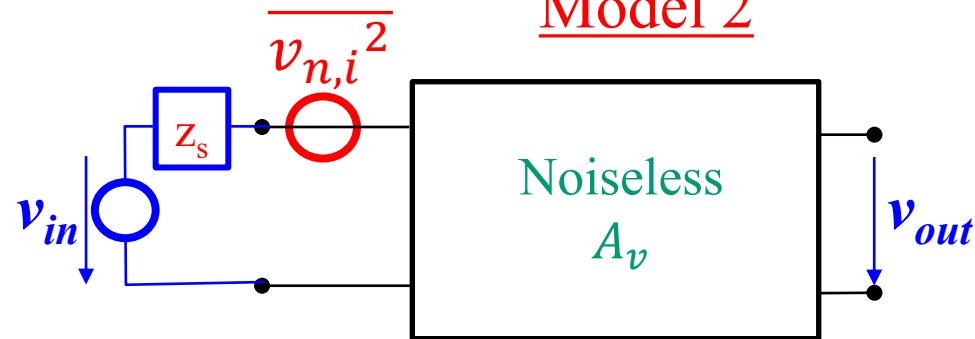


Note:

Z_s have no effect if $z_{in} \rightarrow \infty$
(e.g. CS and CD at low-frequency)

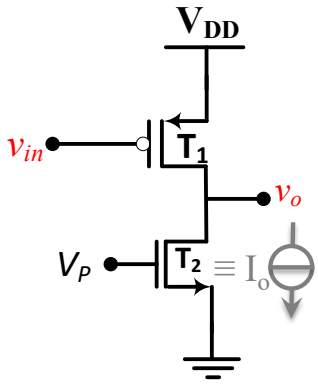Example 3: Input-referred Noise in CS Amplifier

- Determine the input-referred voltage noise of CS amp at **low frequency** (flicker and thermal).




$$|A_v| = g_{m1} r_{o1} // r_{o2}$$

$$\overline{v_{n,o}^2} = 4kT\gamma(g_{m1} + g_{m2})(r_{o1} // r_{o2})^2 + |A_v|^2 \frac{K}{C_{ox}(LW)_1} \cdot \frac{1}{f} + \left(\frac{g_{m2}}{g_{m1}}\right)^2 |A_v|^2 \frac{K}{C_{ox}(LW)_2} \cdot \frac{1}{f}$$

$$\overline{v_{n,i}^2} = \frac{\overline{v_{n,o}^2}}{|A_v|^2} = 4kT\gamma \frac{1}{g_{m1}} \left(1 + \frac{g_{m2}}{g_{m1}}\right) + \frac{K}{C_{ox}(LW)_1} \cdot \frac{1}{f} + \left(\frac{g_{m2}}{g_{m1}}\right)^2 \frac{K}{C_{ox}(LW)_2} \cdot \frac{1}{f} \quad [\text{V}^2/\text{Hz}]$$

Conclusion: improve noise performances \rightarrow maximize g_m of active transistor and minimize g_m of load (current source)

Complete Input-Referred Noise Model : Valid $\forall z_s$

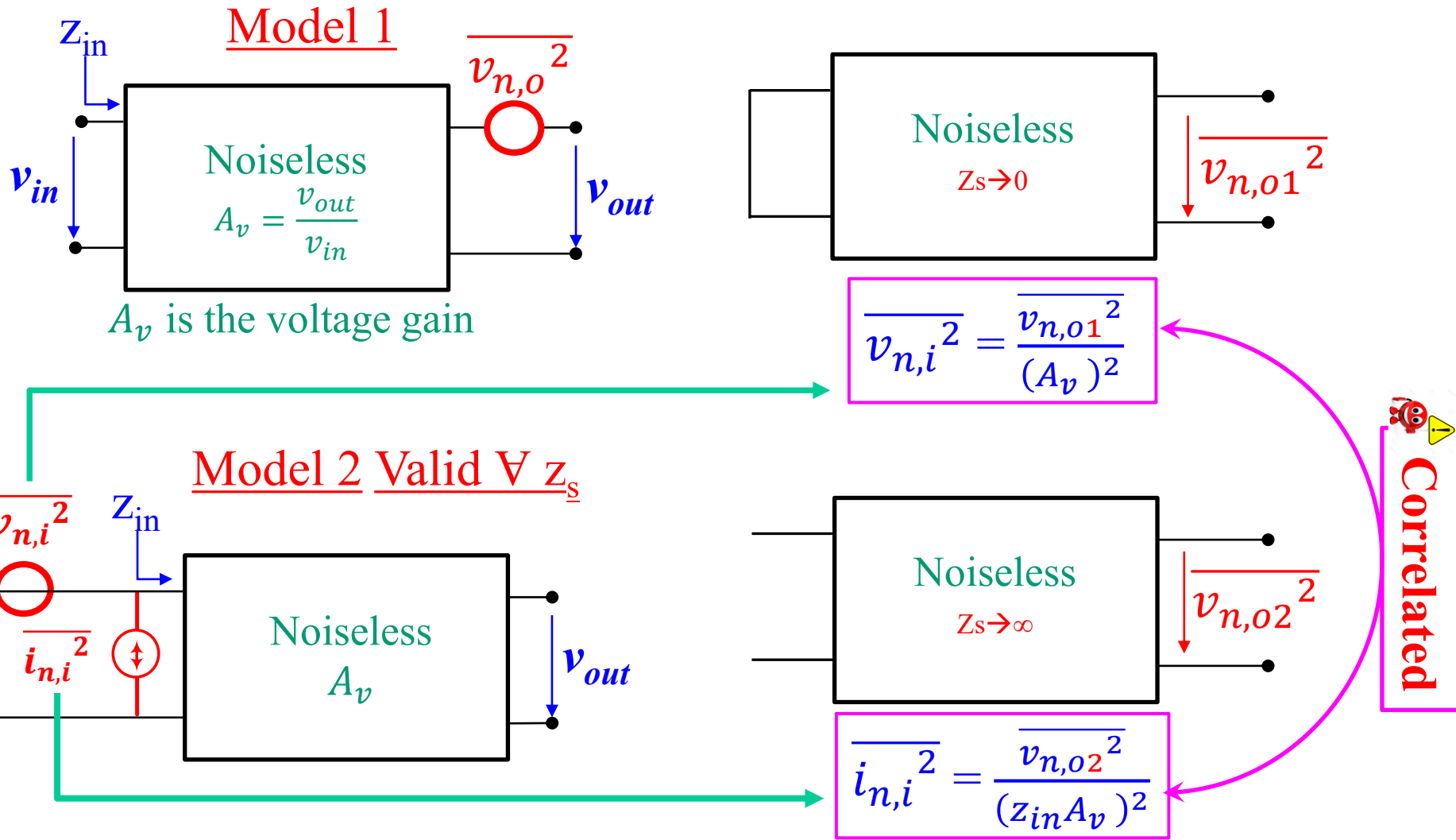


Chap2-Outline1 : Noise in Devices

- MOSFET Channel Thermal Noise
- MOSFET Flicker Noise
- Circuit-Noise Analysis and Modeling
 - Example: Noise and SNR in CS Amplifier
- Input-Referred Noise
 - Effect of source impedance
- Examples: Noise analyses in classical single-stage amplifiers (CS, CG, and CS).

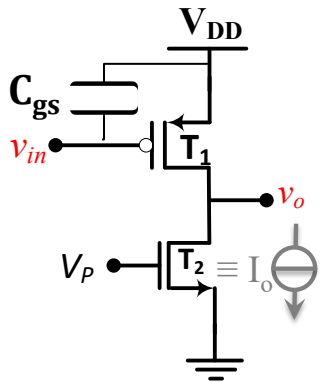Example 3: Noise in CS Amplifier

- Determine the input-referred current noise of CS amp at high frequency (consider C_{gs} capacitor).




$$Z_{in} = \frac{1}{j2\pi f C_{gs}}$$

$$\begin{aligned} \overline{i_{n,i}^2} &= \frac{\overline{v_{no,2}^2}}{|Z_{in} A_v|^2} = (2\pi f C_{gs})^2 4kT\gamma \frac{1}{g_{m1}} \left(1 + \frac{g_{m2}}{g_{m1}}\right) \\ &\quad + (2\pi f C_{gs})^2 \left(\frac{g_{m2}}{g_{m1}}\right)^2 \frac{K}{C_{ox}(LW)_2} \cdot \frac{1}{f} \text{ [A}^2/\text{ Hz]} \end{aligned}$$

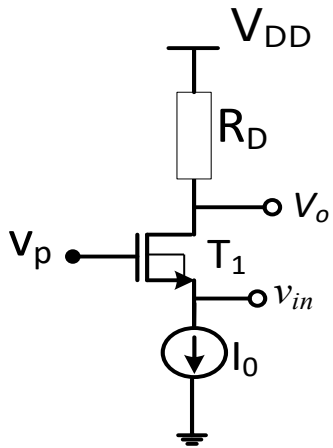Example 4: Noise in CG Amplifier

- Determine the output and input-referred thermal noise voltage and current of a CG amp (neglect the noise of I_0).



$$|A_v| = g_{m1} r_{o1} // R_D \approx g_{m1} R_D$$

$$Z_{in} = \frac{1}{g_{m1}} \left(1 + \frac{R_D}{r_{o1}} \right) // r_{o2} \approx \frac{1}{g_{m1}}$$


$$\overline{v_{n,o}^2} = 4kT\gamma g_{m1} R_D^2 + 4kT R_D$$

$$\overline{v_{n,i}^2} = \frac{\overline{v_{n,o1}^2}}{|A_v|^2} = 4kT\gamma \frac{1}{g_{m1}} + 4kT \frac{1}{R_D (g_{m1})^2} \quad (\text{short-circuit the input})$$

$$\overline{i_{n,i}^2} = \frac{\overline{v_{n,o2}^2}}{|Z_{in} A_v|^2} = 4kT \frac{1}{R_D} \quad (\text{open the input})$$

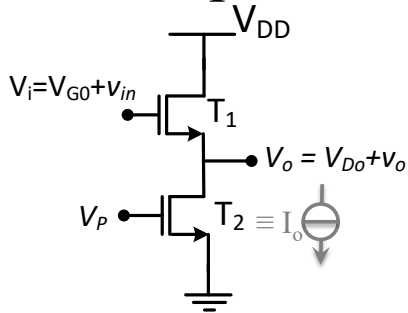Example 5: Noise in CD Amplifier (Source Follower)

- Determine the output and input-referred thermal noise of a Source Follower at low frequency (flicker and thermal) and comment on its noise performances.



$$|A_v| = 1$$

$$\overline{v_{n,o}^2} = 4kT\gamma(g_{m1} + g_{m2}) \left(\frac{1}{g_{m1}}\right)^2 + \frac{K}{C_{ox}(LW)_1} \cdot \frac{1}{f} + \frac{K}{C_{ox}(LW)_2} \cdot \frac{1}{f} \left(\frac{g_{m2}}{g_{m1}}\right)^2$$

$$\overline{v_{n,i}^2} = \frac{\overline{v_{n,o}^2}}{|A_v|^2} = 4kT\gamma \frac{1}{g_{m1}} \left(1 + \frac{g_{m2}}{g_{m1}}\right) + \frac{K}{C_{ox}(LW)_1} \cdot \frac{1}{f} + \left(\frac{g_{m2}}{g_{m1}}\right)^2 \frac{K}{C_{ox}(LW)_2} \cdot \frac{1}{f} \quad [\text{V}^2/\text{Hz}]$$

Note: $\overline{v_{n,i}^2}$ of CD is similar to CS but with no gain for the desired signal