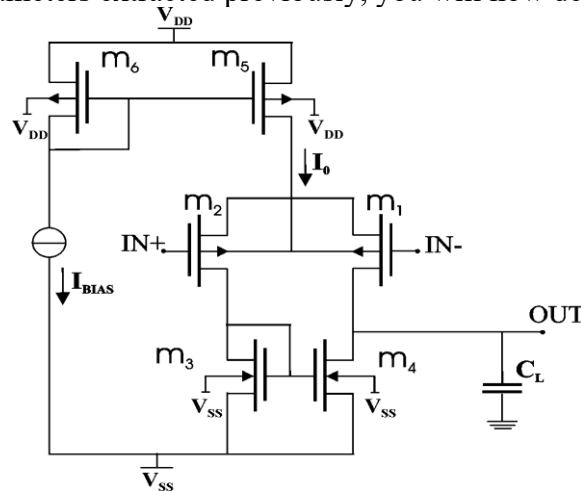


Parameter	Value Extracted	Unit	64nm CMOS Technology $V_{DD} = 1.2\text{ V}$ $V_{SS} = 0\text{ V}$	
K_p	PMOS	90		$\mu\text{A}/\text{V}^2$
	NMOS	220		
U_a	PMOS	10		$\text{V}/\mu\text{m}$
	NMOS	14		
V_{T0}	0.4	V		
n	PMOS	1.25		-
	NMOS	1.2		
C_{ox}	13	$\text{fF}/\mu\text{m}^2$		
C_{ov}	0.2	$\text{fF}/\mu\text{m}$		

1. OTA design

Using the technology parameters extracted previously, you will now design a simple OTA.



1.1. Specifications

The circuit will be designed to meet the following specifications, which will be verified by simulation.

Parameter	Unit	
	Specification	
Open-loop: Gain: A_o	$\approx 35\text{ dB (56)}$	dB
GBW: f_{GBW}	25	MHz
Slew rate: SR	20	$\text{V}/\mu\text{s}$
Load Cap: C_L	1	pF
$I_{F,5}$	10	
I_{BIAS}	10	μA

1.2. Sizing:

The OTA will now be sized. Calculate the following parameters in the proposed order.

	Parameter	Expression	Value	Unit	Guideline
Bias	I_0			μA	
	$\frac{W_5}{L_5}$			μm	$L_5 = 0.5 \mu m$
Differential pair	g_{m2}			μS	GBW
	$\frac{g_{m2}}{I_{d2}}$			V^{-1}	
	$I_{F1,2}$			-	$I_F = I_c$ is the inversion factor
					Strong or weak inversion
	$\frac{W_{1,2}}{L_{1,2}}$			-	
	R_{out}			$k\Omega$	A_o
	$L_{1,2}$			μm	$R_{out}, L_4=L_2$
	$W_{1,2}$			μm	
	$\frac{W_4}{L_4}$			-	$I_F = 10$
	L_4			μm	$L_2=L_4$
	W_4			μm	
	g_{m4}			μS	$\frac{g_m}{I_D} =$

1.3. Determine analytically

- the poles (dominant and non dominant)
- the phase margin PM
- the common mode input range $CMIR^+$ / $CMIR^-$
- the output swing

	Analytical expression	Numerical value
A [dB]		
f_{dom} [Hz]		
f_{nondom} [Hz] (neglect junction cap C_{SB}, C_{DB})		
PM [°]		
$CMIR^+$ [V]		
$CMIR^-$ [V]		
V_{OUTmax} [V]		
V_{OUTmin} [V]		
ΔV_{OUT} [V]		


1.4. Design verification & Performance simulation

Using a prepared set of test-benches, the OTA performances will be verified by simulation.


1. Open the OTA_65n schematic
2. Set all transistor sizes according to your design

 1.4.1. Operating point and Open-loop gain

- The test-bench used to simulate the Dc and AC behavior of the OTA is the following:




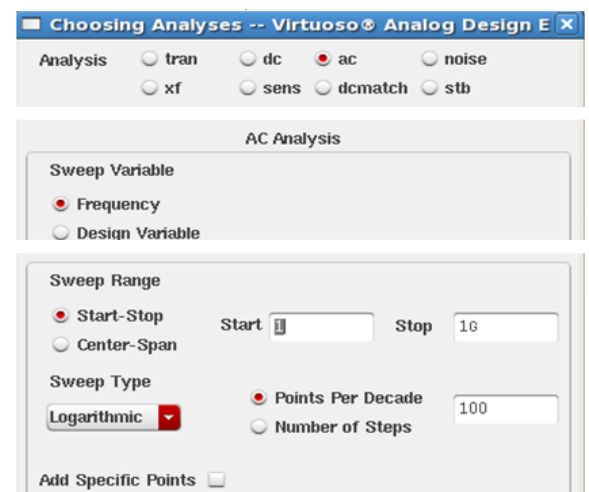1. Open the Testbench TB_OTA_DC_AC schematic
2. Explore the TB to understand how it works
3. Start the simulation environment: Launch **ADE Assembler**
4. Create New View "maestro"
5. Set **Glogal Variables** for "DC voltage, current sources and Load capacitor"
6. Define a new test choosing **DC_Analysis** and select **Save DC operation Point.** (you can change the default test name to **DC_Test**)
7. Define a new test choosing **AC_Analysis** and set the simulation parameters as shown in the snapshot on the right (you can change the default test name to **AC_Test**).
8. Define for AC_Test the following expression to be plotted:
 open loop gain ? dB20(VF("/VOUT_OL"))
 open loop phase ? phase(VF("/VOUT_OL"))
9. Save, Run and Report the values on the following schematic, and fill-in the tables below and verify that they correspond approximately to theory (your calculations).




Note: To display the simulation results

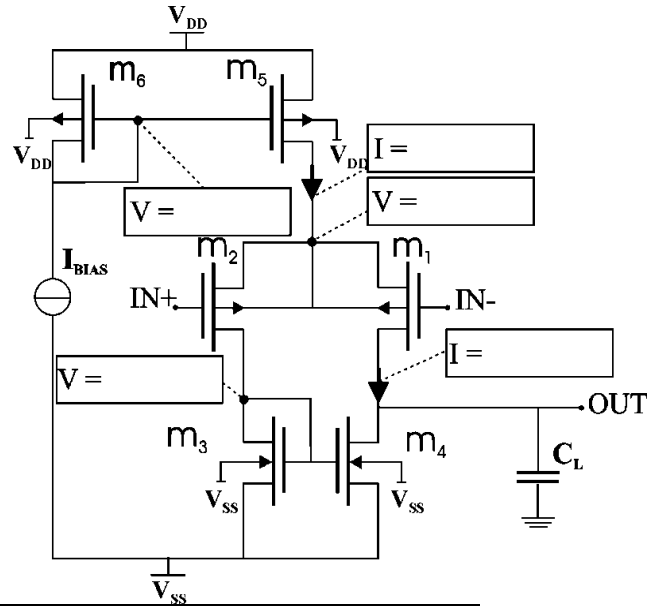- Descend in the hierarchy to the schematic level of the OTA
- Select **maestro** tab
- Select **Results** tab
- Right click on **OP_Test** and select:
 1. **Annotate**→DC Node Voltages
 2. **Annotate**→DC Operating Points



	calculated	simulated
Dominant pole [kHz]		
Non-Dom pole [MHz]		
PM [°]		
A ₀ [dB]		
f _{GBW} [MHz]		

 Provide the hand painted Bode plots for magnitude and phase:



Comment briefly on the stability:


.....

.....


.....

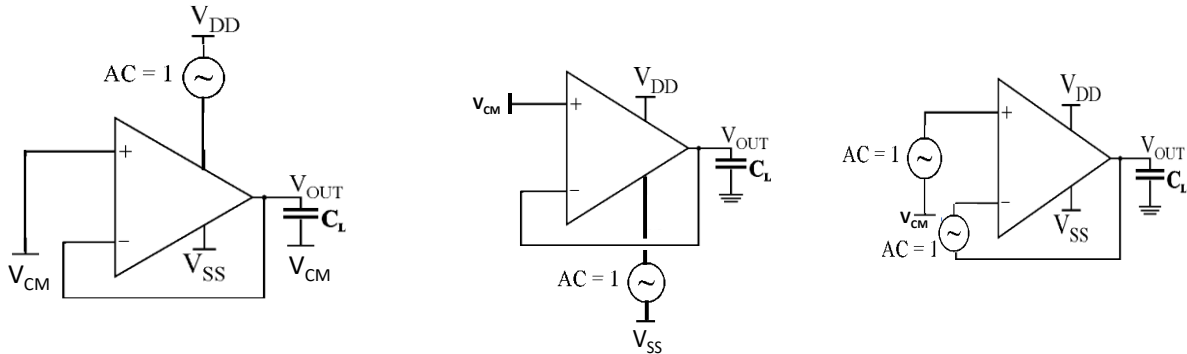1.4.2. Power supply and Common mode rejections ratio (PSSR+, PSSr- & CMRR)

The test-bench for measuring the OTA PSSR + ; PSSR- and CMRR are:



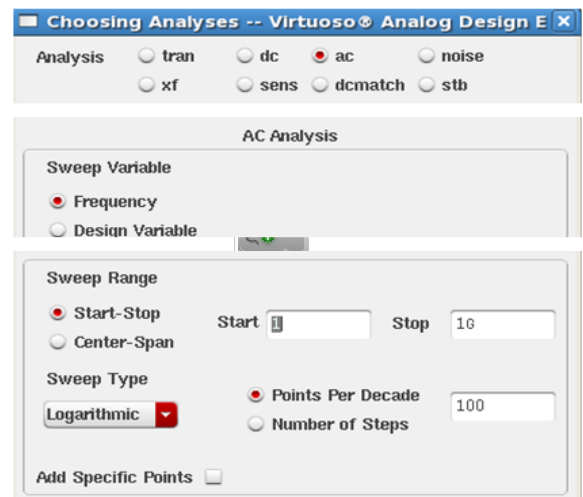1. Open the Testbench TB_OTA_PSRR_CMRR schematic
2. Explore the TB to understand how it works
3. Start the simulation environment: Launch **ADE Assembler**
4. Create New View "maestro"
5. Set **Glogal Variables** for "DC voltage, current sources and Load capacitor"
6. Define a new test choosing **AC_Analysis** and set the simulation parameters as shown in the snapshot on the right (you can change the default test name to **AC_Test2**).
7. Define for AC_Test2 the following expression to be plotted:
 $(-dB20(VF("/VOUT_PSRR+")))$
 $(-dB20(VF("/VOUT_PSRR-")))$
 $(-dB20(VF("/VOUT_CMRR")))$
8. Save, run and report the values on the following schematic, and fill-in the tables below and verify that they correspond approximately to theory (your calculations).



	Simulated @ low fréquency
PSRR+ [dB]	
PSRR- [dB]	
CMRR [dB]	

Explain briefly the equations used:

.....

.....

.....


.....

.....


.....

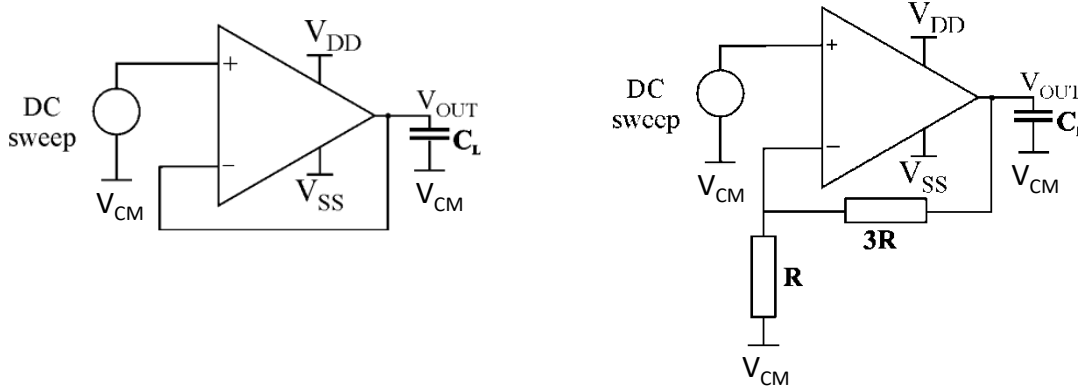1.4.3. Input common-mode range

The test-bench for measuring the OTA input common-mode range and output range are :



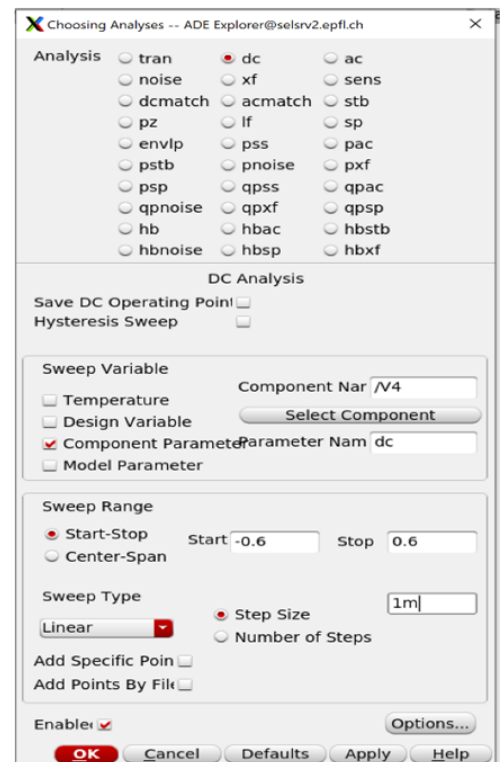1. Open the Testbench TB_OTA_CMIR_DVout
2. Explore the TB to understand how it works
3. Start the simulation environment: Launch **ADE Assembler**Create
4. New View "maestro"
5. Set **Glogal Variables** for "DC voltage, current sources and Load capacitor"
6. Define a new test and choose **DC Analysis** and set the simulation parameters as shown in the snapshot on the right (you can change the default test name to DC_Test).
7. Define the following expression to be plotted:
Common mode input range → `deriv(VDC("/VOUT_CMIR"))`
VDC("/VOUT_SW")
Output swing → `deriv(VDC("/VOUT_SW"))`
8. Save, run the simulation and fill in the table below.



Measure the input and output ranges for a maximum gain variation of -10 %



Parameter	Value		Unit
	Simulation	Optimized	
Input CMR+			V
Input CMR-			V
Output Range+			
Output Range-			

NOTE: For the Output Swing, group `/VOUT_SW` and `deriv(VDC("/VOUT_SW"))` plots in the same subwindow in Virtuoso and Analysis Waveform XL.

- Select the subwindow with the two signals
- select the `deriv(VDC("/VOUT_SW"))` signal and then select Axis → Y vs Y.

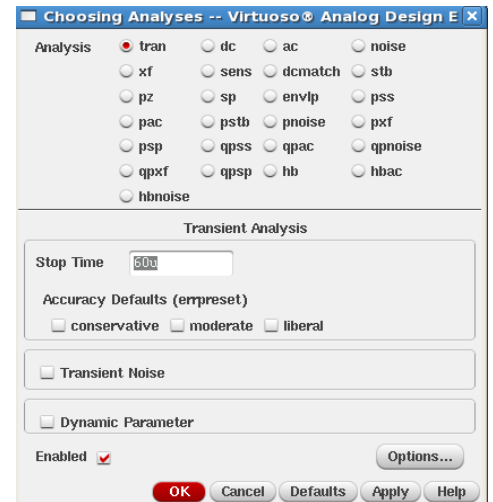 1.4.4. Slew rate

The test-bench for measuring the slew-rate is:



1. Open the Testbench_OTA_SlewRate
2. Start the simulation environment: Launch ADE Assembler
3. Open Existing View
9. Load "maestro"
10. Define a new test and choose **tran Analysis** and set the simulation parameters as shown in the snapshot on the right (you can change the default test name to SR_Test).
11. Define the following expression to be plotted:
Slew Rate \rightarrow `deriv(VT("/VOUT_SR"))`
12. Run the Simulation and fill in the table below.

Parameter	Value		Unit
	Simulation	Optimized	
SR+			V/ μ s
SR-			V/ μ s