	Author(s) Name(s) Amin Darvishzadeh, Celia Hermoso Diaz	Function Teaching Assistants
	Professor Name Dražen Dujić	Date of Release 01.10.2025
Title <b>EXERCISE 4: THREE-PHASE INVERTER MODELING</b>		
Course Name EE-465 Industrial Electronics I		

## 1 INTRODUCTION

A three-phase 2L inverter (see Fig. 1) is connected to the 3ph grid ( $V_{RMS,L-L} = 400\text{ V}$ , 50 Hz) through a RL filter. By appropriately setting the phase and magnitude of the voltage synthesized by the inverter, the power exchange with the AC grid can be modified or set.

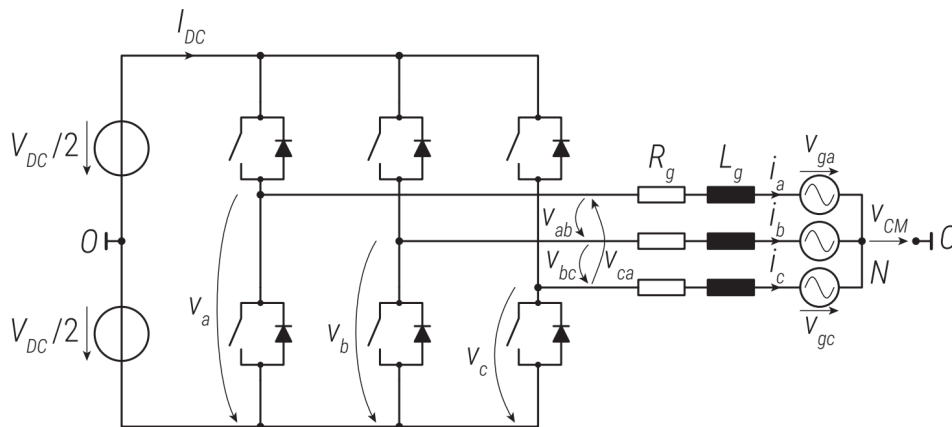


Fig. 1 PV system output stage. The input stage has been replaced by an equivalent voltage source.

## 2 TASKS DESCRIPTION

- Create a switched model of the three-phase 2L inverter as seen in the lecture and as illustrated in fig. 1.
  - A few useful elements are already there in the PLECS template file.
  - Use the signals provided from the PWM block to drive the inverter switches.
In the report, show your implementation by taking a capture of your circuit.
- The Reference signals are modified a few times during the simulation, this is handled by the blocks in the blue frames. Initially, the converter voltage should have the same magnitude as the grid voltage, but with a phase shift of  $\pi/4$ . At  $t = 0.25\text{s}$ , the phase shift is set to 0 (converter and grid voltages should be almost identical). At  $t = 0.5\text{s}$ , the modulation index ( $m$ ) is increased to 1. Finally, at  $t = 0.75\text{s}$  the modulation index is increased to 1.5.

In the report, show a capture of the "Converter Voltages & References" scope. Explain what you see and describe what is happening after  $t = 0.75\text{s}$ .

Show a capture of the "Switched model Voltages and Currents" scope. Explain the behavior of the grid currents for the different converter voltages applied during the sequence.
- Model the system in  $\alpha\beta$  reference frame (c.f. lectures). Use the Clarke transformation to obtain the inverter and grid voltages in  $\alpha\beta$  reference frame. In the report, show your implementation (PLECS block diagram) and a scope capture of converter voltages, grid voltages and grid currents in  $\alpha\beta$  reference frame.
- Model the system in  $dq$  reference frame (c.f. lectures). Use the Park transformation to obtain the inverter and grid voltage components in  $dq$  reference frame. In the report, show your implementation (PLECS block diagram) and a scope capture of converter voltages, grid voltages and grid currents in  $dq$  reference frame.
- Transform the currents obtained with both models into the  $abc$  reference frame (using inverse Clarke/Park transformations), and compare them with the switched model. In the report, show a capture of the "Model Comparison" scope. If you see any difference between the models, discuss them.