

# Smart Sensors for IoT

## Exercise 7 (15.12.2021)

Christian Enz

Swiss Federal Institute of Technology (EPFL), Lausanne, Switzerland

### Problem 1 The Transducer Bridge

Transducer resistances are expressed in the form  $R + \Delta R$ , where  $R$  is the resistance at some reference condition, such as  $0^\circ\text{C}$  in the case of temperature transducers, or the absence of strain in the case of strain gauges, and  $\Delta R$  represents the deviation from the reference value as a consequence of a change in the physical condition affecting the transducer. Transducer resistances are also expressed in the alternative form  $R(1 + \delta)$ , where  $\delta = \Delta R/R$  represents the fractional deviation. Multiplying  $\delta$  by 100 yields the percentage deviation.

Platinum resistance temperature detectors (Pt RTDs) have a temperature coefficient  $\alpha = 0.00392^\circ\text{C}^{-1}$ . Usually, the Pt RTD reference value is given at  $0^\circ\text{C}$  and it is  $100\Omega$ . The expression for the resistance  $R$  as a function of the temperature  $T$  is:

$$R(T) = R(0^\circ\text{C}) \cdot (1 + \alpha T) = 100 \cdot (1 + \alpha T) = 100 \cdot (1 + \delta).$$

An implementation of the Platinum resistance temperature detectors is shown in Fig. 1 and let  $V_{\text{REF}} = 15\text{V}$ .

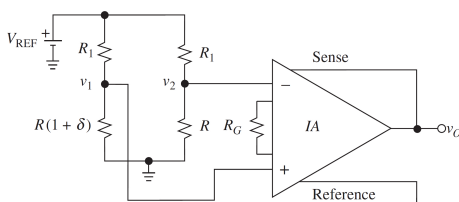


Figure 1: Transducer bridge and IA used as Pt RTD.

- Specify values for  $R_1$  and  $A$  suitable for achieving an output sensitivity of  $0.1\text{V}/^\circ\text{C}$  near  $0^\circ\text{C}$ . To avoid self-heating in the RTD, limit its power dissipation to less than  $0.2\text{mW}$ .
- Compute  $v_O(100^\circ\text{C})$ .

### Problem 2 Wheatstone bridge linearization

The circuit in Figure Fig. 2 is a linearized bridge. Assume the op amps to be ideal:

- show that the output voltage is directly proportional to the measured quantity.

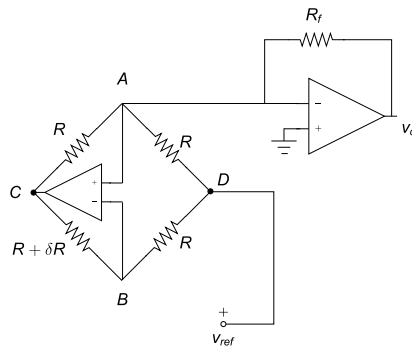


Figure 2: Wheatstone bridge linearization by two op amps.

### Problem 3 Switched Capacitor circuit

Consider the Switched Capacitor circuit in Fig. 3, where the amplifier is ideal except it has a small offset voltage  $V_{os}$ .

- Evaluate the effect the offset voltage on the output.

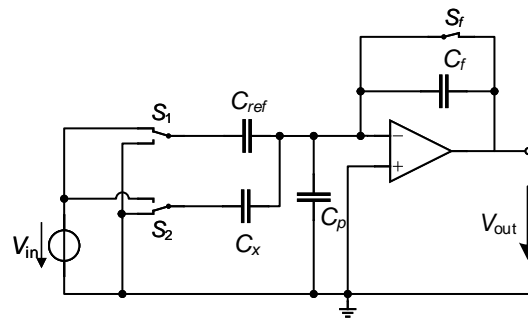


Figure 3: Switched Capacitor circuit.

## Solutions to Exercise 7 (15.12.2021)

### Problem 1 The Transducer Bridge

Platinum resistance temperature detectors (Pt RTDs) have a temperature coefficient  $\alpha = 0.00392 \text{ }^\circ\text{C}^{-1}$ . Usually, the Pt RTD reference value is given at  $0 \text{ }^\circ\text{C}$  and it is  $100 \Omega$ . The expression for the resistance  $R$  as a function of the temperature  $T$  is:

$$R(T) = R(0 \text{ }^\circ\text{C}) \cdot (1 + \alpha T) = 100 \cdot (1 + \alpha T) = 100 \cdot (1 + \delta).$$

An implementation of the Platinum resistance temperature detectors is shown in Fig. 1 and let  $V_{\text{REF}} = 15 \text{ V}$ .

- Specify values for  $R_1$  and  $A$  suitable for achieving an output sensitivity of  $0.1 \text{ V}/^\circ\text{C}$  near  $0 \text{ }^\circ\text{C}$ . To avoid self-heating in the RTD, limit its power dissipation to less than  $0.2 \text{ mW}$ .

The voltage at the node  $v_1$  is given by:

$$v_1 = \frac{R(1 + \delta)}{R(1 + \delta) + R_1} V_{\text{REF}}; \quad (1)$$

whereas the voltage at the node  $v_2$  is given by:

$$v_2 = \frac{R}{R + R_1} V_{\text{REF}}; \quad (2)$$

The voltage  $v_O$  is given, with some manipulation, by:

$$v_O = (v_2 - v_1)A = AV_{\text{REF}} \frac{\delta}{1 + R_1/R + (1 + R_1/R)(1 + \delta)}. \quad (3)$$

Denoting the transducer current as  $i$ , the power dissipation of the resistance temperature detector (RTD) is:

$$P_{\text{RTD}} = Ri^2; \quad (4)$$

therefore, in order to meet the power dissipation requirement,  $i^2 \leq P_{\text{RTD}}/R = 0.2 \text{ mW}/100 \Omega$ , i.e.  $i \leq 1.4 \text{ mA}$ .

To be on the safe side, let us impose  $i = 1 \text{ mA}$ . Since the current flowing in  $R$  is:

$$i = \frac{V_{\text{REF}}}{(R_1 + R)}; \quad (5)$$

this yields to  $R_1 = 15 \text{ k}\Omega$ .

For  $\Delta T = 1 \text{ }^\circ\text{C}$ , we have  $\delta = \alpha \cdot 1 \text{ }^\circ\text{C} = 0.00392$ , and we want  $\Delta v_O = 0.1 \text{ V}$ .

We can use the following equation since  $\delta \ll 1$ :

$$v_O \approx \frac{AV_{\text{REF}}}{2 + R_1/R + R/R_1} \delta; \quad (6)$$

we need  $A = 258.5 \text{ V/V}$ .

- Compute  $v_O(100^\circ\text{C})$ .

For  $\Delta T = 100^\circ\text{C}$  we have  $\delta = \alpha\Delta T = 0.392$ , which is not much smaller than 1 and therefore the following equation should be better used:

$$v_O = AV_{\text{REF}} \frac{\delta}{1 + R_1/R + (1 + R_1/R)(1 + \delta)}; \quad (7)$$

from which we get  $v_O(100^\circ\text{C}) = 9.974 \text{ V}$ . Equation (6) predicts that  $v_O(100^\circ\text{C}) = 100 \text{ V}$ , which exceeds the actual value by  $0.026 \text{ V}$ . Since  $0.1 \text{ V}$  corresponds to  $1^\circ\text{C}$ ,  $0.026 \text{ V}$  corresponds to  $0.026/0.1 = 0.26^\circ\text{C}$ . Therefore, in using the approximated expression, we cause, at  $100^\circ\text{C}$ , an error of about one-quarter of a degree Celsius.

## Problem 2 Wheatstone bridge linearization

The circuit in Fig. 2 is a linearized bridge. Assume the op amps to be ideal:

- show that the output voltage is directly proportional to the measured quantity.

Writing the current summation at nodes  $A$  and  $B$  (which are grounded), respectively:

$$\begin{cases} \frac{V_c}{R} + \frac{V_{ref}}{R} + \frac{V_O}{R_f} = 0; \\ \frac{V_c}{R + \delta R} + \frac{V_{ref}}{R} = 0; \end{cases} \quad (8)$$

leading to:

$$V_O = \frac{R_f \cdot \delta R}{R^2} V_{ref}. \quad (9)$$

## Problem 3 Switched Capacitor circuit

Consider the Switched Capacitor circuit in Fig. 3, where the amplifier is ideal except it has a small offset voltage  $V_{os}$ .

- Evaluate the effect the offset voltage on the output.

Let us apply the charge conservation principle to the two phases (the principle is similar to the Kirchhoff's Current Law):

**Phase 1**

$$Q_1 = (V_{\text{in}} - V_{\text{os}})C_{\text{ref}} - V_{\text{os}}C_p - V_{\text{os}}C_x \quad (10)$$

**Phase 2**

$$Q_2 = -V_{\text{os}}C_{\text{ref}} + (V_{\text{in}} - V_{\text{os}})C_x + (V_{\text{out}} - V_{\text{os}})C_f - V_{\text{os}}C_p \quad (11)$$

By equating (10) and (11):

$$Q_1 = Q_2 \rightarrow (V_{\text{in}} - V_{\text{os}})C_{\text{ref}} - V_{\text{os}}C_p - V_{\text{os}}C_x = -V_{\text{os}}C_{\text{ref}} + (V_{\text{in}} - V_{\text{os}})C_x + (V_{\text{out}} - V_{\text{os}})C_f - V_{\text{os}}C_p; \quad (12)$$

the following result is obtained:

$$V_{\text{out}} = V_{\text{os}} + \frac{C_{\text{ref}} - C_x}{C_f} V_{\text{in}}. \quad (13)$$