

## Exercise 1

A  $p$ - $n$  junction diode obeys the Shockley equation,

$$I_D = I_s \left( e^{V_a/V_T} - 1 \right) \approx I_s e^{V_a/V_T} \quad \text{for } V_a \gg V_T, \quad (1)$$

where  $V_a$  is the applied voltage,  $V_T = kT/q$  is the thermal voltage, and  $I_s$  is the reverse saturation current of the diode. As the temperature ( $T$ ) increases, the exponential factor decreases. However, an increase in  $T$  causes  $I_s$  to increase since  $I_s \propto n_i^2$ , where

$$n_i = \sqrt{N_C(T)N_V(T)} \exp\left(-\frac{E_g(T)}{2kT}\right) \quad (2)$$

is the intrinsic carrier concentration of the material. As  $T$  is increased, the exponential factor in Eq. 2 increases, and so do the effective densities of states  $N_C$  and  $N_V$ . As a result,  $n_i$  increases significantly<sup>1</sup> with  $T$  and so does  $I_s$ . The increase in  $I_s$  more than compensates the decrease in the exponential term in Eq. 1, and the net result is that, for the same applied voltage, the diode current is higher at a higher temperature. In other words, the diode  $I$ - $V$  curve shifts left with temperature, as shown in Fig. 1.

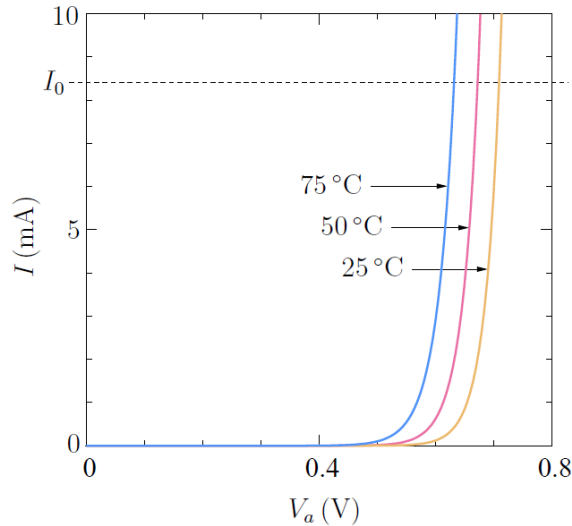


Figure 1:  $I$ - $V$  curve of a silicon diode under forward bias at different temperatures (representative plot)

If the diode current is held constant ( $I$  in the figure), we can see that the diode voltage decreases as the temperature is increased. For a silicon diode, this change is about  $-2\text{mV}/^\circ\text{C}$ .

- 1) In silicon,  $n_i$  is of the order of  $10^{10}$  carriers/ $\text{cm}^3$  at room temperature,  $T=300\text{K}$ , and doubles with every increase of  $10^\circ\text{C}$ . Estimate by calculation what is the increase in the current  $I_D$  of a diode supposing an increase of temperature for  $50^\circ\text{C}$ , from the reference temperature of  $27^\circ\text{C}$  ( $300\text{K}$ ) and a forward bias of  $0.6\text{V}$ .

- 2) In order to make the junction diode a temperature sensor, it has to be biased with a constant current circuit. Demonstrate that circuit of Fig. 2 offers a constant current solution.

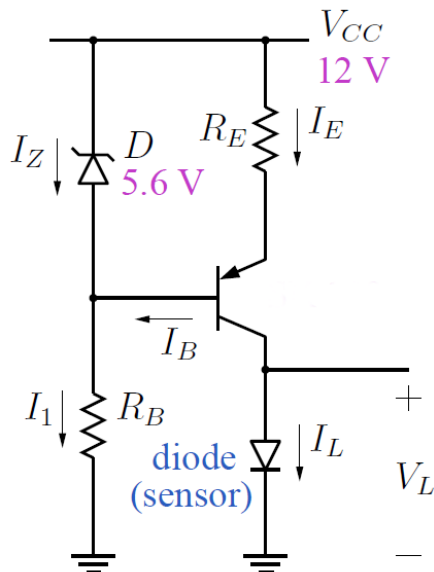


Figure 2: Implementation of a constant current source with a bipolar transistor.

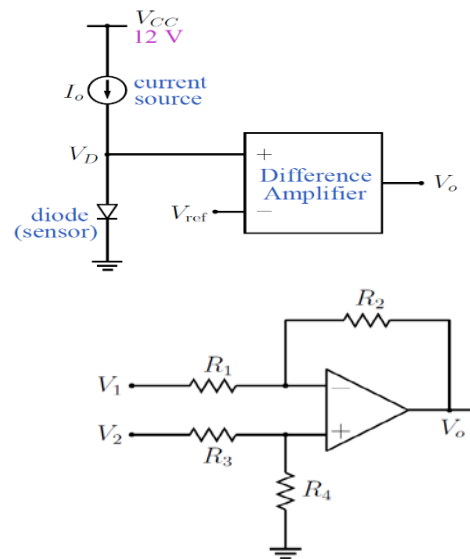


Figure 3: Overall sensor circuit, with diode as sensor and differential amplification.

- 3) If the Zener diode should operate at a current of 2mA, calculate the value of the resistance  $R_B$  in order to impose this value of current.
- 4) Calculate  $R_E$  if we want to impose a current of 1mA in the junction diode used as temperature sensor.
- 5) The circuit works as a constant current source as long as the transistor is in the active operation region (forward mode),  $V_E - V_C > 0.3V$ . Demonstrate that in this case, if  $V_L = 0.7V$ , this condition is satisfied.
- 6) Propose a constant current source circuit similar to the one of Fig.2 implemented with a MOSFET transistor.
- 7) In practice, the temperature-dependent voltage drop on the diode of Fig. 2 is amplified by a differential amplifier scheme as in Fig. 3. Supposing  $V_2$  is the voltage drop on the diode and  $V_1$  a reference voltage, calculate the amplified output of the circuit in Fig. 3. Propose values for the resistances so that the output is amplified by 10x compared to the input.