 


MICRO-435

Quantum and Nanocomputing


Edoardo Charbon
Mariagrazia Graziano



Daniel D. Gajski,
Principles of Digital Design, Prentice Hall, 1st Edition (1997).



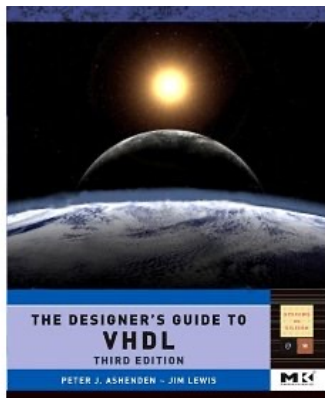Scott Hauck, André Dehon, Ed.
Reconfigurable Computing, Morgan Kaufmann, 1st Edition (2007).



Peter J. Ashenden, *The Designer's Guide to VHDL*, Morgan Kaufmann Publishers,
1st Edition (1995)

Quantum Computing Syllabus (Week 1-7)

- Fundamentals of quantum computing
- Qubit realization & control
- **Cryo-CMOS components**
- Scalable quantum computers
- Quantum communication, sensing, and metrology

Cryo-CMOS Components (2)

- Choosing a technology
- Cryo-CMOS modeling
- LNAs
- ADCs (part I)
- ADCs (part II)
- DACs
- Digital circuits in CMOS


Acknowledgements: Fabio Sebastiano

Analog-to-Digital Converters (Part II)


Digression: Mismatch

- Mismatch = difference between 2 devices that are designed to be identical
- Systematic mismatch (reproducible from die-to-die)
 - Electrical biasing difference, mechanical stress, edge effects, temperature gradients
- Random mismatch
 - Due to microscopic effects (random dopant fluctuations), local mobility fluctuations, polysilicon and oxide granularity, oxide charges, ...)
 - Statistically characterized

Mismatch (2)

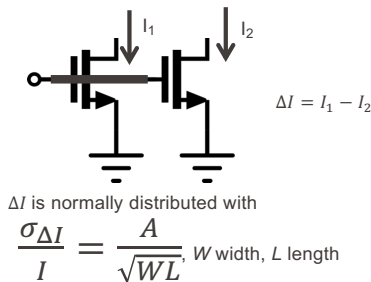


 Example: std deviation of threshold voltage





[Courtesy: Pelgrom, *Analog to Digital Conversion*]

- Mismatch minimized by increasing area (WL)
- Better matching \Rightarrow large area
 - \Rightarrow higher cost
 - \Rightarrow larger parasitic capacitance \Rightarrow slower behavior/larger power
- Aspect ratio (W/L) *usually* determines electrical behavior, not area (WL)
 - Exception: for capacitors $C \propto WL$
- Minimum achievable mismatch depends on technology
 - Typically below ~ 10 - 12 bits in integrated circuits

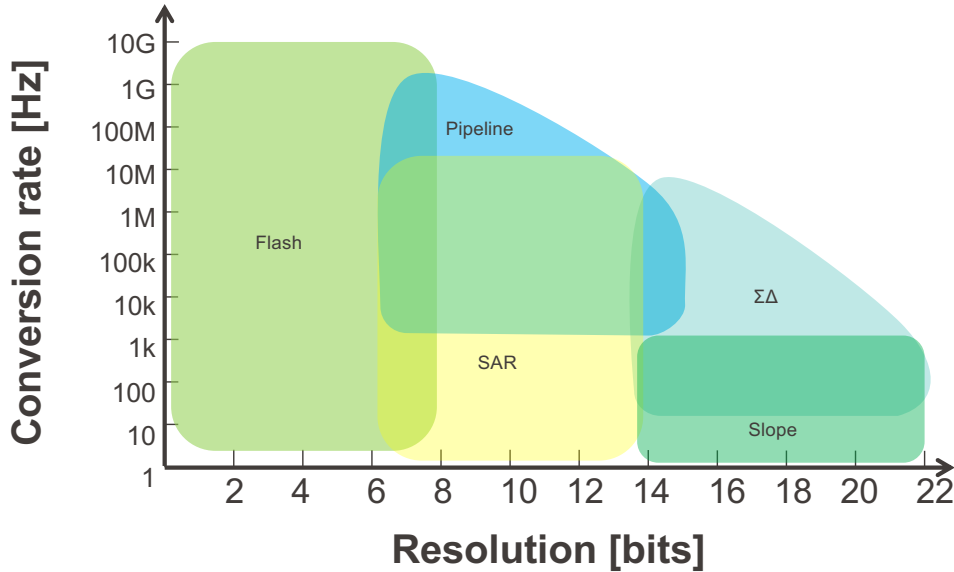


Source: Pelgrom 2006

  

Why This Type of ADC?

- 1-bit ADCs
 - ⇒ Very simple robust circuits
- Run for many cycles
 - ⇒ longer time or *faster execution*
- Modern IC technologies
 - Very fast circuits (GHz microprocessors)
 - Exploit speed and use simple circuits
- ***Fast simple circuit “better” than complex slow circuit***
- Typical applications: low-error/high-resolution
 - Instrumentation, sensors, audio

The Advantage of Oversampling

 


- Sampling at much higher rate than Nyquist rate
- Oversampling ratio

$$OSR = \frac{f_s}{f_{Nyquist}} = \frac{f_s}{2BW}$$

- Relax requirements on anti-aliasing filter
- **Quantization noise shaping**

Quantization Noise

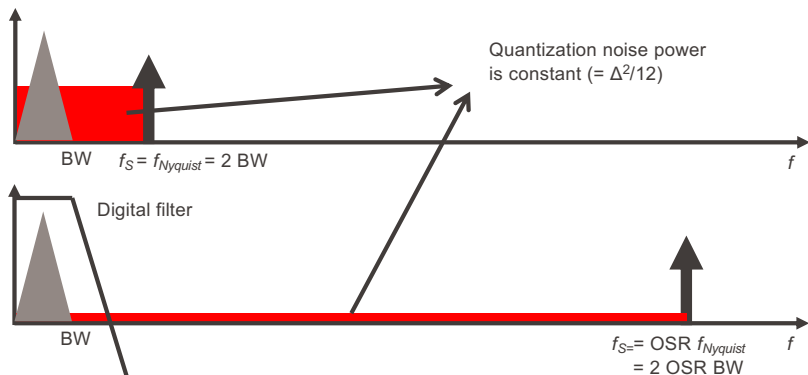


- Quantization noise is spread over a wider bandwidth
- Total quantization noise is lower **in the signal bandwidth**
- Signal-to-Quantization-Noise-Ratio (SQNR) improves:

$$SQNR_{oversampled, dB} = SQNR_{Nyquist} + 10 \log_{10} OSR$$



- **It requires digital filtering**

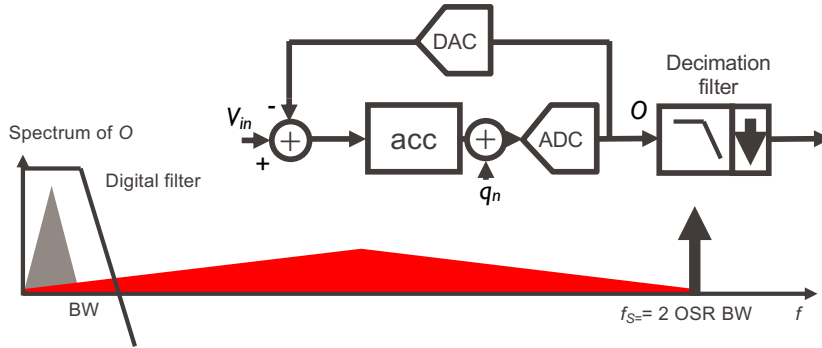Noise Shaping in $\Sigma\Delta$ (or $\Delta\Sigma$) ADC



- Accumulator is a low-pass filter (a.k.a. loop filter)
- Quantization noise (q_n) is attenuated by loop filter
- Quantization noise is shaped
- Even lower noise than just oversampling


Dynamic Element Matching (DEM)

  

Cycle	No DEM	DEM
1		
2		
3		

- DEM average mismatch over multiple cycles

DEM – Randomizing Algorithm

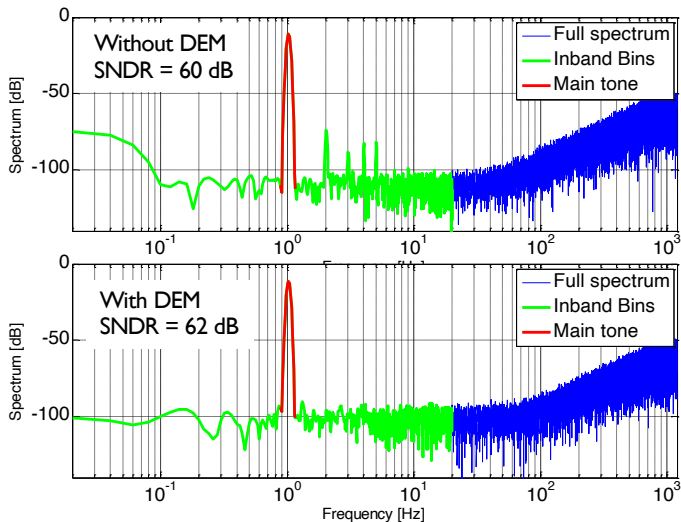


- Distortion energy spread over BW
- SNDR ~ equal but better SFDR

Example of 8-level
Data-Weighted Averaging (DWA)

Cycle	DAC	DAC elements
1	2	■ ■ ■ ■ ■ ■ ■ ■
2	2	■ ■ ■ ■ ■ ■ ■ ■
3	5	■ ■ ■ ■ ■ ■ ■ ■
4	2	■ ■ ■ ■ ■ ■ ■ ■
5	3	■ ■ ■ ■ ■ ■ ■ ■
6	4	■ ■ ■ ■ ■ ■ ■ ■

Resulting spectrum
(with DAC mismatch)

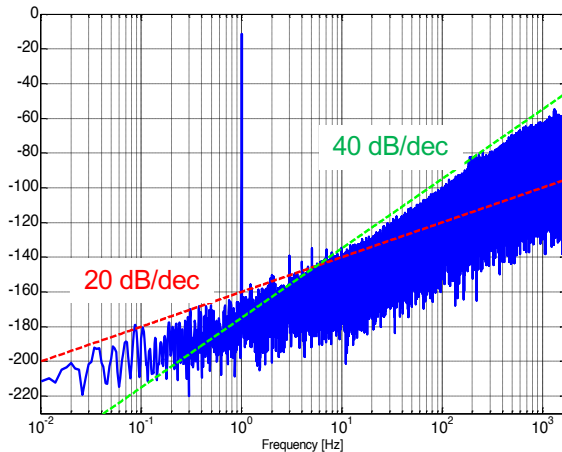

- Other DEM algorithms gives mismatch-error shaping

Oversampled ADC vs. Nyquist ADC

Oversampled ADC

- Simplified anti-aliasing filter
- Requires cascaded digital filter (decimation filter)
- Low distortion
- Limited in bandwidth
- Very high resolution
- Higher speed (OSR) for higher resolution

Nyquist ADC

- Requires anti-aliasing filter
- Digital signal readily available
- Higher distortion
- High speed
- Moderate resolution
- Higher complexity for higher resolution

- Walden FoM

$$FoM_W = \frac{P}{f_s 2^{ENOB}}$$


- Good if power is proportional to the number of levels (2^{ENOB})
- For ADCs limited by quantization-noise

- Schreier FoM

$$FoM_S = SNDR_{dB} + 10 \log_{10} \frac{f_s}{2P} = 10 \log_{10} 3 \frac{2^{2(ENOB-1)} f_s}{P}$$

- Good if power is proportional to the square of the number of levels (2^{2ENOB})
- For ADCs limited by thermal-noise


Figure of Merit (FoM)

 

B. Murmann – “ADC performance summary”,
 Available: <http://web.stanford.edu/~murmman/adcsurvey.html>

$$\text{SNDR} = 6.02 \text{ ENOB} + 1.76, \text{ FOMw} = \text{Energy} / 2^{\text{ENOB}}, \text{ FOMs} = \text{SNDR} - 10 \log_{10} 2 \text{ Energy}$$


Figure of Merit (2)

 

B. Murmann – “ADC performance summary”,
Available: <http://web.stanford.edu/~murmman/adcsurvey.html>

$$SNDR = 6.02 \text{ ENOB} + 1.76, \text{ FOMw} = \text{Energy} / 2^{\text{ENOB}}, \text{ FOMs} = SNDR - 10 \log_{10} 2 \text{ Energy}$$


Figure of Merit (3)

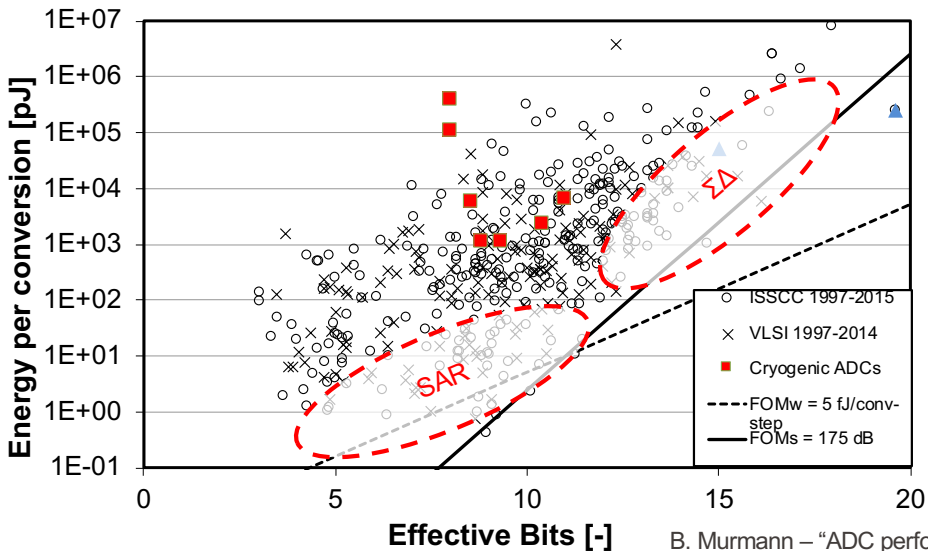

B. Murmann – “ADC performance summary”,
Available: <http://web.stanford.edu/~murmman/adcsurvey.html>


$$\text{SNDR} = 6.02 \text{ ENOB} + 1.76, \text{ FOMw} = \text{Energy} / 2^{\text{ENOB}}, \text{ FOMs} = \text{SNDR} - 10 \log_{10} 2 \text{ Energy}$$

Digital-to-Analog Converters (DACs)

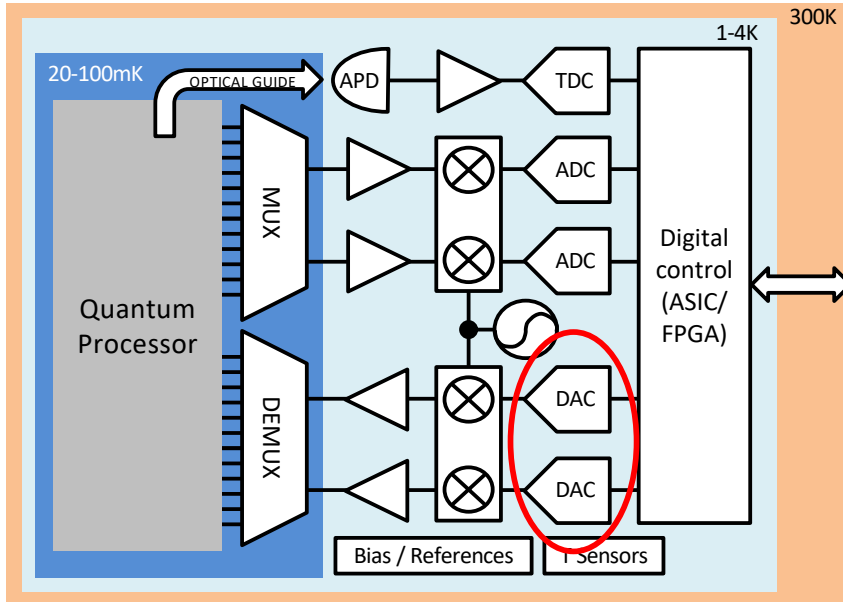


Digital-to-Analog Conversion


Sampling

 


Digital domain

 


After
Digital-to-Analog
conversion

 

Digital-to-Analog Conversion

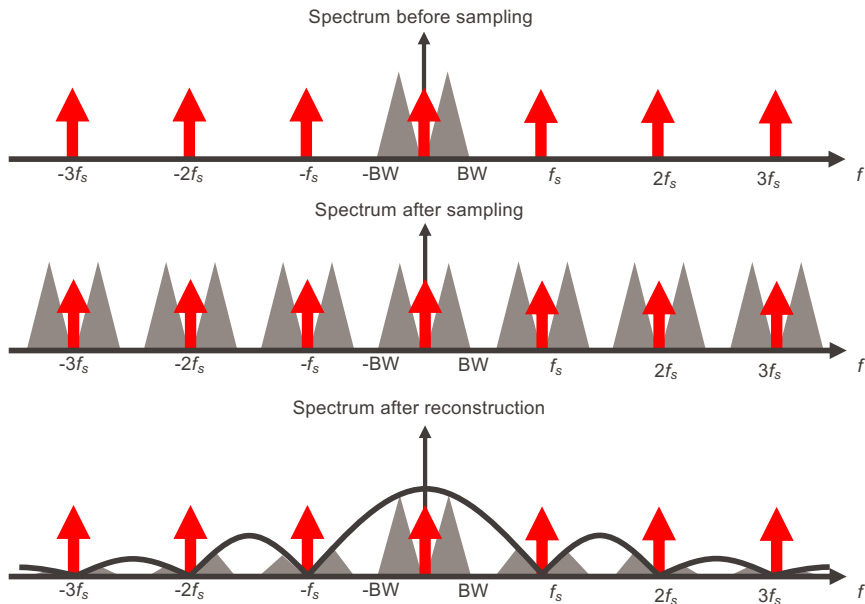

 

$$\text{sinc}(x) = \frac{\sin(x)}{x}$$

- Non-idealities
 - In-band $\text{sinc}(x)$ distortion
 - Replicas around harmonics
- **Need for reconstruction filter**
- Filter requirements can be relaxed by:
 - Oversampling
 - In-band pre-distortion


- Resistive based
- Capacitive based
- Current based

- Nyquist DAC / oversampled DAC


- Linear coded / Binary coded

Resistor string DAC

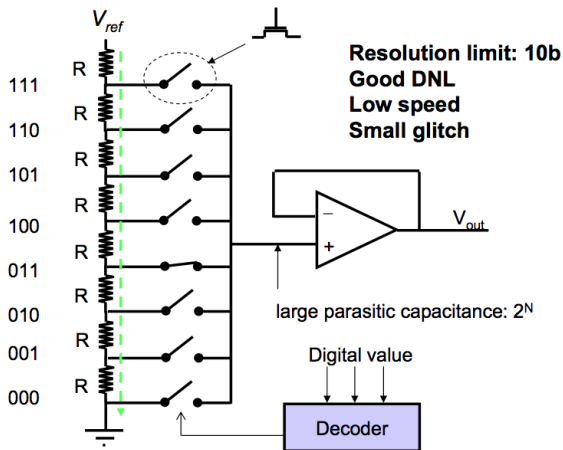- Small DNL
- Large area at high resolution



 - Large DNL
- Small area at high resolution
- Moderate speed
- Large power dissipation




$$v_{out} = R_F \left(I_r \cdot A_0 + \frac{I_r}{2} \cdot A_1 + \frac{I_r}{2^2} \cdot A_1 + \frac{I_r}{2^3} \cdot A_1 \right)$$

$$I_r = \frac{V_{ref}}{2R}$$


Capacitor Array DAC

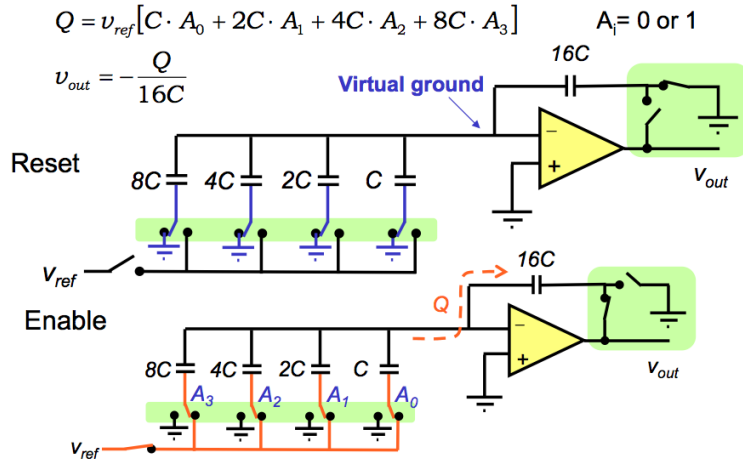- Low power
- No sample and hold required




Current Steering DAC


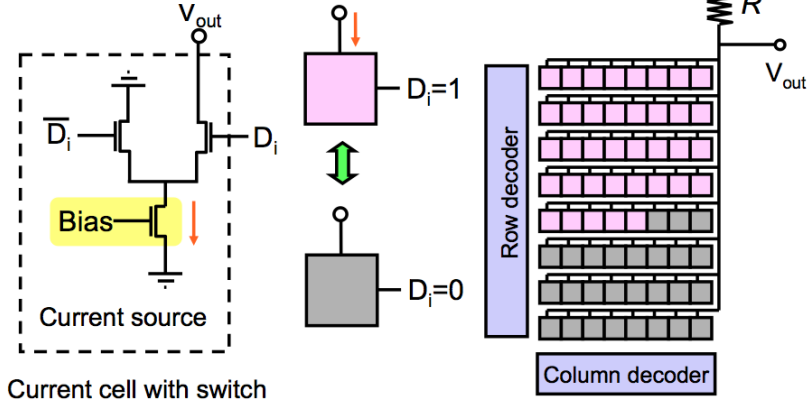
- High speed (1GHz)
- Large area
- Moderate resolution
- Small DNL



Oversampled DAC

 

In a similar way

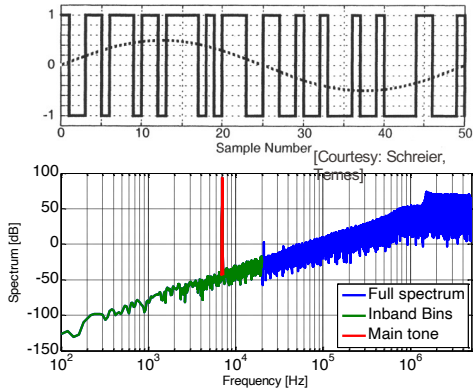 

- Similar advantages of $\Sigma\Delta$ ADC:

- High linearity
- Simple
- Trade-off between amplitude resolution and time resolution

Characterizing a DAC


- Sampling frequency
- Number of quantization levels (bits)
- Static performance
 - Differential non-linearity (DNL)
 - Integral non-linearity (INL)
 - Monotonicity
- Dynamic performance
 - SNR, SFDR, THD, SNDR, ENOB
 - Sampling Jitter

- **Additional: glitch**




Same as ADCs


State 1: [1000]=8

 

State 2: [0111]=7

 


Intermediate: [1111]=15

 

Caused by overlapping of signals
This appears within a few psec,
However, energy is not negligible.
Glitch causes the distortion of signal


$$P_{g,max} = 2^{2N-2} \cdot \Delta^2 \cdot \frac{T_g}{T_s}$$
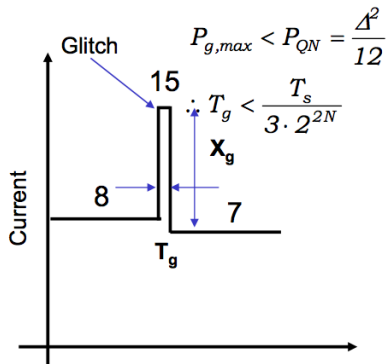
$$P_{g,max} < P_{QN} = \frac{\Delta^2}{12}$$






Digital Circuits in CMOS

 
- Electronic devices are analog
- Why digital processing?
 - Represent information using discrete levels
 - Drastically reduce the probability of errors
- Why CMOS for digital?
 - Any logic function can be implemented with switches
 - CMOS transistors are just very good switches





 - Basic inverter belongs to class of **static circuits**
 - Output always connected to either V_{DD} or V_{SS}
- **Not ideal but:**
 - **Rail to rail** voltage swing
 - **Ratio less** design
 - **Low output impedance**
 - Extremely **high input impedance**
 - **No static power** dissipation
 - Good **noise properties/margins**




  


 


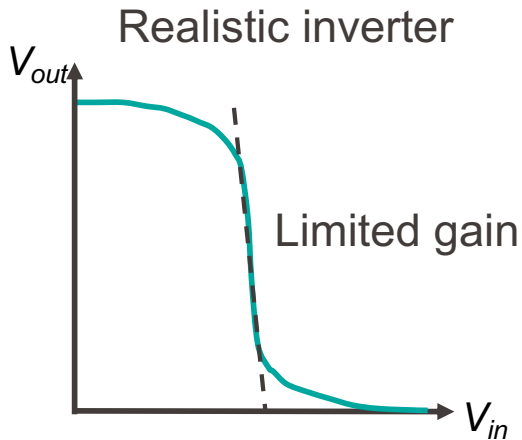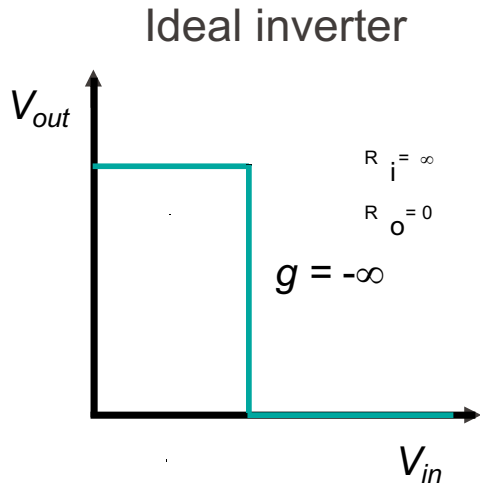

The Regenerative Property


 


A chain of inverters

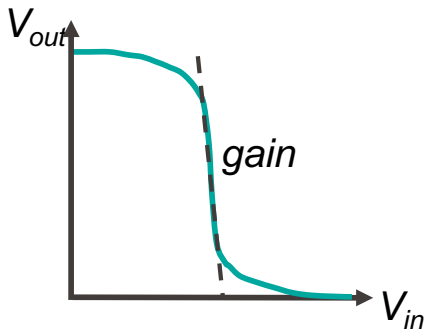 


- **Regenerative property**
 - Ability to regenerate a weak signal in a chain of gates
- Requires $|gain| > 1$

Gain as a Function of VDD

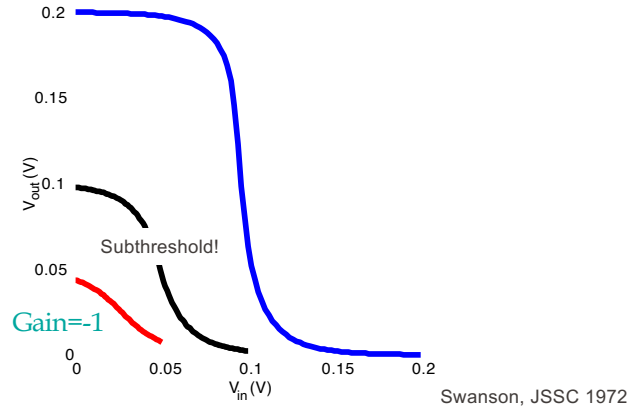 


- Inverter can work at supply voltage too low for turning transistor on, but gain deteriorates
- $|Gain|$ should be > 1 for regeneration $\Rightarrow V_{DDmin} > 4...8 \text{ kT/q}$


Noise in Digital Integrated Circuits

 


(a) Inductive coupling

 


(b) Capacitive coupling

 


(c) Power and ground noise

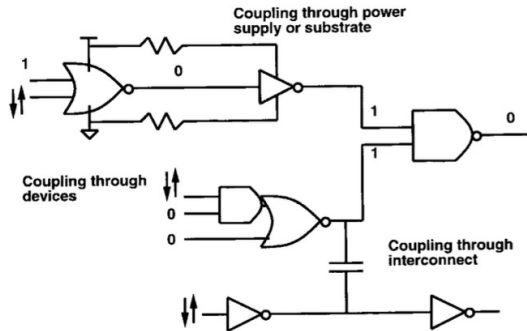

Shepard, IEEE TCAD, 1999


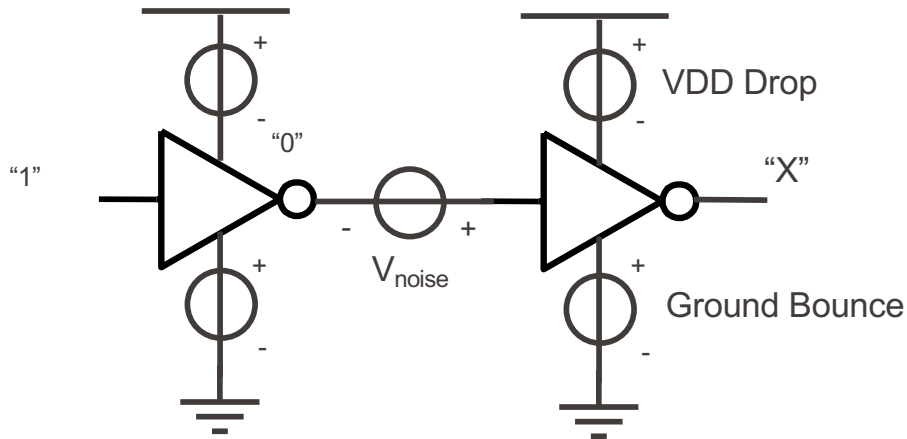


Noise Margins

 

- V_{OL} = Output Low Voltage
- V_{IL} = Input Low Voltage
- $V_{OH}, V_{IH} = \dots$


Noise Margins

 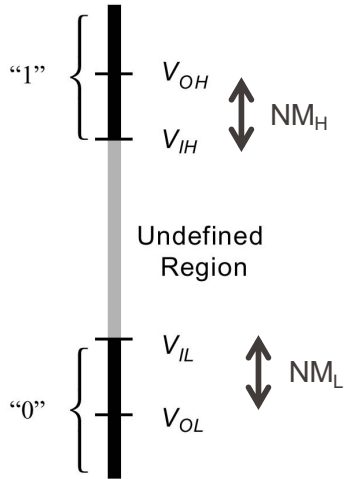



V_{OL} = Output Low Voltage
 V_{IL} = Input Low Voltage
 $V_{OH}, V_{IH} = \dots$

$NM_H = V_{OH} - V_{IH} = \text{High Noise Margin}$
 $NM_L = V_{IL} - V_{OL} = \text{Low Noise Margin}$

Noise Margins for Realistic Gates

 

  
V_{OL} V_{OH} V_{IL} V_{IH} typically defined at slope = -1
(dots on curve is alternative/ambiguous choice)




- $E_{V_{dd}} = \int_0^{+\infty} i(t)V_{dd} dt =$
 $= CV_{dd} \cdot V_{dd} = CV_{dd}^2$
- $E_{cap} = \frac{1}{2} CV_{dd}^2$
- $E_{PMOS} = \frac{1}{2} CV_{dd}^2$



- $E_{cap} = \frac{1}{2} CV_{dd}^2$
- $E_{NMOS} = \frac{1}{2} CV_{dd}^2$
- $E_{tot} = CV_{dd}^2$

 - $Power = \frac{E_{tot}}{T} = E_{tot}f = CV_{dd}^2f$
- Independent of transistor on-resistance
- Reduced as follows:
 - Frequency \Rightarrow slowing the operation rate
 - $V_{dd} \Rightarrow$ but reduce noise margin
 - $C \Rightarrow$ smaller devices, i.e. more advanced (scaled) process



 

Short Circuit Current

 
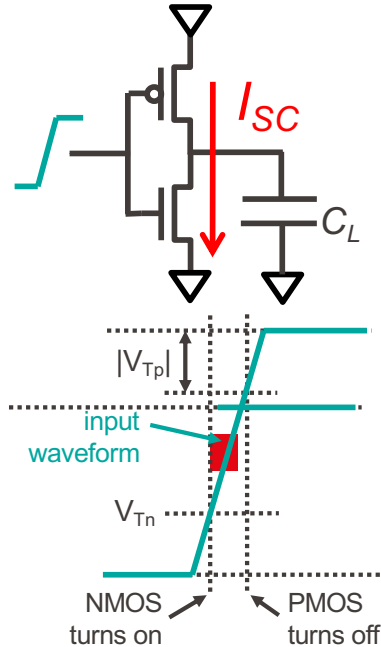


$$P_{SC} = t_{sc} V_{DD} I_{peak} f$$


$$t_{sc} = \frac{V_{DD} - 2V_T}{V_{DD}} t_s$$

- I_{peak} depends on loading C_L :
- Faster gate \Rightarrow more short-circ. current



Leakage and Sub-Threshold Current

  

 - Leakage current of reverse-biased S/D junctions
- Sub-threshold current of MOS devices (parasitic bip. dev.)
- Increases with higher T , V_{DD} , V_{DS}
- Leakage during static operation
⇒ **No zero static power**



Delay of Digital Gates

  




Energy Delay Tradeoff

$$E_{dyn} = CV_{DD}^2$$


$$t_p = \frac{\alpha CV_{DD}}{V_{DD} - V_{TE}}$$
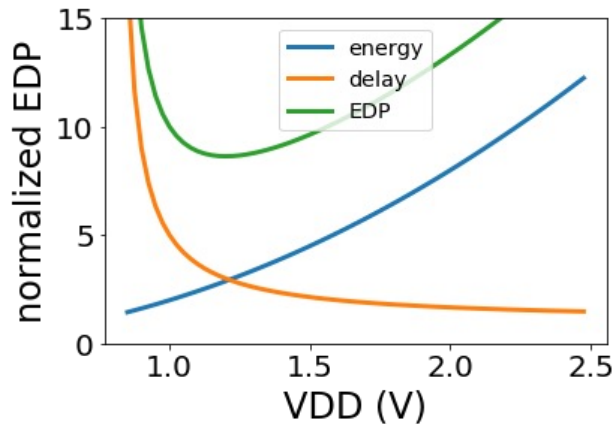
$$EDP = \frac{\alpha C^2 V_{DD}^3}{V_{DD} - V_{TE}}$$



  

 
- Lower VDD \Rightarrow slower gates \Rightarrow longer operation
 \Rightarrow leakage energy increase
- Minimum energy typically at low frequency



- Measured energy per operation for an 8-bit microprocessor in 130-nm CMOS technology


Sequential Circuits

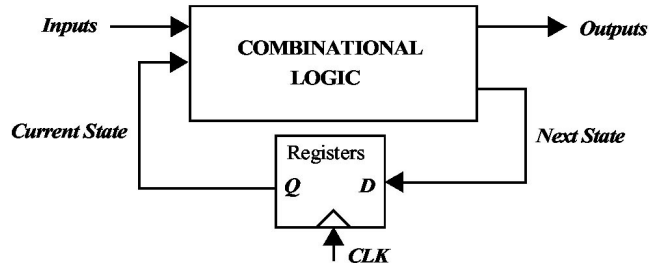- Combinational circuit: all digital function can be implemented
- To implement any algorithm: need for memory \Rightarrow sequential circuit
- Sequential circuits require **ordered computation**
- Several ways for **imposing ordering**
 - **Synchronous** (clock) \rightarrow dominant design strategy
 - **Asynchronous, self-timed** \rightarrow no good/general design tools





Memory Element – Latch


Dynamic latch

 


- Charge leaks away
- Not good for high T, high VDD


Static latch

  

 

 - **Buffered input and buffered output**
 - **Enable to write**
 - **Robust**
 - **Widely used in standard cells**
-
- ☺ No back driving
 - ☺ Very robust (most important)
 - Variant designs:
 - w/o input buffer and/or output buffer,
 - More efficient, less robust
 - Safe in noise-controlled environments



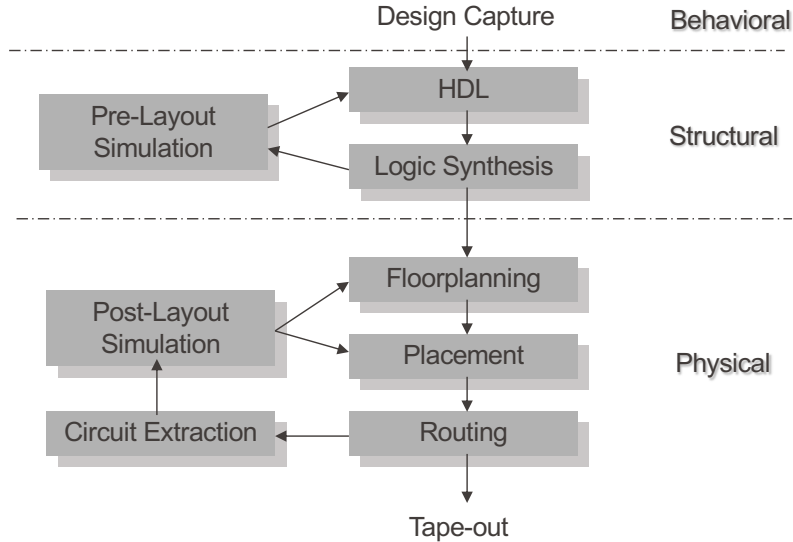

$$V_{DD,min} \approx 2 \frac{kT}{q} \ln(2) = 36\text{mV}$$

CMOS circuits operate in subthreshold wherever this equation holds

$$I_{DS} = I_0 \frac{W}{L} e^{\frac{V_{GS}-V_{TH}}{nv_t}} \left(1 - e^{-\frac{V_{DS}}{v_t}}\right); I_0 = \mu_0 C_{ox} \frac{W}{L} (n-1)v_t^2,$$


n is the sub-threshold slope (SS) factor and $v_t = kT/q$,

The net effect in sub-threshold regimes is a decrease of leakage currents by orders of magnitude, implying a significant increase in the I_{ON}/I_{OFF} ratio

Assuming an ideal SS factor $n = 1$, at 4.2 K, according to well established room temperature models, one could theoretically achieve $V_{DD,min} \approx 2 \ln(2)v_t = 0.48\text{mV}$.

However, at 4.2 K the consensus is that $n \approx 34.9$. Thus, this fundamental limit is actually $V_{DD,min} \approx 2.47\text{mV}$. Additional non-idealities include reverse short-channel effect (RSCE) and inverse narrow-width effect (INWE).

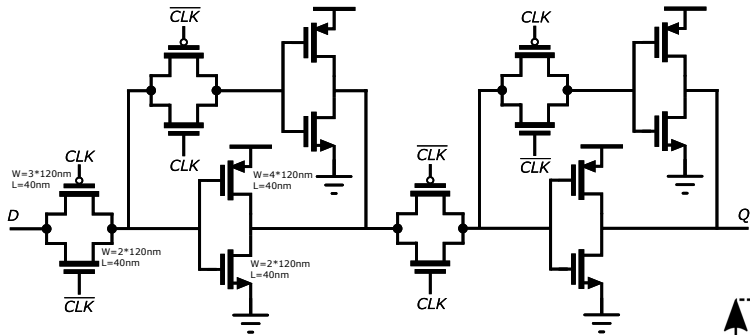Both effects substantially modulate the threshold voltage.




C) add secondary power rails;

D) minimize the length of transistors;

E) when useful, make the layout aware of mismatch by increasing the overall height of the cells.



A) create extensive substrate contacts and well-taps, so as to minimize latch-up;

 
B) resize the transistors, so as to reduce INWE and thus maximize V_{TH} modulation;



Ultra-Low Voltage Library 'cooLib'

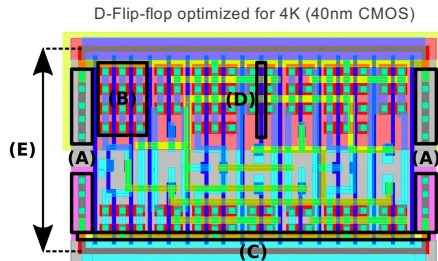 - Digital library optimized for 4K
- Ultra low voltage operation (100s mV)
- Sub-threshold bias of N/P MOS
- Resilient to latchup and hysteresis-free
- Several logic families (static and dynamic CMOS)
- Compatible with commercial P&R tools




 




FEATURES

- RISC-V (picorv32, open-source) implemented using 'CooLib'
- 8 Kb single-port SRAM from TSMC
- SRAM operates at nominal voltage, core at lower voltage
 - Interfacing by 'CooLib' level-shifters
- UART interface for serial in/output
- JTAG interface for SRAM write/read


Fully functional μP operating at 4K

Dynamic vs. Static Power

  


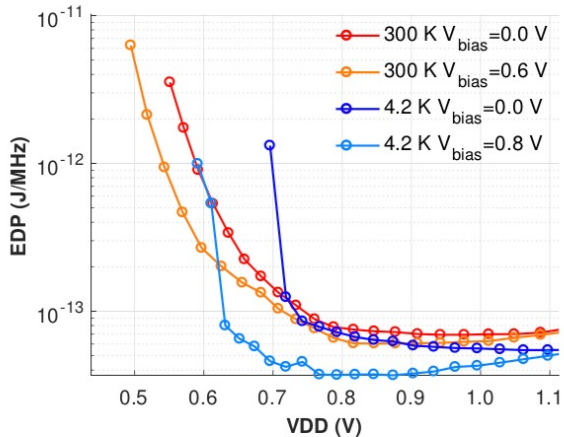 

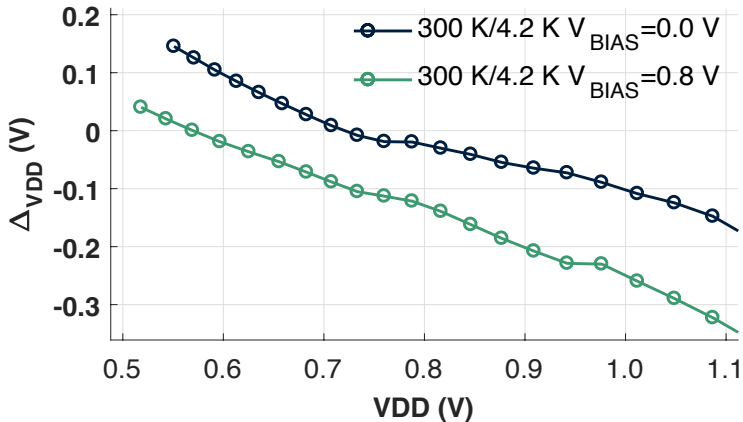
- When a bias is applied to the substrate
- Δ_{VDD} required to achieved equal F_{MAX}



 - When a bias is applied to the substrate
- Average power savings for equal F_{MAX}



Thank you

 

T. Haensch