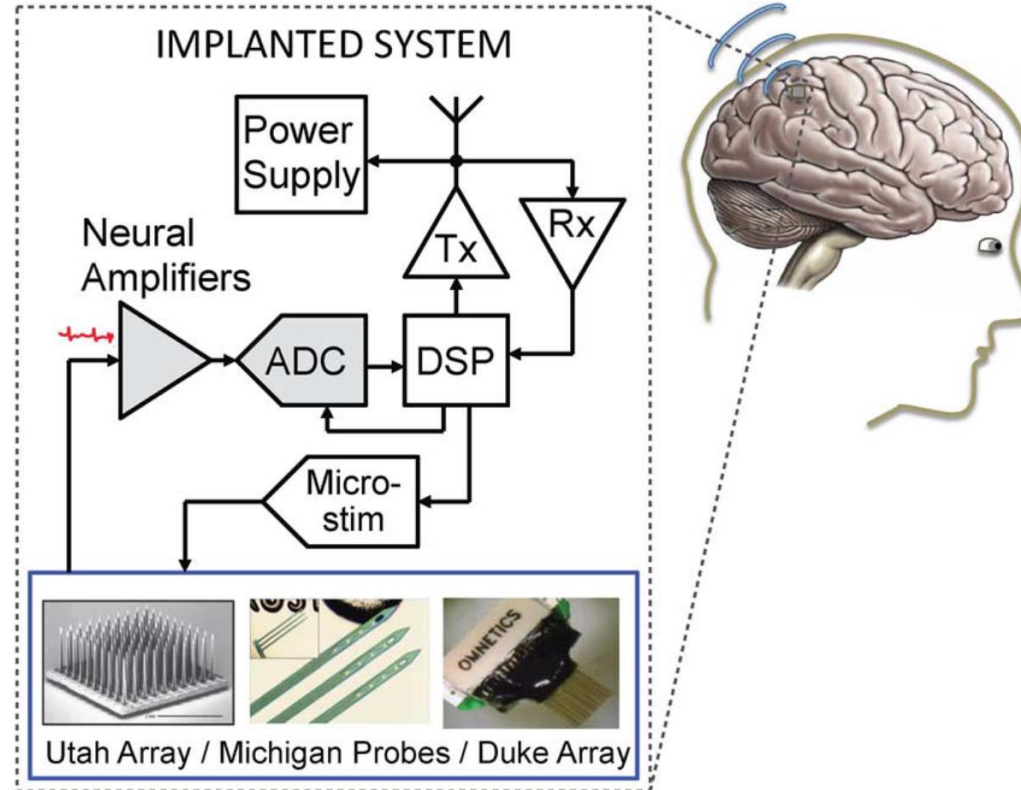


# Neural Interfaces


NX-422  
Digitization

Mahsa Shoaran  
IEM and Neuro-X Institutes

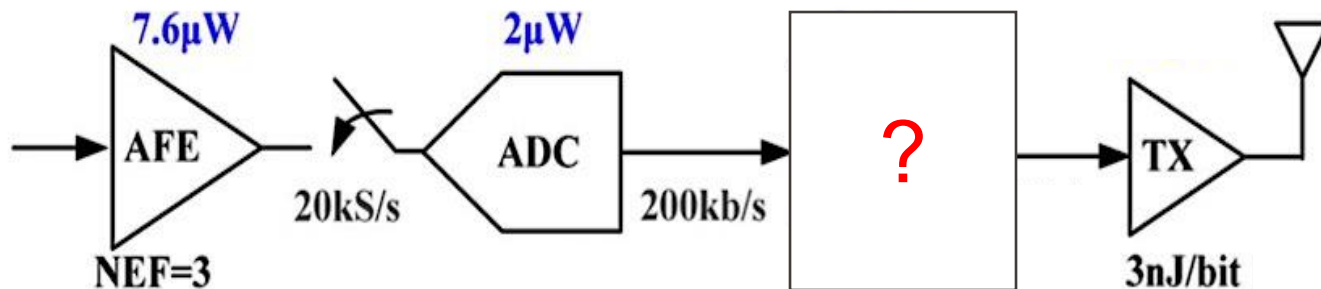
# Circuit Block Diagram of a Neural Interface: ADC




- The typical circuit blocks used in sensors for medical monitoring and their associated energy cost and power consumption



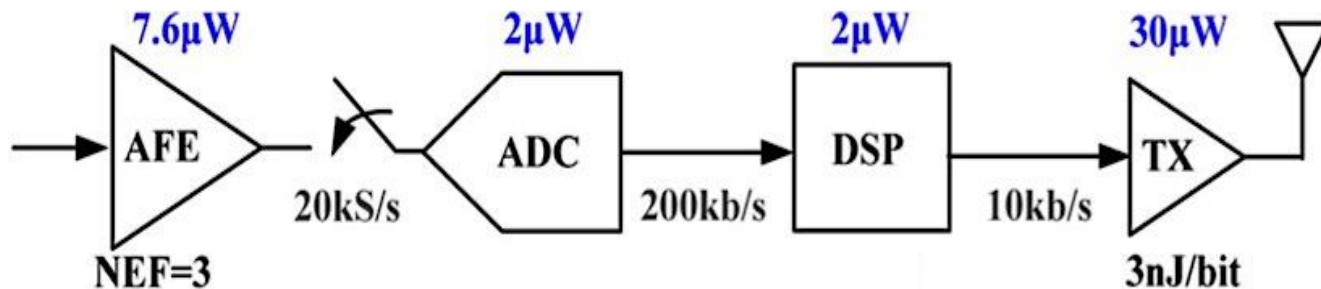
- The typical circuit blocks used in sensors for medical monitoring and their associated energy cost and power consumption



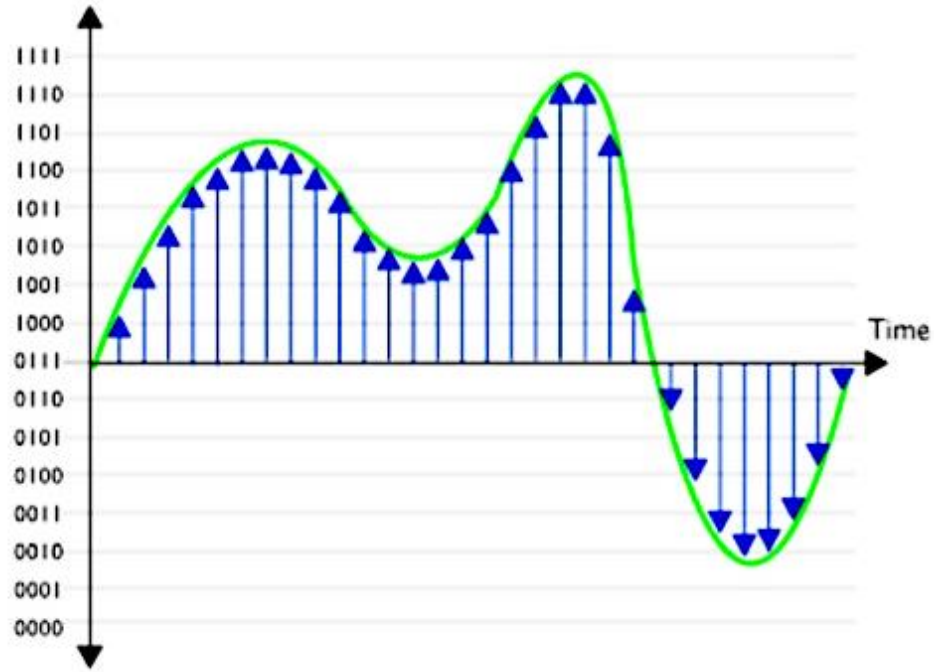- After amplification and filtering, signal is digitized (sampled at a fixed rate)



# Analog and Digital Signals

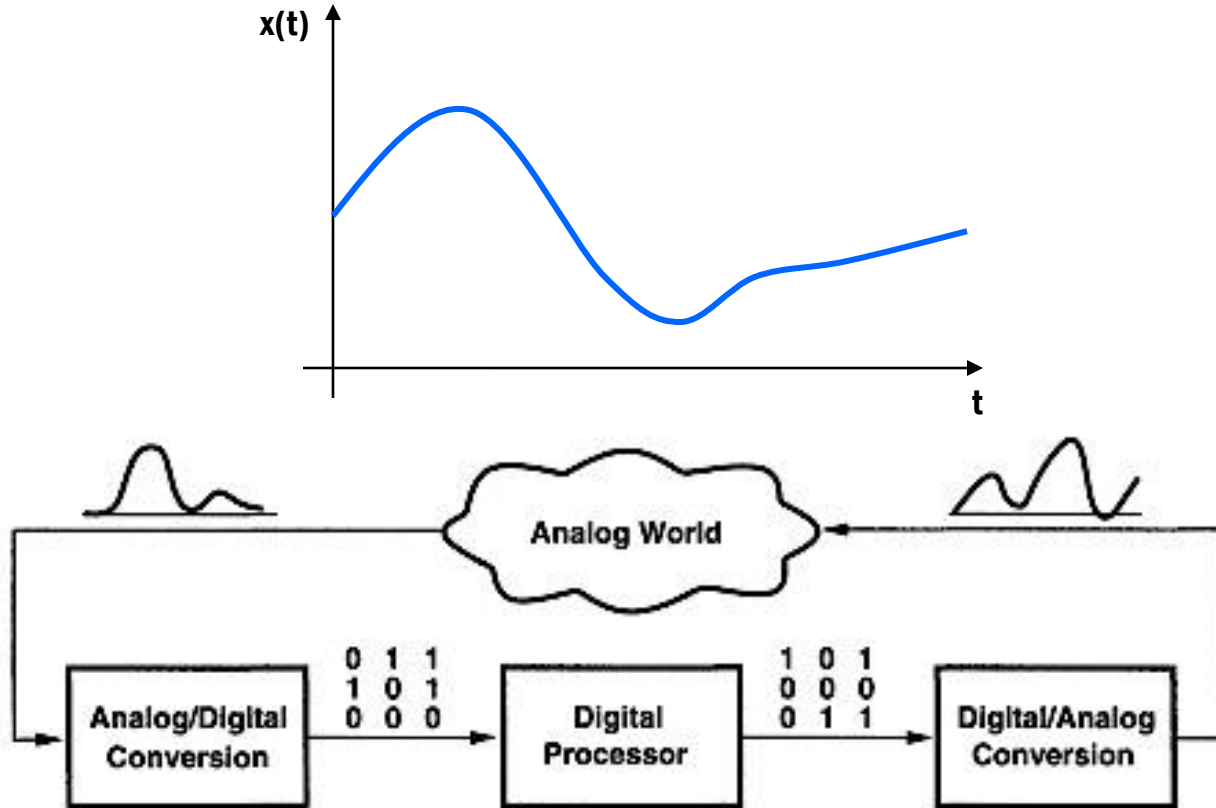

Foundation: *Shannon/Nyquist sampling theorem*





“if you sample densely enough (at the Nyquist rate), you can perfectly reconstruct the original analog data”




- A bandlimited analog signal can be perfectly reconstructed from a sequence of samples if the sampling rate  $f_s$  exceeds  $2f_{\max}$  samples per second, where  $f_{\max}$  is the **highest frequency** in the original signal.

# ADC Basics

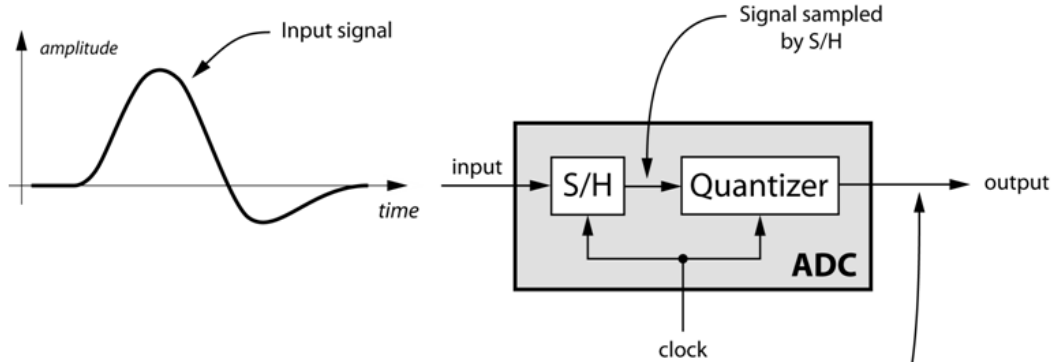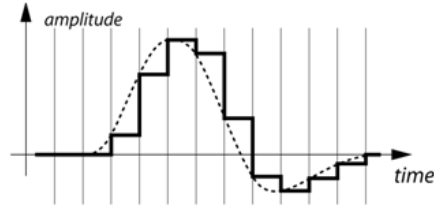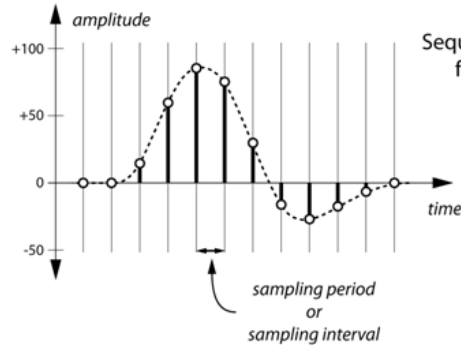Stage 1


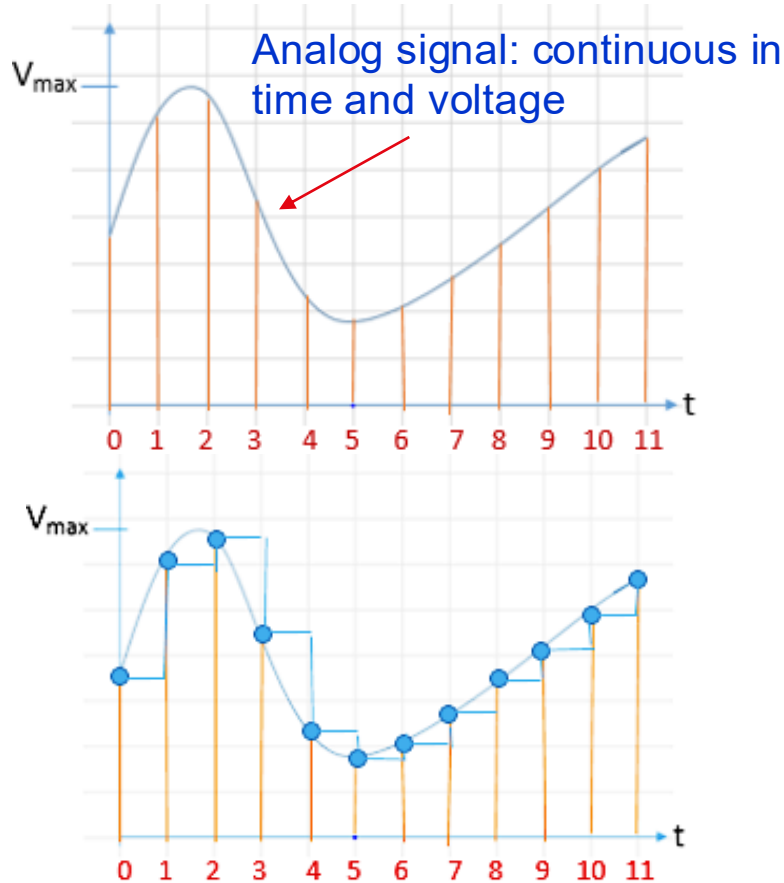


Stage 2

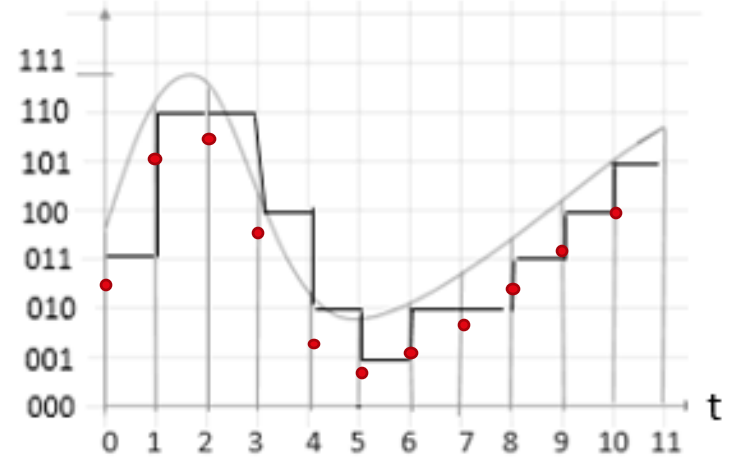


Sequence of numbers from quantizer

⇒ { ..., 0, 0, +15, +60, +85, +72, +28, -17, -30, -21, -8, -1, ... }


Sampling and HoldingQuantization and Encoding

Sequence of digital codes:  
 011, 110, 110, 100, 010, 001, 010, 010,  
 011, 100, 101, ...

# The least significant bit (LSB)

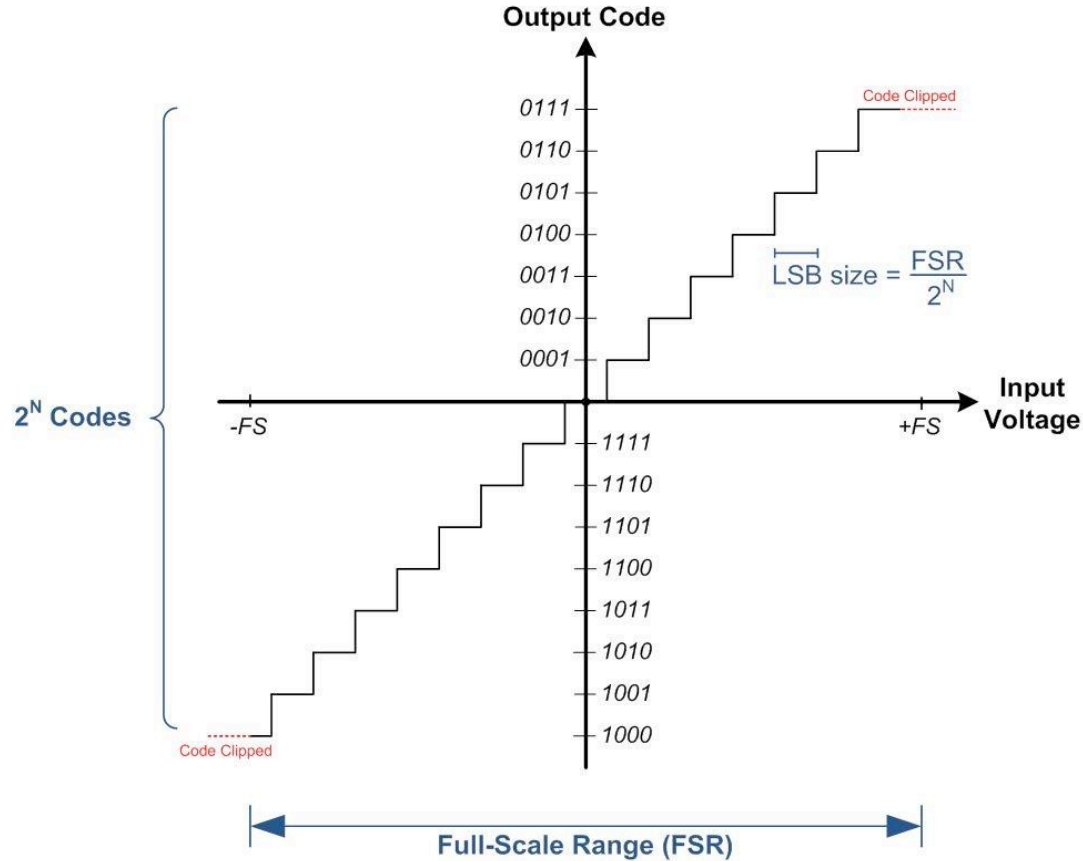

# 3-bit flash (parallel) ADC

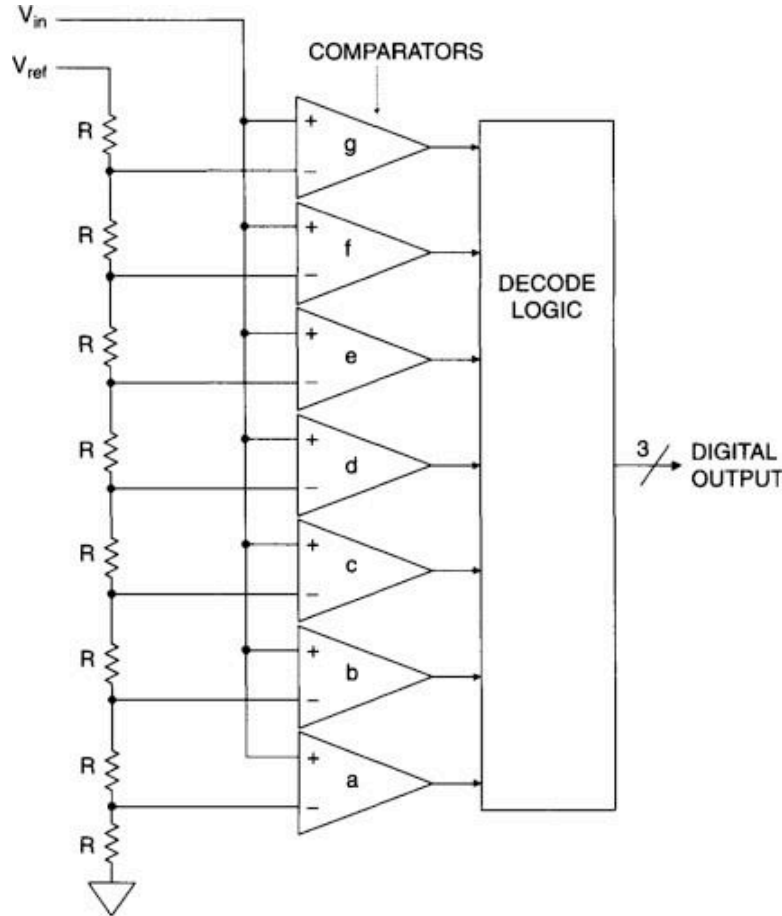

- An  $n$ -bit flash ADC uses  $2^n - 1$  comparators,  $2^n$  resistors and a decode logic.
- Pros: the fastest type of ADC.
- Cons: limited resolution, expensive, large power consumption
- Applications: Sampling oscilloscope and high-density disk drives

# Successive-approximation-register (SAR) ADC

