

## Exercise Sheet 12

Discussion 3.12.2025

### Exercise 1 - Impedance


- Find the complex impedance of a coil with self-inductance  $L$  and resistance  $R$  (of the wire in the coil) in parallel with a capacitor having an imperfect dielectric equivalent to a series resistance of also  $R$ .
- Find the value of  $R$  which makes the above impedance purely resistive (completely real) at all frequencies.
- Find a value of  $\omega$  which makes the impedance purely resistive for all values of  $R$ .

### Exercise 2 - Resonance

Consider an LCR circuit in series. In the lecture the current (or phase) resonance was derived. Using that the circulating charge is given by  $\frac{I}{\omega}$  derive the charge resonance, i.e. the frequency for which the charge is largest.
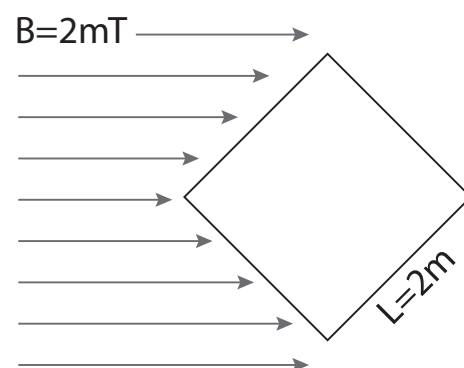
### Exercise 3 - Mu-Metal

A mu-metal box with  $\mu_r = 10^5$  is placed in a homogeneous magnetic field of 2 mT as shown in the figure to the right. How thick does the mu-metal have to be, to shield the magnetic field completely inside the box?



### Exercise 4 - Hysteresis

A ferromagnetic material is inserted and kept in a solenoid where you pass a current. By changing the current, you change the  $H$  field generated by the solenoid from an initial value of  $+h_0$  to  $-h_0$ , and then you come back to the initial one. If you plot the magnetization  $M$  as a function of the  $H$  field you have applied you obtain the graph on the left side ( $m_r = 200 \text{ A/m}$ ,  $m_s = 300 \text{ A/m}$ ,  $h_s = 1000 \text{ A/m}$ ).

- Describe this typical trend, explaining the physical situation in the important points of the hysteresis curve.
- We can simplify the hysteresis curve as in the figure on the right side. Use this simplification to evaluate the coercive  $H$  field. [*Hint: the coercive field is defined in the  $B(H)$  plot*]
- Determine the work done per unit volume on the magnet during the whole cycle. How is this energy dissipated?

