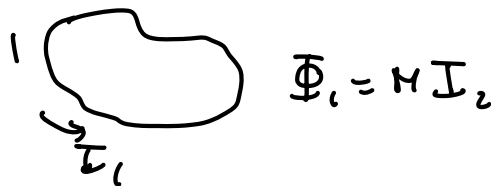


Lecture 20. Alternating current circuits

Last time:

* Mutual inductance M

$M \equiv$ proportionality constant between the mag flux induced on a loop due to a nearby loop



* Self inductance L

$\Phi = LI$ intrinsically geometrical positive.

* Magnetic energy stored in an inductor

$$U_B = \frac{1}{2} LI^2$$

* Kirchhoff's loop rule for inductors:


the "potential change" due to an inductor

$-L \left(\frac{dI}{dt} \right)$ if L is traversed in the direction of I

$L \left(\frac{dI}{dt} \right)$ if L is traversed in the direction opposite to I

Today: LC circuits and circuits with an AC source

Oscillations in LC circuit

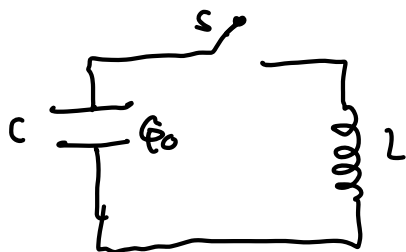

circuit where the capacitor has charge Q_0 at $t < 0$

At $t=0$ we close the switch \rightarrow capacitor begins to discharge \rightarrow current \rightarrow magnetic energy stored into inductor.

Since we don't have a resistance energy is transferred back & forth between capacitor & the inductor \rightarrow electromagnetic oscillation.

The total energy in the LC circuit at $t > 0$:

$$U = U_C + U_L = \frac{1}{2} \frac{Q^2}{C} + \frac{1}{2} L I^2 \leftarrow$$

$$\frac{dU}{dt} = 0 \quad \text{no energy dissipated}$$

$$\Rightarrow \frac{dU}{dt} = \frac{d}{dt} \left(\frac{1}{2} \frac{Q^2}{C} + \frac{1}{2} L I^2 \right) = \frac{Q}{C} \frac{dQ}{dt} + L I \frac{dI}{dt} = 0$$

$$\Rightarrow \frac{Q}{C} + L \frac{d^2 Q}{dt^2} = 0 \quad \text{since } I = -\frac{dQ}{dt} \text{ and } \frac{dI}{dt} = -\frac{d^2 Q}{dt^2}$$

We can also obtain this equation by applying Kirchhoff's rule:

$$\frac{Q}{C} - L \frac{dI}{dt} = 0$$

The solution for this eq is:

$$Q(t) = Q_0 \cos(\omega_0 t + \phi),$$

where

$Q_0 \equiv$ charge amplitude

$\phi \equiv$ phase

$\omega_0 \equiv$ angular frequency $= \frac{1}{\sqrt{LC}}$

We can now calculate the current:

$$I(t) = -\frac{dQ}{dt} = \omega_0 Q_0 \sin(\omega_0 t + \phi) = I_0 \sin(\omega_0 t + \phi)$$

\uparrow

$$I_0 = \omega_0 Q_0$$

From the initial conditions $Q(t=0) = Q_0$ and $I(t=0) = 0$ we can determine ϕ :

$$I(0) = I_0 \sin(\phi) = 0 \Rightarrow \phi = 0$$

Our expressions for Q and I are:


$$Q(t) = Q_0 \cos(\omega_0 t)$$

$$I(t) = I_0 \sin(\omega_0 t)$$

With this we can calculate expressions for electric & magnetic energy:

$$U_E = \frac{Q^2(t)}{2C}$$

$$U_B = \frac{1}{2} L I^2(t)$$

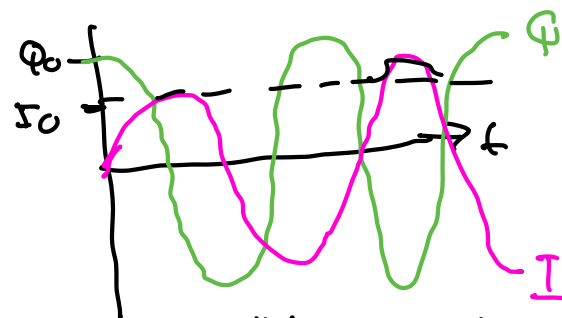

oscillating current
alternating current.

$$U_E = \left(\frac{\Phi_0^2}{2C} \right) \cos^2(\omega t)$$


$$U_B = \frac{L I_0^2}{2} \sin^2(\omega t) = \frac{L (-\omega_0 \Phi_0)^2 \sin^2(\omega_0 t)}{2}$$

$$= \left(\frac{\Phi_0^2}{2C} \right) \sin^2(\omega_0 t)$$


You can verify the total energy remains constant:

$$U = U_E + U_B = \left(\frac{\Phi_0^2}{2C} \right) \cos^2(\omega_0 t) + \left(\frac{\Phi_0^2}{2C} \right) \sin^2(\omega_0 t) =$$

$$= \frac{\Phi_0^2}{2C}$$

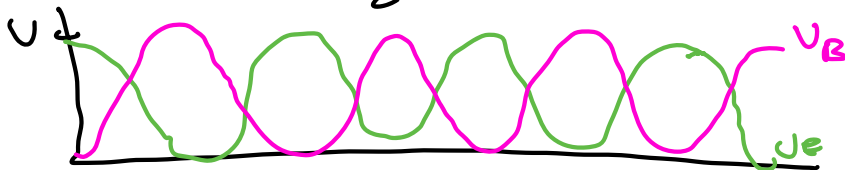

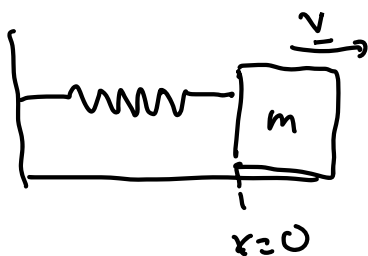this is analogous to a harmonic oscillator.




$$U = K + U_p = \frac{1}{2} m v^2 + \frac{1}{2} k x^2$$

since U is conserved $\frac{dU}{dt} = 0$

$$\frac{dU}{dt} = m v \frac{dv}{dt} + k x \frac{dx}{dt} = 0$$

$$\Rightarrow m \frac{d^2 x}{dt^2} + k x = 0$$

The RLC series circuit

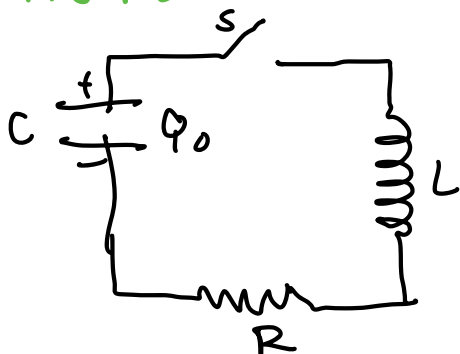

Capacitor with charge Q_0

close the switch at $t=0 \rightarrow$ current flows.

Energy will be dissipated by the resistance


$$\frac{dU}{dt} = -I^2 R$$

the energy is dissipated \rightarrow it decreases

Lecture 12
 $\frac{\Delta U}{\Delta t} = I \Delta V$ & since $V = IR$
 $\Rightarrow \frac{dU}{dt} = -R I^2$

The frequency f of an alternating current is expressed in cycles/second or Hertz (Hz). oscillations

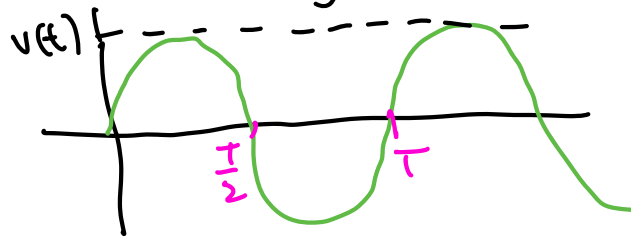The angular frequency $\omega = 2\pi f$ is assumed to be in radians/second.



T is the period
 $v(t) = v(t + T)$
 and recall angular frequency
 $f = \frac{1}{T}$ $\omega = 2\pi f$


If we connect an alternating voltage source to the RLC circuit, the oscillations will not die out.

An AC will flow into the circuit in response to this driving voltage. The current will be:

$$I(t) = I_0 \sin(\omega t - \phi)$$

The current oscillates with the same frequency as the voltage source and the amplitude of the current is I_0 .

Purely resistive load

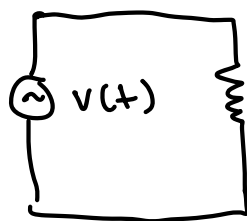

A resistor connected to an AC generator

$$v(t) = V_0 \sin(\omega t)$$

instantaneous voltage drop across the resistor.

Apply Kirchhoff's rule:

$$v(t) - V_R(t) = v(t) - I_R(t)R = 0$$

The voltage drop across the resistor


$$V_R(t) = I_R(t)R \Rightarrow I_R(t) = \frac{V_R(t)}{R} = \frac{V_0 \sin(\omega t)}{R}$$

$$= \frac{V_0 \sin(\omega t)}{R} = I_{R_0} \sin(\omega t)$$

We have defined


$$V_{R_0} = V_0 \text{ and } I_{R_0} = \frac{V_{R_0}}{R} \text{ is the maximum current.}$$

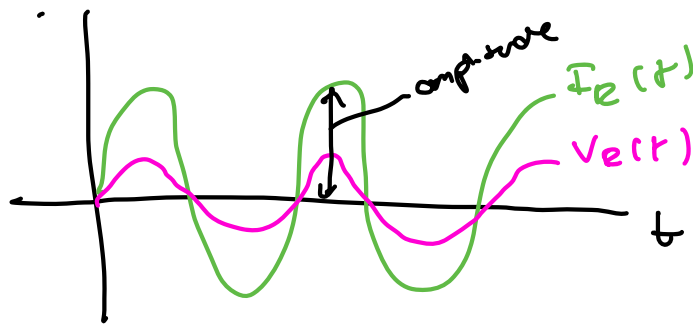in this case $\phi = 0 \Rightarrow$ current & voltage are in phase



current & voltage
are in phase

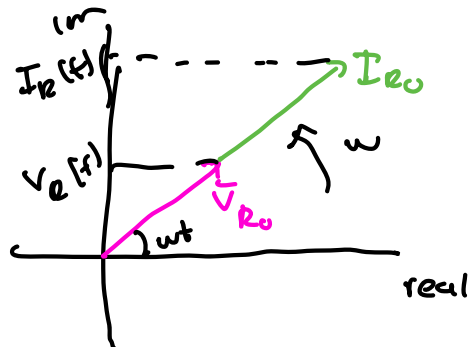We can represent this using a phasor diagram:



phasor is a rotating vector
with the following properties

i) length \rightarrow amplitude

ii) angular speed \rightarrow vector
rotates

counter-clockwise
with an angular speed ω

iii) The projection of the vector
along the vertical axis corresponds to
the value of the alternating quantity
at time t .

The average value of the current over a period.

$$\langle I_e(t) \rangle = \frac{1}{T} \int_0^T I_e(t) dt = \frac{1}{T} \int_0^T I_{e0} \sin \omega t dt = \frac{I_{e0}}{T} \int_0^T \sin \frac{2\pi t}{T} dt = 0$$

The average square of the current is non-vanishing:

$$\langle I_e^2(t) \rangle = \frac{1}{T} \int_0^T I_e^2(t) dt = I_{e0}^2 \frac{1}{T} \int_0^T \sin^2 \left(\frac{2\pi t}{T} \right) dt = \frac{1}{2} I_{e0}^2$$

It's convenient to define the root mean square (rms) current:

$$I_{rms} \equiv \left(\langle I_e^2(t) \rangle \right)^{1/2} = \frac{I_{e0}}{\sqrt{2}}$$

Similarly we can define root mean square voltage:


$$V_{rms} \equiv \left(\langle V_e^2(t) \rangle \right)^{1/2} \\ = \frac{V_{e0}}{\sqrt{2}}$$

The power dissipated by the resistor is:

$$P_R(t) = I_R(t)V_R(t) = I_R^2(t)R \quad \text{and its average over a period:}$$

$$\begin{aligned} \langle P_R(t) \rangle &= \langle I_R^2(t)R \rangle = \frac{1}{2} I_{R_0}^2 R = I_{rms}^2 R \\ &= I_{rms} V_{rms} = \frac{V_{rms}^2}{R} \end{aligned}$$

Purely inductive load

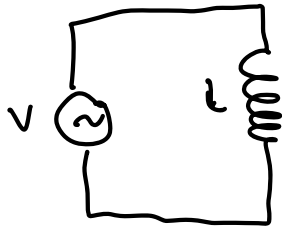

$$V(t) = V_0 \sin \omega t$$

Applying the modified Kirchhoff's rule for inductors

$$V(t) - V_L(t) = V(t) - L \frac{dI_L}{dt} = 0$$

$$\Rightarrow \frac{dI_L}{dt} = \frac{V(t)}{L} = \frac{V_{L0} \sin \omega t}{L} \quad \text{where } V_{L0} = V_0$$

Integrating this we find:

$$I_L(t) = \int dI_L = \frac{V_{L0}}{L} \int \sin \omega t = - \left(\frac{V_{L0}}{\omega L} \right) \cos \omega t$$

$$\Rightarrow \left(\frac{V_{L0}}{\omega L} \right) \sin \left(\omega t - \frac{\pi}{2} \right)$$

current & voltage are not in phase


since
 $-\cos \omega t = \sin \left(\omega t - \frac{\pi}{2} \right)$


$$I_{L0} = \frac{V_{L0}}{\omega L} = \frac{V_{L0}}{X_L}$$

where $X_L \equiv \omega L$ inductive reactance

$[X_L] = \text{Ohms}$ depends linearly with ω

and $\phi = \frac{\pi}{2}$

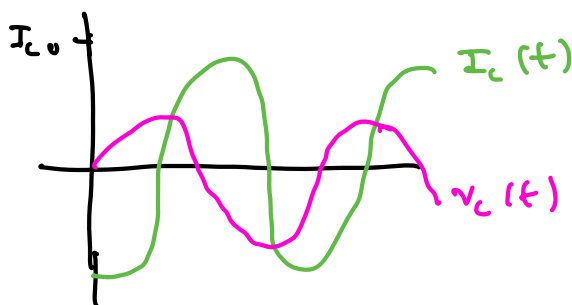


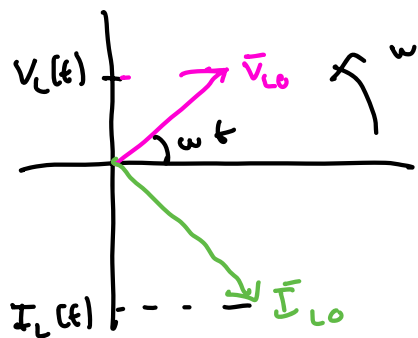

$I_L(t)$ is out of phase with $V_L(t)$ by $\phi = \frac{\pi}{2}$. It reaches its max value after $V_L(t)$ does by $\frac{1}{4}$ cycle

The current lags the voltage by $\pi/2$ in a purely inductive circuit

Purely capacitive load

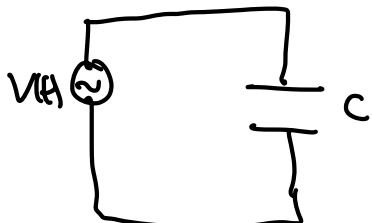

$$V(t) = V_0 \sin \omega t$$

Using Kirchhoff's rule:

$$V(t) - V_C(t) = V(t) = -\frac{Q(t)}{C} = 0$$

$$\Rightarrow Q(t) = CV(t) = CV_C(t) = CV_0 \sin \omega t$$

where $V_0 = V_0$

with rms we can get the current

$$I_C(t) = \frac{dQ}{dt} = \omega CV_0 \cos \omega t = \omega CV_0 \sin \left(\omega t + \frac{\pi}{2} \right)$$


$$\cos \omega t = \sin \left(\omega t + \frac{\pi}{2} \right)$$


$$I_{C0} = \omega CV_0 = \frac{V_{C0}}{X_C} \quad \text{where } X_C \equiv \text{capacitance reactance} = \frac{1}{\omega C}$$

$$\phi = -\frac{\pi}{2}$$

$$[X_C] = \text{Ohms}$$


The current & voltage diagrams are:

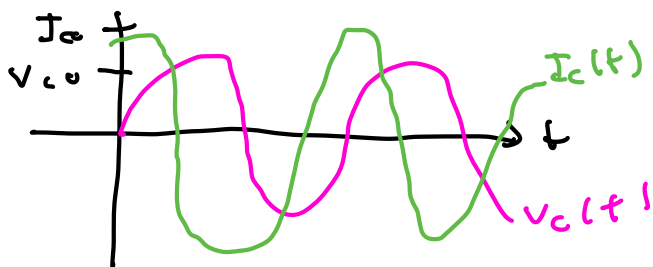

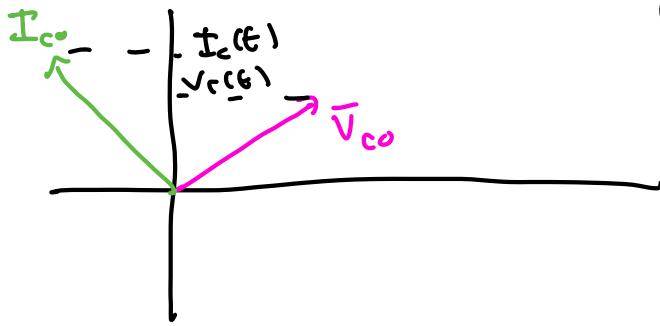

The current leads the voltage by $\frac{\pi}{2}$ in a capacitive circuit.

The RLC series circuit

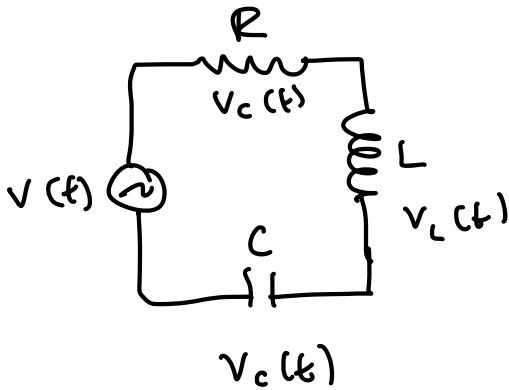

Applying the loop rule:

$$v(t) = -V_R(t) - V_L(t) - V_C(t)$$

$$\Rightarrow v(t) - IR - L \frac{dI}{dt} - \frac{Q}{C} = 0$$

$$\Rightarrow L \frac{dI}{dt} + IR + \frac{Q}{C} = V_0 \sin \omega t$$

Assuming initially the capacitor is uncharged $I = \frac{dQ}{dt}$

$$L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = V_0 \sin \omega t$$

A possible solution $Q(t) = Q_0 \cos(\omega t - \phi)$

where the amplitudes and the phases are

$$Q_0 = \frac{V_0}{L}$$

$$\left[\left(R\omega/L \right)^2 + \left(\omega^2 - 1/LC \right)^2 \right]^{1/2}$$

$$= \frac{V_0}{\omega \sqrt{R^2 + (X_L - X_C)^2}} \quad \text{and}$$

$$\tan \phi = \frac{1}{R} \left(\omega L - \frac{1}{\omega C} \right) = \frac{X_L - X_C}{R}$$

The corresponding current is:

$$i(t) = \frac{d\phi}{dt} = I_0 \sin(\omega t - \phi)$$


the amplitude $I_0 = -Q_0 \omega = \frac{-V_0}{\sqrt{R^2 + (X_L - X_C)^2}}$

* The current has the same amplitude and phase at all points in the RLC circuit

* The instantaneous voltage drop across all elements has a different amplitude & phase relation with the current.


Drawing a phasor diagram:

in the resistor (R)

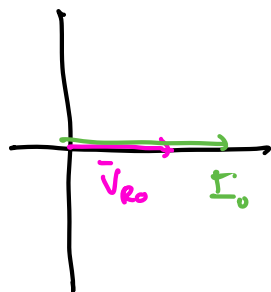


in phase

in the inductor (L)

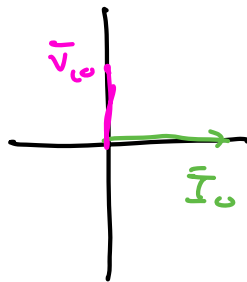

current lags
the voltage by $\pi/2$

in the capacitor (C)

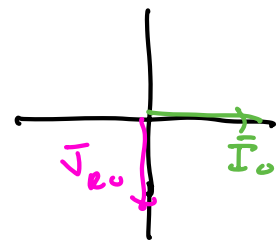

the current leads the
voltage by $\pi/2$

We can obtain the instantaneous voltages:

$$V_R(t) = I_0 R \sin \omega t = V_{R0} \sin \omega t$$

$$V_L(t) = I_0 X_L \sin \left(\omega t + \frac{\pi}{2} \right) = V_{L0} \cos \omega t$$

$$V_C(t) = I_0 X_C \sin \left(\omega t - \frac{\pi}{2} \right) = -V_{C0} \cos \omega t$$

where



$$V_{R0} = I_0 R, \quad V_{L0} = I_0 X_L, \quad V_{C0} = I_0 X_C$$

The sum of all 3 is equal to the instantaneous voltage supplied by the AC source

$$v(t) = V_R(t) + V_L(t) + V_C(t)$$

Or in phasor representation:
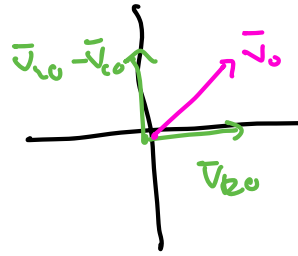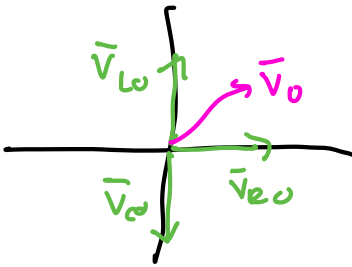
$$\bar{V}_0 = \bar{V}_{R0} + \bar{V}_{L0} + \bar{V}_{C0}$$



$$V_0 = |\bar{V}| = |\bar{V}_{R0} + \bar{V}_{L0} + \bar{V}_{C0}|$$

$$= [V_{R0}^2 + (V_{L0} - V_{C0})^2]^{1/2}$$

$$= [(I_0 R)^2 + (I_0 X_L - I_0 X_C)^2]^{1/2} = I_0 \underbrace{[R^2 + (X_L - X_C)^2]^{1/2}}$$

Voltages are not in phase

$$V_0 \neq V_{R0} + V_{L0} + V_{C0}$$

max amplitude of the source
is not equal to the sum of the
max amplitudes across each
element

Impedance

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$[Z] \equiv \text{Ohm } \Omega$$

effective resistance
in an RLC circuit
(in series).