

# Quantization of a Harmonic Oscillator

— Utilizing Lagrange Equation

Zhuoya Yuan


18.09.2025

# Outline of the Presentation


- Brief Introduction on Quantum Electrical Circuits
- Quantization with Symmetrization Postulate
- Quantization with Lagrange Equation
  - ① Revision on Lagrangian and Hamiltonian Mechanics
  - ② The Algorithm of Quantization
  - ③ Comparison between Symmetrization Postulate and Lagrange Equation
- Summary to the Topic: Questions List
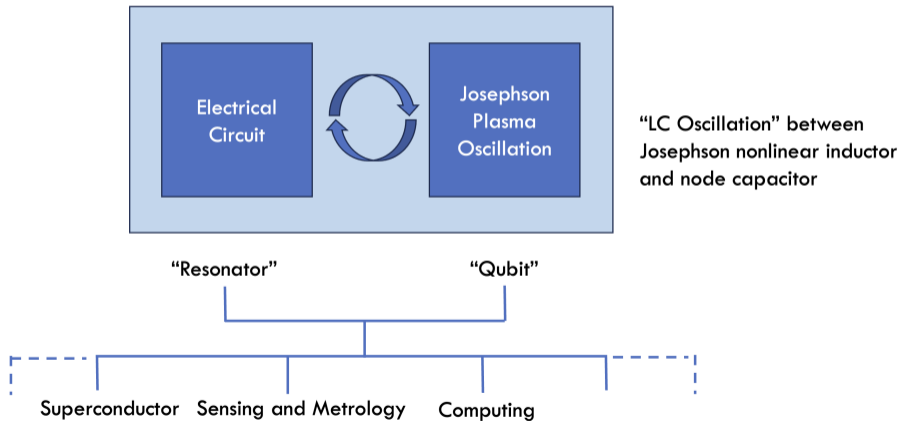
# Quantum Electrical Circuits

- The coupling between electrical oscillators and plasma oscillations in the Josephson junction


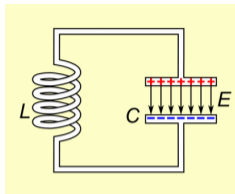
# Quantify LC Circuit Oscillation: Symmetrization Postulate



$$\textcircled{1} H = \frac{1}{2}CU^2 + \frac{1}{2}LI^2 = \frac{1}{2}C \left(\frac{Q}{C}\right)^2 + \frac{1}{2}L \left(\frac{\Phi}{L}\right)^2$$

$$\textcircled{2} \alpha(t) = \frac{\Phi(t)}{A} + i\frac{Q(t)}{B} \quad \alpha^*(t) = \frac{\Phi(t)}{A} - i\frac{Q(t)}{B}$$

$$\textcircled{3} H = \frac{AB}{\sqrt{LC}}(\alpha\alpha^* + \alpha^*\alpha) \quad AB = \frac{\hbar}{2}$$

$\textcircled{4}$  **Quantization:** introducing the canonically conjugate variables

$$\Phi \rightarrow \hat{\Phi}, Q \rightarrow \hat{Q} \quad [\hat{\Phi}, \hat{Q}] = i\hbar \quad \alpha \rightarrow \hat{a}, \alpha^* \rightarrow \hat{a}^\dagger \quad [\hat{a}, \hat{a}^\dagger] = 1$$

$$\hat{H} = \frac{\hbar}{2\sqrt{LC}}(\hat{a}\hat{a}^\dagger + \hat{a}^\dagger\hat{a}) = \frac{\hbar}{\sqrt{LC}}(\hat{a}^\dagger\hat{a} + \frac{1}{2})$$

$$\textcircled{5} \text{Zero point fluctuation: } \Phi_{2pf}^2 = \langle 0|\hat{\Phi}^2|0\rangle = A^2 = \frac{\hbar}{2}\sqrt{\frac{L}{C}} \quad Q_{2pf}^2 = \langle 0|\hat{Q}^2|0\rangle = B^2 = \frac{\hbar}{2}\sqrt{\frac{C}{L}}$$

# Quantify LC Circuit Oscillation: Lagrangian and Hamiltonian

- Lagrange Equation

The system can be characterized by generalized coordinates  $(q_1, q_2, \dots)$  and  $t$

Define  $\mathcal{L} = T - V$   $T = T(\dot{q}_1, \dot{q}_2, \dots)$ ,  $V = V(q_1, q_2, \dots)$

Lagrange Equation:  $\frac{d}{dt} \left( \frac{\partial \mathcal{L}}{\partial \dot{q}_\alpha} \right) = \frac{\partial \mathcal{L}}{\partial q_\alpha}$

- Hamiltonian Canonical Equation

Define generalized momentum:  $p_\alpha = \frac{\partial \mathcal{L}}{\partial \dot{q}_\alpha}$

Hamiltonian is defined:  $H = \sum_\alpha p_\alpha \dot{q}_\alpha - \mathcal{L}$

# Quantify LC Circuit Oscillation: Lagrangian and Hamiltonian

- Poisson Bracket

The Poisson Bracket of  $f(q_1, q_2, \dots, p_1, p_2, \dots, t)$  and  $g(q_1, q_2, \dots, p_1, p_2, \dots, t)$  is defined as:  $\{f, g\} = \sum_i \left( \frac{\partial f}{\partial q_i} \frac{\partial g}{\partial p_i} - \frac{\partial f}{\partial p_i} \frac{\partial g}{\partial q_i} \right)$

Asymmetric relation:  $\{f, g\} = -\{g, f\}$

For conjugate pair, the commutation relation is:  $\{q_i, p_j\} = \delta_{ij}$ ,  $\{q_i, q_j\} = 0$ ,  $\{p_i, p_j\} = 0$

Quantization is  $\{q, p\} = 1 \rightarrow \frac{1}{i\hbar} [\hat{q}, \hat{p}] = 1$

## Quantify LC Circuit Oscillation: Lagrangian Approach


- 1  $I = \dot{q}$ , let  $q$  be the generalized coordinate of this system
- 2 Lagrangian  $\mathcal{L} = T - V = T(\dot{q}) - V(q) = \frac{1}{2}L\dot{q}^2 - \frac{1}{2}\frac{q^2}{C}$
- 3 Lagrange Equation:  $\frac{d}{dt}\left(\frac{\partial\mathcal{L}}{\partial\dot{q}}\right) = \frac{\partial\mathcal{L}}{\partial q}$ ,  $\ddot{q} = -\frac{1}{LC}q = -\Omega^2q$
- 4 **The momentum conjugate** of  $q$  is the generalized momentum of the system:  
 $\frac{\partial\mathcal{L}}{\partial\dot{q}} = L\dot{q} = \Phi$ , which is also the generalized node fluxes:  $\Phi = \int^t U(\tau)d\tau$
- 5 Generalized coordinate  $q$  and generalized momentum  $\Phi$  form the Poisson Bracket:  
 $\{q, \Phi\} = 1$
- 6 Hamiltonian:  $H = \dot{\Phi}q - \mathcal{L} = \frac{1}{2}\frac{q^2}{C} + \frac{1}{2}\frac{\Phi^2}{L}$
- 7 Quantization is  $\{q, \Phi\} \rightarrow \frac{1}{i\hbar}[\hat{q}, \hat{\Phi}]$ . Let  $\hat{a} = \frac{1}{\sqrt{2C\hbar\Omega}}\hat{q} + i\frac{1}{\sqrt{2L\hbar\Omega}}\hat{\Phi}$ ,  $\hat{a}^\dagger = \frac{1}{\sqrt{2C\hbar\Omega}}\hat{q} - i\frac{1}{\sqrt{2L\hbar\Omega}}\hat{\Phi}$   
 $[\hat{q}, \hat{\Phi}] = i\hbar \rightarrow [\hat{a}, \hat{a}^\dagger] = 1$ ,  $\hat{H} = \hbar\Omega(\hat{a}^\dagger\hat{a} + \frac{1}{2})$

## Quantify LC Circuit Oscillation: Lagrangian Approach


- 1 Similarly, if the generalized node flux  $\Phi$  is the generalized coordinate of this system
- 2 Lagrangian  $\mathcal{L} = T - V = T(\dot{\Phi}) - V(\Phi) = \frac{1}{2} \frac{\Phi^2}{L} - \frac{1}{2} C \dot{\Phi}^2$
- 3 Lagrange Equation:  $\frac{d}{dt} \left( \frac{\partial \mathcal{L}}{\partial \dot{\Phi}} \right) = \frac{\partial \mathcal{L}}{\partial \Phi}$
- 4 The momentum conjugate of  $\Phi$  is the generalized momentum of the system:  
 $\frac{\partial \mathcal{L}}{\partial \dot{\Phi}} = -C \dot{\Phi} = C \mathcal{E}_L = -CU = -q$
- 5 Generalized coordinate  $\Phi$  and generalized momentum  $-q$  fulfill the Poisson Bracket:  
 $\{\Phi, -q\} = 1$
- 6 Quantization:  $\{\Phi, -q\} = 1 \rightarrow [\hat{\Phi}, -\hat{q}] = i\hbar$

# Quantify LC Circuit Oscillation: Comparison

## Symmetrization Postulate

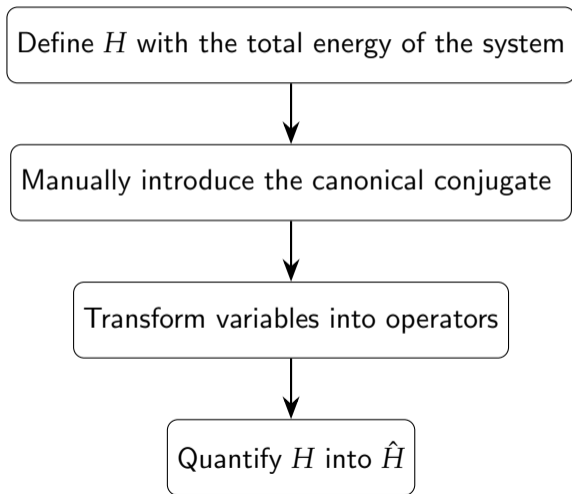

## Lagrangian Approach

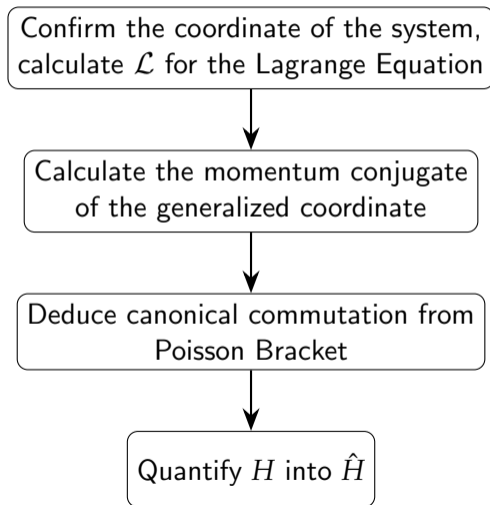

## Summary to the Question List

- 1 What is the algorithm for the quantization procedure using Lagrangian mechanics?
- 2 What is the main benefit of the Lagrangian approach compared to the approach utilizing symmetrization postulate?
  - ▶ Deduce canonical commutation relation directly from Hamiltonian Mechanics, without doing manually hypothesis, making it easier and clearer to figure out the canonical commutator
- 3 How does one identify the variables that should become operators with the canonical commutator?
  - ▶ Generalized coordinate and its conjugate momentum should be the canonical commutators
- 4 What is the classical analog of the canonical commutation relation?
  - ▶ Poisson Bracket, and the quantization is  $\{q, p\} \rightarrow \frac{1}{i\hbar} [\hat{q}, \hat{p}]$
- 5 What are the generalized node fluxes? How are they defined? How do they correspond to other possible variables (charges, currents, voltages, magnetic fluxes through inductors)?
  - ▶ Generalized node flux is particularly defined in electrical circuit oscillators, as the integral of node voltage:  $\Phi = \int^t U(\tau) d\tau = L\dot{q} = LI$ , which is the magnetic fluxes through inductors of the LC circuit