

Digital Logic Circuits

Arithmetic Circuits


CS-173 Fundamentals of Digital Systems

Mirjana Stojilović

Spring 2025


Previously on FDS

 Logic synthesis, NAND and NOR networks,
Don't care conditions, XOR and XNOR gates,
seven-segment display, and multiplexers



Previously

 - Learned **sum-of-products** and **product-of-sums** forms for logic synthesis
 - From truth tables to logic circuits
- Discover techniques to convert an AND/OR/NOT logic network to a NAND-only or NOR-only equivalent
- Discovered the **don't care conditions** and saw how using them wisely can help build efficient circuits
- Learned about **XOR** and **XNOR** gates
- Built multiplexers (**MUX**)




Let's Talk About...

...Ways to build arithmetic circuits



Learning Outcomes

 - Build basic arithmetic circuits for integer addition and subtraction
 - one-bit addition
 - one-bit subtraction
 - n-bit addition and subtraction in two's complement
- Find the worst-case circuit delay (i.e., the critical path delay)
- Build faster adders; reason about the advantages and disadvantages
- Use multiplexers for shifting efficiently



Quick Outline

- Adders
 - Half-adder
 - Full-adder
 - Ripple-carry adder
- Subtractors
 - Full-subtractor
 - Ripple-carry subtractor
- Adders-Subtractors
 - Ripple-carry adder-subtractor
- Fast adders
 - Delay as performance metric
 - Full-adder
 - Full adder-subtractor
 - Ripple-carry adder-subtractor
 - Carry-select adder
- Shifters
 - Barrel shifter
 - Right
 - Bidirectional


Adders

- Half-adder
- Full-adder
- Ripple-carry adder



Addition of Two 1-Bit Binary Numbers

 - Let us start from the simplest binary addition of one-bit numbers
 - The resulting sum is at most on two bits:
 - the rightmost bit is called **sum** (s)
 - the leftmost bit is called **carry** (c); it is produced as a carry-out when both bits being added are logical one



- Corresponding circuit is called **half-adder (HA)**

Half-Adder

Addition of Two 1-Bit Binary Numbers without the Input Carry

- Truth table


		sum	Carry
<i>x</i>	<i>y</i>	<i>s</i>	<i>c</i>
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

- Logical expressions

$$s = \bar{x}y + x\bar{y} = x \oplus y$$

$$c = xy$$

- Digital logic circuit

 

- Graphical symbol



Addition of Two N-Bit Binary Numbers

- A binary n -bit adder has two operands $0 \leq x, y \leq 2^n - 1$ and a carry-in $c_{in} \in \{0, 1\}$ as inputs, and produces as outputs
 - sum $0 \leq s \leq 2^n - 1$ and
 - carry-out $c_{out} \in \{0, 1\}$ such that

$$x + y + c_{in} = 2^n c_{out} + s$$

- The solution to the above equation:

$$s = (x + y + c_{in}) \bmod 2^n$$


$$\begin{aligned} c_{out} &= \begin{cases} 1 & \text{if } (x + y + c_{in}) \geq 2^n \\ 0 & \text{otherwise} \end{cases} \\ &= \lfloor (x + y + c_{in}) / 2^n \rfloor \end{aligned}$$

Addition of Two N-Bit Binary Numbers

- It is **impractical** to start from the truth tables for n -bit addition

- Iterative approach:

 - Add each pair of bits at the position i , $0 \leq i < n$
- The addition at the bit position i needs to include a carry-in at the position i (i.e., carry-out from the position $i - 1$); it also generates a carry-in for the position $i + 1$



- The 1-bit adder reduces to a primitive module called **full-adder (FA)** with three binary inputs and two binary outputs such that

$$x_i + y_i + c_i = 2c_{i+1} + s_i$$

Full-Adder

Addition of Two 1-Bit Binary Numbers with the Input Carry (i.e., three 1-bit numbers)

- Truth table

x_i	y_i	c_i	s_i	c_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- Logical expressions

$$\begin{aligned}s_i &= \overline{x_i} \overline{y_i} c_i + \overline{x_i} y_i \overline{c_i} + x_i \overline{y_i} \overline{c_i} + x_i y_i c_i \\&= (x_i y_i + \overline{x_i} \overline{y_i}) c_i + (\overline{x_i} y_i + x_i \overline{y_i}) \overline{c_i} \\&= \overline{(x_i \oplus y_i)} c_i + (x_i \oplus y_i) \overline{c_i} = x_i \oplus y_i \oplus c_i\end{aligned}$$


$$\begin{aligned}c_{i+1} &= \overline{x_i} y_i c_i + x_i \overline{y_i} c_i + x_i y_i \overline{c_i} + x_i y_i c_i \\&= (\overline{x_i} y_i + x_i \overline{y_i}) c_i + x_i y_i (\overline{c_i} + c_i) \\&= (x_i \oplus y_i) c_i + x_i y_i\end{aligned}$$

- Further optimized:

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

Full-Adder From Half-Adders

Modular Implementation

 

- Recall half-adder


$$s = \bar{x}y + x\bar{y} = x \oplus y$$

$$c = xy$$

- Full-adder

$$s_i = x_i \oplus y_i \oplus c_i$$
 
$$c_{i+1} = (x_i \oplus y_i)c_i + x_i \cdot y_i$$



Full-Adder

Graphical Symbol


- Final logical expressions

$$s_i = x_i \oplus y_i \oplus c_i$$


$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

- Graphical symbol

- Easy chaining

 

- Digital logic circuit

 



Basic Ripple-Carry Adder (RCA)

Adding Two N-bit Binary Numbers

- Starting from the least-significant digit, we add pairs of digits, progressing to the most-significant digit
- Carry “ripples” through the adder stages
 
$$\begin{array}{r} \dots & c_{i+1} & c_i & \dots \\ & \dots & \dots & x_i & \dots \\ + & \dots & \dots & y_i & \dots \\ \hline \dots & \dots & \dots & s_i & \dots \end{array}$$



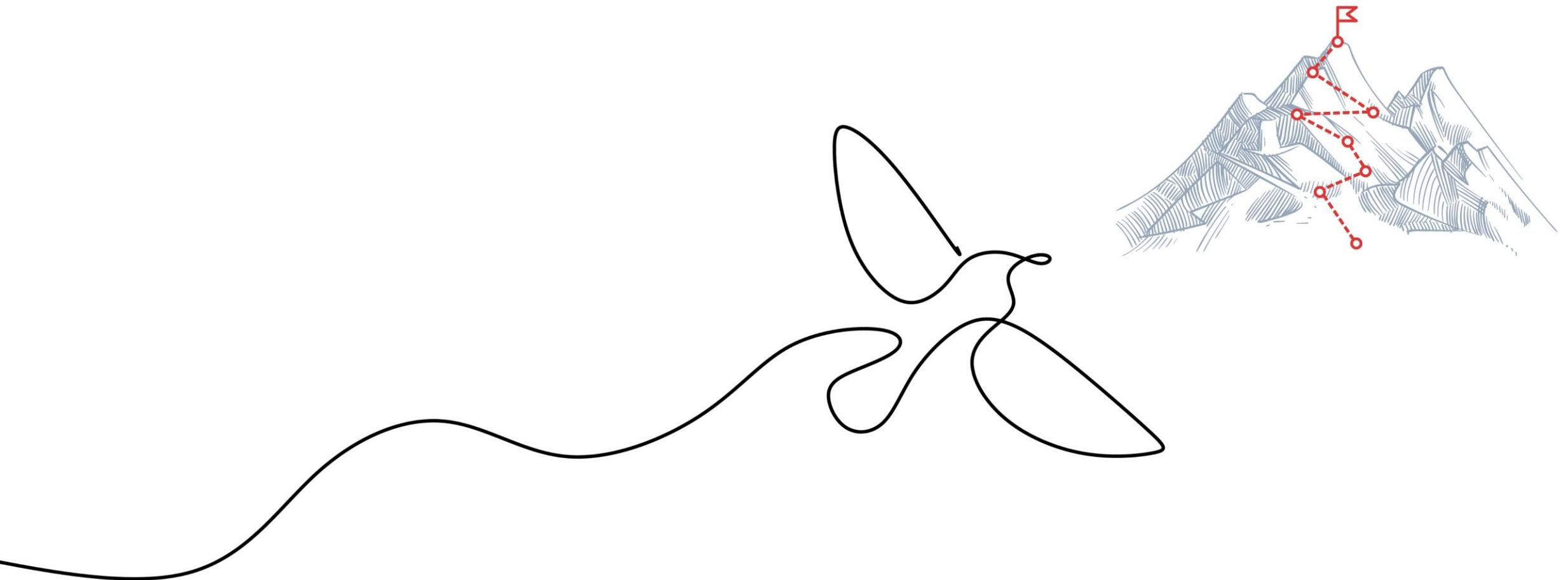


Subtractors

Arithmetic circuits




Subtraction of Two 1-Bit Binary Numbers

 - Recall binary subtraction of two 1-bit binary numbers
 - Subtraction generates two bits:
 - difference** (d), the result of the subtraction,
 - borrow** (b), produced as a borrow-out when the subtrahend is larger than minuend



Subtraction of Two N-Bit Unsigned Numbers

 - It is **impractical** to start from the truth tables for n -bit subtraction
- Iterative approach
 - Subtract each pair of bits at the position $i, 0 \leq i < n$
 - The subtraction at the bit position i needs to include a borrow-in at position i (i.e., borrow-out from the position $i - 1$); it also generates a borrow-in for position $i + 1$



Full Subtractor

Subtraction of Two 1-Bit Binary Numbers Taking into Account the Input Borrow


- Truth table

x_i	y_i	b_i	d_i	b_{i+1}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$\begin{aligned}d_i &= \overline{x_i} \overline{y_i} b_i + \overline{x_i} y_i \overline{b_i} + x_i \overline{y_i} \overline{b_i} + x_i y_i b_i \\&= (\overline{x_i} \overline{y_i} + x_i y_i) b_i + (\overline{x_i} y_i + x_i \overline{y_i}) \overline{b_i} = \overline{(x_i \oplus y_i)} b_i + (x_i \oplus y_i) \overline{b_i} \\&= x_i \oplus y_i \oplus b_i\end{aligned}$$

$$\begin{aligned}b_{i+1} &= \overline{x_i} \overline{y_i} b_i + \overline{x_i} y_i \overline{b_i} + \overline{x_i} y_i b_i + x_i y_i b_i \\&\quad 7b. \quad x + x = x \quad 8b. \quad x + \bar{x} = 1 \\&= (\overline{x_i} \overline{y_i} b_i + \overline{x_i} y_i b_i) + (\overline{x_i} y_i \overline{b_i} + \overline{x_i} y_i b_i) + (\overline{x_i} y_i b_i + x_i y_i b_i) \\&= \overline{x_i} b_i + \overline{x_i} y_i + y_i b_i\end{aligned}$$

- Graphical symbol
 - Easy chaining

 


N-Bit Ripple-Carry Subtractor

Subtracting Two N-bit Binary Numbers

- Starting from the least-significant digit, we subtract pairs of digits, progressing to the most-significant digit
 
$$\begin{array}{r} \dots & b_{i+1} & b_i & \dots \\ \dots & \dots & x_i & \dots \\ - & \dots & y_i & \dots \\ \hline \dots & \dots & d_i & \dots \end{array}$$



Adders-Subtractors

...in Two's complement



Adders-Subtractors in Two's Complement

- Recall that subtracting two numbers in two's complement format requires using the two's complement of one operand:

$$X - Y = X + \bar{Y} + 1$$

- \bar{Y} is obtained by complementing every bit of Y
- Assume a control signal op determines which **operation** to perform ($op = 0$: addition, $op = 1$: subtraction)

Adders-Subtractors in Two's Complement

- Assume a control signal op determines which **operation** to perform ($op = 0$: addition, $op = 1$: subtraction)

$$f(X, Y) = \begin{cases} X + Y, & \text{if } op = 0 \\ X + \bar{Y} + 1, & \text{otherwise} \end{cases}$$

$$f(X, Y, op) = \overline{op}(X + Y) + op(X + \bar{Y} + 1)$$

$$f(X, Y, op) = (\overline{op} + op)X + \overline{op}Y + op\ \bar{Y} + op$$

$$f(X, Y, op) = X + \overline{op}\ Y + op\ \bar{Y} + op$$

\oplus


$$f(X, Y, op) = X + op \oplus Y + op$$


N-Bit Ripple-Carry Adder-Subtractor

Two's Complement

- One circuit, able to perform two operations

$$f(X, Y, op) = X + op \oplus Y + op$$

 

 

Fast Adders

Carry Select vs. Ripple-Carry Adders



Performance Matters

- Addition and subtraction are fundamental operations performed frequently
 - How quickly a result can be produced greatly impacts the system's performance
 - Performance is determined by the worst-case delay
- System's value is measured as a ratio:
$$value = \frac{performance}{price}$$
- A large performance improvement can often be achieved at a modest price/cost increase



Full-Adder

Input-to-Output Delay, Assuming All Inputs are Available at time t = 0

- Delay to generate the sum

$$\begin{aligned} t(x_i, s_i) &= t(y_i, s_i) = t(c_i, s_i) \\ &= t(\text{XOR}) \end{aligned}$$

- Delay to generate carry-out


$$\begin{aligned} t(x_i, c_{i+1}) &= t(y_i, c_{i+1}) = t(c_i, c_{i+1}) \\ &= t(\text{AND}) + t(\text{OR}) \end{aligned}$$

- Worst-case delay

$$\begin{aligned} t_{\max} &= \max(t(s_i), t(c_{i+1})) \\ &= \max(t(\text{XOR}), t(\text{AND}) + t(\text{OR})) \end{aligned}$$

- If all gates had equal delays

 $t_{\max} = t(c_{i+1}) = 2 \text{ Gate Delays}$



Full Adder-Subtractor

Input-to-Output Delay, Assuming All Inputs are Available at time $t = 0$

- Delay to generate the sum

$$t(x_i, s_i) = t(c_i, s_i) = t(\text{XOR})$$

$$t(y_i, s_i) = t(op, s_i) = 2t(\text{XOR})$$

- Delay to generate carry-out

$$t(x_i, c_{i+1}) = t(c_i, c_{i+1}) = t(\text{AND}) + t(\text{OR})$$

$$t(y_i, c_{i+1}) = t(op, c_{i+1}) = t(\text{XOR}) + t(\text{AND}) + t(\text{OR})$$


- Worst-case delay

$$t_{\max} = \max(t(s_i), t(c_{i+1}))$$

$$= \max(2t(\text{XOR}), t(\text{XOR}) + t(\text{AND}) + t(\text{OR}))$$

- If all gates had equal delays:
 
$$t_{\max} = t(c_{i+1}) = 3 \text{ Gate Delays}$$






Basic Ripple-Carry Adder-Subtractor

- What is the **worst-case delay** to find the sum/difference using a basic ripple carry adder-subtractor?
 - Assume the inputs X , Y , and op are available (no waiting to start)
 - Assume all gates have the same delay
- Note: Worst-case delay is commonly referred to as **critical path delay (CPD)**

- **A:** $(2n + 1)$ gate delays

 




Basic Ripple-Carry Adder/Subtractor

■ Solution:

- The worst-case delay is on the path from the op input to the last carry-out output

$$t_{\max} = t_{\max}(c_1) + (n - 2)t(c_i, c_{i+1}) + t_{\max}(t(c_{n-1}, c_n), t(c_{n-1}, s_{n-1}))$$
 
$$t_{\max} = t(\text{XOR}) + t(\text{AND}) + t(\text{OR}) + (n - 2)(t(\text{AND}) + t(\text{OR})) + t(\text{AND}) + t(\text{OR})$$




If all gates have equal delays:

$$t_{\max} = 3 + (n - 2) \cdot 2 + 2 = (2n + 1) \text{ Gate Delays}$$


RCA Performance Issues

 - With the increasing number of bits n , the ripple-carry adder delay increases, and the computation becomes prohibitively slow
- What can be done to make the adder faster?
- A variety of faster implementations exist
 - Switched carry-ripple adder, carry-skip adder, carry-lookahead adder, prefix-adder, conditional-sum adders, ...
 - All but the carry-select adder are **out of scope for CS-173**




Carry-Select Adder

 - **Idea:** Cut the long carry propagation chain in half to save time




Carry-Select Adder, Contd.

 


- How can we compute the carry-in for the second half?
 - Compute **twice**: once for carry-in = 0, once for carry-in = 1
 - Compute **in parallel (double the gates) to save time**
 - Once carry-in is known, use it to select the corresponding sum and carry-out

Carry-Select Adder

Block Diagram

 

 

Shifting

Barrel Shifters




Barrel Shifter

- A **barrel shifter** is a combinational logic circuit with n data inputs, n data outputs, and a set of control inputs that specify how to shift the data between the input and the output
- A barrel shifter inside a processor can typically specify
 - **direction** of shift (left, right)
 - **type** of shift (logical, arithmetic, circular/rotation)
 - **amount** of shift (typically 0 to $n - 1$ bits)
- Implemented as a **sequence of multiplexers** (MUX), each shifting their input by twice as many positions as the previous MUX

Shift Right

By Up to **One** Position

 - **Logical** shift resets the leading bit of the output: $l = 0$
- **Arithmetic** (sign-preserving) shift: $l = x_7$ = Most-significant bit




- Truth table

s_0	$z_7 z_6 z_5 z_4 z_3 z_2 z_1 z_0$
0	$x_7 x_6 x_5 x_4 x_3 x_2 x_1 x_0$
1	$l x_7 x_6 x_5 x_4 x_3 x_2 x_1$

Shift Right

By Up to Three Positions

 


- Truth table
 - Select signals encode the number of positions to shift by (e.g., $s_1 s_0 = (10)_2$ shifts by two places)

s_1	s_0	$z_7 z_6 z_5 z_4 z_3 z_2 z_1 z_0$
0	0	$x_7 x_6 x_5 x_4 x_3 x_2 x_1 x_0$
0	1	$lx_7 x_6 x_5 x_4 x_3 x_2 x_1$
1	0	$llx_7 x_6 x_5 x_4 x_3 x_2$
1	1	$lllx_7 x_6 x_5 x_4 x_3$

Shift Right

By Up to Three Positions, Contd.

 
- Nothing new, just a somewhat more compact drawing



Shift Right

By Up to **Seven** Positions

- Three levels of multiplexing

 

Bidirectional Shifter


By Up to **Seven** Positions

$dir = 0$: Right

$dir = 1$: Left

$l = 0$: Logical shift right or shift left

$l = x_7$: Arithmetic shift right

 

Bidirectional Shifter

By Up to **Seven Positions**, Contd.

$dir = 0$: Right

$dir = 1$: Left

$l = 0$: Logical shift right or shift left

$l = x_7$: Arithmetic shift right

- Truth table (incomplete, only a few example cases are shown):

dir	s_2	s_1	s_0	in	out	z
0	0	1	0	$x_7x_6x_5x_4x_3x_2x_1x_0$	$llx_7x_6x_5x_4x_3x_2$	$llx_7x_6x_5x_4x_3x_2$
0	1	0	1	$x_7x_6x_5x_4x_3x_2x_1x_0$	$lllllx_7x_6x_5$	$lllllx_7x_6x_5$
0	1	1	1	$x_7x_6x_5x_4x_3x_2x_1x_0$	$lllllllx_7$	$lllllllx_7$


Original order

Original order



1	1	0	0	$x_0x_1x_2x_3x_4x_5x_6x_7$	$llllx_0x_1x_2x_3$	$x_3x_2x_1x_0llll$
1	0	1	1	$x_0x_1x_2x_3x_4x_5x_6x_7$	$lllx_0x_1x_2x_3x_4$	$x_4x_3x_2x_1x_0lll$
1	1	1	1	$x_0x_1x_2x_3x_4x_5x_6x_7$	$lllllllx_0$	$x_0llllll$

Swapped order

Swapped order

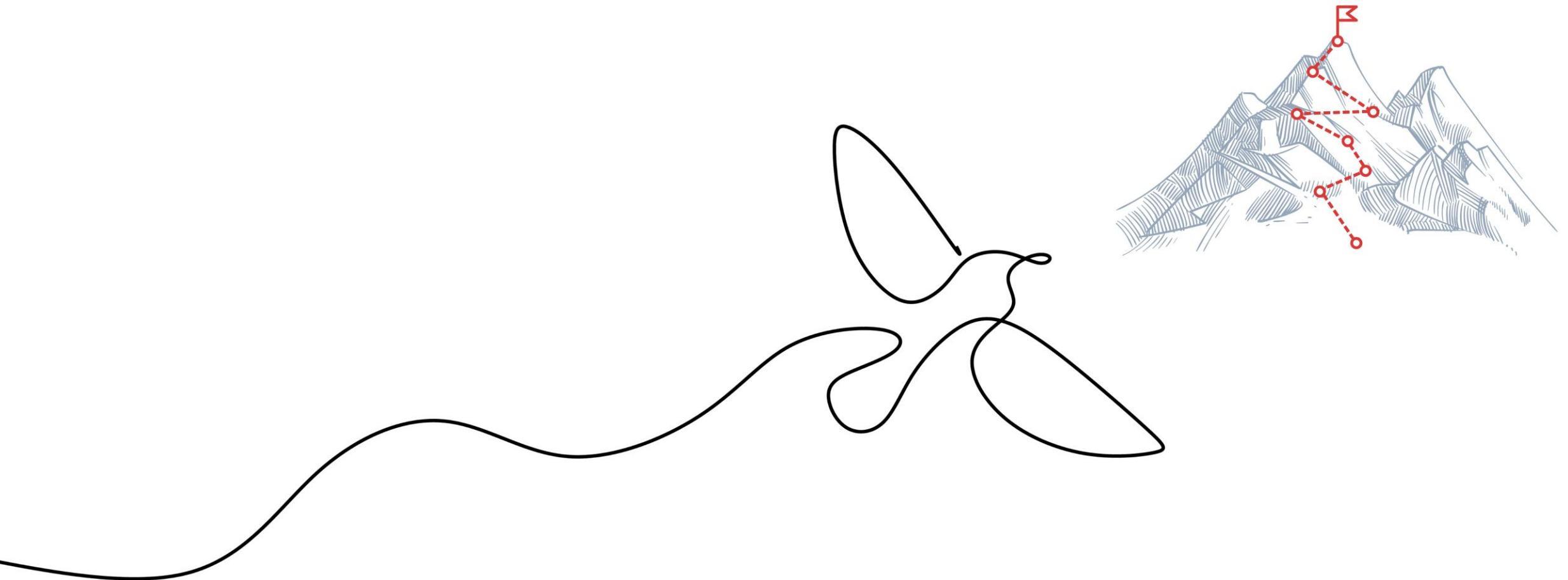

Literature

  

- Chapter 3: Number representation and arithmetic circuits
 - 3.2.1, 3.2.2, 3.3.3, 3.3.6
- Chapter 8: Combinational arithmetic elements
 - 8.1.1-8.1.3
 - 8.2