

Digital Logic Circuits

Implementation Technology


CS-173 Fundamentals of Digital Systems

Mirjana Stojilović

Spring 2025


Previously on FDS

Verilog for Combinational Circuits

 


Previously

 - Discovered tri-state drivers and high-impedance, for building busses
- Used behavioral modeling approach to describe logic circuits
- Verilog, continued
 - Always block
 - If-else statements
 - Switch statements




Let's Talk About...

 ...transistors, CMOS gates,
real gate behavior, dynamic operation,
power consumption



Learning Outcomes

- Discover transistors, the basic components from which real logic gates are built
 - Complementary Metal-Oxide-Semiconductor (**CMOS**) technology
- Understand the difference between **ideal and real gate** behavior
 - Real gate **delays**: the time it takes for the output to reach logic values 0 or 1
- Be aware of the existence of **hazards** in real circuits to understand and avoid unwanted behavior when building complex logic circuits
- Learn which factors impact the working **frequency** and the **dynamic power** consumption of a logic circuit, and in what way

 


Quick Outline

- Transistors
 - NMOS
 - PMOS
 - CMOS
- Real Voltage Waveforms
 - Voltage transfer characteristic
 - Rise time and fall time
 - Propagation delay
- Dynamic operation
 - Fan-in and fan-out
 - Parasitic capacitance
 - Gate delay
 - Power dissipation
- Hazards
- Executive summary

Transistors

NMOS, PMOS, Complementary MOS (CMOS)

 


Transistor Switches – NMOS


Metal-Oxide-Semiconductor (MOS)

- If controlled by an input variable x , the switch is

- Open if $x = 0$

 


- Closed if $x = 1$

 

Transistor Switches – NMOS

Metal-Oxide-Semiconductor (MOS)

- NMOS as a logic gate

 


Transistor Switches – PMOS


Metal-Oxide-Semiconductor (MOS)

- If controlled by an input variable x , the switch is

- Open if $x = 1$

 




- Closed if $x = 0$

 

Transistor Switches – PMOS


Metal-Oxide-Semiconductor (MOS)

- PMOS as a logic gate

   

Complementary MOS – CMOS

- PMOS and NMOS combined

 

- Truth table

A blue circular arrow points from the top truth table to the bottom one, indicating a correspondence between the variables V_x and x .


V_x	T_1	T_2	V_f
Gnd	ON	OFF	V_{DD}
V_{DD}	OFF	ON	Gnd

x	T_1	T_2	f
0	ON	OFF	1
1	OFF	ON	0

- This circuit is a **NOT gate**

CMOS Circuit Structure


N inputs, single output

 

- **Complementary** functions performed by a pull-up and pull-down network:
 - **Pull-up** composed of **PMOS**
 - **Pull-down** composed of **NMOS**
- Pull-up and pull-down networks are **dual** to one another and have an **equal** number of transistors

CMOS Gates

 - Find the functionality of the given CMOS gate




- Truth table

x_1	x_2	T_1	T_2	T_3	T_4	f
0	0	ON	ON	OFF	OFF	1
0	1	ON	OFF	OFF	ON	0
1	0	OFF	ON	ON	OFF	0
1	1	OFF	OFF	ON	ON	0

- Answer: NOR gate
- Cost (size, area): four transistors

CMOS Gates

 - Find the functionality of the given CMOS gate




- Truth table

x_1	x_2	T_1	T_2	T_3	T_4	f
0	0	ON	ON	OFF	OFF	1
0	1	ON	OFF	OFF	ON	1
1	0	OFF	ON	ON	OFF	1
1	1	OFF	OFF	ON	ON	0


- Answer: NAND gate
- Cost (size, area): four transistors

CMOS Gates

 - Find the functionality of the given CMOS gate




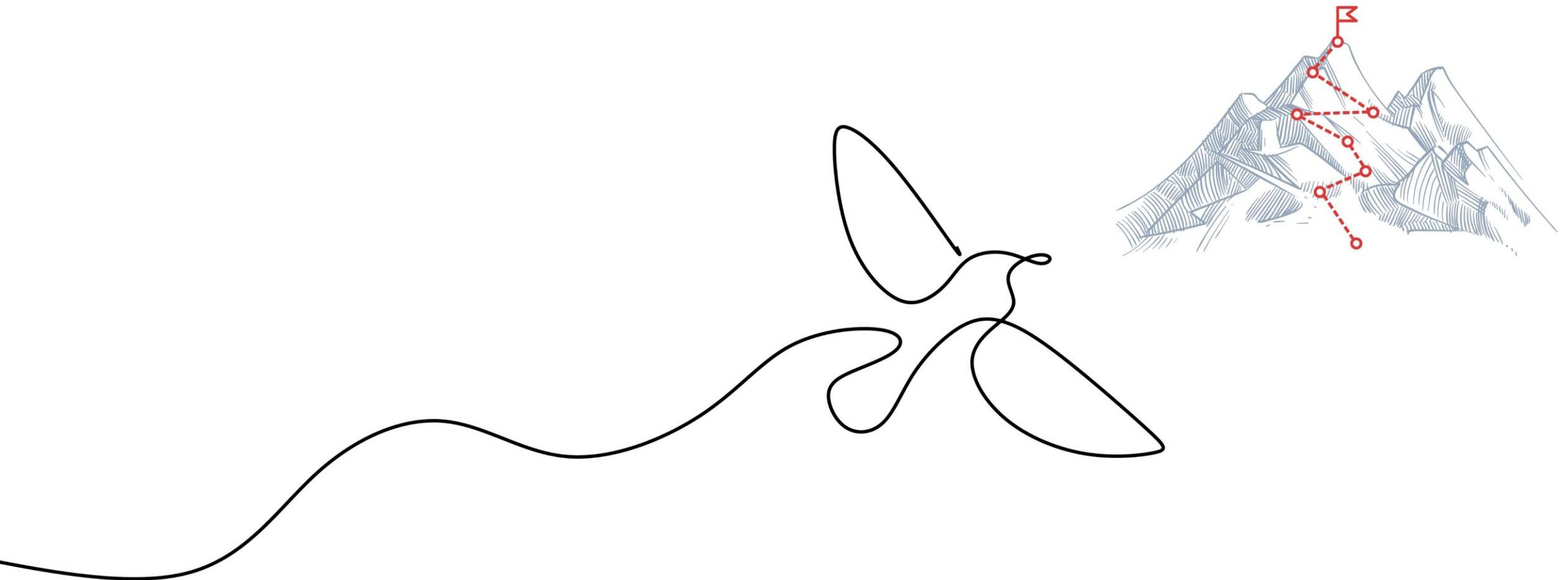- NAND gate followed by a NOT gives us an AND gate
- Cost (size, area): six transistors, two more than the NAND gate




Real Voltage Waveforms

 - Voltage transfer characteristic
- Rise and fall time
- Propagation delay




Logic Values as Voltage Levels

 - Binary values (0, 1) in digital circuits are represented as voltage levels
 - 0: **low** (ground)
 - 1: **high** (supply)
- Thresholds:
 - $V_{0,\max}$ the **max** voltage level that the circuit must interpret as **low**
 - $V_{1,\min}$ the **min** voltage level that the circuit must interpret as **high**



Logic Values as Voltage Levels

 
- Exact threshold values depend on the technology; typically:
 - $V_{0,\max} \sim 0.4V_{DD}$
 - $V_{1,\min} \sim 0.6V_{DD}$
- Range $(V_{0,\max}, V_{1,\min})$ is undefined
 - Logic signals take those intermediate voltage values only while transitioning from one logic value to another



Voltage Transfer Characteristic

CMOS Inverter (NOT Gate)

 
- The input-output voltage relationship in a real CMOS inverter is summarized by the voltage transfer characteristic
- Where the slope of the curve is -1, we have:
 - max input voltage that will be interpreted as low
 - min input voltage that will be interpreted as high



Real Voltage Waveforms for Logic Gates

Rise Time, Fall Time

 
- Consider a logic gate **output** changing from one logic level to another. We used to draw an ideal (instantaneous) transition. In **real circuits**, waveforms do not have the ideal shape; instead, transitions take some time:
 - t_r , **rise time**, the time elapsed from $0.1V_{DD}$ to $0.9V_{DD}$
 - t_f , **fall time**, the time elapsed from $0.9V_{DD}$ to $0.1V_{DD}$






Voltage Waveforms for Logic Gates

 - Consider a NOT gate driven by a voltage pulse.



 
- Idealized in-out waveforms would be drawn like this. What is wrong here?




- A:** First, in real gates, as we saw, the transitions are not ideal; they take time. Second, the time it takes for a signal to propagate from the input to the output is not null. There is a **propagation delay**.

Real Voltage Waveforms for Logic Gates

 - Consider a NOT gate driven by a voltage pulse
- Real-looking input waveform would be, for example:



 
- The corresponding real-looking output waveform:



Real Voltage Waveforms for Logic Gates

Propagation Delay

 - Consider a NOT gate driven by a voltage pulse
- After aligning the waveforms in time, we see the propagation delay




Real Voltage Waveforms for Logic Gates

Propagation Delay, Contd.


- Propagation delay, t_p , is the time from when the input voltage reaches 50% of the V_{DD} , to the time the output voltage reaches the same level
- General case:
 
$$t_{p,\text{high-to-low}} \neq t_{p,\text{low-to-high}}$$



Dynamic Operation

...and Power Dissipation

 

Fan-In of a Logic Gate


Definitions

- **Fan-in** of a logic gate is the number of its inputs
- Examples
 - NOT has a fan-in of one
 - tree-input NOR gate has a fan-in of three
 - four-input XOR gate has a fan-in of four

Fan-Out of a Logic Gate

Definitions

 - **Fan-out** of a logic gate is the number of other gate inputs it drives (i.e., “the load”)
- Example




fan-out(AND₁) = fan-out(AND₂) = 1
fan-out(XOR₁) = 2;
fan-out(XOR₂) = ? (not shown)
fan-out(OR₁) = ? (not shown)

Parasitic Capacitance

Impact of Fan-out on Gate Delay

 
- An undesired but unavoidable side-effect of transistor fabrication is the **input parasitic capacitance** of a logic gate



Parasitic Capacitance

Impact of Fan-out on Gate Delay

 - The **sum** of all **transistor gate terminal capacitances** at an input of a logic gate gives the equivalent per-input capacitance of that logic gate
 - Per-input capacitance acts as a "load" to the logic gate that drives this input
 - Example in the figure: input capacitance of the 2nd NOT gate acts as "load" at the output of the 1st NOT gate





*The *higher* the load capacitance, the *slower* the gate whose output is connected to it

Gate Input Capacitance

NOT Gate

  - Given the NMOS/PMOS transistor gate capacitance C_T , find the input capacitance of a NOT gate
- Solution: identify all transistors connected to the NOT gate input; sum their gate capacitances to find the equivalent per-input C of the NOT gate




Equivalent capacitance of two or more capacitors connected **in parallel** is the **sum** of their individual capacitances
[\[Read more online\]](#)

$$C_x = C_{T1} + C_{T2}$$

Gate Input Capacitance

NOR Gate


 
- Find the input capacitance of a NOR gate
- Solution: identify all transistors connected to the NOR gate inputs; sum their gate capacitances to find the equivalent per-input C of the NOR gate




Gate Input Capacitance

NAND followed by NOT

  - Find the capacitance at terminals V_{x_1} , V_{x_2} and V_y




 Input gate capacitance of the NOT gate acts as the **load capacitance** for the preceding NAND gate





Dynamic Current Flow

 - Current flow when input V_x changes: $0 \rightarrow V_{DD}$
- Load capacitance is **discharged** through the NMOS on-resistance; PMOS is OFF





 - Current flow when input V_x changes: $V_{DD} \rightarrow 0$
- Load capacitance is **charged** through the PMOS on-resistance; NMOS is OFF



 

Discharging a Capacitor

  

- Kirchhoff's voltage law: the total voltage drop in a closed circuit is zero

$$V_c(t) - R \cdot i(t) = 0$$



- Circuit current:

$$i(t) = i_R(t) = i_c(t) = C \frac{dV_c(t)}{dt}$$

- Assuming the initial capacitor voltage is V_{DD} , substituting the expression for the current and solving for the capacitor voltage brings us to

$$V_c(t) = V_{DD} e^{-\frac{t}{RC}}$$

Charging a Capacitor

  

- Kirchhoff's voltage law: the total voltage in a circuit is $0 \sim V$


$$V_{DD} - R \cdot i(t) - V_c(t) = 0$$

- Circuit current:

$$i(t) = i_R(t) = i_c(t) = C \frac{dV_c(t)}{dt}$$

- Assuming the initial capacitor voltage was 0 V, substituting the expression for the current and solving for the capacitor voltage brings us to

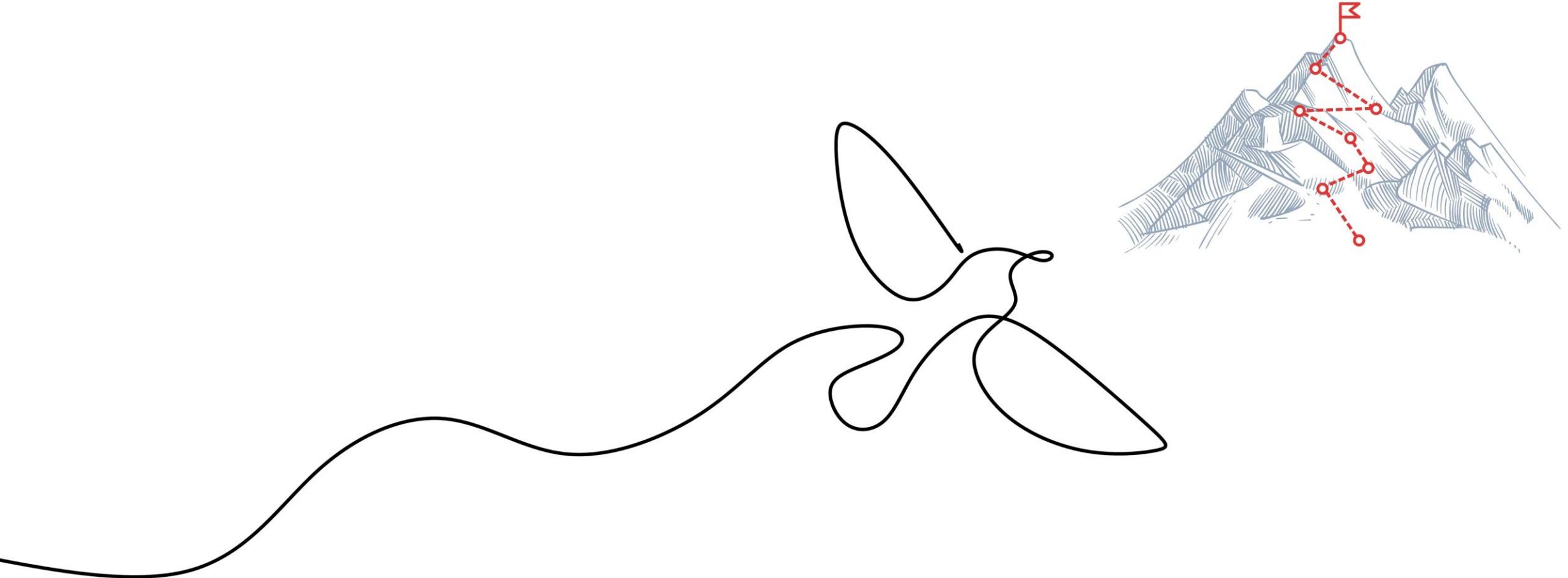
$$V_c(t) = V_{DD} \left(1 - e^{-\frac{t}{RC}}\right)$$



The Speed of a Logic Circuit

Gate Delay

 
- The speed (delay) depends on how fast the load capacitance is charged or discharged through the NMOS (PMOS) resistance R_{DS}
- **Fan-in and fan-out matter**
 - With higher fan-in grows the per-input capacitance
 - The higher the fan-out, the higher the equivalent load capacitance
- The **higher** the load **capacitance**, the **slower** the gate driving it





The Effect of Fan-Out on Gate Delay

 - Consider the inverter with a fan-out n , which drives n other identical inverters. If the propagation delay of the inverter when $n = 1$ is $t_p = 0.2$ ns, find the propagation delay when $n = 5$





Load Capacitance Effect on Gate Delay

- Let us first see how much slower charging/discharging of a capacitor becomes with increased load capacitance
- Capacitor voltage while discharging (left) and charging (right) :

$$V_{C_1}(t) = V_{DD}e^{-\frac{t}{RC_1}}$$

$$V_{C_2}(t) = V_{DD}e^{-\frac{t}{RC_2}}$$

$$V_{low} = V_{DD}e^{-\frac{t_{1,low}}{RC_1}} = V_{DD}e^{-\frac{t_{2,low}}{RC_2}}$$

$$\frac{t_{1,discharge}}{RC_1} = \frac{t_{2,discharge}}{RC_2}$$

$$t_{2,discharge} = \frac{C_2}{C_1} t_{1,discharge}$$

$$V_{C_1}(t) = V_{DD}(1 - e^{-\frac{t}{RC_1}})$$

$$V_{C_2}(t) = V_{DD}(1 - e^{-\frac{t}{RC_2}})$$

$$V_{high} = V_{DD}(1 - e^{-\frac{t_{1,high}}{RC_1}}) = V_{DD}(1 - e^{-\frac{t_{2,high}}{RC_2}})$$

$$\frac{t_{1,charge}}{RC_1} = \frac{t_{2,charge}}{RC_2}$$



$$t_{2,charge} = \frac{C_2}{C_1} t_{1,charge}$$

- Therefore, increasing load capacitance leads to slower charge/discharge and, consequently, longer signal propagation time through the logic gate




The Effect of Fan-Out on Gate Delay

  - Going back to our question...
- The capacitance at the output of the NOT gate is $nC_1 = 5C_1$




- Answer: NOT gate will be five times slower

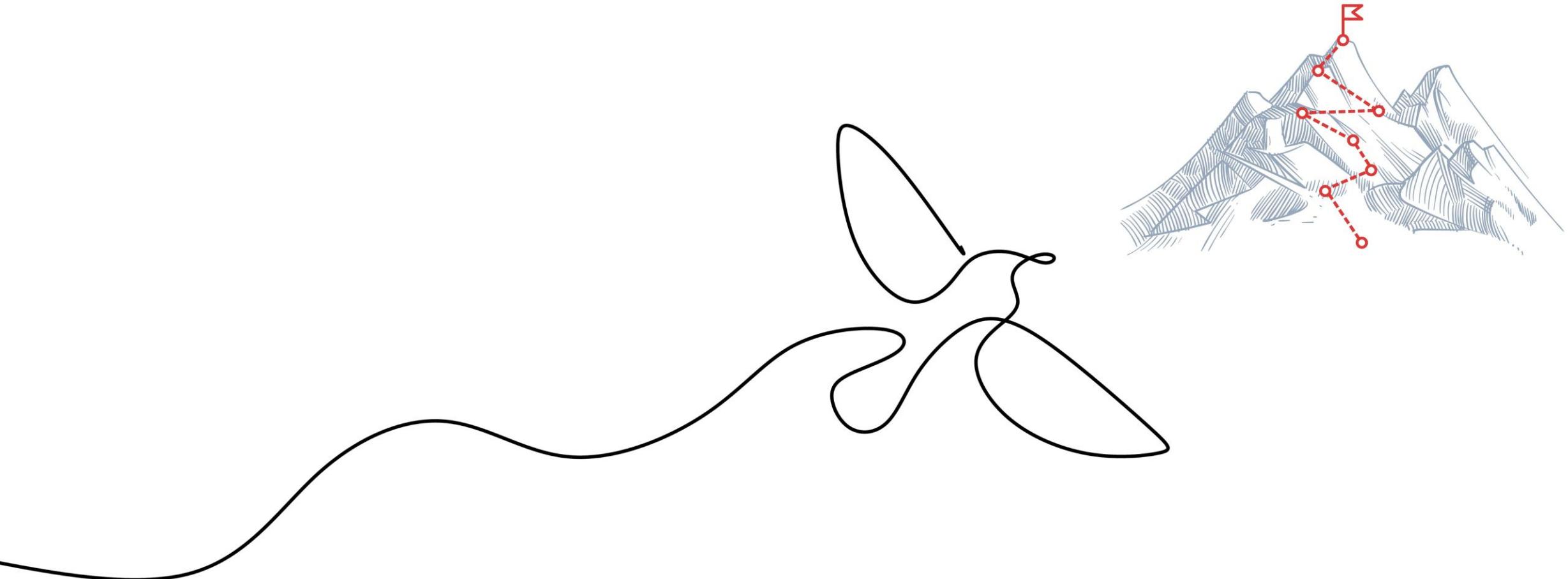Note: In reality, other parasitic components (capacitors, inductors, resistors) exist, and the expressions are more complex.



Power Dissipation in Logic Gates

 - Power dissipation is an important consideration in all applications of logic circuits, especially in battery-operated devices
 - When NMOS is ON, the load capacitor discharges its energy
 - When PMOS is ON, the capacitor charges energy



Total Energy Stored in a Capacitor

- A capacitor C has been charged to the voltage $V_c = V_{DD}$
- Find the amount of energy stored in the capacitor
- Let us compute the energy that will be discharged instead:
 - Current flow through the capacitor: $i(t) = C \frac{dV_c(t)}{dt}$
 - Instantaneous power dissipated in the capacitor: $P(t) = i(t)V_c$
 - Energy is defined as power used over a time period:

$$\begin{aligned} E_c &= \int_0^\infty P(t) dt = \int_0^\infty i(t)V_c dt = \int_0^\infty C \frac{dV_c}{dt} V_c dt = C \int_0^{V_{DD}} V_c dV_c \\ &= \frac{1}{2} C V_{DD}^2 \end{aligned}$$

Power Dissipation in Logic Gates

- Total energy during one charge/discharge cycle:


$$E = E_{\text{charge}} + E_{\text{discharge}} = 2 \times \frac{1}{2} C V_{DD}^2 = C V_{DD}^2$$


- Power is energy over time:

$$P_D = f C V_{DD}^2$$

Dynamic power

 
Switching frequency:
how frequently C charges and discharges



 

Hazards


...also known as glitches

 


Ideal Timing Waveforms

Zero-Delay Model

 - Given the logic circuit and the sequence of inputs shown in the timing diagram, draw the corresponding output waveform
 - Assume **zero delays** (i.e., logic level changes propagate instantaneously)




 
$$Z = \overline{X} Y + X \overline{Y} = X \oplus Y$$



- Such behavior is unrealistic because real circuits have delays



Real Timing Waveforms

  - Once again, now assuming wires with zero delays and
 - $d(\text{NOT}) = 1 \text{ ns}$
 - $d(\text{AND}) = 2 \text{ ns}$
 - $d(\text{OR}) = 3 \text{ ns}$





Real Timing Waveforms

  - Once again, now assuming wires with zero delays and
 - $d(\text{NOT}) = 1 \text{ ns}$
 - $d(\text{AND}) = 2 \text{ ns}$
 - $d(\text{OR}) = 3 \text{ ns}$





Real Timing Waveforms

  - Once again, now assuming wires with zero delays and
 - $d(\text{NOT}) = 1 \text{ ns}$
 - $d(\text{AND}) = 2 \text{ ns}$
 - $d(\text{OR}) = 3 \text{ ns}$





Real Timing Waveforms

  - Once again, now assuming wires with zero delays and
 - $d(\text{NOT}) = 1 \text{ ns}$
 - $d(\text{AND}) = 2 \text{ ns}$
 - $d(\text{OR}) = 3 \text{ ns}$



Real Timing Waveforms

  
- Once again, now assuming wires with zero delays and
 - $d(\text{NOT}) = 1 \text{ ns}$
 - $d(\text{AND}) = 2 \text{ ns}$
 - $d(\text{OR}) = 3 \text{ ns}$




Timing Hazards

Glitches

- Recall: Zero-delay gates

 

- Real gates

 


- Delay-caused unwanted level changes are called hazards or glitches; they often cannot be avoided

Unwanted impulses, called hazards or, often, GLITCHES

Static Hazard

Types of Hazards

 - A **static hazard** exists if a signal is supposed to **remain** at a particular logic value when an input variable changes its value, but instead, the signal undergoes a **momentary change** in its required value




One must be aware of the possibility of hazards happening in real circuits


Dynamic Hazard

Types of Hazards

 - Another type of hazard may occur when a signal is supposed to change: $1 \rightarrow 0$ or $0 \rightarrow 1$. A **dynamic hazard** occurs if such a change involves a short oscillation before the signal settles into its new level.



 One must be aware of the possibility of hazards happening in real circuits





Executive Summary

- **Gate delay:** Real gates take time to produce the output logic value
- **Rise and fall time:** Transitions $0 \rightarrow 1$ and $1 \rightarrow 0$ are never instantaneous
- **Glitches:** Real circuits may exhibit hazards (i.e., undesired glitches)
- **Parasitic capacitance:** Gate inputs act as capacitance, loading the outputs of the gates that are driving them and slowing those gates
- **High fan-out is no good:** Load capacitance grows with the fan-out
 - The higher the fan-out, the slower the gate
- **Power consumption matters:** Dynamic power consumption grows
 - linearly with the load capacitance and switching frequency
 - quadratically with the supply voltage

To save power, we lower the operating frequency or voltage or both



Literature

  

- Appendix B: Implementation Technology
 - B.1-B.4
 - B.8
- Chapter 1: Introduction
 - 1.9