

Digital Logic Circuits

Verilog for Combinational Circuits


CS-173 Fundamentals of Digital Systems

Mirjana Stojilović

Spring 2025


Previously on FDS

Intro to CAD and Verilog

 


Previously

 - Discovered the key phases of computer-aided design (CAD) flow
 - Hardware description language (HDL)
- Learned how to use Verilog HDL for **gate-level modeling** of logic circuits
- Verilog gates, wires, modules, ports, and subcircuits
- Gate-level modeling examples:
 - Full-adder
 - Four-bit ripple-carry adder




Let's Talk About...

 ...Behavioral modeling in Verilog and
some new gates and combinational circuits



Learning Outcomes

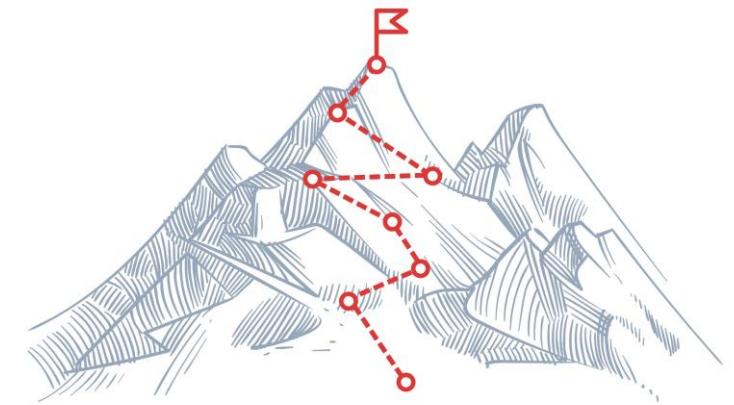- Discover **tri-state drivers**
- Learn about **high-impedance Z**
- Model shared interconnect (a **bus**) using MUXes or tri-state drivers
- Use Verilog **behavioral** modeling to describe logic circuits
 - Understand the difference between **continuous** assignments and **procedural** statements
 - Use **always** blocks and **if-else** and **switch** statements



Quick Outline


- Tri-state drivers
- Bus
 - With multiplexers
 - With tri-state drivers
- Verilog HDL
 - Logic gates
 - Values: scalar and vector
 - Constants, Concatenation
 - Parameters, Nets
- Behavioral Modeling in Verilog
 - Continuous assignments
 - assign keyword
 - Procedural statements
 - always block
 - reg type for variables
 - if-else statement
 - Example: 2-to-1 multiplexer
 - case statement
 - Example: full-adder

Tri-State Drivers




Multiple Gates Driving Same Inputs

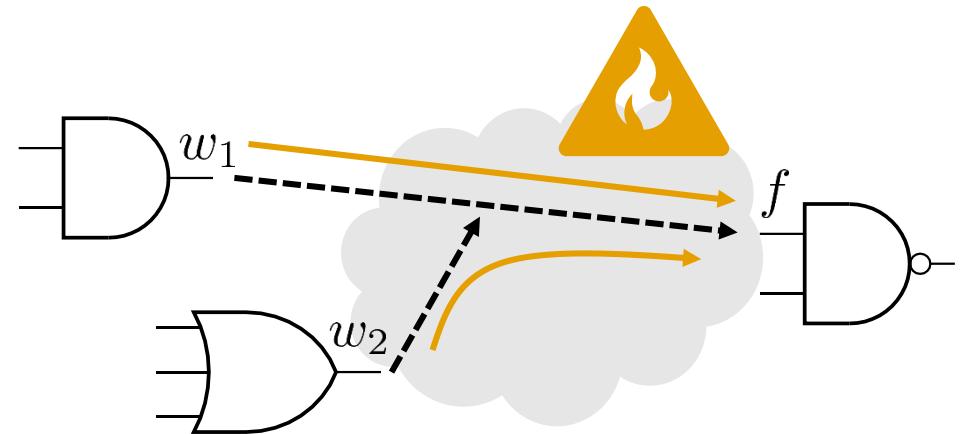- Example: Two logic gates wanting to drive an input of a third logic gate
- **Issue:** The logic gates outputs should not be directly connected
 - If one gate forces '1' while the other forces '0', a low resistance path between the power supply and the ground would be created, and the resulting current would be high. We call that situation a **short-circuit**
- **Solution:** Insert MUXes or tri-state drivers on the conflicting signal paths




Tri-State Drivers

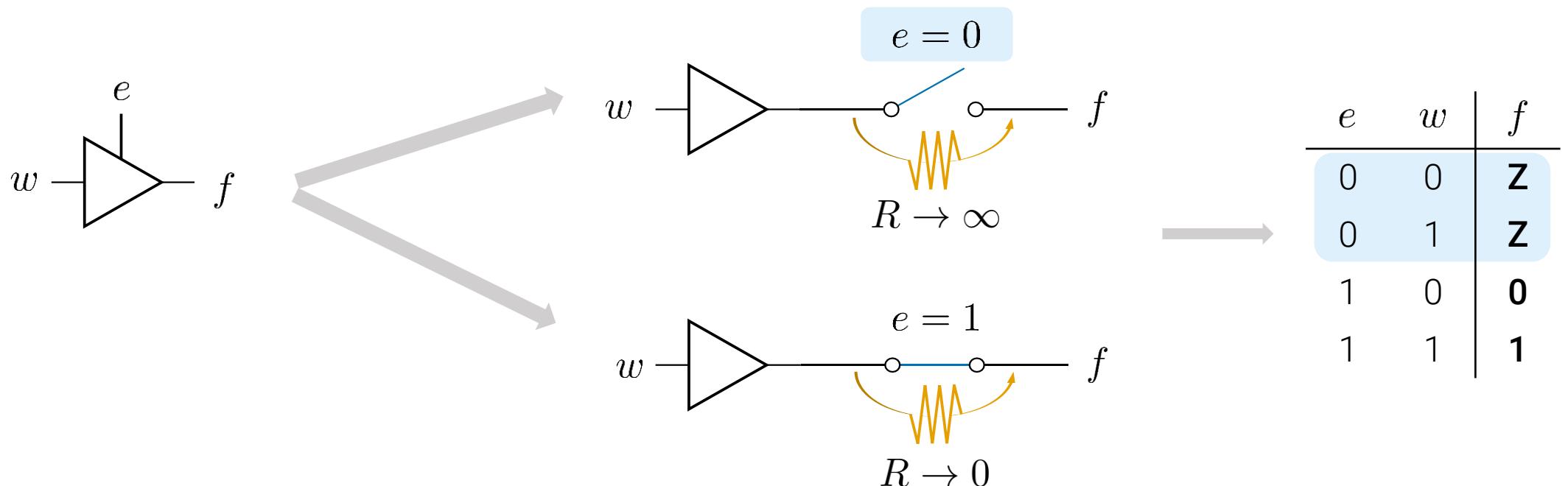- A tri-state driver has a data input, an output, and an **enable** input



* In electrical engineering, R stands for resistance; resistance is the real part of the impedance.

Tri-State Drivers

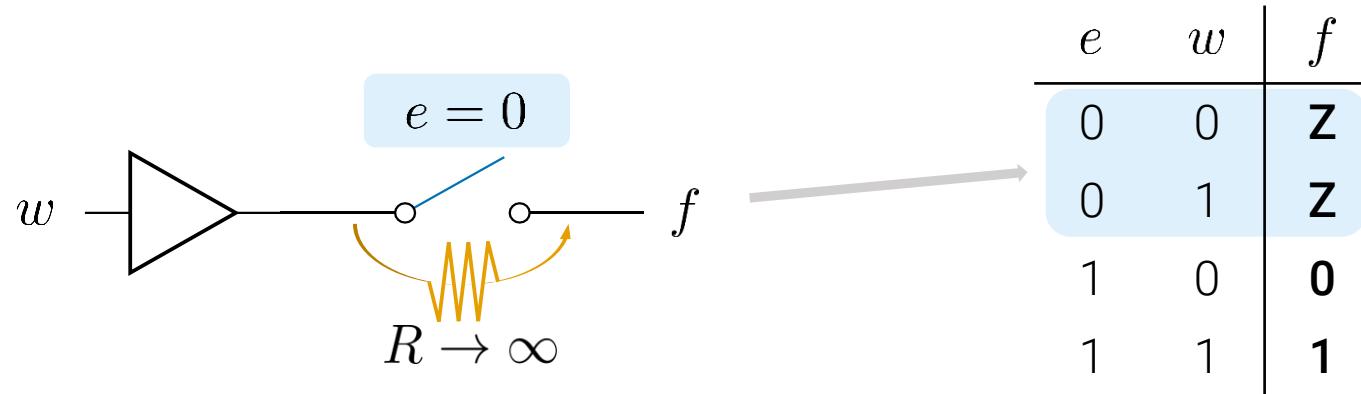


- When the enable input is inactive, the output is electrically disconnected from the data input; disconnected state is referred to as **high-impedance** state and usually denoted as **Z** (or **z**)
 - Three states of a tri-state driver are logical 0, logical 1, and Z


- In electrical engineering, **impedance** is the opposition to alternating current presented by the combined effect of resistance and reactance in a circuit.
- https://en.wikipedia.org/wiki/Electrical_impedance

Types of Tri-State Drivers

- Enable **active high**

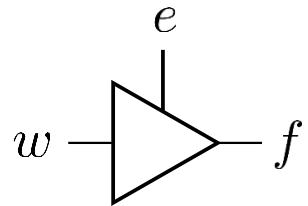


e	w	f
0	0	Z
0	1	Z
1	0	0
1	1	1

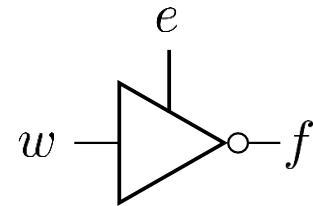


e	w	f
0	0	Z
0	1	Z
1	1	0
1	0	1

- Enable **active low**

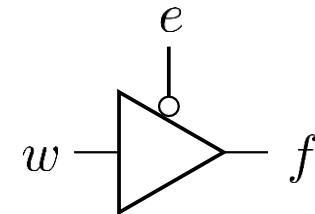


e	w	f
0	0	0
0	1	1
1	0	Z
1	1	Z

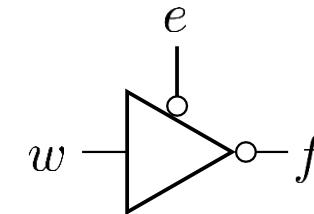



e	w	f
0	0	1
0	1	0
1	0	Z
1	1	Z

Example: Tri-State Drivers

- Two gate outputs driving a wire

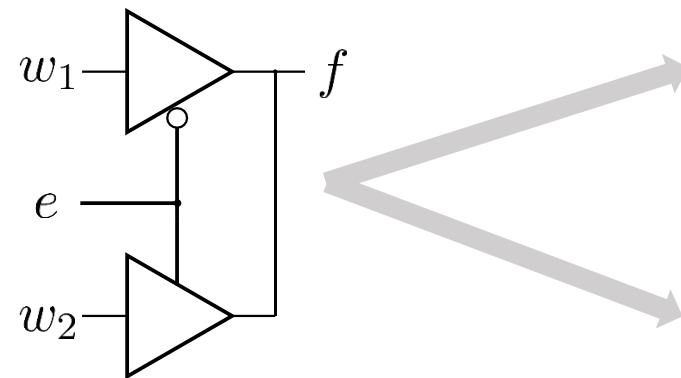


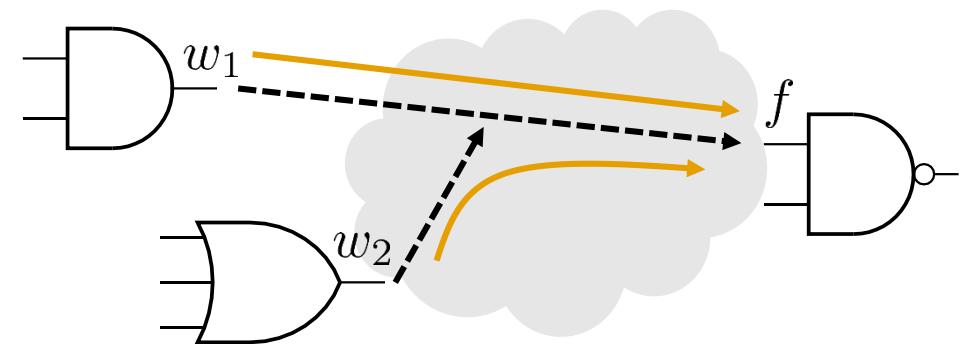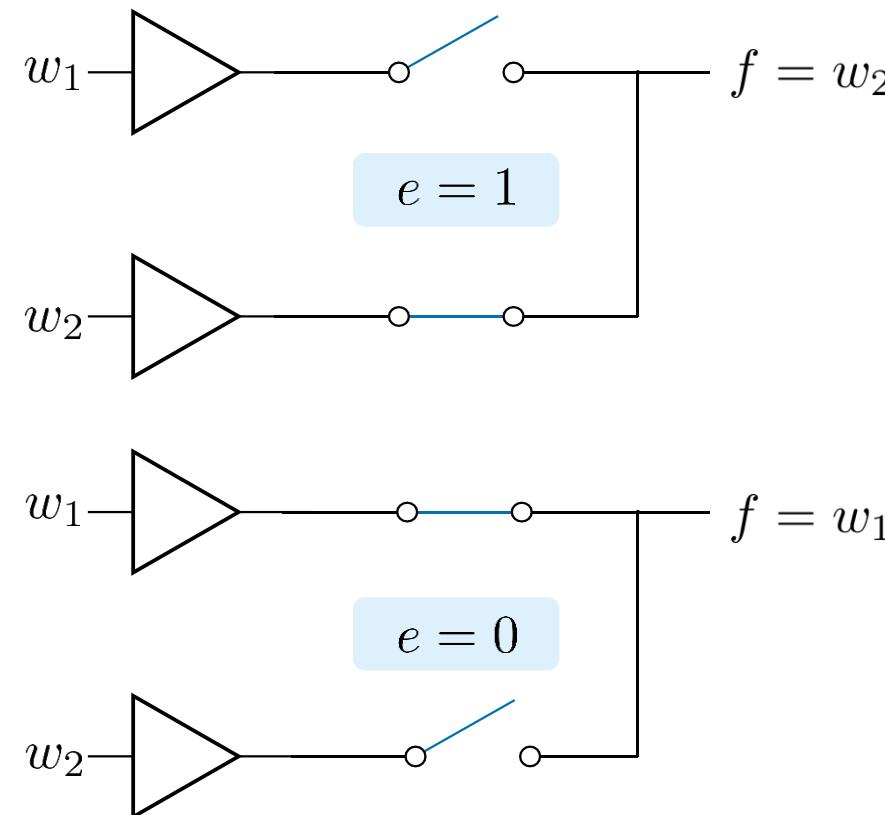To avoid short circuits, only one driver at a time is enabled




Bus

- With MUXes
- With tri-state drivers

 


Bus

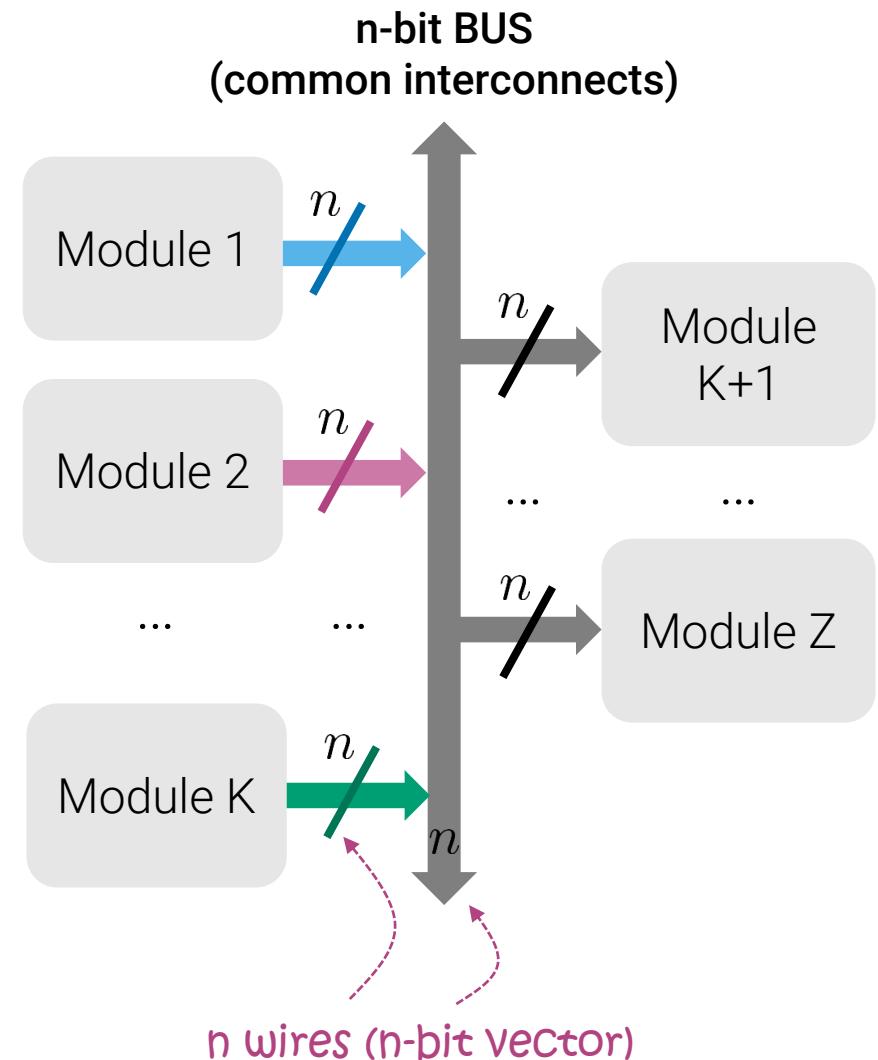- Digital systems are commonly composed of several modules exchanging data by means of a **common** set of interconnects (wires)
- The set of wires grouped under a common name is referred to as a **bus**




Bus

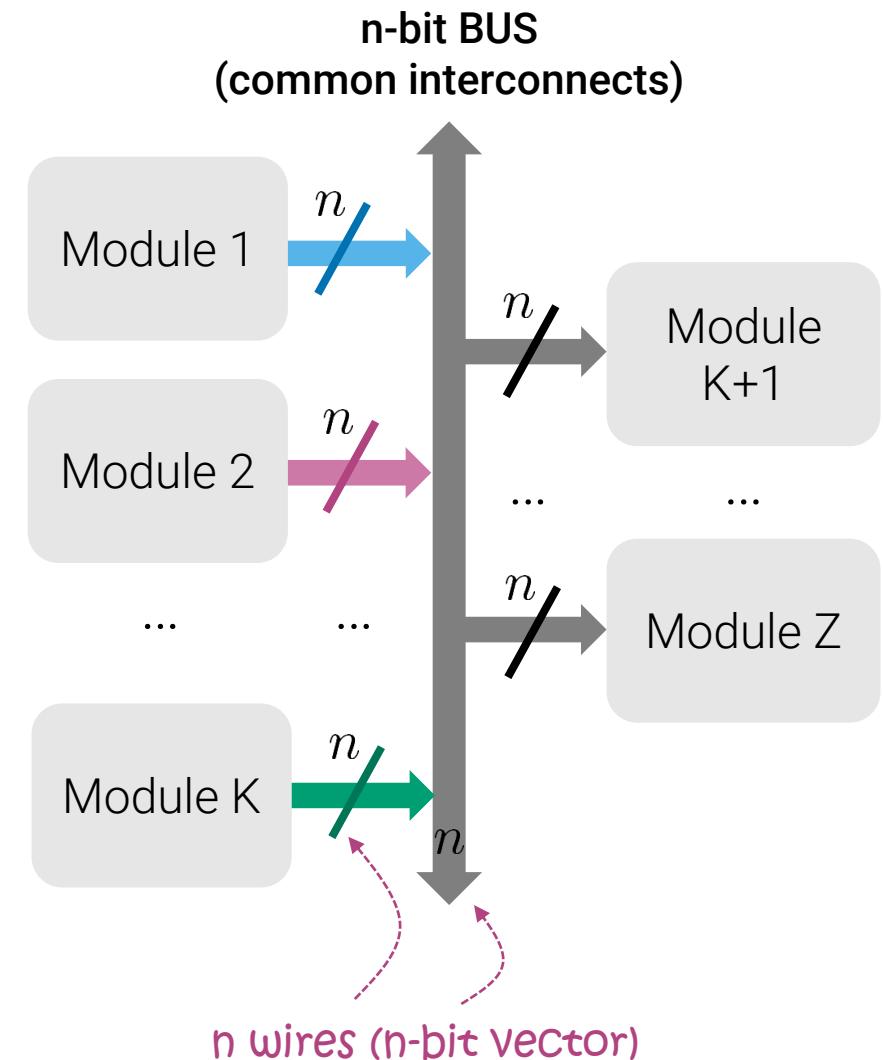- Bus receives data from several modules (one at a time) and brings that data to the inputs of other modules
- Buses are typically n -bit wide, where $n > 1$
- Example: An n -bit bus **DATA** groups n wires, each carrying one signal
 - $\text{DATA}[0], \dots, \text{DATA}[n-1]$
- In Verilog, n -bit and 1-bit signals are called **vectors** and **scalars**, respectively




Implementing a Bus With MUXes

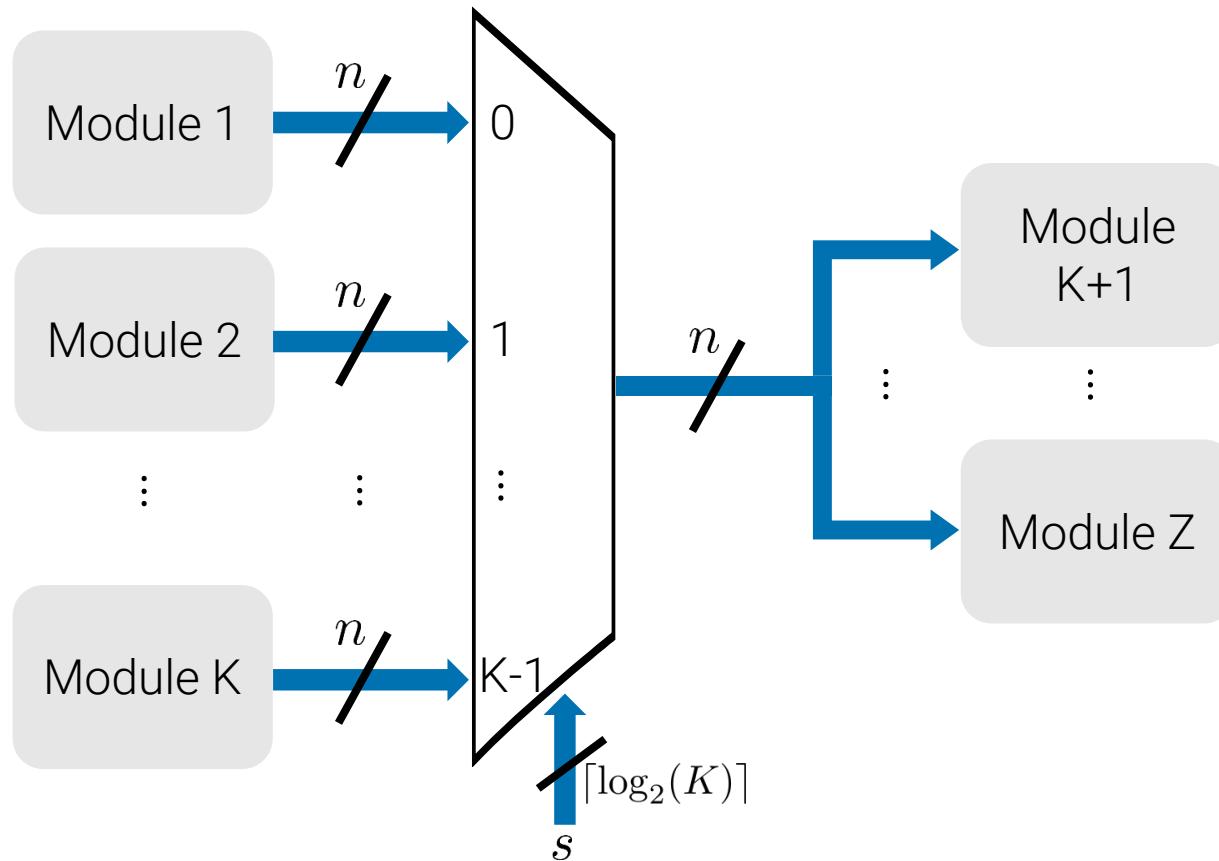


- The multiplexer takes K ($K \geq 2$) n -bit data inputs and an $\lceil \log_2(K) \rceil$ -bit select signal s to select which of the inputs to pass to the output
- An additional circuit that controls the activation of the **select** signals is typically present

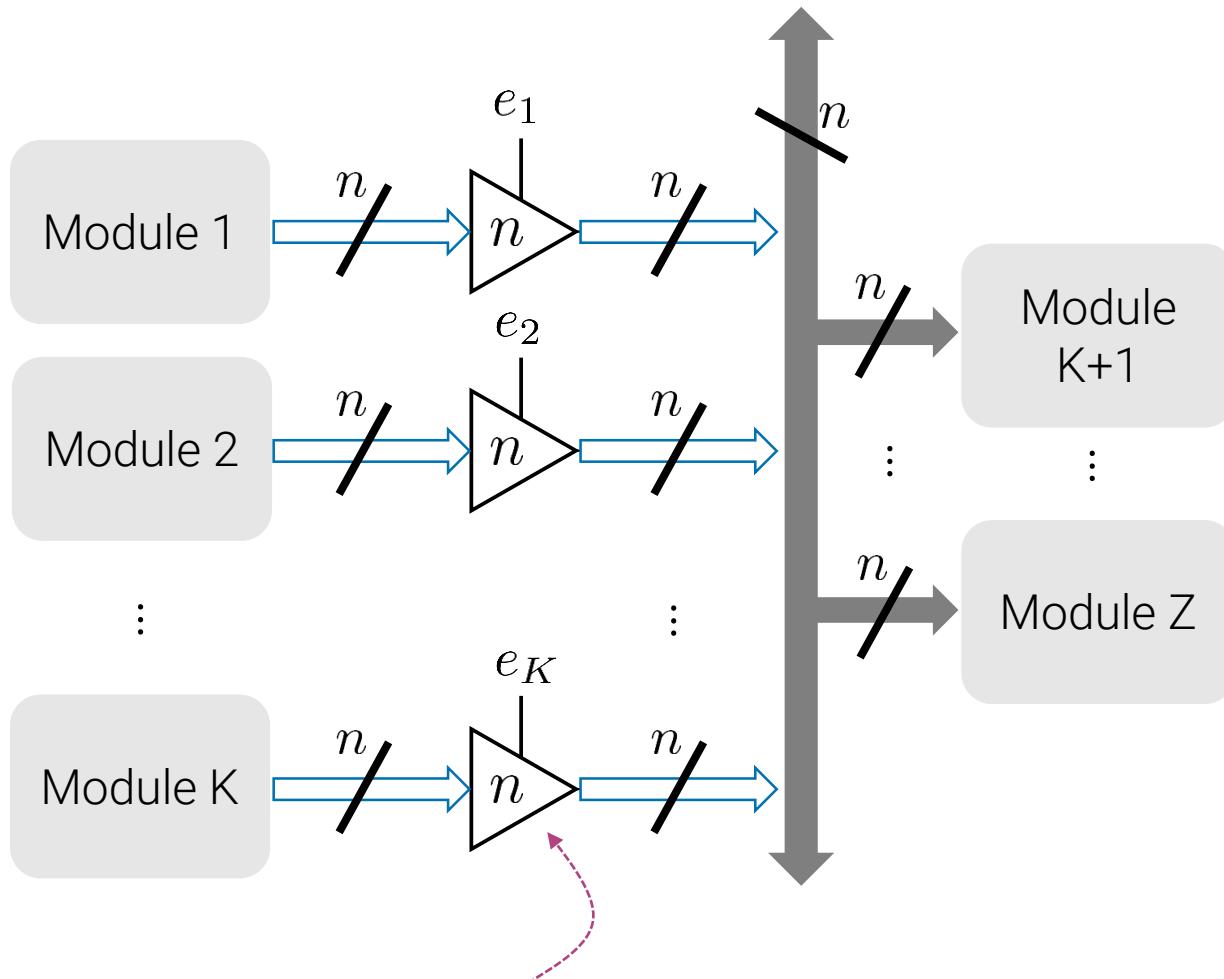Implementing a Bus With Tri-State Drivers




n tri-state drivers, all controlled
by the same enable signal e_K

 - **Only one** of the enable signals is **active** at a time so that short circuits are avoided
- An additional circuit that controls the activation of the **enable** signals is typically present



Verilog, Contd.

- Signal values, numbers, and parameters

 

Verilog Built-In Gates


Complete List

- Complete list of built-in gates
 - **bufif** is a tri-state buffer
 - **notif** is a tri-state inverter


and	xor	bufif0
nand	xnor	bufif1
or	buf	notif0
nor	not	notif1

- Tri-state driver usage

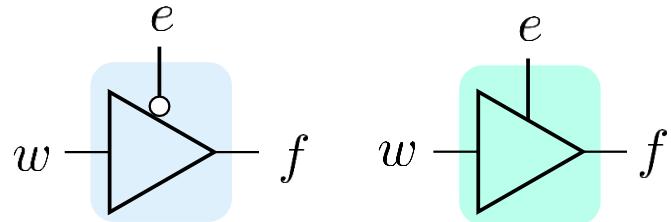- **bufif0(f, w, e)**
- **bufif1(f, w, e)**



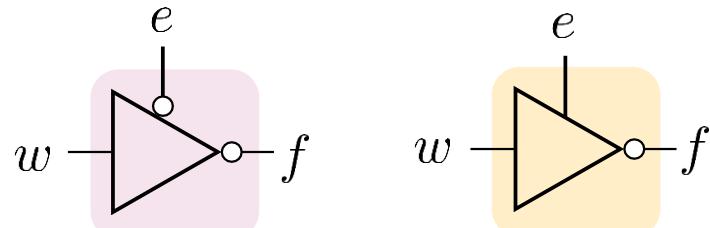- **notif0(f, w, e)**
- **notif1(f, w, e)**



Scalar Signal Values

In Verilog

- Verilog supports one-bit signals (scalars)
- Each individual signal can have one of the four values:

Value	Meaning
0	logic value 0
1	logic value 1
z	or Z, tri-state (high-impedance)
x	or X, unknown value or don't care

Vector Signal Values

In Verilog

- Verilog supports multi-bit signals (vectors)
- The value of a vector variable is specified by giving a **constant** of the form

[size][’radix]constant

where **size** is the number of bits in the constant

Radix	Meaning
d	decimal (default if no radix is specified)
b	binary
h	hexadecimal
o	octal

Constants

In Verilog

- Recall: **[size][‘radix]constant**
- If size specifies more bits than are needed to represent the given constant, then in most cases, the constant is padded with zeros
 - The exceptions to this rule are when the first character of the constant is either **x** or **z**, in which case the padding is done using that value

■ Examples of constants

Constant	Meaning
0	number 0
10	decimal number 10
-8'd10	-10 as an 8-bit two's complement
'b10	binary number $(10)_2 = (2)_{10}$
'h10	hex number $(10)_{16} = (16)_{10}$
4'b100	binary number $(0100)_2 = (4)_{10}$
4'bx	unknown 4-bit value xxxx
8'b1000_0011	_ can be inserted for readability
8'hfx	hex number $(f\text{x})_{16}$, equivalent to 8'b1111_ xxxx

Concatenation Operator

In Verilog

- Verilog concatenation operator `{,}` allows vectors to be combined to produce a wider resulting vector
- Example:

```
wire [3:0] upper = 4'b1100;  
wire [3:0] lower = 4'b0011;  
wire [7:0] combined;  
  
assign combined = {upper, lower}; // Result: 8'b11000011
```

Parameters

In Verilog

- Parameters associate an identifier name with a constant
- Examples:
 - `parameter n = 4;`
The identifier `n` can be used in place of the number 4
 - `parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;`
The name `S0` can be substituted for the binary vector $(00)_2$, etc.
- We will use them when working with parameterized subcircuits

Nets

In Verilog

- Nets represent connections between circuit components
 - Do not store values, but transmit signals
- Most common net types are **wire** and **tri**
- The **wire** type is used to connect an output of one logic element in a circuit to an input of another logic element
 - Examples: `wire x;`
`wire [3:0] s;`

Note: *[MSB:LSB] specify the vector range*

*MSB (most-significant bit): the leftmost bit (highest index);
LSB (least-significant bit): the rightmost bit (lowest index)*


Nets

In Verilog

- Nets represent connections between circuit components
 - Do not store values, but transmit signals
- Most common net types are **wire** and **tri**
- The **tri** type denotes tri-state connections;
tri nets are treated the **same way** as the **wires**; serve to enhance **readability**
 - Examples: `tri z1;`
`tri [7:0] data_out;`

*Note: [MSB:LSB] specify
the vector range*

 
*MSB (most-significant bit):
the leftmost bit (highest index);
LSB (least-significant bit):
the rightmost bit (lowest index)*




Behavioral Modeling

In Verilog

 - Continuous assignments with **assign**
- Procedural assignments with **always@**



Recall Gate-Level Modeling

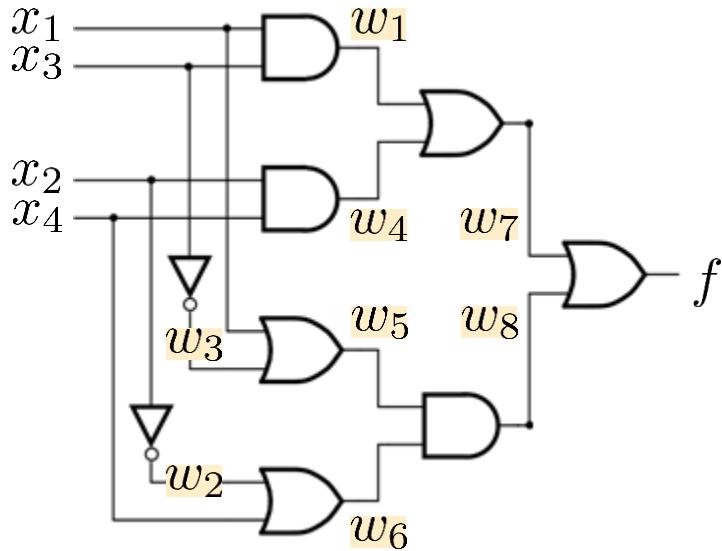

- Structural (gate level) modeling

```
module my_circuit_structural (
    input x1, x2, x3, x4,
    output f
);

    wire w1, w2, w3, w4, w5, w6, w7, w8;

    and (w1, x1, x3);
    not (w2, x2);
    not (w3, x3);
    and (w4, x2, x4);
    or (w5, x1, w3);
    or (w6, w2, x4);
    or (w7, w1, w4);
    and (w8, w5, w6);
    or (f, w7, w8);


endmodule
```

Inputs and outputs can be defined between the parentheses, for readability

Behavioral Modeling

With Continuous Assignments

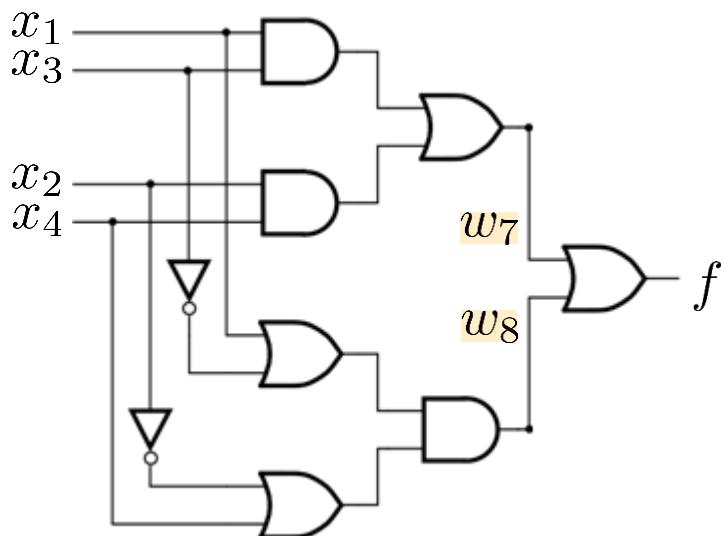- Gate-level modeling becomes tedious for large circuits
- Alternative: use more abstract expressions and programming constructs to **describe the behavior** of a logic circuit



```
module my_circuit_behavioral (
  input x1, x2, x3, x4,
  output f
);

  wire w7, w8;

  assign w7 = (x1 & x3) | (x2 & x4);
  assign w8 = (x1 | ~x3) & (~x2 | x4);
  assign f = w7 | w8;

endmodule
```

Verilog operators:
& - bitwise AND
| - bitwise OR
~ - bitwise NOT
Bitwise: applied on every bit in isolation

Continuous Assignments

Assign keyword

- The **assign** keyword provides a **continuous assignment** for a signal
- The term continuous stems from the use of Verilog in the simulation of logic circuits
 - Whenever any signal on the right-hand side of the assignment changes its value, the signal on the left-hand side will be re-evaluated
 - **Continuous assignments are executed in parallel:** therefore, the order in which they appear in the code is irrelevant

Verilog Assign Statement

- General form:

```
assign net_assignment {, net_assignment} ;
```

- Examples:

- **assign** f = w7 | w8;

```
// Whenever w7 or w8 change,  
// f will be re-evaluated
```

- **wire** [3:1] A, B, C;

```
assign C = A & B;
```

```
// Whenever vectors A or B change,  
// C will be reevaluated
```

```
// C[1] = A[1] & B[1], C[2] = A[2] & B[2], C[3] = A[3] & B[3]
```

*Note: Braces indicate
that additional entries
are permitted*

Behavioral Modeling

With Procedural Statements

- Verilog allows us to use an even higher level of abstraction with **procedural statements**
 - Also called sequential statements
 - Examples: **if-else**, **case**, loops
- Procedural statements must be contained inside an **always**-block
 - **Evaluated in the order** given in the code
- To describe circuit behavior, **variables** are used instead of wires
 - For circuit modeling, **variables of type reg** are used

Always Block

Behavioral Modeling with Procedural Statements

- General format

(for combinational circuits)

```
always @*
[begin]
  [procedural assignments]
  [if-else statements]
  [case statements]
  [while, repeat, and for loops]
  [task and function calls]
[end]
```

Note: The square brackets indicate an optional field

- When multiple statements are included in the block, the **begin** and **end** keywords are needed; otherwise, they can be omitted*

[] Not recommended because it is error-prone*

Always Block

Behavioral Modeling with Procedural Statements

- General format

(for combinational circuits)

```
always @*
[begin]
  [procedural assignments]
  [if-else statements]
  [case statements]
  [while, repeat, and for loops]
  [task and function calls]
[end]
```

Note: The square brackets indicate an optional field

- **always @*** treats **all input** signals used in the block as relevant
 - If **any** input signal mentioned in the block changes its value, all statements using that signal are evaluated **in the order** presented. A signal **assigned multiple** values inside the block **retains the last one**

If-Else Statement

- If the expression is **True**, the statements inside the **begin-end** block are evaluated
 - When **multiple** statements are involved, they have to be included inside a begin-end block
- **else if** and **else** clauses are optional
 - When included, they are paired with the most recent unfinished **if** or **else if**

- General format

```
if (expression1)
begin
    statement;
end
else if (expression2)
begin
    statement;
end
else
begin
    statement;
end
```


2-to-1 MUX

Always Block and an If-Else Statement

- Write a behavioral model of a 2-to-1 MUX using procedural statements in Verilog

```
module my_2to1mux (
    input w1, w2, s,
    output reg f);

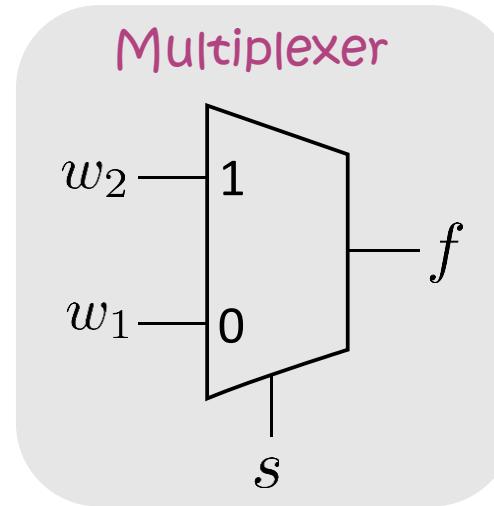    always @* begin
        if (s == 0) begin
            f = w1;
        end
        else begin
            f = w2;
        end
    end
endmodule
```



Note the output is of the type **reg**, because this is a behavioral model (in an always block)

Verilog relational operators **op** return 1 (True) or 0 (False) based on the result of the specified comparison **A op B**:

A == B: equality check **operator**

A != B: inequality check

A > B, A >= B, A < B, A <= B: comparisons

Case Statement

- The bits in the expression, called the **controlling expression**, are checked for a match with each alternative
 - **Each digit in each alternative** is compared for an exact match of the four values **0, 1, x, z**
 - A special case is the **default** clause, which takes effect if **no other** alternative matches
- The **first successful** match causes the associated statements to be evaluated
- The form of the case statement

```
case (expression)
alternative1: begin
    statements;
end
alternative2: begin
    statements;
end
begin
    statements;
end]
```

endcase

Note: The square brackets indicate an optional field

Full-Adder

Always Block and a Case Statement


- **case** statements can be used to describe truth tables
 - model a full adder using a case statement

x	y	Cin	s	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


```
module fulladd (
  input x, y, Cin,
  output reg s, Cout);

  always @* begin
    case ({x, y, Cin})
      3'b000: {s, Cout} = 'b00;
      3'b001: {s, Cout} = 'b10;
      3'b010: {s, Cout} = 'b10;
      3'b011: {s, Cout} = 'b01;
      3'b100: {s, Cout} = 'b10;
      3'b101: {s, Cout} = 'b01;
      3'b110: {s, Cout} = 'b01;
      3'b111: {s, Cout} = 'b11;
    endcase
  end
endmodule
```

 
Verilog concatenation operator {,}
allows vectors to be combined
to produce a wider resulting vector.



Literature

 

 - Chapter 2: Introduction to Logic Circuits
 - 2.10.2
- Appendix A: Verilog Reference
 - A.1 – A.11.4



- Chapter 5: Verilog Hardware Description Language
 - 5.9