

EPFL

FUNDAMENTALS OF
DIGITAL
SYSTEMS

Digital Logic Circuits

Examples of FSMs in Verilog

CS-173 Fundamentals of Digital Systems

Mirjana Stojilović

Spring 2025

Examples of FSMs




Quick Outline

- [Mealy FSM](#)
- [Moore FSM](#)
- [Serial Adder FSM](#)



Recall: Finite State Machines

 
- Two types of FSMs exist
- Mealy state machines
 - Named after [George H. Mealy](#)
- Moore state machines
 - Named after [Edward F. Moore](#)



- State transitions occur in sync with the clock edges (e.g., rising)


Recall: Mealy FSM Modeling

In Verilog

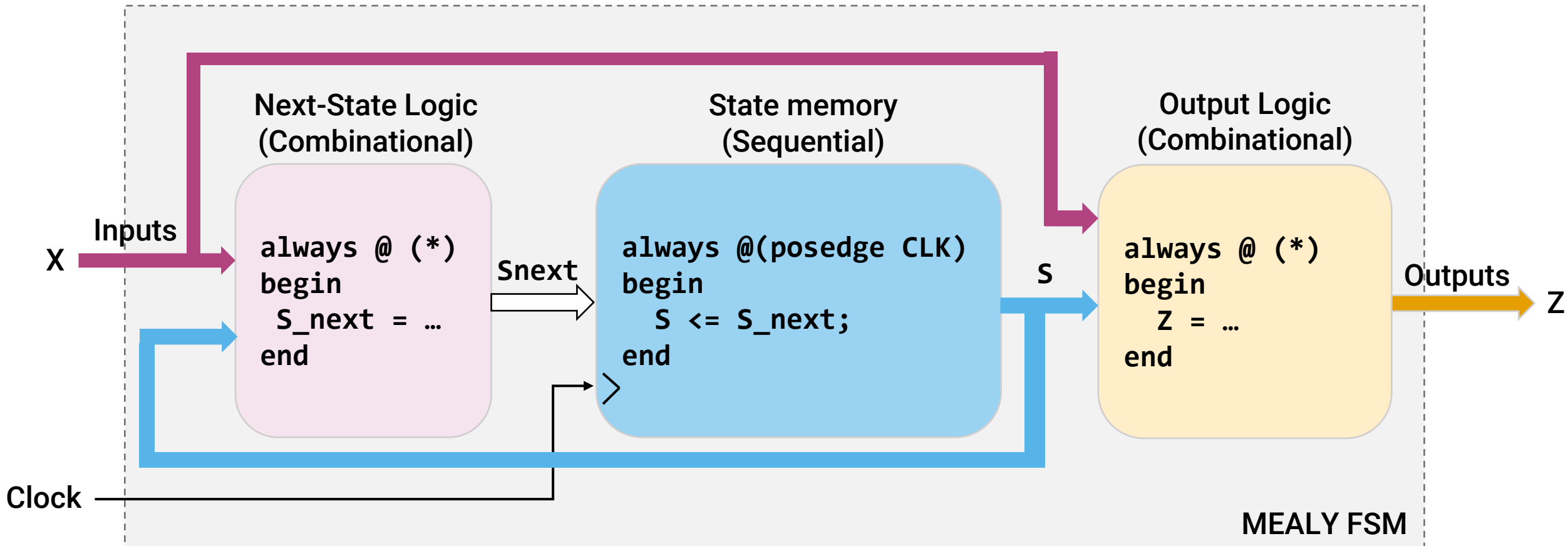

Recall: Moore FSM Modeling

In Verilog

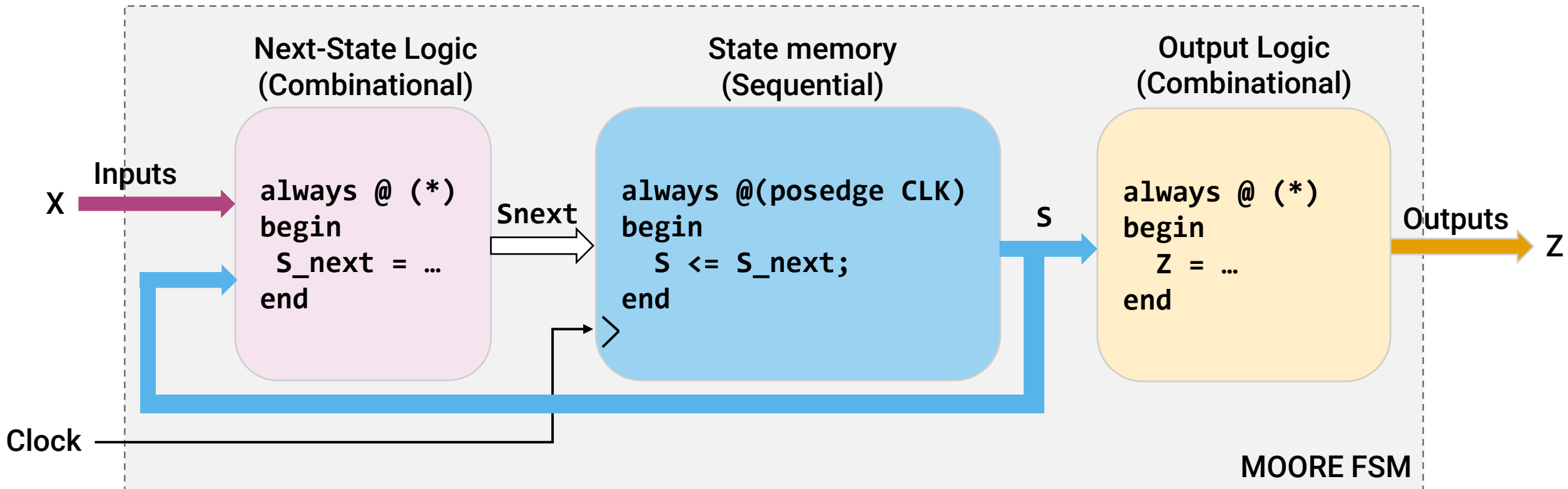

Mealy FSM


Example



Mealy FSM

From state diagram to Verilog

 
- Figure shows the state diagram of...
 - Mealy FSM
- Write the Verilog description



Mealy FSM

From state diagram to Verilog, Contd.

 - States are...
 - A, B;
 - At least 1 bit is required to present them
- Inputs are...
 - 1-bit input w
- Outputs are...
 - 1-bit z
- Reset input is...
 - Asynchronous, active high
 - Strictly speaking, an edge from every state to A, in case of active Reset, could also be shown




Mealy FSM – State/Output Table

From state diagram to Verilog, Contd.

- Let us fill in the state/output table

Current state S	Input	Next state	Output
S	w	S_next	z
A	0	A	0
A	1	B	0
B	0	A	0
B	1	B	1

 


Note: We cannot "compress" the table here, as every combination of (S, w) may lead to a different output z

Mealy FSM – Verilog

From state diagram to Verilog, Contd.

Current state S	Input	Next state	Output
S	w	S_next	z
A	0	A	0
A	1	B	0
B	0	A	0
B	1	B	1

 

```

module fsm_Mealy (
    input w, CLK, Reset,
    output reg z
);
reg S_next, S;
parameter A = 1'b0, B = 1'b1; // states
// Next-state logic
always @ (*) begin
    S_next = A; // chosen as default
    case (S)
        A: if (w == 0) S_next = A;
           else       S_next = B;
        B: if (w == 0) S_next = A;
           else       S_next = B;
        default:      S_next = A; // chosen as default
    endcase
end
// State memory
always @ (posedge CLK or posedge Reset) begin
    if (Reset == 1) S <= A;
    else S <= S_next;
end
// Output logic
always @ (*) begin
    if ((S == B) && (w == 1)) z = 1'b1;
    else z = 1'b0;
end
endmodule

```

Moore FSM


Example



Moore FSM

From state diagram to Verilog

 
- Figure shows the state diagram of...
 - Moore FSM
- Write the Verilog description



Moore FSM

From state diagram to Verilog, Contd.

 - States are...
 - A, B, C;
 - At least 2 bits are required to present them
- Inputs are...
 - 1-bit input w
- Outputs are...
 - 1-bit z
- Reset input is...
 - Synchronous, active high
 - Strictly speaking, an edge from every state to A, in case of active Reset, could also be shown




Moore FSM – State/Output Table

From state diagram to Verilog, Contd.

- Let us fill in the state/output table

Current state S	Next state S_next		Output
S	Input w		z
	0	1	
A	A	B	0
B	A	C	0
C	A	C	1

 
Note: We are able to "compress" the table here as the output z does not depend on the input w



Moore FSM – Verilog

From state diagram to Verilog, Contd.

Current state S	Next state S_next		Output
S	Input w		z
	0	1	
A	A	B	0
B	A	C	0
C	A	C	1

 



```

module fsm_Moore (
    input w, CLK, Reset,
    output reg z);

    reg [1:0] S_next, S;
    parameter A = 2'b00, B = 2'b01, C = 2'b10; // states
    // Next-state logic
    always @ (*) begin
        S_next = A; // chosen as default
        case (S)
            A: if (w == 0) S_next = A;
               else      S_next = B;
            B: if (w == 0) S_next = A;
               else      S_next = C;
            C: if (w == 0) S_next = A;
               else      S_next = C;
            default:      S_next = A; // chosen as default
        endcase
    end
    // State memory
    always @ (posedge CLK) begin
        if (Reset == 1) S <= A; // effect of Reset active
        else S <= S_next;
    end
    // Output logic
    always @ (*) begin
        z = (S == C);
    end
endmodule

```

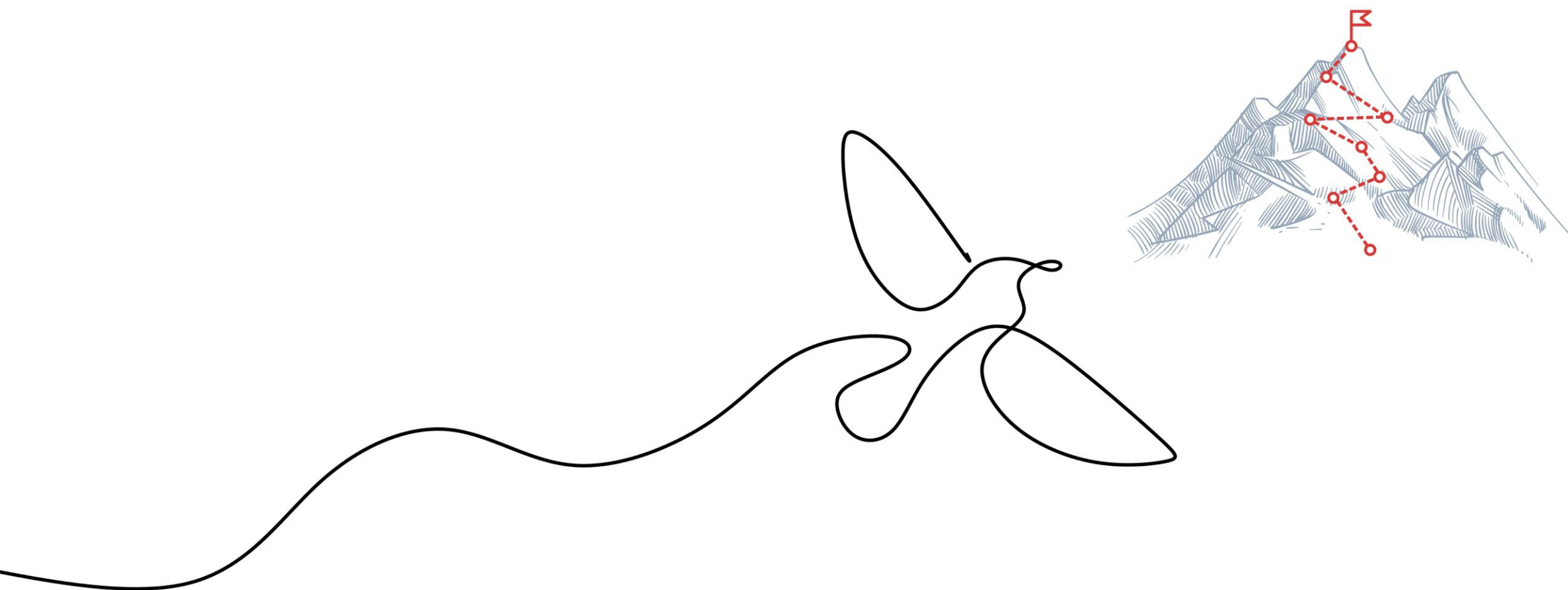

 

Serial Adder FSM

Example





Serial Adders

- Fast adders are complex and expensive
- If speed is not a priority, one could consider a cost-effective alternative of adding a pair of bits at a time using a **serial adder**
 - **Serial adder sums one bit of each of the two operands and produces one bit of the sum per clock cycle**

Designing Serial Adder

  
- Suggested building blocks
 - Shift right register
 - Serial input: 1-bit IN
 - Parallel 8-bit input, taken when LOAD is active
 - Serial output: 1-bit
 - Enable input: EN, enables shifting
 - Down counter (**timer**)
 - Parallel 4-bit input, taken when LOAD is active
 - Enable input: EN, enables counting
 - Output **decreases** by one in every clock cycle



Serial Adder

Block Diagram

 
- Shift-right registers output one bit of operands **A** and **B** in every clock cycle
- Down-counter (timer) counts the number of cycles for addition (the number of pairs of bits to sum to obtain **S**)



Serial Adder

INIT

 
- **INIT** loads new operands and reinitializes the sum and the timer
 - Operands A and B initialized to new values
 - Sum S initialized to **zero**
 - Timer initialized to nine (the number of operand bits + 1), as that many cycles will be required to compute the sum



Serial Adder

Count Down

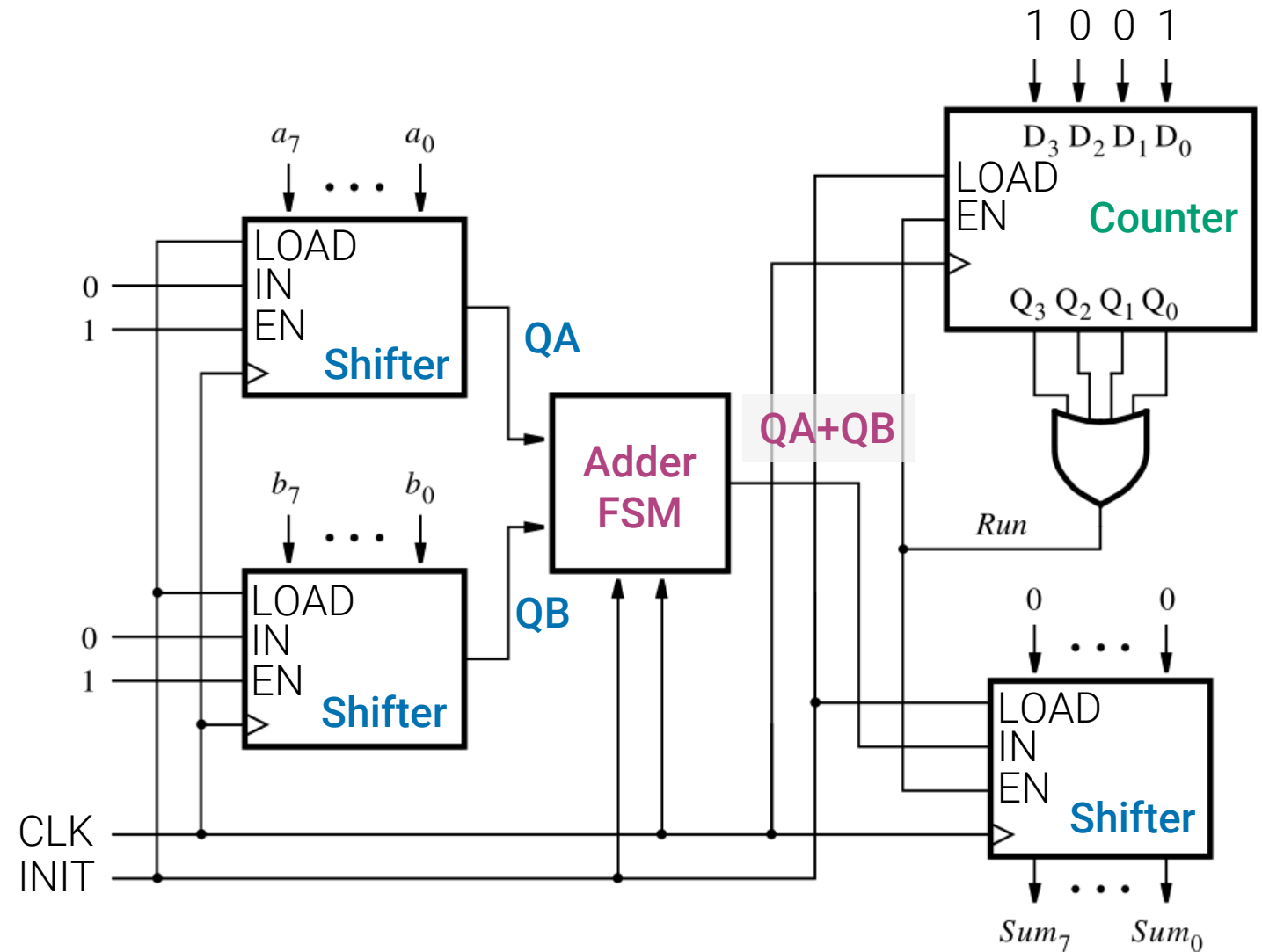- Time's up when the output of the timer (down counter) drops to all zeros
- Sequence at the output of the counter
 - 1001 -> 1000
 - > 0111 -> 0110 ->
 - > 0101 -> 0100 ->
 - > 0011 -> 0010 ->
 - > 0001 -> 0000
- Run** signal becomes '0' after nine clock cycles



Serial Adder


Count Down, Contd.

■ While **Run** = '1'

- The timer and the sum register are enabled (EN = '1')
- The counter counts (time passes, clock cycles elapse) and the sum register receives one new bit every clock cycle

■ While **Run** = '0'

 
- The timer and the sum register are disabled (EN = '0')
- The counter does not count
- The sum **S** does not change



Serial Adder

Operation, Summary

- Initialize the shift registers and the counter
 - Load (in parallel) vectors A and B in their respective shift registers
 - Load the initial value in the timer
 - Clear the contents of the sum register
- In each clock cycle
 - Add a pair of bits using the **Adder FSM**
 - Shift the resulting sum bit into the output register
 - Shift the input vectors A and B to release the next pair of bits to be added
 - Decrement the counter (count down...)
- Stop when the timer finishes counting
 - The number of clock cycles should be chosen so that all eight bits of the sum get stored in the corresponding register, one per cycle

 

Serial Adder

Example Sum

- Consider $A = (0010\ 1011)_2$ and $B = (0011\ 0010)_2$
- The expected sum S is $(0101\ 1101)_2$
- Sequence at the output of the sum register
 - 0000 0000 -> 1 000 0000
 - -> 0100 0000 -> 1010 0000
 - -> 1101 0000 -> 1110 1000
 - -> 0111 0100 -> 1011 1010
 - -> 0101 1101
 - The initial value is all zeros
 - Eight clock cycles are required to shift in the eight bits of the sum

$(0100\ 0100)_2$ Carry


$$\begin{array}{r} (0010\ 1011)_2 \\ + (0011\ 0010)_2 \\ \hline (0101\ 1101)_2 \\ = (5D)_{16} \end{array}$$

Serial Adder

Timing Diagram

Carry $(0100\ 0100)_2$
 
$$\begin{array}{r} (0010\ 1011)_2 \\ + (0011\ 0010)_2 \\ \hline (0101\ 1101)_2 \\ = (5D)_{16} \end{array}$$




Serial Adder

Timing Diagram, Contd.

Carry $(0100\ 0100)_2$

$$\begin{array}{r} (0010\ 1011)_2 \\ + (0011\ 0010)_2 \\ \hline \end{array}$$

 
$$\begin{array}{r} (0101\ 1101)_2 \\ = (5D)_{16} \end{array}$$




Serial Adder FSM

When INIT is Active

 - Adder FSM needs only two states
 - S0: when carry is '0'
 - S1: when carry is '1'



$$s = x + y + \text{carry}$$

 


Note: INIT active means that new operands are loaded and new addition can commence; carry-in is therefore 0, and so the state machine must remain in or return to the S0 state (in which carry-in is '0');


Serial Adder FSM

When INIT is Inactive

 - Adder FSM needs only two states
 - S0: when carry is '0'
 - S1: when carry is '1'




$$s = x + y + \text{carry}$$

 

Note: INIT inactive means the addition is in process

Serial Adder FSM, Contd.

 - Adder FSM with two states
 - S0: when carry is '0'
 - S1: when carry is '1'
- State/output tables




$$s = x + y + \text{carry}$$

INIT = 0								
Present State S	Next state S_next				Output s			
	One-bit Inputs xy				One-bit Inputs xy			
	00	01	10	11	00	01	10	11
S0	S0	S0	S0	S1	0	1	1	0
S1	S0	S1	S1	S1	1	0	0	1

INIT = 1								
Present State S	Next state S_next				Output s			
	One-bit Inputs xy				One-bit Inputs xy			
	00	01	10	11	00	01	10	11
S0	S0	S0	S0	S0	0	1	1	0
S1	S0	S0	S0	S0	1	0	0	1

Serial Adder FSM


In Verilog

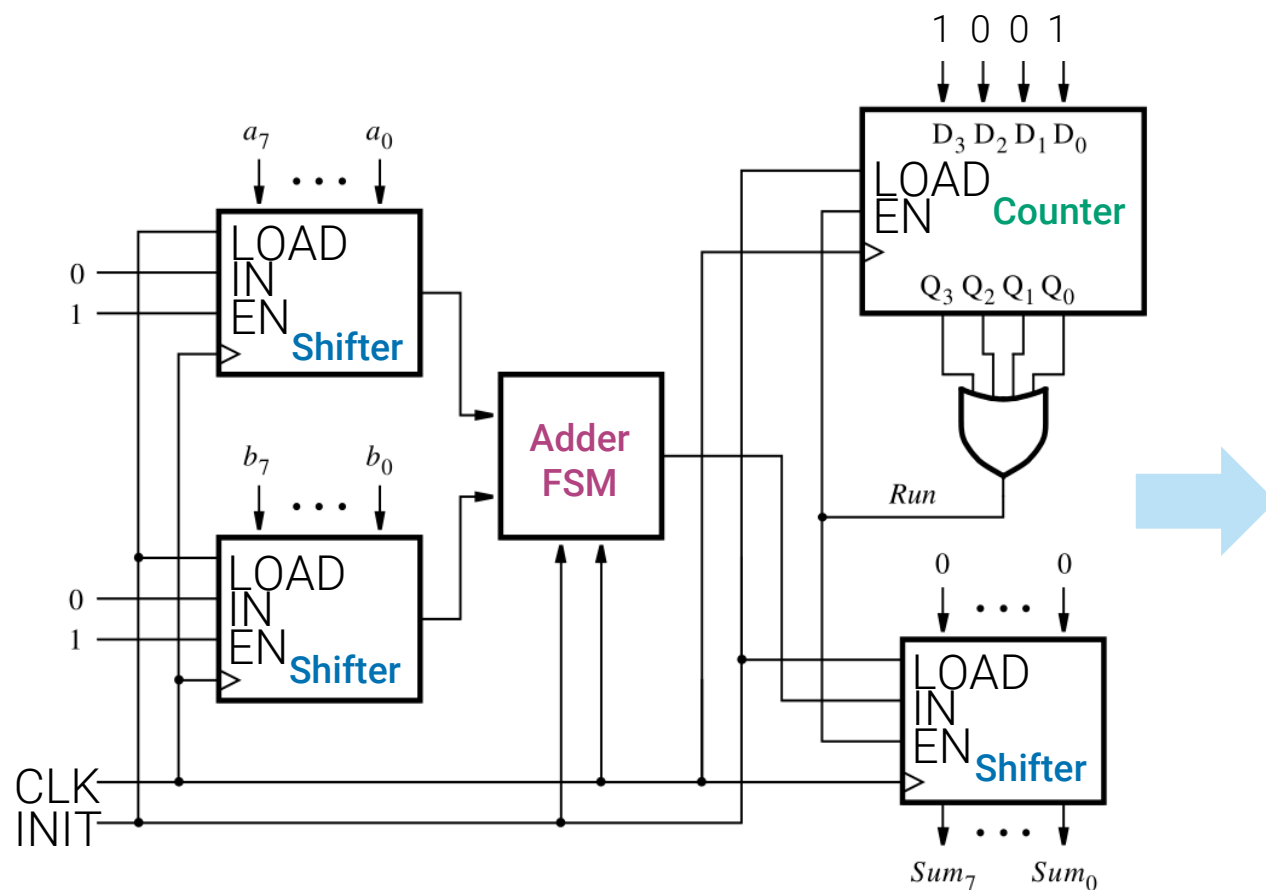

```

module serialadderfsm (a, b, init, clk, sum);
    parameter n = 8;
    input a, b, init, clk;
    output reg sum;
    parameter S0 = 1'b0, S1 = 1'b1;
    reg S_next, S;
    // Next-state logic
    always @(*) begin
        end
    
```

In Verilog

 


```
module serialadderfsm (a, b, init, clk, sum);
    parameter n = 8;
    input a, b, init, clk;
    output reg sum;
    parameter S0 = 1'b0, S1 = 1'b1;
    reg S_next, S;
    // Next-state logic
    always @(*) begin

end
```

Serial Adder FSM


In Verilog

 

```
module serialadderfsm (a, b, init, clk, sum);
    parameter n = 8;
    input a, b, init, clk;
    output reg sum;
    parameter S0 = 1'b0, S1 = 1'b1;
    reg S_next, S;
    // Next-state logic
    always @(*) begin
        S_next = S0;
        case (S)
            S0: begin
                if (init)          S_next = S0;
                else if (a & b) S_next = S1;
                else                S_next = S0;
            end
            S1: begin
                if (init)          S_next = S0;
                else if (~a & ~b) S_next = S0;
                else                S_next = S1;
            end
            default: S_next = S0;
        endcase
    end
end
```

Serial Adder FSM

In Verilog

 


```

module serialadderfsm (a, b, init, clk, sum);
    parameter n = 8;
    input a, b, init, clk;
    output reg sum;
    parameter S0 = 1'b0, S1 = 1'b1;
    reg S_next, S;
    // Next-state logic
    always @(*) begin
        S_next = S0;
        case (S)
            S0: begin
                if (init) S_next = S0;
                else if (a & b) S_next = S1;
                else S_next = S0;
            end
            S1: begin
                if (init) S_next = S0;
                else if (~a & ~b) S_next = S0;
                else S_next = S1;
            end
            default: S_next = S0;
        endcase
    end
end
  
```

Serial Adder FSM


In Verilog

 


```
// State memory
// Synchronous reset
always @ (posedge clk) begin
    if (init) S <= S0;
    else      S <= S_next;
end

// Output logic
always @(*) begin
    if (S == S0) sum = a ^ b;
    else        sum = ~(a ^ b);
end

endmodule
```

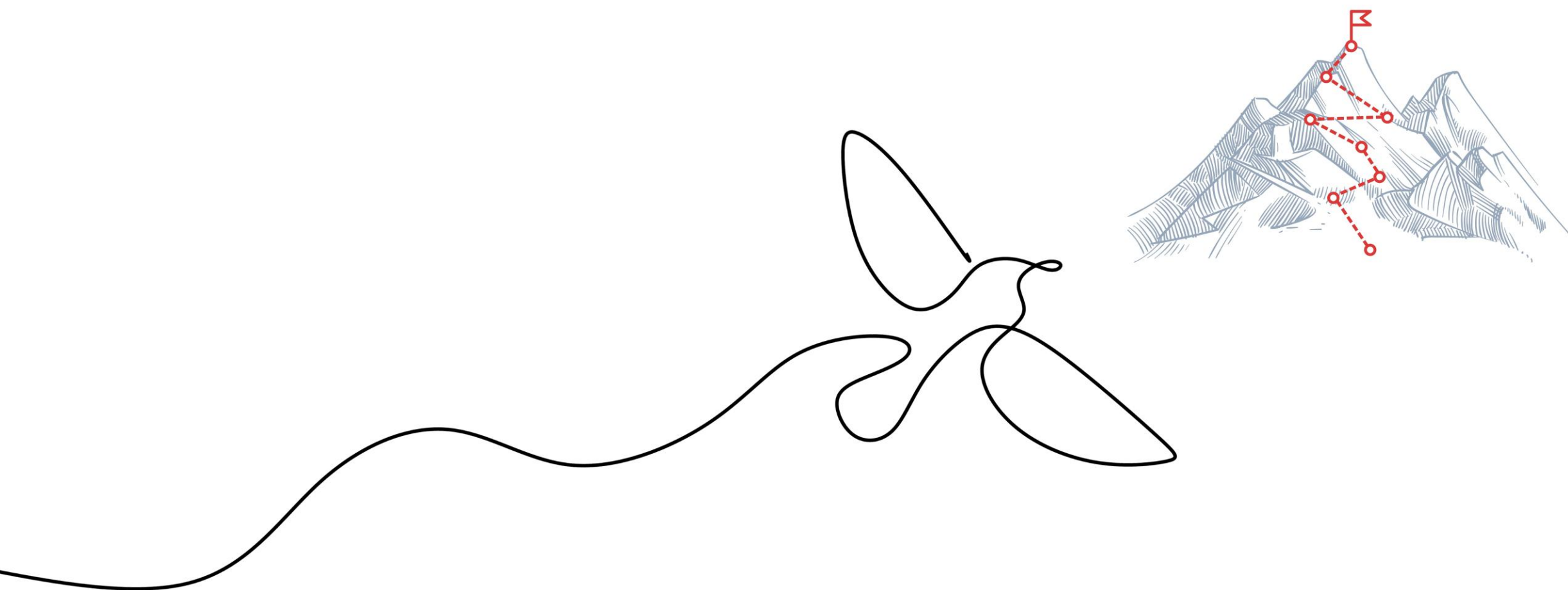

Literature

 

- Appendix A: Verilog Reference
 - A.14.8, A.14.9
- Chapter 6: Synchronous Sequential Circuits
 - 6.5 Serial Adder Example