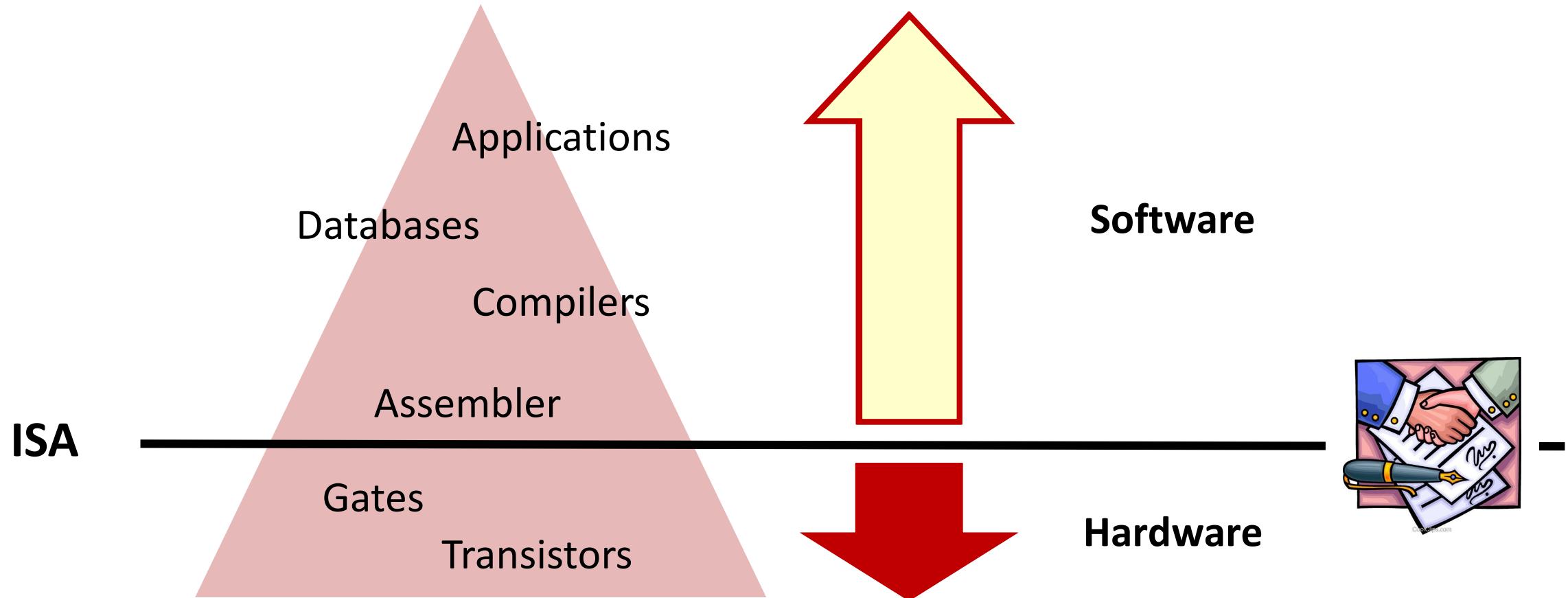


CS-200
Computer Architecture


Part 2a. Processor, I/Os, and Exceptions
Multicycle Processor

Paolo lenne
<paolo.ienne@epfl.ch>


The Contract between HW and SW




The Processor

 


Unified Memory

 


A Big Finite-State Machine

 


Single-Cycle Processor

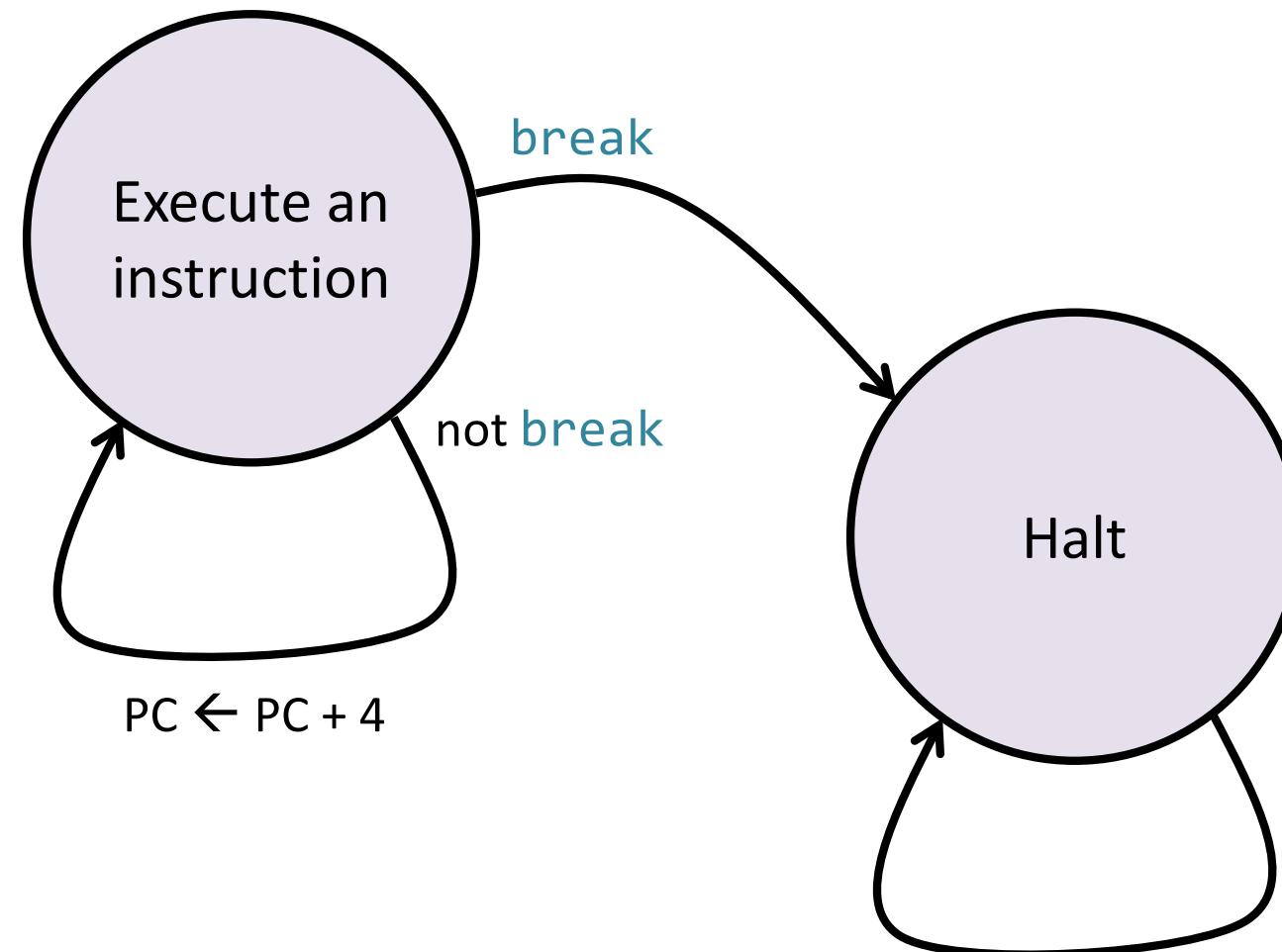

Propagation Time

 

Increasing the Frequency?

 


Two-Cycle Processor


Did we gain anything?

1 instruction per cycle
at frequency F


 
1 instruction every **two cycles**
at frequency $2F$




Not All Paths Are Born Equal!

 


And Maybe Memories Are Sequential

  

Multi-Cycle Processor

 


Multi-Cycle Processor

 


“Understand” the instruction and take a different path as needed (different resources to control, different complexity)

Multi-Cycle Processor

 


Multi-Cycle Processor

 


Multi-Cycle Processor

We will try

 - ① not to have too many stages
- ② to have paths as balanced as possible




Mealy or Moore?

 

Mealy FSM

Output depends on
input and state

Sometimes
this needs
more cycles...

 


Moore FSM


Output depends on
state only

...and
sometimes
this is not
acceptable

Building the Circuit

 


Add Progressively What We Need

 

We will need an **Instruction Register** to memorize the instruction coming from memory


We will need to **enable** these registers when there is something new to record
→ we will have the **FSM generate them**

Follow the Functionality

 


When an instruction arrives into IR,
the controller needs to know what it is
(the next state depends on it!)
→ connect IR to the controller


I-Type Instructions Need RF and ALU

 


I-Type Instructions Need RF and ALU

 

 
R-Type Instructions Need a Second Operand




U-Type Instructions Write an Immediate

 


Load and Stores Produce a Memory Address

 


Loads Write the Read Data into the RF

 


Stores Send an Operand to Memory

 

 
Branches Need to Write an Offset to the PC




jal Needs to Store PC + 4 in the RF

 




Jumps Need to Write an Address to the PC

 

Time to Go Back to the FSM!

 

And We Can Still Change the FSM...

 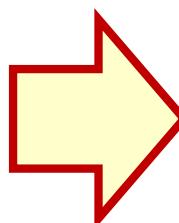 


Two separate states **may** be simpler and cleaner...
(but either solution is fine!)

Do Not Write Verilog until Done!


- Verilog and VHDL are **HDLs** → Hardware **Description** Languages
- Describe something only when it is perfectly **clear**:
 - You have **drawn a diagram** like the one of the previous slide
 - You have clearly identified **combinational** and **sequential** blocks
- Always **decompose complex sequential** blocks
 - Describe **only** sequential blocks that are **simple registers** (e.g., IR)
 - Draw **hierarchical diagrams** until sequential blocks are trivial
- Use a **hierarchical approach** (much as in programming) and use your diagrams to guide the creation of modules (e.g., PC)

Formal FSM
→ Ready to write






Write Only Simple Stuff

 

“Open the Box” of Complex Stuff

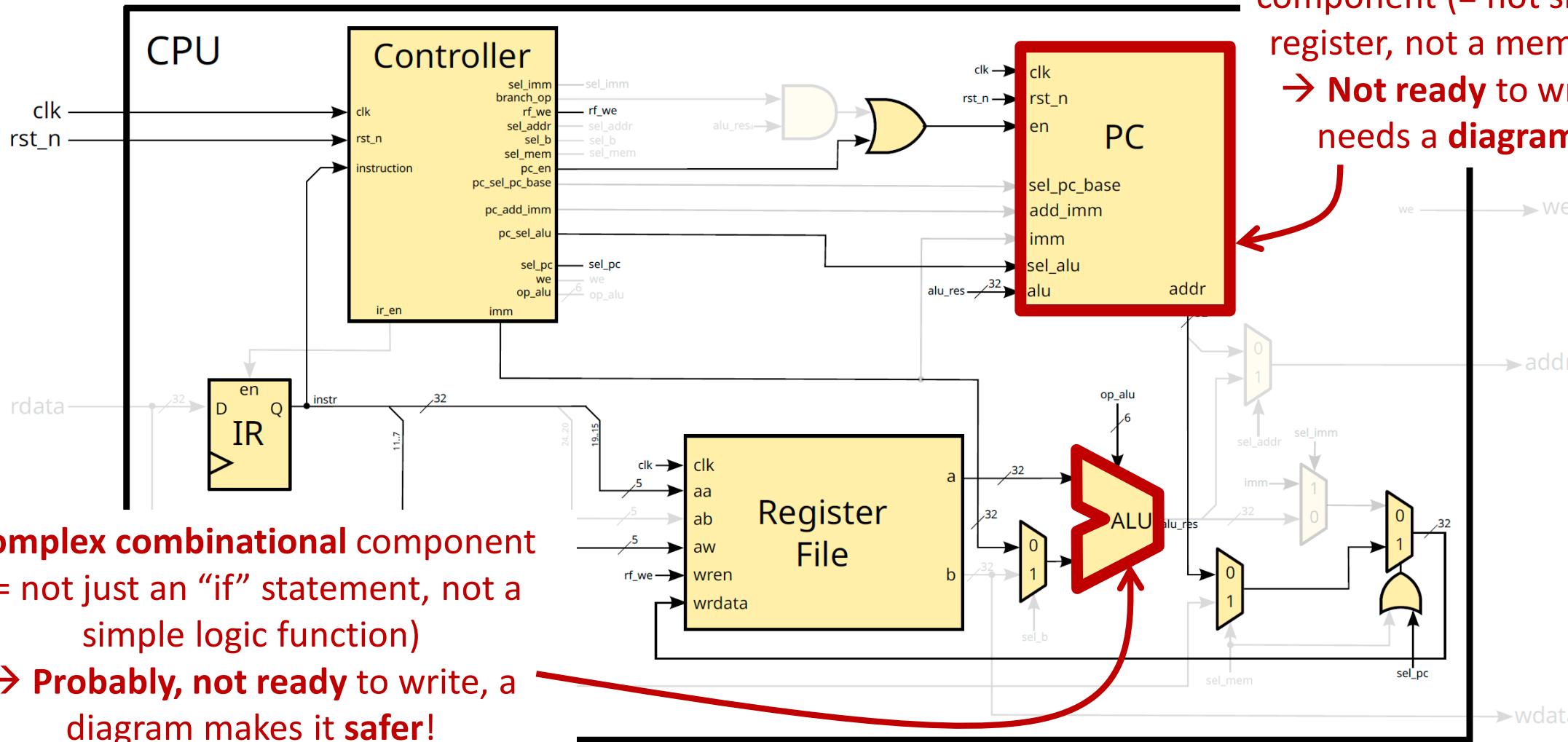

Detail Complex Combinational Modules

     

Write Verilog by Sticking to Basic Patterns

Combinational

- `always@ (*)` is used to describe a block with combinational logic. The `*` symbol is used in the sensitivity list to trigger the block whenever any of the inputs are changed; therefore, the outputs reflect the inputs change.

Verilog guidelines in Moodle

```
always @ (posedge clk)
begin
  if (reset == 1)
    q <= 0;
  else if ((enable1 == 1) && (enable2 == 1))
    q <= d;
end
```

```
always @ (*)
begin
  if (a)
    y = ~b;
  else
    y = b;
end
```


You can write much more complex combinational blocks (e.g., next state in FSMs)...

...but this is just about the most complex sequential block you want to write!
(only registers and counters)


Sequential

- `always@ (posedge clk)` is used to describe a block with sequential logic i.e., has flip-flops. The two keywords `posedge` and `negedge` determine whether the active clock edge of the flip-flops is the rising or the falling clock edge respectively.

Three always Blocks per FSM, Always!

 


Mealy

 


Moore

Beware of Zero-Delay Simulation!

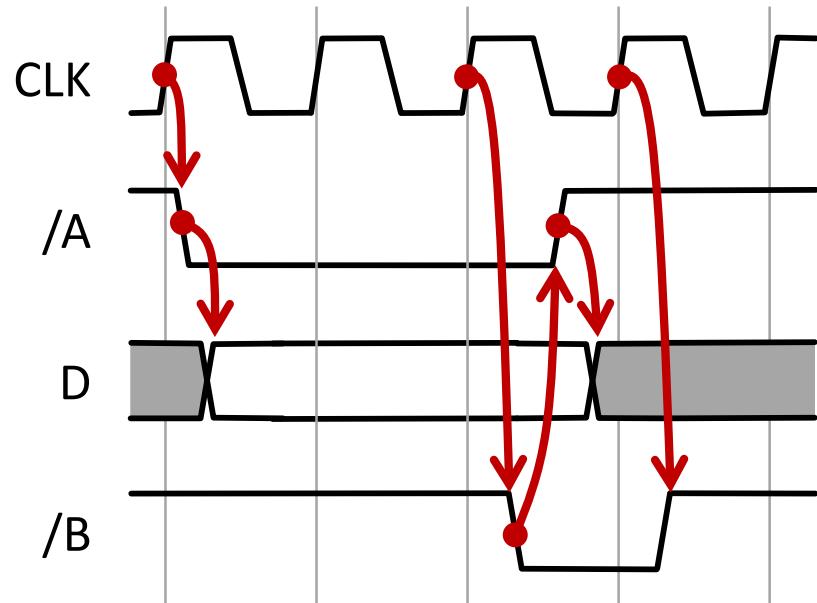

Real delays suggest **causality**

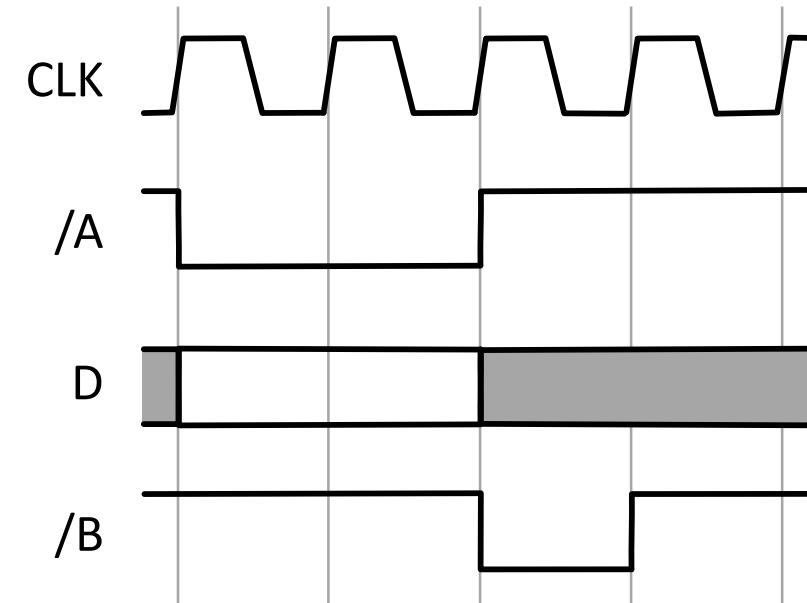A good timing diagram
even **shows causality explicitly**
with arrows



Alas, all this is **lost** in
zero-delay simulation

Consider redrawing by hand
in difficult debugging situations

References

- Patterson & Hennessy, COD – RISC-V Edition
 - **Chapter 4**; only **Section 4.1** to **4.5**