

Plan du cours

- Circuits convertisseurs
 - Inductor volt-second balance
 - Capacitor charge balance
 - Small-ripple approximation

References additionnelles:

Fundamentals of Power Electronics, Robert W. Erickson, Dragan Maksimović, SECOND EDITION University of Colorado Boulder, Colorado


Fundamentals of Power Semiconductor Devices, B. J. Baliga, Springer (2008)

Dispositifs de Puissance à Semiconducteurs: Utilisation en circuits, Prof. A. Rufer, EPFL (2002)


Introduction – buck converter

Single Pole Double Throw (SPDT) Switch

SPDT switch changes dc component

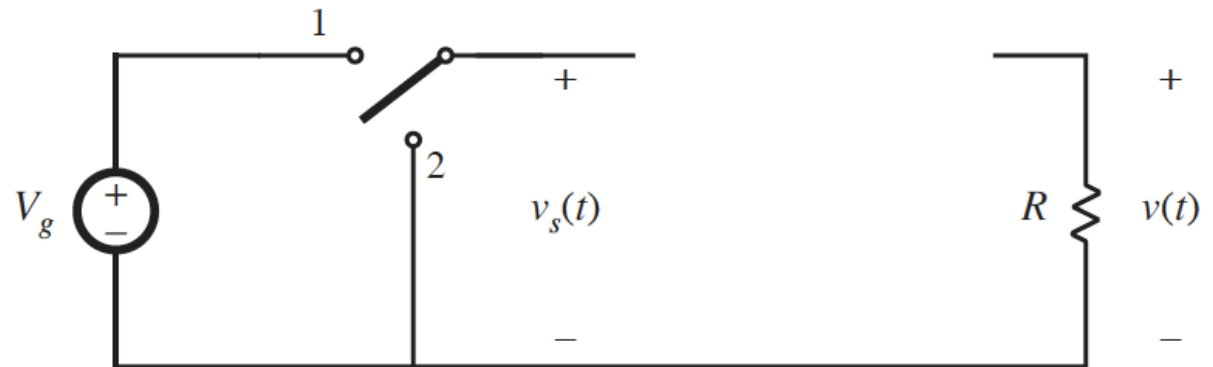


Switch output voltage waveform

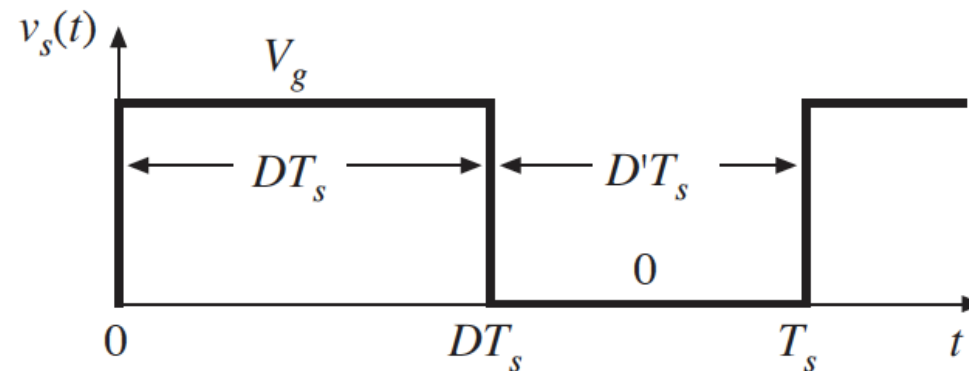

Duty cycle D :
 $0 \leq D \leq 1$

complement D' :
 $D' = 1 - D$

Switch position: 1 2 1

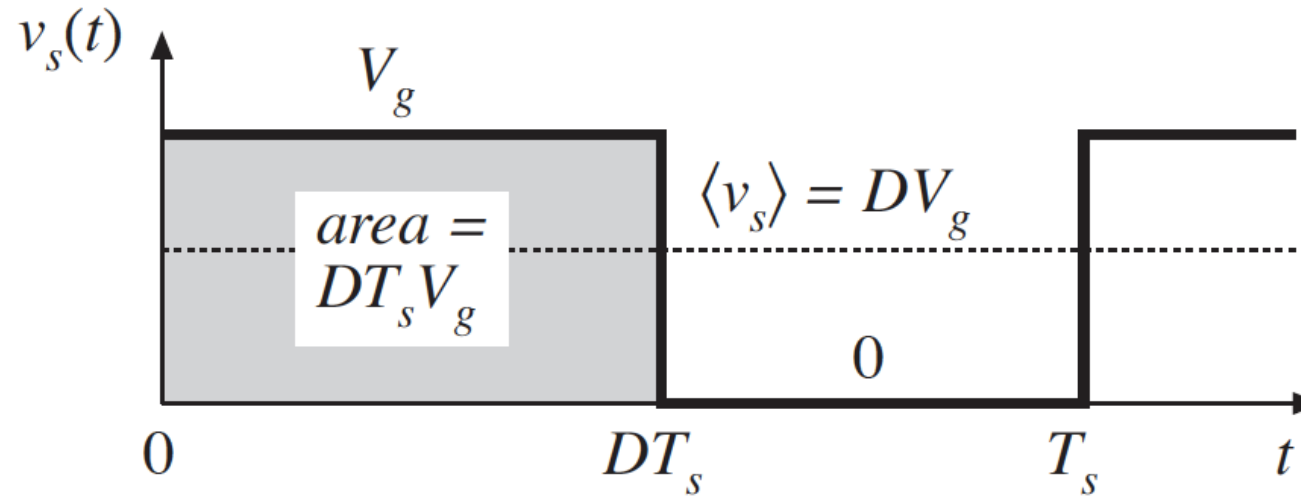
buck converter

Fourier analysis: Dc component = average value


$$\langle v_s \rangle = \frac{1}{T_s} \int_0^{T_s} v_s(t) dt$$

$$\langle v_s \rangle = \frac{1}{T_s} (DT_s V_g) = DV_g$$

buck converter

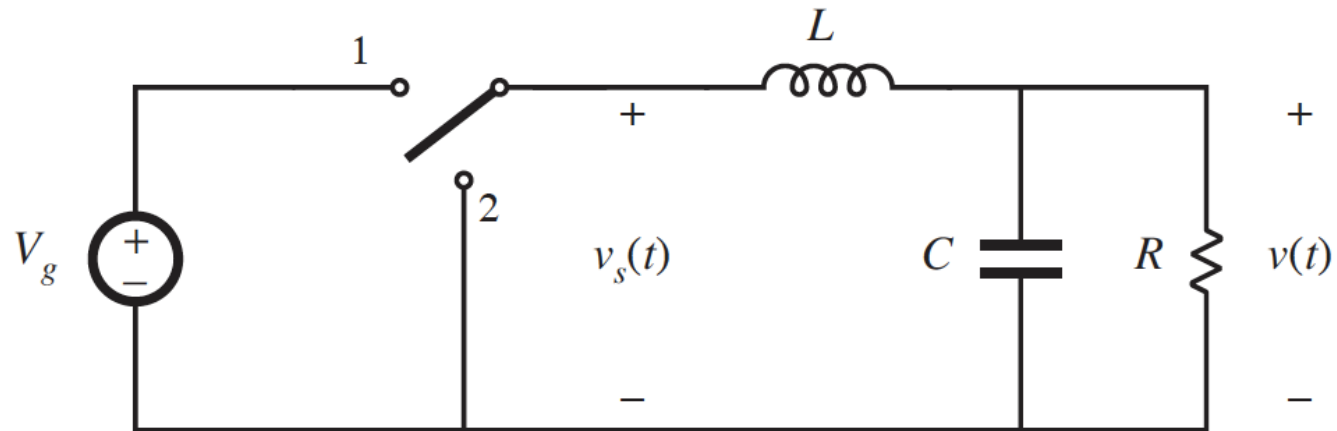


$$v \approx \langle v_s \rangle = DV_g$$

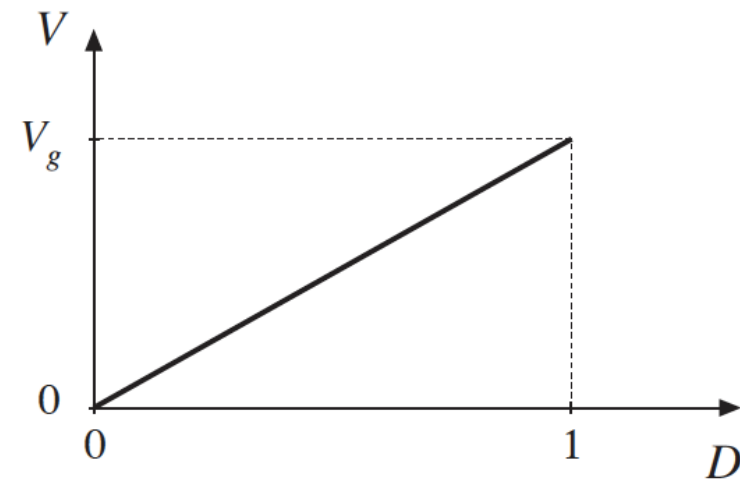


Filtre LC pour éliminer les harmoniques à haute fréquence

Convertisseurs DC/DC


Buck

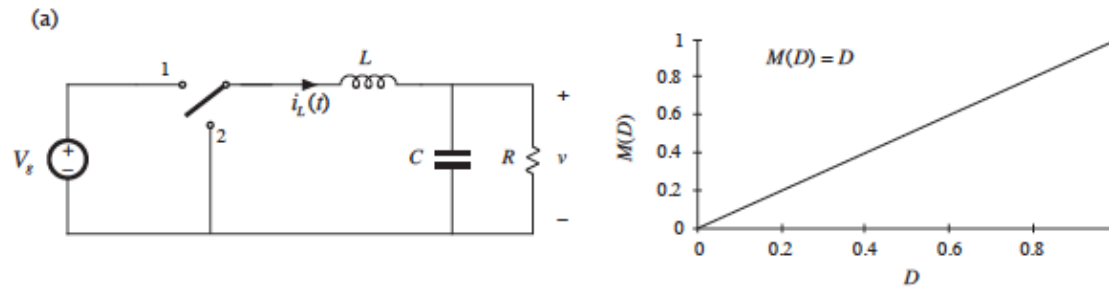

Boost

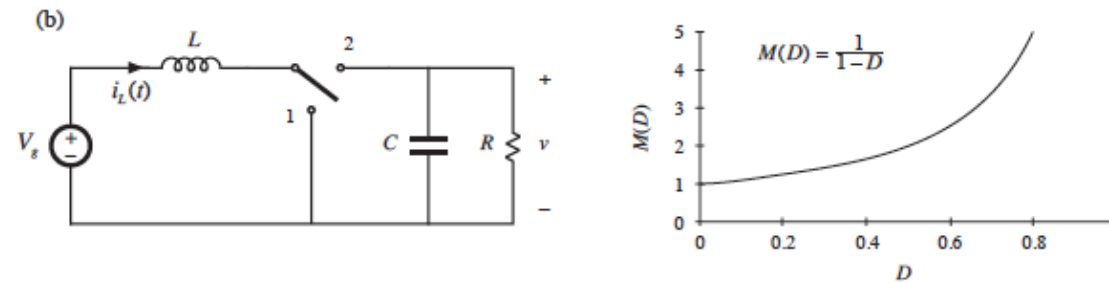

Buck-boost

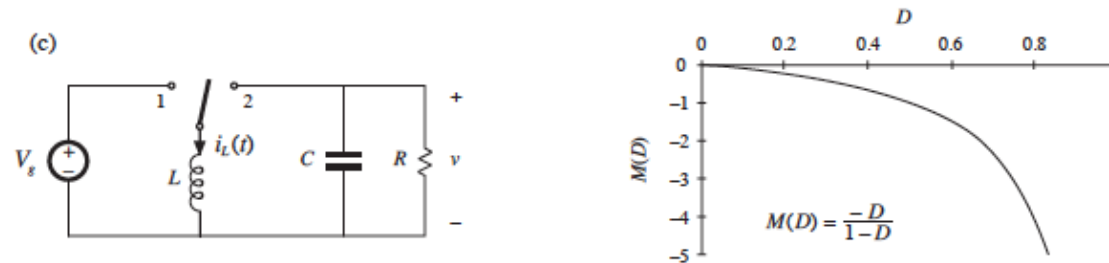


Comment calculer le facteur $M(D)$?

Introduire les principes de:

- Inductor volt-second balance
- Capacitor charge balance
- Small-ripple approximation


Méthode: volt-second balance et capacitor-charge balance

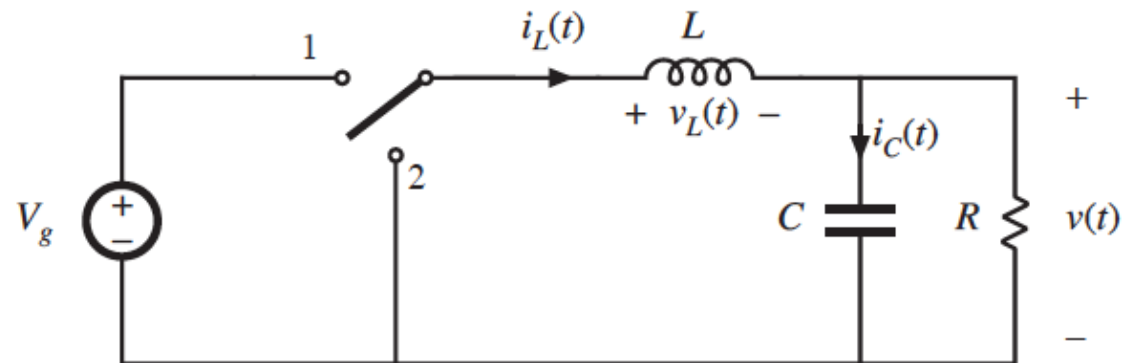*Buck converter
containing practical
low-pass filter*




*Actual output voltage
waveform*

$$v(t) = V + v_{\text{ripple}}(t)$$

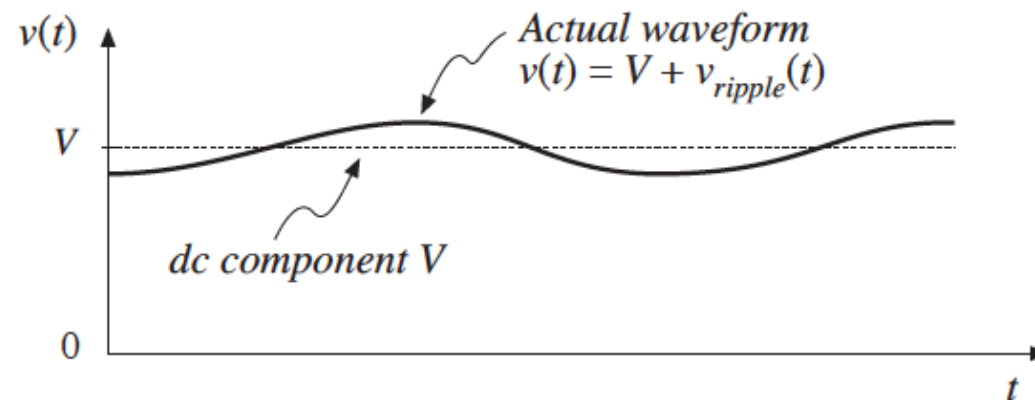

Impossible de construire un filtre passe bas parfait:

- Il y aura toujours des ondulations à la sortie... mais nous les considérons très faibles
- **Approximation de faibles ondulations** (small-ripple approximations)

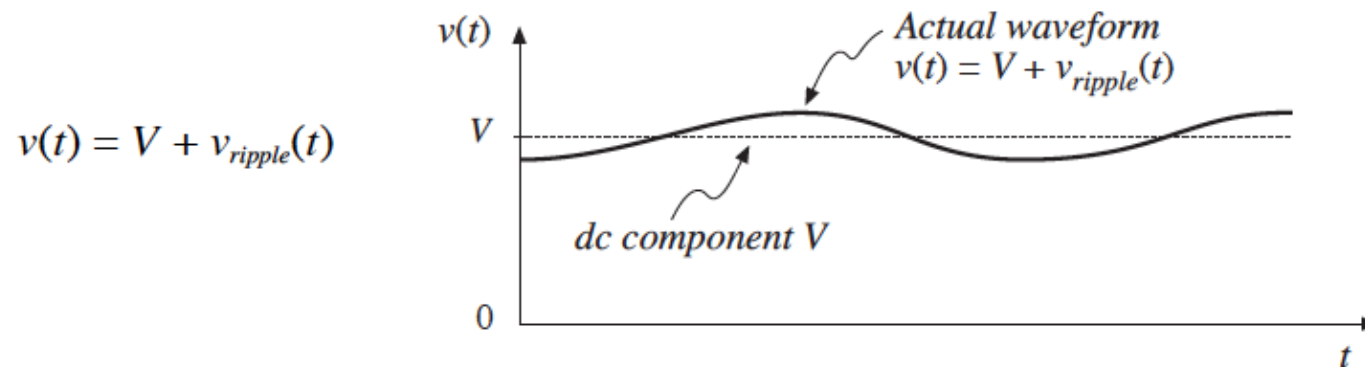Approximation de faibles ondulations (small ripple approximation)

In a well-designed converter, the output voltage ripple is small. Hence, the waveforms can be easily determined by ignoring the ripple:

$$\|v_{\text{ripple}}\| \ll V$$

$$v(t) \approx V$$

- On considère que la composante DC est beaucoup plus grande que l'AC: $v(t) \sim V$
- Cela élimine la dépendance des variables d'intérêt avec t

Approximation de faibles ondulations (small ripple approximation)

Approximation de **faibles ondulations** (small-ripple approximation) **est valable pour:**


- Des ondulations faibles
- Forme d'ondes continue
- **N'est pas valable pour des signaux discontinus** (provenus des commutations, par exemple v_L)
- Cette approximation est appliquée pour: **courant sur les inducteurs** ou **tension sur les condensateurs**
- La période T_s est petite comparée aux constants de temps du circuit.

Cette approximation simplifie la solution, spécialement sur les filtres:

Il n'y a pas besoin de résoudre des équations différentielles

Méthode: volt-second balance et capacitor charge balance

Application: convertisseur "buck"

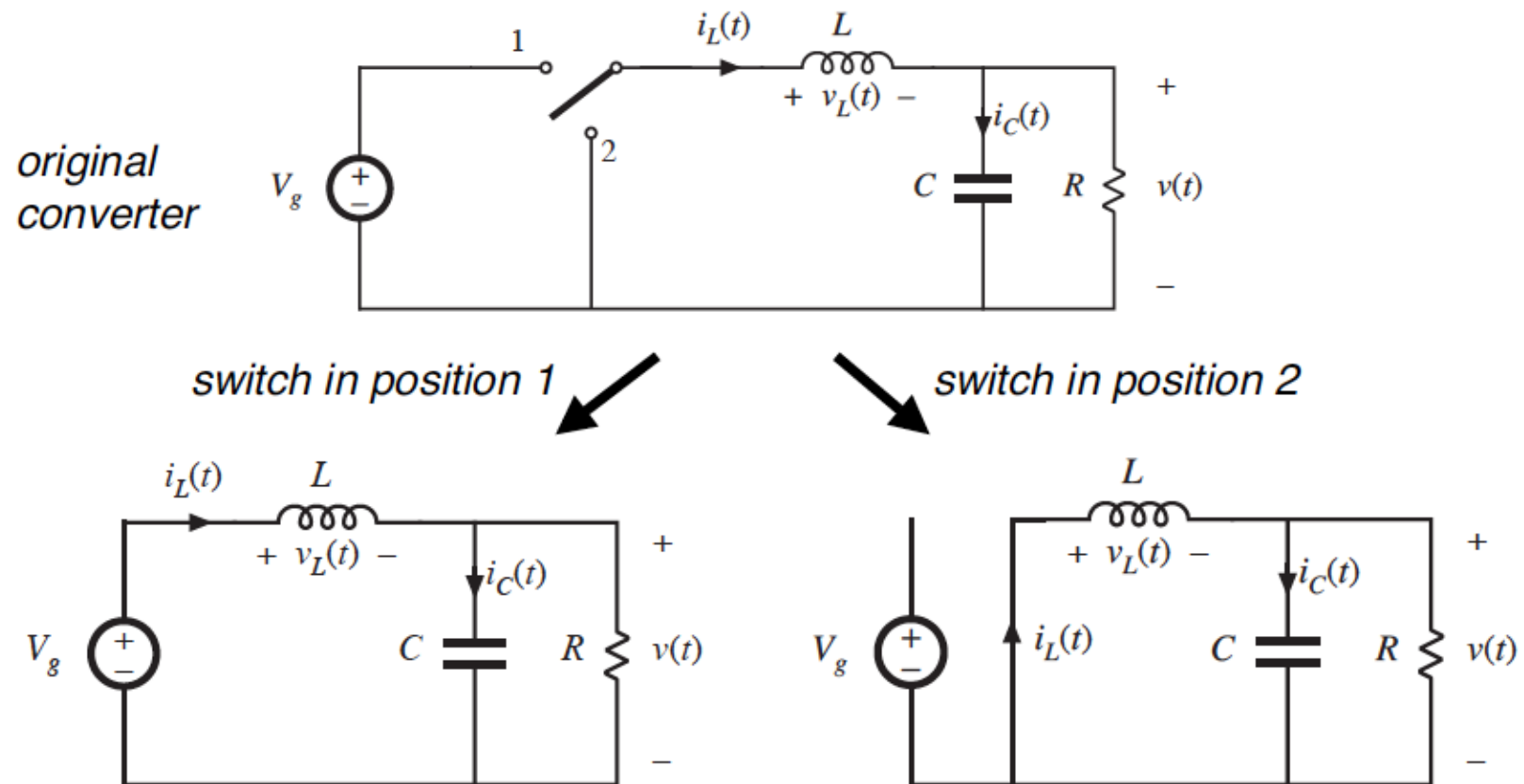


Méthode: volt-second balance et capacitor charge balance**Application: convertisseur “buck”****Position 1***Inductor voltage*

$$v_L = V_g - v(t)$$

Small ripple approximation:

$$v_L \approx V_g - V$$

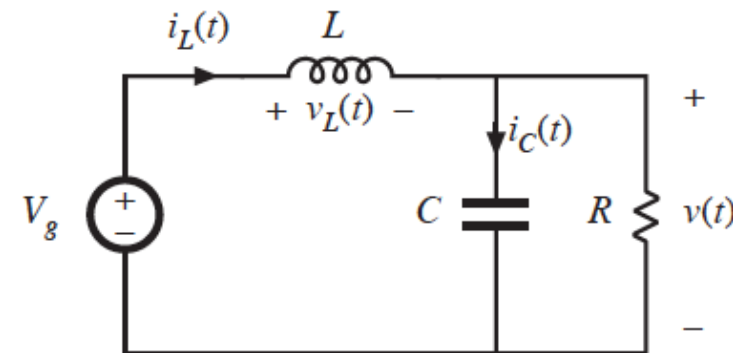*Knowing the inductor voltage, we can now find the inductor current via*

$$v_L(t) = L \frac{di_L(t)}{dt}$$

Solve for the slope:

$$\frac{di_L(t)}{dt} = \frac{v_L(t)}{L} \approx \frac{V_g - V}{L}$$

⇒ The inductor current changes with an essentially constant slope

Méthode: volt-second balance et capacitor charge balance

Application: convertisseur “buck”


Position 2

Inductor voltage

$$v_L(t) = -v(t)$$

Small ripple approximation:

$$v_L(t) \approx -V$$

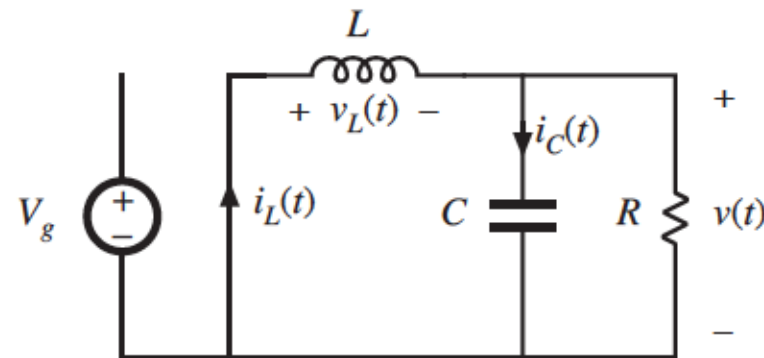

Knowing the inductor voltage, we can again find the inductor current via

$$v_L(t) = L \frac{di_L(t)}{dt}$$

Solve for the slope:

$$\frac{di_L(t)}{dt} \approx -\frac{V}{L}$$


$\Rightarrow$ *The inductor current changes with an essentially constant slope*

Negative slope

Méthode: volt-second balance et capacitor charge balance

Application: convertisseur "buck"

Plots de courant et tension

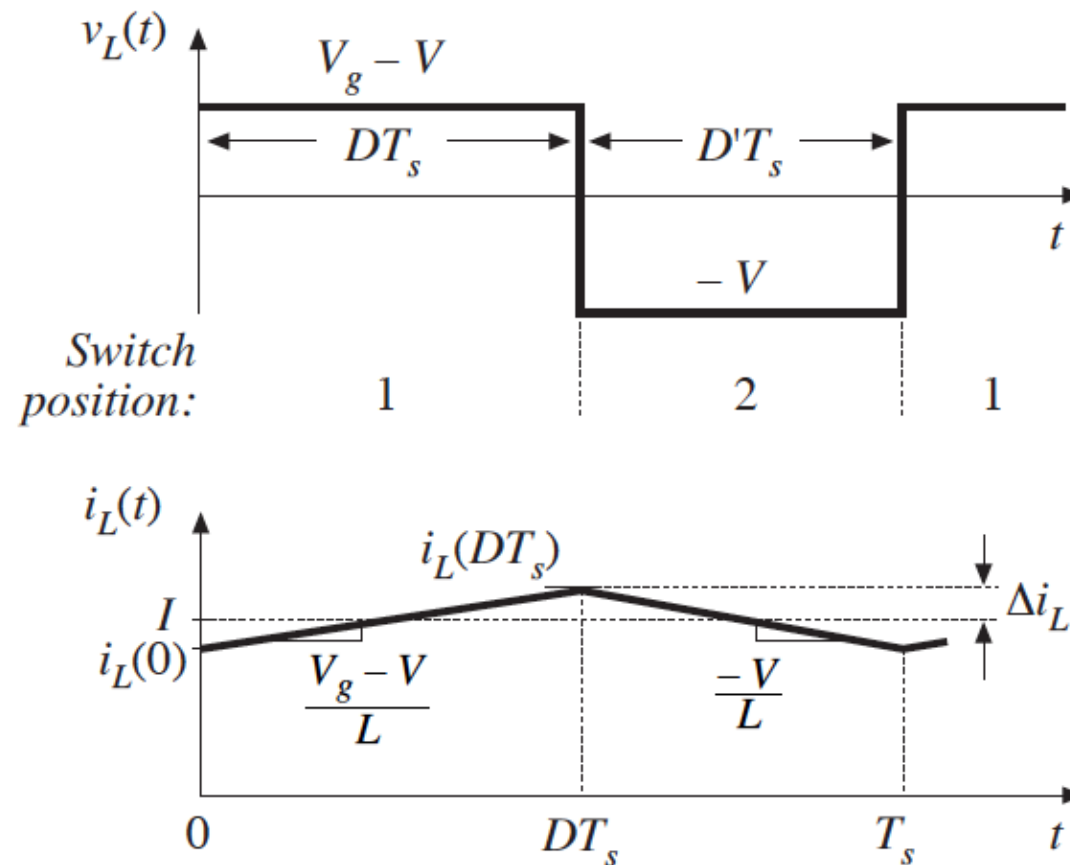


$$v_L(t) = L \frac{di_L(t)}{dt}$$

inductor current slope is constant

Méthode: volt-second balance et capacitor charge balance

Application: convertisseur "buck"

Ripple

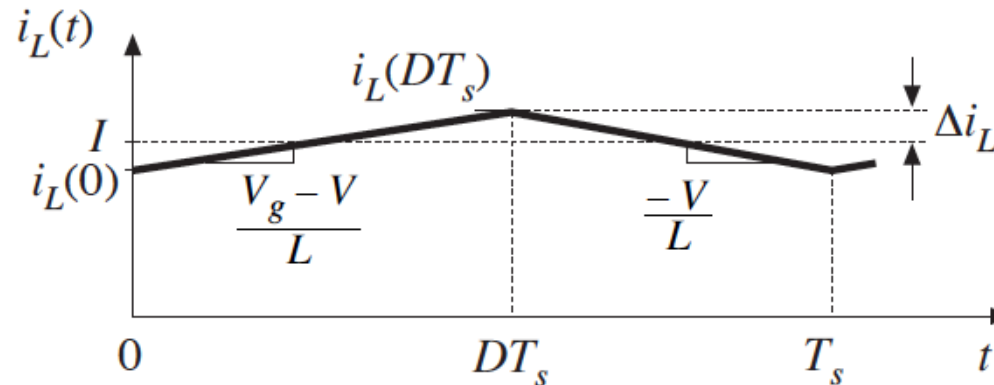(change in i_L) = (slope)(length of subinterval)

$$(2\Delta i_L) = \left(\frac{V_g - V}{L} \right) (DT_s)$$

$$\Rightarrow \Delta i_L = \frac{V_g - V}{2L} DT_s$$

$$L = \frac{V_g - V}{2\Delta i_L} DT_s$$


value of inductance in the
buck converter

- Knowledge of the **peak current** is necessary when specifying the ratings of these devices
- Typical values of Δi_L lie in the **range of 10% to 20%** of the full-load value of the dc component I
- It is undesirable to allow Δi_L to become too large:
 - increase the peak currents of the inductor and of the semiconductor switching devices
 - increase the size and cost of the inductors
- The small-ripple approximation $I_L = I$ is usually justified for the inductor current
 - The problem could be solved exactly but results are typically very close to this approximation.

Méthode: volt-second balance et capacitor charge balance

Application: convertisseur “buck”

Régime de transitoire (turn on)

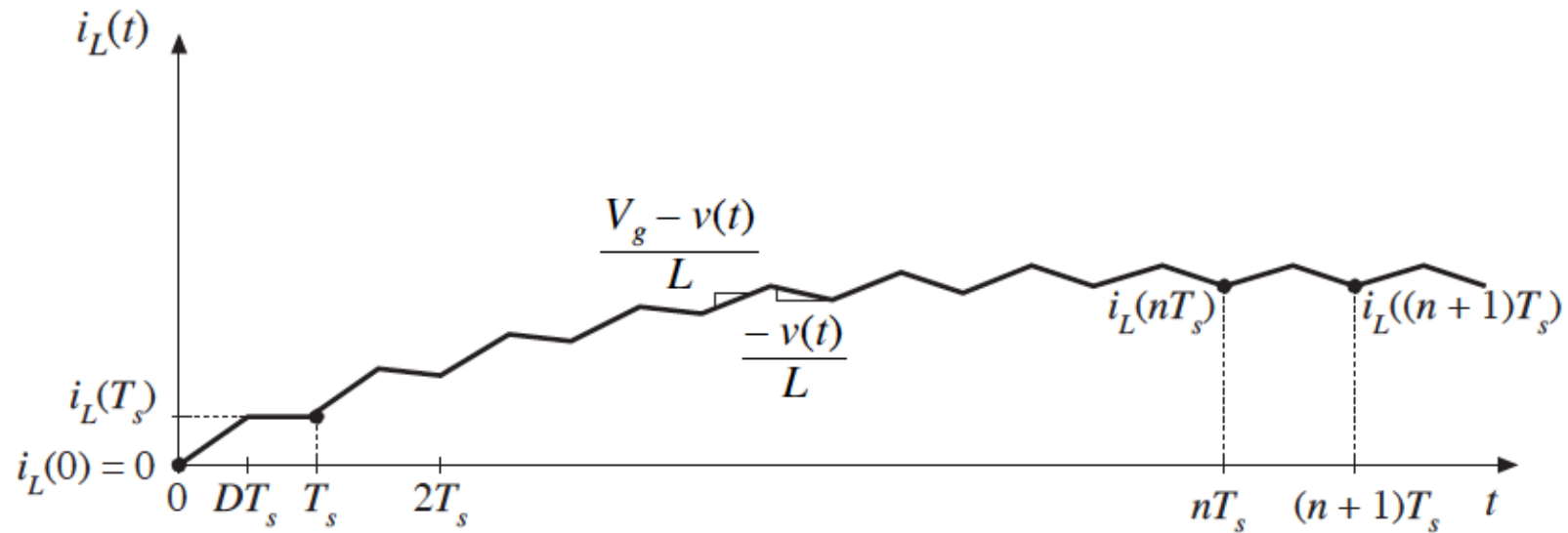

When the converter operates in equilibrium:

$$i_L((n+1)T_s) = i_L(nT_s)$$

Principe “volt-second balance”

Inductor defining relation:

$$v_L(t) = L \frac{di_L(t)}{dt}$$

Integrate over one complete switching period:

$$i_L(T_s) - i_L(0) = \frac{1}{L} \int_0^{T_s} v_L(t) dt$$

In periodic steady state, the net change in inductor current is zero:

$$0 = \int_0^{T_s} v_L(t) dt$$


Hence, the total area (or volt-seconds) under the inductor voltage waveform is zero whenever the converter operates in steady state.

An equivalent form:

$$0 = \frac{1}{T_s} \int_0^{T_s} v_L(t) dt = \langle v_L \rangle$$

The average inductor voltage is zero in steady state.

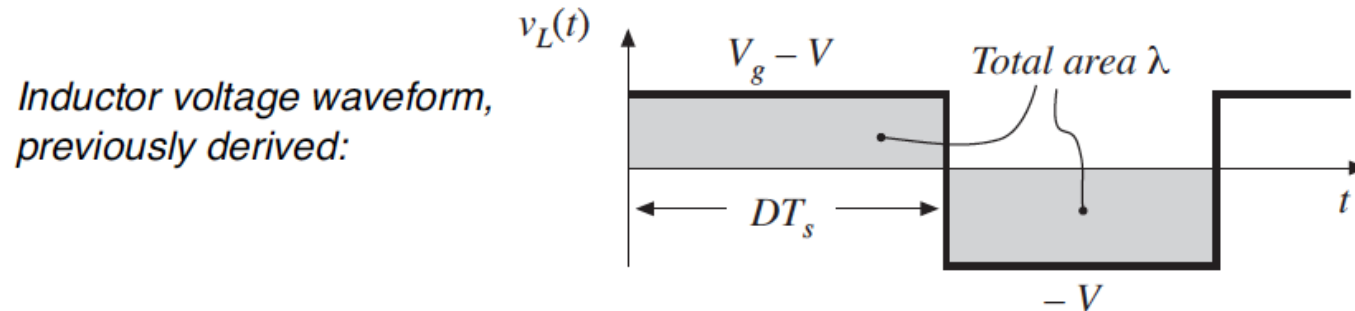Principe “volt-second balance”: convertisseur “buck”



Integral of voltage waveform is area of rectangles:

$$\lambda = \int_0^{T_s} v_L(t) dt = (V_g - V)(DT_s) + (-V)(D'T_s)$$

Average voltage is

$$\langle v_L \rangle = \frac{\lambda}{T_s} = D(V_g - V) + D'(-V)$$

Equate to zero and solve for V :

$$0 = DV_g - (D + D')V = DV_g - V \quad \Rightarrow \quad V = DV_g$$

Principe inducteur volt-second balance:

- Nous permet de dériver facilement l'expression DC de la tension de sortie
- Le même résultat, sans utiliser l'argument de transformé de Fourier pour la composante DC
- C'est un principe général pour tous les types de convertisseurs

Principe “capacitor-charge balance”: convertisseur “buck”

Capacitor defining relation:

$$i_c(t) = C \frac{dv_c(t)}{dt}$$

Integrate over one complete switching period:

$$v_c(T_s) - v_c(0) = \frac{1}{C} \int_0^{T_s} i_c(t) dt$$

In periodic steady state, the net change in capacitor voltage is zero:

$$0 = \frac{1}{T_s} \int_0^{T_s} i_c(t) dt = \langle i_c \rangle$$

Hence, the total area (or charge) under the capacitor current waveform is zero whenever the converter operates in steady state. The average capacitor current is then zero.


Intuitive result:

- If a dc current is applied to a capacitor:
then the capacitor will charge continually and its voltage will increase without bound
- if a dc voltage is applied to an inductor:
then the flux will increase continually and the inductor current will increase without bound


Principle of capacitor charge balance: steady-state currents in a switching converter

Exercise: convertisseur boost

*Boost converter
with ideal switch*

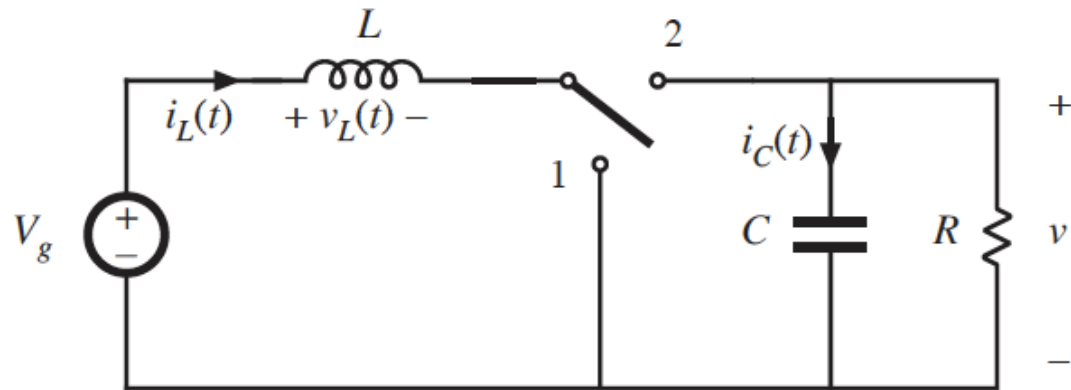

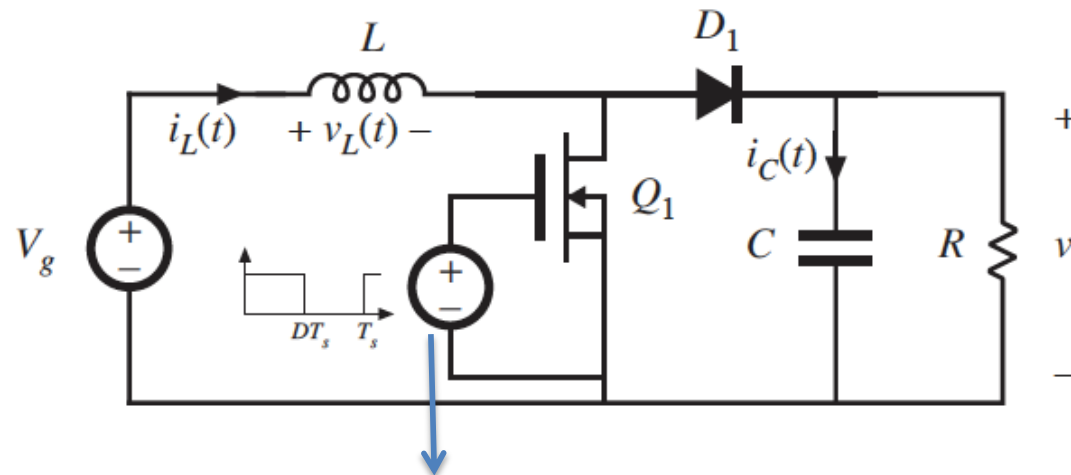*Realization using
power MOSFET
and diode*




Gate driver:

Position1: driver turns on the MOSFET

Position2: driver turns off the MOSFET

Exercise: convertisseur boost

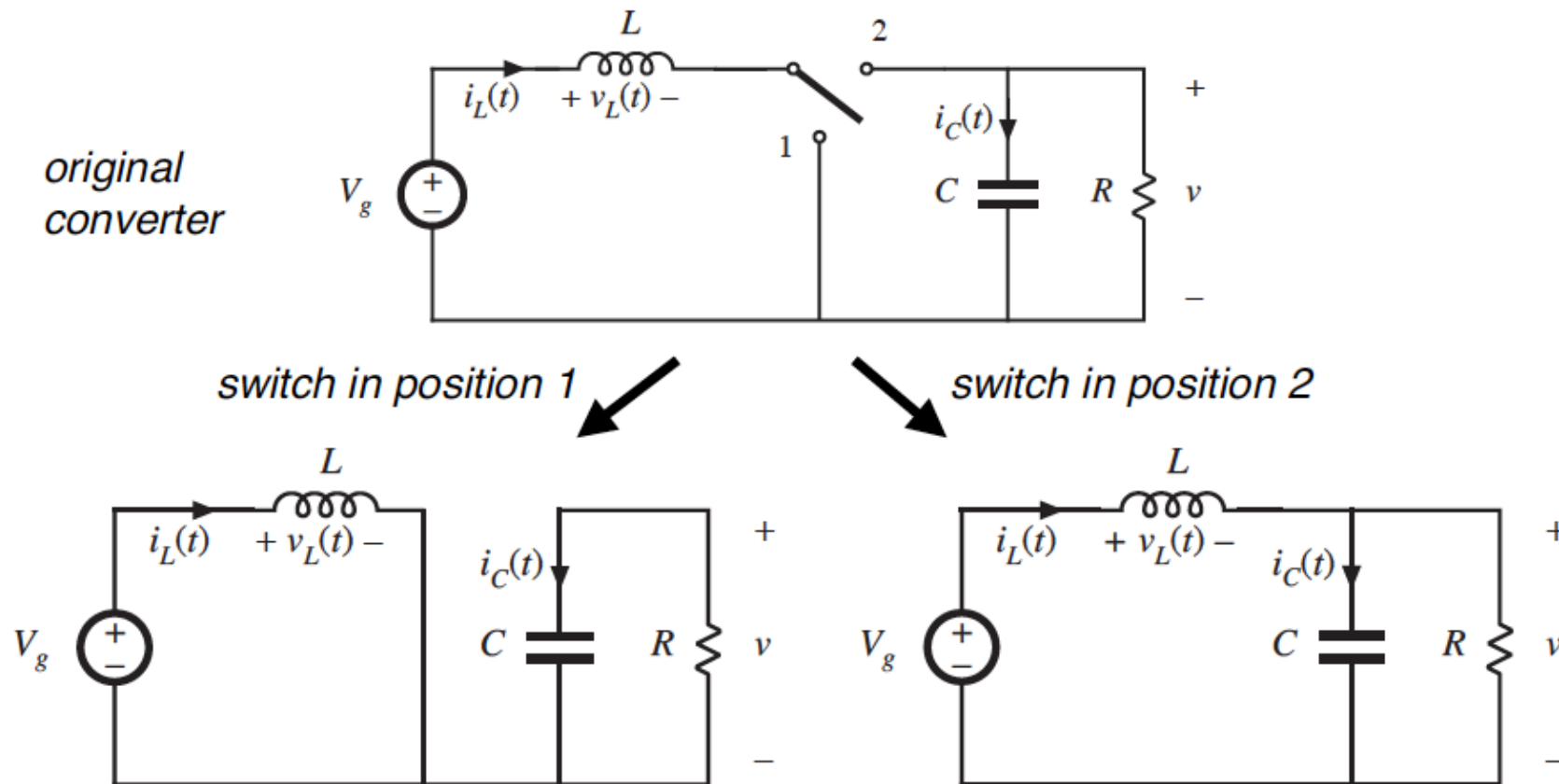

Ecrivez l'orientation des tensions et courants avant de commencer la résolution

Exercise: convertisseur boost

Position 1

Inductor voltage and capacitor current


$$v_L = V_g$$

$$i_C = -v / R$$

Small ripple approximation:

$$v_L = V_g$$

$$i_C = -V / R$$

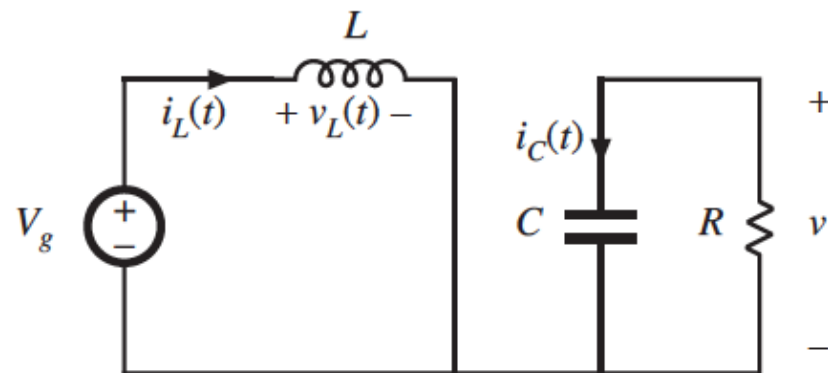

Exercise: convertisseur boost

Position 2

Inductor voltage and capacitor current


$$v_L = V_g - v$$

$$i_C = i_L - v / R$$

Small ripple approximation:


$$v_L = V_g - V$$

$$i_C = I - V / R$$

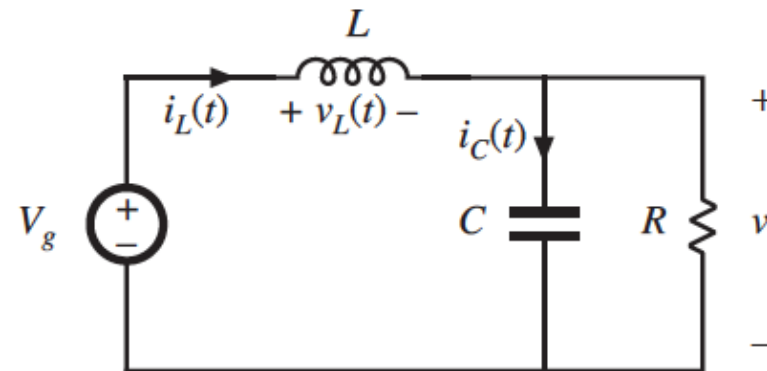

Exercise: convertisseur boost

Tension et courant

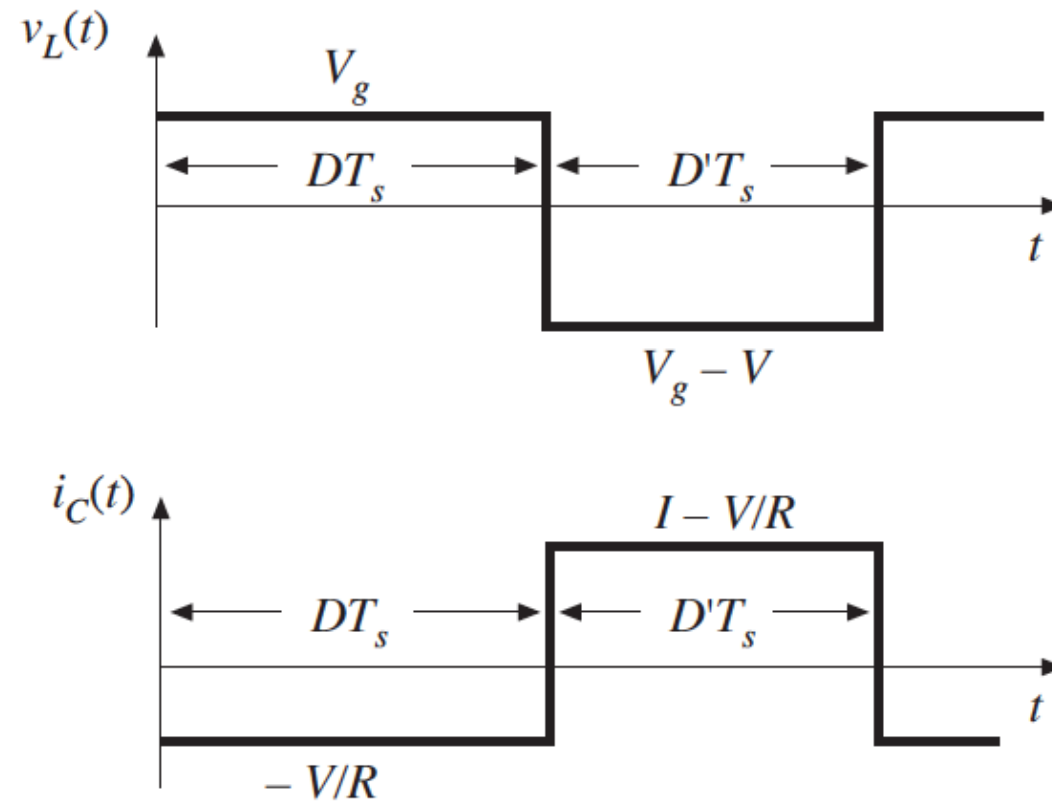


Exercise: convertisseur boost

Calcul de la tension DC de sortie V:

Net volt-seconds applied to inductor over one switching period:
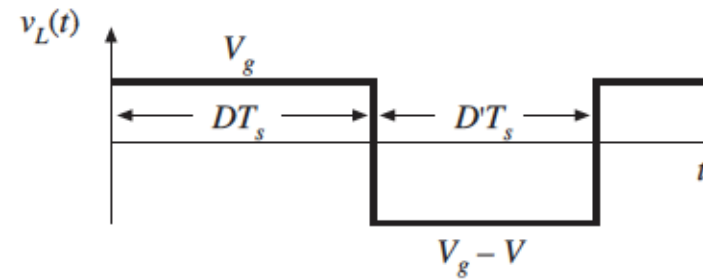
$$\int_0^{T_s} v_L(t) dt = (V_g) DT_s + (V_g - V) D'T_s$$



Equate to zero and collect terms:

$$V_g (D + D') - V D' = 0$$

Solve for V:


$$V = \frac{V_g}{D'}$$

The voltage conversion ratio is therefore

$$M(D) = \frac{V}{V_g} = \frac{1}{D'} = \frac{1}{1-D}$$

Exercise: convertisseur boost

Conversion ratio $M(D)$

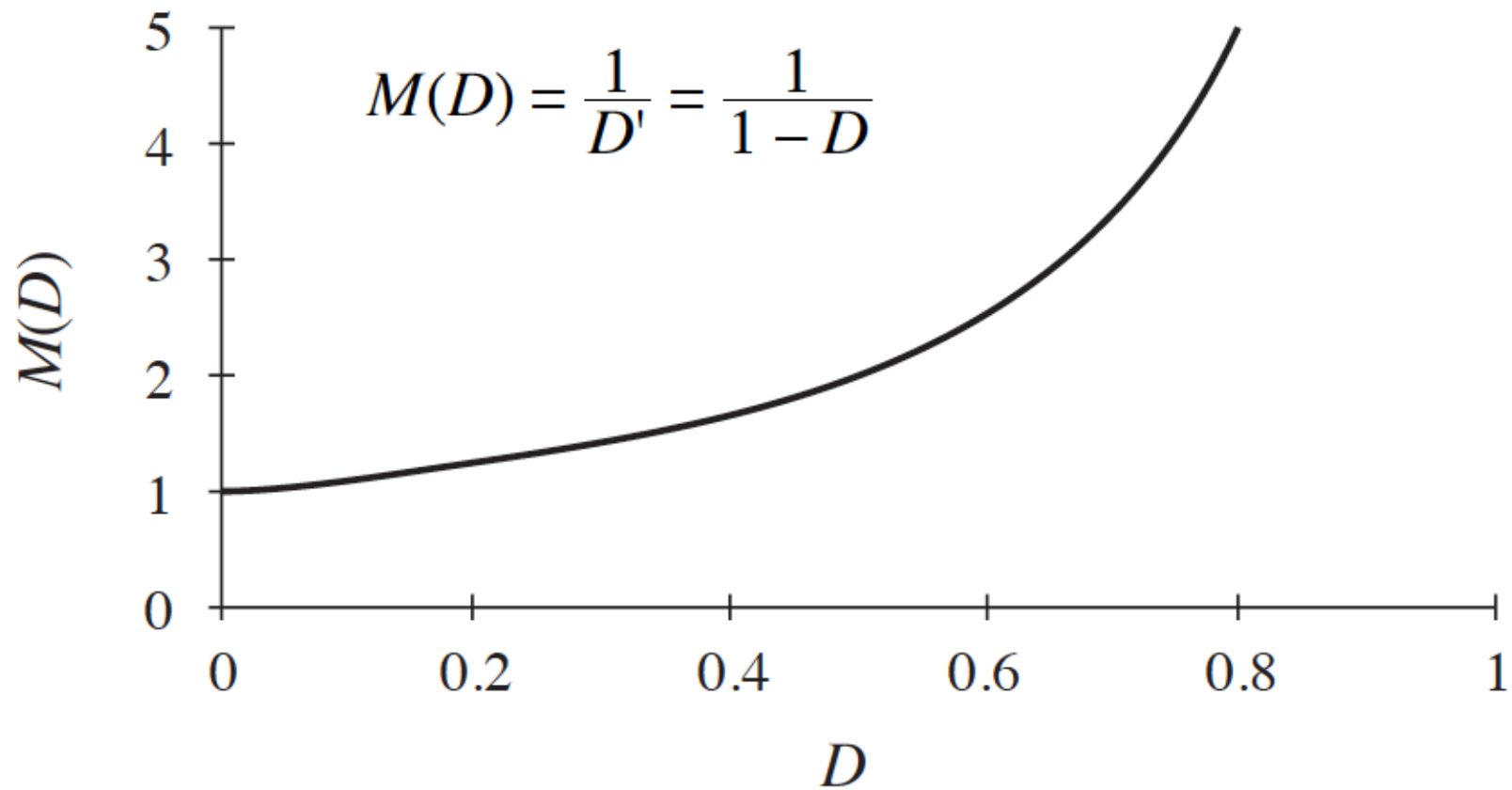

Exercise: convertisseur boost

Calcul du courant DC sur l'inductance L

Capacitor charge balance:

$$\int_0^{T_s} i_C(t) dt = \left(-\frac{V}{R}\right) DT_s + \left(I - \frac{V}{R}\right) D'T_s$$

Collect terms and equate to zero:



$$-\frac{V}{R} (D + D') + I D' = 0$$

Solve for I :

$$I = \frac{V}{D' R}$$

Eliminate V to express in terms of V_g :

$$I = \frac{V_g}{D'^2 R}$$

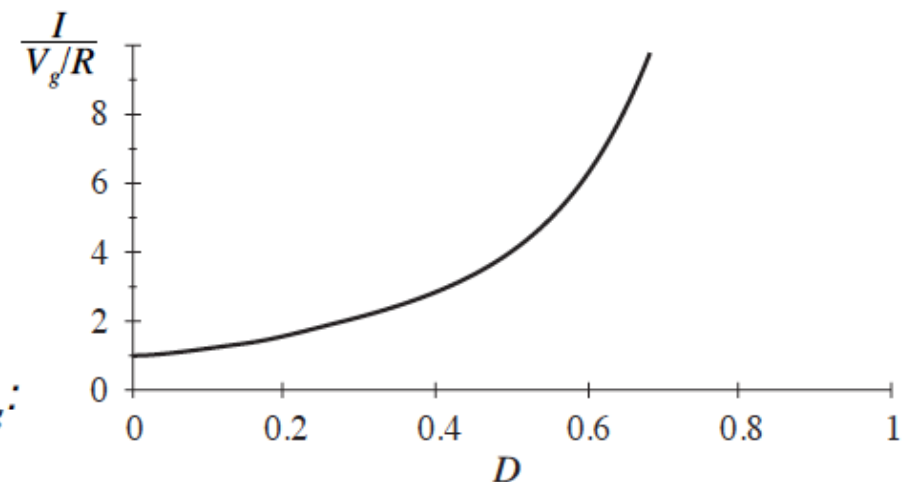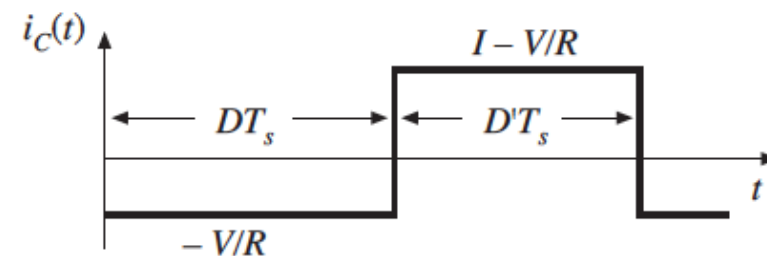

Exercise: convertisseur boost


Calcul du courant “ripple” de l'inducteur

Inductor current slope during subinterval 1:

$$\frac{di_L(t)}{dt} = \frac{v_L(t)}{L} = \frac{V_g}{L}$$

Inductor current slope during subinterval 2:
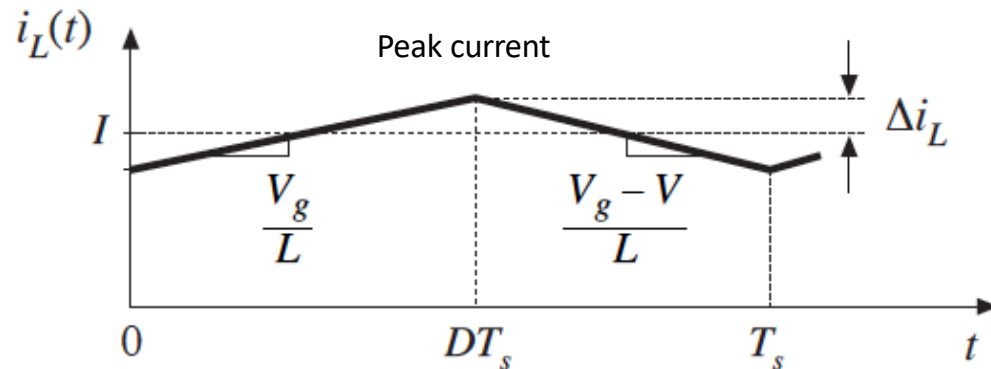
$$\frac{di_L(t)}{dt} = \frac{v_L(t)}{L} = \frac{V_g - V}{L}$$



Change in inductor current during subinterval 1 is (slope) (length of subinterval):

$$2\Delta i_L = \frac{V_g}{L} DT_s$$

Solve for peak ripple:

$$\Delta i_L = \frac{V_g}{2L} DT_s$$

- Choose L such that desired ripple magnitude is obtained

Exercise: convertisseur boost


Calcul de la tension “ripple” du condensateur

Capacitor voltage slope during subinterval 1:

$$\frac{dv_c(t)}{dt} = \frac{i_c(t)}{C} = \frac{-V}{RC}$$

Capacitor voltage slope during subinterval 2:
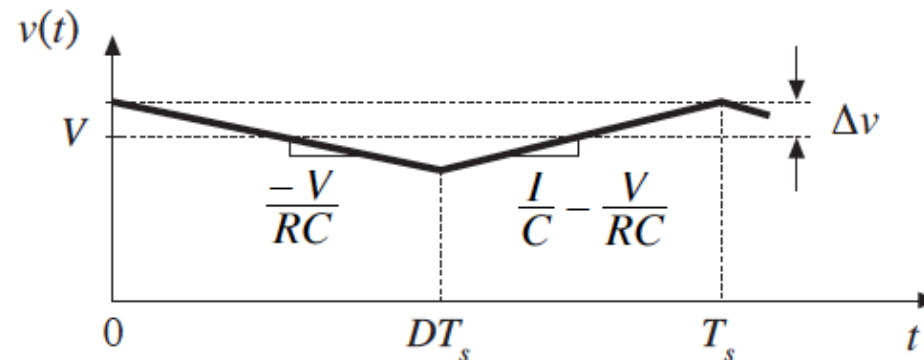
$$\frac{dv_c(t)}{dt} = \frac{i_c(t)}{C} = \frac{I}{C} - \frac{V}{RC}$$



Change in capacitor voltage during subinterval 1 is *(slope) (length of subinterval)*:

$$-2\Delta v = \frac{-V}{RC} DT_s$$

Solve for peak ripple:

$$\Delta v = \frac{V}{2RC} DT_s$$

- Choose C such that desired voltage ripple magnitude is obtained
- In practice, capacitor *equivalent series resistance* (esr) leads to increased voltage ripple