



2024-2025  
Fall Semester

# Course of Power System Analysis **Initial Transient of the Short-Circuit Current**

**Prof. Mario Paolone**

Distributed Electrical Systems Laboratory  
École Polytechnique Fédérale de Lausanne (Switzerland)

# Outline

Initial transient of the short-circuit current


Switching and protection devices for  
electrical networks

# Initial transient of the short-circuit current

Hypothesis: we assume the **generators to be distant from the short circuit location and without any influence associated to their time-varying behaviour after a short circuit** → the Thévenin equivalent electrical parameters are **constant**. The equivalent circuit can be modelled as shown below.

The differential equation driving this circuit is:
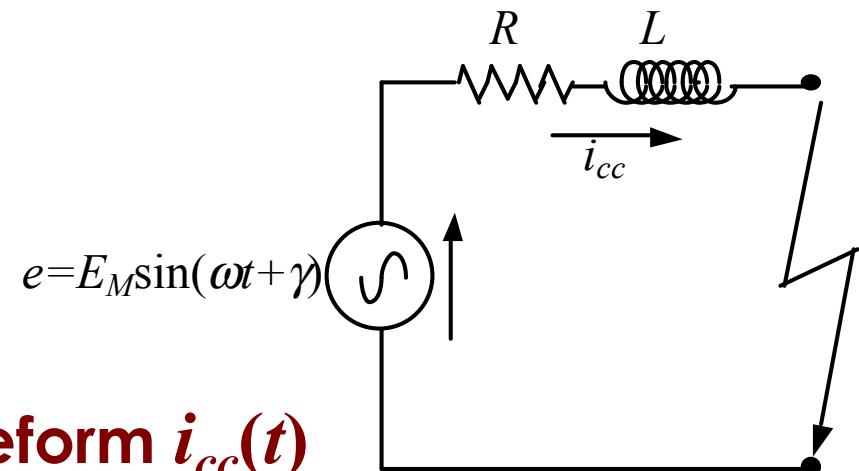
$$E_M \sin(\omega t + \gamma) = R i_{cc}(t) + L \frac{di_{cc}(t)}{dt}$$



**Objective: determine the waveform  $i_{cc}(t)$**

# Initial transient of the short-circuit current

The **homogeneous equation** associated with the previous equation is:

$$Ri_{cc}(t) + L \frac{di_{cc}(t)}{dt} = 0$$

The solution is:

$$i_0(t) = K_1 e^{-\frac{R}{L}t} = K_1 i_1(t)$$

(where  $K_1$  is a constant)

A **particular integral** of the differential equation driven by the DC transient, in the case of **sinusoidal excitation**, is given by:

$$i_p(t) = K(t) e^{-\frac{R}{L}t} = K(t) i_1(t)$$

# Initial transient of the short-circuit current

The value of  $K(t)$ , capable of providing a solution to the original differential equation, can be used to **determine a particular integral**

$$E_M \sin(\omega t + \gamma) = RK(t)i_1(t) + L \frac{dK(t)}{dt} i_1(t) + LK(t) \frac{di_1(t)}{dt}$$

$$E_M \sin(\omega t + \gamma) = K(t) \left( Ri_1(t) + L \frac{di_1(t)}{dt} \right) + L \frac{dK(t)}{dt} i_1(t)$$

as long as  $i_1$  is a **solution of the associated homogeneous equation**, the first term of the second expression is equal to zero, therefore:

$$E_M \sin(\omega t + \gamma) = L \frac{dK(t)}{dt} i_1(t)$$

$$K(t) = \frac{E_M}{L} \int e^{\frac{R}{L}t} \sin(\omega t + \gamma) dt$$

# Initial transient of the short-circuit current

If we integrate the previous equation by parts, we obtain

$$\begin{aligned}
 K(t) &= \frac{E_M}{\omega L} e^{-\frac{R}{\omega L}t} \frac{R\omega L}{R^2 + \omega^2 L^2} e^{\frac{R}{\omega L}(t+\gamma)} \left[ \sin(\omega t + \gamma) - \frac{\omega L}{R} \cos(\omega t + \gamma) \right] = \\
 &= \frac{E_M R}{R^2 + \omega^2 L^2} e^{\frac{R}{\omega L}t} \left[ \sin(\omega t + \gamma) - \frac{\omega L}{R} \cos(\omega t + \gamma) \right]
 \end{aligned}$$

The following parameters are defined:

$$Z_{cc} = \sqrt{R^2 + \omega^2 L^2}, \quad \operatorname{tg} \varphi_{cc} = \frac{\omega L}{R}, \quad \cos \varphi_{cc} = \frac{R}{Z_{cc}}$$

# Initial transient of the short-circuit current

We obtain:

$$\begin{aligned}
 K(t) &= \frac{E_M}{Z_{cc}} \cos \varphi_{cc} e^{\frac{R}{L}t} \left[ \sin(\omega t + \gamma) - \frac{\sin \varphi_{cc}}{\cos \varphi_{cc}} \cos(\omega t + \gamma) \right] = \\
 &= \frac{E_M}{Z_{cc}} e^{\frac{R}{L}t} \left[ \sin(\omega t + \gamma) \cos \varphi_{cc} - \cos(\omega t + \gamma) \sin \varphi_{cc} \right] = \\
 &= \frac{E_M}{Z_{cc}} e^{\frac{R}{L}t} \sin(\omega t + \gamma - \varphi_{cc})
 \end{aligned}$$

Therefore, the **particular integral** is:

$$i_p(t) = K(t) i_1(t) = \frac{E_M}{Z_{cc}} e^{\frac{R}{L}t} e^{-\frac{R}{L}t} \sin(\omega t + \gamma - \varphi_{cc})$$

# Initial transient of the short-circuit current

The solution becomes:

$$i_{cc}(t) = i_0(t) + i_p(t) = K_1 e^{-\frac{R}{L}t} + \frac{E_M}{Z_{cc}} \sin(\omega t + \gamma - \varphi_{cc})$$

If we assume that  $t=0 \rightarrow i_{cc}(0)=0$  we can determine the value of the constant  $K_1$

$$0 = K_1 + \frac{E_M}{Z_{cc}} \sin(\gamma - \varphi_{cc})$$

Therefore, by substitution:

$$i_{cc}(t) = -\frac{E_M}{Z_{cc}} e^{-\frac{R}{L}t} \sin(\gamma - \varphi_{cc}) + \frac{E_M}{Z_{cc}} \sin(\omega t + \gamma - \varphi_{cc})$$

# Initial transient of the short-circuit current

9

$$i_{cc}(t) = -\frac{E_M}{Z_{cc}} e^{-\frac{R}{L}t} \sin(\gamma - \varphi_{cc}) + \frac{E_M}{Z_{cc}} \sin(\omega t + \gamma - \varphi_{cc})$$


Observation: the short-circuit current results from **superposition** of a **sinusoidal (permanent) component** and an **aperiodic (transient) component**.

The term  $E_M/Z_{cc}$  is the **maximum value (amplitude)** of the **permanent component** of the short-circuit current, indicated by  $I_M$ .
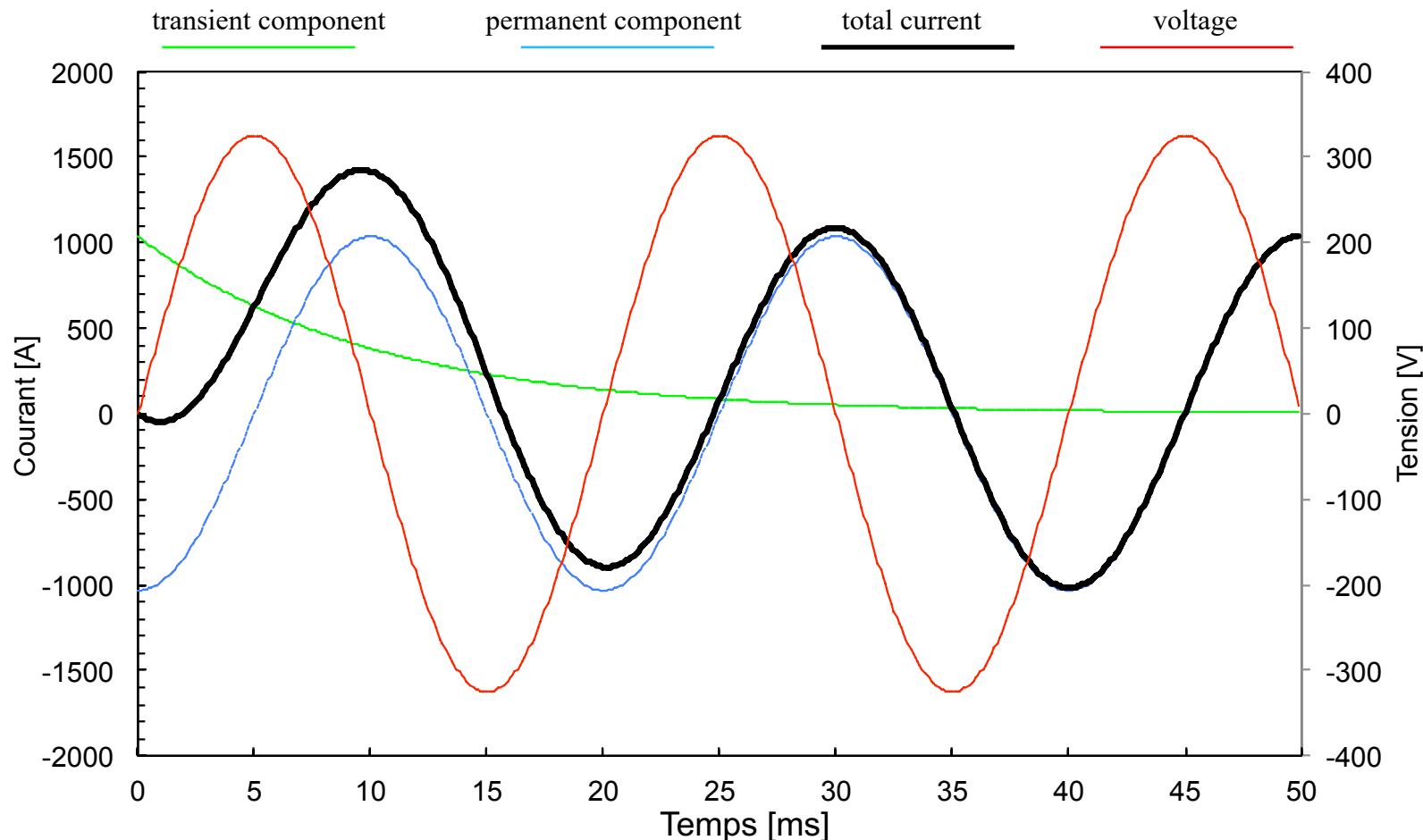
# Initial transient of the short-circuit current

10

$$i_{cc}(t) = -\frac{E_M}{Z_{cc}} e^{-\frac{R}{L}t} \sin(\gamma - \varphi_{cc}) + \frac{E_M}{Z_{cc}} \sin(\omega t + \gamma - \varphi_{cc})$$



# Initial transient of the short-circuit current

## Observations:

1. The maximum value of the short-circuit current (peak  $I_P$ ) **depends on the time at which the short circuit is established**. If  $\gamma = \varphi_{cc}$ , the transient component is zero, if  $\gamma < \varphi_{cc}$  the transient component is **positive**, if  $\gamma > \varphi_{cc}$  the transient component is **negative**.
2. The duration of the transient and peak current  $I_P$  depend on the  $R$  and  $L$  parameters of the circuit, i.e.,  $\cos\varphi_{cc}$ . The exponential term has a time constant  $T_0 = L / R = \tan\varphi_{cc} / \omega$ . Therefore, if  $R=0$  ( $\cos\varphi_{cc}=0$ )  $T_0 \rightarrow \infty$  and  $I_P=2I_M$ . **Thus, the more inductive the circuit, the greater the value of the aperiodic component and the greater the peak short-circuit current.**

# Initial transient of the short-circuit current

12

To consider the aperiodic component of the short-circuit current, we introduce the factor  $\chi$  which gives the **ratio between the peak value and the maximum value** of the symmetrical component of the short-circuit current:

$$I_P = \sqrt{2}\chi I_{cc} = \chi I_M$$

where  $I_{cc}$  is the **RMS value of the symmetrical component** of the short-circuit current.

**Problem: compute the parameter  $\chi$**

# Initial transient of the short-circuit current


13

To determine the value of the parameter  $\chi$  we should **maximize the value of the current**  $i_{cc}(t)$  as a function of the parameter  $\gamma$  (i.e., the instant at which the short-circuit begins). **For each value of the phase  $\varphi_{cc}$  there is only one value  $\gamma$  for which the peak value is reached.**

# Initial transient of the short-circuit current
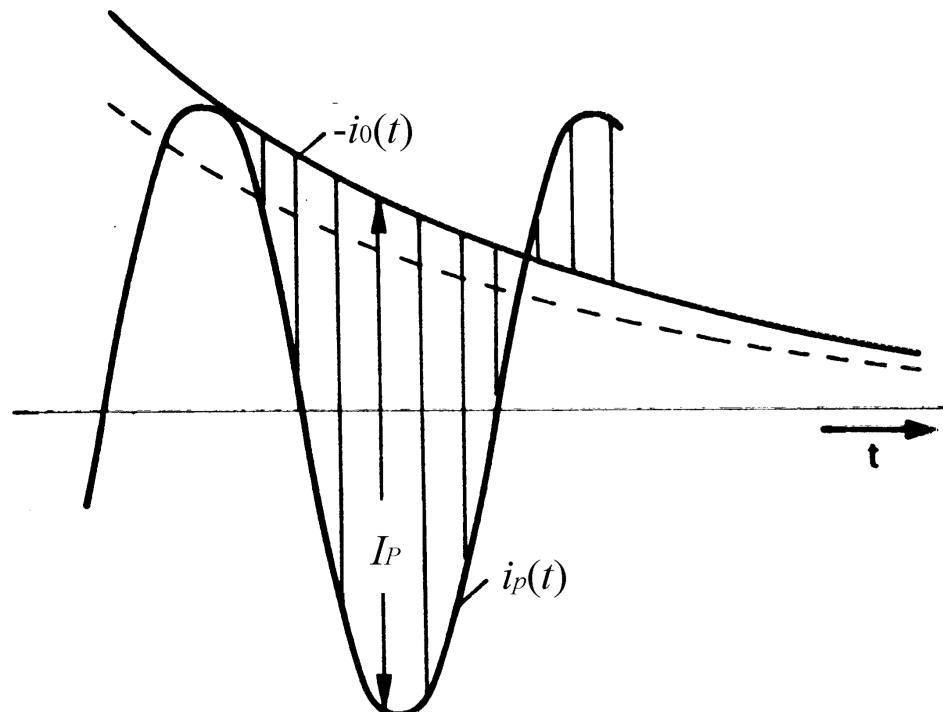
## Considerations:

- for  $t = 0$ , in order to meet the condition  $i(0)=0$ , it must be true that  $i_0(0)+i_P(0)=0$  (initial values of the aperiodic and permanent components equal and opposite);
- **the maximum amplitude of  $i(t)$ , equal to the sum of  $i_P(t)$  and  $-i_0(t)$ , is attained if the waveform  $-i_0(t)$  is tangent to  $i_P(t)$  for  $t=0$ .**




# Initial transient of the short-circuit current

Therefore:

$$-\left[ \frac{di_0(t)}{dt} \right]_{t=0} = \left[ \frac{di_p(t)}{dt} \right]_{t=0} \Rightarrow$$
$$-\frac{1}{T_0} \sin(\gamma - \varphi_{cc}) = \omega \cos(\gamma - \varphi_{cc})$$

If the relation  $\omega T_0 = \tan \varphi_{cc}$  is satisfied:
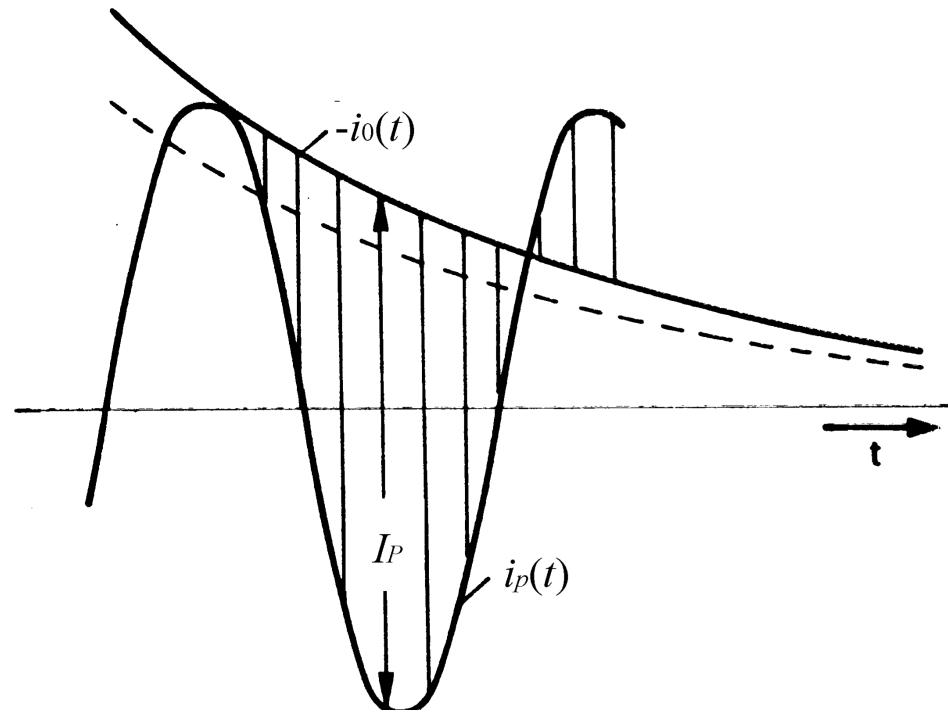
$$\tan(\gamma - \varphi_{cc}) = -\tan \varphi_{cc}$$



This equation is verified for  $\gamma=0$  and also  $\gamma=\pi \rightarrow$  **the largest value of  $I_p$**  is reached if the short-circuit occurs **when the voltage crosses zero, for any value of  $\varphi_{cc}$** .

# Initial transient of the short-circuit current

16

The time  $\hat{t}$  at which the value  $I_P$  is reached occurs if  $\frac{di_{cc}(t)}{dt} = 0$   
i.e., for  $\gamma = 0$  or for  $\gamma = \pi$  in the derivation of the equation:


$$\frac{di_{cc}(t)}{dt} = \frac{d}{dt} \left[ -\frac{E_M}{Z_{cc}} e^{-\frac{R}{L}t} \sin(\gamma - \phi_{cc}) + \frac{E_M}{Z_{cc}} \sin(\omega t + \gamma - \phi_{cc}) \right] = 0$$

$$\cos(\omega \hat{t} - \phi_{cc}) - e^{-\frac{R}{L}\hat{t}} \cos \phi_{cc} = 0$$

The value  $\hat{t}$  enables calculation of the values  $I_P$  and  $\chi$ , if substituted in the equation for  $i_{cc}(t)$ .
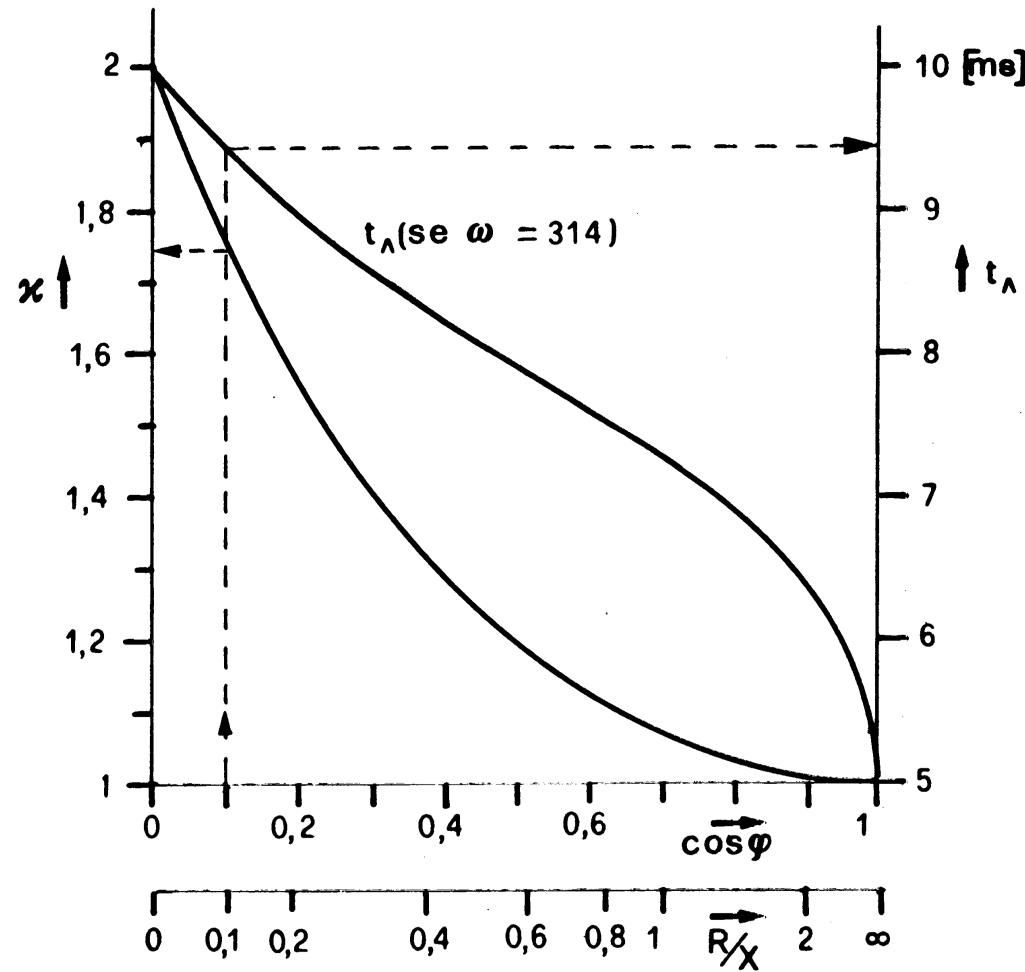
# Initial transient of the short-circuit current

The figure shows the relation between  $\hat{t}$  and  $\chi$  as a function of the ratio  $R/X$  or  $\cos\varphi_{cc}$



# Initial transient of the short-circuit current

18

Summary of the descriptive parameters of the initial transient of the short-circuit current:

- $I_M = E_M / Z_{cc}$  maximum value of the permanent component of the short-circuit current;
- $T_0 = L / R$  time constant of the transient component of the short-circuit current;
- $I_{cc}$  RMS value of the permanent component of the short-circuit current;
- $I_P$  peak value of the short-circuit current;
- $\cos\varphi_{cc}$  power factor in short-circuit conditions
- $\chi$  relation between  $I_P$  and  $\sqrt{2}I_{cc}$

# Initial transient of the short-circuit current

19

Observation: knowing the value of the parameter  $\chi$  (and therefore the value  $I_P$ ) enables evaluation of **thermal stresses directly after the start of the short-circuit**.

During this period, the aperiodic component  $i_0(t)$  is not damped and therefore its contribution to Joule's specific energy is considerable, in addition to the contribution of the periodic component. Network heating upstream of the short circuit is highly dependent on the specific energy. **It is possible to determine an RMS current value equivalent in terms of Joule integral to  $i_{cc}(t)$ .**


# Initial transient of the short-circuit current

20

This value is given by:

$$I_{eff} = \frac{I_M}{\sqrt{2}} \sqrt{m+1}$$

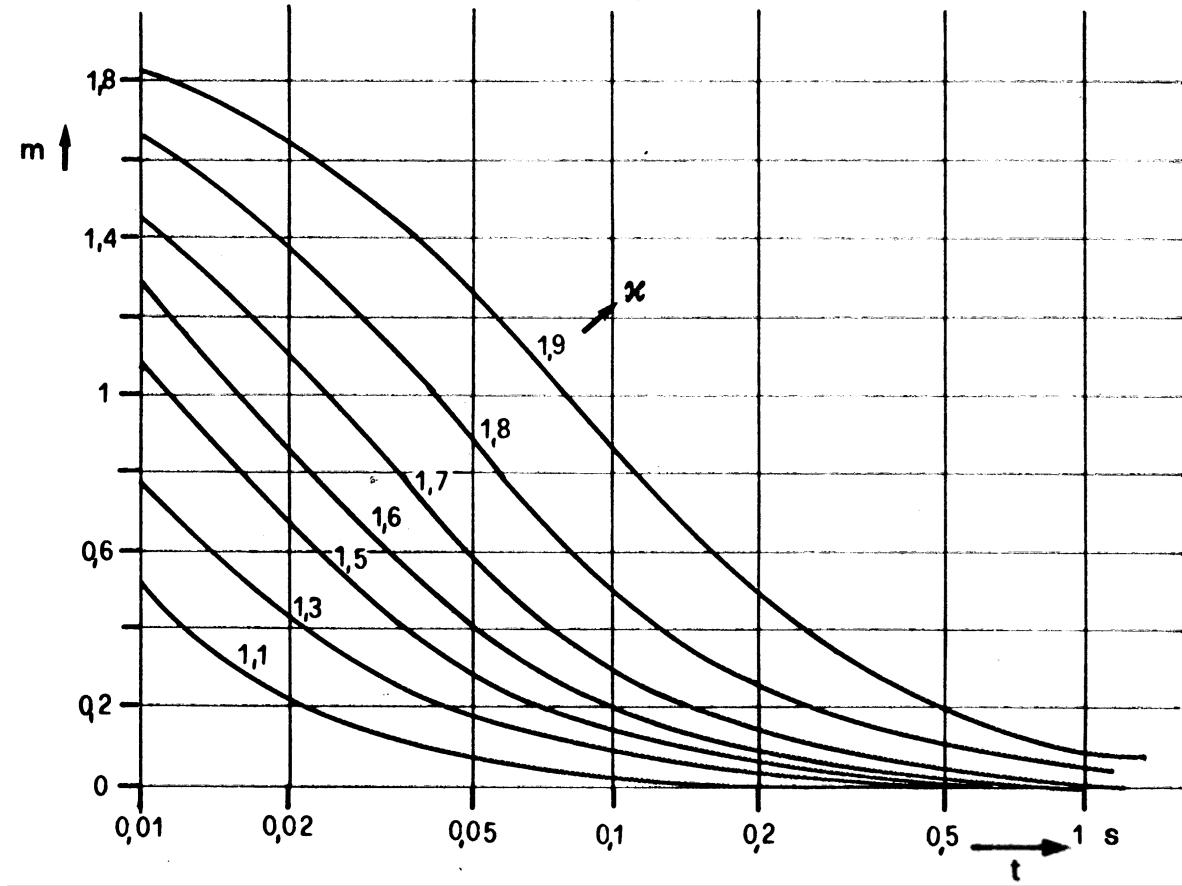the coefficient  $m$  depends on  $i_0(t)$ , and therefore on parameter  $\chi$  and the duration of the short-circuit. The figure shows the value of  $m$  as a function of these two quantities.



# Outline

Initial transient of the short-circuit current

Switching and protection devices for  
electrical networks

# Switching and protection devices for electrical networks

22

The nominal characteristics of devices for operation and protection of electrical networks (i.e., circuit breakers) are:

- Rated voltage  $U_r$
- Maximum voltage  $U_m$
- Level of insulation (steady-state voltage  $U_d$  at 50 Hz and impulse voltage  $U_p$ )
- Nominal current  $I_r$
- Nominal acceptable current for short duration  $I_k$
- Nominal duration of short-circuit  $t_k$

# Switching and protection devices for electrical networks

23

The **nominal voltage** is the voltage assigned by the manufacturer, indicated by  $U_r$  in product standards and by  $U_n$  in network standards.

The **maximum voltage** is represented by  $U_m$  and represents the highest voltage value at any point on the network under normal operating conditions.

The maximum voltage is necessary to evaluate the **level of insulation of electrical devices**. The insulation level of an electrical device is linked to the rated voltage, and is assessed using **two reference values**:

- The **steady-state operating voltage** at 50 Hz  $U_d$  applied for 60 s;
- the **impulse voltage**  $U_p$ , for the waveform 1.2/50  $\mu$ s

# Switching and protection devices for electrical networks

24

The **nominal current** for short duration  $I_k$  is the RMS value of the short-circuit current that can flow through the device during the time  $t_k$ .

Common values of  $I_k$  are 8, 10, 12.5, 16, 20, 25 kA.

The value  $t_k$  is commonly equal to **1 second**, but it notably must be **larger than the time necessary for the protection to interrupt the short-circuit**.

# Switching and protection devices for electrical networks

25

The additional characteristics for **circuit breakers** in medium-voltage networks are as follows:

- **interruption time**: time needed for the circuit breaker to completely interrupt the short-circuit, given by the sum of the opening time (i.e., the time for the circuit breaker to open the contacts) and the arc extinction time.
- **rated breaking capacity**: the highest power value that the circuit breaker is capable of interrupting under nominal conditions.
- **restoring capacity**: the highest power value under which the circuit breaker is capable of closing when the circuit is re-established.