



2024-2025 Course of Power System Analysis
Fall Semester

Short-Circuit Current Calculation

Prof. Mario Paolone

Distributed Electrical Systems Laboratory
École Polytechnique Fédérale de Lausanne (Switzerland)

Outline

Study of symmetrical components of a symmetrical three-phase system with a generic triplet of impedances to ground

Three-phase short-circuit

Ungrounded two-phase short-circuit

Two-phase short-circuit with connection to ground

Single-phase short-circuit to ground

Study of symmetrical components of a symmetrical three-phase system with a generic triplet of impedances to ground


3

This part describes the approach necessary to study the **behaviour of an electric circuit in the event of a short-circuit (three-phase, two-phase, single-phase, etc.)** at any point in the network. A short-circuit in the network involves the connection of a **generic triplet of impedances to ground** and therefore an **asymmetrical and unbalanced regime**.

Study of symmetrical components of a symmetrical three-phase system with a generic triplet of impedances to ground

Hypotheses:


- electric networks made up of symmetrical elements (i.e., represented by circulant impedance matrices);
- an **asymmetrical set of impedances is connected at a generic point** in the network (see figure);
- at the point where the asymmetrical system of impedances is connected, the triplet of phase voltages across the impedances is $\bar{E}'_a, \bar{E}'_b, \bar{E}'_c$ and the trio of currents through the impedances is $\bar{I}'_a, \bar{I}'_b, \bar{I}'_c$

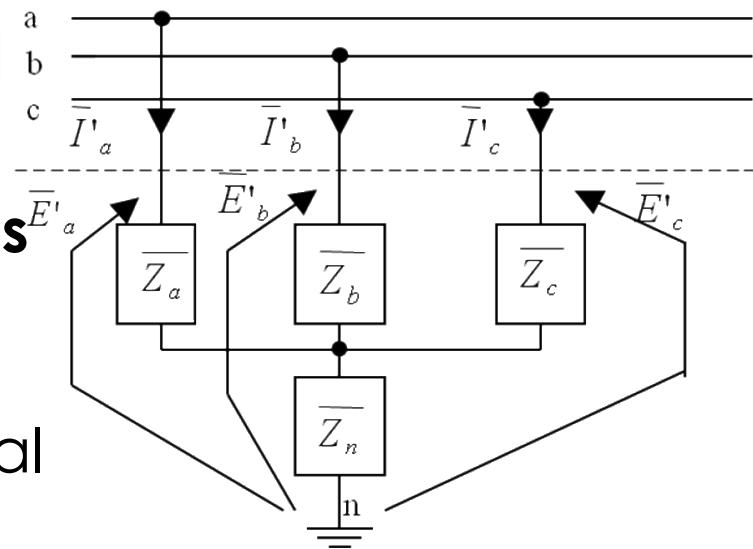

Study of symmetrical components of a symmetrical three-phase system with a generic triplet of impedances to ground

Observation:

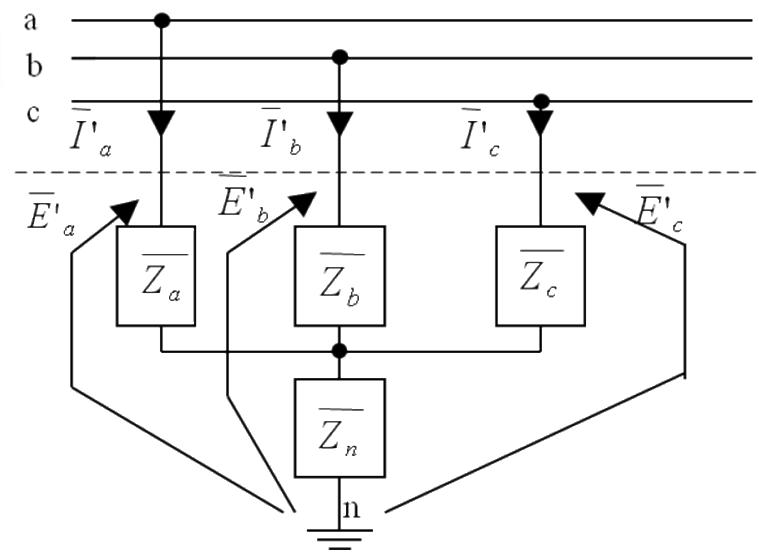We have already shown that **a triplet of generic impedances, in general, cannot be decomposed into three decoupled networks** and therefore the network in the figure must be studied using **symmetrically coupled components**.




Study of symmetrical components of a symmetrical three-phase system with a generic triplet of impedances to ground

Observation:


Simplification \rightarrow connecting the star of impedances shown in the previous figure to a generic network point is **equivalent to inserting a star of voltage sources**

$\bar{E}'_a, \bar{E}'_b, \bar{E}'_c$ (figure a) or a star of **current sources** $\bar{I}'_a, \bar{I}'_b, \bar{I}'_c$ (figure b) or any combination of voltage and current sources (figure c).


a)

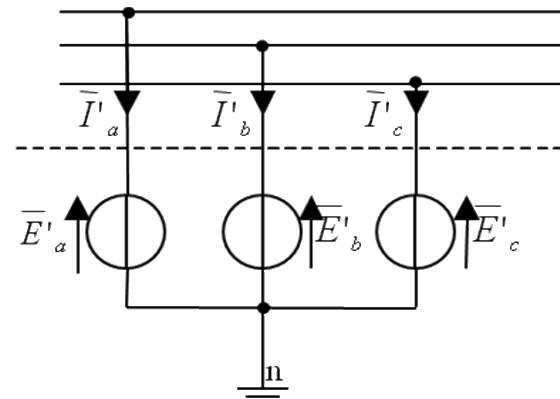

b)

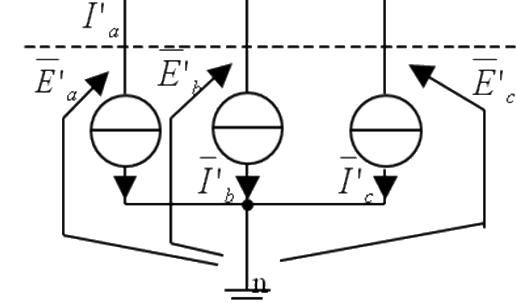

c)


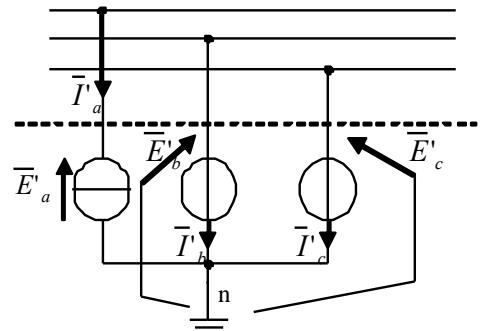


Study of symmetrical components of a symmetrical three-phase system with a generic triplet of impedances to ground

Observation:


Thanks to this assumption, the star of the voltage generators in a) can be decomposed by means of the matrix, i.e., by the relation:
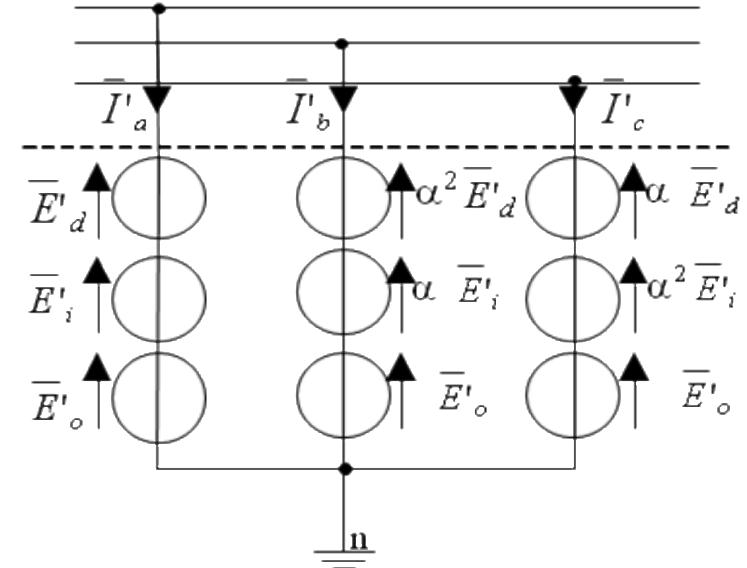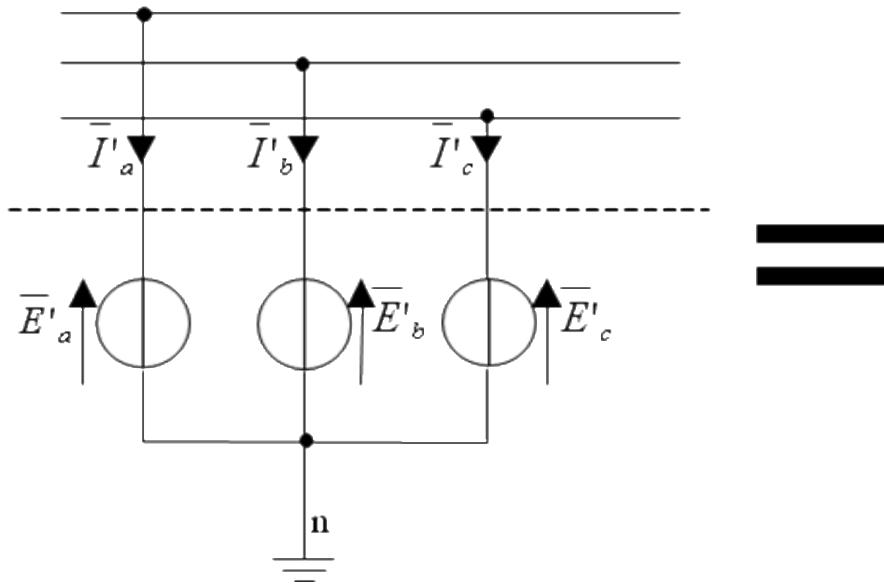
$$\begin{bmatrix} \bar{E}'_a \\ \bar{E}'_b \\ \bar{E}'_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} \bar{E}'_0 \\ \bar{E}'_d \\ \bar{E}'_i \end{bmatrix}$$



Study of symmetrical components of a symmetrical three-phase system with a generic triplet of impedances to ground

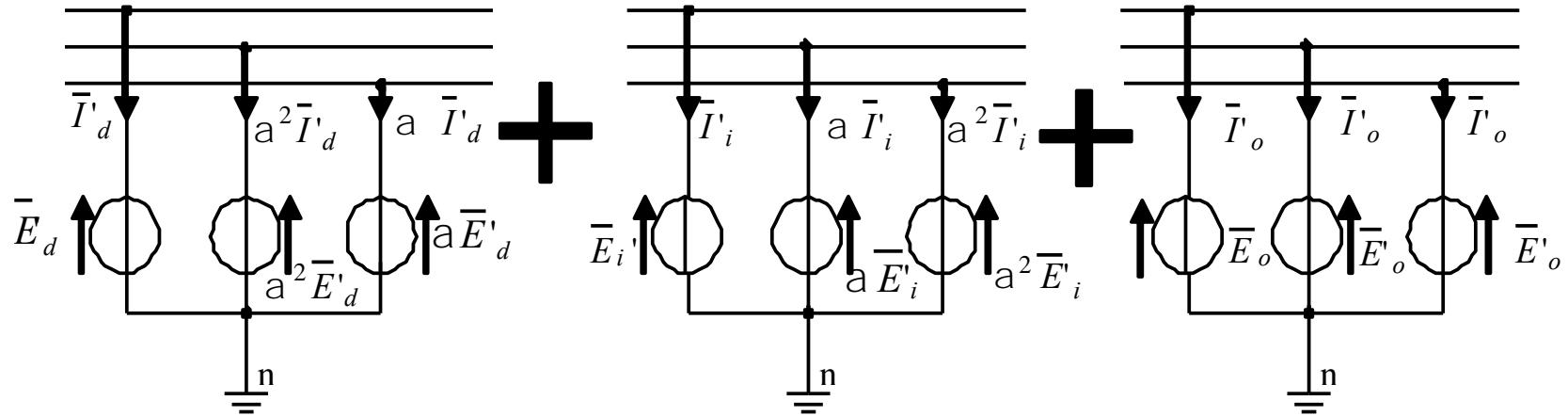
If we apply the **principle of superposition**, the circuit in the previous figure can be decomposed into the symmetrical components shown below. So the initial asymmetrical three-phase network has been decomposed into three symmetrical three-phase networks.



Study of symmetrical components of a symmetrical three-phase system with a generic triplet of impedances to ground

Remarks:


- as long as the starting network is symmetrical, its internal electromotive forces comprise a single sequence, which is the direct sequence;
- The **direct, inverse, and homopolar** currents circulate in the three respective circuits in the figure;
- the three networks in the figure are **symmetrical** and therefore **can be studied as monophasic networks**;
- as soon as the various quantities with symmetrical components are calculated, the currents and voltages of the original system are determined using the inverse transformation.

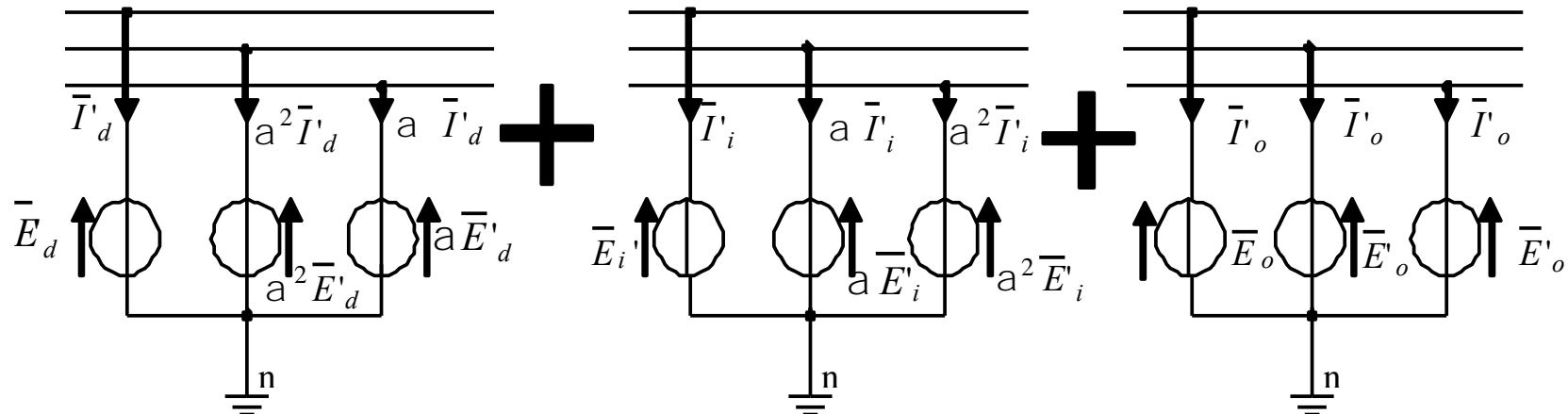


Study of symmetrical components of a symmetrical three-phase system with a generic triplet of impedances to ground

10

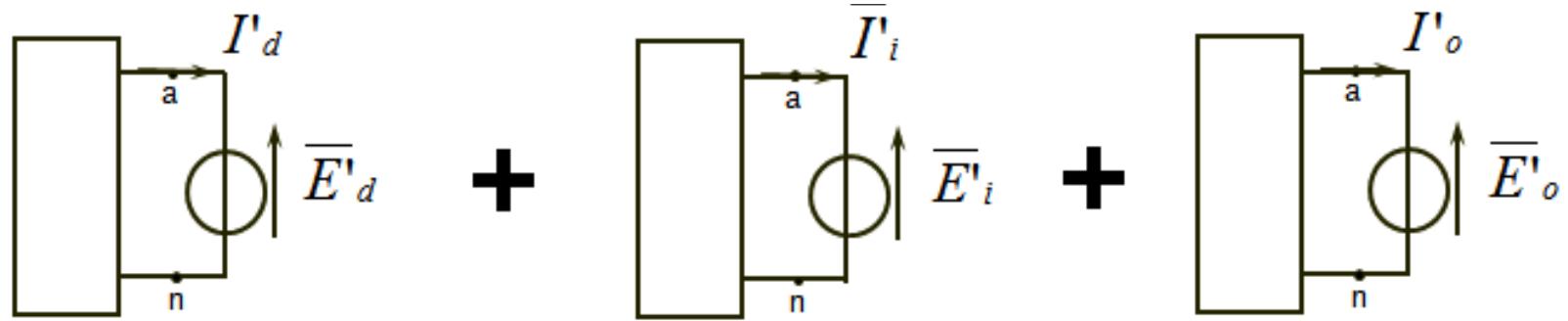Therefore, we can reduce the three-phase networks shown in the previous figure to three single-phase networks.



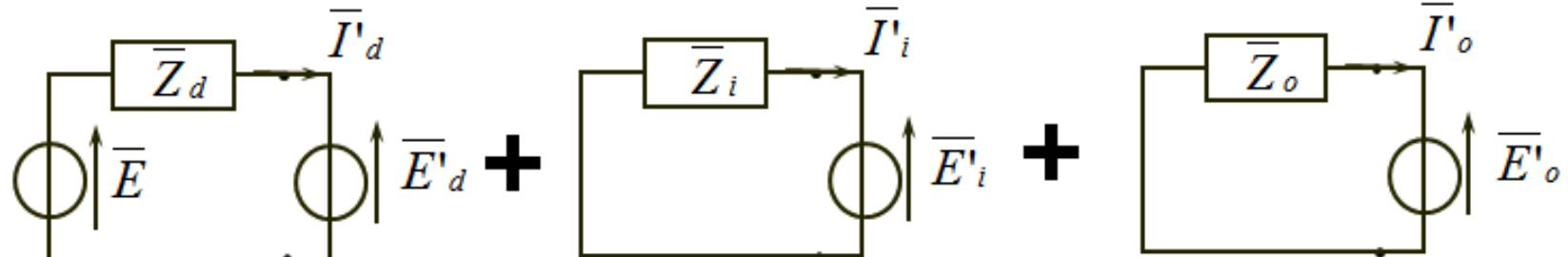
If we use the **Thévenin theorem**, the three networks between points a and n can be decomposed to the following circuits:



Study of symmetrical components of a symmetrical three-phase system with a generic triplet of impedances to ground

In these circuits, the term \bar{E} is the **voltage before insertion of the asymmetrical impedances** (i.e., before the short-circuit) at the considered point in the network. **This voltage only exists in the direct sequence circuit.** $\bar{Z}_d, \bar{Z}_i, \bar{Z}_o$ are the **equivalent impedances of the network for each sequence as seen from the considered point.** The three equivalent impedances of the network can be calculated if the schematic of the network is known. We should then compute the 6 unknowns $\bar{E}'_d, \bar{E}'_i, \bar{E}'_o, \bar{I}'_d, \bar{I}'_i, \bar{I}'_o$ knowing the 4 quantities $\bar{Z}_a, \bar{Z}_b, \bar{Z}_c, \bar{Z}_n$

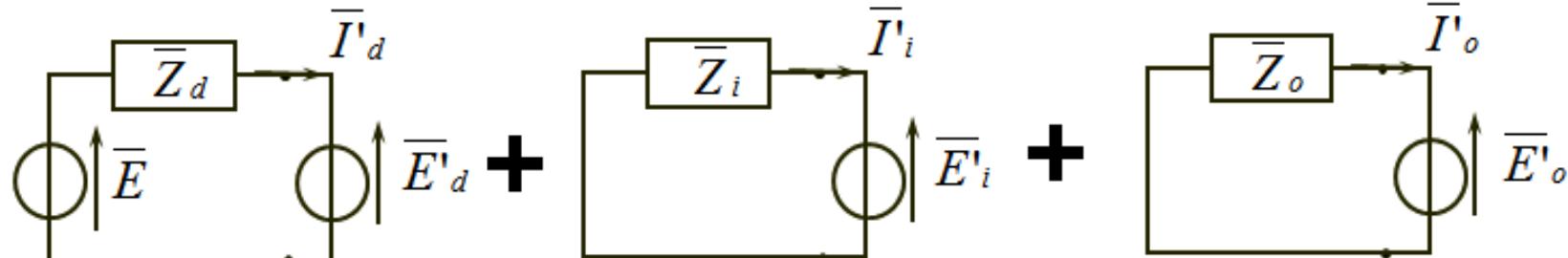As will be shown in the next sections, it is needed to determine three vectors (6 scalars) according to the characteristics of the short-circuit.



Outline

Study of symmetrical components of a symmetrical three-phase system with a generic triplet of impedances to ground

Three-phase short-circuit

Ungrounded two-phase short-circuit



Two-phase short-circuit with connection to ground

Single-phase short-circuit to ground

Three-phase short-circuit



Consider a three-phase short-circuit shown in the figure (a) where, at a **generic point in the network**, a **star impedance with value \bar{Z} is connected to ground** in series with an impedance \bar{Z}_n .

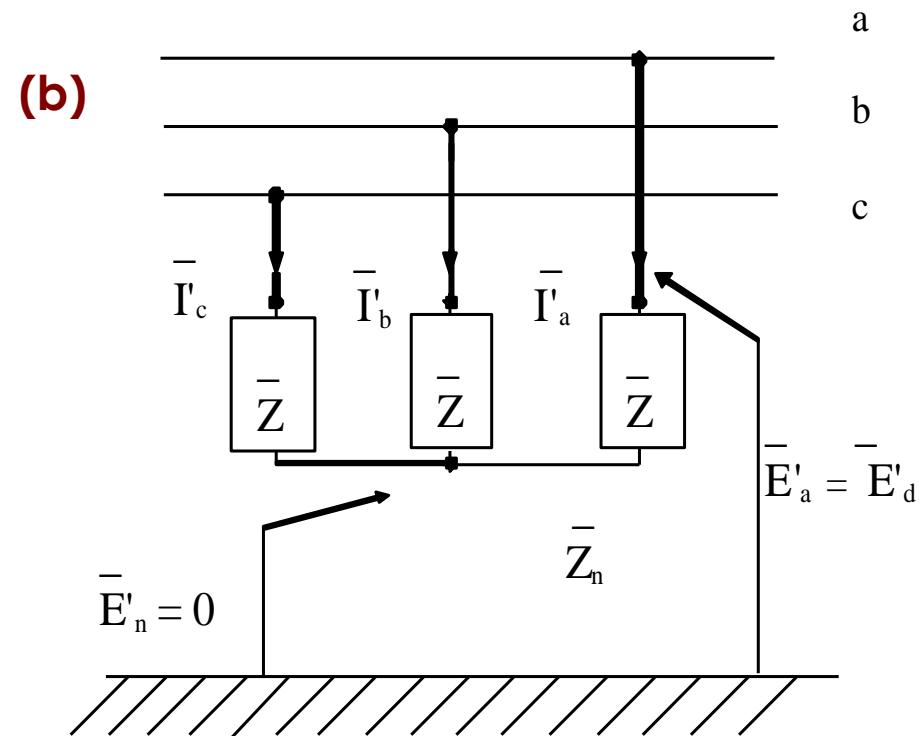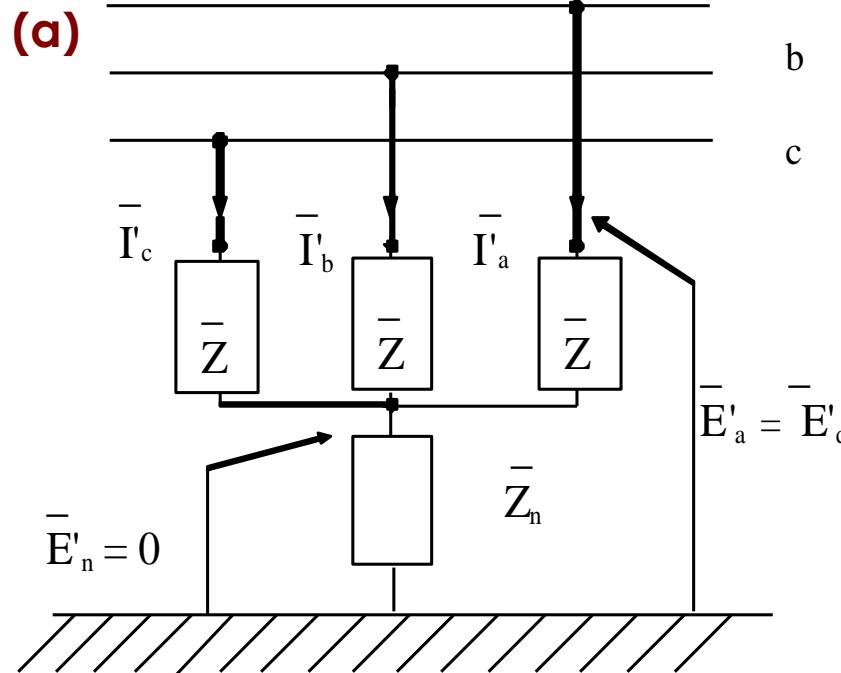The impedance \bar{Z} is the **impedance of the short-circuit**.





Three-phase short-circuit

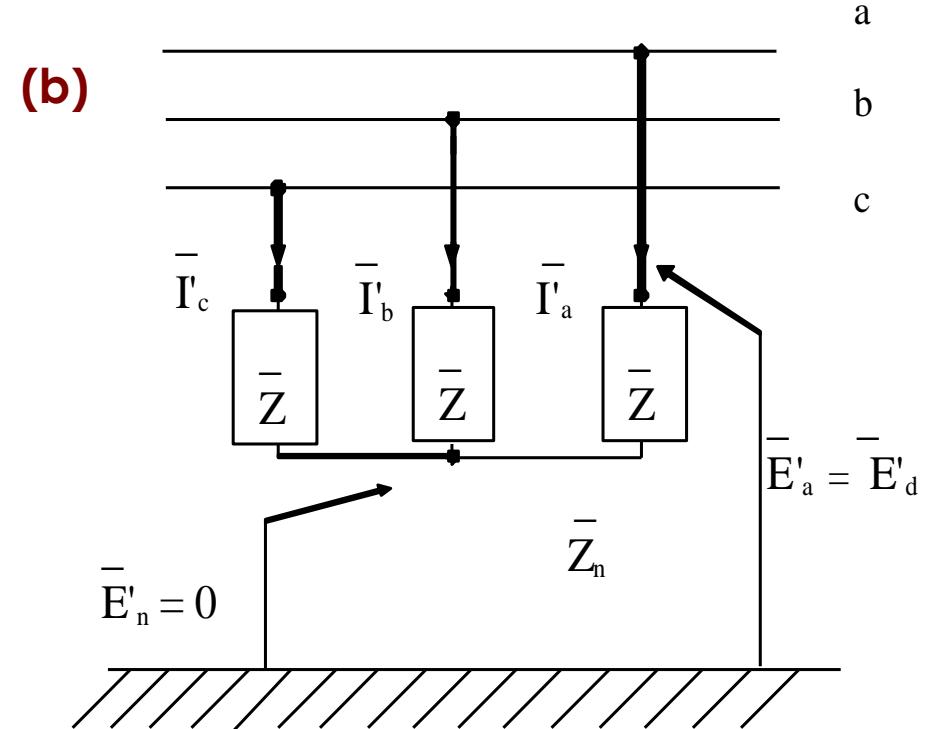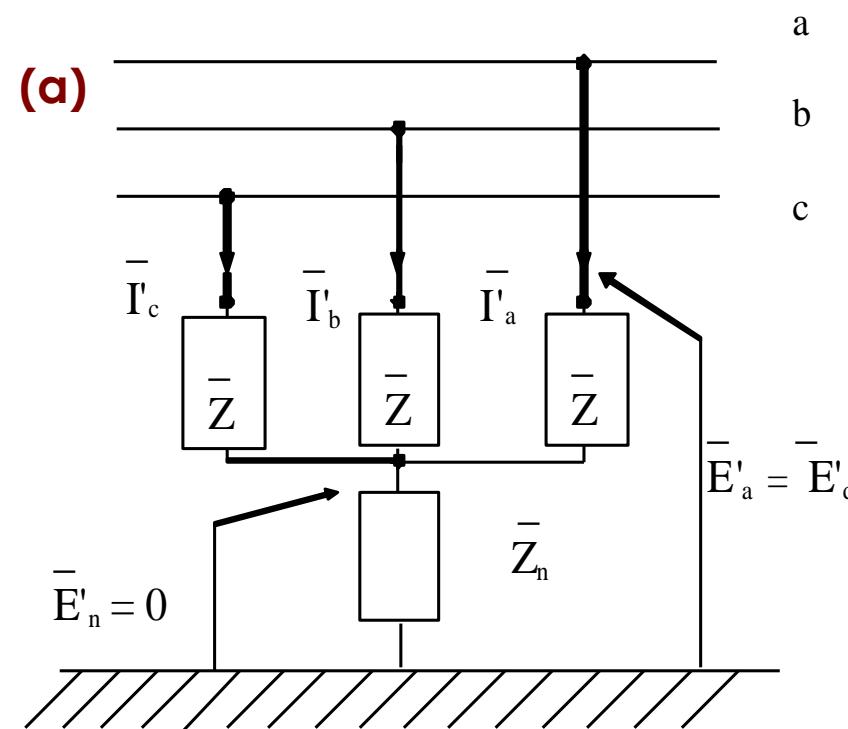Observation: as long as the upstream network is symmetrical, the center of the star of the three impedances \bar{Z} has the same value as the voltage of the star center of the network. Therefore, the impedance \bar{Z}_n can be eliminated.



Three-phase short-circuit

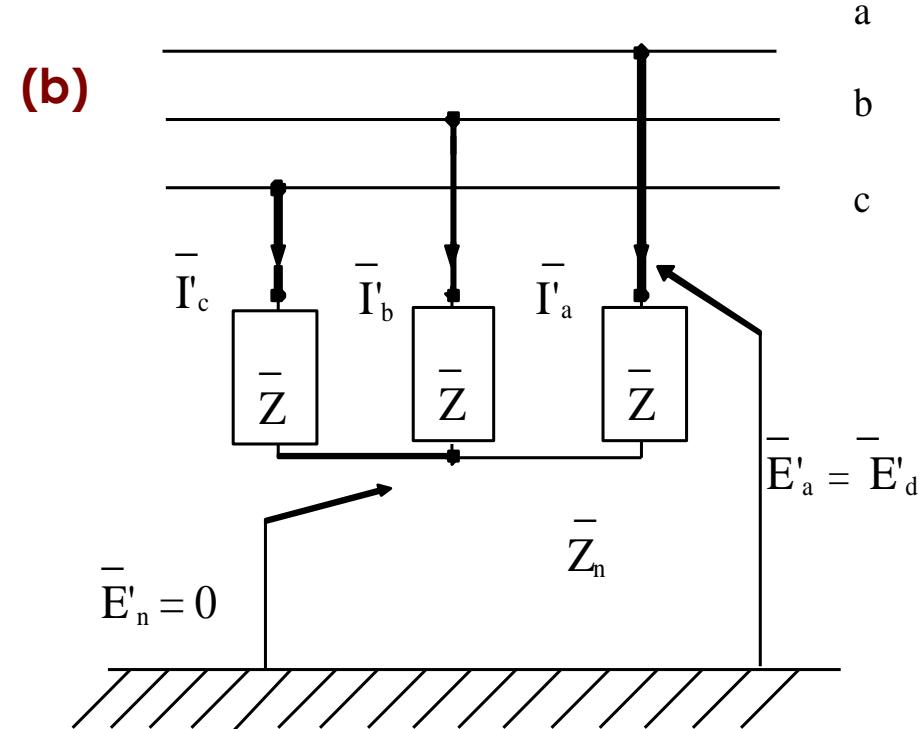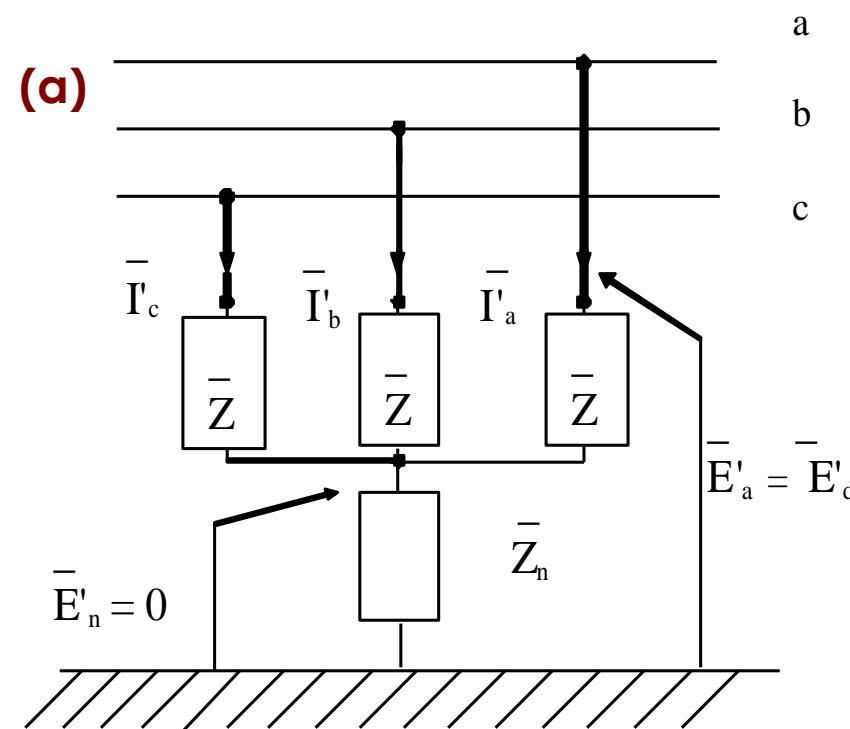Since the considered short-circuit is **symmetrical**, the **triplet of voltages** $\bar{E}_a, \bar{E}_b, \bar{E}_c$ and **triplet of currents** $\bar{I}_a, \bar{I}_b, \bar{I}_c$ at the point of the short-circuit only has **direct sequence components**, and there are no indirect and homopolar sequence components.





Three-phase short-circuit

The current of the short circuit is, therefore:

$$\bar{I}'_a = \bar{I}'_d = \frac{\bar{E}'_d}{\bar{Z}}$$

For the **direct sequence component**:
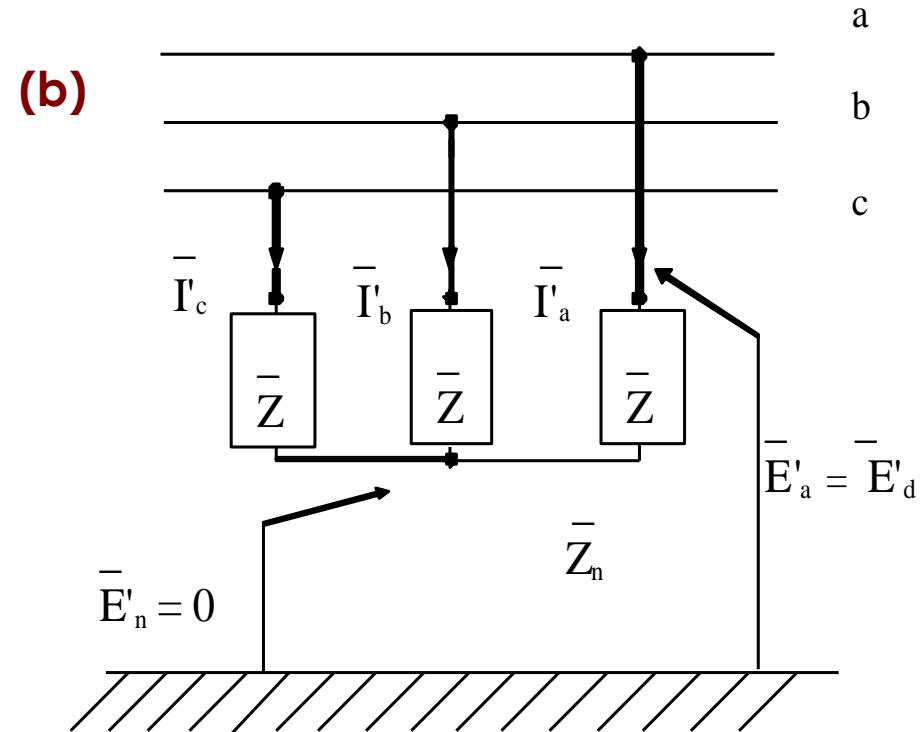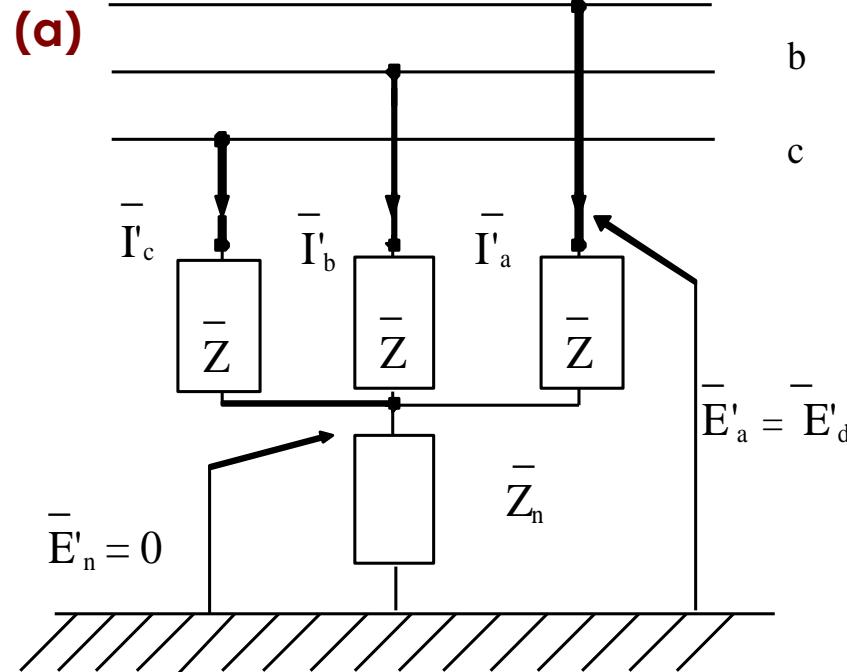
$$\bar{E}' - \bar{E}'_d = \bar{Z}_d \bar{I}'_d$$



Outline

Study of symmetrical components of a symmetrical three-phase system with a generic triplet of impedances to ground

Three-phase short-circuit

Ungrounded two-phase short-circuit

Two-phase short-circuit with connection to ground

Single-phase short-circuit to ground

Ungrounded two-phase short-circuit

18

We will consider the two-phase short-circuit shown in the figure where, at a generic point in the network, **an impedance is connected between two phases with a short-circuit impedance of $2\bar{Z}$** .

According to Kirchhoff's Law, we can analyze the circuit in the figure to determine **three equations linking the voltages, currents, and short-circuit impedances**:


$$\bar{I}_a' = 0$$

$$\bar{I}_b' + \bar{I}_c' = 0$$

$$\bar{E}_b' - \bar{Z}\bar{I}_b' = \bar{E}_c' - \bar{Z}\bar{I}_c'$$



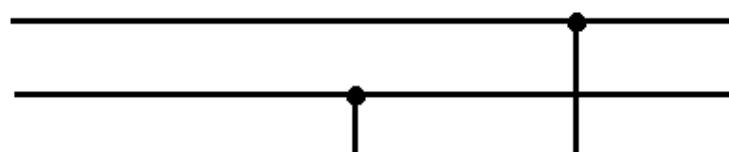Ira 2 si ha $\bar{Z}_a = \infty$, $\bar{Z}_b = \bar{Z}_c = \bar{Z}$ ($2\bar{Z}$ impedenza d



Ungrounded two-phase short-circuit

The **symmetrical component transformation for currents** is introduced, using the first two relations on the preceding slide:

$$\begin{bmatrix} \bar{I}_0 \\ \bar{I}_d \\ \bar{I}_i \end{bmatrix} = [T_s]^{-1} \begin{bmatrix} \bar{I}_a \\ \bar{I}_b \\ \bar{I}_c \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} \bar{I}_a \\ \bar{I}_b \\ \bar{I}_c \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} 0 \\ \bar{I}_b \\ -\bar{I}_b \end{bmatrix}$$

$\bar{I}_a' = 0$
 $\bar{I}_b' + \bar{I}_c' = 0$

For this particular case, this relation enables us to obtain the **first two equations in the sequence domain**:

$$\bar{I}_0' = 0$$

$$\bar{I}_d' = -\bar{I}_i' = \frac{(a - a^2)}{3} \bar{I}_b'$$

Ungrounded two-phase short-circuit

The link between phase currents and symmetrical component currents is as follows:

$$\begin{bmatrix} \bar{I}_a \\ \bar{I}_b \\ \bar{I}_c \end{bmatrix} = [T_s] \begin{bmatrix} \bar{I}_0 \\ \bar{I}_d \\ \bar{I}_i \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} \bar{I}_0 \\ \bar{I}_d \\ \bar{I}_i \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} 0 \\ \bar{I}_d \\ -\bar{I}_d \end{bmatrix}$$

Therefore:

$$\bar{I}_a = 0$$

$$\bar{I}_b = (a^2 - a)\bar{I}_d$$

$$\bar{I}_c = (a - a^2)\bar{I}_d = -\bar{I}_b$$

Ungrounded two-phase short-circuit

21

To obtain the **third equation in the sequence domain**, we can use the third equation in the phase domain, specifically:

$$\bar{E}_b' - \bar{ZI}_b' = \bar{E}_c' - \bar{ZI}_c'$$

We can write this equation in matrix form:

$$\bar{E}_b' - \bar{E}_c' = \bar{Z}(\bar{I}_b' - \bar{I}_c') = 2\bar{ZI}_b'$$

$$\bar{E}_b' - \bar{E}_c' = \begin{bmatrix} 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} \bar{E}_a' \\ \bar{E}_b' \\ \bar{E}_c' \end{bmatrix}$$

Ungrounded two-phase short-circuit

If we use the **sequence transformation for voltages**:

$$\begin{aligned}
 \bar{E}'_b - \bar{E}'_c &= \begin{bmatrix} 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} \bar{E}'_a \\ \bar{E}'_b \\ \bar{E}'_c \end{bmatrix} = \begin{bmatrix} 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} \bar{E}'_0 \\ \bar{E}'_d \\ \bar{E}'_i \end{bmatrix} = \\
 &= \begin{bmatrix} 0 & a^2 - a & a - a^2 \end{bmatrix} \begin{bmatrix} \bar{E}'_0 \\ \bar{E}'_d \\ \bar{E}'_i \end{bmatrix} = (a^2 - a)(\bar{E}'_d - \bar{E}'_i)
 \end{aligned}$$

Therefore, we can write $\bar{E}'_b - \bar{E}'_c = \bar{Z}(\bar{I}'_b - \bar{I}'_c) = 2\bar{Z}\bar{I}'_b$ as:

$$(a^2 - a)(\bar{E}'_d - \bar{E}'_i) = 2\bar{Z}(a^2 - a)\bar{I}'_d \quad \text{or} \quad (\bar{E}'_d - \bar{E}'_i) = 2\bar{Z}\bar{I}'_d$$

Ungrounded two-phase short-circuit

23


In summary, the necessary equations in the sequence domain are as follows:

$$\bar{I}_0' = 0$$

$$\bar{I}_d' = -\bar{I}_i'$$

$$(\bar{E}_d' - \bar{E}_i') = 2\bar{Z}\bar{I}_d'$$

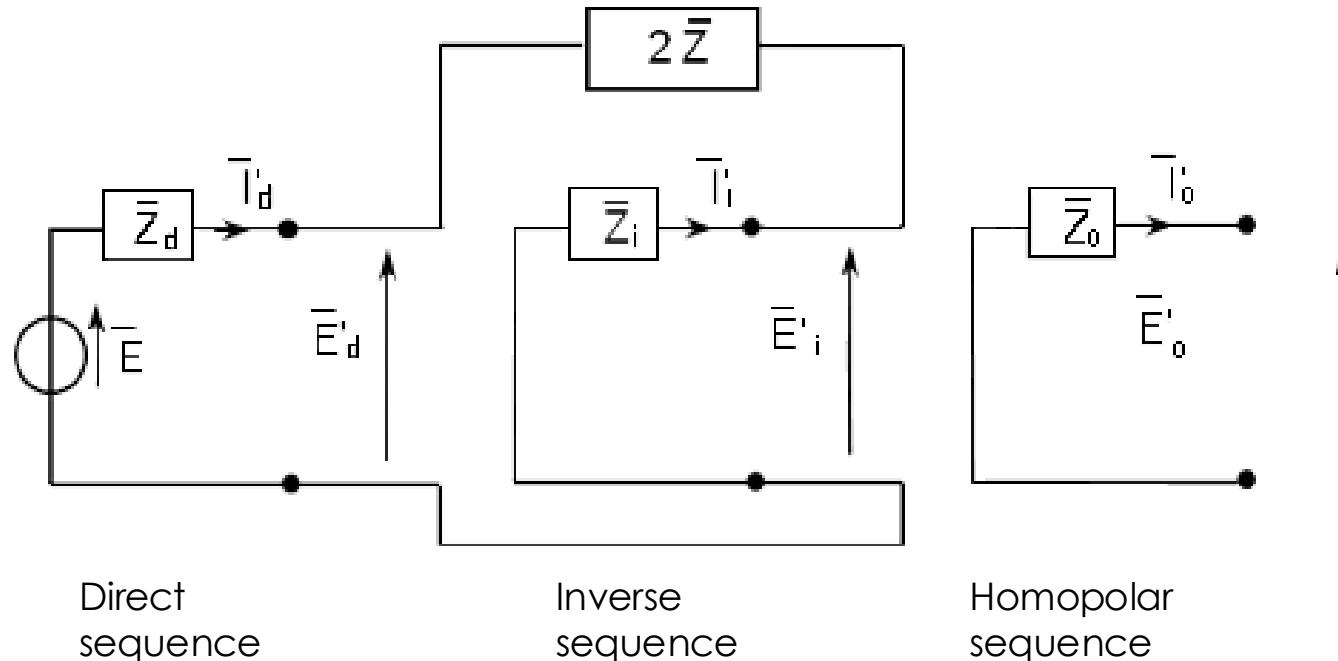These three equations can be seen as **coupling between sequence circuits**.




Ungrounded two-phase short-circuit

24

The solution of the circuit enables **determination of the direct and inverse sequence currents** (the homopolar sequence current is zero):
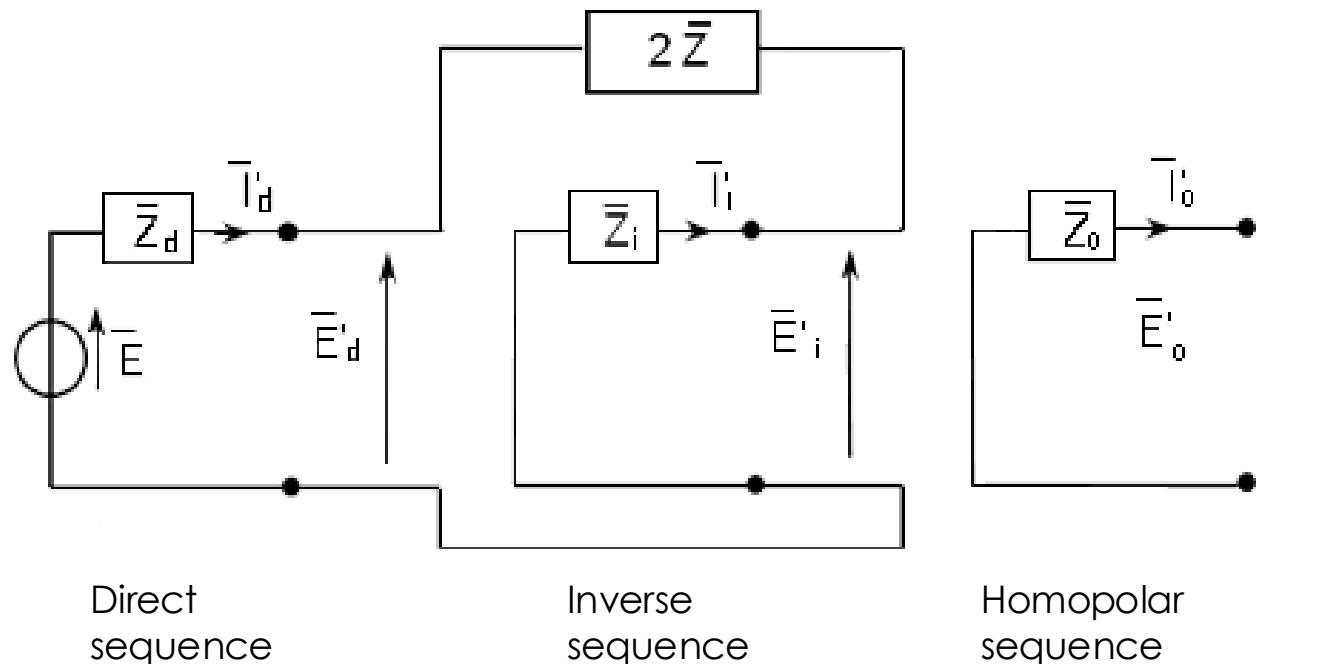
$$\bar{I}_d = \frac{\bar{E}}{\bar{Z}_d + \bar{Z}_i + 2\bar{Z}} = -\bar{I}_i$$



Ungrounded two-phase short-circuit


25

The two **voltages of the direct and inverse sequences** can be determined using the figure:

$$\bar{E}_0 = 0$$

$$\bar{E}_d = \frac{\bar{E}(\bar{Z}_i + 2\bar{Z})}{\bar{Z}_d + \bar{Z}_i + 2\bar{Z}}$$
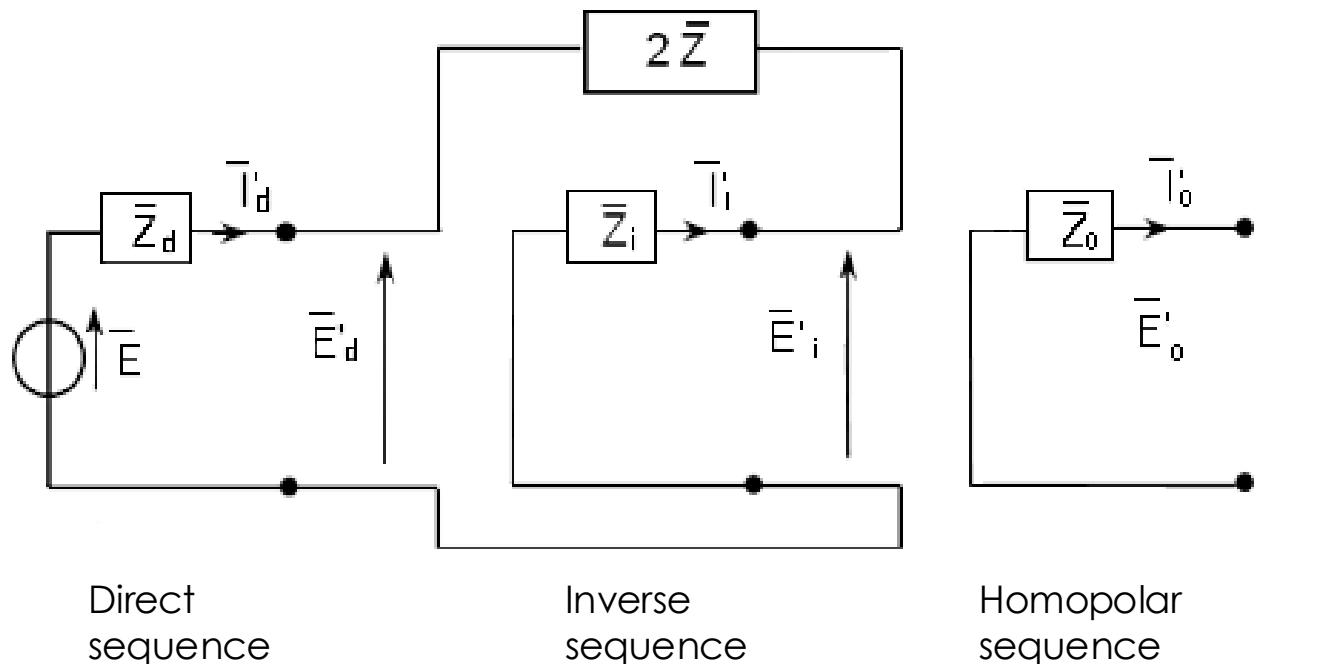
$$\bar{E}_i = \frac{\bar{E}\bar{Z}_i}{\bar{Z}_d + \bar{Z}_i + 2\bar{Z}}$$




Ungrounded two-phase short-circuit

26

The **short-circuit current in the phase domain** is given by:

$$\bar{I}_b = - (a - a^2) \bar{I}_d = (a^2 - a) \frac{\bar{E}}{\bar{Z}_d + \bar{Z}_i + 2\bar{Z}} = -j\sqrt{3} \frac{\bar{E}}{\bar{Z}_d + \bar{Z}_i + 2\bar{Z}} =$$

$$= -j\sqrt{3} \frac{\bar{E}}{\bar{Z}_d + \bar{Z}_i} \Big|_{\bar{Z}=0}$$

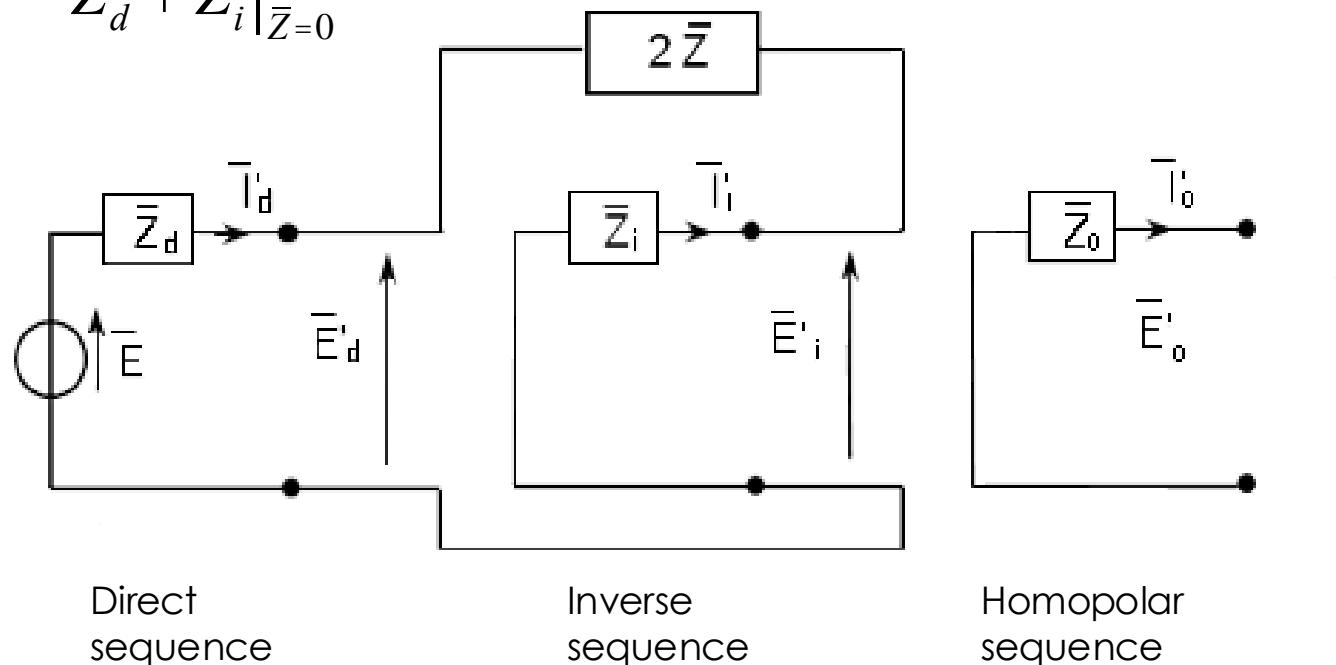

Outline

Study of symmetrical components of a symmetrical three-phase system with a generic triplet of impedances to ground

Three-phase short-circuit

Ungrounded two-phase short-circuit

Two-phase short-circuit with connection to ground

Single-phase short-circuit to ground

Two-phase short-circuit with connection to ground


We will consider a **two-phase short circuit** shown in the figure where, at a generic point in the network, **an impedance is connected between two phases and the ground with a short-circuit impedance of \bar{Z}** .

According to Kirchhoff's Law, we can analyze the circuit in the figure to determine **three equations linking the voltages, currents, and short-circuit impedances**:

$$\bar{I}'_a = 0$$

$$\bar{E}'_b = \bar{E}'_c$$
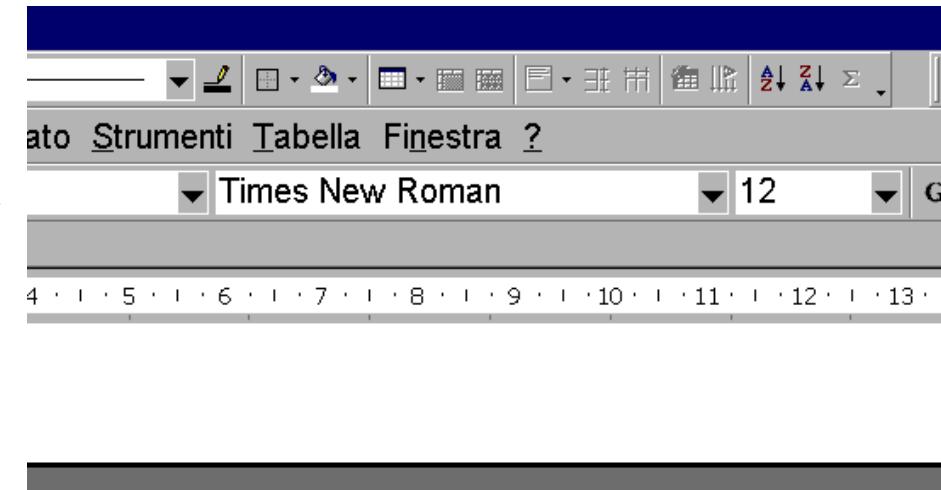
$$\bar{E}'_b = \bar{Z}(\bar{I}'_b + \bar{I}'_c)$$



Two-phase short-circuit with connection to ground

Using the **sequence transformation for currents** with $\bar{I}_a' = 0$, we obtain:

$$\boxed{\bar{I}_a' = 0} \quad \downarrow$$

$$\begin{bmatrix} \bar{I}_a' \\ \bar{I}_b' \\ \bar{I}_c' \end{bmatrix} = \begin{bmatrix} 0 \\ \bar{I}_b' \\ \bar{I}_c' \end{bmatrix} = [T_s] \begin{bmatrix} \bar{I}_0 \\ \bar{I}_d \\ \bar{I}_i \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} \bar{I}_0 \\ \bar{I}_d \\ \bar{I}_i \end{bmatrix}$$

Thus:

$$\bar{I}_0' + \bar{I}_d' + \bar{I}_i' = 0$$

Two-phase short-circuit with connection to ground

Using the **inverse sequence transformation for voltages**, we obtain:

$$\begin{bmatrix} \bar{E}_0 \\ \bar{E}_d \\ \bar{E}_i \end{bmatrix} = [T_s]^{-1} \begin{bmatrix} \bar{E}_a \\ \bar{E}_b \\ \bar{E}_c \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} \bar{E}_a \\ \bar{E}_b \\ \bar{E}_c \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} \bar{E}_a \\ \bar{E}_b \\ \bar{E}_b \end{bmatrix}$$

\uparrow

$\bar{E}_b = \bar{E}_c$

Therefore:

$$\bar{E}_0 = \frac{1}{3} (\bar{E}_a + 2\bar{E}_b)$$

$$\bar{E}_d = \frac{1}{3} (\bar{E}_a + (a + a^2)\bar{E}_b)$$

$$\bar{E}_i = \frac{1}{3} (\bar{E}_a + (a + a^2)\bar{E}_b) = \bar{E}_d \quad \text{P} \quad \bar{E}_i = \bar{E}_d$$

Two-phase short-circuit with connection to ground

Recall that:

$$\bar{E}_b = \bar{Z}(\bar{I}_b + \bar{I}_c)$$

$$\bar{E}_0 = \frac{1}{3}(\bar{E}_a + \bar{E}_b + \bar{E}_c) \quad \bar{E}_a = (\bar{E}_0 + \bar{E}_d + \bar{E}_i)$$

We obtain:

$$\bar{E}_0 = \frac{1}{3}(\bar{E}_a + 2\bar{E}_b) \longrightarrow \bar{E}_0 = \frac{1}{3}(\bar{E}_0 + \bar{E}_d + \bar{E}_i + 2\bar{Z}(\bar{I}_b + \bar{I}_c))$$

The term $(\bar{I}_b + \bar{I}_c)$ can be determined using the inverse sequence transformation for currents

$$\begin{bmatrix} \bar{I}_0 \\ \bar{I}_d \\ \bar{I}_i \end{bmatrix} = [T_s]^{-1} \begin{bmatrix} \bar{I}_a \\ \bar{I}_b \\ \bar{I}_c \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} \bar{I}_a \\ \bar{I}_b \\ \bar{I}_c \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} 0 \\ \bar{I}_b \\ \bar{I}_c \end{bmatrix}$$

Two-phase short-circuit with connection to ground

Therefore:

$$\bar{I}_0' = \frac{\bar{I}_b' + \bar{I}_c'}{3}$$

Finally, by substitution:

$$\bar{E}_0' = \frac{1}{3} \left(\bar{E}_0' + \bar{E}_d' + \bar{E}_i' + 6\bar{Z}\bar{I}_0' \right)$$

If we substitute the following

$$\bar{E}_i' = \frac{1}{3} \left(\bar{E}_a' + (a + a^2) \bar{E}_b' \right) = \bar{E}_d' \quad \text{P} \quad \bar{E}_i' = \bar{E}_d'$$

in the preceding expression for \bar{E}_0' we obtain:

$$3\bar{E}_0' = \bar{E}_0' + 2\bar{E}_d' + 6\bar{Z}\bar{I}_0' \quad \text{P} \quad \bar{E}_0' = \bar{E}_d' + 3\bar{Z}\bar{I}_0'$$

Two-phase short-circuit with connection to ground


The **three equations of the two-phase grounded short-circuit in the sequence domain** are summarized as follows:

$$\bar{I}_0' + \bar{I}_d' + \bar{I}_i' = 0$$

$$\bar{E}_i' = \bar{E}_d'$$

$$\bar{E}_0' = \bar{E}_d' + 3\bar{Z}\bar{I}_0'$$

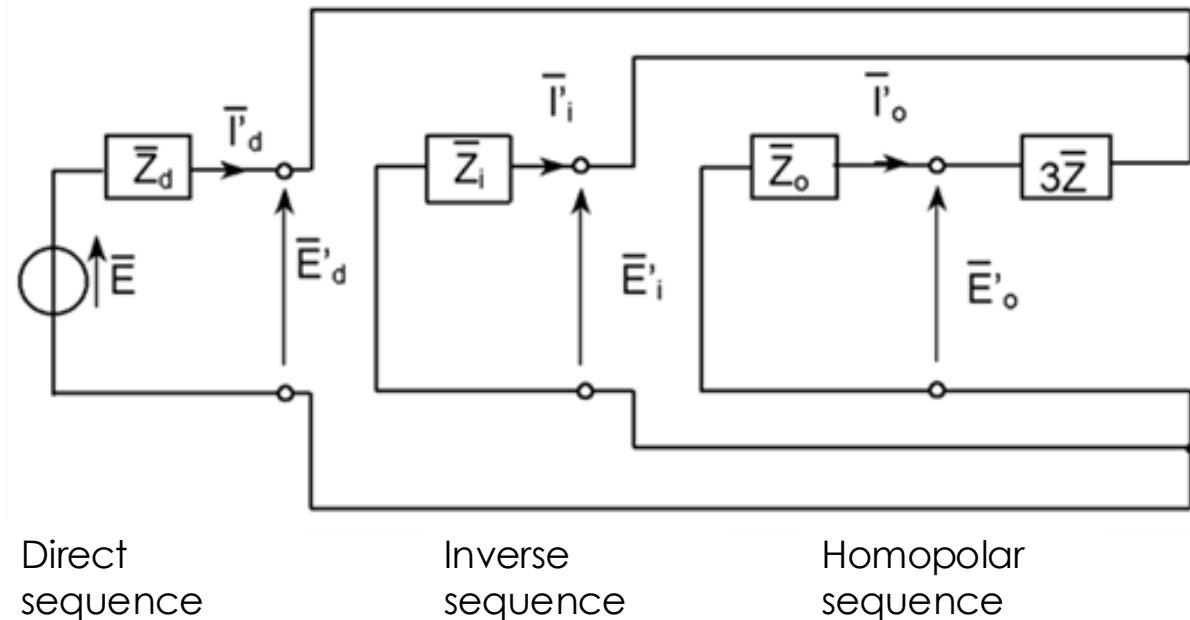
These three equations can be seen as **coupling between sequence circuits**.



Two-phase short-circuit with connection to ground

The circuit solution is as follows:
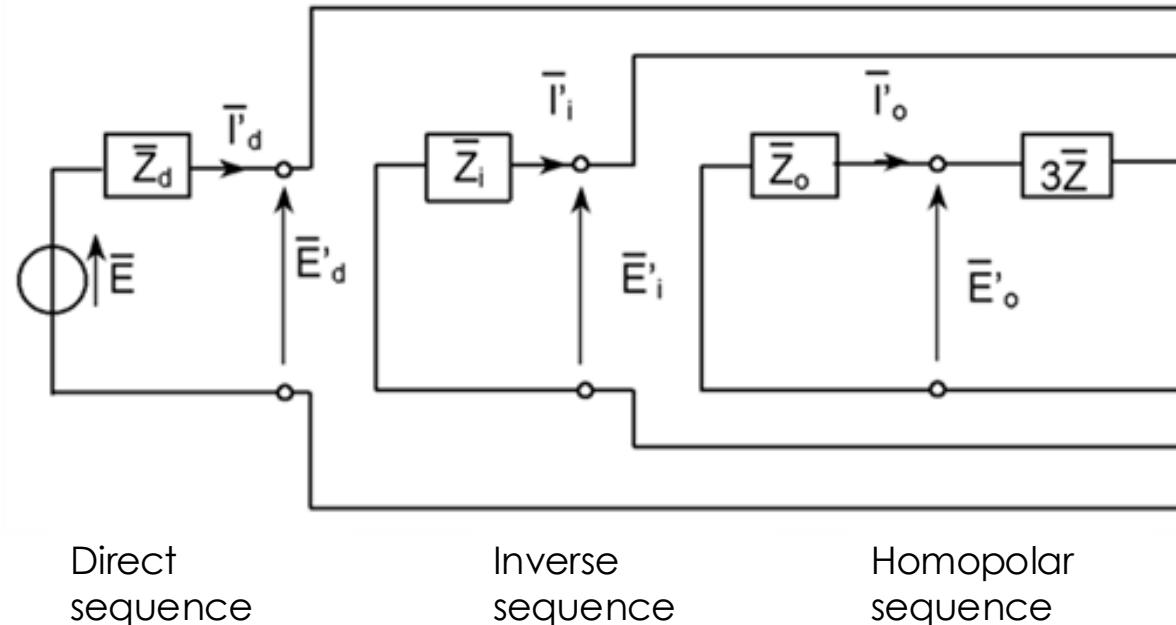
$$\bar{I}_d = \frac{\bar{E}}{\bar{Z}_d + \frac{\bar{Z}_i(\bar{Z}_0 + 3\bar{Z})}{\bar{Z}_i + \bar{Z}_0 + 3\bar{Z}}}$$




Two-phase short-circuit with connection to ground

The **inverse and homopolar** currents can be determined if we notice that the impedances $\bar{Z}_0 + 3\bar{Z}$ and \bar{Z}_i are a **current divisor** for \bar{I}_d :

$$\bar{I}_i = -\bar{I}_d \frac{\bar{Z}_0 + 3\bar{Z}}{\bar{Z}_i + \bar{Z}_0 + 3\bar{Z}}$$
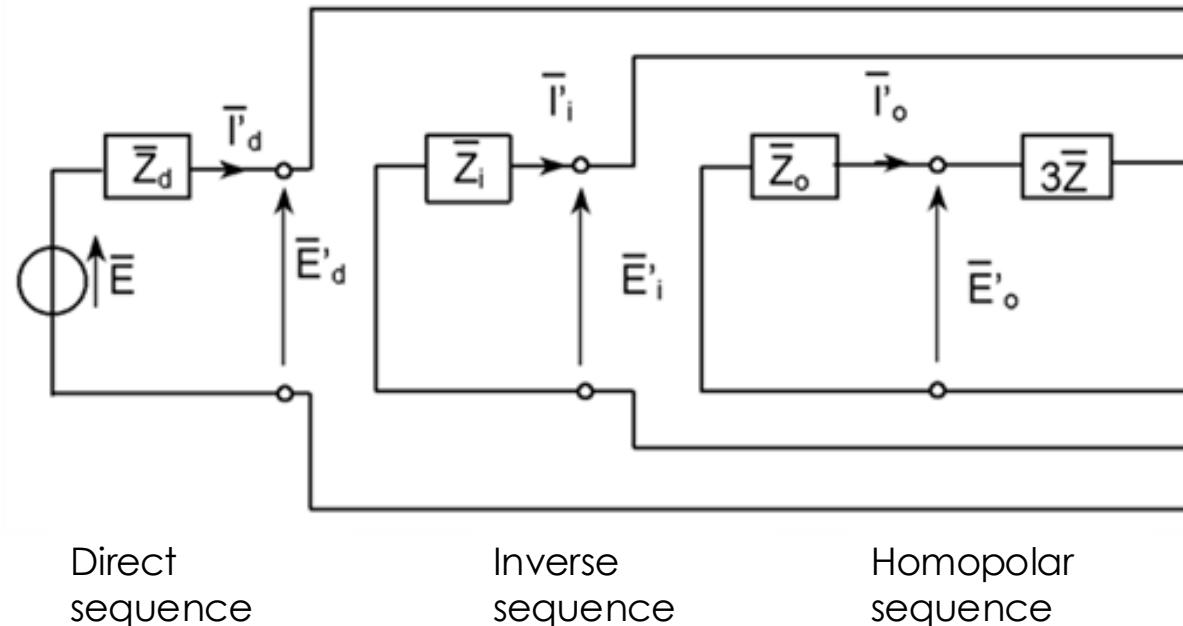
$$\bar{I}_0 = -\bar{I}_d \frac{\bar{Z}_i}{\bar{Z}_i + \bar{Z}_0 + 3\bar{Z}}$$




Two-phase short-circuit with connection to ground

The **direct, inverse, and homopolar sequence voltages** are determined using the circuit:

$$\bar{E}'_d = \bar{E} - \bar{Z}_d \bar{I}'_d = \bar{E}'_i$$

$$\bar{E}'_0 = -\bar{Z}_0 \bar{I}'_0$$

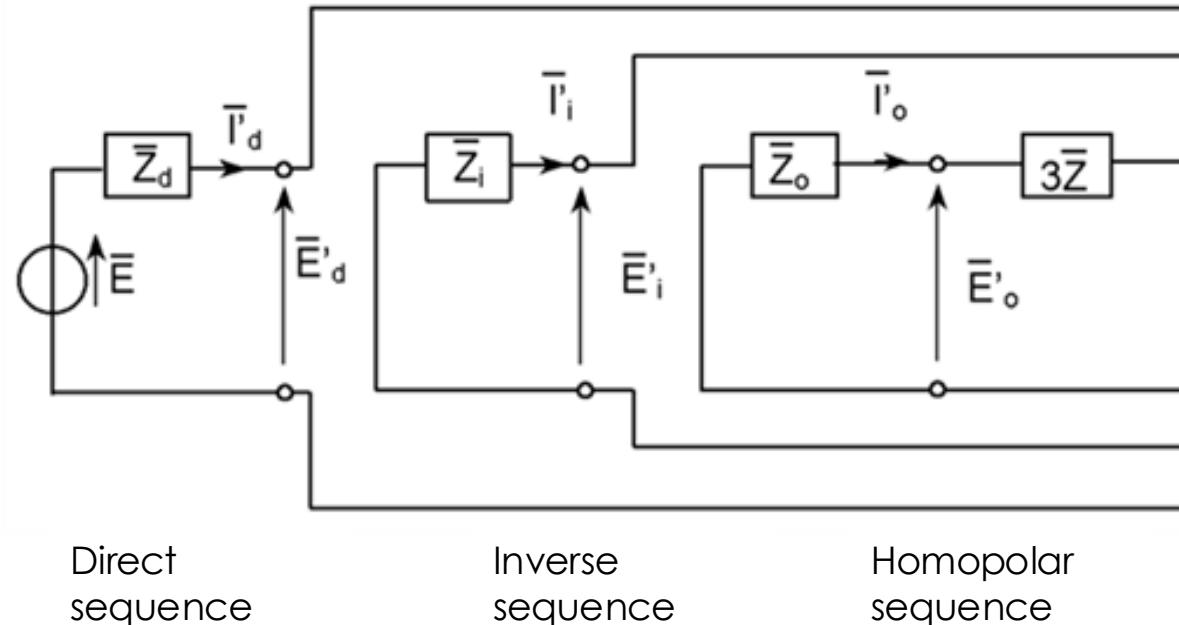

Two-phase short-circuit with connection to ground

The **short-circuit currents in the phase domain** are:

$$\begin{bmatrix} \bar{I}_a \\ \bar{I}_b \\ \bar{I}_c \end{bmatrix} = [T_s] \begin{bmatrix} \bar{I}_0 \\ \bar{I}_d \\ \bar{I}_i \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} -\bar{I}_d \frac{\bar{Z}_i}{\bar{Z}_i + \bar{Z}_0 + 3\bar{Z}} \\ \bar{E} \\ \bar{Z}_d + \frac{\bar{Z}_i(\bar{Z}_0 + 3\bar{Z})}{\bar{Z}_i + \bar{Z}_0 + 3\bar{Z}} \\ -\bar{I}_d \frac{\bar{Z}_0 + 3\bar{Z}}{\bar{Z}_i + \bar{Z}_0 + 3\bar{Z}} \end{bmatrix}$$

Two-phase short-circuit with connection to ground

Therefore, the phase currents for a **two-phase strongly grounded short-circuit** (i.e., assuming that $\bar{Z} = 0$) are as follows:

$$\begin{aligned}
 \bar{I}'_a &= 0 \\
 \bar{I}'_b &= -\bar{I}'_d \frac{\bar{Z}_i}{\bar{Z}_i + \bar{Z}_0 + 3\bar{Z}} + \alpha^2 \bar{I}'_d - \alpha \bar{I}'_d \frac{\bar{Z}_0 + 3\bar{Z}}{\bar{Z}_i + \bar{Z}_0 + 3\bar{Z}} = \\
 &= \bar{I}'_d \left(-\frac{\bar{Z}_i}{\bar{Z}_i + \bar{Z}_0 + 3\bar{Z}} + \alpha^2 - \alpha \frac{\bar{Z}_0 + 3\bar{Z}}{\bar{Z}_i + \bar{Z}_0 + 3\bar{Z}} \right) = \\
 &= \bar{I}'_d \left[\frac{-\bar{Z}_i + \alpha^2(\bar{Z}_i + \bar{Z}_0 + 3\bar{Z}) - \alpha(\bar{Z}_0 + 3\bar{Z})}{\bar{Z}_i + \bar{Z}_0 + 3\bar{Z}} \right] = \\
 &= \bar{I}'_d \left[\frac{\bar{Z}_i(\alpha^2 - 1) + \bar{Z}_0(\alpha^2 - \alpha) + 3\bar{Z}(\alpha^2 - \alpha)}{\bar{Z}_i + \bar{Z}_0 + 3\bar{Z}} \right] = \\
 &= \frac{\bar{E}[\bar{Z}_i(\alpha^2 - 1) + \bar{Z}_0(\alpha^2 - \alpha) + 3\bar{Z}(\alpha^2 - \alpha)]}{\bar{Z}_d(\bar{Z}_i + \bar{Z}_0 + 3\bar{Z}) + \bar{Z}_i(\bar{Z}_0 + 3\bar{Z})}
 \end{aligned}$$

Two-phase short-circuit with connection to ground

Therefore, the phase currents for a **two-phase strongly grounded short-circuit** (i.e., assuming that $\bar{Z} = 0$) are as follows:

$$\begin{aligned}
 \bar{I}'_c &= -\bar{I}'_d \frac{\bar{Z}_i}{\bar{Z}_i + \bar{Z}_0 + 3\bar{Z}} + \alpha \bar{I}'_d - \alpha^2 \bar{I}'_d \frac{\bar{Z}_0 + 3\bar{Z}}{\bar{Z}_i + \bar{Z}_0 + 3\bar{Z}} = \\
 &= \bar{I}'_d \left(-\frac{\bar{Z}_i}{\bar{Z}_i + \bar{Z}_0 + 3\bar{Z}} + \alpha - \alpha^2 \frac{\bar{Z}_0 + 3\bar{Z}}{\bar{Z}_i + \bar{Z}_0 + 3\bar{Z}} \right) = \\
 &= \bar{I}'_d \left[\frac{-\bar{Z}_i + \alpha(\bar{Z}_i + \bar{Z}_0 + 3\bar{Z}) - \alpha^2(\bar{Z}_0 + 3\bar{Z})}{\bar{Z}_i + \bar{Z}_0 + 3\bar{Z}} \right] = \\
 &= \bar{I}'_d \left[\frac{\bar{Z}_i(\alpha - 1) + \bar{Z}_0(\alpha - \alpha^2) + 3\bar{Z}(\alpha - \alpha^2)}{\bar{Z}_i + \bar{Z}_0 + 3\bar{Z}} \right] = \\
 &= \frac{\bar{E}[\bar{Z}_i(\alpha - 1) + \bar{Z}_0(\alpha - \alpha^2) + 3\bar{Z}(\alpha - \alpha^2)]}{\bar{Z}_d(\bar{Z}_i + \bar{Z}_0 + 3\bar{Z}) + \bar{Z}_i(\bar{Z}_0 + 3\bar{Z})}
 \end{aligned}$$

Outline

Study of symmetrical components of a symmetrical three-phase system with a generic triplet of impedances to ground

Three-phase short-circuit

Ungrounded two-phase short-circuit

Two-phase short-circuit with connection to ground

Single-phase short-circuit to ground


Single-phase short-circuit to ground

The schematic of the short-circuit is shown below. For this case, the **equations linking voltages, currents, and short-circuit impedance** in the phase domain are:

$$\bar{E}'_a = \bar{Z} \bar{I}'_a$$

$$\bar{I}'_b = 0$$

$$\bar{I}'_c = 0$$

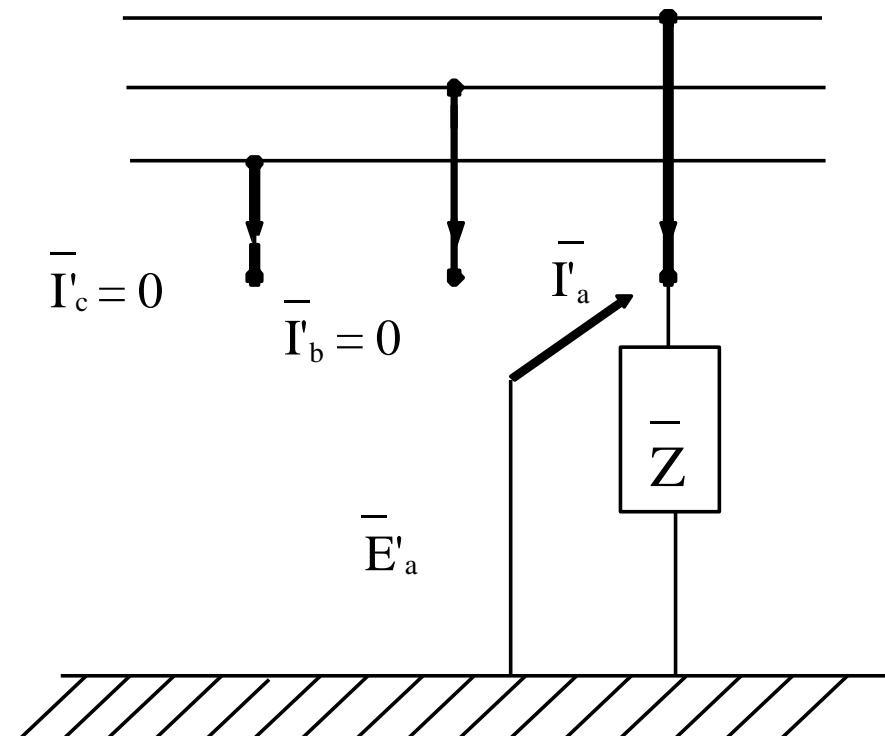

Single-phase short-circuit to ground

We can use the **inverse sequence transformation for currents**:

$$\begin{bmatrix} \bar{I}_0 \\ \bar{I}_d \\ \bar{I}_i \end{bmatrix} = [T_s]^{-1} \begin{bmatrix} \bar{I}_a \\ \bar{I}_b \\ \bar{I}_c \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} \bar{I}_a \\ \bar{I}_b \\ \bar{I}_c \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} \bar{I}_a \\ 0 \\ 0 \end{bmatrix}$$

$\bar{I}_b = 0$
 $\bar{I}_c = 0$

Therefore:

$$\bar{I}_0 = \frac{\bar{I}_a}{3}$$

$$\bar{I}_d = \frac{\bar{I}_a}{3} \quad \boxed{\bar{I}_0 = \bar{I}_d = \bar{I}_i}$$

$$\bar{I}_i = \frac{\bar{I}_a}{3}$$

Single-phase short-circuit to ground

43

The last constraint equation in the sequence domain is determined using the **sequence transformation for voltages**:

$$\begin{bmatrix} \bar{E}_a \\ \bar{E}_b \\ \bar{E}_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} \bar{E}_0 \\ \bar{E}_d \\ \bar{E}_i \end{bmatrix}$$

If we make the following substitutions:

$$\bar{I}_0 = \frac{\bar{I}_a}{3} \quad \bar{E}_a = \bar{Z}\bar{I}_a$$

The result is:

$$\bar{E}_a = 3\bar{Z}\bar{I}_0 = \bar{E}_0 + \bar{E}_d + \bar{E}_i$$

Single-phase short-circuit to ground

44


The **three equations in the sequence domain** are summarized as follows:

$$\bar{I}'_0 = \bar{I}'_d$$

$$\bar{I}'_d = \bar{I}'_i$$

$$\bar{E}'_0 + \bar{E}'_d + \bar{E}'_i = 3\bar{Z}\bar{I}'_0$$

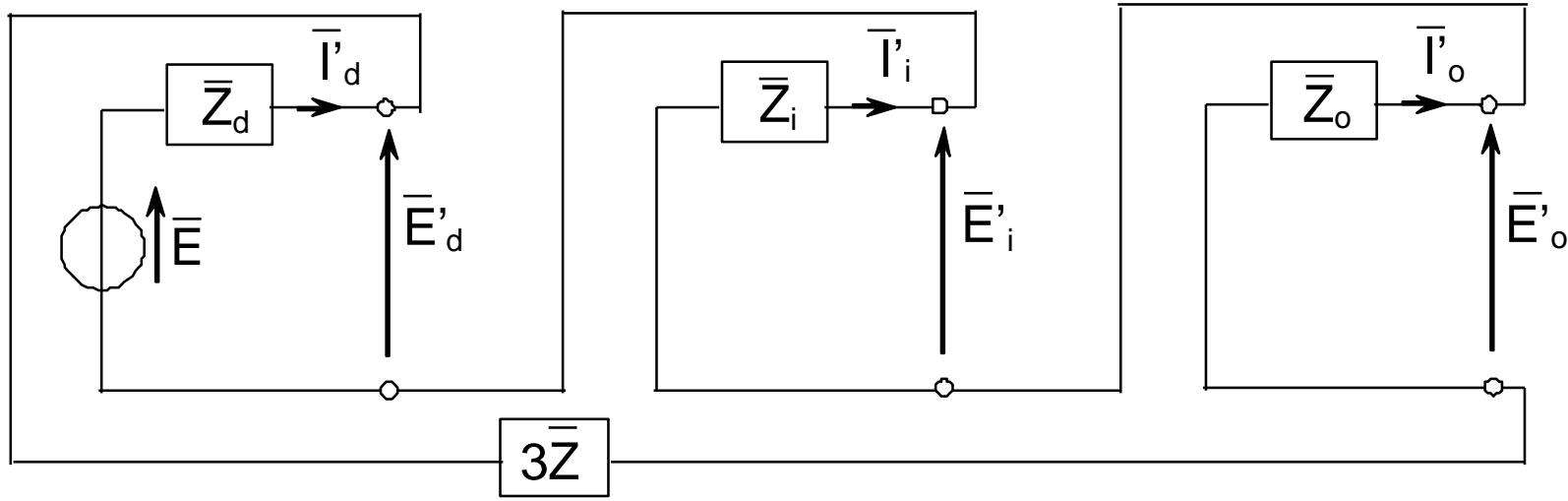These equations can be seen as a **coupling of the sequence circuits**.




Single-phase short-circuit to ground

45

The circuit solution enables the determination of the **sequence currents**:
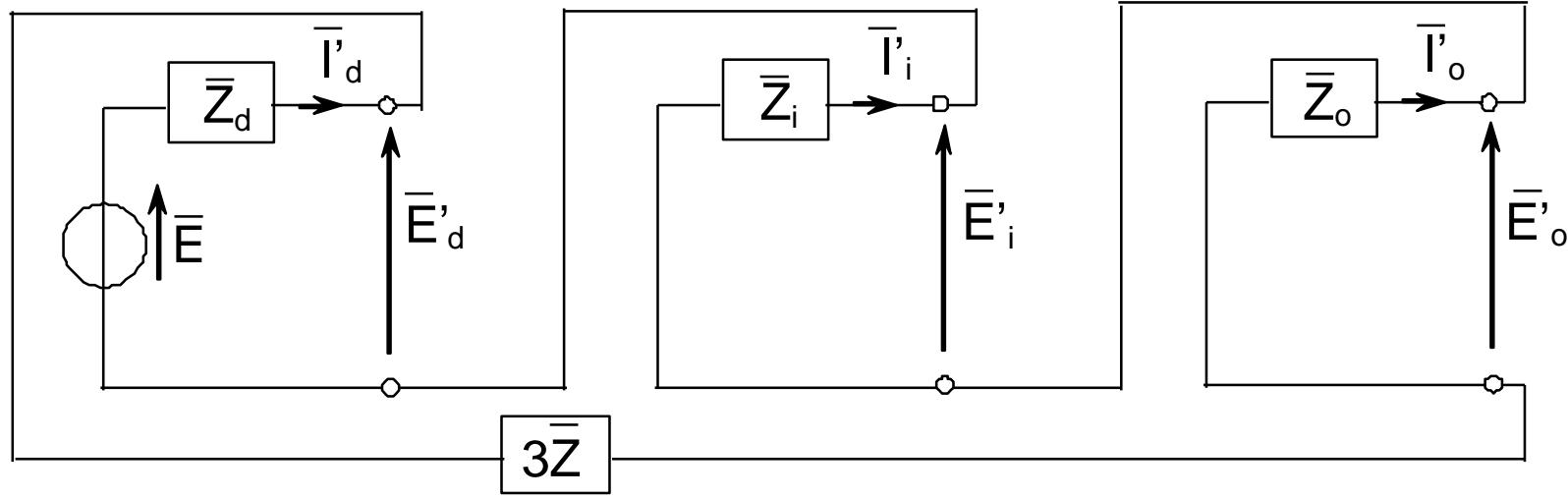
$$\bar{I}'_0 = \bar{I}'_d = \bar{I}'_i = \frac{\bar{E}}{\bar{Z}_d + \bar{Z}_i + \bar{Z}_0 + 3\bar{Z}}$$



Single-phase short-circuit to ground


46

The **voltages of each sequence** are:

$$\bar{E}'_d = \bar{E} - \bar{Z}_d \bar{I}'_d$$

$$\bar{E}'_i = -\bar{Z}_i \bar{I}'_i$$

$$\bar{E}'_0 = -\bar{Z}_0 \bar{I}'_0$$

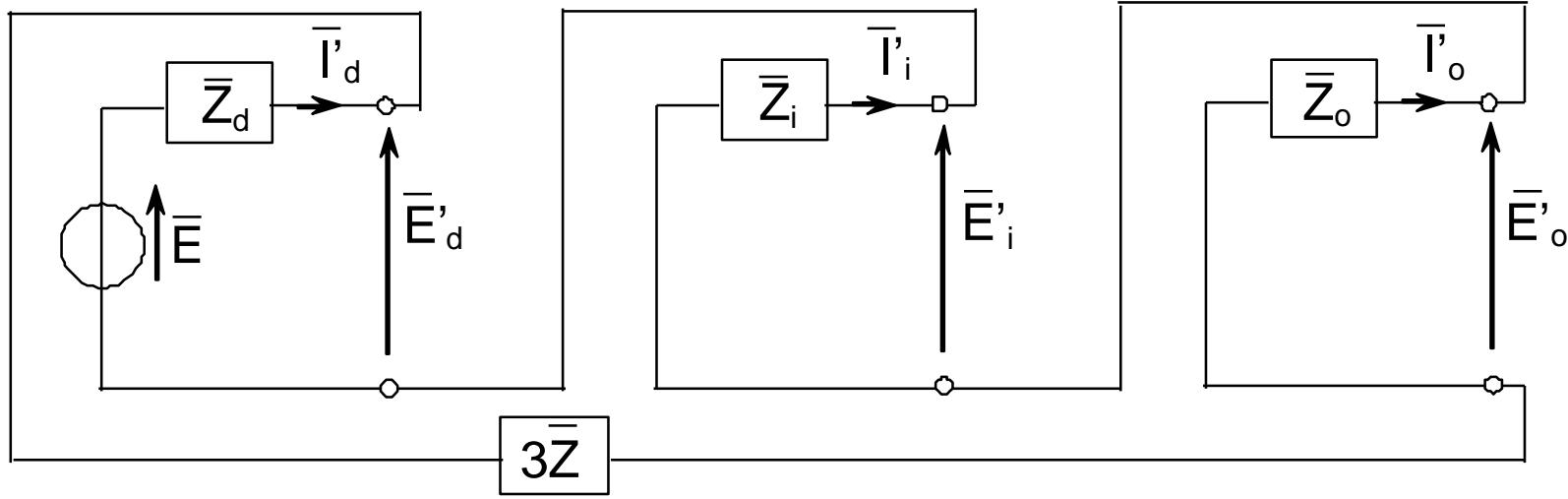

Single-phase short-circuit to ground

47

The **short-circuit current in the phase domain** is as follows:

$$\bar{I}'_a = \frac{3\bar{E}}{\bar{Z}_d + \bar{Z}_i + \bar{Z}_0 + 3\bar{Z}} = \frac{3\bar{E}}{\bar{Z}_d + \bar{Z}_i + \bar{Z}_0} \Big|_{\bar{Z}=0}$$

