

EE-365 - W1

DC-DC CONVERTERS

BUCK-BOOST, FLYBACK

Prof. D. Dujic

École Polytechnique Fédérale de Lausanne
Power Electronics Laboratory
Switzerland



DC-DC CONVERTERS

Numerous topologies are available

Power Supply Topologies

Texas Instruments, the Power Behind Your Designs

Type of Converter	BUCK	BOOST	BUCK BOOST (Inverting)	SEPIC	FLYBACK	FORWARD	2 SWITCH FORWARD	ACTIVE CLAMP FORWARD	HALF BRIDGE	PUSH PULL	FULL BRIDGE	PHASE SHIFT ZVT
Circuit Configuration												
Ideal Transfer Function*	$\frac{V_{OUT}}{V_{IN}} = \left(\frac{N_o}{N_p}\right) - D$	$\frac{V_{OUT}}{V_{IN}} = \left(\frac{N_o}{N_p - N_{ZT}}\right) - \frac{1}{(1-D)}$	$\frac{V_{OUT}}{V_{IN}} = \left(\frac{N_o}{N_p - N_{ZT}}\right) - \left(\frac{D}{1-D}\right)$	$\frac{V_{OUT}}{V_{IN}} = \left(\frac{D}{1-D}\right)$	$\frac{V_{OUT}}{V_{IN}} = D + \sqrt{2 \times \frac{V_{OUT}}{V_{IN}} \times \left(\frac{N_o}{N_p}\right) - \left(\frac{N_o}{N_p}\right) \times D}$	$\frac{V_{OUT}}{V_{IN}} = \left(\frac{N_o}{N_p}\right) \times \left(\frac{N_o}{N_p}\right) - \left(\frac{N_o}{N_p}\right) \times D$	$\frac{V_{OUT}}{V_{IN}} = \left(\frac{N_o}{N_p}\right) \times \left(\frac{N_o}{N_p}\right) - \left(\frac{N_o}{N_p}\right) \times D$	$\frac{V_{OUT}}{V_{IN}} = \left(\frac{N_o}{N_p}\right) \times \left(\frac{N_o}{N_p}\right) - \left(\frac{N_o}{N_p}\right) \times D$	$\frac{V_{OUT}}{V_{IN}} = \left(\frac{N_o}{N_p}\right) \times \left(\frac{N_o}{N_p}\right) - 2 \times \left(\frac{N_o}{N_p}\right) \times D$	$\frac{V_{OUT}}{V_{IN}} = \left(\frac{N_o}{N_p}\right) \times \left(\frac{N_o}{N_p}\right) - 2 \times \left(\frac{N_o}{N_p}\right) \times D$	$\frac{V_{OUT}}{V_{IN}} = \left(\frac{N_o}{N_p}\right) \times \left(\frac{N_o}{N_p}\right) - 2 \times \left(\frac{N_o}{N_p}\right) \times D$	$\frac{V_{OUT}}{V_{IN}} = \left(\frac{N_o}{N_p}\right) \times \left(\frac{N_o}{N_p}\right) - 2 \times \left(\frac{N_o}{N_p}\right) \times D$
Drain Current*	$I_{D1} = I_{LOAD} = V_{OUT}$	$I_{D2} = I_{LOAD} = I_{OUT} \times \left(\frac{1}{1-D}\right)$	$I_{D1} = I_{LOAD} = I_{OUT} \times \left(\frac{1}{1-D}\right)$	$I_{D2} = I_{LOAD} = \left(\frac{D}{1-D}\right) \times I_{OUT}$	$I_{D1} = I_{LOAD} = \left(\frac{N_o}{N_p}\right) \times I_{OUT}$	$I_{D2} = I_{LOAD} = \left(\frac{N_o}{N_p}\right) \times I_{OUT}$	$I_{D1} = I_{LOAD} = \left(\frac{N_o}{N_p}\right) \times I_{OUT}$	$I_{D2} = I_{LOAD} = \left(\frac{N_o}{N_p}\right) \times I_{OUT}$	$I_{D1} = I_{LOAD} = \left(\frac{N_o}{N_p}\right) \times I_{OUT}$	$I_{D2} = I_{LOAD} = \left(\frac{N_o}{N_p}\right) \times I_{OUT}$	$I_{D1} = I_{LOAD} = \left(\frac{N_o}{N_p}\right) \times I_{OUT}$	$I_{D2} = I_{LOAD} = \left(\frac{N_o}{N_p}\right) \times I_{OUT}$
Drain Voltage*	$V_{DS} = V_{IN}$	$V_{DS} = V_{OUT}$	$V_{DS} = V_{IN} - V_{OUT}$	$V_{DS} = V_{IN} - V_{OUT}$	$V_{DS} = V_{IN} + V_{OUT} \times \left(\frac{N_o}{N_p}\right)$	$V_{DS} = 2 \times V_{IN}$	$V_{DS} = V_{IN}$	$V_{DS} = V_{IN} \times \left(\frac{1}{1-D}\right)$	$V_{DS} = V_{IN}$	$V_{DS} = 2 \times V_{IN}$	$V_{DS} = V_{IN}$	$V_{DS} = V_{IN}$
Diode Current*	$I_{D1} = I_{LOAD} \times (1-D)$	$I_{D2} = V_{OUT}$	$I_{D1} = V_{OUT}$	$I_{D2} = V_{OUT}$	$I_{D1} = I_{LOAD} \times D$	$I_{D2} = I_{LOAD} \times D$	$I_{D1} = I_{LOAD} \times D$	$I_{D2} = I_{LOAD} \times D$	$I_{D1} = \left(\frac{I_{LOAD}}{2} + \frac{I_{OUT}}{2} \times (1-2D)\right)$	$I_{D2} = \left(\frac{I_{LOAD}}{2} + \frac{I_{OUT}}{2} \times (1-2D)\right)$	$I_{D1} = \left(\frac{I_{LOAD}}{2} + \frac{I_{OUT}}{2} \times (1-2D)\right)$	$I_{D2} = \left(\frac{I_{LOAD}}{2} + \frac{I_{OUT}}{2} \times (1-2D)\right)$
Diode Reverse Voltage*	$V_{D1} = V_{IN}$	$V_{D2} = V_{OUT}$	$V_{D1} = V_{IN} - V_{OUT}$	$V_{D2} = V_{IN}$	$V_{D1} = V_{OUT} + V_{DS} \times \left(\frac{N_o}{N_p}\right)$	$V_{D2} = V_{OUT} + V_{DS} \times \left(\frac{N_o}{N_p}\right)$	$V_{D1} = V_{OUT} + V_{DS} \times \left(\frac{N_o}{N_p}\right)$	$V_{D2} = \frac{V_{IN}}{2} + \left(\frac{N_o}{N_p}\right) \times \left(\frac{1}{1-D}\right)$	$V_{D1} = \frac{V_{IN}}{2} + \left(\frac{N_o}{N_p}\right)$	$V_{D2} = V_{IN} \times \left(\frac{N_o}{N_p}\right)$	$V_{D1} = V_{IN} \times \left(\frac{N_o}{N_p}\right)$	$V_{D2} = V_{IN} \times \left(\frac{N_o}{N_p}\right)$
Voltage and Current Waveforms												

*Excludes ripple current and output diode voltage drop.

Go to power.ti.com and click on the "Search" button in the "Key Word" box. For STEM topics, go to power.ti.com/standards

Independence Buck Power Stage in Switch-mode Power Supplies Using the TPS65401 Buck Controller (12.5Watt) (SLVAD011) (Rev. A) (Rev. A)

Independence Boost Power Stage in Switch-mode Power Supplies Using the TPS65402 Boost Controller (12.5Watt) (SLVAD012) (Rev. A) (Rev. A)

Independence Buck-Boost Power Stage in Switch-mode Power Supplies Using the TPS65403 Buck-Boost Controller (12.5Watt) (SLVAD013) (Rev. A) (Rev. A)

Buck-Boost Low Power SEPIC Converter Across Wide Input Voltage Range (SLVAD014) (Rev. A) (Rev. A)

Design of Inductor and Transformer for SEPIC Converter Using the TPS65404 SEPIC Controller (12.5Watt) (SLVAD015) (Rev. A) (Rev. A)

Design of Inductor and Transformer for Forward Converter Using the TPS65405 Forward Controller (12.5Watt) (SLVAD016) (Rev. A) (Rev. A)

Forward Converter Design Review for SEPIC and Forward Topologies in Current Mode Power Supplies (SLVAD017) (Rev. A) (Rev. A)

1

Forward Converter Design Review for SEPIC and Forward Topologies in Current Mode Power Supplies (SLVAD018) (Rev. A) (Rev. A)

Forward Converter Design Review for SEPIC and Forward Topologies in Current Mode Power Supplies (SLVAD019) (Rev. A) (Rev. A)

Forward Converter Design Review for SEPIC and Forward Topologies in Current Mode Power Supplies (SLVAD020) (Rev. A) (Rev. A)

Forward Converter Design Review for SEPIC and Forward Topologies in Current Mode Power Supplies (SLVAD021) (Rev. A) (Rev. A)

Forward Converter Design Review for SEPIC and Forward Topologies in Current Mode Power Supplies (SLVAD022) (Rev. A) (Rev. A)

Forward Converter Design Review for SEPIC and Forward Topologies in Current Mode Power Supplies (SLVAD023) (Rev. A) (Rev. A)

Forward Converter Design Review for SEPIC and Forward Topologies in Current Mode Power Supplies (SLVAD024) (Rev. A) (Rev. A)

Forward Converter Design Review for SEPIC and Forward Topologies in Current Mode Power Supplies (SLVAD025) (Rev. A) (Rev. A)

Forward Converter Design Review for SEPIC and Forward Topologies in Current Mode Power Supplies (SLVAD026) (Rev. A) (Rev. A)

1

power.ti.com

© 2008 Texas Instruments Incorporated Printed in the USA. All rights reserved.

REAL WORLD SIGNAL PROCESSING™

TEXAS INSTRUMENTS

Figure 1 Texas Instruments SMPS poster.

BUCK-BOOST CONVERTER

Non-isolated step-up-down DC-DC converter

BUCK-BOOST CONVERTER - STEP-UP/STEP-DOWN CONVERTER

Third basic non-isolated converter is Buck-Boost:

- as the name indicates, output voltage can be lower or higher than input voltage
- polarity of output voltage is reversed
- it is used for many battery powered devices
- Buck-Boost converter could be obtained by cascade connection of Buck and Boost
- conversion ratio is then product of two converter ratios in cascade

This allows for output voltage to be lower or higher than input voltage

$$\frac{V_o}{V_d} = D \frac{1}{1-D}$$

During the t_{on}

- Switch is ON and Diode is OFF (reverse biased)
- input voltage source V_d provides the energy to the inductor
- output capacitor is supplying the load

During the t_{off}

- Switch is OFF and Diode is ON
- energy stored in inductor is released to the load
- no energy is supplied by the input V_d

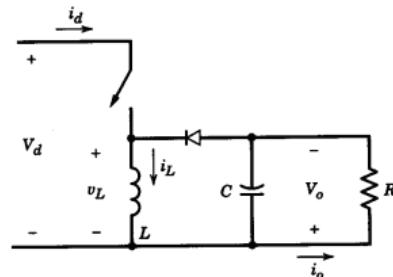


Figure 2 Buck-Boost Converter.

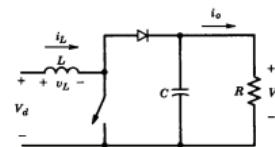


Figure 3 Boost Converter.

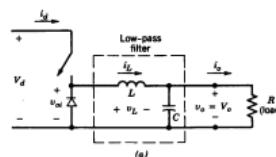


Figure 4 Buck Converter.

BUCK-BOOST CONVERTER - CCM

During the CCM:

- inductor current i_L is flowing continuously (it never reaches zero value)
- the average inductor current is equal to $I_L = I_d + I_o$

For the Buck-Boost converter we have:

$$v_L = L \frac{di_L}{dt}, \quad i_C = C \frac{dV_o}{dt}, \quad i_L(t_{on}) = i_d \quad i_L(t_{off}) = i_C + i_R = C \frac{dV_o}{dt} + \frac{V_o}{R}$$

During the t_{on} - Switch is ON and Diode is OFF

$$v_L = V_d, \quad i_L = i_d, \quad i_C = C \frac{dV_o}{dt} = -i_o = -\frac{V_o}{R}$$

During the t_{off} - Switch is OFF and Diode is ON

$$v_L = -V_o, \quad i_L = i_C + i_o = C \frac{dV_o}{dt} + \frac{V_o}{R}$$

Considering the steady state, the average voltage across the inductor is zero

$$\int_0^{T_s} v_L dt = 0 \quad \Rightarrow \quad \int_0^{t_{on}} v_L dt + \int_{t_{on}}^{T_s} v_L dt = 0 \quad \Rightarrow \quad V_d t_{on} - V_o t_{off} = 0$$

Finally, input-output voltage relation (transfer function) of a Boost converter is:

$$\frac{V_o}{V_d} = \frac{t_{on}}{t_{off}} = \frac{D}{1-D}$$

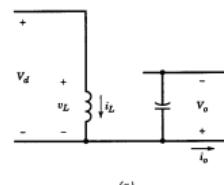
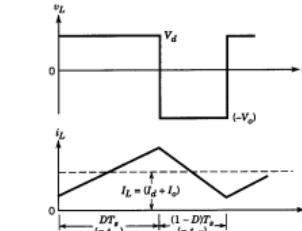


Figure 5 Buck-Boost Converter during CCM.

Neglecting the power losses:

$$P_d = P_o \Rightarrow V_d I_d = V_o I_o$$

$$\frac{I_o}{I_d} = \frac{V_d}{V_o} = \frac{1-D}{D}$$

BUCK-BOOST CONVERTER - BOUNDARY BETWEEN CCM AND DCM

At the boundary condition, inductor current goes to zero at the end of a period (note that $I_o = I_L - I_d = (1 - D)I_L$):

$$I_{LB} = \frac{1}{2}i_{L,peak} = \frac{V_d}{2L}t_{on} = \frac{T_s V_d}{2L}D = \frac{T_s V_o}{2L}(1 - D) \Rightarrow I_{oB} = \frac{T_s V_o}{2L}(1 - D)^2$$

With constant V_o , I_{oB} can be plotted as function of duty cycle D , and we can calculate::

$$I_{LB,max}(D = 0) = \frac{T_s V_o}{2L} \Rightarrow I_{LB} = (1 - D)I_{LB,max}, \quad I_{oB,max}(D = 0) = \frac{T_s V_o}{2L} \Rightarrow I_{oB} = (1 - D)^2 I_{oB,max}$$

For a given D with constant V_o : if I_o drops below I_{oB} (or I_L drops below I_{LB}) Buck-Boost converter changes its mode from CCM to DCM

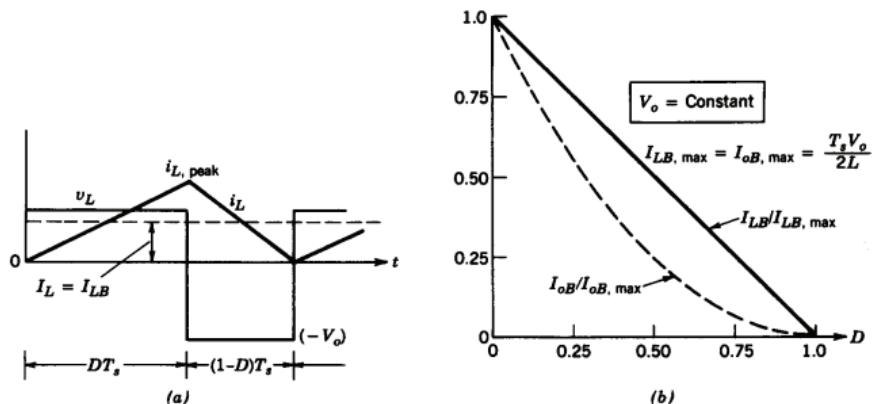


Figure 6 Current waveform at the boundary of CCM and DCM.

BUCK-BOOST CONVERTER - DCM - CONSTANT V_o

We assume that Buck-Boost converter:

- operates with constant V_d and D when a load decreases
- while D would be modified by control, we assume that is not changed
- decrease of load ($P_o = P_d$) reduces inductor average current
- t_{off} interval is split into two sub-intervals
- during $\Delta_1 T_s$ the inductor current is reducing to zero
- during $\Delta_2 T_s$ the inductor current/voltage is zero and load is supplied by capacitor

The average voltage across the inductor is zero

$$\int_0^{T_s} v_L dt = 0 \Rightarrow V_d DT_s + -V_o \Delta_1 T_s = 0 \Rightarrow \frac{V_o}{V_d} = \frac{D}{\Delta_1} = \frac{I_d}{I_o}$$

Inductor peak current and average currents are:

$$i_{L,peak} = \frac{V_d}{L} DT_s \Rightarrow I_L = i_{L,peak} \frac{D + \Delta_1}{2} = \frac{V_d}{2L} DT_s (D + \Delta_1)$$

Finally D as function of load current for various V_o/V_d is:

$$D = \frac{V_o}{V_d} \sqrt{\frac{I_o}{I_{oB,max}}}$$

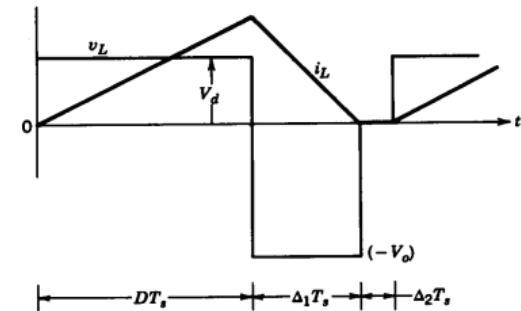


Figure 7 Buck-Boost Converter during DCM.

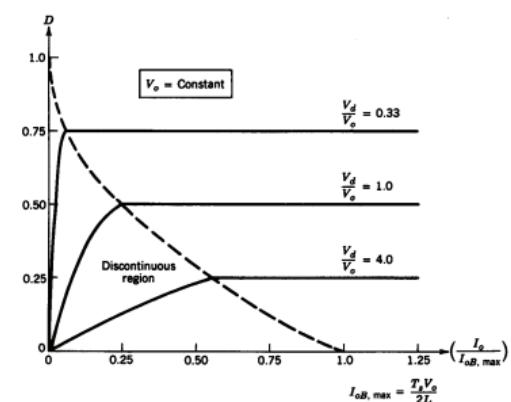


Figure 8 Buck-Boost characteristic with constant V_o .

BUCK-BOOST CONVERTER - INDUCTOR CURRENT RIPPLE - OUTPUT VOLTAGE RIPPLE

Considering the CCM operation, we can derive sizing rules for the L and C

During $t_{on} = DT_s$ interval, current rise for ΔI_L (peak-to-peak ripple)

$$\Delta I_L = \frac{V_d}{L} DT_s$$

Inductor average current is:

$$I_L = I_d + I_o = \frac{D}{1-D} I_o + I_o = \frac{1}{1-D} I_o = \frac{V_o}{R} \frac{1}{1-D} = \frac{V_d}{R} \frac{D}{(1-D)^2}$$

L can be selected as:

$$L = \frac{V_d}{\Delta I_L} DT_s = \frac{V_o}{\Delta I_L} (1-D)T_s$$

Output capacitor voltage ripple:

$$\Delta V_o = \frac{\Delta Q}{C} = \frac{I_o DT_s}{C} = \frac{V_o}{R} \frac{DT_s}{C}$$

From here we have:

$$\frac{\Delta V_o}{V_o} = \frac{DT_s}{RC} = \frac{DT_s}{\tau} \Rightarrow C = \frac{DT_s}{R} \frac{V_o}{\Delta V_o}$$

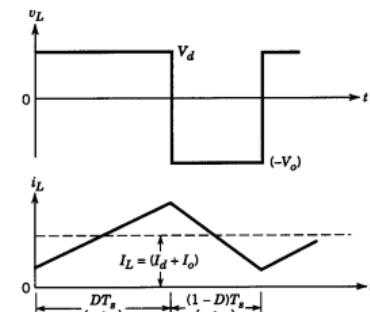


Figure 9 Buck-Boost converter inductor current ripple.

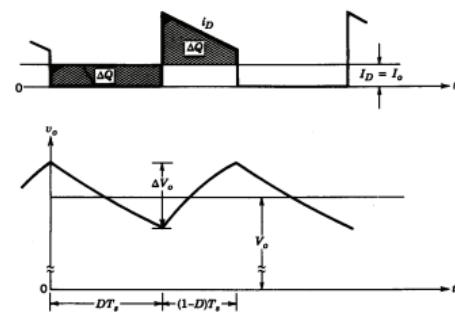


Figure 10 Buck-Boost converter output voltage ripple.

FLYBACK CONVERTER

Using coupled inductors and air-gap for energy exchange...

FLYBACK CONVERTER

Flyback converter is derived from the Buck-Boost converter

- ▶ second winding is added to the inductor to achieve galvanic isolation
- ▶ this is not truly a transformer, but a two-winding inductor (observe the dots and secondary diode)
- ▶ primary current and secondary current do not flow at the same time - as in regular transformer
- ▶ energy is stored in the air gap and released to the output
- ▶ two-winding inductor thus achieves energy storage and galvanic isolation, at the same time
- ▶ we can still analyse circuit using the transformer notion
- ▶ magnetizing inductance design will not aim for the highest possible value
- ▶ Flyback converter is widely used SMPS topology for low power applications

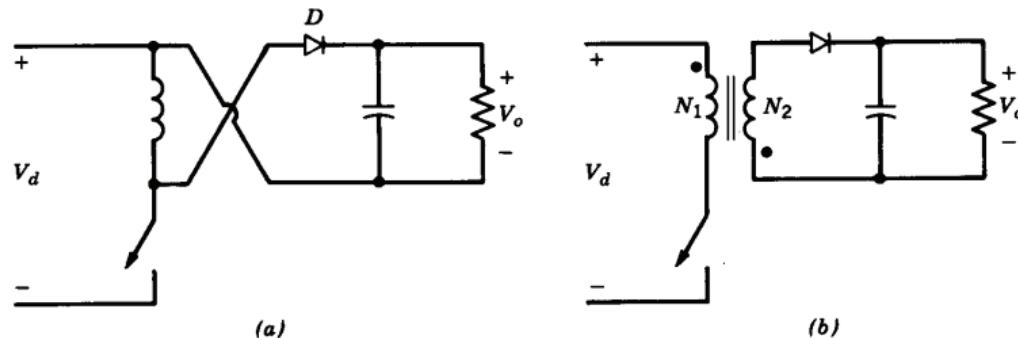


Figure 11 Flyback converter.

FLYBACK CONVERTER - CCM (I)

Using transformer representation for two winding inductor:

During the t_{on}

- ▶ Switch is ON
- ▶ Diode is OFF (reverse biased due to winding polarities)
- ▶ output capacitor is supplying the load
- ▶ CCM mode implies incomplete demagnetization of the core
- ▶ inductor core flux increases linearly from the initial value

$$\Phi(t) = \Phi(0) + \frac{V_d}{N_1} t \quad \Rightarrow \quad \hat{\Phi} = \Phi(t_{on}) = \Phi_0 + \frac{V_d}{N_1} t_{on}$$

During the t_{off}

- ▶ Switch is OFF and Diode is ON
- ▶ voltage across secondary winding is $v_2 = -V_o$
- ▶ energy is released to the secondary side
- ▶ inductor core flux decreases from the initial value

$$\Phi(t) = \hat{\Phi} - \frac{V_o}{N_2} (t - t_{on}) \quad \Rightarrow \quad \Phi(T_s) = \Phi_0 + \frac{V_d}{N_1} t_{on} - \frac{V_o}{N_2} (T_s - t_{on})$$

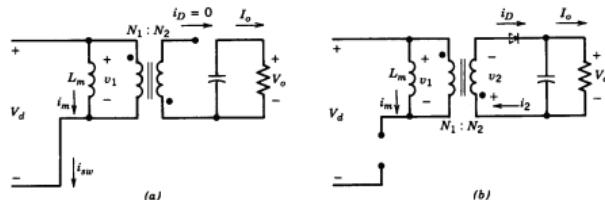


Figure 12 Flyback converter: a) switch ON; b) switch OFF.

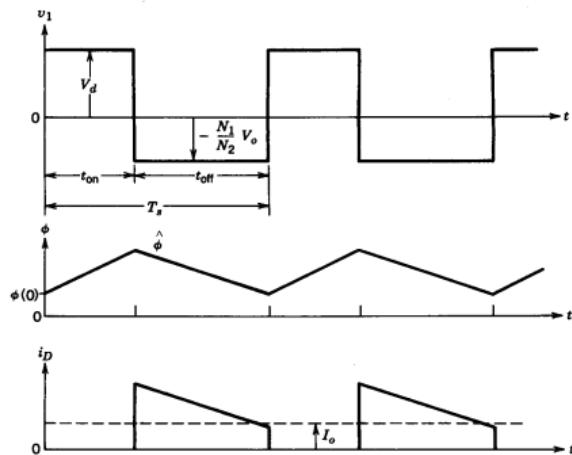


Figure 13 Flyback converter waveforms.

FLYBACK CONVERTER - CCM (II)

Considering that net change of flux through the core is zero in steady state:

$$\Phi(T_s) = \Phi(0) \Rightarrow \frac{V_o}{V_d} = \frac{N_2}{N_1} \frac{D}{1-D}$$

Voltage transfer ratio of Flyback converter:

- depends on duty cycle D as for Buck-Boost converter
- transformer turns ratio allow for additional voltage adaptation

During the t_{on} we have $v_1 = V_d$ and rise of inductor current:

$$i_m(t) = i_{sw}(t) = I_m(0) + \frac{V_d}{L_m} t \Rightarrow \hat{I}_m = \hat{I}_{sw} = I_m(0) + \frac{V_d}{L_m} t_{on}$$

During the t_{off} we have $v_1 = -(N_1/N_2)V_o$ and $i_{sw} = 0$

Inductor current i_m and diode current i_D can be expressed as:

$$i_m(t) = \hat{I}_m - \frac{V_o(N_1/N_2)}{L_m}(t - t_{on})$$

$$i_D(t) = \frac{N_1}{N_2} i_m(t) = \frac{N_1}{N_2} \left[\hat{I}_m - \frac{V_o(N_1/N_2)}{L_m}(t - t_{on}) \right]$$

With average diode current being I_o we have switch stresses as:

$$\hat{I}_m = \hat{I}_{sw} = \frac{N_2}{N_1} \frac{1}{1-D} I_o + \frac{N_1}{N_2} \frac{(1-D)T_s}{2L_m} V_o, v_{sw} = V_d + \frac{N_1}{N_2} V_o = \frac{V_d}{1-D}$$

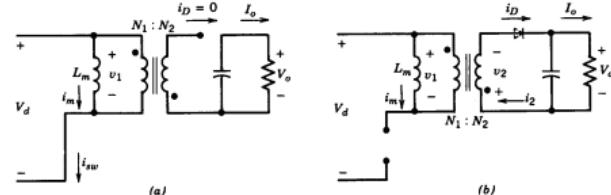


Figure 14 Flyback converter: a) switch ON; b) switch OFF.

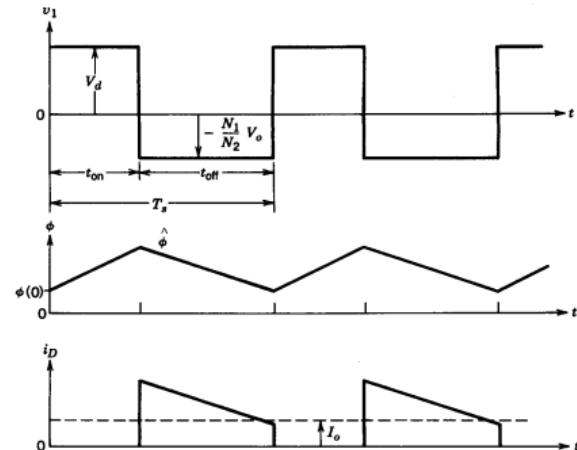


Figure 15 Flyback converter waveforms.

VOLTAGE TRANSFER FUNCTION, DUTY CYCLE RANGE

- ▶ Input-output voltage transfer function $\frac{U_{out}}{U_{in}} = f(D)$ of a Flyback converter is already derived
- ▶ it is easy to solve it for the duty cycle $D = f(U_{in}, U_{out})$
- ▶ IC PWM controller has limited maximum duty cycle
- ▶ Input voltage has minimum, rated and maximum value


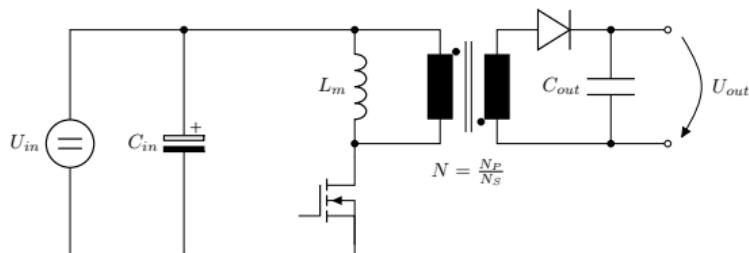


Figure 16 The power path of a Flyback Converter (leakage inductance and auxiliary supply windings are now shown).

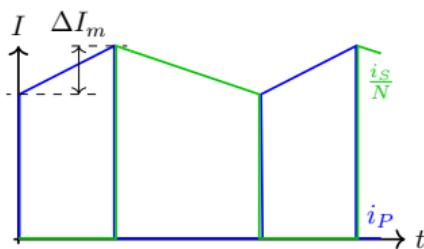

- ▶ Blue - Primary MOSFET current waveform
- ▶ Green - Secondary DIODE current waveform
- ▶ Magnetizing current - triangular current waveform with ripple ΔI_m
- ▶ While the structured looks like a transformer, these are coupled inductors

Figure 17 Current of the Flyback Converter.

MAGNETIZING INDUCTANCE, CCM, DCM

- ▶ Flyback should operate in CCM until $P_{out,min,CCM}$
- ▶ DCM operation below that power is OK
- ▶ Recall equations for primary side current (at CCM-DCM border it starts from zero)
- ▶ Recall simple geometry of a triangle - relation between average and peak value of current


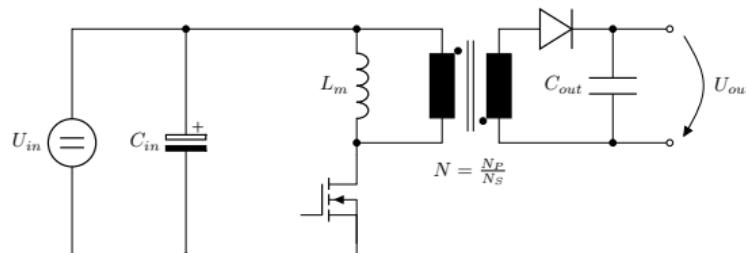


Figure 18 The power path of a Flyback Converter (leakage inductance and auxiliary supply windings are now shown).

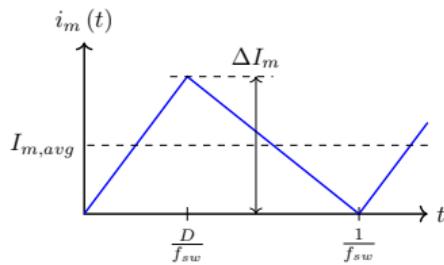

Magnetizing current peak and Average value are:

$$\Delta I_m = \frac{U_{in}}{L_m} \cdot t_{on} = \frac{U_{in}}{L_m} \cdot \frac{D}{f_{sw}} \quad I_{m,avg} = \frac{P_{out}}{U_{in}} \cdot \frac{1}{D}$$

L_m can be calculated considering current shape at the CCM-DCM border and:

$$\Delta I_m = 2 \cdot I_{m,avg}$$

Figure 19 Inductor current $i_m(t)$ at the border to discontinuous conduction mode.

OUTPUT CAPACITANCE

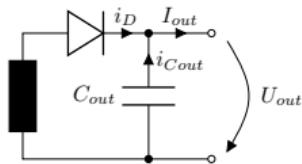


Figure 20 The secondary side with the relevant currents.

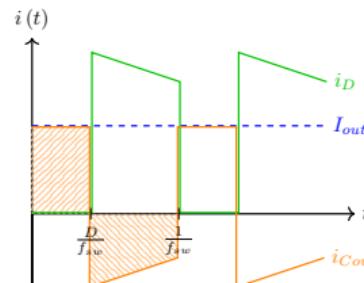


Figure 21 Kirchhoff's current law for the output capacitor.

- ▶ Output capacitance C_{out} should fulfill requested ripple requirements
- ▶ Worst operating conditions should be considered
- ▶ In the steady state, the capacitor voltage $u_{Cout} = \frac{1}{C_{out}} \cdot \int \{i_{Cout}\} dt$ has periodic ripple - net voltage gain should be zero
- ▶ voltage also has average value - output voltage
- ▶ Two shaded areas, representing charge, have to be identical - choose one

$$Q_{Cout,1} = I_{out} \cdot \frac{D}{f_{sw}} = \frac{P_{out}}{U_{out}} \cdot \frac{U_{out}/U_{in}}{U_{out}/U_{in} + 1/N} \cdot \frac{1}{f_{sw}}$$
$$C_{out} = \frac{Q_{Cout,1}}{\Delta U} = \frac{P_{out}}{U_{out}} \cdot \frac{U_{out}/U_{in}}{U_{out}/U_{in} + 1/N} \cdot \frac{1}{f_{sw} \cdot \Delta U_{out}}$$

- ▶ the charge Q - and thus the ripple - increase with P_{out} - Choose correctly power for design calculations!
- ▶ Input voltage U_{in} also has an effect on the C_{out} - Choose correctly input voltage for design calculations!
- ▶ You should fulfill requirements under all operating conditions

INPUT CAPACITANCE, HOLD-UP TIME, SAFETY DISCHARGE

DC-DC converters are often part of a larger power supply system connected to the AC supply through a rectifier

- ▶ input rectifier is connected to AC supply line ($50\text{ H}\mu\text{z}$) and provides DC voltage as input to DC-DC stage
- ▶ rectifier normally has Capacitor at the output, smoothing DC voltage at the input of DC-DC converter
- ▶ DC-DC stage regulates the output DC voltage, and operates correctly with defined input voltage range (V_{in-min}, V_{in-max})
- ▶ AC network may have problems, and there may be complete loss of AC power supply for some time
- ▶ often, a loss of a half-cycle (10 ms) of AC supply, should not be visible at the output of DC-DC converter
- ▶ **HOLD-UP** time is defined as the time required for the output voltage to remain within regulation after the AC input voltage is removed
- ▶ capacitor between AC-DC and DC-DC stage must be sized to buffer loss of AC supply during half-cycle ($t_{UP} = 10\text{ ms}$)
- ▶ Your task 1: **Calculate C** for scenario "adapted" for your problem (simplified problem, since efficiency is considered as 100%)
- ▶ Your task 2: **Calculate R** to discharge C, in defined time, once we turn off everything ($\tau = RC$, it takes roughly 5τ to discharge)

Energy stored in capacitor C at voltage V :

$$E = \frac{1}{2}CV^2$$

Energy difference in capacitor C due to voltage drop:

$$\Delta E = \frac{1}{2}C(V_{high}^2 - V_{low}^2)$$

Energy needed to supply output rated power:

$$\Delta E = P_{out} \cdot t_{UP}$$

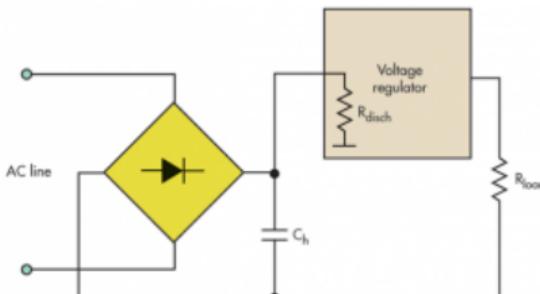


Figure 22 Simplified illustration of DC-DC converter fed from an AC-DC converter

MOSFET AND DIODE V-I STRESS, RMS AND AVG CALCULATIONS

Adequate MOSFET and DIODE should be selected considering: Expressions for RMS and AVERAGE current can be easily derived

- ▶ Maximum voltage stress of the MOSFET in the circuit
- ▶ Maximum current of the MOSFET in the circuit
- ▶ Maximum voltage stress of the DIODE in the circuit
- ▶ Maximum current stress of the DIODE in the circuit
- ▶ Calculate theoretically from the circuit
- ▶ Use PLECS to verify (if in doubt)
- ▶ Determined values are minimum requirements
- ▶ List of devices is provided to you
- ▶ Choose final devices accordingly

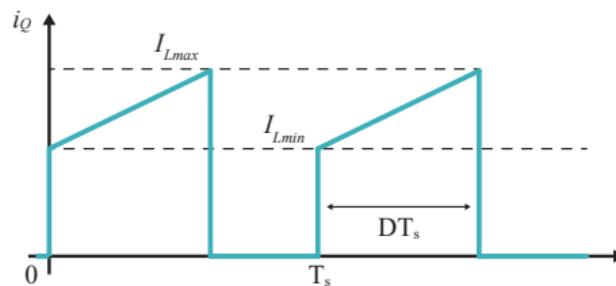


Figure 23 Current waveform of the MOSFET in the steady-state

- ▶ recall basic definition for RMS calculation

$$I_{rms} = \sqrt{\frac{1}{T_s} \int_0^{T_s} i^2(t) dt}$$

- ▶ recall basic definition for AVG calculation

$$I_{avg} = \frac{1}{T_s} \int_0^{T_s} i(t) dt$$

- ▶ from the typical current waveforms define $i(t)$ for MOSFET
- ▶ from the typical current waveforms define $i(t)$ for DIODE
- ▶ these calculations are available in many textbooks

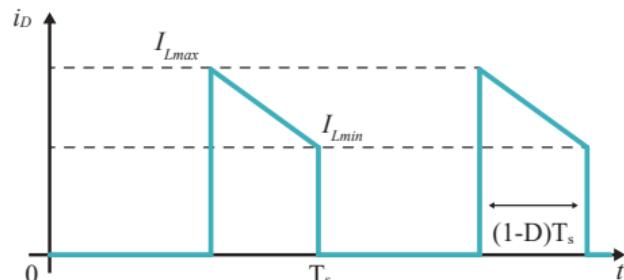


Figure 24 Current waveforms of the diode in the steady-state

OTHER FLYBACK CONVERTER TOPOLOGIES

Two-Switch Flyback Converter

- ▶ T_1 and T_2 are turned ON and OFF simultaneously
- ▶ voltage ratings of switches is one half of the the single-switch version
- ▶ diodes provide freewheeling path to dissipate energy stored in leakage inductance

Paralleling Flyback Converters

- ▶ added redundancy in the system
- ▶ increased effective switching frequency seen at the output
- ▶ modularity of design

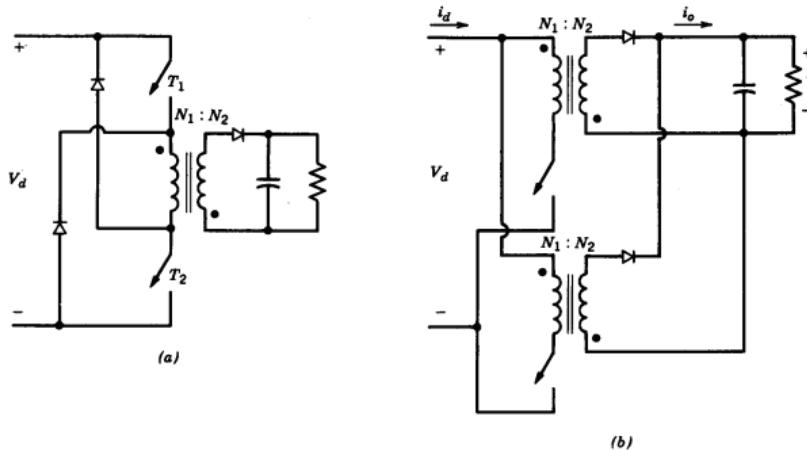


Figure 25 a) Two-switch Flyback converter; b) paralleled Flyback converters.

TWO-SWITCH FLYBACK CONVERTER

Minimizing the impact of leakage inductance

2-SWITCH FLYBACK CONVERTER

Single-switch Flyback suffers from:

- ▶ high turn-off voltage stress of primary switch
- ▶ ringing due to leakage inductance and switch output capacitance
- ▶ energy stored in the leakage inductance
- ▶ increased switching loss
- ▶ need for RCD clamp, further increasing complexity and losses

Two-switch Flyback:

- ▶ increased complexity: 2 MOSFETs, 2 Diodes
- ▶ diodes effectively clamp and reduce switching overvoltages
- ▶ diodes provide return path for the leakage inductance discharge
- ▶ MOSFET turn off loss is reduced

Material is adopted from the paper:

D. Murthy-Bellur, M.K. Kazimierczuk, "Two-switch flyback PWM DC-DC converter in continuous-conduction mode", Int. J. Circ. Theor. Appl. 2011; 39: 1145-1160


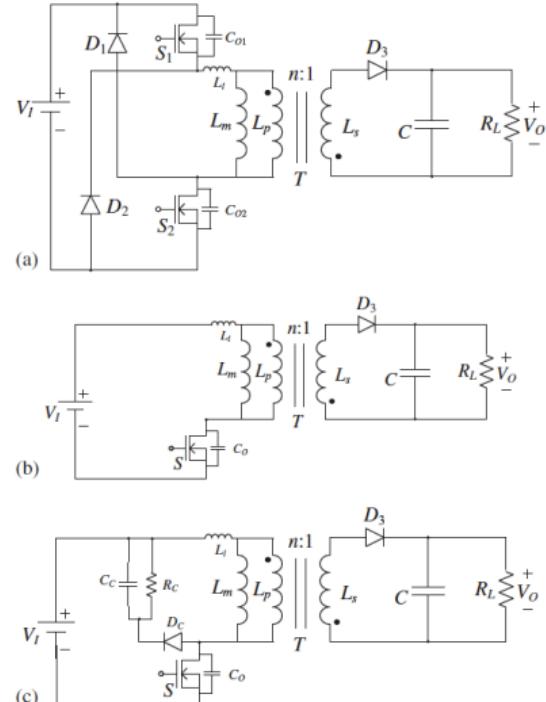


Figure 26 (a) two-switch flyback; (b) single-switch flyback;(c) single-switch flyback PWM DC-DC converter with RCD clamp.

2-SWITCH FLYBACK CONVERTER - CCM

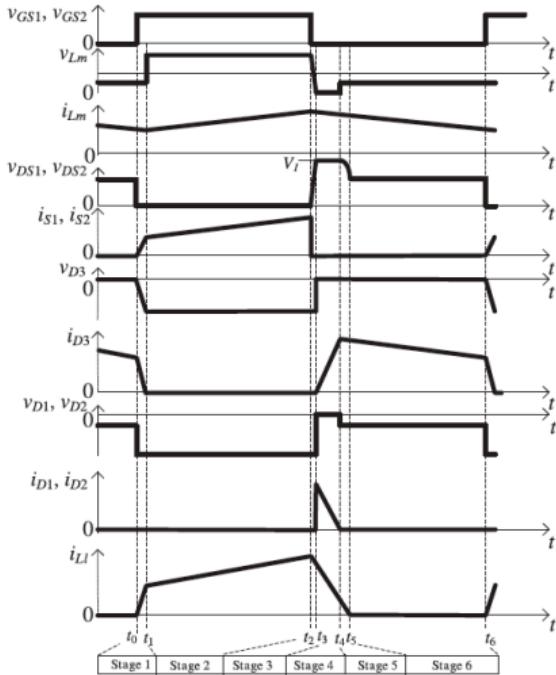Relevant waveforms in CCM in steady state



6 stages (intervals) during the switching period

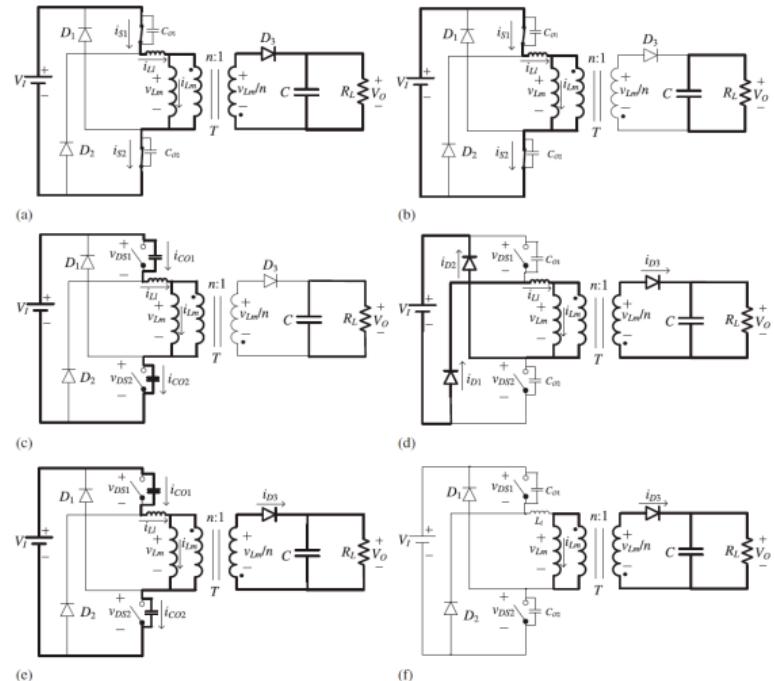


Figure 27 Voltage and current waveforms of the two-switch flyback in CCM

Figure 28 Equivalent circuits of the two-switch flyback

2-SWITCH FLYBACK CONVERTER - CCM

Nomenclature

- ▶ Active switches: S_1 and S_2
- ▶ Diodes: D_1 , D_2 and D_3
- ▶ Magnetizing inductance: L_m
- ▶ Total leakage inductance: L_l
- ▶ Output capacitor: C
- ▶ Output capacitance of switches: C_{O1} and C_{O2}
- ▶ Transformer turns ratio: n
- ▶ Input DC voltage: V_I
- ▶ Output DC voltage: V_O
- ▶ Load resistance: R_L
- ▶ Switching period: T_s

6 stages (intervals) during the switching period

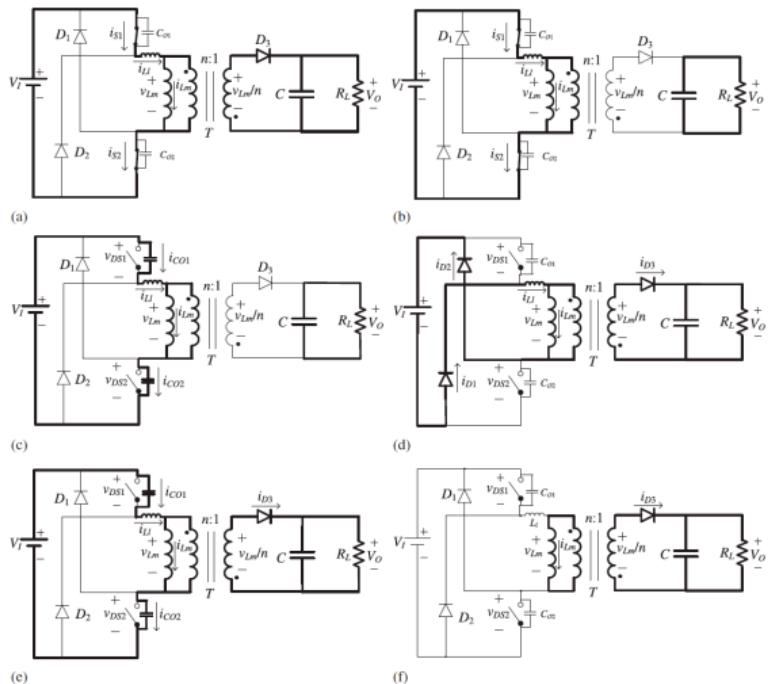


Figure 29 Equivalent circuits of the two-switch flyback

2-SWITCH FLYBACK CONVERTER - STAGE 1

During the time interval $[t_0 < t \leq t_1]$

- ▶ D_1 and D_2 are OFF, D_3 is ON (conducting) and S_1 and S_2 are turned ON
- ▶ due to leakage inductance L_l , magnetizing current i_{L_m} cannot be instantaneously transferred from the secondary to the primary
- ▶ voltage across clamping diodes D_1 and D_2 is: $v_{D1} = v_{D2} = -V_I$
- ▶ D_1 and D_2 are reversed biased (blocking), hence: $i_{D1}(t) = i_{D2}(t) = 0$
- ▶ the voltage across magnetizing inductance L_m is: $v_{L_m} = -nV_O$. Hence:

$$i_{L_m}(t) = \frac{nV_O}{L_m}(t - t_0) + i_{L_m}(t_0), \quad i_{L_m}(t_0) = \text{init.v.}(CCM)$$

- ▶ the voltage across leakage inductance L_l is $V_{L_l} = V_I + nV_O$
- ▶ the leakage inductance L_l limits the rise of current through S_1 and S_2

$$i_{S_1}(t) = i_{S_2}(t) = i_{L_l}(t) = \underbrace{\frac{V_I + nV_O}{L_l}(t - t_0)}_{\text{slope}} + i_{L_l}(t_0), \quad i_{L_l}(t_0) = 0$$

- ▶ the current through D_3 is:

$$i_{D_3}(t) = -n(i_{L_l}(t) - i_{L_m}(t)) = -n \frac{V_I L_m + nV_O(L_m + L_l)}{L_m L_l}(t - t_0) + n i_{L_m}(t_0)$$

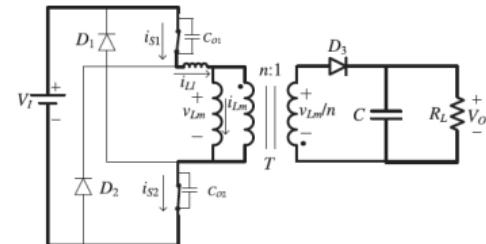


Figure 30 Equivalent circuit during the Stage 1

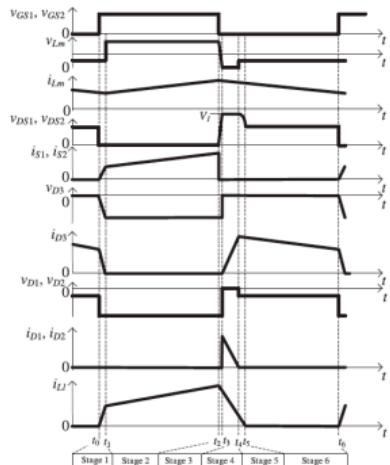


Figure 31 Voltage and current waveforms...
Power Electronics Laboratory | 24 of 32

2-SWITCH FLYBACK CONVERTER - STAGE 1 (CONT.)

During the time interval $[t_0 < t \leq t_1]$

- the current through D_3 is:

$$i_{D_3}(t) = -n(i_{L_l}(t) - i_{L_m}(t)) = -n \frac{V_I L_m + nV_O(L_m + L_l)}{L_m L_l} (t - t_0) + n i_{L_m}(t_0)$$

- in a good design $L_m \gg L_l$ and simplification yields:

$$i_{D_3}(t) = -n \underbrace{\frac{V_I + nV_O}{L_l} (t - t_0)}_{\text{slope}} + n i_{L_m}(t_0)$$

- the voltages across switches are: $v_{S_1} = v_{S_2} = 0$
- the stage 1 ends at the time $t = t_1$ when the $i_{L_l} = i_{L_m}$ and $i_{D_3}(t) = 0$
- substituting $i_{D_3}(t_1) = 0$ into simplified expression yields duration of the stage as:

$$\Delta t_1 = t_1 - t_0 = \frac{L_l}{V_I + nV_O} i_{L_m}(t_0)$$

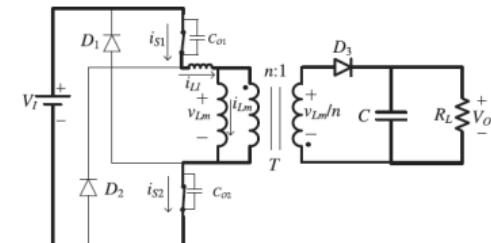


Figure 32 Equivalent circuit during the Stage 1

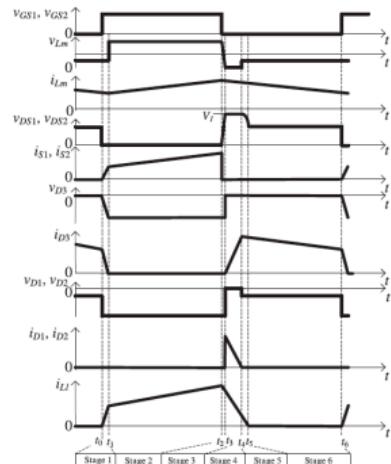


Figure 33 Voltage and current waveforms...
Power Electronics Laboratory | 25 of 32

2-SWITCH FLYBACK CONVERTER - STAGE 2

During the time interval $[t_1 < t \leq t_2]$

- ▶ S_1 and S_2 are ON; all diodes D_1 , D_2 and D_3 are OFF
- ▶ the output load R_L is supplied by the output capacitor C
- ▶ the voltages across switches are: $v_{S1} = v_{S2} = 0$
- ▶ the primary side current is:

$$i_{S1}(t) = i_{S2}(t) = i_{Ll}(t) = i_{Lm}(t) = \underbrace{\frac{V_I}{L_m + L_l}}_{\text{slope}}(t - t_1) + i_{Lm}(t_1)$$

- ▶ the peak current of the magnetizing inductance L_m is:

$$i_{Lm}(t_2) = \frac{V_I D T_s}{L_m + L_l} + i_{Lm}(t_1) = \frac{V_I D}{f_s(L_m + L_l)} + i_{Lm}(t_1)$$

- ▶ the peak-to-peak value of the ripple current through magnetizing inductance is

$$\Delta i_{Lm} = i_{Lm}(t_2) - i_{Lm}(t_1) = \frac{V_I D}{f_s(L_m + L_l)}$$

- ▶ the stage 2 ends at the time $t = t_2$ when both switches S_1 and S_2 are turned OFF

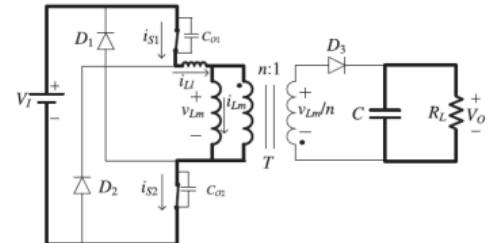


Figure 34 Equivalent circuit during the Stage 2

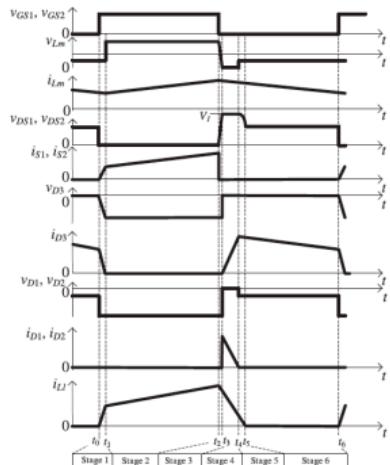


Figure 35 Voltage and current waveforms...

2-SWITCH FLYBACK CONVERTER - STAGE 3

During the time interval $[t_2 < t \leq t_3]$

- ▶ S_1, S_2, D_1, D_2 and D_3 are all OFF; the R_L is supplied by the output capacitor C
- ▶ the magnetizing current (equal to leakage current) is charging output capacitances C_{O1} and C_{O2} of primary switches S_1 and S_2
- ▶ an LC resonant circuit is formed due to opening of switches S_1 and S_2
- ▶ the primary side current is:

$$i_{CO1}(t) = i_{CO2}(t) = i_{Ll}(t) = i_{Lm}(t) = \frac{V_I}{Z_1} \sin \omega_1(t - t_2) + i_{Lm}(t_2) \cos \omega_1(t - t_2)$$

- ▶ where:

$$Z_1 = \sqrt{\frac{(L_m + L_l)(C_{O1} + C_{O2})}{C_{O1}C_{O2}}} \quad \omega_1 = \sqrt{\frac{C_{O1} + C_{O2}}{(L_m + L_l)C_{O1}C_{O2}}}$$

- ▶ assuming identical output capacitances $C_{O1} = C_{O2} = C_O$, the switch voltages are:

$$v_{DS1}(t) = v_{DS2}(t) = v_{CO1}(t) = v_{CO2}(t) = \frac{i_{Lm}(t_2)Z_1}{2} \sin \omega_1(t - t_2) + \frac{V_I}{2}(t_2) \cos \omega_1(t - t_2)$$

- ▶ the stage 3 ends at the time $t = t_3$ when the voltage across each switch S_1 and S_2 equals V_I , resulting in clamping diodes D_1, D_2 (and D_3) being turned ON

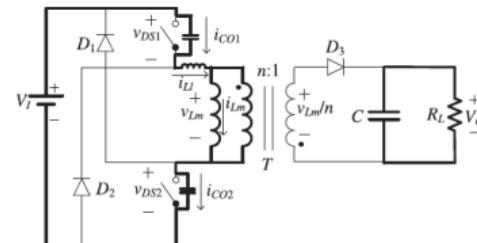


Figure 36 Equivalent circuit during the Stage 3

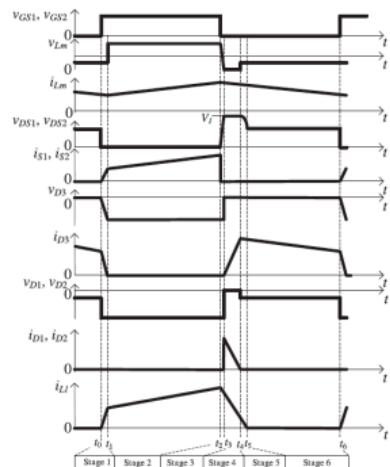


Figure 37 Voltage and current waveforms...
Power Electronics Laboratory | 27 of 32

2-SWITCH FLYBACK CONVERTER - STAGE 4

During the time interval $[t_3 < t \leq t_4]$

- ▶ S_1, S_2 are OFF, all diodes D_1, D_2 and D_3 are ON
- ▶ the voltage across each switch is clamped to $V_I + V_F$, where V_F is the forward voltage drop across the clamping diode
- ▶ the current through the leakage inductance is charging the input voltage source V_I through the diodes D_1 and D_2

$$i_{D1}(t) = i_{D2}(t) = i_{L_l}(t) = \underbrace{\frac{V_I - nV_O}{L_l}}_{\text{slope}}(t - t_3) + i_{L_l}(t_3)$$

- ▶ where $i_{L_l}(t_3)$ is the initial leakage inductance current
- ▶ this is regenerative clamping mode
- ▶ the stage 4 ends at the time $t = t_4$ when the rectifier diode current $i_{D3}(t)$ equals the reflected magnetizing current nI_{L_m} , which results in diodes D_1 and D_2 being turned OFF

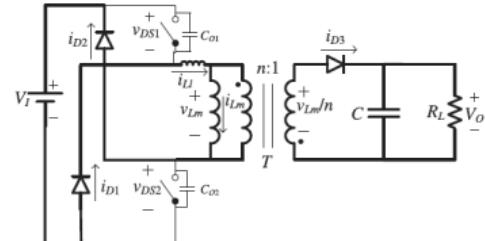


Figure 38 Equivalent circuit during the Stage 4

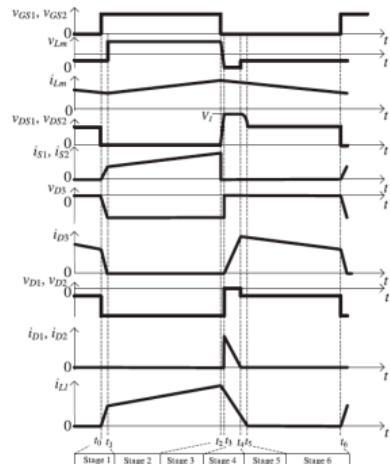


Figure 39 Voltage and current waveforms...
Power Electronics Laboratory | 28 of 32

2-SWITCH FLYBACK CONVERTER - STAGE 5

During the time interval $[t_4 < t \leq t_5]$

- ▶ S_1, S_2, D_1 , and D_2 are all OFF; D_3 is ON
- ▶ the magnetizing inductance L_m is clamped due to conduction of D_3
- ▶ the resonant current on the primary is:

$$i_{L_l}(t) = i_{CO1}(t) = i_{CO2}(t) = i_{L_l}(t_4) \cos \omega_2(t - t_4)$$

- ▶ where $i_{L_l}(t_4)$ is the initial leakage inductance current
- ▶ the voltage across the leakage inductance L_l is

$$v_{L_l}(t) = -i_{L_l}(t_4)Z_2 \sin \omega_2(t - t_4)$$

$$Z_2 = \sqrt{\frac{L_l(C_{O1} + C_{O2})}{C_{O1}C_{O2}}} \quad \omega_2 = \sqrt{\frac{C_{O1} + C_{O2}}{L_lC_{O1}C_{O2}}}$$

- ▶ assuming identical output capacitances $C_{O1} = C_{O2} = C_O$, the switch voltages are:

$$v_{DS1}(t) = v_{DS2}(t) = v_{CO1}(t) = v_{CO2}(t) = V_I - i_{L_l}(t_4) \sin \omega_2(t - t_4)$$

- ▶ the stage 5 ends at the time $t = t_5$ when the leakage currents $i_{L_l}(t)$ drops to zero

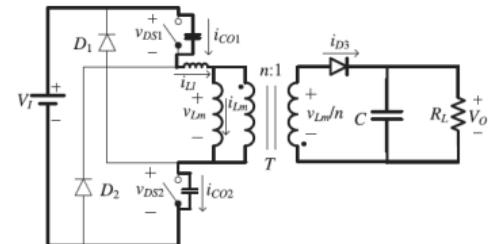


Figure 40 Equivalent circuit during the Stage 5

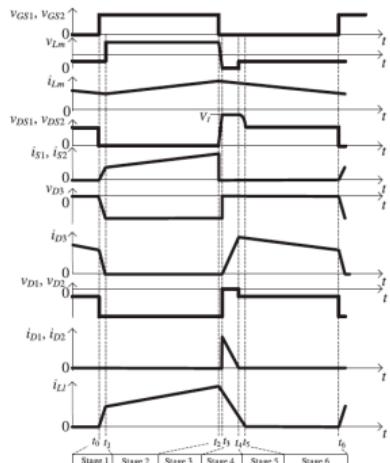


Figure 41 Voltage and current waveforms...

2-SWITCH FLYBACK CONVERTER - STAGE 6

During the time interval $[t_5 < t \leq t_6]$

- ▶ S_1, S_2, D_1 and D_2 are OFF, D_3 is ON
- ▶ resonance between L_l , C_{O1} and C_{O2} has stopped
- ▶ the voltage across magnetizing inductance L_m is: $v_{L_m} = -nV_O$
- ▶ Magnetizing current and rectifier diode D_3 current are:

$$i_{L_m}(t) = -\underbrace{\frac{nV_O}{L_m}(t - t_5)}_{\text{slope}} + i_{L_m}(t_5), \quad i_{D_3}(t) = -\underbrace{\frac{n^2V_O}{L_m}(t - t_5)}_{\text{slope}} + ni_{L_m}(t_5)$$

- ▶ the voltages across the switches S_1 and S_2 , and clamping diodes D_1 and D_2 are:

$$v_{DS1}(t) = v_{DS2}(t) = \frac{V_I + nV_O}{2} \quad v_{D1}(t) = v_{D2}(t) = \frac{nV_O - V_I}{2}$$

- ▶ there are no currents on the primary side
- ▶ the stage 6 ends at the time $t = t_6$ when the switches S_1 and S_2 are turned ON

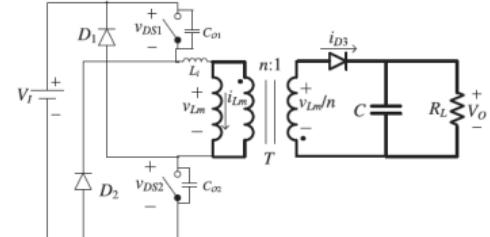


Figure 42 Equivalent circuit during the Stage 6

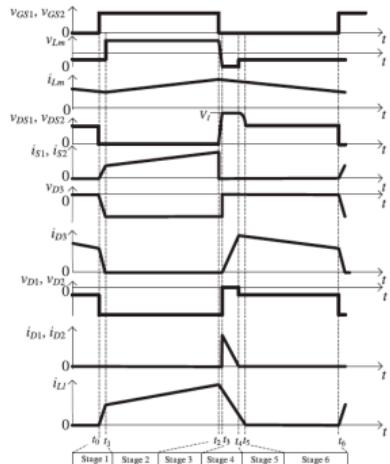


Figure 43 Voltage and current waveforms...
Power Electronics Laboratory | 30 of 32

DC VOLTAGE TRANSFER FUNCTION

Relevant waveforms in CCM in steady state

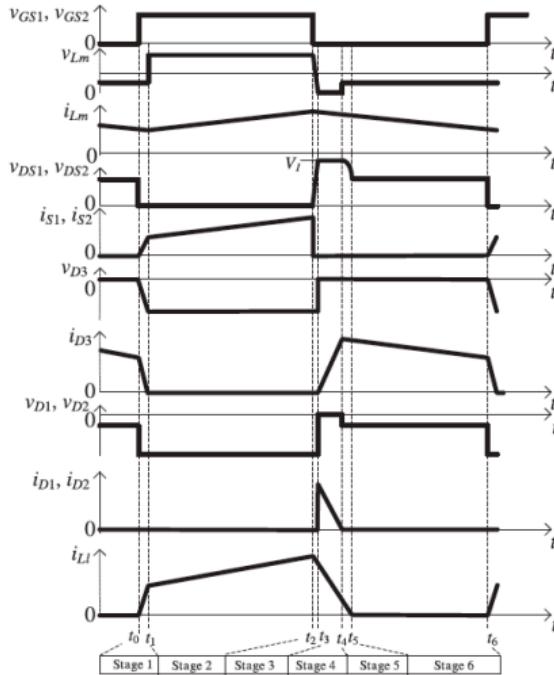


Figure 44 Voltage and current waveforms of the two-switch flyback in CCM

Input-output voltage relation:

- ▶ Applying the volt-second balance to the magnetizing inductance voltage

$$0 = V_I(\Delta t_2 - \Delta t_3 - \Delta t_4) - nV_O(\Delta t_1 + \Delta t_5 + \Delta t_6)$$

$$\frac{V_O}{V_I} = \frac{\Delta t_2 - \Delta t_3 - \Delta t_4}{n(\Delta t_1 + \Delta t_5 + \Delta t_6)}$$

- ▶ neglecting duration of stages 1, 3, 4, and 5, as it is typically much smaller in comparison to duration of stages 2 and 6, one has:

$$\frac{V_O}{V_I} = \frac{\Delta t_2}{n\Delta t_6} = \frac{D}{n(1-D)}$$

- ▶ the same voltage transfer function as for the single switch flyback

DEVICE STRESSES

Relevant waveforms in CCM in steady state

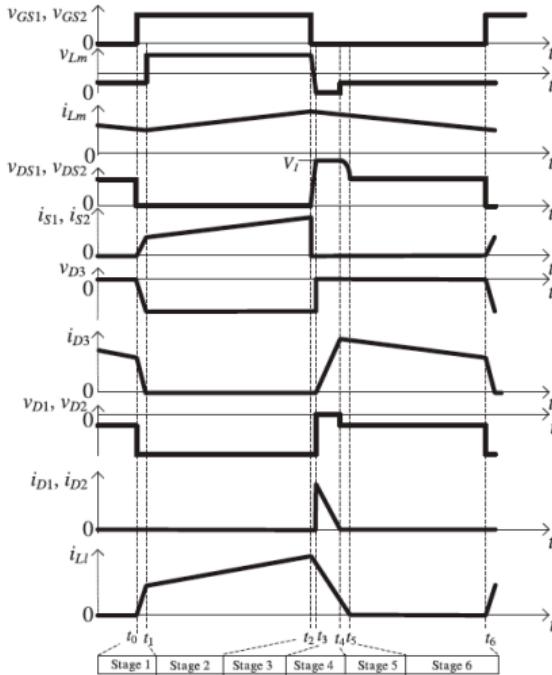


Figure 45 Voltage and current waveforms of the two-switch flyback in CCM

Primary side switches S_1 and S_2

- ▶ maximum voltage appears during the stage 4
- ▶ maximum current appears during the stage 2

$$V_{S1,2(max)} = V_{I(max)}, \quad I_{S1,2(max)} = \frac{I_{Omax}}{n(1 - D_{max})} + \frac{\Delta I_{Lm}}{2}$$

Clamping diodes D_1 and D_2

- ▶ maximum voltage appears during the stage 1 and 2
- ▶ maximum current appears during the stage 4

$$V_{D1,2(max)} = V_{I(max)}, \quad I_{D1,2(max)} = \frac{I_{Omax}}{n(1 - D_{max})} + \frac{\Delta I_{Lm}}{2}$$

Rectifier diode D_3

- ▶ maximum voltage appears during the stage 2
- ▶ maximum current appears during the stage 4

$$V_{D3(max)} = \frac{V_I}{n} + V_O, \quad I_{D3(max)} = \frac{I_{Omax}}{1 - D_{max}} + \frac{n\Delta I_{Lm}}{2}$$