

SOLUTION SET V

EXERCISE V.1 : RLC CIRCUIT IN SINUSOIDAL REGIME

The impedance of the serial RLC circuit has been established in Exercise II.1:

$$\underline{Z} = R + j \frac{\omega_k^2 LC - 1}{\omega_k C} \quad \text{with : } \omega_k = 2 \pi f_k$$

The rms value of the current, I , and the power factor, $\cos\phi$, are given by relationships:


$$I = \frac{U}{|\underline{Z}|} \quad \text{and} \quad \cos\phi = \cos(\arg(\underline{Z}))$$

The results obtained for the two frequencies are summarized in the table below :

| f [Hz] | $\underline{Z} [\Omega]$ | $\arg(\underline{Z}) [^\circ]$ | $I [A]$ | $\cos\phi$ | Nature of the impedance |
|---------------|--|--|---------------------------|------------------------------|--------------------------------|
| 1000 | 13,88 | - 43,93 | 7,20 | 0,72 | capacitive |
| 2000 | 11,01 | 24,74 | 9,08 | 0,91 | inductive |

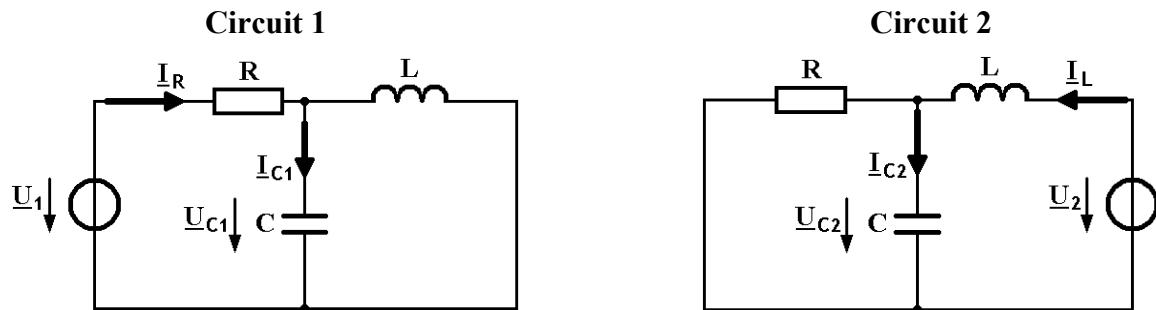EXERCISE V.2 : SUPERPOSITION IN SINUSOIDAL REGIME

The superposition principle allows to break down the studied circuit into two circuits :



In circuit 1, the equivalent impedance \underline{Z}_1 is written (case 3 of Exercise II.1) :

$$\underline{Z}_1 = R + j \frac{\omega_1 L}{1 - \omega_1^2 LC}$$

Currents and voltages will be given by:

$$I_R = \frac{U_1}{\underline{Z}_1} ; \quad U_{C1} = U_1 - R \cdot I_R ; \quad I_{C1} = U_{C1} j \omega_1 C$$

Numerical application :

$$\underline{U}_1 = 100 \cdot e^{j90^\circ} \text{ V} ; \quad \underline{Z}_1 = 31,48 \cdot e^{j17,66^\circ} \Omega$$

$$\Rightarrow \underline{I}_R = 3,18 \cdot e^{j72,33^\circ} \text{ A} = (0,964 + j3,03) \text{ A}$$

$$\Rightarrow \underline{U}_R = R \cdot \underline{I}_R = 95,3 \cdot e^{j72,33^\circ} \quad \underline{U}_{C1} = \underline{U}_1 - \underline{U}_R = 30,34 \cdot e^{j162,34^\circ} \text{ V}$$

$$\Rightarrow \underline{I}_{C1} = \underline{U}_{C1} / \underline{Z}_{C1} = \underline{U}_{C1} \cdot j\omega_1 C = 2,86 \cdot e^{-j107,66^\circ} \text{ A}$$

In circuit 2, the equivalent impedance \underline{Z}_2 is written (case 4 of Exercise II.1) :

$$\underline{Z}_2 = \frac{R + j\omega_2(\omega_2^2 R^2 L C^2 + L - R^2 C)}{1 + (\omega_2 R C)^2}$$

Currents and voltages will be given by:

$$\underline{I}_L = \frac{\underline{U}_2}{\underline{Z}_2} ; \quad \underline{U}_{C2} = \underline{U}_2 - j\omega_2 L \cdot \underline{I}_L ; \quad \underline{I}_{C2} = \underline{U}_{C2} j\omega_2 C$$

Numerical application :

$$\underline{U}_2 = 100 \cdot e^{j90^\circ} \text{ V} ; \quad \underline{Z}_2 = 4,99 \cdot e^{j79,50^\circ} \Omega$$

$$\Rightarrow \underline{I}_L = 20,03 \cdot e^{j10,50^\circ} \text{ A} = (19,7 - j3,65) \text{ A} ;$$

$$\underline{U}_{C2} = (36,69 - j98,0) \text{ V} = 104,64 \cdot e^{j69,47^\circ} \text{ V}$$

$$\Rightarrow \underline{I}_{C2} = 19,72 \cdot e^{j20,53^\circ} \text{ A}$$

At this point, it is time to remember that we can not add two phasors of different frequencies: only the instantaneous values add up in such a case. We will write (with the angles in radians) :

$$\left. \begin{aligned} u_{c1}(t) &= |\underline{U}_{C1}| \sqrt{2} \cos(\omega_1 \cdot t + \arg(\underline{U}_{C1})) = \underline{42,9 \cos(314,2 \cdot t + 2,827)} \text{ V} \\ u_{c2}(t) &= |\underline{U}_{C2}| \sqrt{2} \cos(\omega_2 \cdot t + \arg(\underline{U}_{C2})) = \underline{148,0 \cos(628,3 \cdot t - 1,212)} \text{ V} \\ i_{c1}(t) &= |\underline{I}_{C1}| \sqrt{2} \cos(\omega_1 \cdot t + \arg(\underline{I}_{C1})) = \underline{4,04 \cos(314,2 \cdot t - 1,879)} \text{ A} \\ i_{c2}(t) &= |\underline{I}_{C2}| \sqrt{2} \cos(\omega_2 \cdot t + \arg(\underline{I}_{C2})) = \underline{27,89 \cos(628,3 \cdot t + 0,358)} \text{ A} \end{aligned} \right\} \begin{aligned} u_c(t) &= u_{c1}(t) + u_{c2}(t) \\ i_c(t) &= i_{c1}(t) + i_{c2}(t) \end{aligned}$$

Graphically, we obtain the results below:

