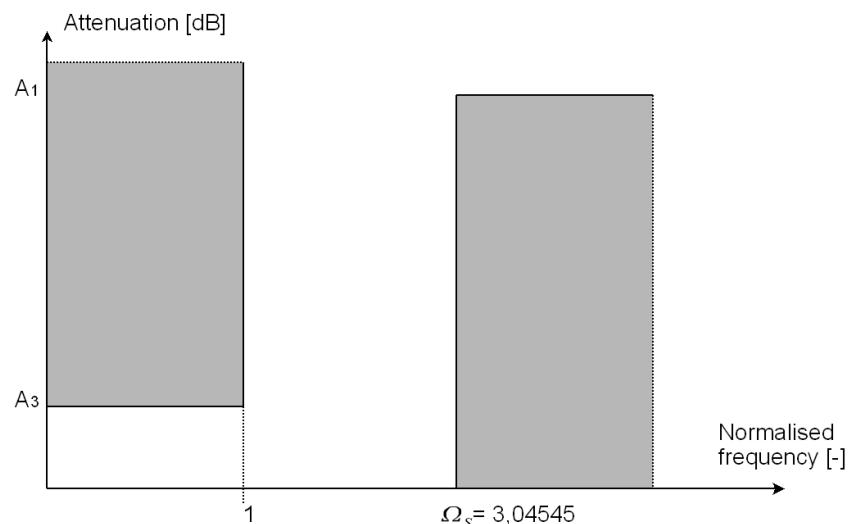


Corrections of Serie 8:
Determination of the L and C components of a Chebyshev filter

a) The specifications of the low-pass filter with respect to the attenuation are given below :


Pass-band : $A_3 = 1$ dB ; Stop-band: $A_1 = 30$ dB



Calculate the L and C components of the Chebyshev low-pass filter. The topology with two parallel capacitors and one series inductor is chosen. The resistor R_s of the voltage source is equal to 1 Ohm.

Answer:

The topology with two parallel capacitors and one series inductor for the 3rd order low-pass Chebyshev filter is drawn below.

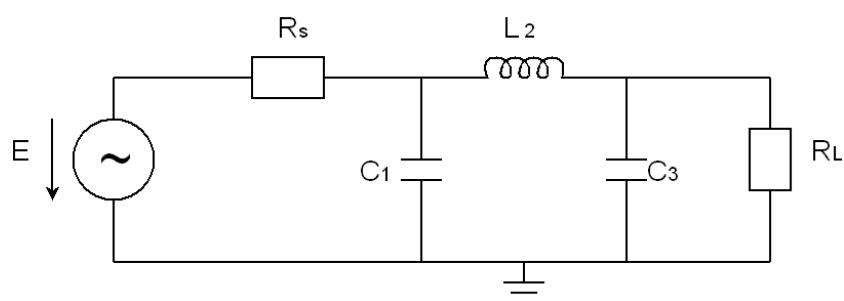

Serie 8:

Determination of the L and C components of a Chebyshev filter- Chap. 4

Winter semester 2015-2016

Prof. Catherine Dehollain

Page 1 sur 4

We calculate the L and C components value by following the procedure described in page 4-22 of the course. We first need to calculate the h and ξ constants value as follows :

$$h = \frac{1}{\varepsilon} + \sqrt{1 + \frac{1}{\varepsilon^2}}^{1/N} = \frac{1}{0.50885} + \sqrt{1 + \frac{1}{0.50885^2}}^{1/3} \approx 1.60961$$

and

$$\xi = h - \frac{1}{h} = 1.60961 - \frac{1}{1.60961} \approx 0.9883$$

The normalized values of the components are given by relations (4.26), (4.27) and (4.28) of the course.

Note that the components values are not expressed in F and H but in $F \cdot rad/s$ and $H \cdot rad/s$ because of the frequency normalization (see the x-axis of the specifications with respect to attenuation on page 1). Since R_s is equal to 1Ω , we have :

$$C_1 = \frac{4\sin \frac{\pi}{2N}}{\xi R_s} = \frac{4\sin \frac{\pi}{6}}{0.9883 \cdot 1} \approx 2.0236 F \cdot rad/s$$

Setting $k = 1$ in the first relation (4.27) gives :

$$L_2 = \frac{1}{C_1} \cdot \frac{16\sin \frac{\pi}{6} \sin \frac{3\pi}{6}}{\xi^2 + 2\sin \frac{\pi}{3}^2} = \frac{1}{2.0236} \cdot \frac{16 \cdot 0.5 \cdot 1}{0.9883^2 + 2 \cdot \frac{\sqrt{3}}{2}^2} \approx 0.9941 H \cdot rad/s$$

Setting $k = 1$ in the second relation (4.27) gives :

$$C_3 = \frac{1}{L_2} \cdot \frac{16\sin \frac{3\pi}{6} \sin \frac{5\pi}{6}}{\xi^2 + 2\sin \frac{2\pi}{3}^2} = \frac{1}{0.9941} \cdot \frac{16 \cdot 1 \cdot 0.5}{0.9883^2 + 2 \cdot \frac{\sqrt{3}}{2}^2} \approx 2.0236 F \cdot rad/s$$

Since we finish the filter by a capacitor, we calculate the load resistance with the first relation (4.28) as follows :

$$C_N = \frac{4\sin \frac{\pi}{2N}}{\xi R_L} \Rightarrow R_L = \frac{4\sin \frac{\pi}{2N}}{\xi C_N} = \frac{4\sin \frac{\pi}{6}}{0.9883 \cdot 2.0236} = 1 \Omega$$

Note that resistances are expressed in Ohm since they are not affected by the frequency normalization.

Serie 8:

Determination of the L and C components of a Chebyshev filter- Chap. 4

Winter semester 2015-2016

Prof. Catherine Dehollain

Page 2 sur 4

b)

Calculate the L and C components of the Chebyshev band-pass filter associated to the low pass filter whose components have been calculated in a). It is recalled that this band-pass filter will fulfill the specifications determined in question a) of Serie 7.

Answer:


As we have calculated the low-pass filter components values, we can now apply the low-pass to band-pass transformation described in page 4-11. In serie 7, we obtained :

$$B = 2\pi(f_4 - f_3) = 2\pi 10\text{kHz} \approx 62.832 \text{ k rad/s}$$

and

$$\omega_0 = 2\pi f_0 = 2\pi 454.9725\text{kHz} \approx 2.8587 \text{ M rad/s}$$

The pass-band filter is as follows :

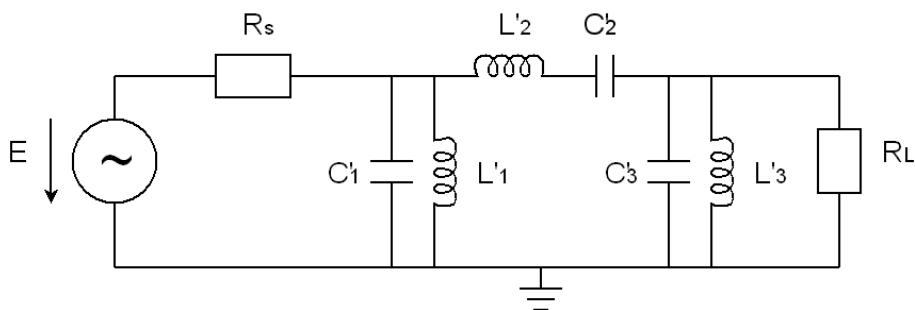

where the components values are given by the following relations :

$$C'_1 = \frac{C_1}{B} = \frac{2.0236 \text{ F} \cdot \text{rad/s}}{62'832 \text{ rad/s}} = 32.2 \mu\text{F}$$

$$C_1 \Rightarrow \{$$

$$L'_1 = \frac{B}{\omega_0^2 \cdot C_1} = \frac{62.832 \text{ k rad/s}}{(2.8587 \text{ M rad/s})^2 \cdot 2.0236 \text{ F} \cdot \text{rad/s}} = 3.7994 \text{ nH}$$

$$L'_2 = \frac{L_2}{B} = \frac{0.9941 \text{ H} \cdot \text{rad/s}}{62'832 \text{ rad/s}} = 15.82 \mu\text{H}$$

$$L_2 \Rightarrow \{$$

$$C'_2 = \frac{B}{\omega_0^2 \cdot L_2} = \frac{62.832 \text{ k rad/s}}{(2.8587 \text{ M rad/s})^2 \cdot 0.9941 \text{ H} \cdot \text{rad/s}} = 7.734 \text{ nF}$$

Serie 8:

Determination of the L and C components of a Chebyshev filter- Chap. 4

Winter semester 2015-2016

Prof. Catherine Dehollain

Page 3 sur 4

$$C'_3 = \frac{C_3}{B} = \frac{2.0236 F \cdot rad/s}{62'832 rad/s} = 32.2 \mu F$$

$$C_3 \Rightarrow \{$$

$$L'_3 = \frac{B}{\omega_0^2 \cdot C_3} = \frac{62.832 k rad/s}{(2.8587 M rad/s)^2 \cdot 2.0236 F \cdot rad/s} = 3.7994 nH$$

c)

Draw the gain in dB of the band-pass filter whose components have been calculated in b).

Answer:


The low-pass to band-pass transformation is given by : $s = \frac{p^2 + \omega_0^2}{p \cdot B}$

wheres $= j\Omega$ and $p = j\omega$. We thus have :

$$j\Omega = \frac{-\omega^2 + \omega_0^2}{j\omega \cdot B} = -j \frac{-\omega^2 + \omega_0^2}{\omega \cdot B} = -j \frac{(\omega_0^2 - \omega^2)}{\omega \cdot B} \Rightarrow \Omega = - \left(\frac{\omega_0^2 - \omega^2}{\omega \cdot B} \right)$$

So the gain of the filter in dB is expressed as : $20\log|H(j\omega)| = 20\log \frac{1}{\sqrt{1 + \varepsilon^2 C_3^2(\Omega)}}$

with $C_3(\Omega) = 4\Omega^3 - 3\Omega$. This gives the following transfer function:

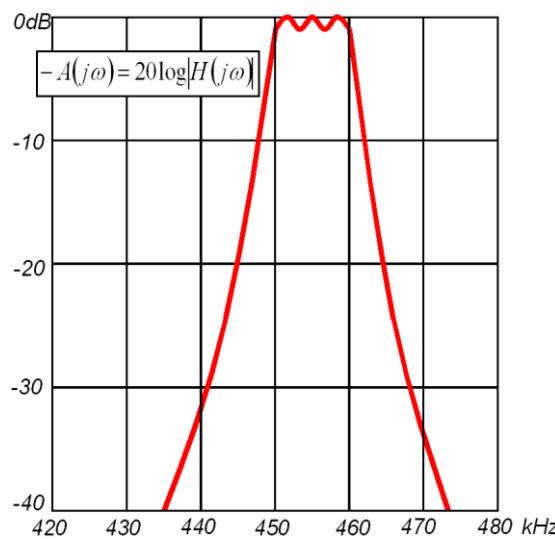

Serie 8:

Determination of the L and C components of a Chebyshev filter- Chap. 4

Winter semester 2015-2016

Prof. Catherine Dehollain

Page 4 sur 4