

## Serie 11

### Noise Figure, Power Gain and Noise Temperature of an Amplifier

---

- The temperature  $T$  is equal to 290 Kelvin.
- We do the assumption that the power gain of each amplifier is constant on the frequency bandwidth  $B = 100$  kHz and equal to zero outside this bandwidth  $B$ .
- We do the assumption that the noise factor of each amplifier is constant on the frequency bandwidth  $B = 100$  kHz.

#### **Question A**

We consider the amplifier 1 such that its power gain in the frequency bandwidth  $B = 100$  kHz is equal to  $G_1 = 30$  dB and its noise figure is equal to  $NF_1 = 6.02$  dB.

We consider the amplifier 2 such that its power gain in the frequency bandwidth  $B = 100$  kHz is equal to  $G_2 = 10$  dB and its noise figure is equal to  $NF_2 = 9.03$  dB.

Calculate the noise factor  $F$  of the circuit constituted by the cascade of the amplifier 1 and of the amplifier 2.

#### **Question B**

We consider the amplifier 3 such that its power gain in the frequency bandwidth  $B = 100$  kHz is equal to  $G_3 = 10$  dB and its noise figure is equal to  $NF_3 = 6.02$  dB.

We consider the amplifier 4 such that its power gain in the frequency bandwidth  $B = 100$  kHz is equal to  $G_4 = 30$  dB and its noise figure is equal to  $NF_4 = 9.03$  dB.

Calculate the noise factor  $F$  of the circuit constituted by the cascade of the amplifier 3 and of the amplifier 4.

#### **Question C**

Calculate the power gain  $G$  of the circuit constituted by the cascade of the amplifier 1 and of the amplifier 2.

Calculate the power gain  $G$  of the circuit constituted by the cascade of the amplifier 3 and of the amplifier 4.

#### **Question D**

Calculate the noise temperature  $T_r$  associated to the circuit constituted by the cascade of the amplifier 1 and of the amplifier 2.

Calculate the noise temperature  $T_r$  associated to the circuit constituted by the cascade of the amplifier 3 and of the amplifier 4.

---

Series 11:

Noise Figure, Power Gain and Noise Temperature of an Amplifier- Chap. 5

Winter semester 2020-2021

Prof. Catherine Dehollain

Page 1 sur 3

# EPFL

## HF&VHF Circuits and Techniques I

---

### Question E

Calculate the Power Spectral Density of the basic noise generated by the circuit constituted by the cascade of the amplifier 1 and of the amplifier 2 by considering this noise at the input of the circuit (notation  $N_p$  on p. 5-3 or  $N_a$  on p. 5-6 of the HF&VHF course).

Calculate the Power Spectral Density of the basic noise generated by the circuit constituted by the cascade of the amplifier 3 and of the amplifier 4 by considering this noise at the input of the circuit (notation  $N_p$  on p. 5-3 or  $N_a$  on p. 5-6 of the HF&VHF course).

### Question F

Calculate the average value of the noise factor  $F$  of the circuit constituted by the cascade of the amplifier 1 and of the amplifier 2 on the bandwidth  $B = 100$  kHz.

Calculate the average value of the noise factor  $F$  of the circuit constituted by the cascade of the amplifier 3 and of the amplifier 4 on the bandwidth  $B = 100$  kHz.

### Question G

We do the assumption that the Signal over Noise Ratio at the input (SNR<sub>i</sub>) is equal to 10.

Calculate the Signal over Noise Ratio at the output (SNR<sub>out</sub>) of the circuit constituted by the cascade of the amplifier 1 and of the amplifier 2.

Calculate the Signal over Noise Ratio at the output (SNR<sub>out</sub>) of the circuit constituted by the cascade of the amplifier 3 and of the amplifier 4.

### Question H

We do the assumption that the Signal over Noise Ratio at the output (SNR<sub>out</sub>) is equal to 1.

It is recalled that the bandwidth  $B = 100$  kHz and that the temperature  $T = 290$  Kelvin.

Calculate the minimum detectable signal (MDS) associated to the circuit constituted by the cascade of the amplifier 1 and of the amplifier 2.

Calculate the RMS value  $V_{in\ RMS}$  of the input voltage; we do the assumption that the input impedance is equal to  $R_{in} = 50$  Ohms.

Calculate the minimum detectable signal (MDS) associated to the circuit constituted by the cascade of the amplifier 3 and of the amplifier 4.

Calculate the RMS value  $V_{in\ RMS}$  of the input voltage; we do the assumption that the input impedance is equal to  $R_{in} = 50$  Ohms.

### Question I

The circuit constituted by the cascade of the amplifier 1 and of the amplifier 2 is considered.

Calculate the output signal level  $L_{out}$  when the minimum detectable signal MDS is applied to the input of the circuit.

The circuit constituted by the cascade of the amplifier 3 and of the amplifier 4 is considered.

---

Series 11:

Noise Figure, Power Gain and Noise Temperature of an Amplifier- Chap. 5

Winter semester 2020-2021

Prof. Catherine Dehollain

Page 2 sur 3

**EPFL**  
**HF&VHF Circuits**  
**and Techniques I**

---

Calculate the output signal level  $L_{out}$  when the minimum detectable signal MDS is applied to the input of the circuit.

---

Series 11:

Noise Figure, Power Gain and Noise Temperature of an Amplifier- Chap. 5

Winter semester 2020-2021

Prof. Catherine Dehollain

Page 3 sur 3