

TRANSISTOR-LEVEL ANALOG IC DESIGN

Nonlinear analog design: Comparators

A. KOUKAB

Swiss Federal Institute of Technology (EPFL)

Electronics Laboratory

1015 Lausanne- Switzerland


E_mail: maher.kayal@epfl.ch




Outline

- Performance parameters (delay and resolution)
- High performances comparator
- Basic topologies
- High-speed comparators
- External and internal positive feedback
- Clocked comparator



COMPARATOR

 

a)

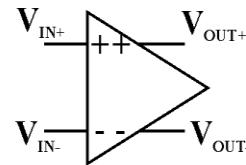


b)

 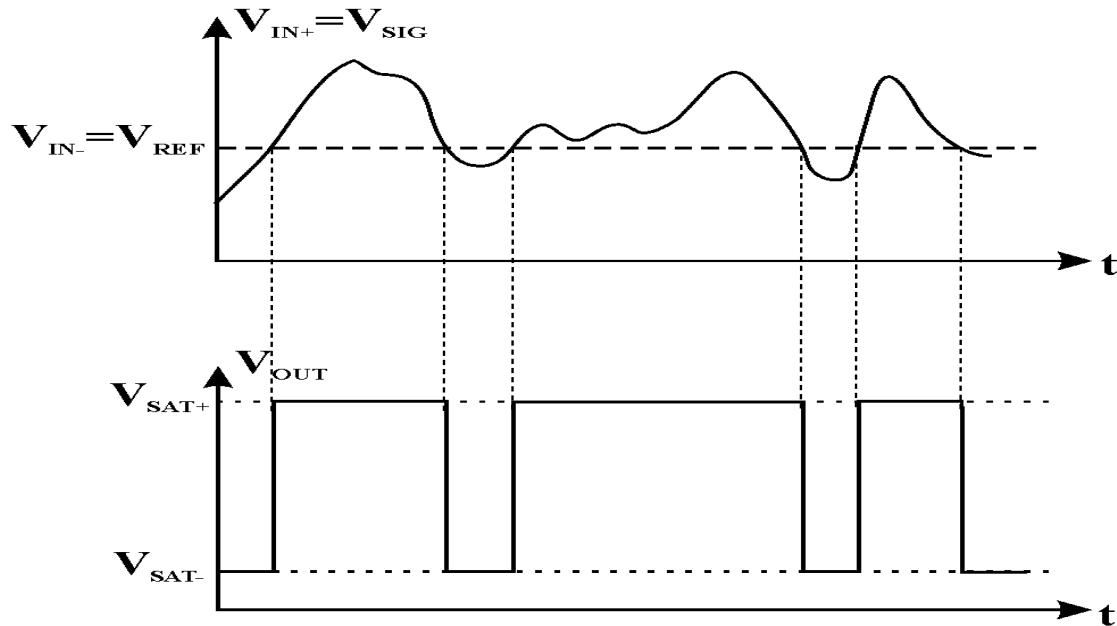

- Binary output as a result of comparison of input signal with the reference:

Performance parameters (propagation delay)

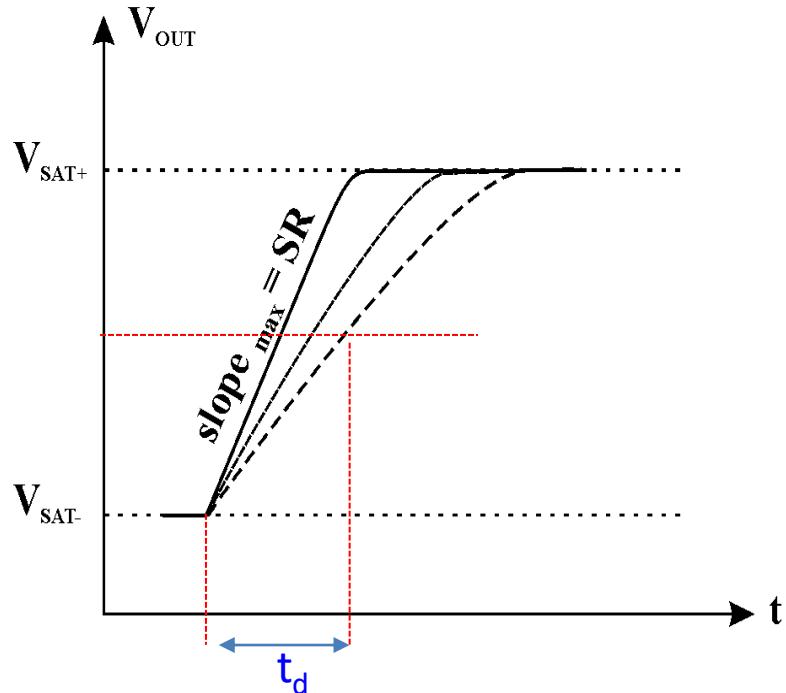- Propagation delay t_d is the time required for the output to reach the 50% point of a transition (i.e., when ΔV_{out} reaches $(V_{SAT+} - V_{SAT-})/2$):



Jitter (noise in time domain) ↘ when $t_d \downarrow$

- Cas1: small input change with a first-order system $\Delta V_{out}/\Delta V_{in} = A_0/(1+s\tau_1)$

$$\Delta V_{out}(t) = A_0 \cdot \left(1 - e^{-\frac{t}{\tau_1}}\right) \cdot \Delta V_{in}$$

$$t_d = -\tau_1 \ln \left(1 - \frac{V_{SAT+} - V_{SAT-}}{2A_0 \Delta V_{in}} \right)$$

- Case 2: Large input change


$$SR = [dV_{out}/dt]_{max} = I_o/C_L$$

$$t_d = \frac{\frac{V_{SAT+} - V_{SAT-}}{2}}{\frac{I_o}{C_L}} = \frac{V_{SAT+} - V_{SAT-}}{2 \cdot SR}$$

Performance parameters: (Resolution)


- The resolution represents the minimum input difference that changes the logic value at the output state.
- It is limited by the offset and the gain variation of the comp.

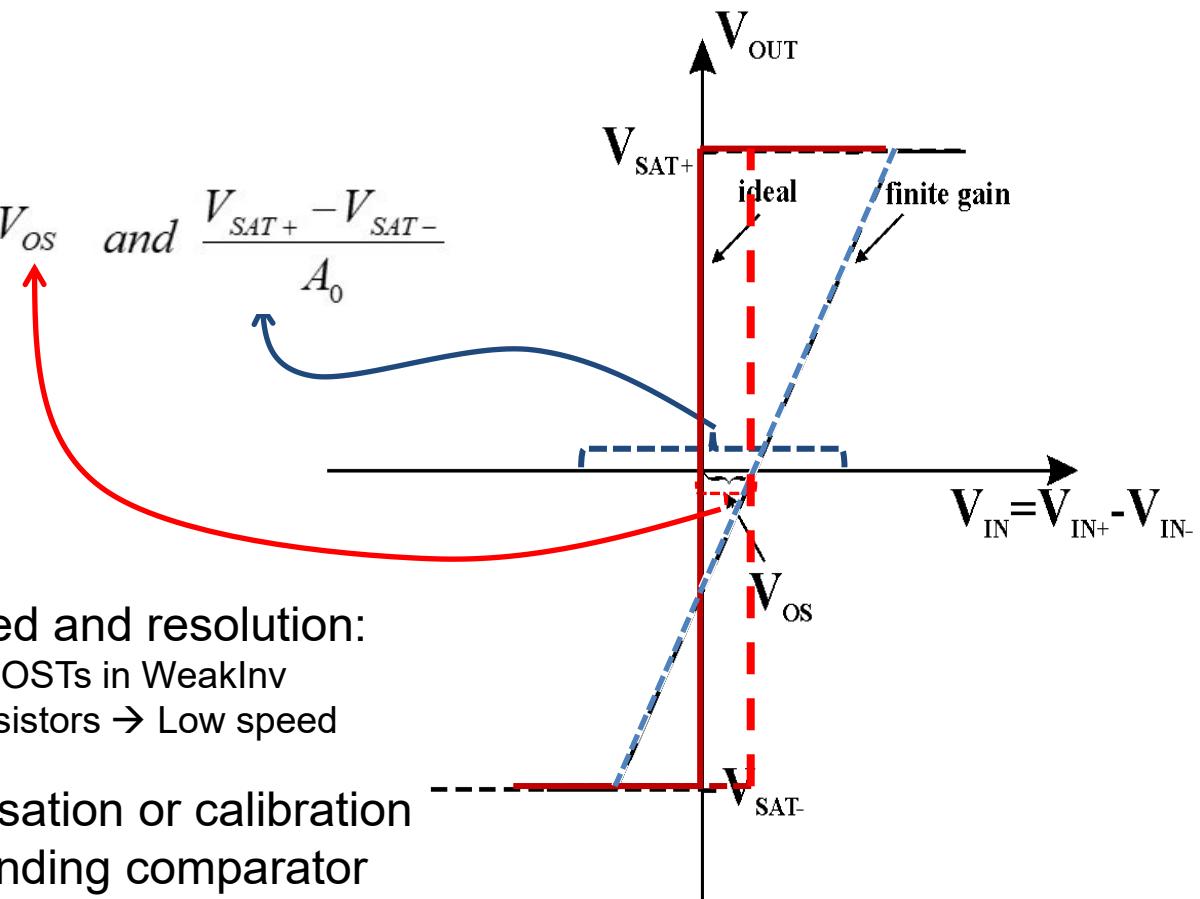$(\Delta V_{IN})_{min}$ given by V_{OS} and $\frac{V_{SAT+} - V_{SAT-}}{A_0}$



- Tradeoff between speed and resolution:
 - Low offset \rightarrow input MOSTs in WeakInv
 - WeakInv \rightarrow large transistors \rightarrow Low speed
- Usually offset compensation or calibration is a mandatory in demanding comparator circuits.


High performances comparator

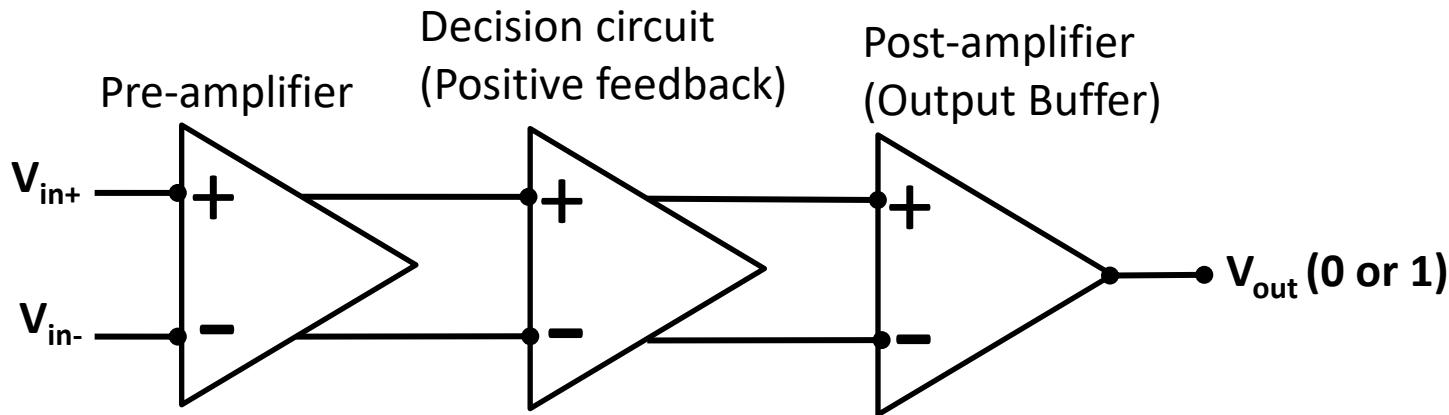

- Preamplifier:
 - Amplifies the input signal to improve the comparator sensitivity;
 - increases the minimum input signal with which the comparator can make a decision;
 - isolates the input from switching noise coming from the positive feedback;
 - usually cascade of 3 or 4 low gain-high BW amplification stages
- Decision Circuit: determines which of the input signals is larger
- Buffer: amplifies this information and outputs a digital signal


Basic topology

- Two-stage class A amplifier:

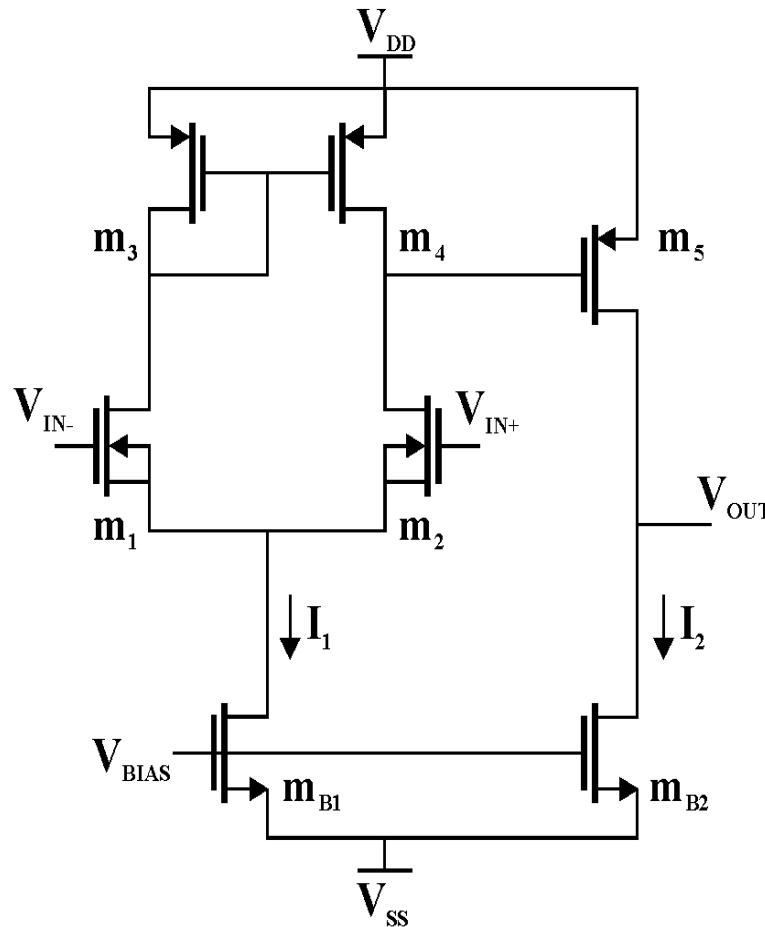

- Requires high-gain amplifiers in order to make its output saturate to the positive or negative supply rail for a small input difference (i.e., high resolution)
- No need for frequency compensation (i.e. Miller Cap)
- High R_{out} for high gain means High RC (i.e. time constant) and high L so low Frequency transition.
- Unsuitable for high-speed and low-power applications.

Basic topology: Inverter

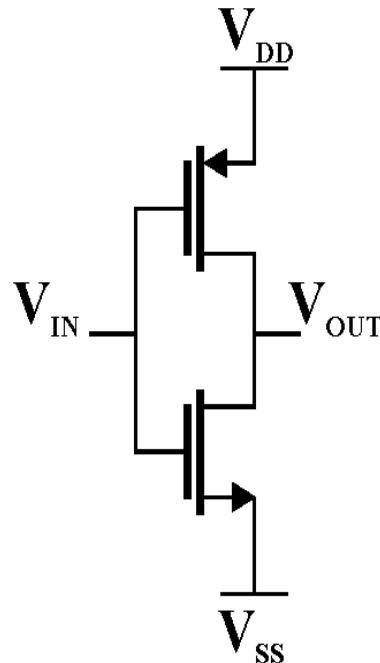


- if $V_{IN} < V_{T0n}$
NMOS is off, PMOS is on
 $V_{out} = V_{DD}$
- if $V_{IN} > V_{DD} - V_{T0p}$
PMOS is off, NMOS is on,
 $V_{out} = V_{ss}$

- Two drawbacks:
 - V_{T0} is PVT dependent
 - if $V_{Ton} < V_{IN} < V_{DD} - V_{Top}$, V_{out} is not defined (NMOS is on, PMOS is on)
- To overcome this issues the inverter input signal is usually driven by a pre-amplifier (for example, a simple OTA) that amplifies the input signal of the inverter.

Basic topology 2

- Two-stage class B amplifier:

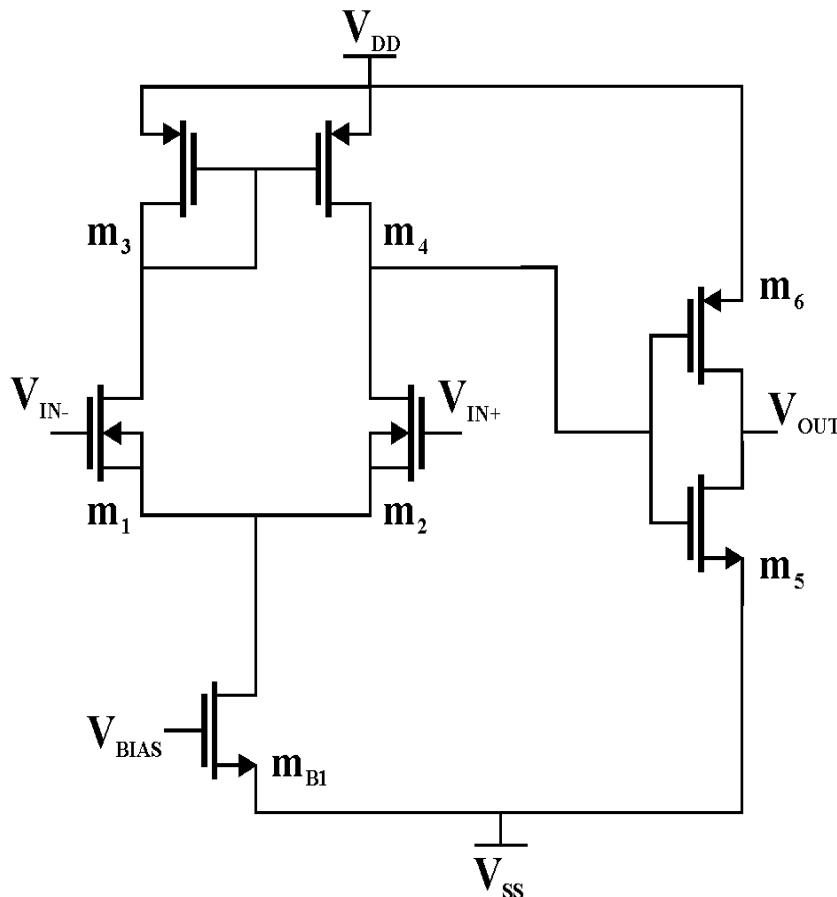


- Suitable for moderate speed and moderate power consumption.
- Output stage is class B
- Required preamplifier gain quite low: just enough to guarantee $V_{pre} < V_{TOn}$ or $V_{pre} > V_{DD} - V_{TOP}$.
- Still PVT dependent

High-speed comparators

- Another way to realize high speed comparator is to cascade several preamplifier stages followed by several cascaded inverters or analog latches.


Principle illustration:

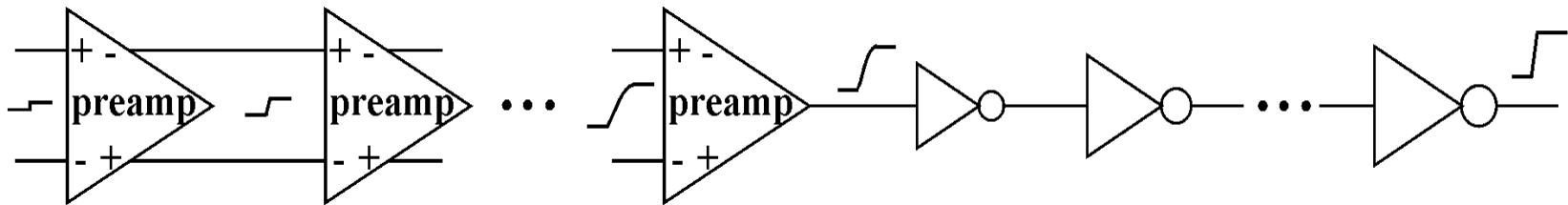

- One high gain amplifier is in general slower than several low gain amplifiers ($GBW = Cst$).
- Cascading several inverter stages allows to increase the load capacitance of each stage gradually without important degradation of the response time.

Basic topologies: regenerative comparators


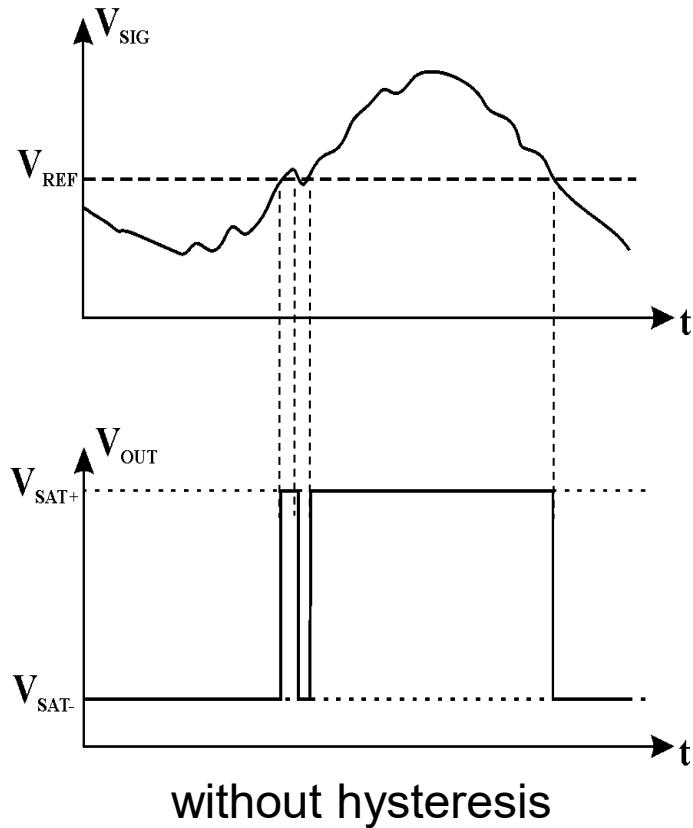
- Comparator response in a noisy environment:



- A hysteresis is required to avoid erroneous responses.
- Hysteresis is implemented in the comparator by the use of positive (regenerative) feedback.
- The positive feedback can be external or internal.

Basic topologies: regenerative comparators

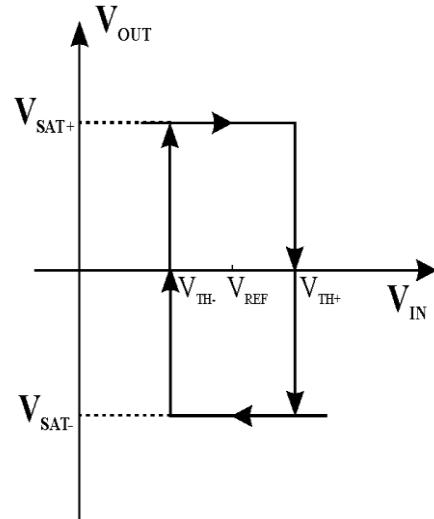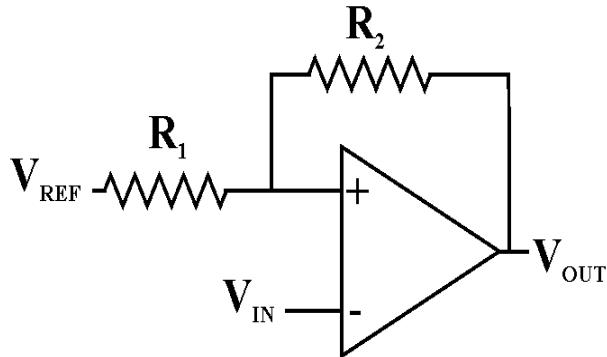
- Inverting comparator with external positive feedback:



$$V_{TH+} = \left(\frac{R_1}{R_1 + R_2} \right) V_{SAT+} + \left(\frac{R_2}{R_1 + R_2} \right) V_{REF}$$

$$V_{TH-} = \left(\frac{R_1}{R_1 + R_2} \right) V_{SAT-} + \left(\frac{R_2}{R_1 + R_2} \right) V_{REF}$$
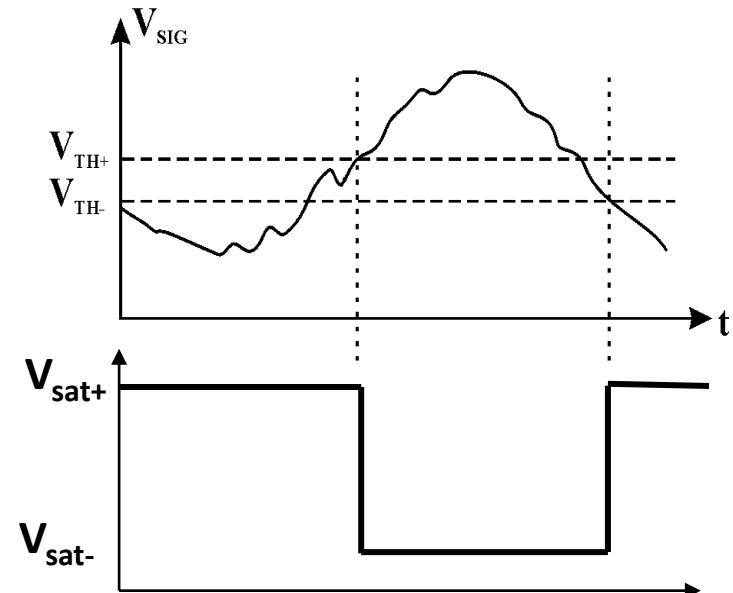
$$\Delta V_{TH} = V_{TH+} - V_{TH-} = \frac{R_1}{R_1 + R_2} (V_{SAT+} - V_{SAT-})$$




with hysteresis

- Drawback: Resistances overload the OTA and occupy a relatively large area.
- **In ICs internal feedback is preferred**

Basic topologies: regenerative comparators

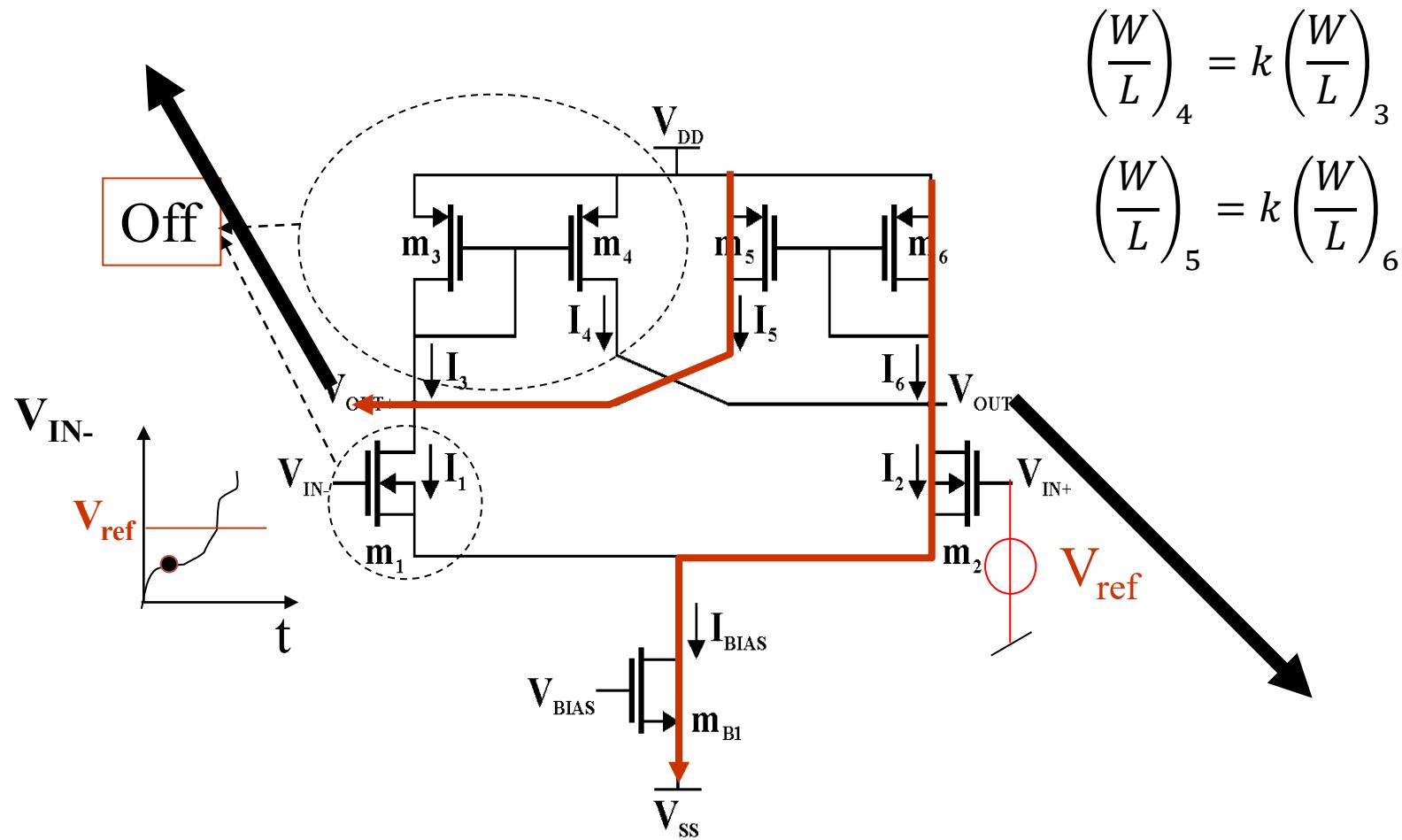
- Cross-coupled m_4 and m_5 for a **Positive Feedback**
- If $k \geq 1$ with k is the positive feedback factor




$$\left(\frac{W}{L}\right)_4 = k \left(\frac{W}{L}\right)_3$$

$$\left(\frac{W}{L}\right)_5 = k \left(\frac{W}{L}\right)_6$$

Switching condition

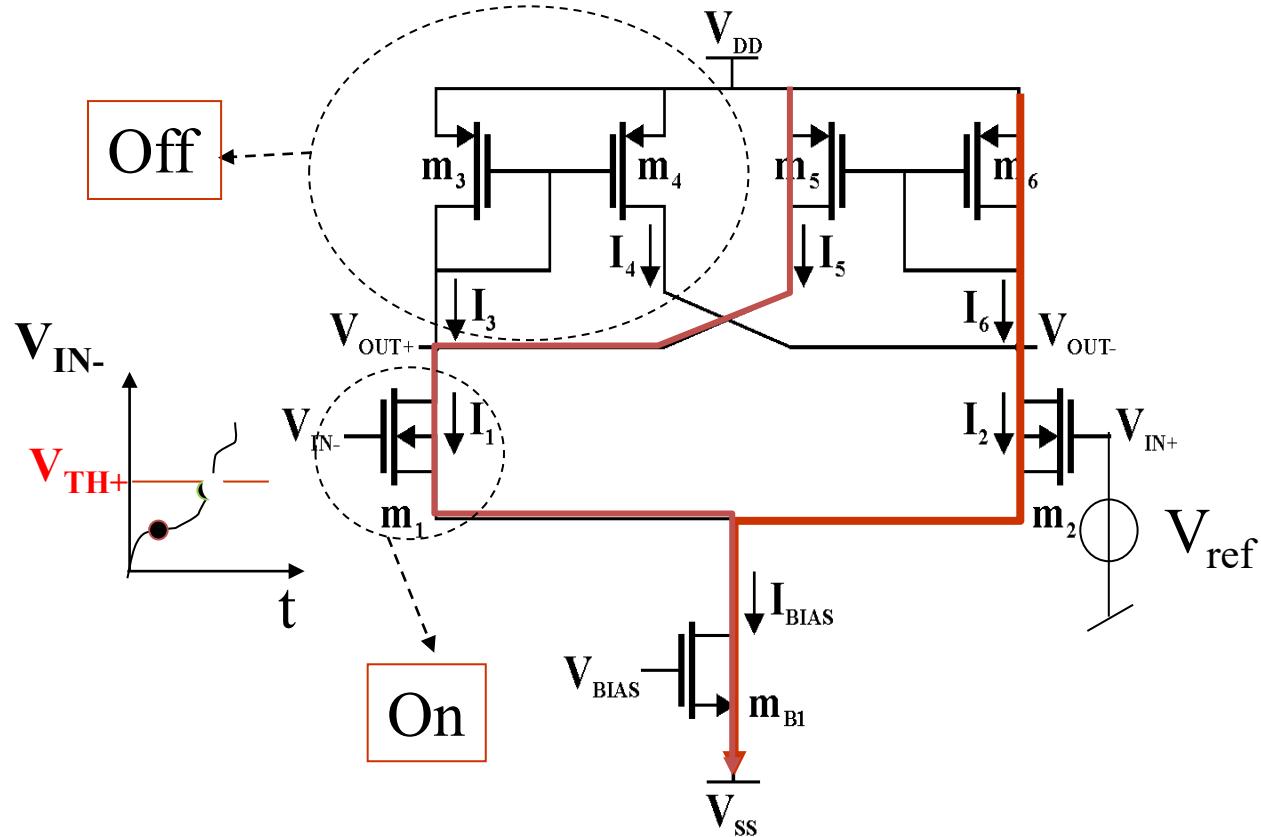

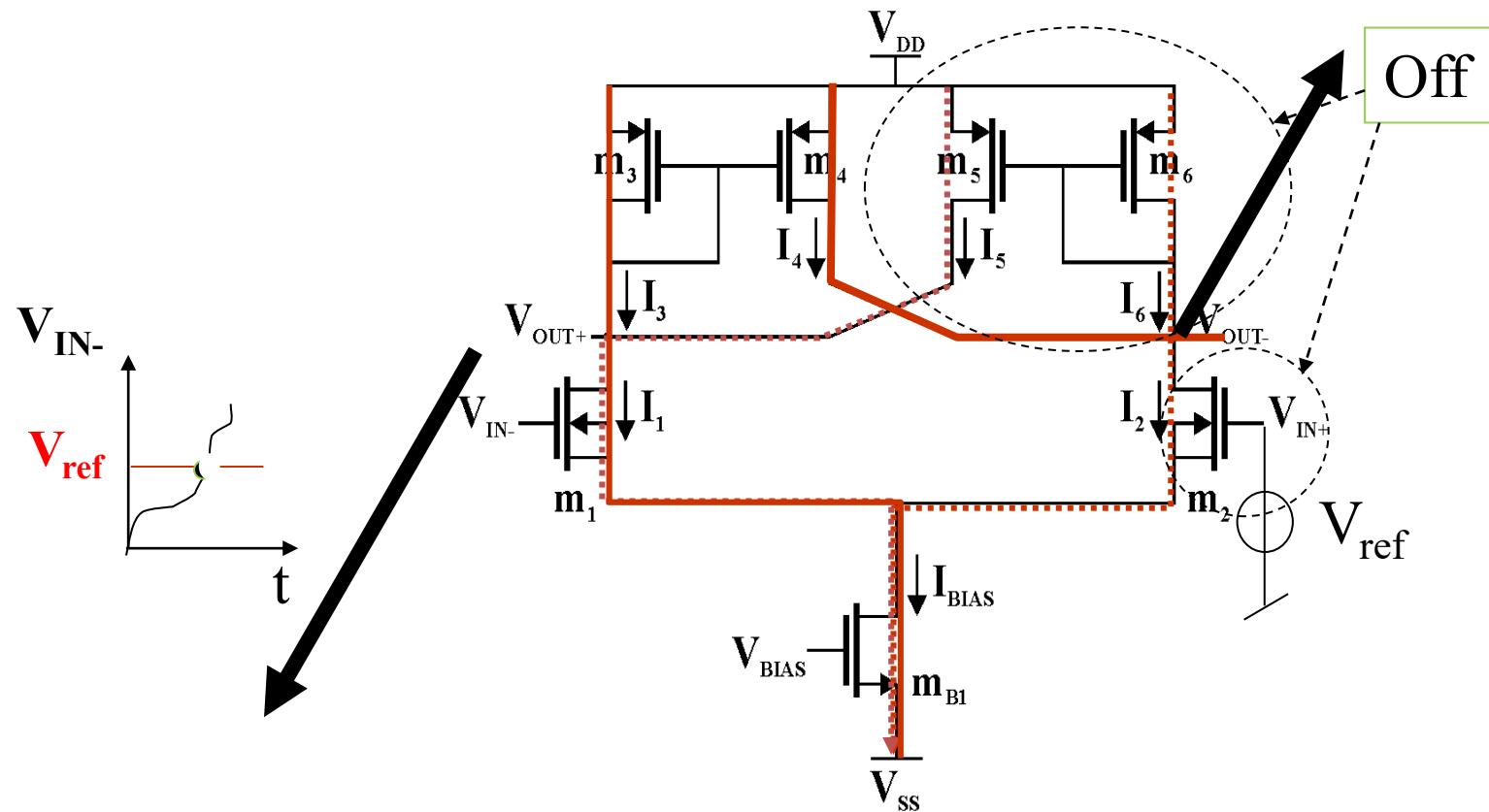Basic topologies: regenerative comparators




Basic topologies: regenerative comparators

- Threshold voltages V_{TH+} and V_{TH-} calculation:
Starting point just before switching states
($V_{in-} = V_{TH+}$ and V_{out+} still at V_{DD})

$$I_1 = kI_2 \quad \text{and} \quad I_1 + I_2 = I_{Bias}$$

$$\rightarrow I_2 = \frac{I_{Bias}}{1+k} \quad \text{and} \quad I_1 = \frac{kI_{Bias}}{1+k}$$

M1,2 in Strong inversion (for speed):

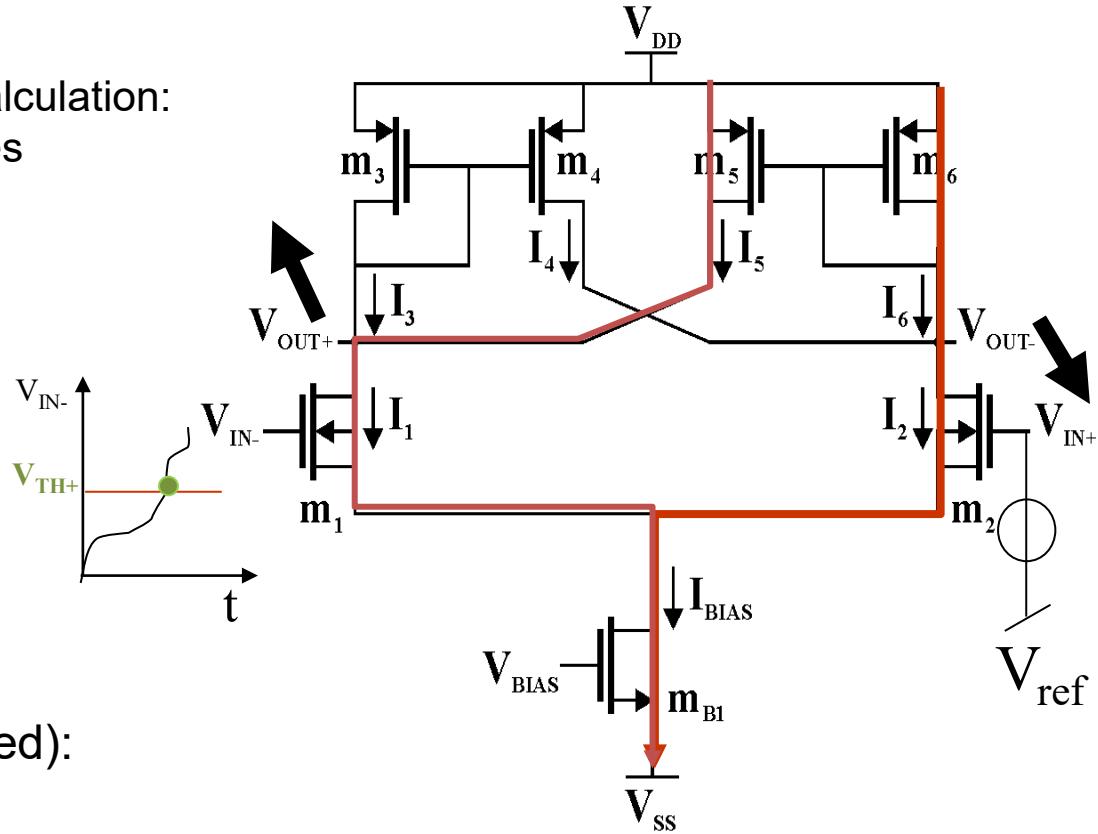

$$\frac{kI_{BIAS}}{1+k} = \frac{\beta_1}{2} (V_{GS1} - V_{T0})^2 \rightarrow V_{G1} = V_{T0} + \sqrt{\frac{2kI_{BIAS}}{\beta_1(1+k)}} + V_{S1}$$


$$\frac{I_{BIAS}}{1+k} = \frac{\beta_2}{2} (V_{GS2} - V_{T0})^2 \rightarrow V_{G2} = V_{T0} + \sqrt{\frac{2I_{BIAS}}{\beta_2(1+k)}} + V_{S2}$$

$$V_{G1} = V_{TH+}, \quad V_{G2} = V_{ref}, \quad V_{S2} = V_{S1}$$

$$V_{TH+} - V_{ref} = \sqrt{\frac{2I_{BIAS}}{\beta_1(1+k)}} (\sqrt{k} - 1)$$

Basic topologies: regenerative comparators

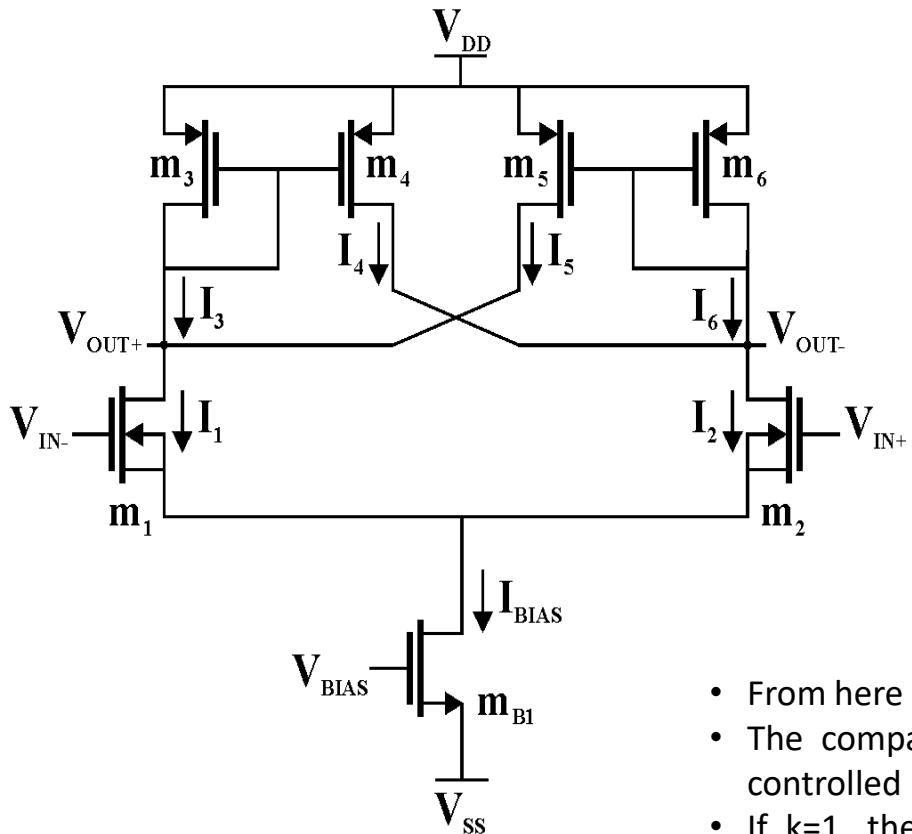- Inverting comparator with internal positive feedback with $\beta_1 = \beta_2 = \beta$ and $V_{in+} = V_{ref}$



$$V_{TH+} = V_{ref} + \sqrt{\frac{2I_{BIAS}}{\beta_1}} \left(\frac{\sqrt{k} - 1}{\sqrt{1+k}} \right)$$

$$V_{TH-} = V_{ref} - \sqrt{\frac{2I_{BIAS}}{\beta_1}} \left(\frac{\sqrt{k} - 1}{\sqrt{1+k}} \right)$$

$$\Delta V_{TH} = 2 \sqrt{\frac{2I_{BIAS}}{\beta_1}} \left(\frac{\sqrt{k} - 1}{\sqrt{1+k}} \right)$$

$$\left(\frac{W}{L} \right)_4 = k \left(\frac{W}{L} \right)_3 \quad \left(\frac{W}{L} \right)_5 = k \left(\frac{W}{L} \right)_6$$

- From here we notice that only when $k > 1$, the hysteresis occurs
- The comparator transfer function is clockwise and the hysteresis is controlled by the ratio k , the tail current and β of the input transistors
- If $k=1$, the threshold voltages are equal and there is no hysteresis (residual hysteresis due to mismatch)
- In practical realizations, the presented circuit is usually followed by an output stage (a common source or an inverter) in order to have a logic 0 or 1 (V_{ss} or V_{DD}) at the output.

Basic topologies: regenerative comparators

- Finally, if $k < 1$, the circuit behaves more as a gain stage with a higher speed thanks to the positive feedback.

DC analysis



$$I_1 = I_2 \rightarrow g_{m1} = g_{m2}; g_{m3} = g_{m6}; g_{m4} = g_{m5}$$

$$g_{ds1} = g_{ds2}; g_{ds4} = g_{ds5}$$

$$I_4 = kI_3 \rightarrow g_{m4} = k g_{m3}$$

ac analysis


$$A_0 = \frac{v_{odif}}{v_{idif}} = ?$$

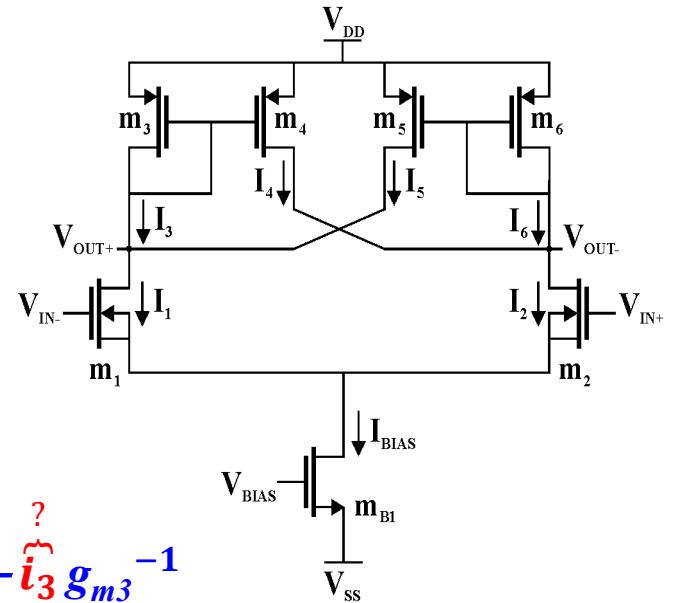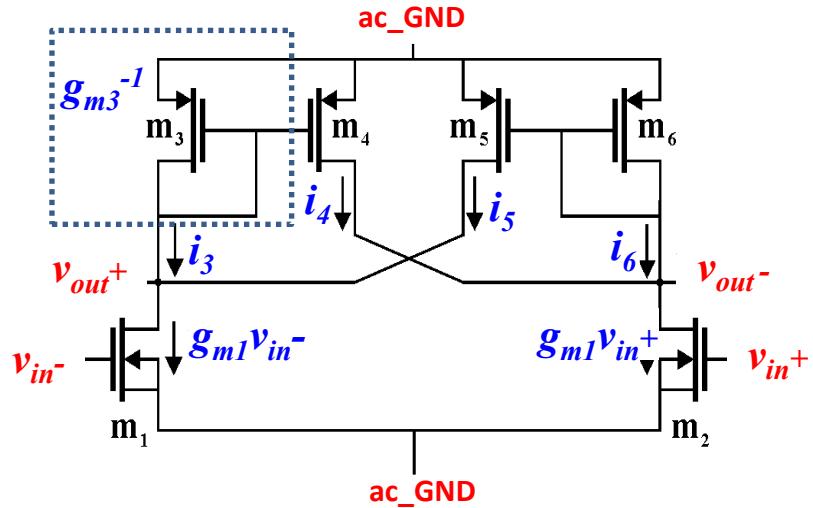

$$v_{out}^+ = -\hat{i}_3 g_{m3}^{-1}$$

$$\begin{cases} i_5 = k i_6 = -k i_3 \rightarrow i_3 = \frac{g_{m1} v_{in}^-}{1 - k} \\ i_3 + i_5 = g_{m1} v_{in}^- \end{cases}$$

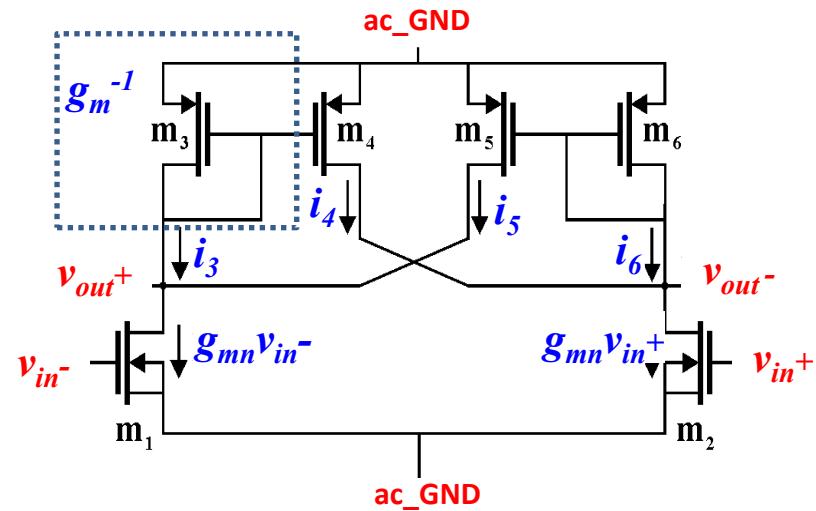
$$\rightarrow -\frac{v_{out}^+}{v_{in}^-} = \frac{v_{odif}}{v_{idif}} = A_0 = \frac{g_{m1}}{(1 - k) g_{m3}}$$



$$\begin{cases} i_5 = k i_6 = -k i_3 \rightarrow i_3 = \frac{g_m v_{in-}}{1 - k} \\ i_3 + i_5 = g_m v_{in-} \end{cases}$$

Basic topologies: analog latch

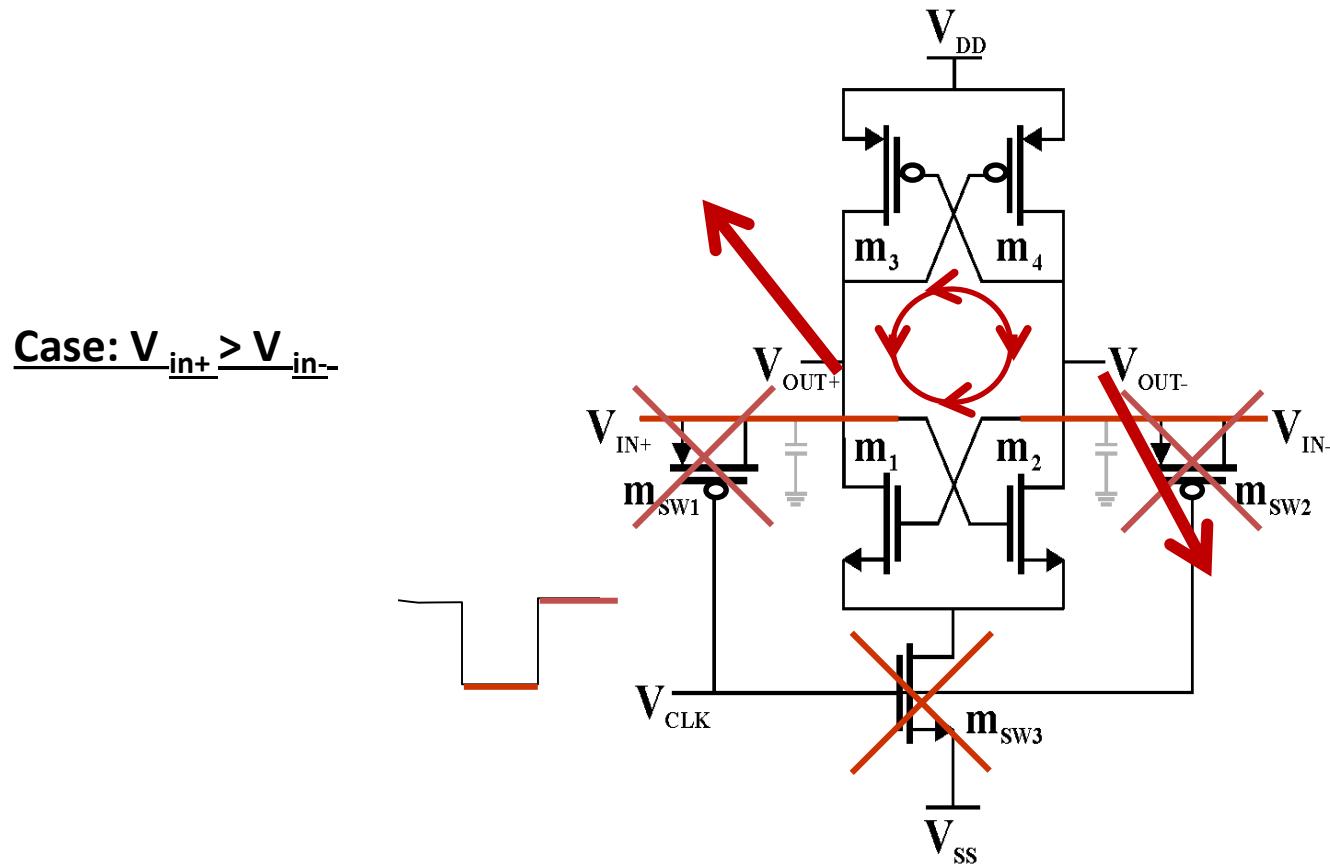A clocked comparator: A comparator whose outputs change on the rising (or falling) edge of a clock (Sample, Hold and compare).



Warning: Charge injection, switching noise of the positive feedback
Need to isolate the inputs (i.e. use a preamplifier) 20