

Noise

Analog ICs
Adil KOUKAB

Contents

- Chap1: Time and Frequency Domain Analysis of Noise
- Chap2: Noise in Devices & Noise in Circuits


Chap2-Outline1 : Noise in Devices

- Resistor Thermal Noise:
 - Ex: Resistor divider and RC circuits
- MOSFET Channel Thermal Noise
- MOSFET Flicker Noise

Thermal (Johnson) Noise of a Resistor

Resistor: thermal agitation → Random motion of electrons

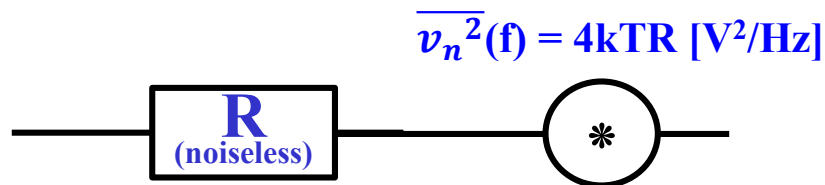→ Noise voltage with PSD: $\overline{v_n^2}(f) = 4kTR$ [V²/Hz]




Where

k is Boltzmann constant = $1,38 \cdot 10^{-23}$ [J/K]


T = Temperature in [°K]

R = resistance in Ω

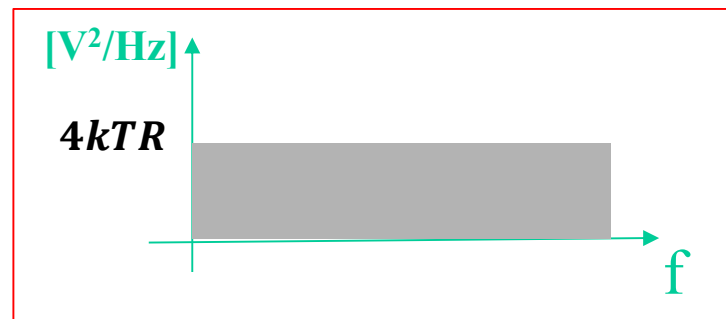

Norton representation


$\overline{i_n^2}(f) = 4kT/R$ [A²/Hz]

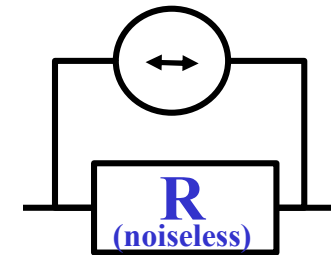

- Particular case: 1k Ω resistor @ 300 °K exhibits an RMS noise voltage of $\sqrt{\overline{v_n^2}} = \sqrt{4kTR} = 4 \text{ nV}/\sqrt{\text{Hz}}$.
- → **R = x k Ω** results in a noise of $\sqrt{\overline{v_n^2}} = \sqrt{x} \cdot 4 \text{ nV}/\sqrt{\text{Hz}}$

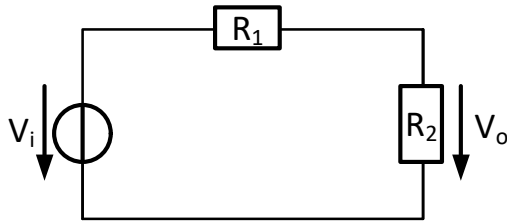Example 3 : Resistive divider

- Determine the output noise of a resistive divider (R_1 , R_2) and deduce the impact of each resistor on noise performance.
- Reevaluate the noise performance using the signal-to-noise ratio (SNR).



$$\overline{v_{n,o}^2}(f) = 4kT(R_1//R_2) \text{ [V}^2/\text{Hz]}$$

$$\overline{v_{n,o}^2} = 4kT(R_1//R_2) \Delta f \text{ [V}^2]$$

Output Noise $\searrow$ if $R_1 \searrow$ and $R_2 \searrow$

$$|A_v| = \frac{R_2}{R_2 + R_1}$$


$$SNR = \frac{\overline{v_o^2}}{\overline{v_{n,o}^2}} = \frac{\left(\frac{R_2}{R_2 + R_1}\right)^2 \overline{v_i^2}}{4kT \frac{R_2 R_1}{R_2 + R_1} \Delta f} = \frac{1}{\Delta f} \frac{R_2}{4kT R_1 (R_2 + R_1)} \overline{v_i^2} = \frac{1}{\Delta f} \frac{\overline{v_i^2}}{4kT} \frac{1}{R_1 \left(1 + \frac{R_1}{R_2}\right)}$$

SNR $\nearrow$ if $R_1 \searrow$ and $R_2 \nearrow$

Example 4:

- Demonstrate that the total noise power of a simple low-pass RC circuit is:
- Explain intuitively why this noise is independent of the value of R:

$$\overline{v_n^2} = \frac{kT}{C}$$

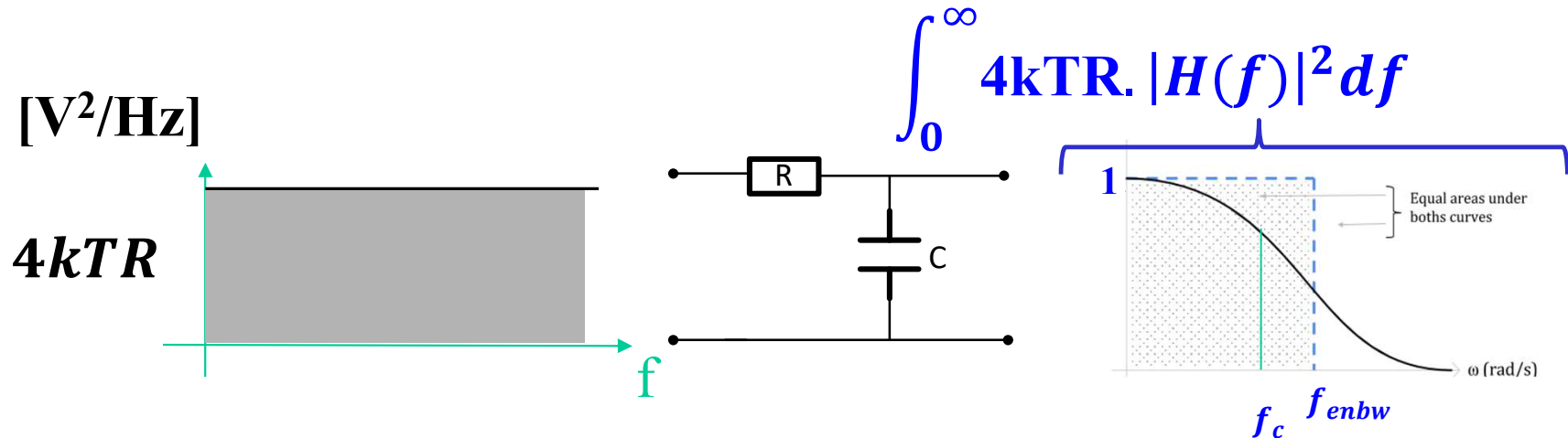


$$\overline{v_{n,o}^2} = 4kTR f_{enbw} = 4kTR \frac{\pi}{2} f_c = 4kTR \frac{\pi}{2} \frac{1}{2\pi RC} = \frac{kT}{C}$$

If $R \nearrow \rightarrow$ Noise PSD $\nearrow$ but $f_c \searrow$


Chap2-Outline1

- Resistor Thermal Noise
- MOSFET Channel Thermal Noise
- MOSFET Flicker Noise

Channel Thermal Noise

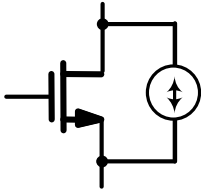

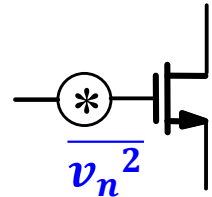$\overline{i_n^2} = 4kT\gamma g_m \text{ [A}^2/\text{Hz]}$
(in saturation)




$\overline{v_n^2} = 4kT\gamma \frac{1}{g_m}$
Input Voltage representation

- With $\gamma \approx 2/3$ for long channel MOSFETs ($\rightarrow 1$ for modern technologies)
- nMOS has a larger g_m and so larger channel current thermal noise
- Should we minimize or maximize g_m ?

Chap2-Outline1


- Resistor Thermal Noise
- MOSFET Channel Thermal Noise
- MOSFET Flicker Noise

Flicker Noise


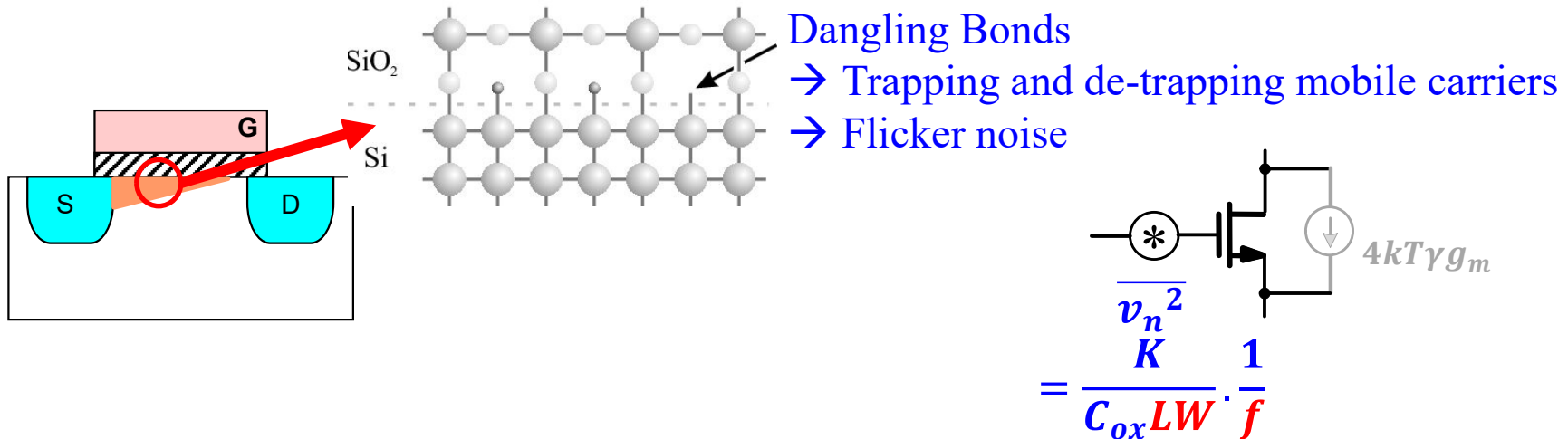


- K is a constant empirically determined
- Big transistors have less flicker noise
- K is generally lower for PMOS
- Ex: The total noise power from f_1 to f_2 [V²]:
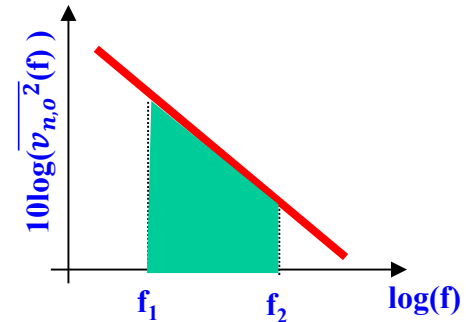
$$\overline{v_n^2} = \int_{f_1}^{f_2} \frac{K}{C_{ox}LW} \cdot \frac{1}{f} df = \frac{K}{C_{ox}LW} \cdot \ln\left(\frac{f_2}{f_1}\right)$$



Total Noise in MOSFETs

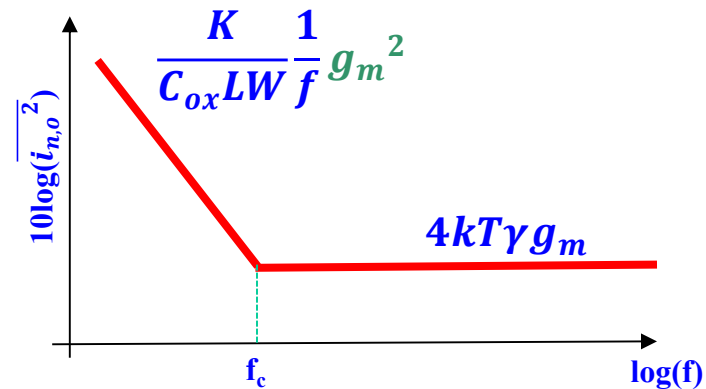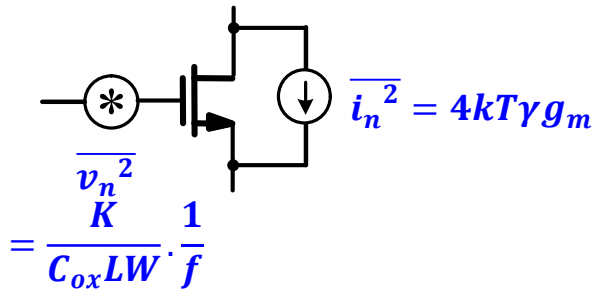


f_c : Flicker noise “corner frequency”: usually $\in [500 \text{ kHz}, 1 \text{ MHz}]$

$$f_c = \frac{K}{C_{ox} W L} g_m \frac{3}{8kT}$$

- Flicker noise is detrimental for low-frequency circuits
- Or if it is upconverted the signal Band.


nMOS vs pMOS

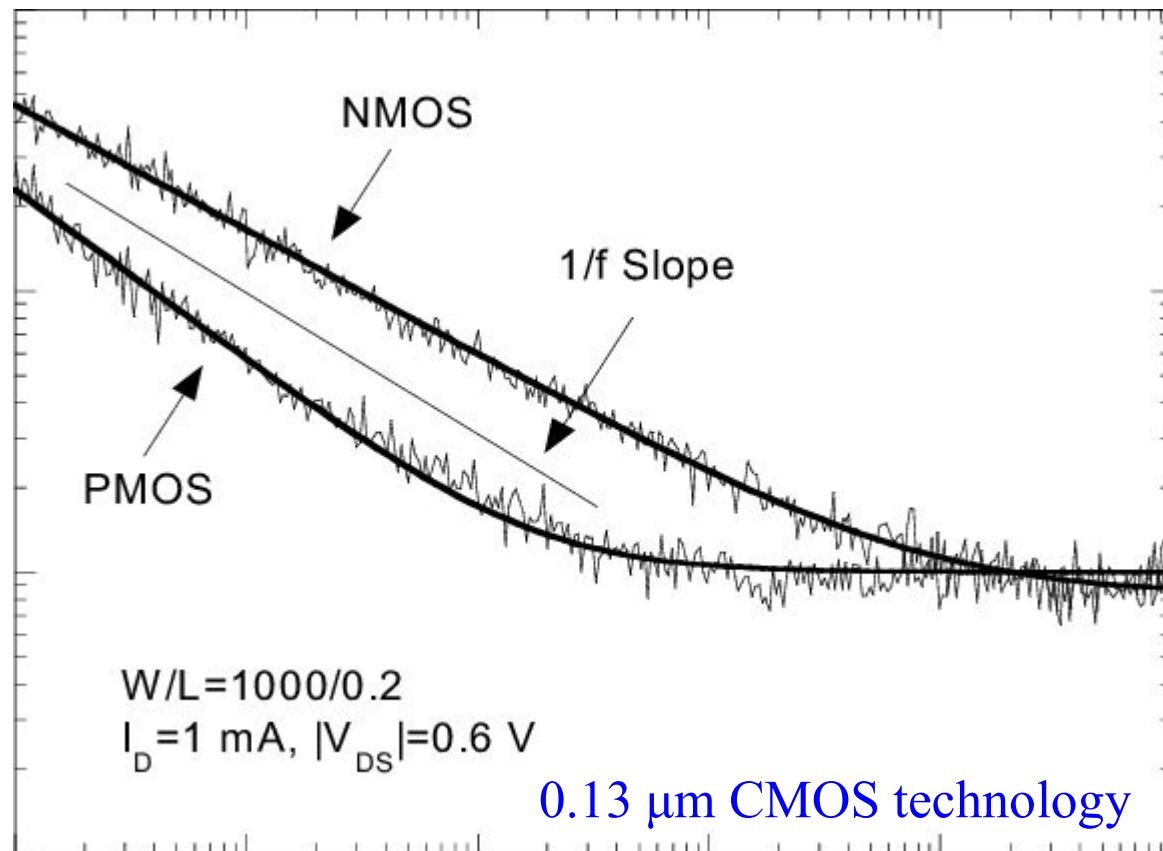

Chap2-Outline2: Noise in Circuits

- Circuit-Noise Analysis and Modeling
 - Example: Noise in CS Amplifier
- Input-Referred Noise
 - Effect of source impedance
- Example: Noise CS, CG amplifier and source follower.

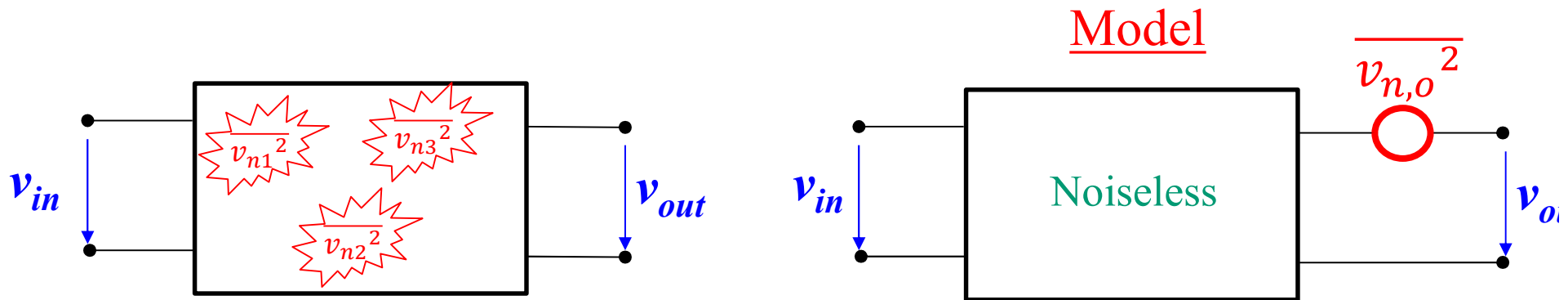Circuit-Noise Analysis and Modeling Procedure




- Identify noise sources.
- Determine ($H_i(s)$) from $\overline{v_{ni}^2}$ to the output.
- Add all of the contributions to the output

The diagram shows three input noise power spectral densities $\overline{v_{n,1}^2}(f)$, $\overline{v_{n,2}^2}(f)$, and $\overline{v_{n,3}^2}(f)$ entering blocks labeled $|H_1|^2$, $|H_2|^2$, and $|H_3|^2$ respectively. The outputs of these blocks are summed at a junction (represented by a circle with a plus sign) to produce the total output noise power spectral density $\overline{v_{n,o}^2}(f)$. A red arrow points from this diagram back to the noiseless model in the top right.

$$\overline{v_{n,o}^2}(f) = \sum_{j=1}^3 \overline{v_{n,j}^2}(f) |H_j(f)|^2$$

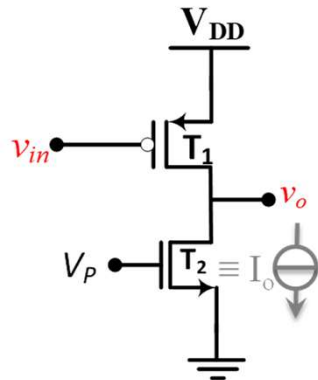Example: Noise in CS Amplifier

- Determine the output thermal noise voltage of a common source amplifier and deduce the impact of g_{m1} and g_{m2} on noise performance.




$$\overline{i_{n1,2}^2} = 4kT\gamma g_{m1,2} \text{ [A}^2/\text{Hz]}$$

$$\overline{v_{n,o}^2} = 4kT\gamma(g_{m1} + g_{m2})(r_{o1} // r_{o2})^2 \text{ [V}^2/\text{Hz]}$$

Output Noise $\searrow$ if $g_{m1} \searrow$ and $g_{m2} \searrow$

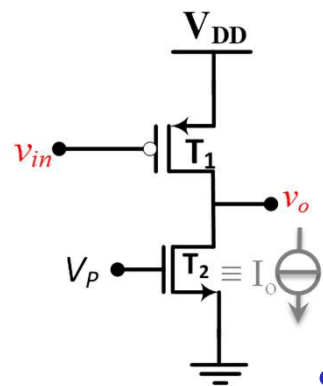Example: Noise in CS Amplifier

- Reevaluate the noise performance using the signal-to-noise ratio (SNR).



$$|A_v| = g_{m1} r_{o1} // r_{o2}$$

$$\overline{v_{n,o}^2} = 4kT\gamma(g_{m1} + g_{m2})(r_{o1} // r_{o2})^2 \text{ [V}^2/\text{Hz]}$$

$$SNR = \frac{\overline{v_o^2}}{\overline{v_{n,o}^2}} = \frac{|A_v|^2 \overline{v_i^2}}{\overline{v_{n,o}^2}} = \frac{g_{m1}^2}{4kT\gamma(g_{m1} + g_{m2})\Delta f} \overline{v_i^2} = \frac{1}{\Delta f} \frac{g_{m1}}{4kT\gamma\left(1 + \frac{g_{m2}}{g_{m1}}\right)} \overline{v_i^2}$$


$$SNR \nearrow \text{ if } g_{m1} \nearrow \text{ and } g_{m2} \searrow$$

Conclusion: improve noise performances $\rightarrow$ maximize g_m of active transistor and minimize g_m of load (current source)

Chap2-Outline2


- Circuit-Noise Analysis and Modeling
 - Example: Noise in CS Amplifier
- Input-Referred Noise
 - Effect of source impedance
- Example: Noise CS, CG amplifier and source follower.

Input-Referred Noise

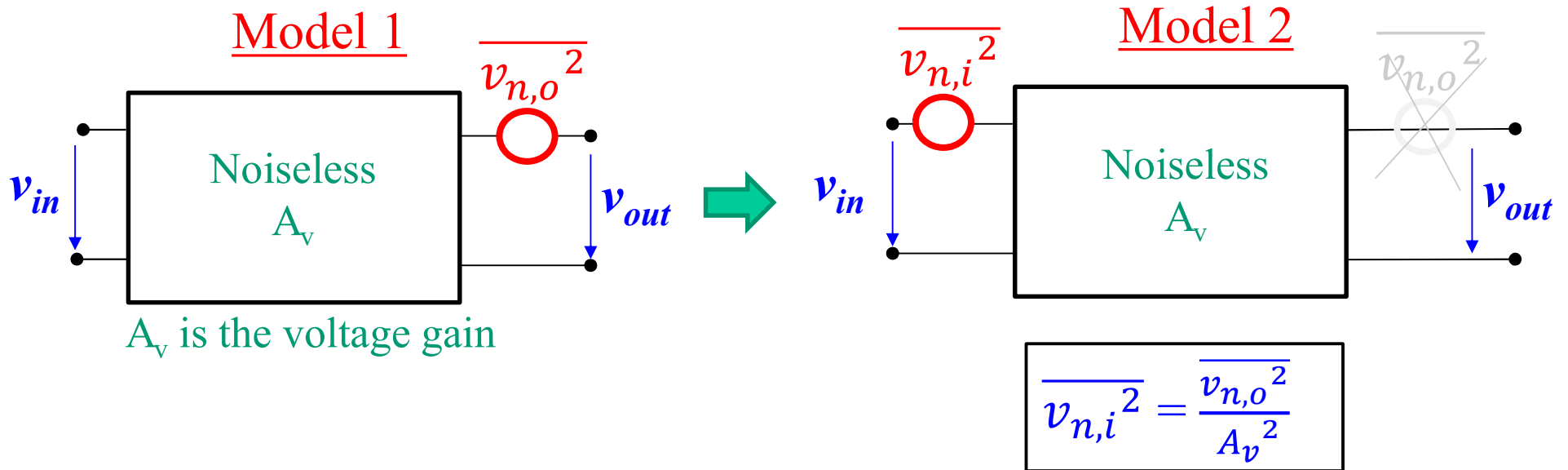


- Why is $\overline{v_{n,i}^2}$ important?:
 - Optimizing $\overline{v_{n,o}^2}$ can degrade the gain (A_v) and so the desired signal
→ Better optimize $\overline{v_{n,i}^2}$

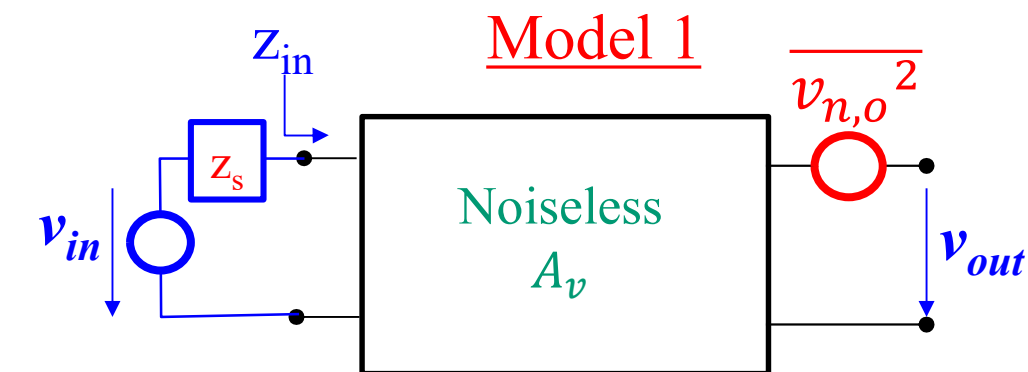Effect of source Impedance on Input-Referred Noise


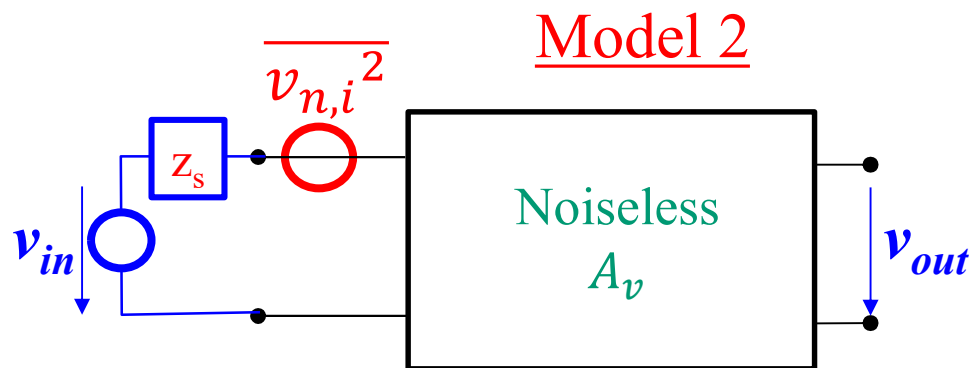
$$\overline{v_{n,i}^2} = \frac{\overline{v_{n,o}^2}}{\left(A_v \frac{Z_{in}}{Z_{in} + Z_s}\right)^2}$$




Note:

Z_s have no effect if $Z_{in} \rightarrow \infty$
(e.g. CS and CD at low-frequency)

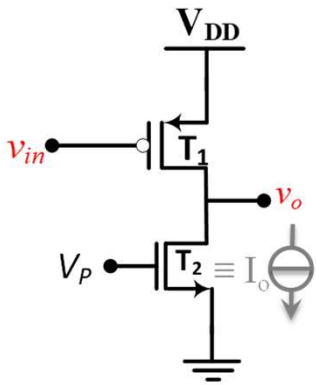Example: Noise in CS Amplifier

- Determine the input-referred voltage noise of CS amp at **low frequency** (flicker and thermal).




$$|A_v| = g_{m1} r_{o1} // r_{o2}$$

$$\overline{v_{n,o}^2} = 4kT\gamma(g_{m1} + g_{m2})(r_{o1} // r_{o2})^2 + |A_v|^2 \frac{K}{C_{ox}(LW)_1} \cdot \frac{1}{f} + \left(\frac{g_{m2}}{g_{m1}}\right)^2 |A_v|^2 \frac{K}{C_{ox}(LW)_2} \cdot \frac{1}{f}$$

$$\overline{v_{n,i}^2} = \frac{\overline{v_{n,o}^2}}{|A_v|^2} = 4kT\gamma \frac{1}{g_{m1}} \left(1 + \frac{g_{m2}}{g_{m1}}\right) + \frac{K}{C_{ox}(LW)_1} \cdot \frac{1}{f} + \left(\frac{g_{m2}}{g_{m1}}\right)^2 \frac{K}{C_{ox}(LW)_2} \cdot \frac{1}{f} \text{ [V}^2/\text{Hz]}$$


Conclusion: improve noise performances $\rightarrow$ maximize g_m of active transistor and minimize g_m of load (current source)

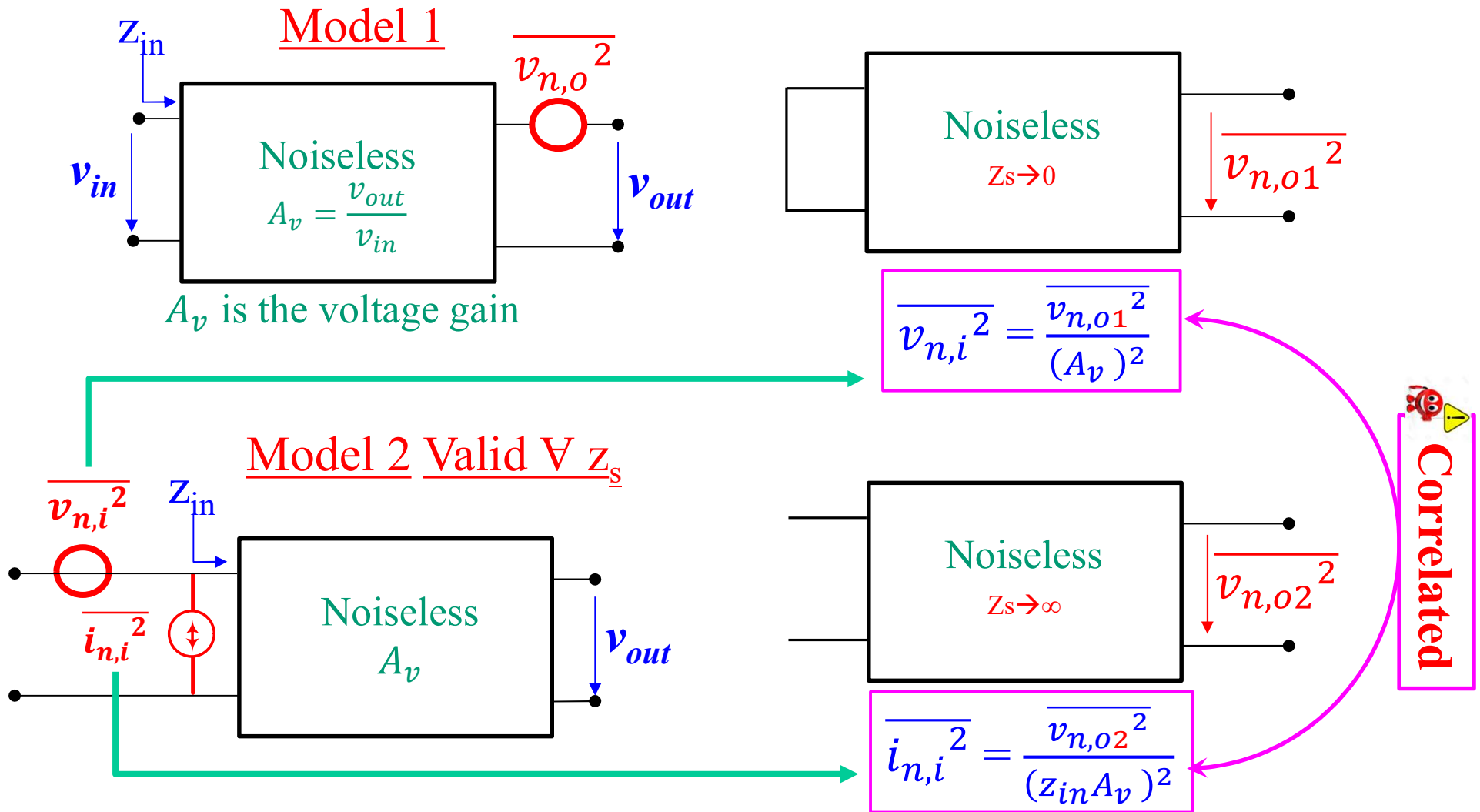Complete Input-Referred Noise Model : Valid $\forall Z_s$



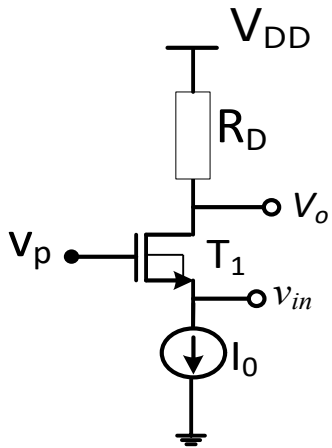Example: Noise in CG Amplifier

- Determine the output and input-referred thermal noise voltage and current of a CG amp (neglect the noise of I_0).



$$|A_v| = g_{m1} r_{o1} // R_D \approx g_{m1} R_D$$

$$Z_{in} = \frac{1}{g_{m1}} \left(1 + \frac{R_D}{r_{o1}} \right) // r_{o2} \approx \frac{1}{g_{m1}}$$


$$\overline{v_{n,0}^2} = 4kT\gamma g_{m1} R_D^2 + 4kT R_D$$

$$\overline{v_{n,i}^2} = \frac{\overline{v_{n,o1}^2}}{|A_v|^2} = 4kT\gamma \frac{1}{g_{m1}} + 4kT \frac{1}{R_D (g_{m1})^2} \quad (\text{short-circuit the input})$$

$$\overline{i_{n,i}^2} = \frac{\overline{v_{n,o2}^2}}{|Z_{in} A_v|^2} = 4kT \frac{1}{R_D} \quad (\text{open the input})$$

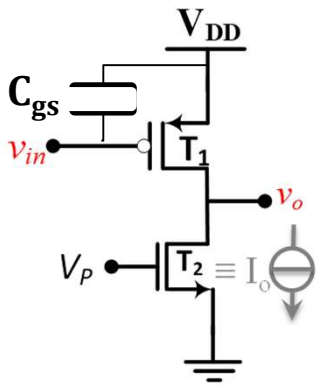Example: Noise in CS Amplifier

- Determine the input-referred current noise of CS amp at high frequency (consider C_{gs} capacitor).




$$Z_{in} = \frac{1}{j2\pi f C_{gs}}$$

$$\overline{i_{n,i}^2} = \frac{\overline{v_{no,2}^2}}{|Z_{in} A_v|^2} = (2\pi f C_{gs})^2 4kT\gamma \frac{1}{g_{m1}} \left(1 + \frac{g_{m2}}{g_{m1}}\right) + (2\pi f C_{gs})^2 \left(\frac{g_{m2}}{g_{m1}}\right)^2 \frac{K}{C_{ox}(LW)_2} \cdot \frac{1}{f} \text{ [A}^2/\text{Hz]}$$

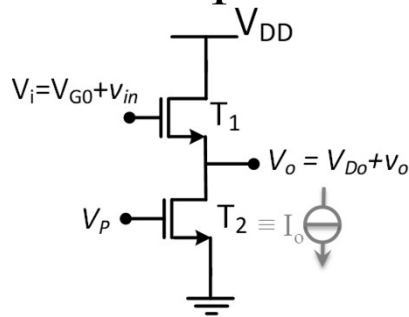Example: Noise in CD Amplifier (Source Follower)

- Determine the output and input-referred thermal noise of a Source Follower at low frequency (flicker and thermal) and comment on its noise performances.



$$|A_v| = 1$$

$$\overline{v_{n,o}^2} = 4kT\gamma(g_{m1} + g_{m2}) \left(\frac{1}{g_{m1}} \right)^2 + \frac{K}{C_{ox}(LW)_1} \cdot \frac{1}{f} + \frac{K}{C_{ox}(LW)_2} \cdot \frac{1}{f} \left(\frac{g_{m2}}{g_{m1}} \right)^2$$

$$\overline{v_{n,i}^2} = \frac{\overline{v_{n,o}^2}}{|A_v|^2} = 4kT\gamma \frac{1}{g_{m1}} \left(1 + \frac{g_{m2}}{g_{m1}} \right) + \frac{K}{C_{ox}(LW)_1} \cdot \frac{1}{f} + \left(\frac{g_{m2}}{g_{m1}} \right)^2 \frac{K}{C_{ox}(LW)_2} \cdot \frac{1}{f} \text{ [V}^2/\text{Hz]}$$

Note: $\overline{v_{n,i}^2}$ of CD is similar to CS but with no gain for the desired signal