


Operational Transconductance Amplifiers: OTA: Analysis, Design and Applications

Operational Transconductance
Amplifiers A. KOUKAB

Contents


- Single vs Multistage OpAmp
- Basic and sophisticated OTA topologies
- DC analysis
 - LF Gain
 - Input and output dynamic range
 - Common mode rejection ratio: CMRR
 - Feedback for accuracy and stability
- Frequency analysis
 - Basic OTA analysis

Why OpAmp?

 



OpAmp: Evolution

"General Purpose"

 

- Diff. gain $\rightarrow \infty$
- $R_{in} \rightarrow \infty$
- $R_{out} \rightarrow 0$
- High cost, power, area complexity...


ASICs "Specific Purpose"

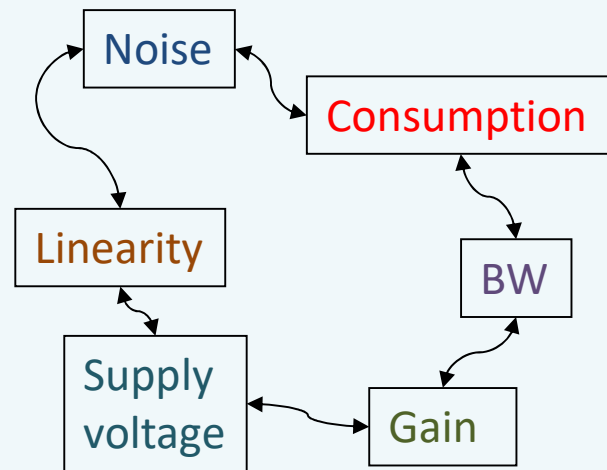 

- Usually OTA designed with Relatively
 - High gain
 - High BW
 - Low Rout
 - (depend on the load)
 - High R_{in} (usually ∞ in CMOS)
 - Optimized cost, power, area complexity...


Single vs Multistage OpAmp

One-stage

 

Gain boosting:
Cascode
Folded-Cascode
Auxiliary Amp.
Pb. Low swing


Two-stage

 

**Compensation
Tech. For
stability**

OTA for H. Gain
CS for H. Swing:


Three-stage

 

**Current Gain
Amplifier**


Flower
Class AB

Class A: Basic OTA Structures

 


➤ Simple OTA

- Limited gain
- Large output swing

 

➤ Telescopic OTA

- Boosted gain
- Low output swing

 


➤ Folded cascode OTA

- Boosted gain
- Large output swing

Contents

- Single vs Multistage OpAmp
- Basic and sophisticated OTA topologies
- AC and DC analysis
 - LF Gain
 - Common mode rejection ratio: CMRR
 - Input and output dynamic range
- Frequency analysis
 - Feedback theory: Gain vs Band Width
 - Stability
 - Basic OTA analysis

Small signal (ac): LF Gain

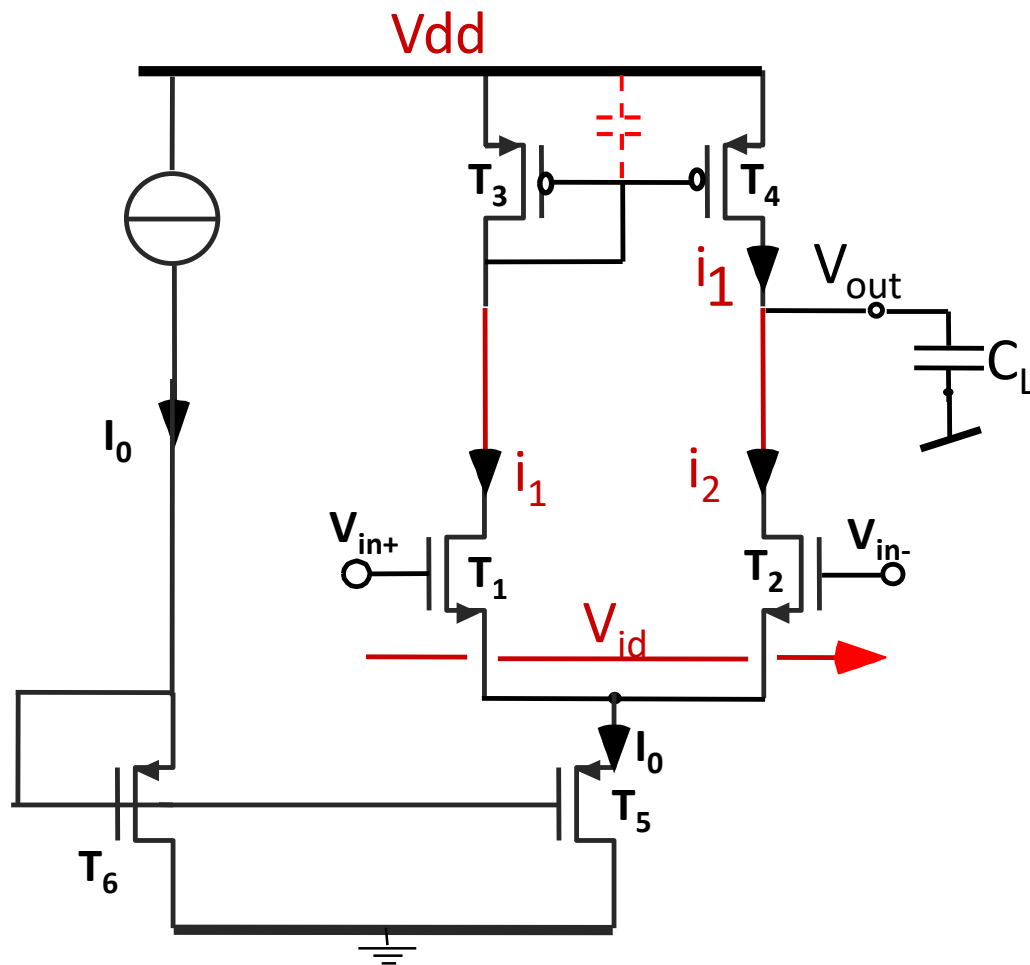

$$V_{in+} = V_{ic} + v_{in+}$$

$$V_{in-} = V_{ic} + v_{in-}$$

V_{ic} is the input DC voltage
and v_{in-} , v_{in+} the input ac diff. voltages


$$v_{id} = v_{in+} - v_{in-} = 2 v_{in+}$$

$$A = \frac{v_{out}}{v_{id}} = \frac{g_{m1,2}}{g_o}$$

$$g_o = g_{ds4} + g_{ds2}$$

- Determine the gain at LF: $A_o = V_{out}/V_{id}$?
- What would be the impact of a resistive load?

 Common Mode Gain (A_{cm}) & Rejection Ratio (CMRR)



Asymmetry + non-ideal current source
 $\rightarrow A_{cm} \neq 0$

$$A_{cm} = \frac{v_{out}}{v_{cm}} \approx \frac{-1}{2g_{m3,4}r_o^*}$$

$$CMRR = 20\log \left| \frac{A_o}{A_{cm}} \right| \approx 20\log \left(\frac{g_{m1,2}}{g_o} 2g_{m3,4}r_o^* \right)$$

- Determine A_{cm} due to the finite output resistance of the current source (suppose that the circuit is fully symmetric (*i.e.* $v_{out,DC} = v_{out,DC}^*$))
- Deduce CMRR



Analog Integrated Circuits Design (2024-25)

- **MOST Operation, Modelling**
 - [13-17 Sep](#) MOSFETs: Operation and Modelling
 - [20-24 Sep](#) Noise1 : (in time and frequency domains)
 - [27 Sep-1 Oct](#) Noise-2 : (Analog circuits noise analysis)
- **Voltage references and regulators**
 - [04 Oct](#) Current Sources and Mirrors
 - [08 Oct](#) Voltage and Temperature independent References
 - [11 Oct](#) Exercises
- **OTA and Op-Amp Design**
 - [15 Oct](#) OTA Analysis and Design (DC, AC, Stability ...) (1)
 - [18-22-25 Oct](#) Vacation
 - [29 Oct](#) OTA Analysis and Design (DC, AC, Stability ...) (2)
 - [1 Nov](#) **Lab1-a: OTA Structural Design (g_m/I_D Methodology) theory**
 - [05 Nov](#) **Lab1-b: OTA Structural Design (g_m/I_D Methodology) Lab (CO5)**
 - [08 Nov](#): Multistage OTA (Stability and Frequency Compensation)
 - [12 Nov](#): Fully-Diff Amplifiers & CMFB
 - [15 Nov](#): Variability, offset and noise in OpAmp (1)
 - [19 Nov](#) **Lab2: Fully diff doloed cascode amplifier & its CMFB (CO5)**
 - [22 Nov](#): Variability, offset and noise in OpAmp (2)
 - [26 Nov](#): Rail to Rail input and output amplifiers
- **Mixed-signal design**
 - [29 Nov](#): Comparators
 - [03 Dec](#) **Lab3: Comparators (CO5)**
 - [06-10 Dec](#): AD and DA converters (introduction)
 - [13 Dec](#): Digital calibration of analog circuits
- [20 Dec](#) General revision (zoom)

Output Dynamic Range

Dynamic Range = ratio between **smallest** and **largest** signal that the system can process


Distortion

  


highest level,
determined by
distortion

lowest level,
determined by
noise

Noise

 

Large signal: Output Dynamic

 


$$V_{out,max} = V_{dd} - V_{SD,sat4}$$

$$= V_{dd} - (V_{SG4} - V_{Tp})$$

$$V_{out,min} = V_{D,sat2} = V_{in,DC} - V_{Tn}$$

- Determine $V_{out,max}$ and $V_{out,min}$? (all the transistors in strong inversion, $V_{in,DC}$ is set by a biasing circuit (e.g. to $V_{DD}/2$))

Large signal: T_1, T_2 in weak inversion

 


$$\begin{aligned} V_{out,max} &= V_{dd} - V_{SD,sat4} \\ &= V_{dd} - (V_{SG4} - V_{Tp}) \end{aligned}$$

$$\begin{aligned} V_{out,min} &= V_{S2} + V_{DS,sat2} \\ &\approx (V_{in,DC} - V_{SG2}) + 4U_T \\ &\approx (V_{in,DC} - V_{Tn}) + 4U_T \end{aligned}$$

- Determine $V_{out,max}$ and $V_{out,min}$ (T_1 and T_2 in weak inversion (wi))?

Large signal: Input Common Mode Range

 

$$V_{in+} = V_{ic} + v_{in+}$$

$$V_{in-} = V_{ic} + v_{in-} = V_{ic} - v_{in+}$$

$$\begin{aligned} V_{ic,max} &= \text{Max}(V_{cm}) \\ &= V_{dd} - V_{SG3} + V_{Tn} \end{aligned}$$


$$\begin{aligned} V_{ic,min} &= \text{Min}(V_{cm}) \\ &= V_{GS1} + V_{Dsat5} \\ &= V_{GS1} + (V_{GS5} - V_{T05}) \end{aligned}$$

- Determine $V_{ic,max}$ and $V_{ic,min}$


Contents

- Single vs Multistage OpAmp
- Basic and sophisticated OTA topologies
- AC and DC analysis
 - LF Gain
 - Common mode rejection ratio: CMRR
 - Input and output dynamic range
- Frequency analysis
 - Basic OTA analysis

OTA- Frequency analysis

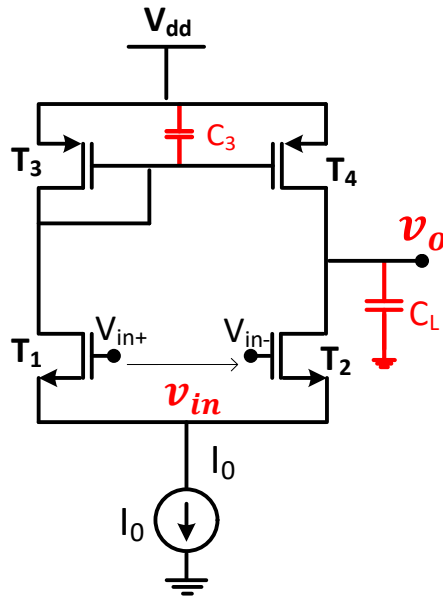

$$H(s) = \frac{v_o}{v_{in}} = ?$$

 

ac model with parasitic capacitors

$$v_o = \left(g_{m4,3} v_{sg4} + \frac{g_{m2,1} v_{in}}{2} \right) \frac{1}{g_o} \frac{1}{1 + s \frac{C_L}{g_o}}$$

i_o
 $\times \frac{1}{g_o} // C_L$

$$v_{sg4} = \frac{g_{m1,2} v_{in}}{2} \frac{1}{g_{m3,4}} \frac{1}{1 + s \frac{C_3}{g_{m3,4}}}$$


$\frac{1}{g_{m3,4}} // C_3$

$g_{m1} = g_{m2}$ and $g_{m3} = g_{m4}$

$$v_o = \frac{g_{m1,2} v_{in}}{2} \left(1 + \frac{1}{1 + s \frac{C_3}{g_{m3,4}}} \right) \frac{1}{g_o} \frac{1}{1 + s \frac{C_L}{g_o}}$$

i_o

OTA- Frequency analysis

 

$$v_o = \frac{g_{m1,2} v_{in}}{2} \left(1 + \frac{1}{1 + s \frac{C_3}{g_{m3,4}}} \right) \frac{1}{g_o} \frac{1}{1 + s \frac{C_L}{g_o}}$$

$$v_o = \frac{g_{m1,2} v_{in}}{2} \left(\frac{2 + s \frac{C_3}{g_{m3,4}}}{1 + s \frac{C_3}{g_{m3,4}}} \right) \frac{1}{g_o} \frac{1}{1 + s \frac{C_L}{g_o}}$$


$$H(s) = \frac{v_o}{v_{in}} = \underbrace{A_o}_{\text{DC Gain}} \underbrace{\left(\frac{1 + s \frac{C_3}{2g_{m3,4}}}{\left(1 + s \frac{C_3}{g_{m3,4}} \right) \left(1 + s \frac{C_L}{g_o} \right)} \right)}_{\text{Zero, N Dom Pole, Dom. Pole}}$$

$$\begin{aligned} \omega_{p1} &= \frac{g_o}{C_L} \\ \omega_{p2} &= \frac{g_{m3,4}}{C_3} \\ \omega_z &= \frac{2g_{m3,4}}{C_3} \end{aligned}$$

$$\begin{aligned} \text{GBW} &= A_o \omega_{p1} \\ &= \frac{g_{m1,2}}{C_L} \end{aligned}$$

Bode Plot
 
$$H(s) = \frac{V_{out}}{V_{in}} = A_o \left(\frac{1 + j \frac{\omega}{\omega_z}}{\left(1 + j \frac{\omega}{\omega_{p1}}\right) \left(1 + j \frac{\omega}{\omega_{p2}}\right)} \right)$$



$$A_o = \frac{g_{m1,2}}{g_o}$$

$$\omega_{p1} = \frac{g_o}{C_L} : \text{dominant pole}$$

$$\omega_{p2} = \frac{g_{m3,4}}{C_3} : \text{non-dominant pole}$$


$$\omega_z = 2\omega_{p2} = \frac{2g_{m3,4}}{C_3} : \text{zero}$$

$$\omega_u = \omega_{GBW} = A_o \omega_{p1} = \frac{g_{m1,2}}{C_L}$$

$$\text{Ph}(H(j\omega)) \approx \text{Arctg}(\omega/\omega_z) - \text{Arctg}(\omega/\omega_{p1}) - \text{arctg}(\omega/\omega_{p2})$$

Miller Effect

 
- the Miller effect accounts for the increase in the equivalent input capacitance of an inverting voltage amplifier due to amplification of the effect of capacitance between the input and output terminals.



$$Z_1 = \frac{v_1}{i_1} = \frac{v_1}{\frac{v_1 + A_o v_1}{Z_C}} = \frac{1}{j\omega C(1 + A_o)}$$

$$Z_2 = \frac{-A_o v_1}{i_2} = \frac{-A_o v_1}{\frac{-A_o v_1 - v_1}{Z_C}} = \frac{1}{j\omega C(1 + A_o^{-1})}$$


$\omega_{p2} = ? : \text{Miller effect}$

 

- $C_p \approx C_{gs3} + C_{gs4} \approx 2 \frac{2}{3} C_{ox} W_3 L_3$
- $C^* \approx A_{T4} C_{gd4} \approx \frac{g_{m4}}{g_o} C_{gd4} \approx \frac{g_{m4}}{g_o} W_4 C_{gd.ov}$
- $C_3 = C_p + C^*$

$$\omega_{p2} = \frac{g_{m3,4}}{C_3} = \frac{g_{m3,4}}{\frac{4}{3} C_{ox} W_3 L_3 + \frac{g_{m4}}{g_o} W_3 C_{gd.ov}}$$

OTA stability

 

$$H(s) = \frac{V_{out}}{V_{in}} = A_o \left(\frac{1 + j \frac{\omega}{\omega_z}}{\left(1 + j \frac{\omega}{\omega_{p1}}\right) \left(1 + j \frac{\omega}{\omega_{p2}}\right)} \right)$$

Phase Margin for stability

$$PM = \text{Ph}(H(j\omega_{GBW})) - (-180) \approx$$

$$\arctg(\omega_{GBW}/\omega_z) \rightarrow \approx 0^\circ (\omega_{GBW} \ll \omega_z)$$

$$- \arctg(\omega_{GBW}/\omega_{p1}) \rightarrow \approx -90^\circ (\omega_{p1} \ll \omega_{GBW})$$

$$- \arctg(\omega_{GBW}/\omega_{p2}) \approx ?$$



$$+ 180$$

(Stability over PVT variation) $\rightarrow$ Phase-Margin $PM \approx 60^\circ - 70^\circ \rightarrow \underline{\omega_{p2} \approx 3 \omega_{GBW}}$

$$\equiv \frac{g_{m3,4}}{C_3} \geq 3 \frac{g_{m1,2}}{C_L}$$

OTA-Slew Rate

  - Slew Rate (Sr) $\equiv$ maximum rate of change possible for the output voltage
- Sr limited by the currents charging and discharging the capacitors of Amps.



$$Sr = \frac{dV_{out}}{dt} = \frac{I_0}{C_L} \quad GBW = \frac{g_{m1}}{C_L} = \frac{g_{m1}}{I_0} \frac{I_0}{C_L} \quad \frac{GBW}{Sr} = \frac{g_{m1}}{I_0} = \frac{1}{2} \frac{g_{m1}}{I_{D1}}$$


During OTA design: usually, Sr gives I_0 and GBW gives g_m

Slew Rate consequences

- Ex: $U_{\text{out}} = \hat{U}_{\text{out}} \sin(\omega t) \rightarrow (dU_{\text{out}}/dt)_{\text{max}} = \hat{U}_{\text{out}} \omega$

If $\hat{U}_{\text{ou}} \omega > \text{Sr}$

 → large signal mode → Speed limited by Sr
i.e. distortion occurs even if $\omega < \omega_{\text{BW}}$



Circuit Level Tradeoffs

Consumption/Speed	$I_0 V_{DD} = S_R \cdot C_L \cdot V_{DD}$
Gain / BW	$GBW = g_m / (2\pi C_L)$
$I_{F,diff}$	$\frac{g_m}{I_D} = \frac{1}{nU_T} \cdot \frac{2}{1 + \sqrt{4I_F + 1}}$
Size	$I_F = \frac{I_D}{I_s} = \frac{I_D}{2n\mu C_{ox} \frac{W}{L} U_T^2}$
DC Gain	$g_m R_{out} = g_m / I_D \cdot [(\mathbf{L}_n U_{an})^{-1} + (\mathbf{L}_p U_{ap})^{-1}]^{-1}$
Stability	$\frac{g_{m, mir}}{C_{mir}} \geq 3 \frac{g_{m, diff}}{C_L}$
Noise & Offset	