

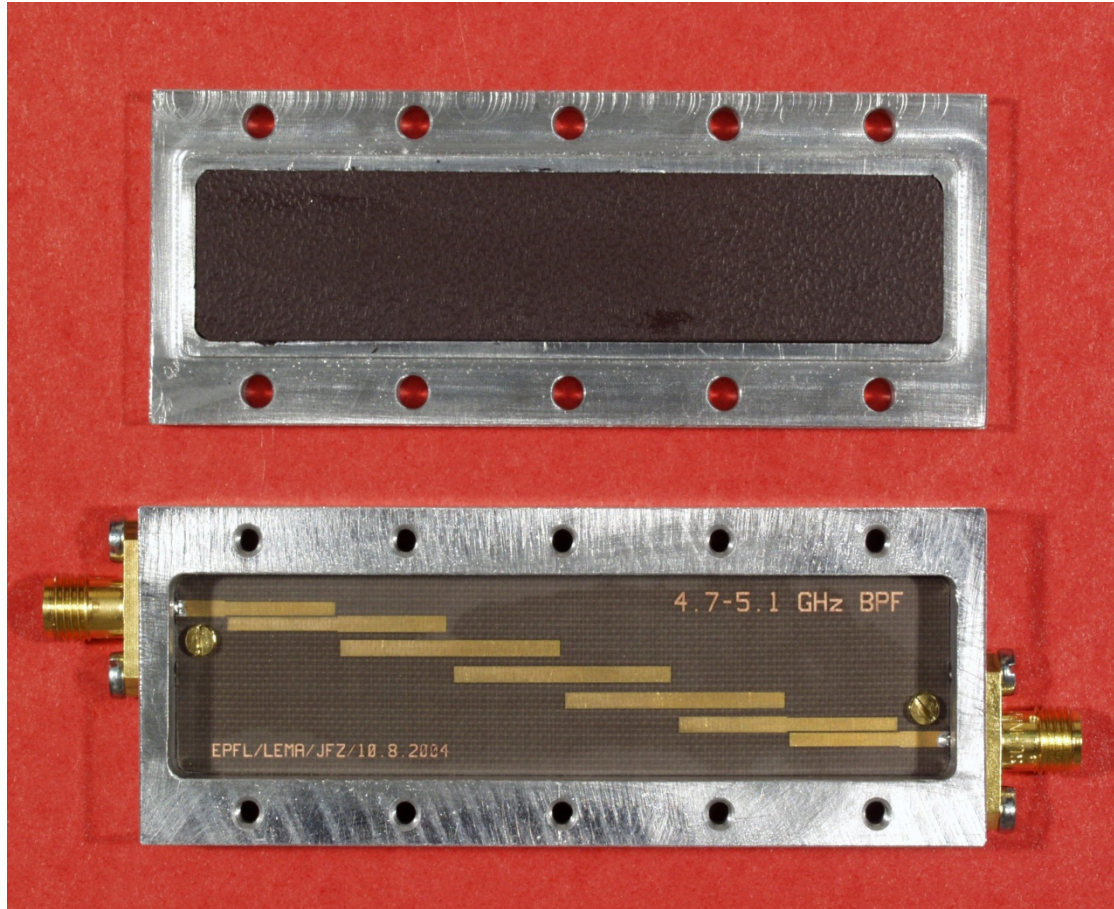



Transmission lines


Chapter 3

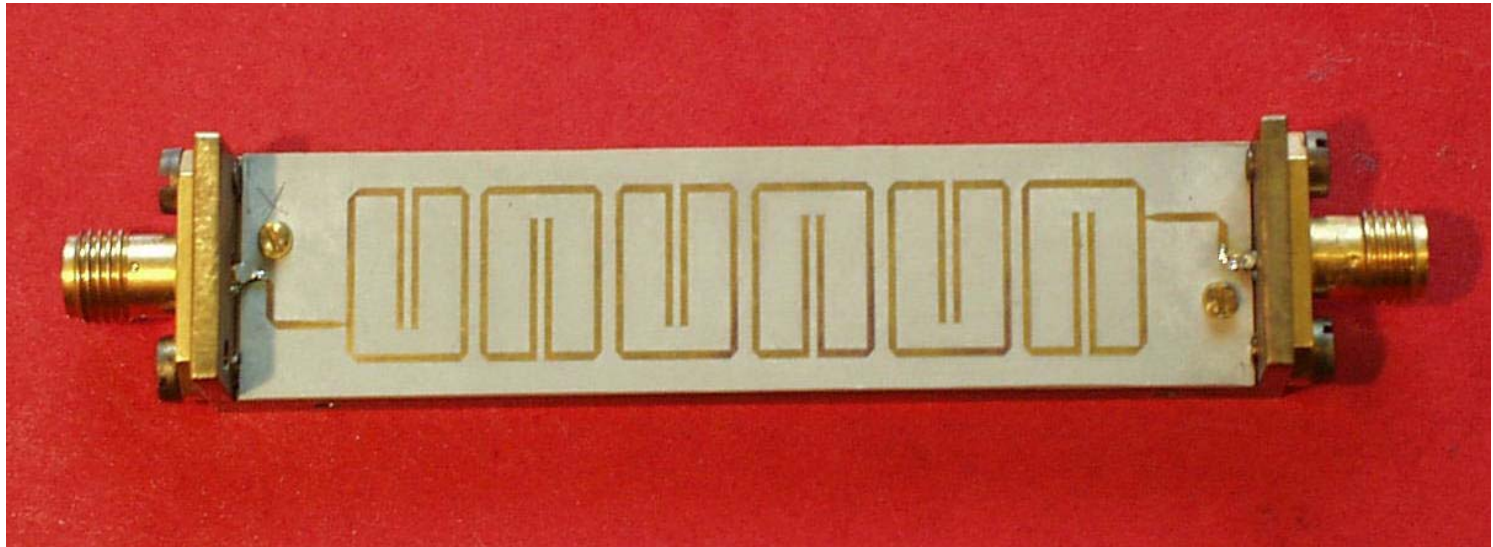


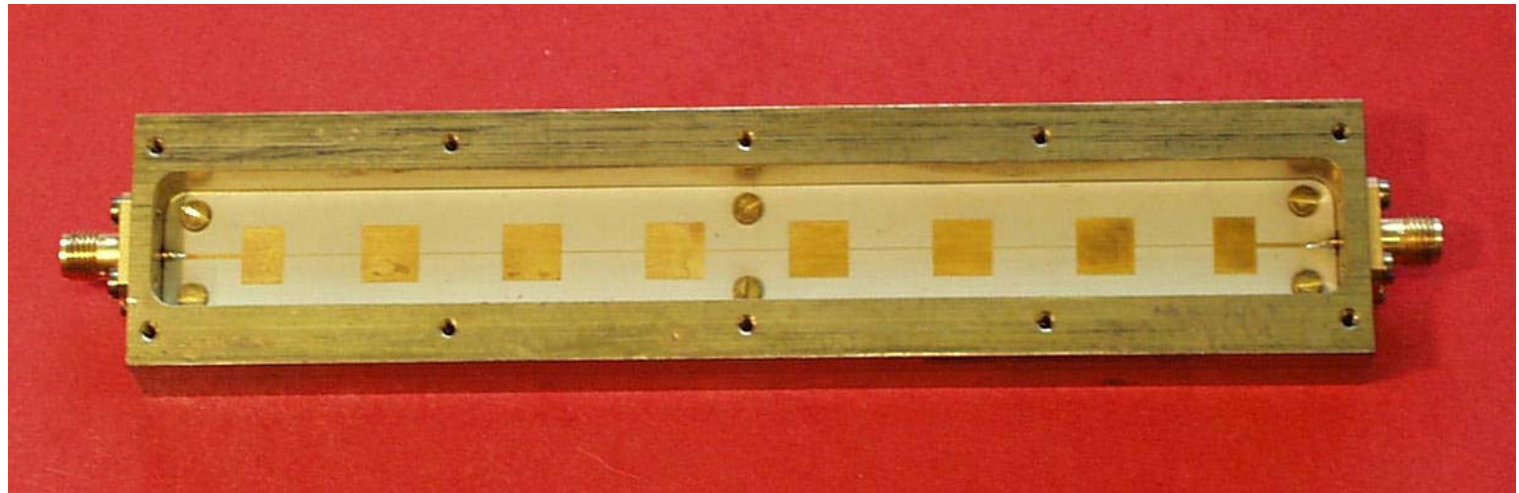





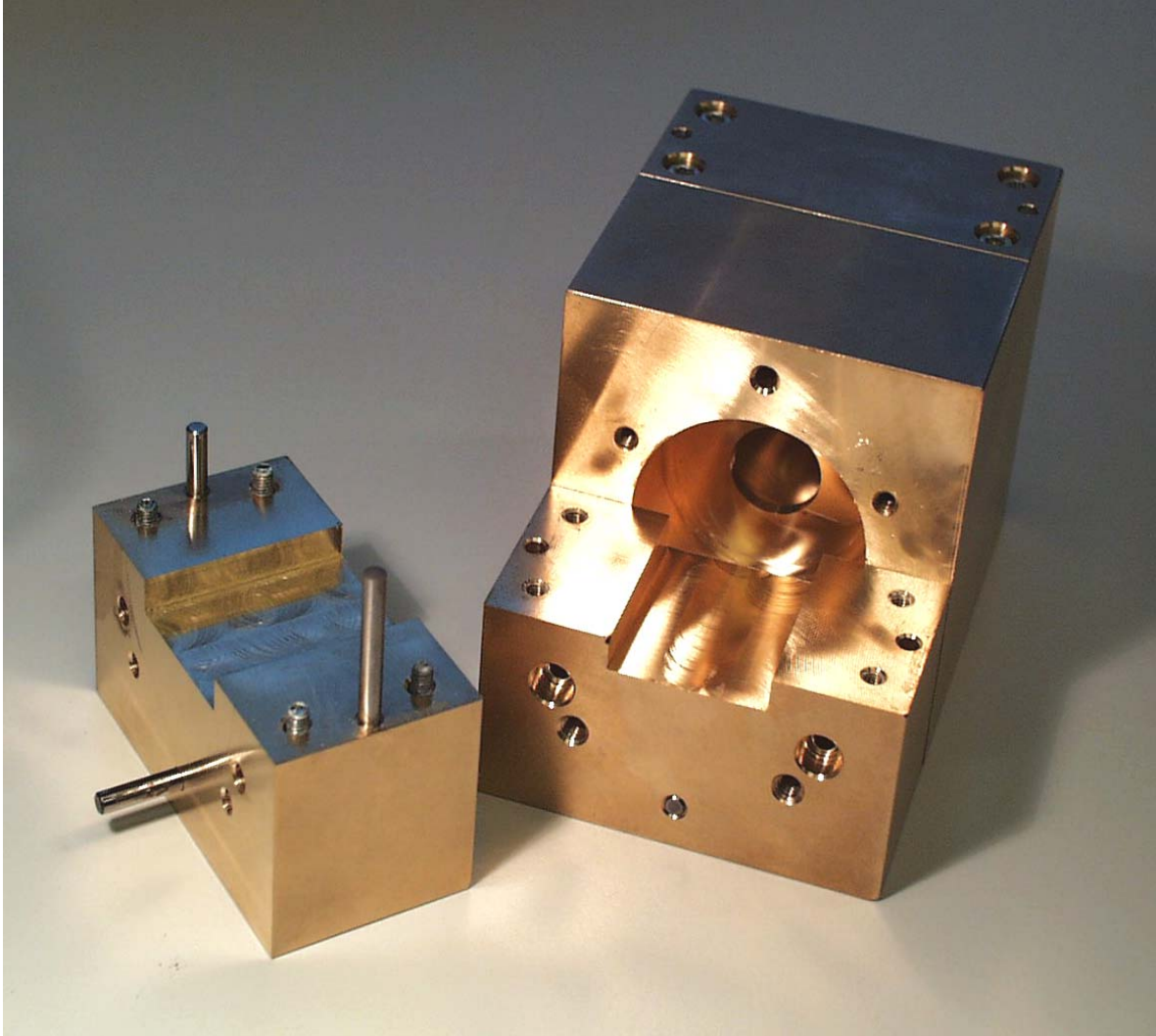


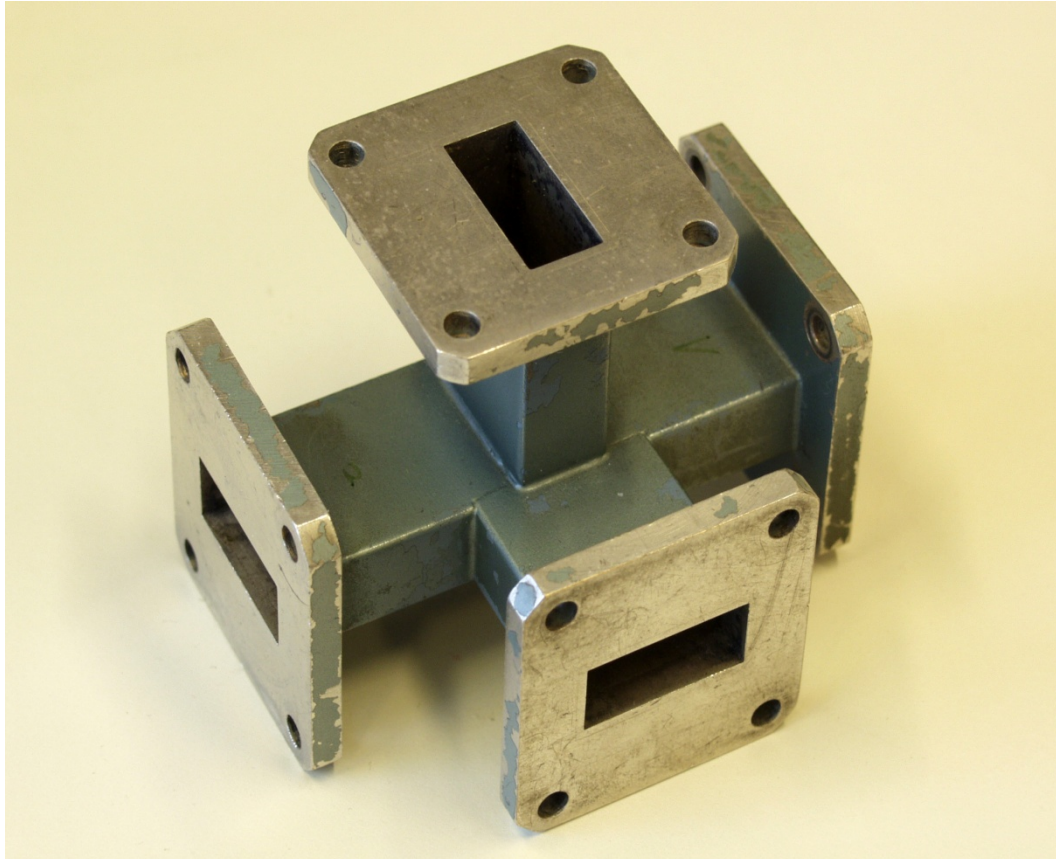


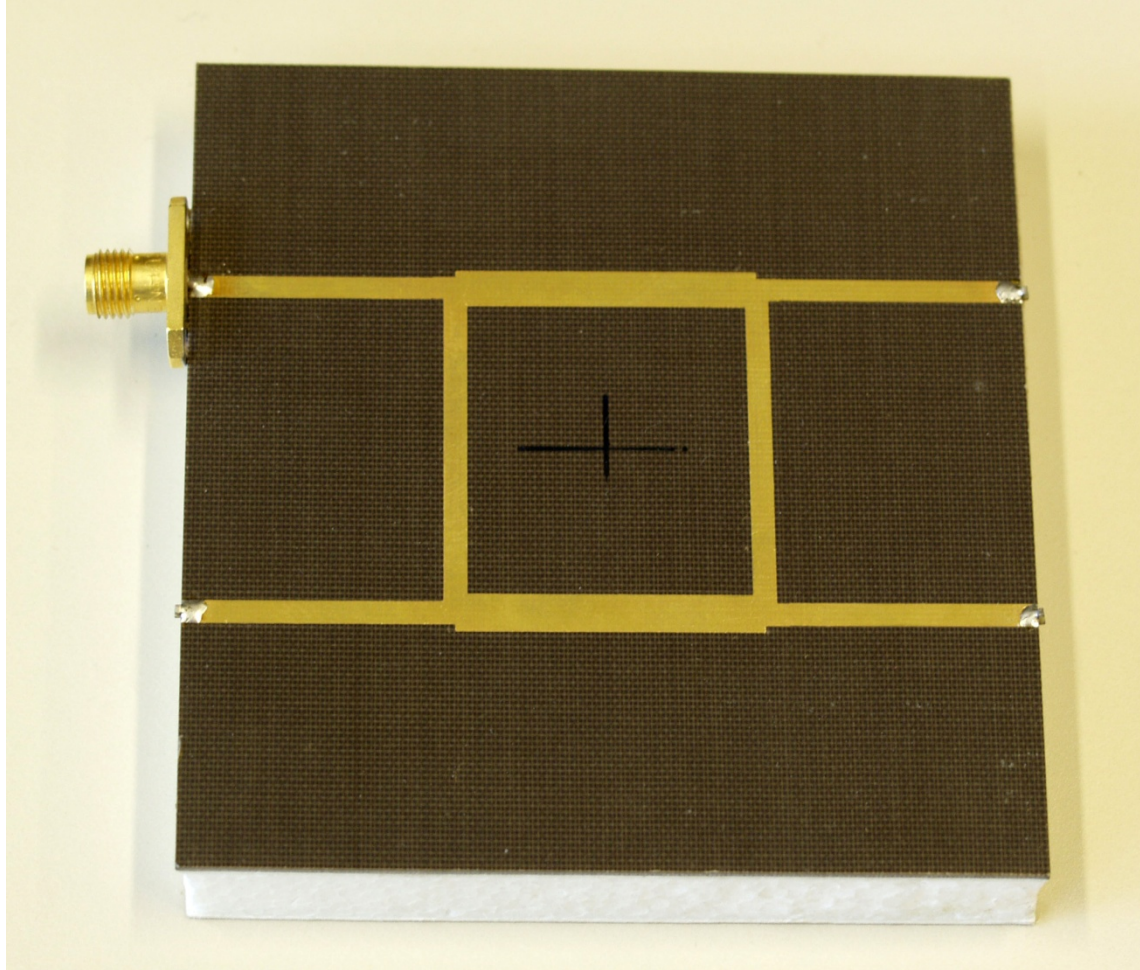

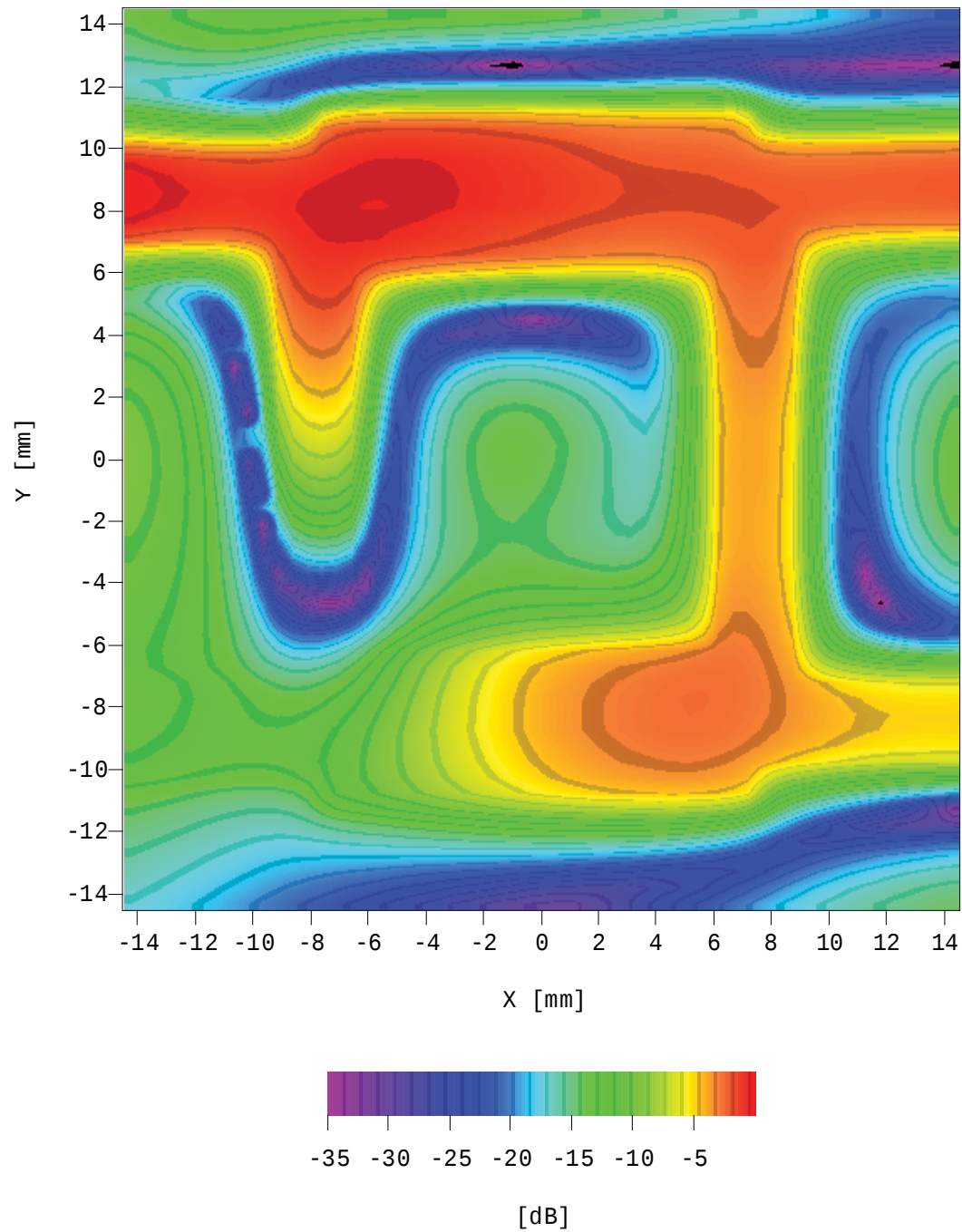

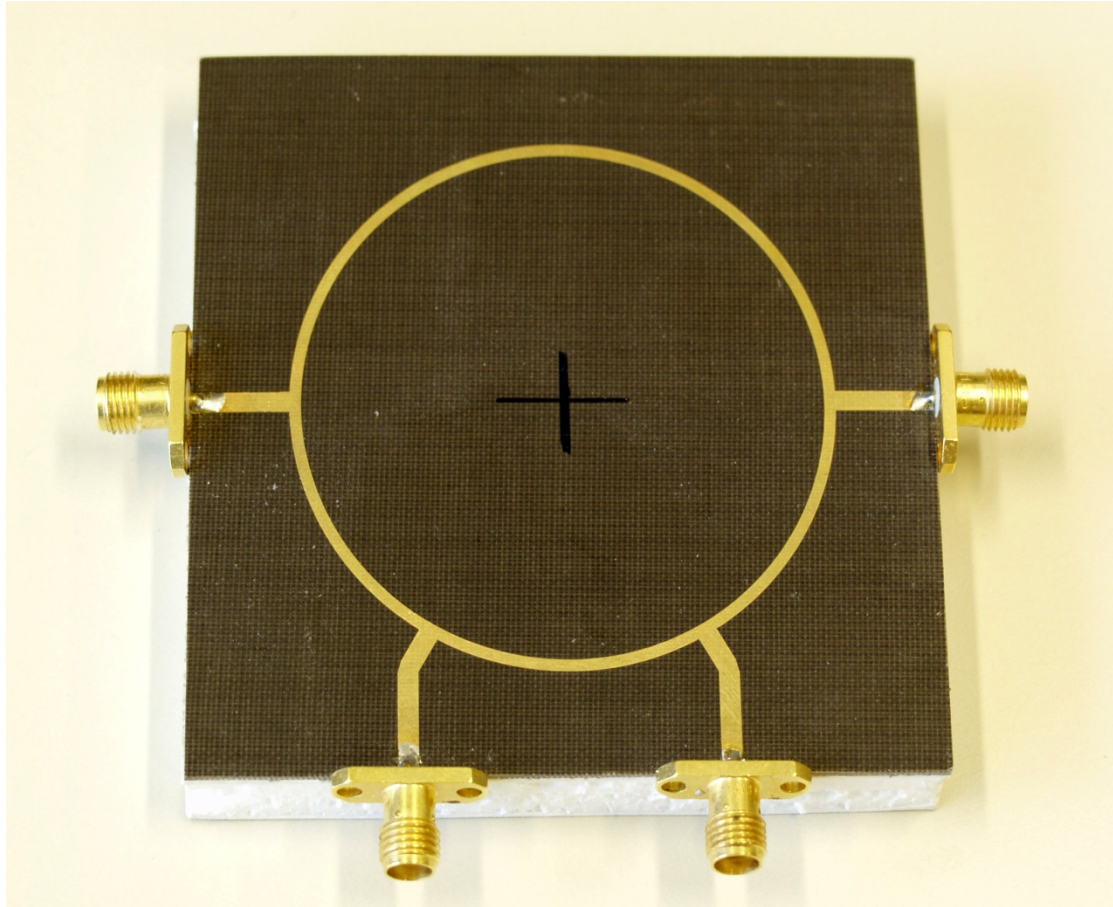


Incremental model (1)

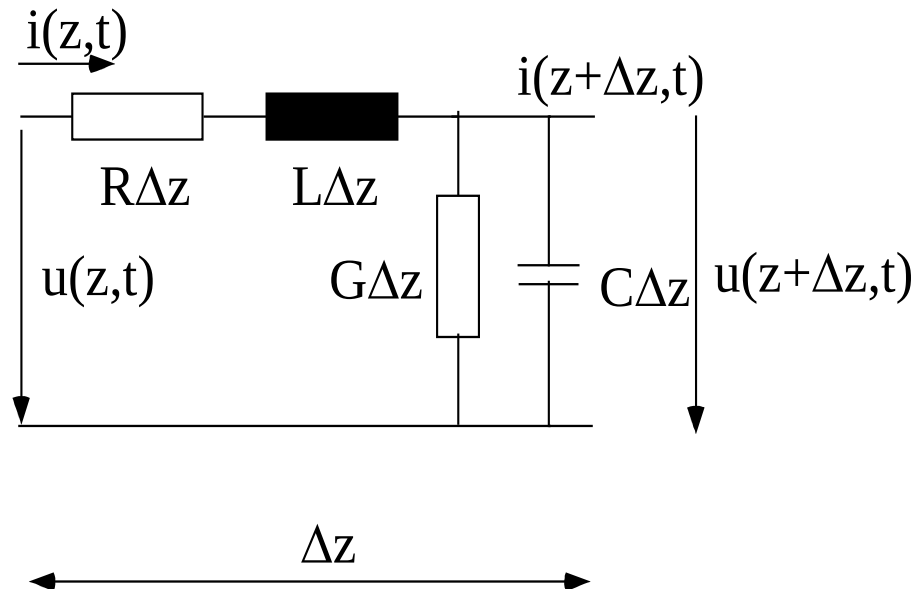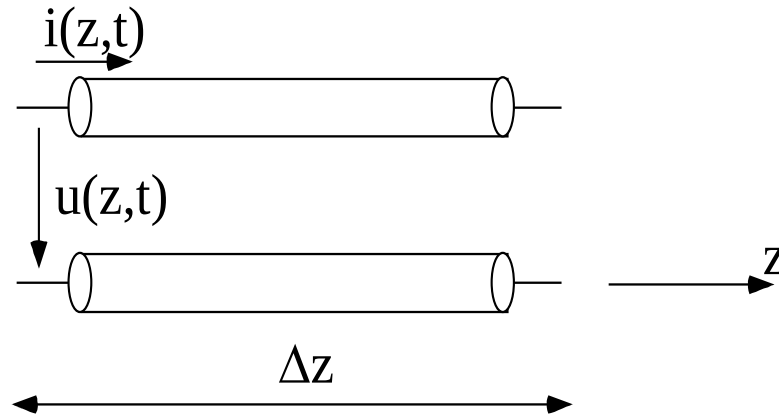

Incremental model (2)

Kirchhoff's laws : $v(z,t) - R\Delta z i(z,t) - L\Delta z \frac{\partial i(z,t)}{\partial t} - v(z + \Delta z, t) = 0$
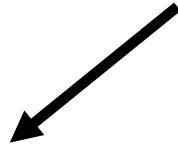
$$i(z,t) - G\Delta z v(z + \Delta z, t) - C\Delta z \frac{\partial v(z + \Delta z, t)}{\partial t} - i(z + \Delta z, t) = 0$$



$$\frac{\partial v(z,t)}{\partial z} = -Ri(z,t) - L \frac{\partial i(z,t)}{\partial t}$$

$$\frac{\partial i(z,t)}{\partial z} = -Gv(z,t) - C \frac{\partial v(z,t)}{\partial t}$$



$$\frac{dV(z)}{dz} = -(R + j\omega L)I(z)$$

$$\frac{dI(z)}{dz} = -(G + j\omega C)V(z)$$

Incremental model (3)

$$\begin{aligned}\frac{d^2 V(z)}{dz^2} - \gamma^2 V(z) &= 0 \\ \frac{d^2 I(z)}{dz^2} - \gamma^2 I(z) &= 0\end{aligned}$$

with

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

Incremental model (4)

Solutions :

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$$

$$I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}$$

or :

$$I(z) = \frac{\gamma}{R + j\omega L} \left(V_0^+ e^{-\gamma z} - V_0^- e^{\gamma z} \right)$$

$$I(z) = \frac{V_0^+}{Z_o} e^{-\gamma z} - \frac{V_0^-}{Z_o} e^{\gamma z} \quad \text{with} \quad Z_o = \frac{R + j\omega L}{\gamma} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

Incremental model (5)

wave length : $\lambda = 2\pi/\beta$

Phase velocity : $v_\phi = dz/dt = \omega/\beta = \lambda f$


$$\gamma = j\beta = j\omega\sqrt{LC}$$
$$Z_o = \sqrt{\frac{L}{C}}$$

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}$$
$$I(z) = I_0^+ e^{-j\beta z} + I_0^- e^{j\beta z} = \frac{V_0^+}{Z_o} e^{-j\beta z} - \frac{V_0^-}{Z_o} e^{j\beta z}$$

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{\omega\sqrt{LC}}$$

$$v_\phi = \frac{dz}{dt} = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$

Terminated lines (1)

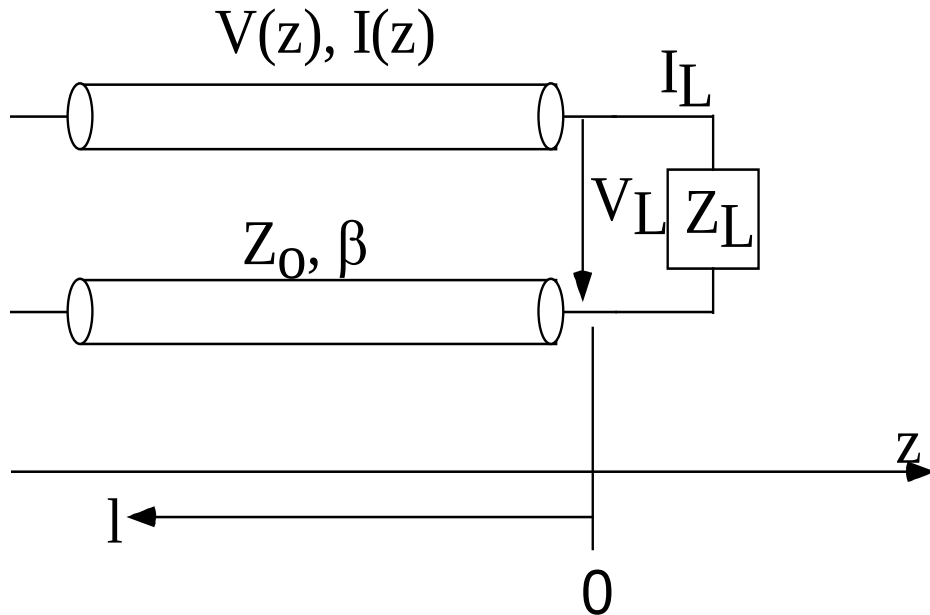

$$Z_L = \frac{V(0)}{I(0)} = \frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} Z_0$$

$$V_0^- = \frac{Z_L - Z_0}{Z_L + Z_0} V_0^+$$

$$\Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$V(z) = V_0^+ \left(e^{-j\beta z} + \Gamma e^{j\beta z} \right)$$

$$I(z) = \frac{V_0^+}{Z_o} \left(e^{-j\beta z} - \Gamma e^{j\beta z} \right)$$


$$P_{av} = \operatorname{Re} \left[V(z) I^*(z) \right] = \frac{|V_o^+|^2}{Z_o} \operatorname{Re} \left[1 - \Gamma^* e^{-2j\beta z} + \Gamma e^{2j\beta z} - |\Gamma|^2 \right]$$

$$P_{av} = \operatorname{Re} \left[V(z) I^*(z) \right] = \frac{|V_o^+|^2}{Z_o} (1 - |\Gamma|^2)$$

Terminated lines (3)

Losses due to mismatch : $RL = -20\log_{10}|\Gamma|$ dB

Terminated lines : VSWR

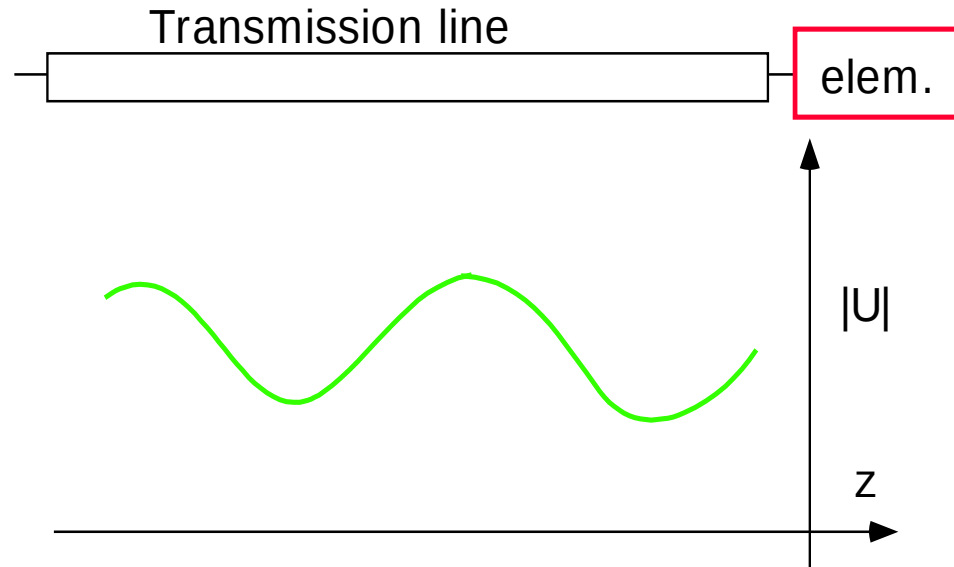

$$|V(z)| = |V_0^+| \left| 1 + \Gamma e^{2j\beta z} \right| = |V_0^+| \left| 1 + \Gamma e^{-2j\beta l} \right| = |V_0^+| \left| 1 + |\Gamma| e^{j(\theta - 2\beta)l} \right|$$

$$\Gamma(l) = \frac{V_0^- e^{-j\beta l}}{V_0^+ e^{j\beta l}} = \Gamma(0) e^{-2j\beta l}$$

$$|V(z)| = |V_0^+| \left| 1 + \Gamma e^{2j\beta z} \right| = |V_0^+| \left| 1 + \Gamma e^{-2j\beta l} \right| = |V_0^+| \left| 1 + |\Gamma| e^{j(\theta - 2\beta)l} \right|$$




$$V_{\max} = |V_0^+| (1 + |\Gamma|)$$


$$V_{\min} = |V_0^+| (1 - |\Gamma|)$$



$$SWR = \frac{V_{\max}}{V_{\min}} = \frac{(1 + |\Gamma|)}{(1 - |\Gamma|)}$$

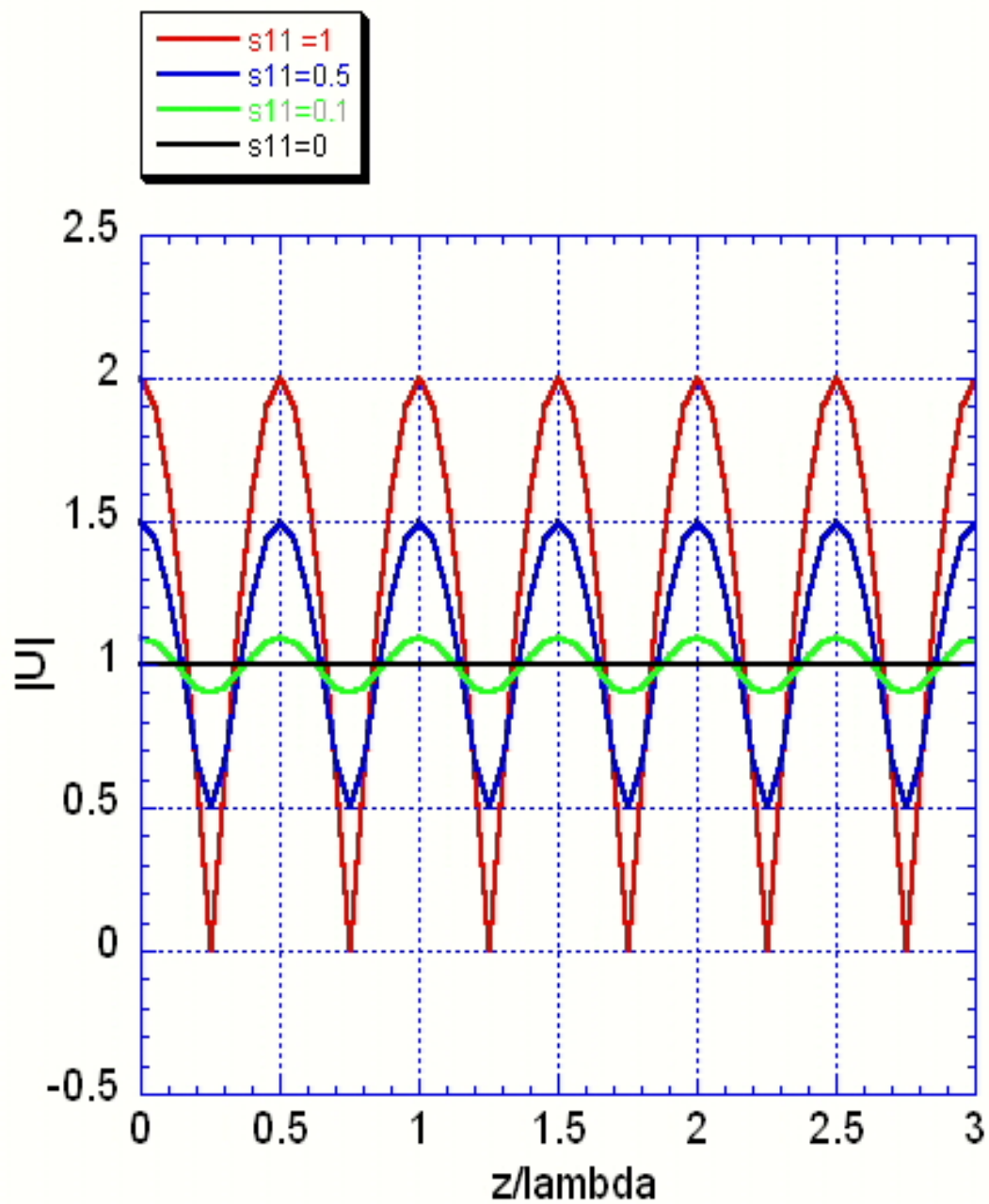

EPFL Terminated lines : input impedance

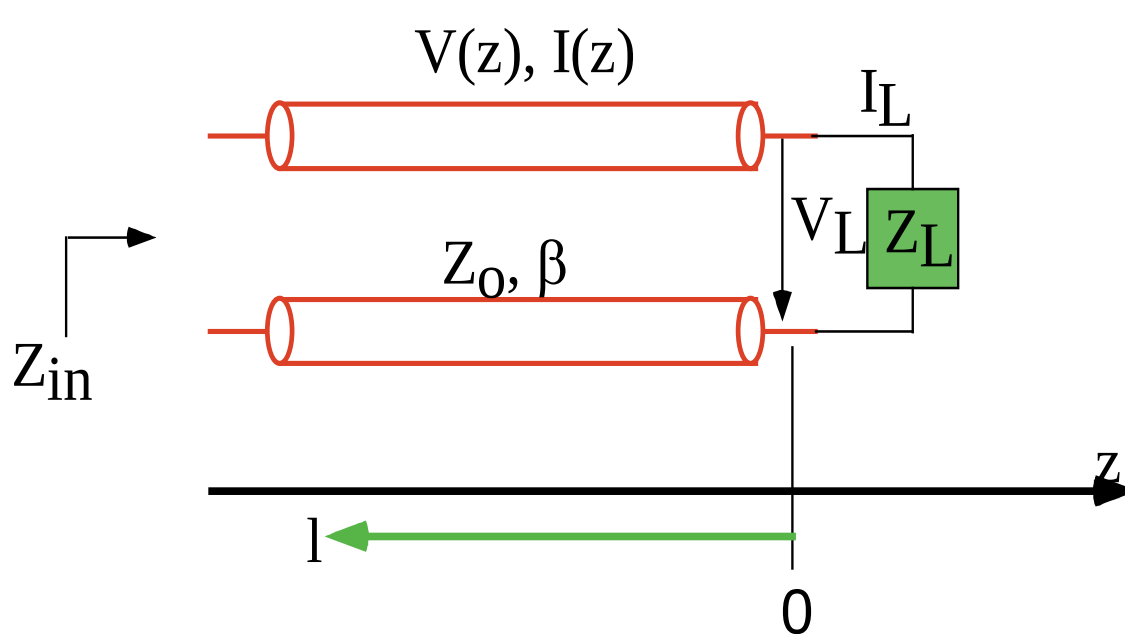


$$\begin{aligned}
 Z_{in} &= \frac{V(-l)}{I(-l)} \\
 &= Z_0 \frac{V_0^+ (e^{j\beta l} + \Gamma e^{-j\beta l})}{V_0^+ (e^{j\beta l} - \Gamma e^{-j\beta l})} \\
 &= Z_0 \frac{1 + \Gamma e^{-j2\beta l}}{1 - \Gamma e^{-j2\beta l}}
 \end{aligned}$$

EPFL Terminated lines : input impedance

Thus, using $\Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_o}{Z_L + Z_o}$
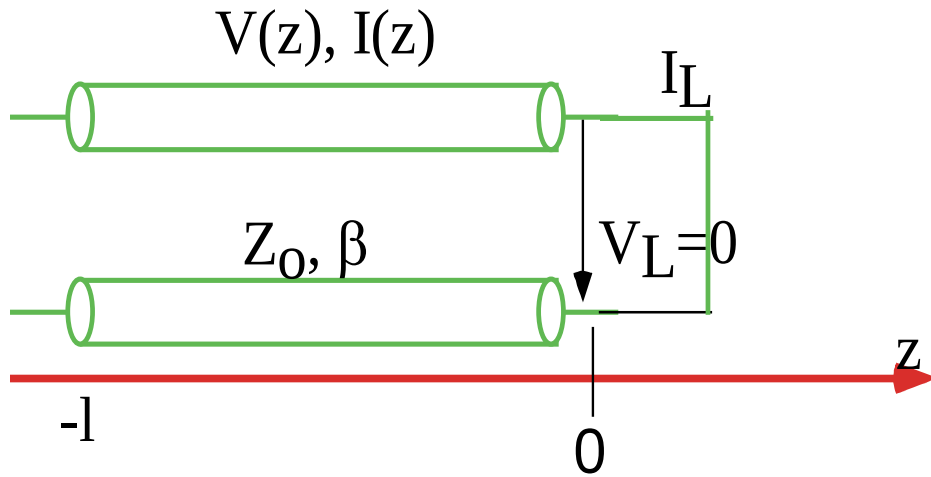
$$\begin{aligned} Z_{in} &= Z_o \frac{(Z_L + Z_o)e^{j\beta l} + (Z_L - Z_o)e^{-j\beta l}}{(Z_L + Z_o)e^{j\beta l} - (Z_L - Z_o)e^{-j\beta l}} = Z_o \frac{Z_L \cos \beta l + jZ_o \sin \beta l}{Z_o \cos \beta l + jZ_L \sin \beta l} \\ &= Z_o \frac{Z_L + jZ_o \tan \beta l}{Z_o + jZ_L \tan \beta l} \end{aligned}$$






$$V(z) = V_0^+ \left(e^{-j\beta z} - e^{j\beta z} \right) = -2jV_0^+ \sin \beta z$$

$$I(z) = \frac{V_0^+}{Z_0} \left(e^{-j\beta z} + e^{j\beta z} \right) = \frac{2V_0^+}{Z_0} \cos \beta z$$




$$Z_{in} = jZ_0 \tan \beta z$$

Terminated lines : short circuit

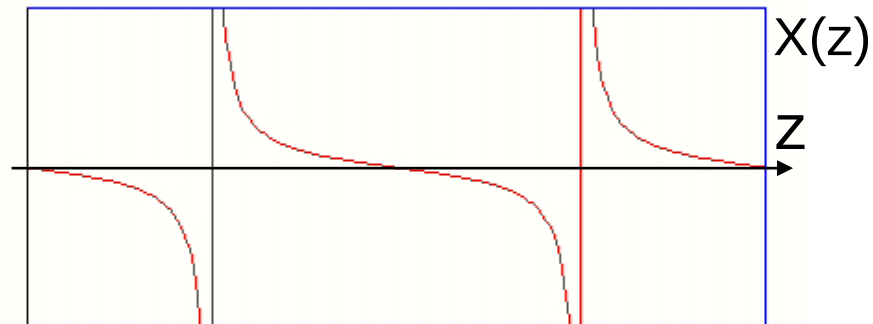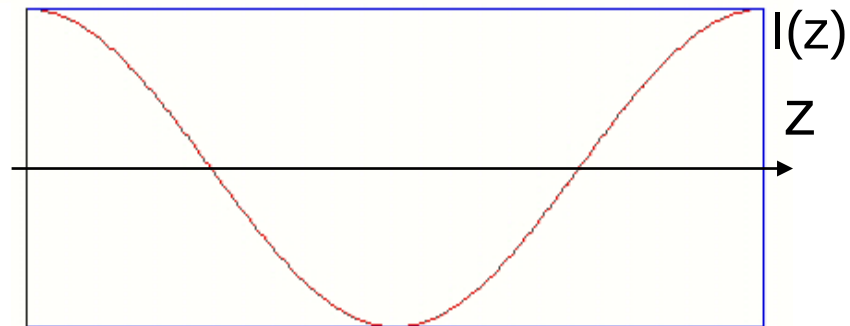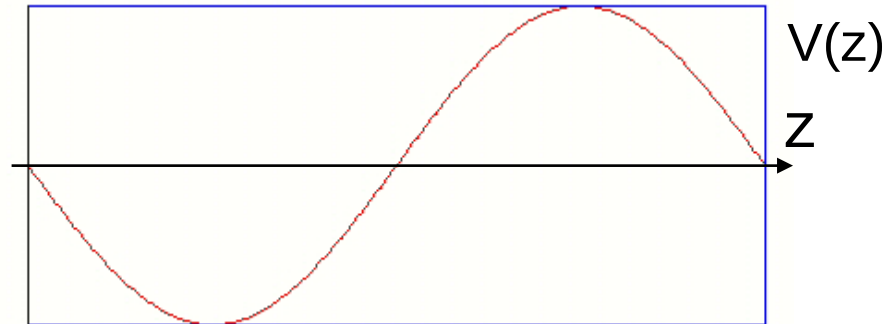

Terminated lines : open circuit

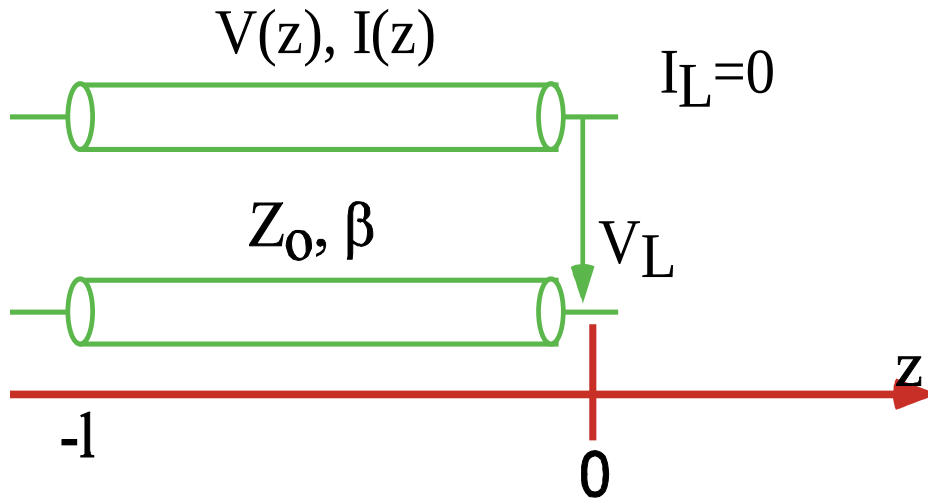



$$V(z) = V_0^+ \left(e^{-j\beta z} + e^{j\beta z} \right) = 2V_0^+ \cos \beta z$$

$$I(z) = \frac{V_0^+}{Z_o} \left(e^{-j\beta z} - e^{j\beta z} \right) = \frac{-2jV_0^+}{Z_o} \sin \beta z$$




$$Z_{in} = -jZ_o \cot \beta z$$

Terminated lines : open circuit

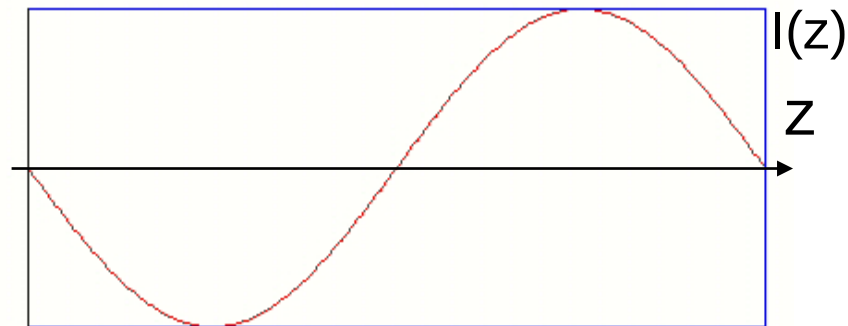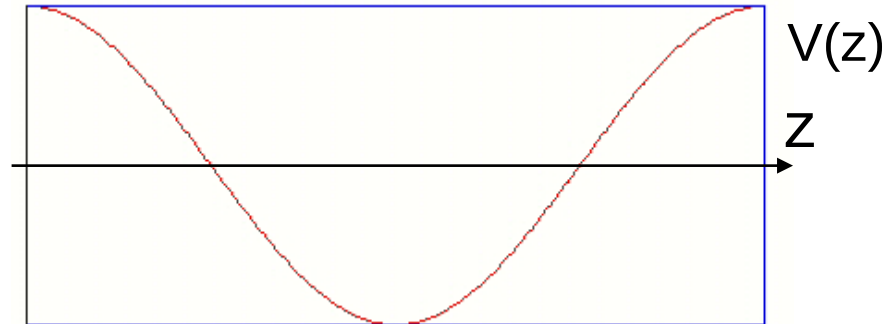

Generator and load mismatches

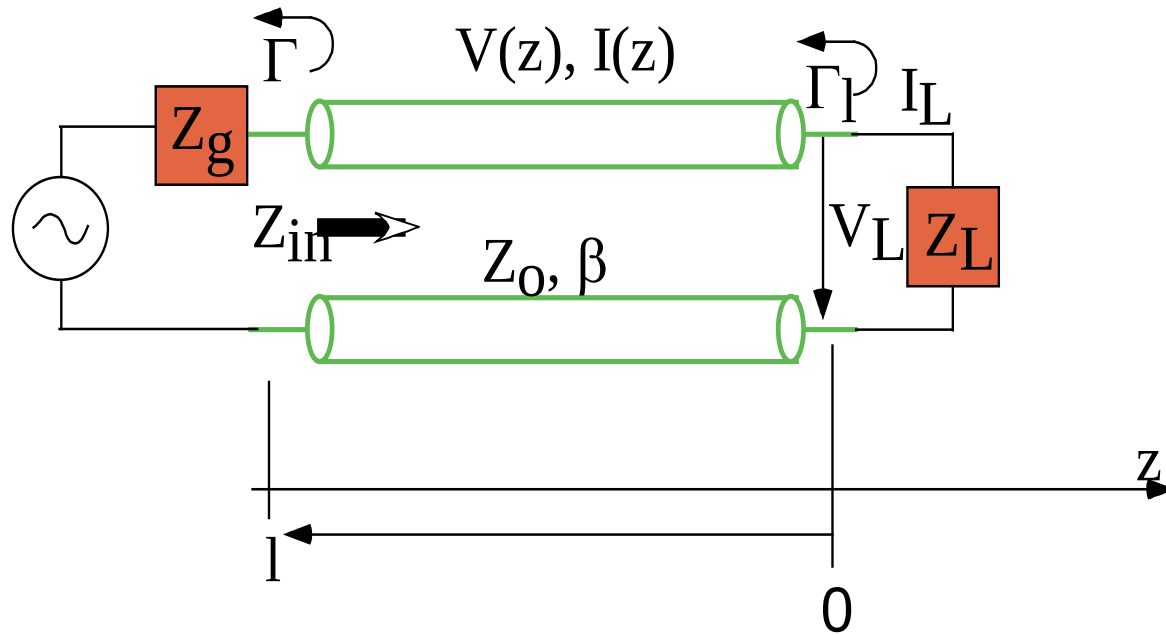

Input impedance (at l) looking towards the load :

$$Z_{in} = Z_o \frac{1 + \Gamma_l e^{-j2\beta l}}{1 - \Gamma_l e^{-j2\beta l}} = Z_o \frac{Z_l + jZ_o \tan \beta l}{Z_o + jZ_l \tan \beta l}$$

with

$$\Gamma_l = \frac{Z_l - Z_o}{Z_l + Z_o}$$

Amplitude of the incident wave from the generator :

$$V(-l) = V_g \frac{Z_{in}}{Z_{in} + Z_g} = V_0^+ \left(e^{j\beta l} + \Gamma_l e^{-j\beta l} \right)$$

Thus
$$V_0^+ = V_g \frac{Z_{in}}{Z_{in} + Z_g} \frac{1}{\left(e^{j\beta l} + \Gamma_l e^{-j\beta l} \right)}$$

and

$$V_0^+ = V_g \frac{Z_{in}}{Z_{in} + Z_g} \frac{1}{\left(e^{j\beta l} + \Gamma_l e^{-j\beta l} \right)} = V_g \frac{Z_o}{Z_o + Z_g} \frac{e^{-j\beta l}}{\left(1 - \Gamma_l \Gamma_g e^{-2j\beta l} \right)}$$

Power delivered to the load

$$P_l = \operatorname{Re} \left[V_{in} I_{in}^* \right] = |V_{in}|^2 \operatorname{Re} \left[\frac{1}{Z_{in}} \right] = |V_g|^2 \left| \frac{Z_{in}}{Z_{in} + Z_g} \right|^2 \operatorname{Re} \left[\frac{1}{Z_{in}} \right]$$

$$P_l = |V_g|^2 \frac{R_{in}}{(R_{in} + R_g)^2 + (X_{in} + X_g)^2}$$

If the load is matched ($Z_l = Z_o$)

$$P_l = |V_g|^2 \frac{Z_o}{(Z_o + R_g)^2 + X_g^2}$$

If the generator is matched to the mismatched line ($Z_g = Z_{in}$)

$$\Gamma = \frac{Z_{in} - Z_g}{Z_{in} + Z_g} = 0, \Gamma_g \neq 0, \Gamma_l \neq 0 \quad P_l = |V_g|^2 \frac{R_g}{4(R_g^2 + X_g^2)}$$

optimum power transfer

$$\frac{\partial P_l}{\partial R_{in}} = 0 \rightarrow \frac{1}{(R_{in} + R_g)^2 + (X_{in} + X_g)^2} - \frac{2R_{in}(R_{in} + R_g)}{\left[(R_{in} + R_g)^2 + (X_{in} + X_g)^2\right]^2} = 0$$

$$Z_{in} = Z_g^*$$

$$P_{l \max} = |V_g|^2 \frac{1}{4R_g} \geq |V_g|^2 \frac{Z_o}{(Z_o + R_g)^2 + X_g^2} \geq |V_g|^2 \frac{R_g}{4(R_g^2 + X_g^2)}$$


Impedance matching

Aim : achieve maximum power transfer



A narrowband matching network can always be found for a passive load

Quarter wave transformer

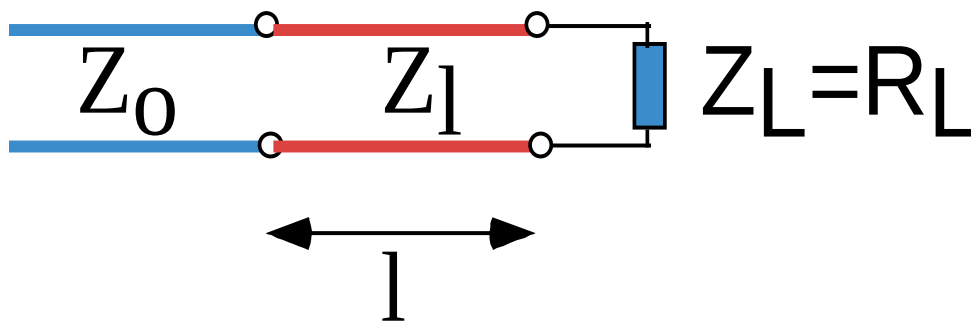

$$Z_l = \sqrt{Z_o Z_L}$$

$$l = \frac{\lambda_o}{4} \Rightarrow \beta l = \frac{\pi}{2}$$

$$Z_{in} = Z_l \frac{Z_L + jZ_l \tan \beta l}{Z_l + jZ_L \tan \beta l}$$


$$\Gamma = \frac{Z_{in} - Z_o}{Z_{in} + Z_o} = \frac{Z_l (Z_L - Z_o) + j \tan \beta l (Z_l^2 - Z_o Z_L)}{Z_l (Z_L + Z_o) + j \tan \beta l (Z_l^2 + Z_o Z_L)}$$

$$\Gamma = \frac{Z_L - Z_o}{Z_L + Z_o + j 2 \tan \beta l \sqrt{Z_o Z_L}}$$


$$\begin{aligned}
 |\Gamma| &= \frac{|Z_L - Z_o|}{\sqrt{(Z_L + Z_o)^2 + 4 \tan^2 \beta l Z_o Z_L}} = \frac{1}{\sqrt{\frac{(Z_L + Z_o)^2}{(Z_L - Z_o)^2} + \frac{4 \tan^2 \beta l Z_o Z_L}{(Z_L - Z_o)^2}}} \\
 &= \frac{1}{\sqrt{\frac{1 + 4 Z_o Z_L}{(Z_L - Z_o)^2} + \frac{4 \tan^2 \beta l Z_o Z_L}{(Z_L - Z_o)^2}}} = \frac{1}{\sqrt{1 + \frac{[4 Z_o Z_L] \sec^2 \beta l}{(Z_L - Z_o)^2}}}
 \end{aligned}$$

$$1 + \tan^2 \beta l = \sec^2 \beta l$$

Quarter wave transformer

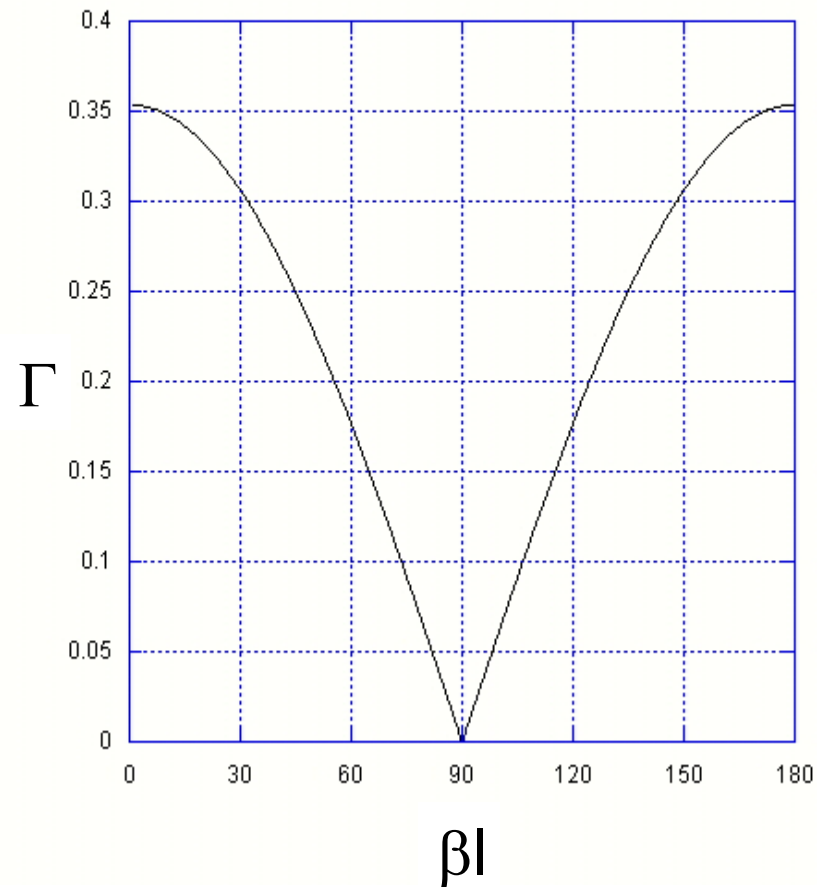



L sections

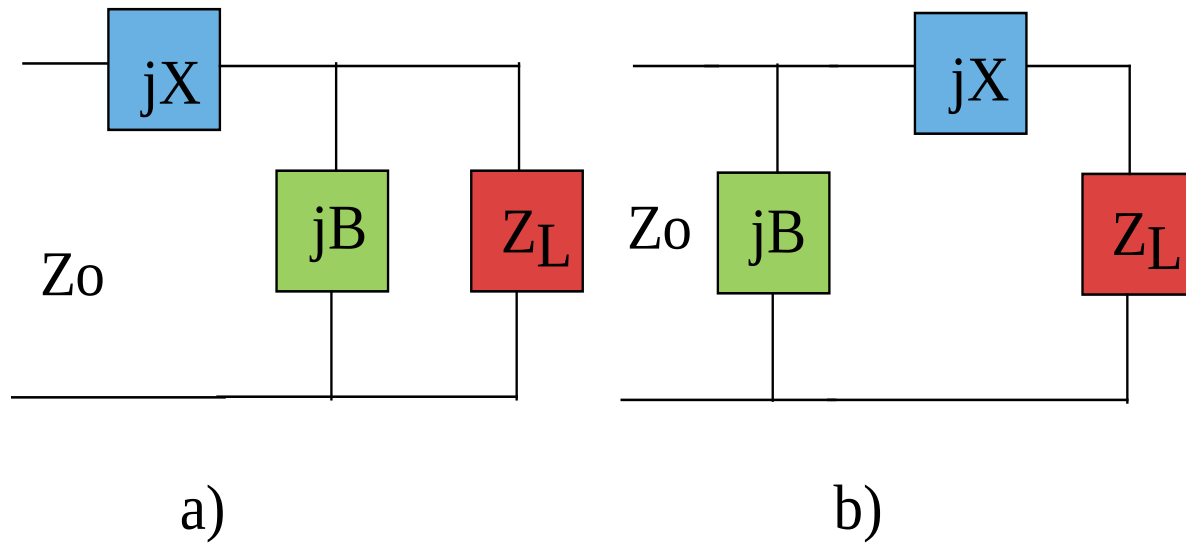

Example: we want to design an L-section matching network to match a series RC load having an impedance $Z_L = 200 - j100 \, \Omega$, to a $100 \, \Omega$ line, at a frequency of 500 MHz.

L sections

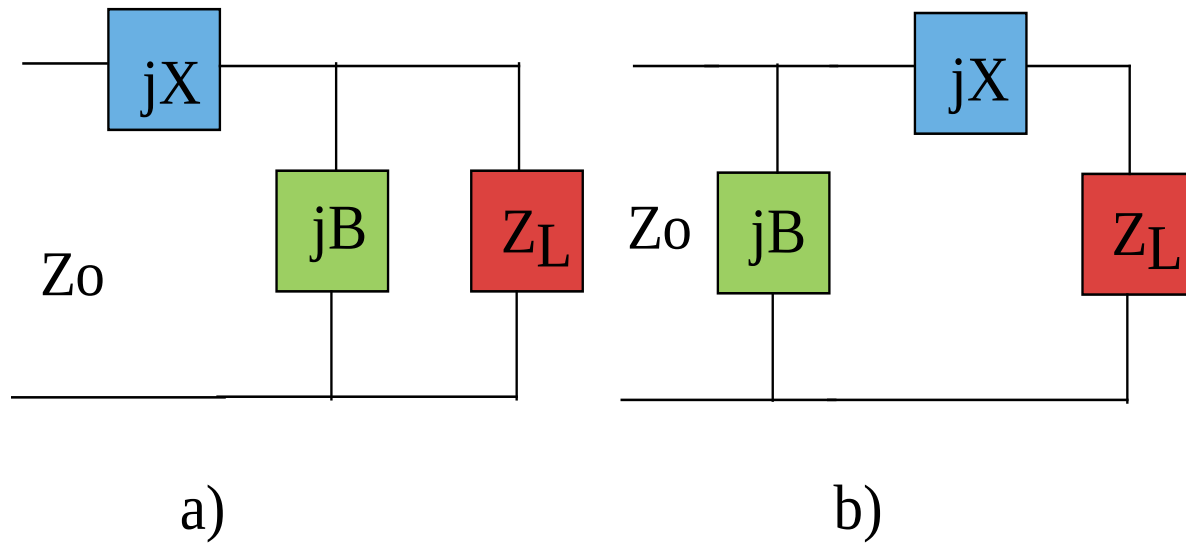


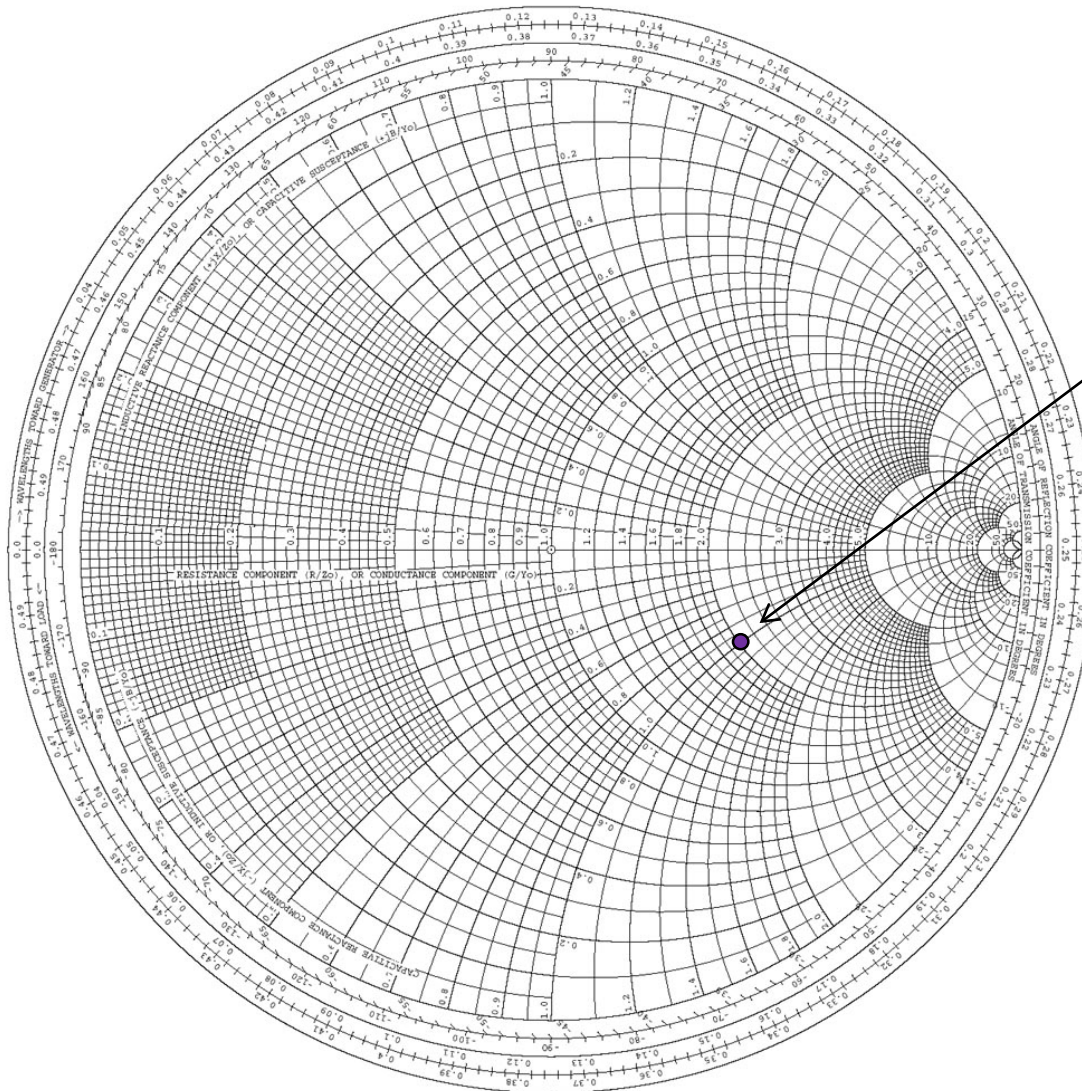

$$Z_L = 200 - j100 \, \Omega$$

$$Z_0 = 100 \, \Omega$$

$$z_l = 2 - j$$

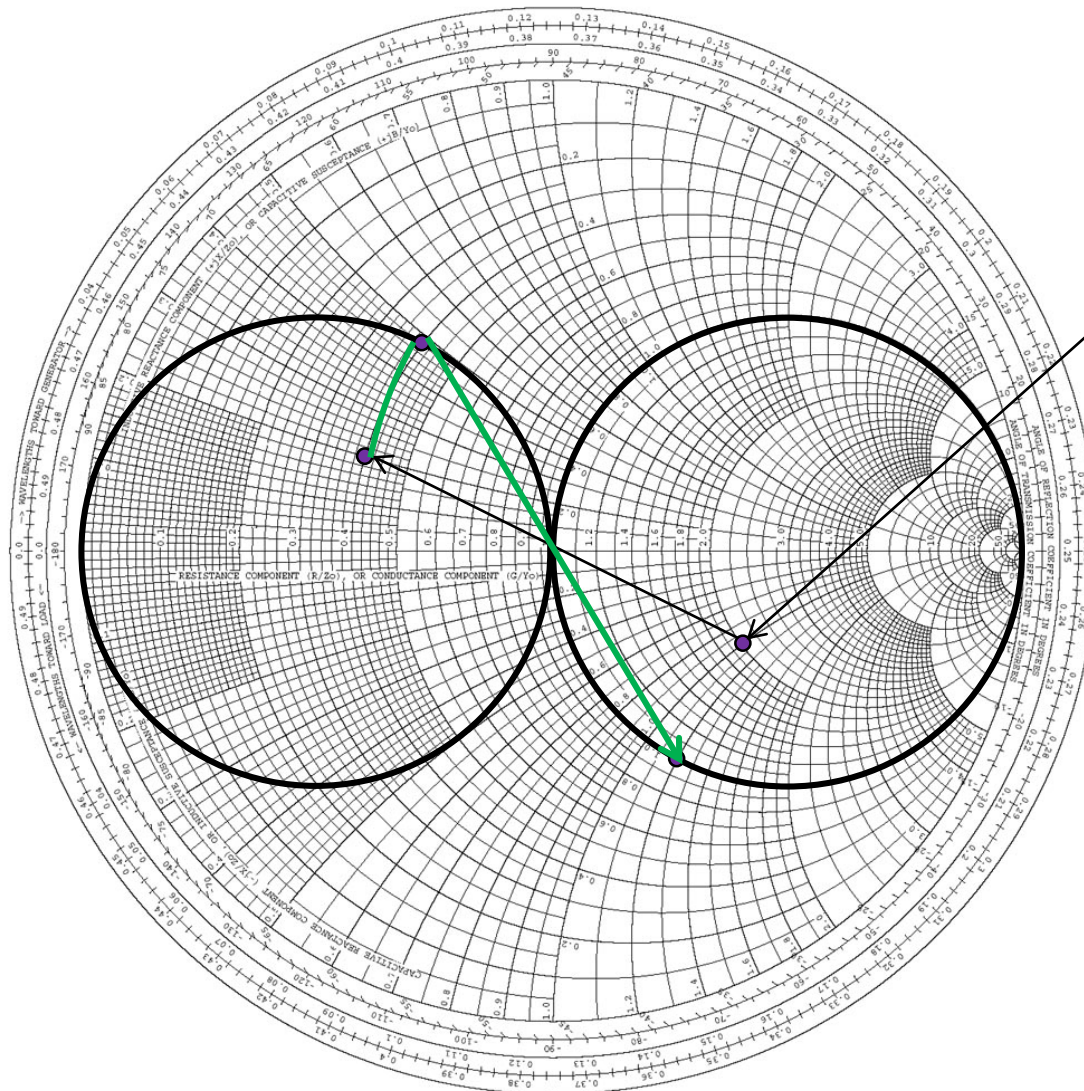


$$Z_L = 200 - j100 \Omega$$

$$Z_0 = 100 \Omega$$

$$z_1 = 2 - j$$

$$y_1 = 0.4 + 0.2j$$

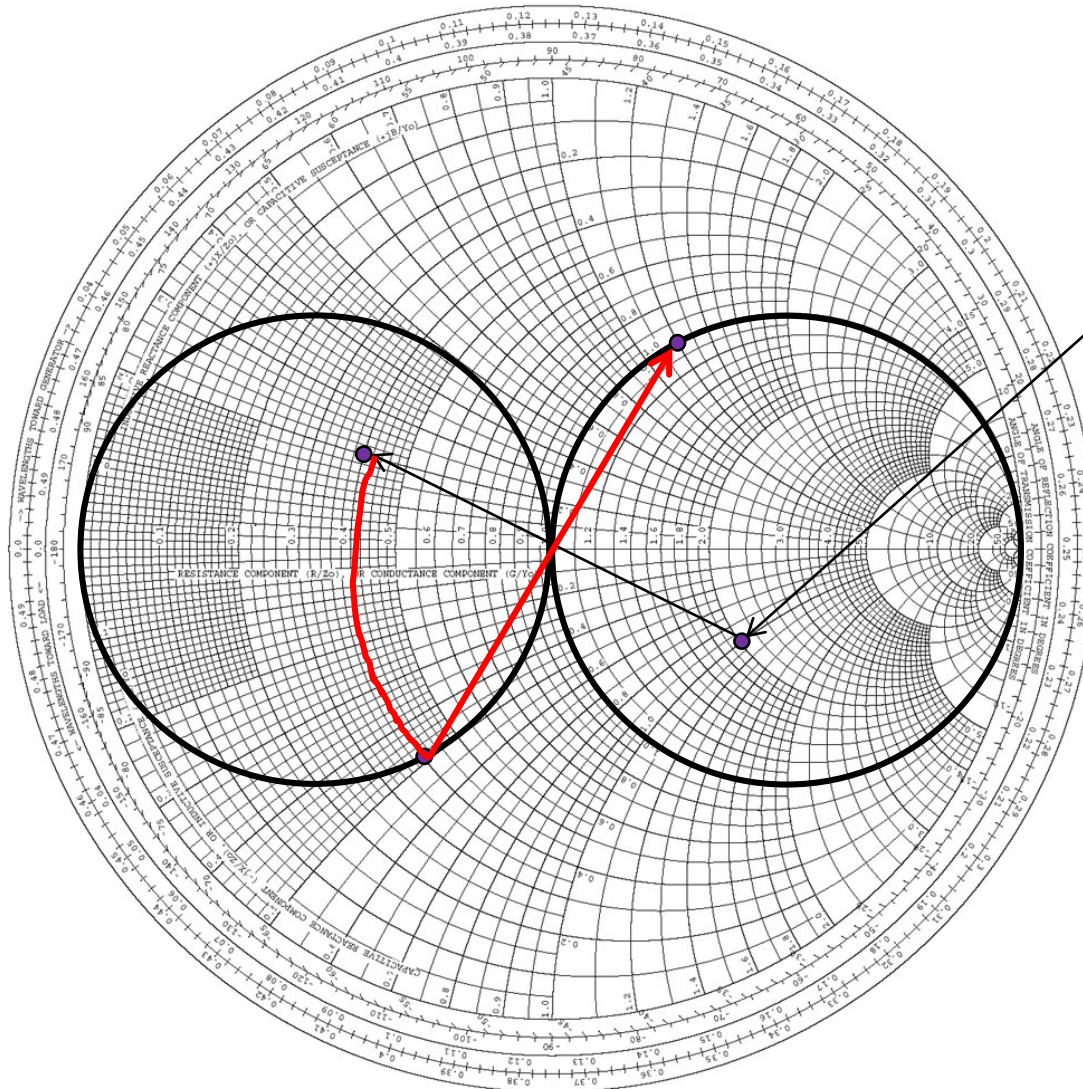


$$Z_L = 200 - j100 \Omega$$


$$Z_0 = 100 \Omega$$

$$z_1 = 2 - j$$


$$y_1 = 0.4 + 0.2j$$

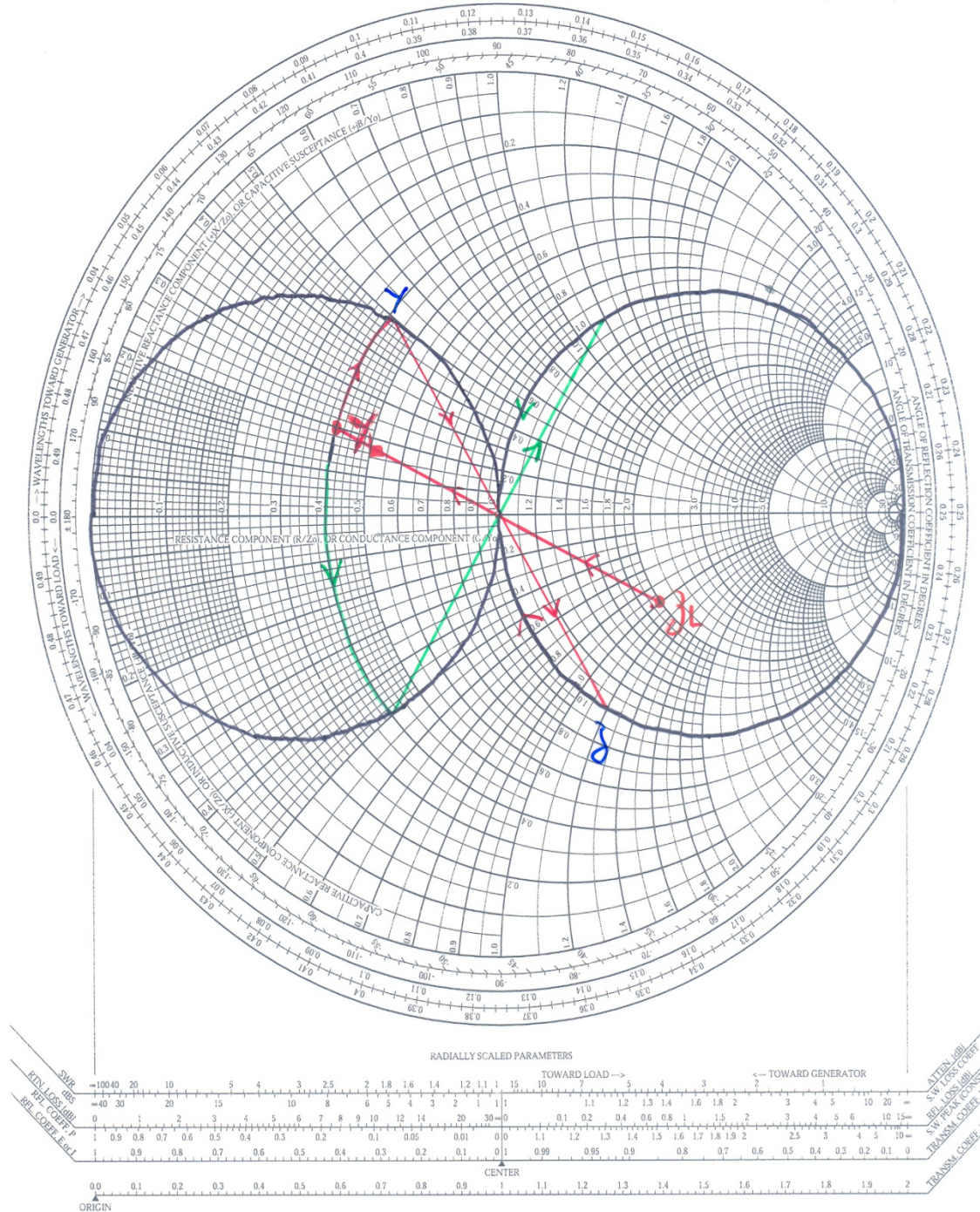



Example

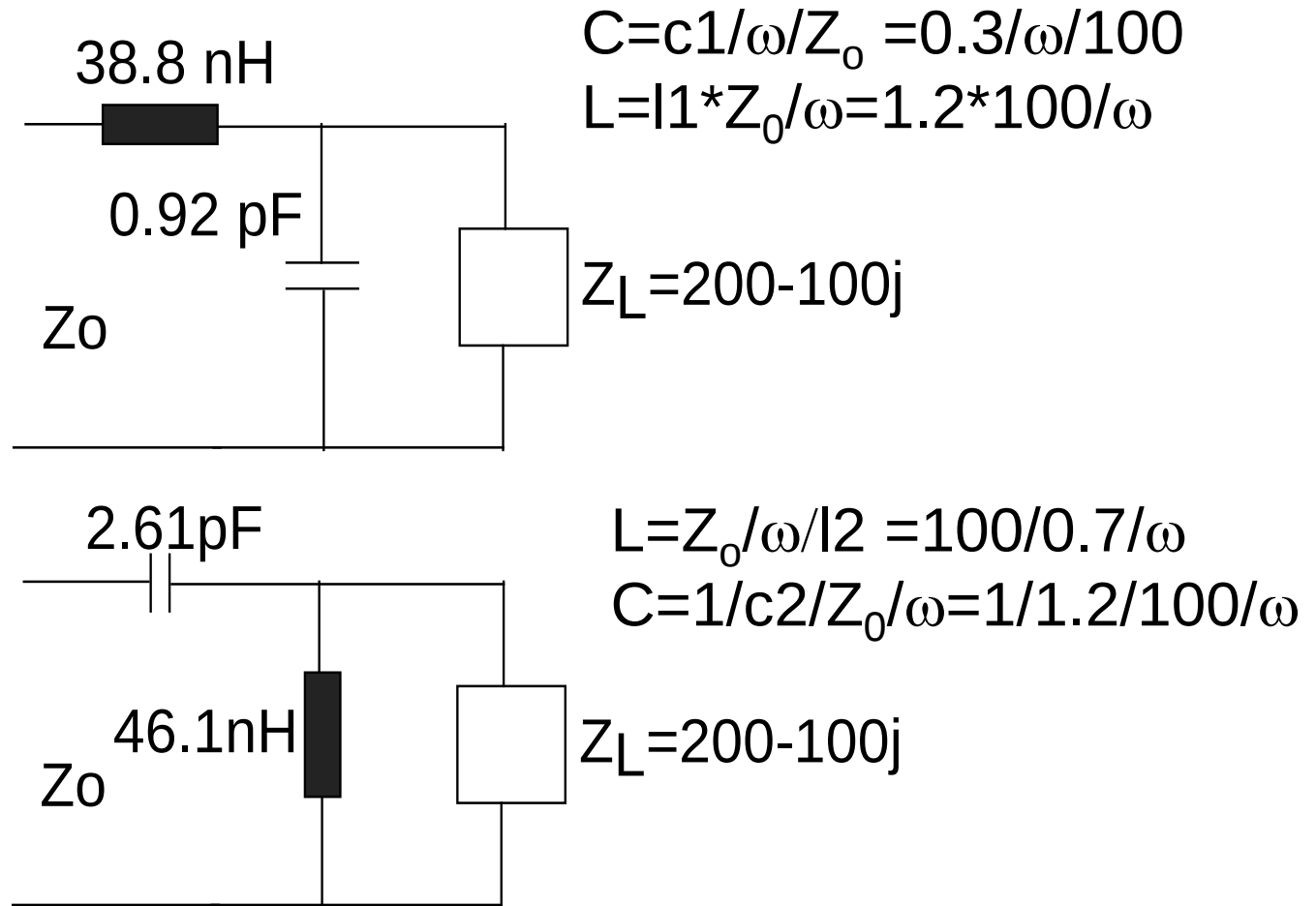


Single-stub tuning

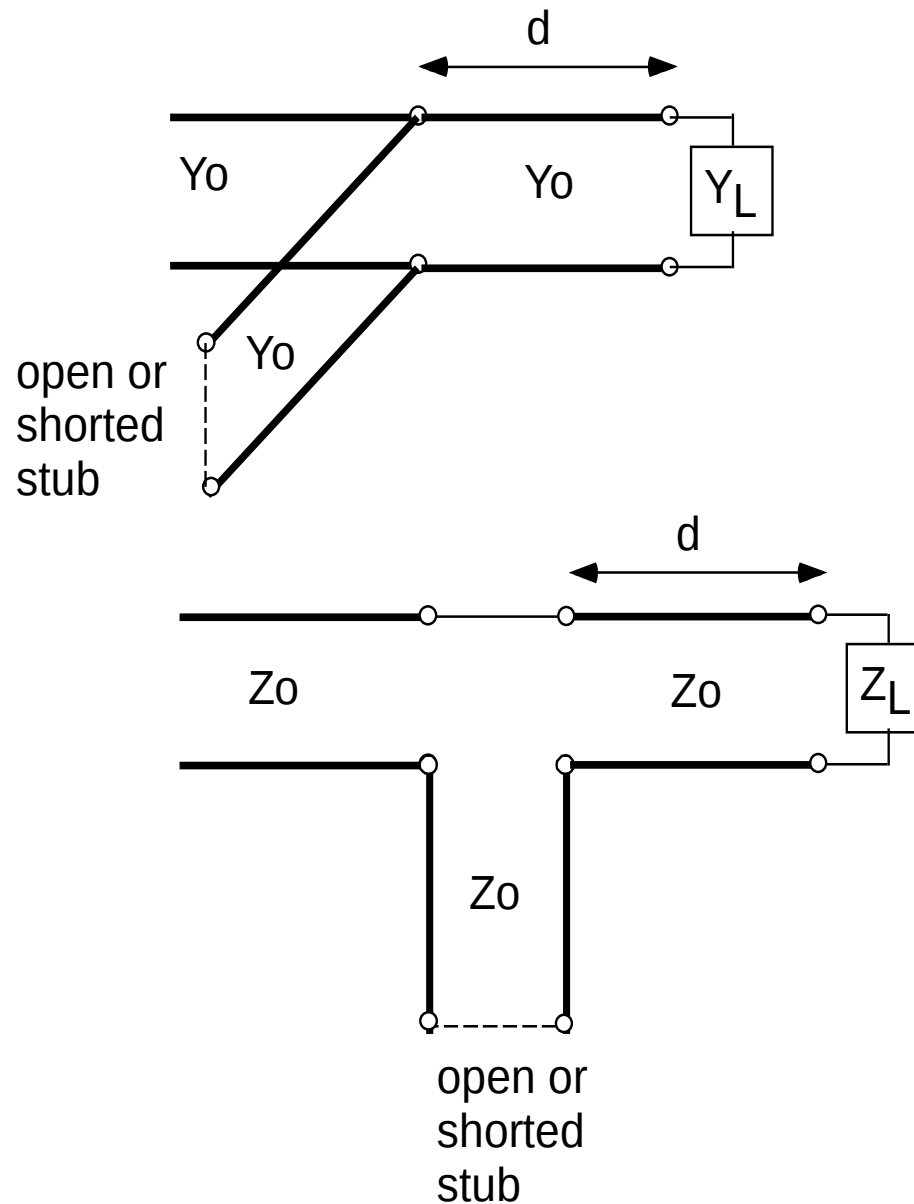

Single-stub tuning

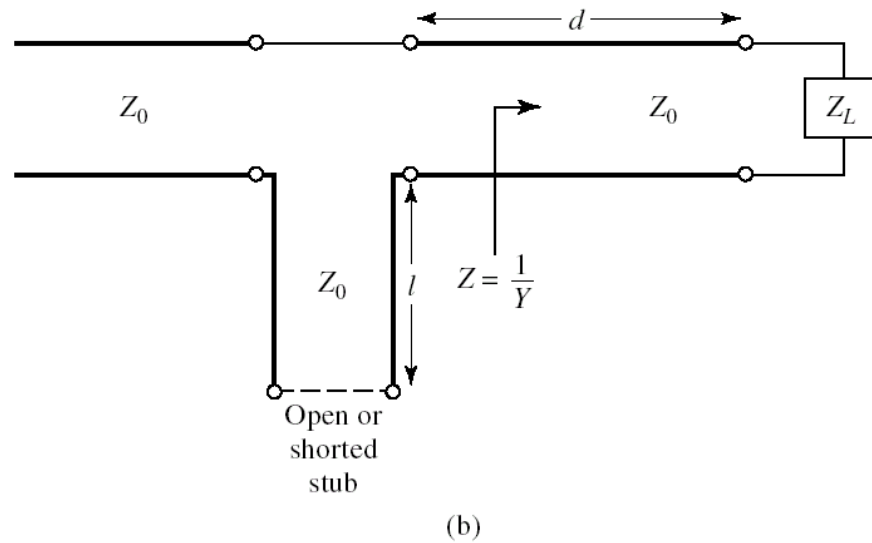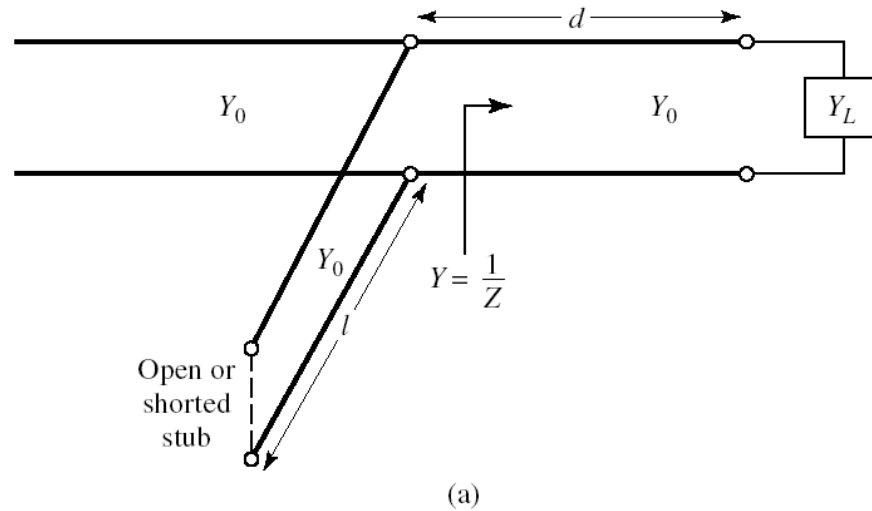


Single-stub tuning

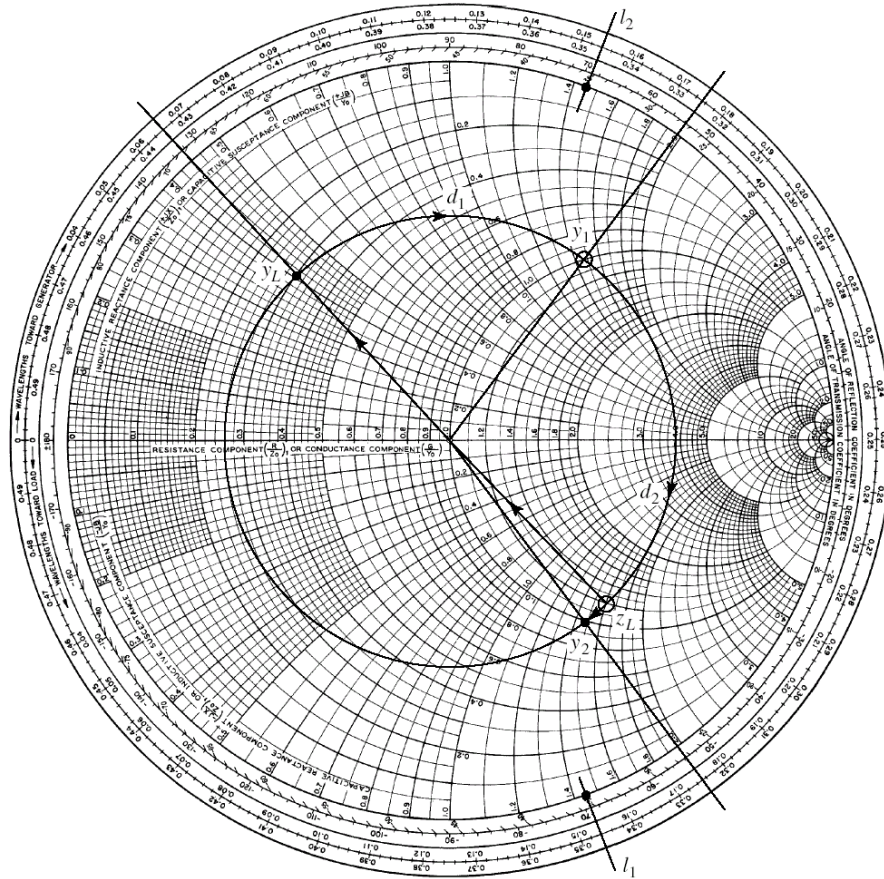


(a)

Single stub tuning

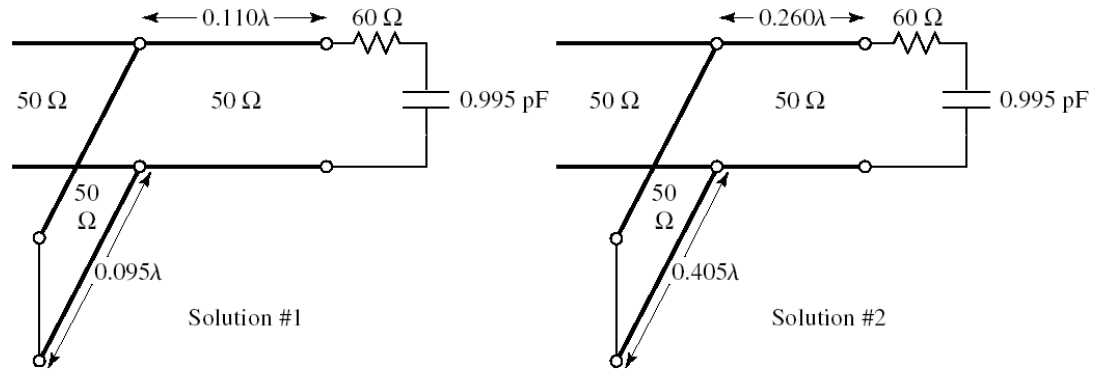

(b)

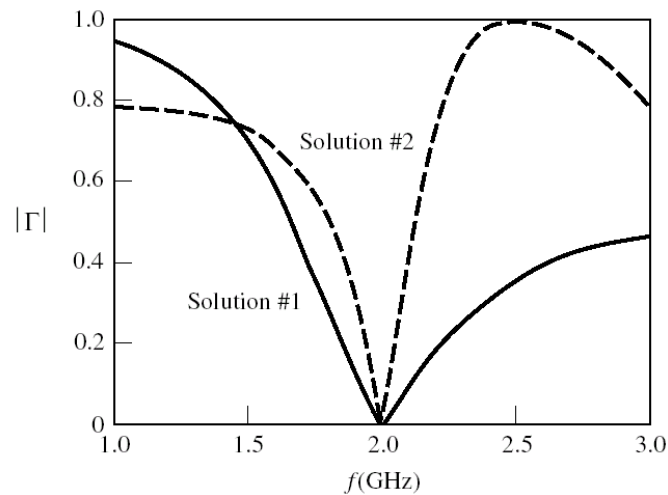

(c)

Example: Single stub tuning

Example:
match an antenna
 $Z_{in} = 44.8 - j 107 \Omega$ to
 $Z_0 = 75 \Omega$