

EE-472 Smart Grids Technologies

Module 2 Quiz (Graded)

28. 04. 2025 - With Solutions

Full Name: _____


Sciper Number:

Question 1

Marked out of 10

A radial network is divided to k subnetworks connected with $k - 1$ transformers, $TF_1, TF_2, \dots, TF_{k-1}$, with nominal voltage ratios $n_1 : 1, n_2 : 1, \dots, n_{k-1} : 1$, respectively (see Figure below). In absolute units, transformers are modelled by short-circuit impedance and an ideal transformer with the corresponding nominal ratio.

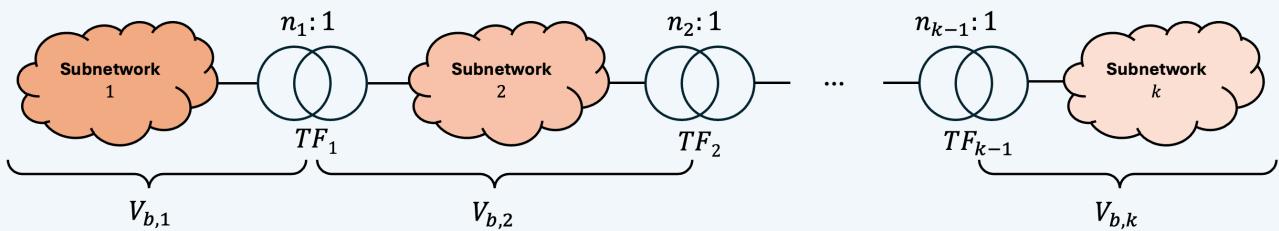A base voltage k -tuple $(V_{b,1}, V_{b,2}, \dots, V_{b,k})$ is called *model-friendly* if base voltages satisfy the condition such that all transformers per-unit equivalent circuits contain only branch elements, i.e., per-unit short-circuit impedance and no additional shunt elements.



For a model-friendly k -tuple $(V_{b,1}, V_{b,2}, \dots, V_{b,k})$, what can you say about the ratio $\frac{V_{b,1}}{V_{b,k}}$?

a. $\frac{V_{b,1}}{V_{b,k}} = \prod_{i=1}^{k-1} n_i$

b. $\frac{V_{b,1}}{V_{b,k}} = \prod_{i=1}^{k-1} \frac{n_i}{n_{i+1}}$


c. $\frac{V_{b,1}}{V_{b,k}} = \frac{1}{\prod_{i=1}^{k-1} n_i}$

d. It cannot be uniquely determined.

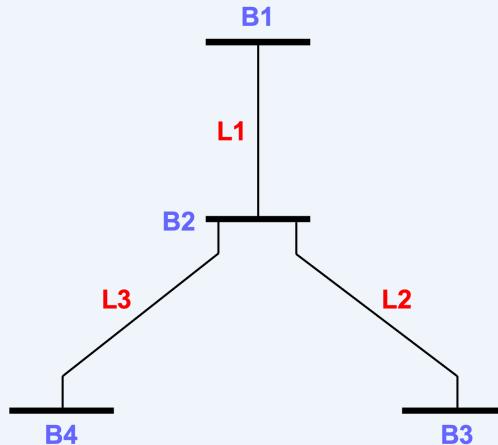Question 2

Marked out of 10

A small radial network (shown in Figure below) where all the shunts are neglected is described by the admittance matrix \bar{Y} .



Knowing only elements (in per-unit) $\bar{Y}_{11} = -j5$, $\bar{Y}_{22} = -j11$ and $\bar{Y}_{44} = -j4$ what is the value of \bar{Y}_{33} ?

- a. $-j3$
- b. It cannot be uniquely determined. We need additional matrix elements.
- c. $-j4$
- d. $-j2$

Question 3

Not yet answered

Marked out of 10

Consider a transformer with the following nameplate:

| | | |
|--------------------------------|---------------|--------|
| Nominal voltage primary side | $V_{n,1}$ (V) | 11 000 |
| Nominal voltage secondary side | $V_{n,2}$ (V) | 415 |
| Short-circuit voltage | V_{sc} (%) | 4 |
| Short-circuit active power | P_{sc} (W) | 1740 |
| Nominal power | A_n (kVA) | 100 |

What is the value of the complex short-circuit impedance $\bar{z}_{sc} = r_{sc} + jx_{sc}$ in per-unit, if the base voltages are $V_{b,1} = V_{n,1}$, $V_{b,2} = V_{n,2}$ and base power $A_b = 200$ kVA?

- a. $(0.87 + j1.80) \%$
- b. $(1.74 + j3.60) \%$
- c. $(0.00 + j4.00) \%$
- d. $(3.48 + j7.20) \%$

Question 4

Marked out of 10

Consider a small electrical grid of four buses. We assume that the system is balanced and consider a single-phase representation of the grid. The complex nodal injected power of each node is defined as $\bar{S} = P + jQ$ where P and Q are active and reactive power, respectively. The nodal voltages in Cartesian coordinates for each bus are $\bar{V} = V' + jV''$. For each bus, the imposed and unknown parameters are specified in the following table:

| Bus No. | Imposed Parameter 1 | Imposed Parameter 2 | Unknown Parameter 1 | Unknown Parameter 2 |
|---------|---------------------|---------------------|---------------------|---------------------|
| 1 | P_1 | Q_1 | $\arg(\bar{V}_1)$ | $ \bar{V}_1 $ |
| 2 | P_2 | Q_2 | $\arg(\bar{V}_2)$ | $ \bar{V}_2 $ |
| 3 | $\arg(\bar{V}_3)$ | $ \bar{V}_3 $ | P_3 | Q_3 |
| 4 | P_4 | $ \bar{V}_4 $ | $\arg(\bar{V}_4)$ | Q_4 |

To solve the Load-flow equations, one can write the system equations in Cartesian coordinates and use the Newton-Raphson algorithm. In the iterative process:

$$\begin{bmatrix} \Delta \mathbf{P} \\ \Delta \mathbf{Q} \\ \Delta(\mathbf{V}^2) \end{bmatrix} = \begin{bmatrix} \mathbf{J}_{PR} & \mathbf{J}_{PX} \\ \mathbf{J}_{QR} & \mathbf{J}_{QX} \\ \mathbf{J}_{VR} & \mathbf{J}_{VX} \end{bmatrix} \times \begin{bmatrix} \Delta \mathbf{V}' \\ \Delta \mathbf{V}'' \end{bmatrix}$$

we compute the reduced Jacobian matrix that corresponds to load-flow equations excluding the identities. Which of the following matrices correspond to the node types described in the table?

$$\mathbf{J}^a = \begin{bmatrix} \frac{\partial P_1}{\partial V'_1} & \frac{\partial P_1}{\partial V'_2} & \frac{\partial P_1}{\partial V'_4} & \frac{\partial P_1}{\partial V''_1} & \frac{\partial P_1}{\partial V''_2} & \frac{\partial P_1}{\partial V''_3} \\ \frac{\partial P_2}{\partial V'_1} & \frac{\partial P_2}{\partial V'_2} & \frac{\partial P_2}{\partial V'_4} & \frac{\partial P_2}{\partial V''_1} & \frac{\partial P_2}{\partial V''_2} & \frac{\partial P_2}{\partial V''_3} \\ \frac{\partial P_4}{\partial V'_1} & \frac{\partial P_4}{\partial V'_2} & \frac{\partial P_4}{\partial V'_4} & \frac{\partial P_4}{\partial V''_1} & \frac{\partial P_4}{\partial V''_2} & \frac{\partial P_4}{\partial V''_3} \\ \frac{\partial Q_1}{\partial V'_1} & \frac{\partial Q_1}{\partial V'_2} & \frac{\partial Q_1}{\partial V'_4} & \frac{\partial Q_1}{\partial V''_1} & \frac{\partial Q_1}{\partial V''_2} & \frac{\partial Q_1}{\partial V''_3} \\ \frac{\partial Q_2}{\partial V'_1} & \frac{\partial Q_2}{\partial V'_2} & \frac{\partial Q_2}{\partial V'_4} & \frac{\partial Q_2}{\partial V''_1} & \frac{\partial Q_2}{\partial V''_2} & \frac{\partial Q_2}{\partial V''_3} \\ \frac{\partial V'^2_4}{\partial V'_1} & \frac{\partial V'^2_4}{\partial V'_2} & \frac{\partial V'^2_4}{\partial V'_4} & \frac{\partial V'^2_4}{\partial V''_1} & \frac{\partial V'^2_4}{\partial V''_2} & \frac{\partial V'^2_4}{\partial V''_3} \end{bmatrix} \quad \mathbf{J}^b = \begin{bmatrix} \frac{\partial P_1}{\partial V'_1} & \frac{\partial P_2}{\partial V'_1} & \frac{\partial P_4}{\partial V'_1} & \frac{\partial P_1}{\partial V''_1} & \frac{\partial P_2}{\partial V''_1} & \frac{\partial P_4}{\partial V''_1} \\ \frac{\partial P_1}{\partial V'_2} & \frac{\partial P_2}{\partial V'_2} & \frac{\partial P_4}{\partial V'_2} & \frac{\partial P_1}{\partial V''_2} & \frac{\partial P_2}{\partial V''_2} & \frac{\partial P_4}{\partial V''_2} \\ \frac{\partial P_1}{\partial V'_4} & \frac{\partial P_2}{\partial V'_4} & \frac{\partial P_4}{\partial V'_4} & \frac{\partial P_1}{\partial V''_4} & \frac{\partial P_2}{\partial V''_4} & \frac{\partial P_4}{\partial V''_4} \\ \frac{\partial Q_1}{\partial V'_1} & \frac{\partial Q_2}{\partial V'_1} & \frac{\partial Q_4}{\partial V'_1} & \frac{\partial Q_1}{\partial V''_1} & \frac{\partial Q_2}{\partial V''_1} & \frac{\partial Q_4}{\partial V''_1} \\ \frac{\partial Q_1}{\partial V'_2} & \frac{\partial Q_2}{\partial V'_2} & \frac{\partial Q_4}{\partial V'_2} & \frac{\partial Q_1}{\partial V''_2} & \frac{\partial Q_2}{\partial V''_2} & \frac{\partial Q_4}{\partial V''_2} \\ \frac{\partial V'^2_1}{\partial V'_4} & \frac{\partial V'^2_2}{\partial V'_4} & \frac{\partial V'^2_3}{\partial V'_4} & \frac{\partial V'^2_1}{\partial V''_4} & \frac{\partial V'^2_2}{\partial V''_4} & \frac{\partial V'^2_3}{\partial V''_4} \end{bmatrix}$$


$$\mathbf{J}^c = \begin{bmatrix} \frac{\partial P_1}{\partial V'_1} & \frac{\partial P_1}{\partial V'_2} & \frac{\partial P_1}{\partial V'_4} & \frac{\partial P_1}{\partial V''_1} & \frac{\partial P_1}{\partial V''_2} & \frac{\partial P_1}{\partial V''_4} \\ \frac{\partial P_2}{\partial V'_1} & \frac{\partial P_2}{\partial V'_2} & \frac{\partial P_2}{\partial V'_4} & \frac{\partial P_2}{\partial V''_1} & \frac{\partial P_2}{\partial V''_2} & \frac{\partial P_2}{\partial V''_4} \\ \frac{\partial P_4}{\partial V'_1} & \frac{\partial P_4}{\partial V'_2} & \frac{\partial P_4}{\partial V'_4} & \frac{\partial P_4}{\partial V''_1} & \frac{\partial P_4}{\partial V''_2} & \frac{\partial P_4}{\partial V''_4} \\ \frac{\partial Q_1}{\partial V'_1} & \frac{\partial Q_1}{\partial V'_2} & \frac{\partial Q_1}{\partial V'_4} & \frac{\partial Q_1}{\partial V''_1} & \frac{\partial Q_1}{\partial V''_2} & \frac{\partial Q_1}{\partial V''_4} \\ \frac{\partial Q_2}{\partial V'_1} & \frac{\partial Q_2}{\partial V'_2} & \frac{\partial Q_2}{\partial V'_4} & \frac{\partial Q_2}{\partial V''_1} & \frac{\partial Q_2}{\partial V''_2} & \frac{\partial Q_2}{\partial V''_4} \\ \frac{\partial V'^2_4}{\partial V'_1} & \frac{\partial V'^2_4}{\partial V'_2} & \frac{\partial V'^2_4}{\partial V'_4} & \frac{\partial V'^2_4}{\partial V''_1} & \frac{\partial V'^2_4}{\partial V''_2} & \frac{\partial V'^2_4}{\partial V''_4} \end{bmatrix} \quad \mathbf{J}^d = \begin{bmatrix} \frac{\partial P_1}{\partial V'_1} & \frac{\partial P_1}{\partial V'_2} & \frac{\partial P_1}{\partial V'_4} & \frac{\partial P_1}{\partial V''_1} & \frac{\partial P_1}{\partial V''_2} & \frac{\partial P_1}{\partial V''_4} \\ \frac{\partial P_2}{\partial V'_1} & \frac{\partial P_2}{\partial V'_2} & \frac{\partial P_2}{\partial V'_4} & \frac{\partial P_2}{\partial V''_1} & \frac{\partial P_2}{\partial V''_2} & \frac{\partial P_2}{\partial V''_4} \\ \frac{\partial P_4}{\partial V'_1} & \frac{\partial P_4}{\partial V'_2} & \frac{\partial P_4}{\partial V'_4} & \frac{\partial P_4}{\partial V''_1} & \frac{\partial P_4}{\partial V''_2} & \frac{\partial P_4}{\partial V''_4} \\ \frac{\partial Q_1}{\partial V'_1} & \frac{\partial Q_1}{\partial V'_2} & \frac{\partial Q_1}{\partial V'_4} & \frac{\partial Q_1}{\partial V''_1} & \frac{\partial Q_1}{\partial V''_2} & \frac{\partial Q_1}{\partial V''_4} \\ \frac{\partial Q_2}{\partial V'_1} & \frac{\partial Q_2}{\partial V'_2} & \frac{\partial Q_2}{\partial V'_4} & \frac{\partial Q_2}{\partial V''_1} & \frac{\partial Q_2}{\partial V''_2} & \frac{\partial Q_2}{\partial V''_4} \\ \frac{\partial Q_4}{\partial V'_1} & \frac{\partial Q_4}{\partial V'_2} & \frac{\partial Q_4}{\partial V'_4} & \frac{\partial Q_4}{\partial V''_1} & \frac{\partial Q_4}{\partial V''_2} & \frac{\partial Q_4}{\partial V''_4} \end{bmatrix}$$

- 1. \mathbf{J}^a .
- 2. \mathbf{J}^d .
- 3. \mathbf{J}^c .
- 4. \mathbf{J}^b .

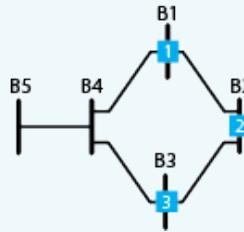Question 5

Marked out of 10

Let's consider the following 5-node grid that is equipped with 3 PMUs. Every PMU measures the current injection and the nodal voltage phasors.



Assume the measurement matrix is composed as: $\mathbf{H} = \begin{bmatrix} \mathbf{H}_V \\ \mathbf{H}_I \end{bmatrix}$.

The state vector is constructed as: $\mathbf{x} = \begin{bmatrix} \Re\{\bar{\mathbf{V}}\} \\ \Im\{\bar{\mathbf{V}}\} \end{bmatrix}$ and the measurement vector as: $\mathbf{z} = \begin{bmatrix} \mathbf{z}_V \\ \mathbf{z}_I \end{bmatrix}$, with $\mathbf{z}_V = \begin{bmatrix} \Re\{\widetilde{\mathbf{V}}\} \\ \Im\{\widetilde{\mathbf{V}}\} \end{bmatrix}$ and $\mathbf{z}_I = \begin{bmatrix} \Re\{\widetilde{\mathbf{I}}\} \\ \Im\{\widetilde{\mathbf{I}}\} \end{bmatrix}$.

Furthermore, the compound admittance matrix of the system is given as $\bar{\mathbf{Y}} = \mathbf{G} + j\mathbf{B}$, where the non-zero (i, j) -th element is expressed as $g_{ij} + jb_{ij}$.

Which of the following matrices correctly represents the measurement model of the above-given system?

$$\mathbf{H}^a = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & g_{12} & 0 & g_{14} & 0 & 0 & -b_{12} & 0 & -b_{14} & 0 \\ g_{21} & 0 & g_{23} & 0 & 0 & -b_{21} & 0 & -b_{23} & 0 & 0 \\ 0 & g_{32} & 0 & g_{34} & 0 & 0 & -b_{32} & 0 & -b_{34} & 0 \\ 0 & b_{12} & 0 & b_{14} & 0 & 0 & g_{12} & 0 & g_{14} & 0 \\ b_{21} & 0 & b_{23} & 0 & 0 & g_{21} & 0 & g_{23} & 0 & 0 \\ 0 & b_{32} & 0 & b_{34} & 0 & 0 & g_{32} & 0 & g_{34} & 0 \end{bmatrix} \quad \mathbf{H}^b = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ g_{11} & g_{12} & 0 & g_{14} & 0 & -b_{11} & -b_{12} & 0 & -b_{14} & 0 \\ g_{21} & g_{22} & g_{23} & 0 & 0 & -b_{21} & -b_{22} & -b_{23} & 0 & 0 \\ 0 & g_{32} & g_{33} & g_{34} & 0 & 0 & -b_{32} & -b_{33} & -b_{34} & 0 \\ b_{11} & b_{12} & 0 & b_{14} & 0 & g_{11} & g_{12} & 0 & g_{14} & 0 \\ b_{21} & b_{22} & b_{23} & 0 & 0 & g_{21} & g_{22} & g_{23} & 0 & 0 \\ 0 & b_{32} & b_{33} & b_{34} & 0 & 0 & g_{32} & g_{33} & g_{34} & 0 \end{bmatrix}$$

$$\mathbf{H}^c = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & g_{32} & g_{33} & g_{34} & 0 & 0 & -b_{32} & -b_{33} & -b_{34} & 0 \\ g_{21} & g_{22} & g_{23} & 0 & 0 & -b_{21} & -b_{22} & b_{23} & 0 & 0 \\ g_{11} & g_{12} & 0 & g_{14} & 0 & -b_{11} & -b_{12} & 0 & -b_{14} & 0 \\ 0 & b_{32} & g_{33} & b_{34} & 0 & 0 & g_{32} & g_{33} & g_{34} & 0 \\ b_{21} & b_{22} & b_{23} & 0 & 0 & g_{21} & g_{22} & g_{23} & 0 & 0 \\ b_{11} & b_{12} & 0 & b_{14} & 0 & g_{11} & g_{12} & 0 & g_{14} & 0 \end{bmatrix}$$

1. \mathbf{H}^c

2. \mathbf{H}^a


3. None of the above.

4. \mathbf{H}^b

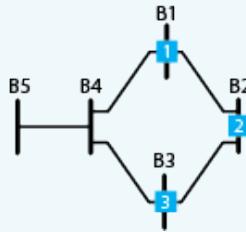Question 6

Marked out of 10

Let's consider the following 5-node grid that is equipped with 3 PMUs. Every PMU measures the current injection and the nodal voltage phasors.



What can you say about the observability of the system?

- a. The system is observable. However, the measurements from PMU 2 and PMU 3 are both critical measurements. Therefore, if any of these measurements is removed, the state cannot be inferred anymore.
- b. The rule-of-thumb is satisfied, and therefore this system is observable.
- c. The only sufficient condition to guarantee observability is for the measurement model to have full rank.
- d. The system comprises 10 state variables and 12 measurements, resulting in an overdetermined measurement model since the number of measurements exceeds the number of states. This is a sufficient condition to guarantee observability.

Question 7

Marked out of 10

For the branch connecting nodes i and j in a generic network, the branch-flow model equations are given by (\star) .

Branch connecting nodes i and j .

$$\left. \begin{aligned} \bar{S}_{ij} - \bar{Z}_{ij}i_{Z_{ij}} - \bar{Y}_i v_i - \bar{Y}_j v_j + \bar{s}_j &= \sum_k \bar{S}_{jk} \\ v_j = v_i + |\bar{Z}_{ij}|^2 i_{Z_{ij}} - 2\Re[\bar{Z}_{ij}(\bar{S}_{ij} - \bar{Y}_i v_i)] \\ \sum_k \bar{S}_{ki} + \bar{s}_i &= \bar{S}_{ij} \\ i_{Z_{ij}} &= \frac{|\bar{S}_{ij} - \bar{Y}_i v_i|^2}{v_i} \\ v_i = |\bar{V}_i|^2, v_j = |\bar{V}_j|^2 \text{ and } i_{Z_{ij}} = |\bar{I}_{Z_{ij}}|^2 \\ \arg(\bar{V}_i) + \arg(\bar{V}_j) &= \arg(v_i - \bar{Z}_{ij}(\bar{S}_{ij} - \bar{Y}_i v_i)^2) \end{aligned} \right\} (\star)$$

Which of the following statements is correct?

- a. For a radial network with N nodes, once the squared voltage magnitudes are obtained from the branch-flow model, we can retrieve the voltage angles by solving the system of $N - 1$ linear equations, written by using the last equation of (\star) expressing $\arg(\bar{V}_i) + \arg(\bar{V}_j)$ for each branch, with one angle chosen as the reference.
- b. The power balance over a branch can be expressed as a linear combination of the voltage and current magnitudes, $|\bar{V}_i|$, $|\bar{V}_j|$ and $|\bar{I}_{Z_{ij}}|$.
- c. The system of equations (\star) can be written for equivalent circuits of transformers, modelled in per-unit, only if we include the transformer shunt admittance.
- d. For radial networks (without loops), load flow equations are formulated as a branch flow model, whereas for meshed networks, we use the nodal load-flow model.

Question 8

Marked out of 10

Consider the following statements about the nodal admittance matrix \bar{Y} of a linear, passive and reciprocal AC network.

1. \bar{Y} is diagonally dominant if inductances and capacitances are not null.
2. \bar{Y} is symmetric.


Which statement is correct?

- a. Both 1 and 2.
- b. Only 1.
- c. Only 2.
- d. None.

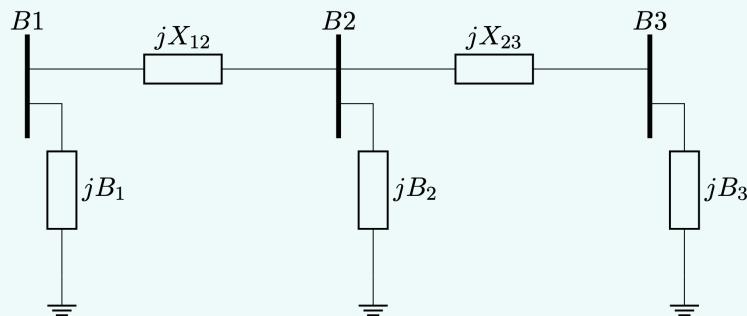Question 9

Marked out of 10

Consider a simple three-bus power system shown in the Figure below. In absolute units, longitudinal reactances X_{12} and X_{23} are in ohms (Ω), and shunt susceptances are in siemens (S).



Consider the following matrices:

$$\bar{Y}_a = \begin{bmatrix} -j\frac{1}{X_{12}} + jB_1 & j\frac{1}{X_{12}} & 0 \\ j\frac{1}{X_{12}} & -j\left(\frac{1}{X_{12}} + \frac{1}{X_{23}}\right) + jB_2 & j\frac{1}{X_{23}} \\ 0 & j\frac{1}{X_{23}} & -j\frac{1}{X_{23}} + jB_3 \end{bmatrix} \quad \bar{Y}_c = \begin{bmatrix} j\frac{1}{X_{12}} + jB_1 & -j\frac{1}{X_{12}} & 0 \\ -j\frac{1}{X_{12}} & j\left(\frac{1}{X_{12}} + \frac{1}{X_{23}}\right) + jB_2 & -j\frac{1}{X_{23}} \\ 0 & -j\frac{1}{X_{23}} & j\frac{1}{X_{23}} + jB_3 \end{bmatrix}$$

$$\bar{Y}_b = \begin{bmatrix} -j\frac{1}{X_{12}} - jB_1 & j\frac{1}{X_{12}} & 0 \\ j\frac{1}{X_{12}} & -j\left(\frac{1}{X_{12}} + \frac{1}{X_{23}}\right) - jB_2 & j\frac{1}{X_{23}} \\ 0 & j\frac{1}{X_{23}} & -j\frac{1}{X_{23}} - jB_3 \end{bmatrix} \quad \bar{Y}_d = \begin{bmatrix} j\frac{1}{X_{12}} - jB_1 & -j\frac{1}{X_{12}} & 0 \\ -j\frac{1}{X_{12}} & j\left(\frac{1}{X_{12}} + \frac{1}{X_{23}}\right) - jB_2 & -j\frac{1}{X_{23}} \\ 0 & -j\frac{1}{X_{23}} & j\frac{1}{X_{23}} - jB_3 \end{bmatrix}$$

The admittance matrix of the system is:

- \bar{Y}_d .
- \bar{Y}_a .
- \bar{Y}_c .
- \bar{Y}_b .

Question 10

Marked out of 10

The dependency on the voltage of the absorbed active/reactive powers absorbed by the loads can be represented using exponential models:

$$P = P_0 \left(\frac{V}{V_0} \right)^{\alpha_p} \text{ and } Q = Q_0 \left(\frac{V}{V_0} \right)^{\alpha_q}.$$

Which statement about coefficients α_p and α_q is **incorrect**?

- a. $0 \leq \alpha_p \leq 2$ and $0 \leq \alpha_q \leq 2$.
- b. α_p and α_q cannot change throughout the day.
- c. $\alpha_p = \alpha_q = 0$ if all the loads behave as constant power.
- d. If all the loads behave as constant current, then $\alpha_p = \alpha_q = 1$.