

3.1 Linear Feeder

Consider the linear feeder shown in Fig. 4, which consists of a synchronous machine (SM), two transformers (TF1, TF2), a transmission line (TL), and a load (L). The electrical parameters of these components are listed in Tab. 1.


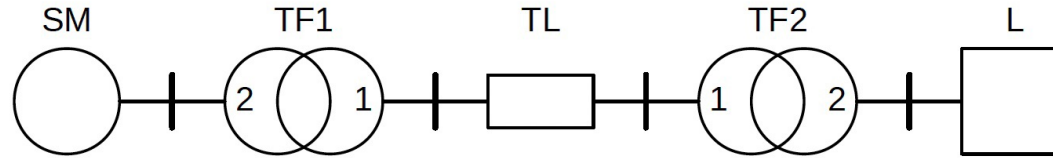


Figure 4: Schematic of the linear feeder.

Table 1: Electrical parameters of the components forming the linear feeder.

Component	Parameters
SM	$A_n=50$ MVA, $V_n=12$ kV, $x_{SM}=1.1$ pu ($\bar{Z}_{SM} = jX_{SM}$)
TF1	$A_n=60$ MVA, $V_{n,1}=220$ kV, $V_{n,2}=10$ kV, $V_{sc,\%}=10\%$
TL	$X_{TL}= 65 \Omega$ ($\bar{Z}_{TL} = jX_{TL}$)
TF2	$A_n=30$ MVA, $V_{n,1}=220$ kV, $V_{n,2}=20$ kV, $V_{sc,\%}=10\%$
L	$P_L=24$ MW, $Q_L=15$ MVar, $V_L=19$ kV

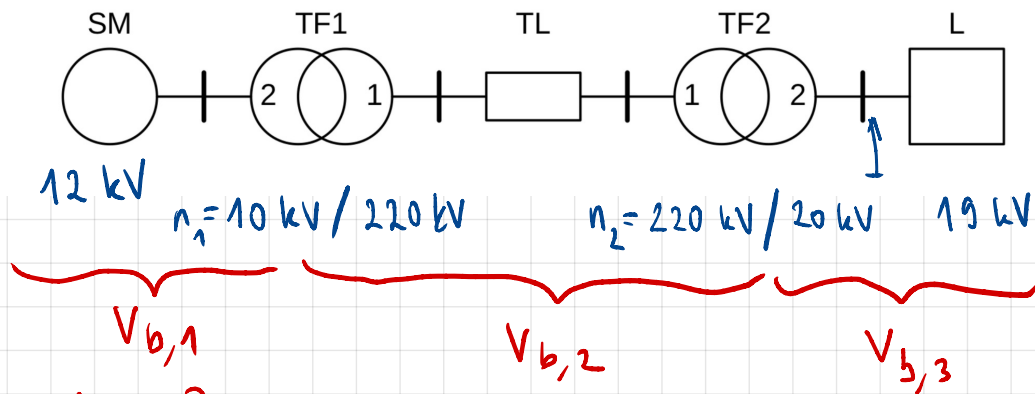Q1/ Compute the voltage magnitudes on the primary sides of the two transformers and at the internal bus of the synchronous machine.



Component	Parameters
SM	$A_n=50 \text{ MVA}$, $V_n=12 \text{ kV}$, $x_{SM}=1.1 \text{ pu}$ ($\bar{Z}_{SM} = jX_{SM}$)
TF1	$A_n=60 \text{ MVA}$, $V_{n,1}=220 \text{ kV}$, $V_{n,2}=10 \text{ kV}$, $V_{sc,\%}=10\%$
TL	$X_{TL}= 65 \Omega$ ($\bar{Z}_{TL} = jX_{TL}$)
TF2	$A_n=30 \text{ MVA}$, $V_{n,1}=220 \text{ kV}$, $V_{n,2}=20 \text{ kV}$, $V_{sc,\%}=10\%$
L	$P_L=24 \text{ MW}$, $Q_L=15 \text{ MVar}$, $V_L=19 \text{ kV}$

$$A_b = ?$$

$$A_b = 60 \text{ MVA}$$

$$\frac{V_{b,1}}{V_{b,2}} = n_1$$


$$\frac{V_{b,2}}{V_{b,3}} = n_2$$

$$V_{b,1} = 10 \text{ kV}$$



$$V_{b,2} = 220 \text{ kV}$$


$$V_{b,2} = 220 \text{ kV}$$

$$V_{b,3} = 20 \text{ kV}$$

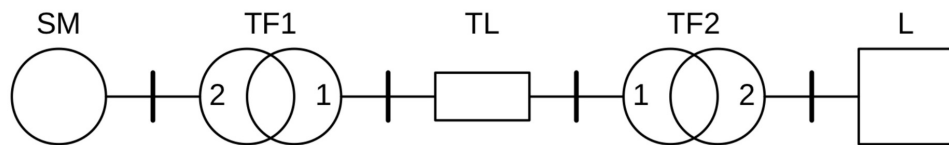


Component	Parameters
SM	$A_n=50$ MVA, $V_n=12$ kV, $x_{SM}=1.1$ pu ($\bar{Z}_{SM} = jX_{SM}$)
TF1	$A_n=60$ MVA, $V_{n,1}=220$ kV, $V_{n,2}=10$ kV, $V_{sc,\%}=10\%$
TL	$X_{TL}=65 \Omega$ ($\bar{Z}_{TL} = jX_{TL}$)
TF2	$A_n=30$ MVA, $V_{n,1}=220$ kV, $V_{n,2}=20$ kV, $V_{sc,\%}=10\%$
L	$P_L=24$ MW, $Q_L=15$ MVar, $V_L=19$ kV

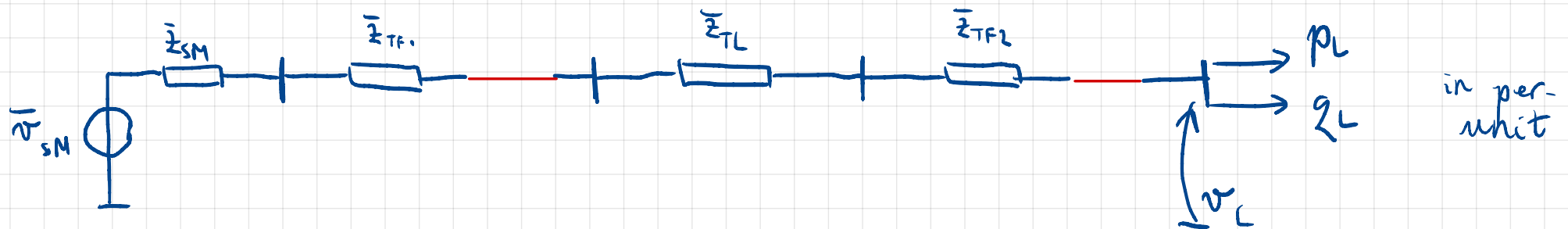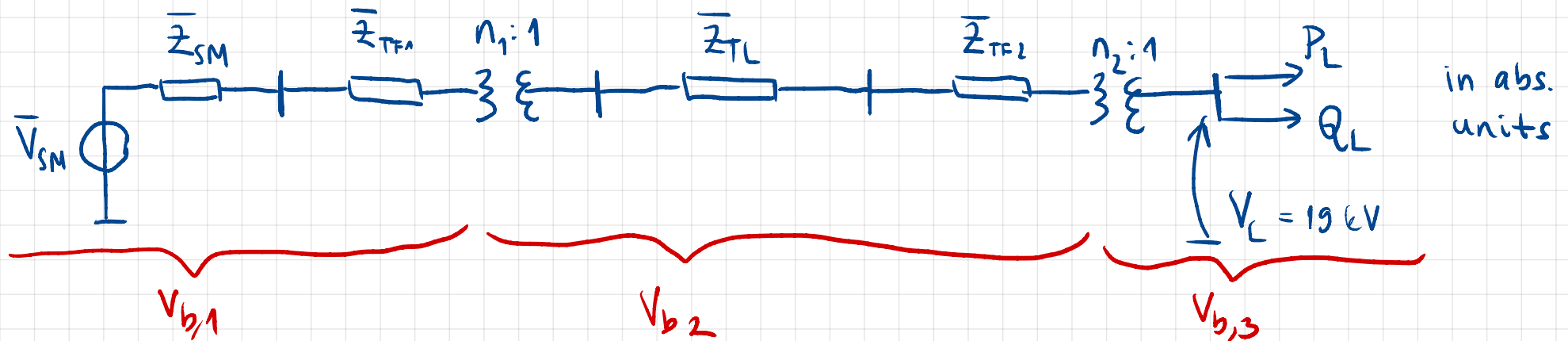

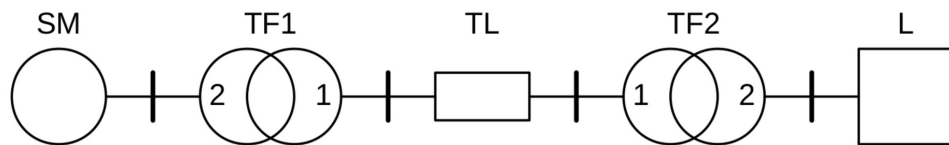

Component	Parameters
SM	$A_n=50$ MVA, $V_n=12$ kV, $x_{SM}=1.1$ pu ($\bar{Z}_{SM} = jX_{SM}$)
TF1	$A_n=60$ MVA, $V_{n,1}=220$ kV, $V_{n,2}=10$ kV, $V_{sc,\%}=10\%$
TL	$X_{TL}=65 \Omega$ ($\bar{Z}_{TL} = jX_{TL}$)
TF2	$A_n=30$ MVA, $V_{n,1}=220$ kV, $V_{n,2}=20$ kV, $V_{sc,\%}=10\%$
L	$P_L=24$ MW, $Q_L=15$ MVar, $V_L=19$ kV

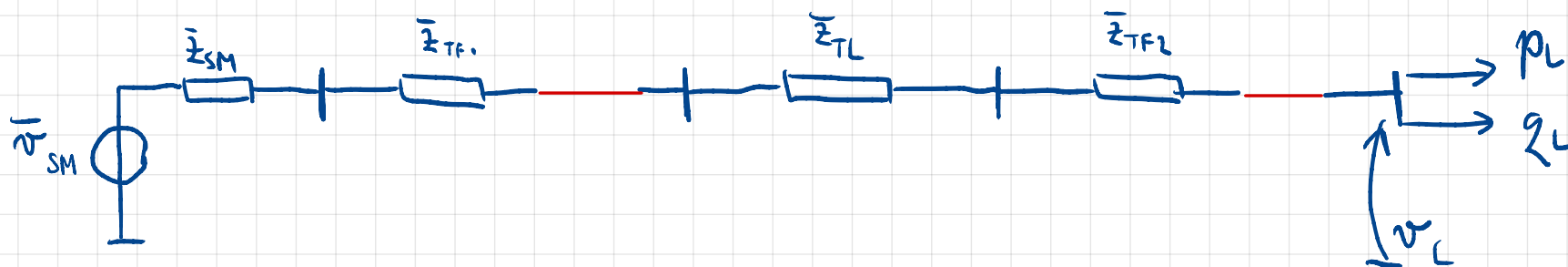


$$x_{SM}^{ds} = 1.1 \text{ p.u.} \longrightarrow X_{SM} = x_{SM}^{ds} \cdot \frac{V_n^2}{A_n}$$


$$\downarrow$$

$$x_{SM} = \frac{X_{SM}}{\frac{V_{b,1}^2}{A_b}} = x_{SM}^{ds} \cdot \frac{V_n^2}{A_n} \cdot \frac{A_b}{V_{b,1}^2} = 1.901 \text{ p.u.}$$
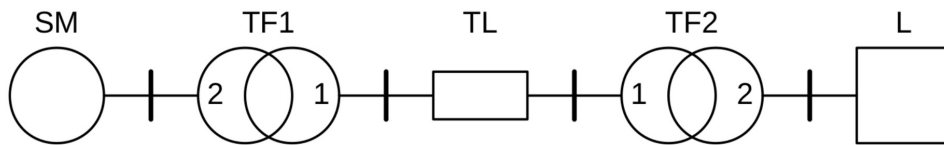
$$\bar{Z}_{SM} = jx_{SM} = j1.901 \text{ p.u.}$$




Component	Parameters
SM	$A_n=50$ MVA, $V_n=12$ kV, $x_{SM}=1.1$ pu ($\bar{Z}_{SM} = jX_{SM}$)
TF1	$A_n=60$ MVA, $V_{n,1}=220$ kV, $V_{n,2}=10$ kV, $V_{sc,\%}=10\%$
TL	$X_{TL} = 65 \Omega$ ($\bar{Z}_{TL} = jX_{TL}$)
TF2	$A_n=30$ MVA, $V_{n,1}=220$ kV, $V_{n,2}=20$ kV, $V_{sc,\%}=10\%$
L	$P_L=24$ MW, $Q_L=15$ MVar, $V_L=19$ kV

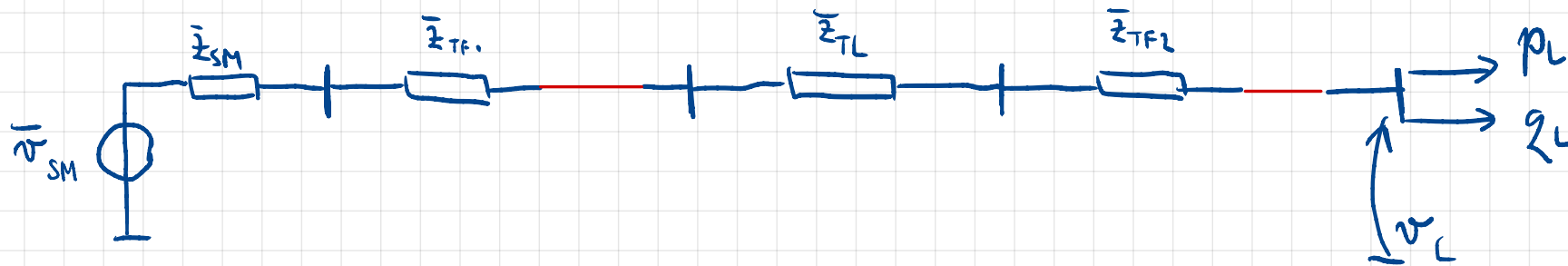

$$V_{sc, \text{op}} = 10\%$$

short-circuit test:

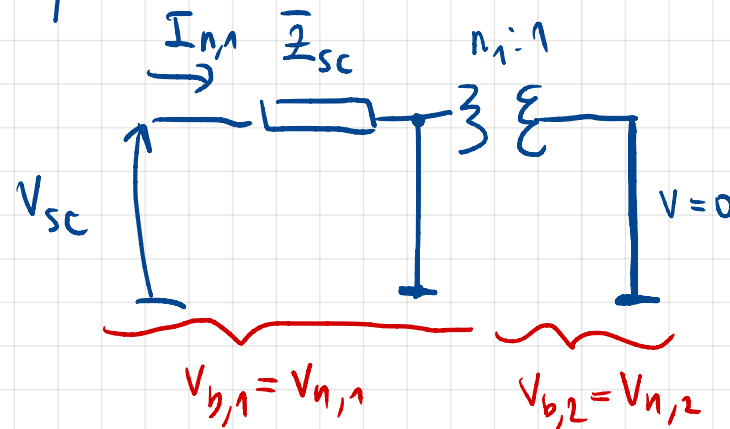


$$V_{sc} = \bar{Z}_{sc} \cdot I_{n,1}$$

$$\frac{V_{sc}}{V_{n,1}} = \frac{\bar{Z}_{sc} \cdot I_{n,1}}{V_{n,1}} = \frac{\bar{Z}_{sc}}{\bar{Z}_b} = \bar{Z}_{sc}$$


$$\bar{Z}_{TF1} = V_{sc, \text{op}} = 0.1,$$

$$\bar{Z}_{TF1} = j0.1 \text{ p.u.}$$

$$\parallel V_{sc, \text{op}}$$

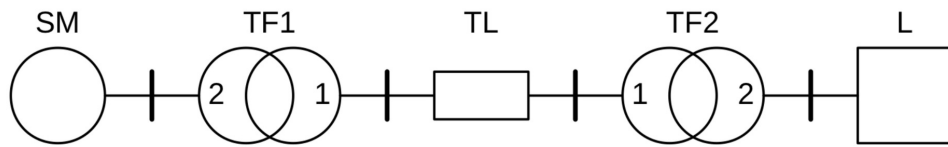

Component	Parameters
SM	$A_n=50$ MVA, $V_n=12$ kV, $x_{SM}=1.1$ pu ($\bar{Z}_{SM} = jX_{SM}$)
TF1	$A_n=60$ MVA, $V_{n,1}=220$ kV, $V_{n,2}=10$ kV, $V_{sc,\%}=10\%$
TL	$X_{TL}= 65 \Omega$ ($\bar{Z}_{TL} = jX_{TL}$)
TF2	$A_n=30$ MVA, $V_{n,1}=220$ kV, $V_{n,2}=20$ kV, $V_{sc,\%}=10\%$
L	$P_L=24$ MW, $Q_L=15$ MVar, $V_L=19$ kV

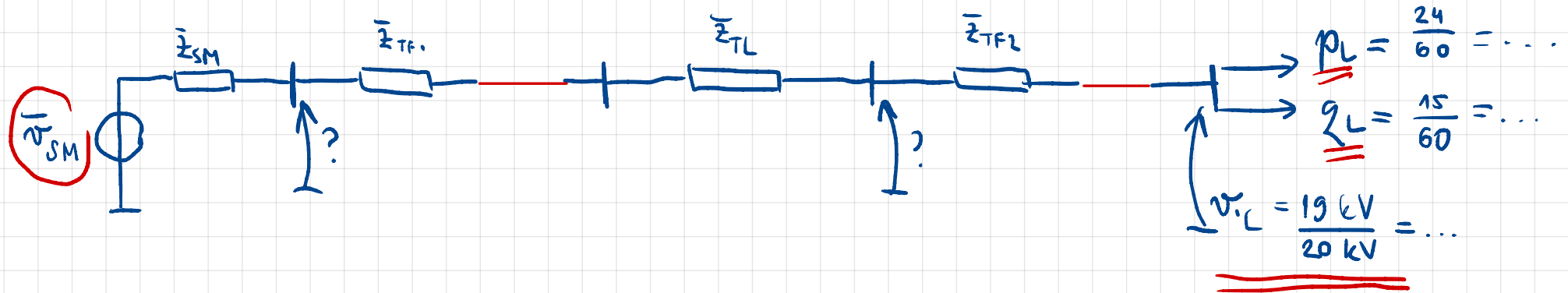

TL

$$x_{TL} = \frac{X_{TL}}{Z_{b,2}} = \frac{X_{TL}}{\frac{V_{b,2}^2}{A_b}} = 0.081 \Rightarrow \boxed{\bar{Z}_{TL} = j0.081 \text{ p.u.}}$$

TF2 $V_{sc,\%} = 10\%$

$$Z_{sc} = 10\% \cdot \frac{V_{n,1}^2}{A_n} : \frac{V_{n,1}^2}{A_b} = 10\% \cdot \frac{A_b}{A_n} = 0.2$$

$$\boxed{\bar{Z}_{TF2} = j0.2 \text{ p.u.}}$$