

ADVANCED VLSI DESIGN


Project Definition

04/03/2025

Contents

- **Design Overview: 64-bit Kogge-Stone Adder (Accumulator)**
- **Reminder on Parallel Prefix Adders**
 - Propagate, Generate Signals
 - Carry Merging
 - 16 Bit Kogge Stone Adder
- **Radix**
- **Sparsity**
- **64 Bit Kogge Stone Carry Merge Block with Radix 4, Sparseness 4**
- **Carry Select Adder**
- **Top Level Blocks**


Top Level Diagram: 64-bit Accumulator

 

$$\text{Out}[n+1] = \text{In}[n] + \text{Out}[n]$$

Specification:
Reg-Reg Delay < 500ps


64 Bit Accumulator

 


$$\text{OUT}_{64:0}[n+1] = \text{OUT}_{63:0}[n] + \text{IN}_{63:0}[n]$$

n : time index in discrete time domain


64 Bit Adder (Dynamic Logic)

 

16 Bit Kogge- Stone

 


16 Bit Kogge- Stone

 

Propagate, Generate, Merging

 
$$\begin{array}{ccccccc}
 & & \dots & A_N & A_{N-1} & \dots & \\
 + & & \dots & B_N & B_{N-1} & \dots & \\
 \hline
 \end{array}$$



$$\begin{aligned}
 P_{N-1} &= A_{N-1} + B_{N-1} \\
 G_{N-1} &= A_{N-1} \cdot B_{N-1}
 \end{aligned}$$

$$\begin{aligned}
 P_N &= A_N + B_N \\
 G_N &= A_N \cdot B_N
 \end{aligned}$$

 Predict C_N (carry)
considering the
stages N and $N-1$




$$G_{N:N-1} = G_N + P_N G_{N-1}$$

$$P_{N:N-1} = P_N P_{N-1}$$


**This Week
Design!!**

Implement with
Dynamic Logic

16 Bit Kogge-Stone

 


16 Bit Kogge-Stone (Radix 4)

 


Radix 2,3,4

Radix 2
2 Inputs
Fanout: 2
2 Series MOS

 


$$G_{1:0} = G_1 + P_1 G_0$$
$$P_{1:0} = P_1 P_0$$

Radix 3
3 Inputs
Fanout: 3
3 Series MOS

 

$$G_{2:0} = G_2 + P_2 G_1 + P_2 P_1 G_0$$
$$P_{2:0} = P_2 P_1 P_0$$

Radix 4
4 Inputs
Fanout: 4
4 Series MOS

 

$$G_{3:0} = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0$$
$$P_{3:0} = P_3 P_2 P_1 P_0$$

↑ Radix

↓ Logic depth

↓ Area


↑ Number of stacked MOS switches

↑ Fanout


↑ Gate complexity

↑ Top level routing Complexity

Atomic Element (Radix 4)

 

 
- More inputs per gate
- More stacked switches (4)
- Lower Logic Depth
- Smaller Area



- Less inputs per gate
- Less stacked switches (2)
- Higher Logic Depth
- Bigger Area




- Speed ??? Decision depends on your simulations

Atomic Element (Radix 4)

 


- Speed ??? Decision depends on your simulations

Atomic Element (Radix 4)

   


- Speed ??? Decision depends on your simulations

16 Bit Kogge-Stone (Radix 4)

 

Sparsity

Sparseness 1

 


Sparseness 2



Sparseness 3



Sparseness 4

 


↑ Sparseness

↓ Routing Complexity


↓ Area (Carry Merge Block)

↑ Need for Higher Number Bit Carry Select Adders


16 Bit Kogge-Stone (Radix 4)

 


16 Bit Kogge-Stone (Radix 4, Sparsity 2)

 


16 Bit Kogge-Stone (Radix 4, Sparsity 4)

 

 64 Bit Kogge-Stone (Radix 4, Sparsity 4) Structure/Slicing




4-Bit SLICE

 

Carry Select Adder

The result of the 4 bit addition is calculated in advance for both cases where

- Carry = 0
- Carry = 1

 

Carry Select Adder

- **G-P Block & CSA: 1 week (4-bit slice)**
- **Carry Merge Block: 1 week**
- **D-FlipFlop: $\frac{1}{2}$ week**
- **Top-level including clock tree: $1\frac{1}{2}$ weeks**

Questions?

16 Bit Kogge-Stone (Radix 2, Sparsity 4)

