

Date	Lecture (14–16 h)		Exercises (16–17 h)
20.02†	Basic safety of ME equipment		
27.02†	Biopotentials, bioimpedances		Session 1
06.03†	Electrodes, metrology of biopotentials		Session 2
13.03†	Metrology of bioimpedances		Session 3
20.03†	TEST 1	Optical sensors (PPG, oBPM)	Session 4
27.03†	Optical sensors (SpO2, NIRS)		Session 5
3.04*	Resistive sensors		Session 6
10.04*	Inductive sensors		Session 7
17.04*	TEST 2	Resistive & Inductive sensors	Session 8
24.04	Easter holiday		
1.05*	Capacitive sensors		Mock test
8.05*	Capacitive sensors		Session 9
15.05*	Piezoelectric sensors		Session 10
22.05*	TEST 3	Capacitive & Piezoelectric sensors	Session 11
29.05	Ascension holiday		

† Olivier Chételat, * Anisoara Ionescu

Rules for TEST 1 (copied from moodle)

- 14:15–15:00, MX F1 (same place as for the class)
- scope: what has been taught until March 13 (included)
- on paper, individually
- 25 questions, single choice (only one answer is correct)
 - correct answer: 3 points
 - no or multiple answers: 0 point
 - wrong answer: –1 point
- all questions with the same weight, 5% of course grade
- with Camipro Card
- no internet, no SMS
- OK: personal notes, EE-511 documents on moodle (paper or electronic support)

Example:

The questions may be written in the form of statements. If so, **indicate which statement is true:**

Work is produced by muscles from

- ☒ chemical energy
- ☐ electrical energy
- ☐ thermal energy
- ☐ nuclear energy

In the above example, there are four statements:


- Work is produced by muscles from chemical energy.
- Work is produced by muscles from electrical energy.
- Work is produced by muscles from thermal energy.
- Work is produced by muscles from nuclear energy.

The first one is correct; the three|others are incorrect.

Quiz

We have

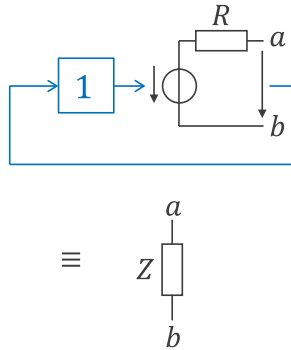- ☐ $Z = 0$
- ☐ $Z = -R$
- ☐ $Z = \infty$
- ☐ $Z = 2R$




Electrodes N and RL are

- ☐ averaged for Wilson CT potential
- ☐ negative and right-lead electrodes
- ☐ white and purple electrodes
- ☐ two names for the same electrode


We have

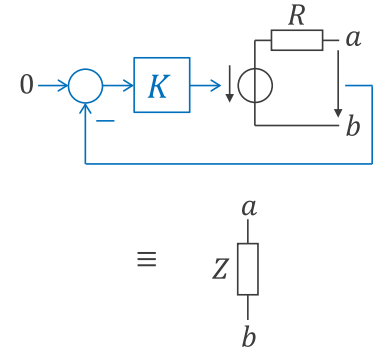- ☐ $Z = 0$
- ☐ $Z = -R$
- ☐ $Z = \infty$
- ☐ $Z = 2R$



We have

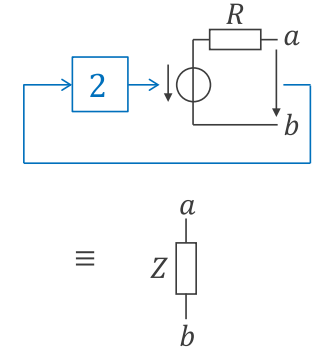- ☐ $Z = 0$
- ☐ $Z = -R$
- ☐ $Z = \infty$
- ☐ $Z = 2R$



EE-511 Sensors in medical instrumentation

Lesson 7 – Metrology of bioimpedances

- 4.6.1 Devices for bioimpedance measurement
- 4.6.2 Bipolar method
- 4.6.3 Tetrapolar method
- 4.6.4 Impedance signals at a given frequency
- ~~4.6.5 Sinewave current~~
- 4.6.6 Demodulator
- 4.6.7 Wire and cable leakages
- 4.6.8 Example of complete circuit

Objectives

understand:

- bipolar method, tetrapolar method
- AM, IQ demodulation
- leakage, shielding

4.6.1 Devices for bioimpedance measurement


- Impedance plethysmography



- Bioimpedance analysis



- Electrodermal activity


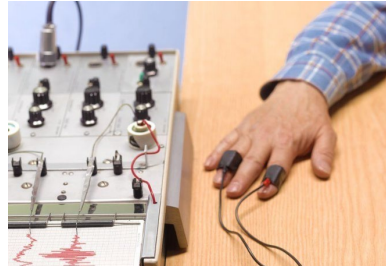


- Electrical impedance tomography



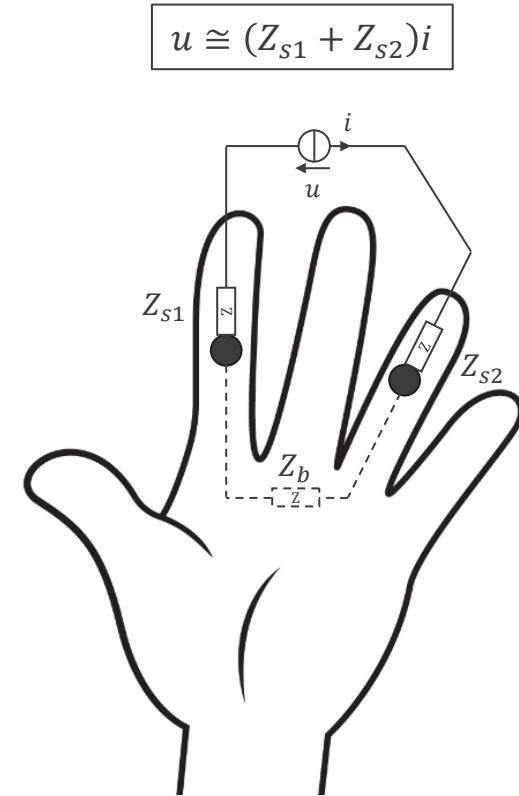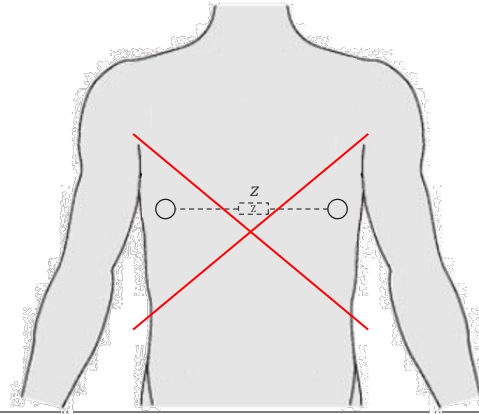4.6.2 Bipolar method

- $Z_{s1}, Z_{s2} \gg Z_b$
- therefore, measured bioimpedance is $\cong Z_{s1} + Z_{s2}$
- good for EDA (electrodermal activity)




$$u \cong (Z_{s1} + Z_{s2})i$$

4.6.3 Tetrapolar method


- different pair of electrodes
 - one as potential electrodes
 - one as current electrodes
- independent of skin impedance

$$u = Zi$$

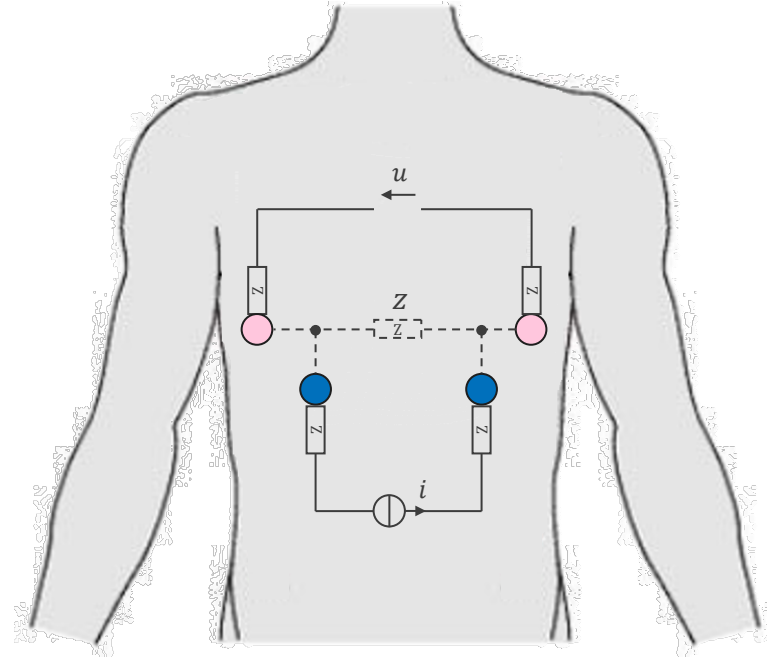

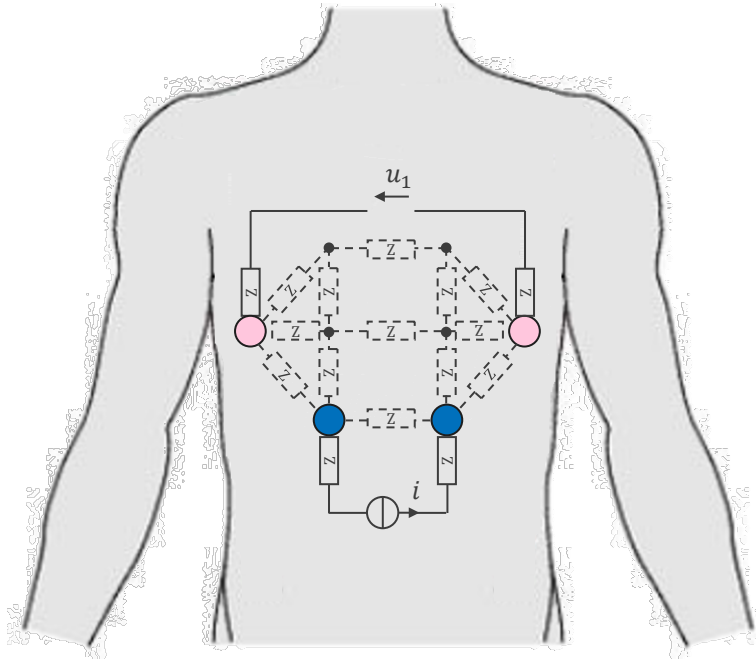
4.6.3 Tetrapolar method (continued)

- in reality, bioimpedance is a distributed network



$$? \\ u_1 = u_2$$


(yes: reciprocity theorem)

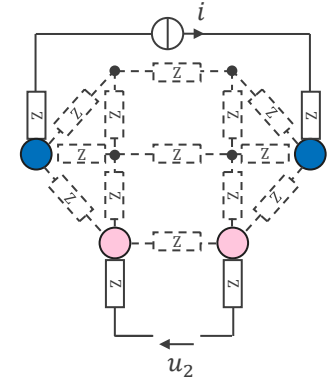





4.6.4 Impedance signals at a given frequency

$$u(t) = RI \cos \omega t + XI \sin \omega t$$
$$u = RI + jXI$$



$$i(t) = I \cos \omega t$$
$$i = I$$

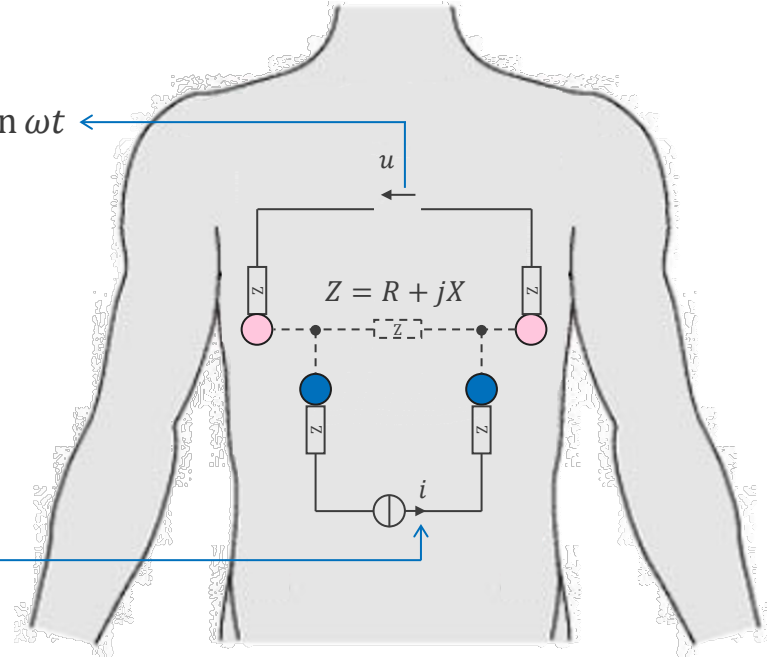

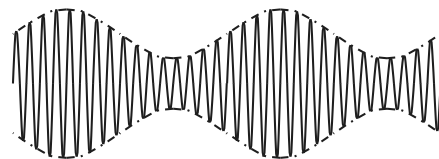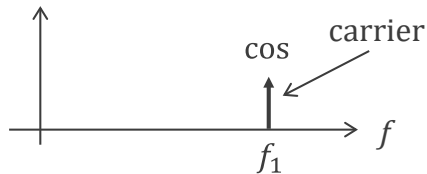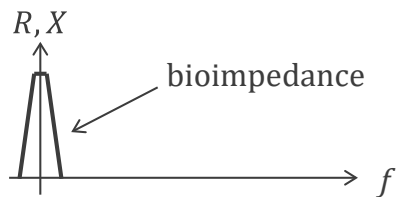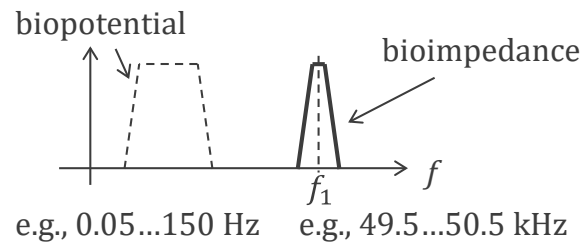4.6.4 Impedance signals at a given frequency (continued)





$$Z_1(t) = R_1(t) + jX_1(t)$$

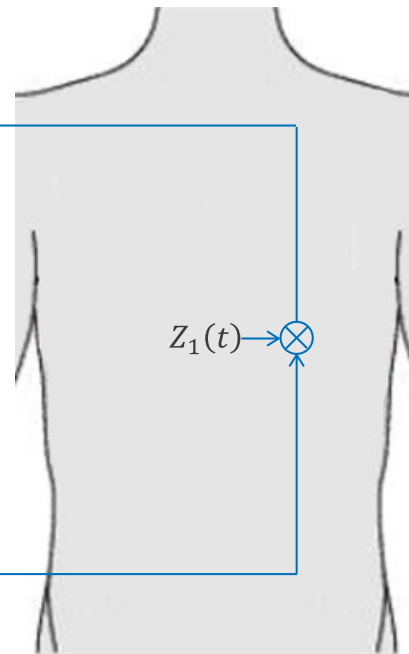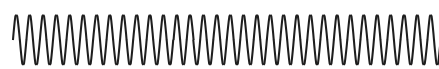


4.6.6 Demodulator

IQ demodulation

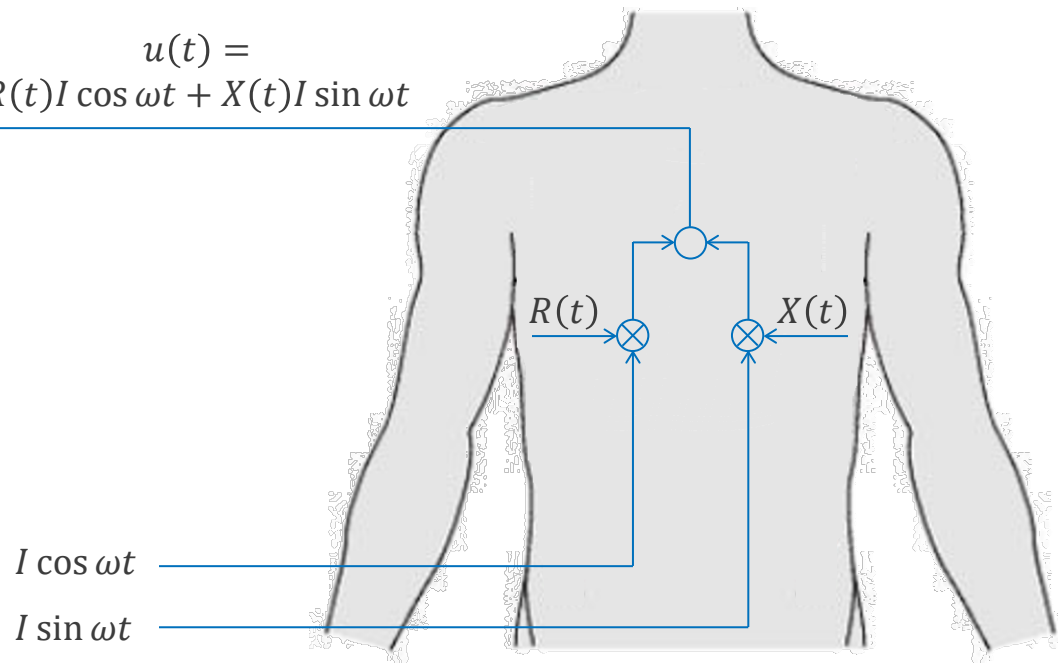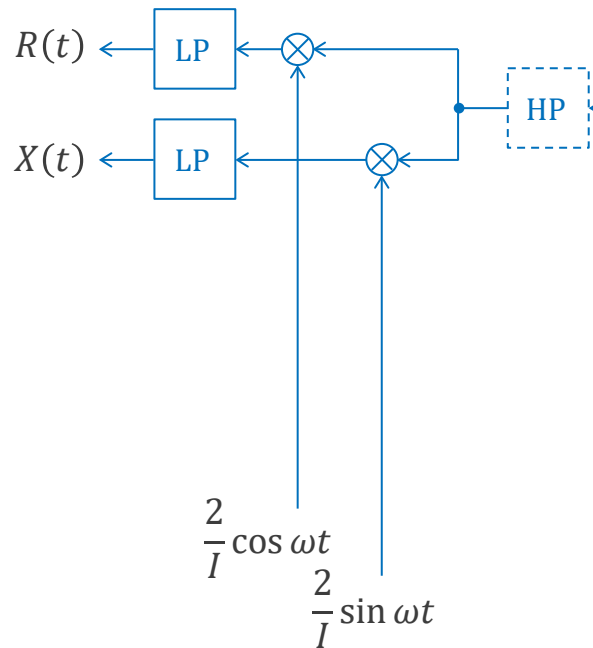


4.6.6 Demodulator (continued)

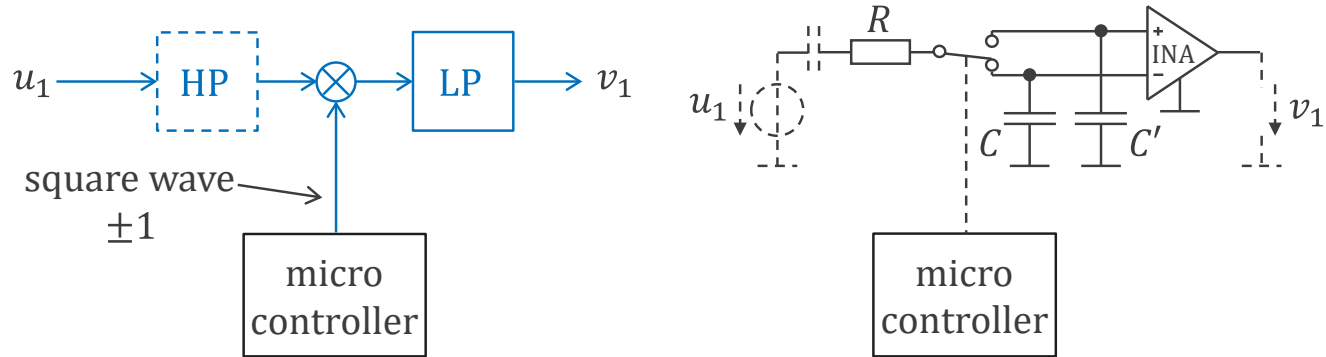


4.6.7 Wire and cable leakages

- stray capacitance between wires

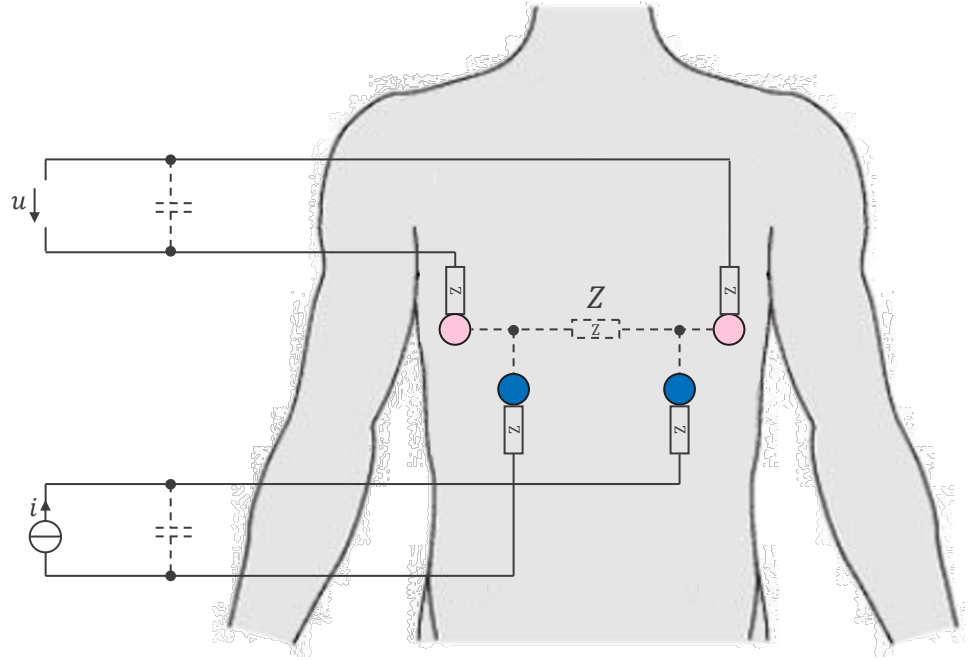


4.6.7 Wire and cable leakages (continued)

- solution: driven shield

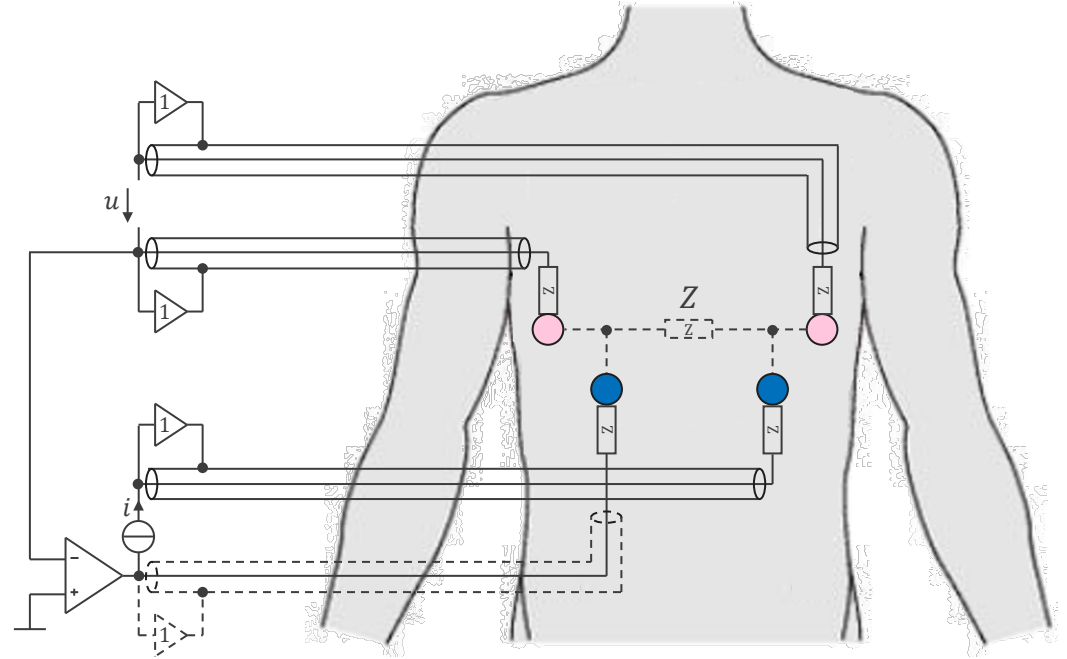


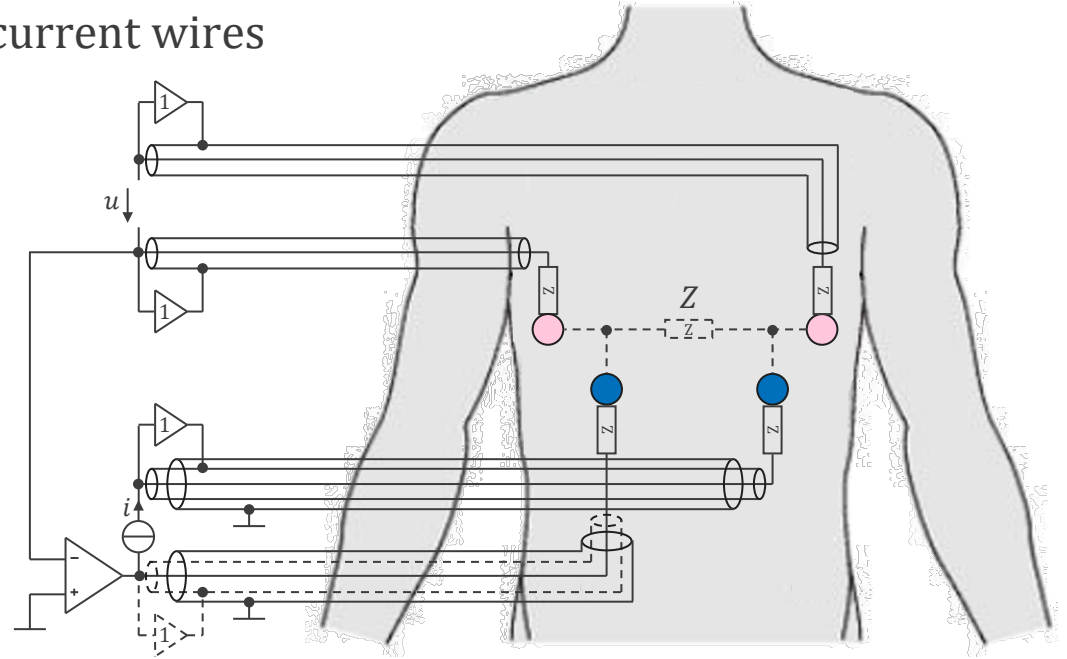4.6.7 Wire and cable leakages (continued)

- solution: double shielding of current wires



4.6.8 Example of complete circuit

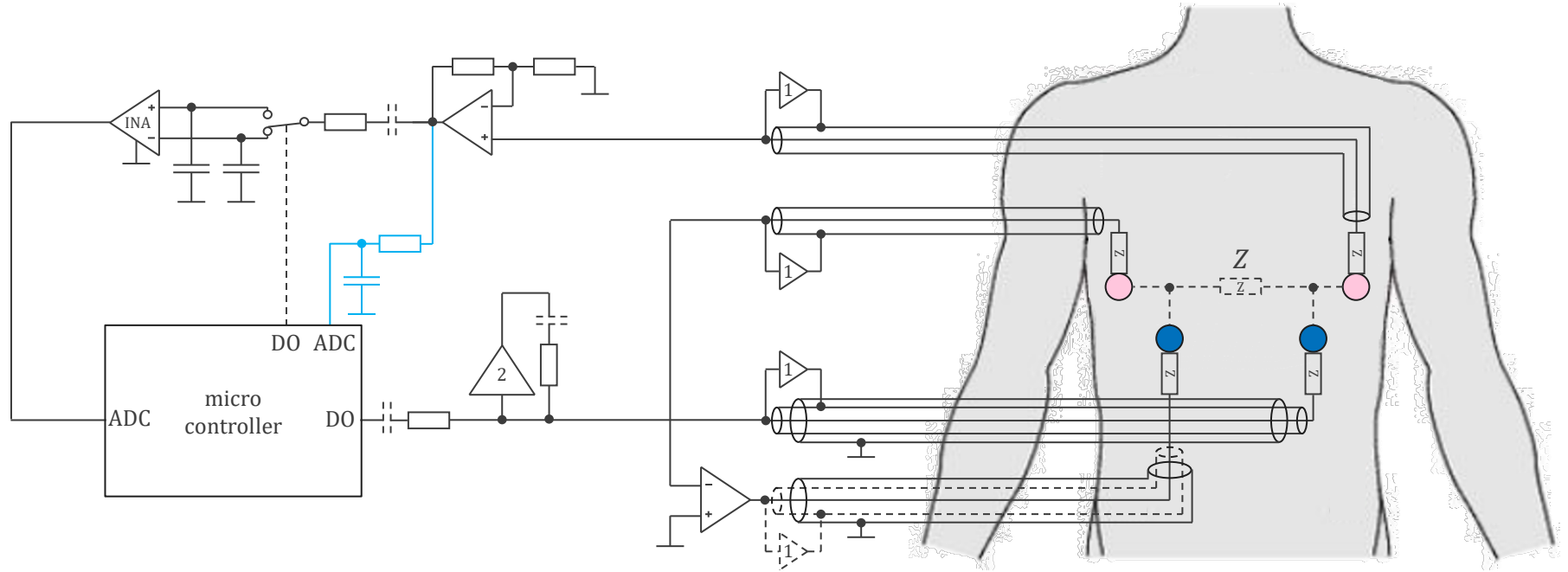

Example

