



**Master in Electrical and Electronics Engineering**

**EE-517**: Bio-Nano-Chip Design

# **Lecture #13**

## CMOS Circuits for DNA Detection

# Lecture Outline

(Book Bio/CMOS: Chapter' paragraphs § 7.1-8)

- CMOS for DNA capacitance detection
- Charge-Based Capacitance Measurement (CBCM) Method
- Frequency-to-Capacitance Measurement (FTCM) Method
- CMOS for DNA Amperometric detection

# CMOS architectures for VLSI



in DNA Detection




Q1

# Do we really need point-of-care portable DNA detectors?


- A. No, that's just an academic fashion!
- B. Not really, even though it might be useful for precision medicine
- C. Yes, since it is useful for precision medicine
- D. Yes, since it might be useful to establish genetic predispositions**
- E. Yes, of course!

# Electrochemical Interface

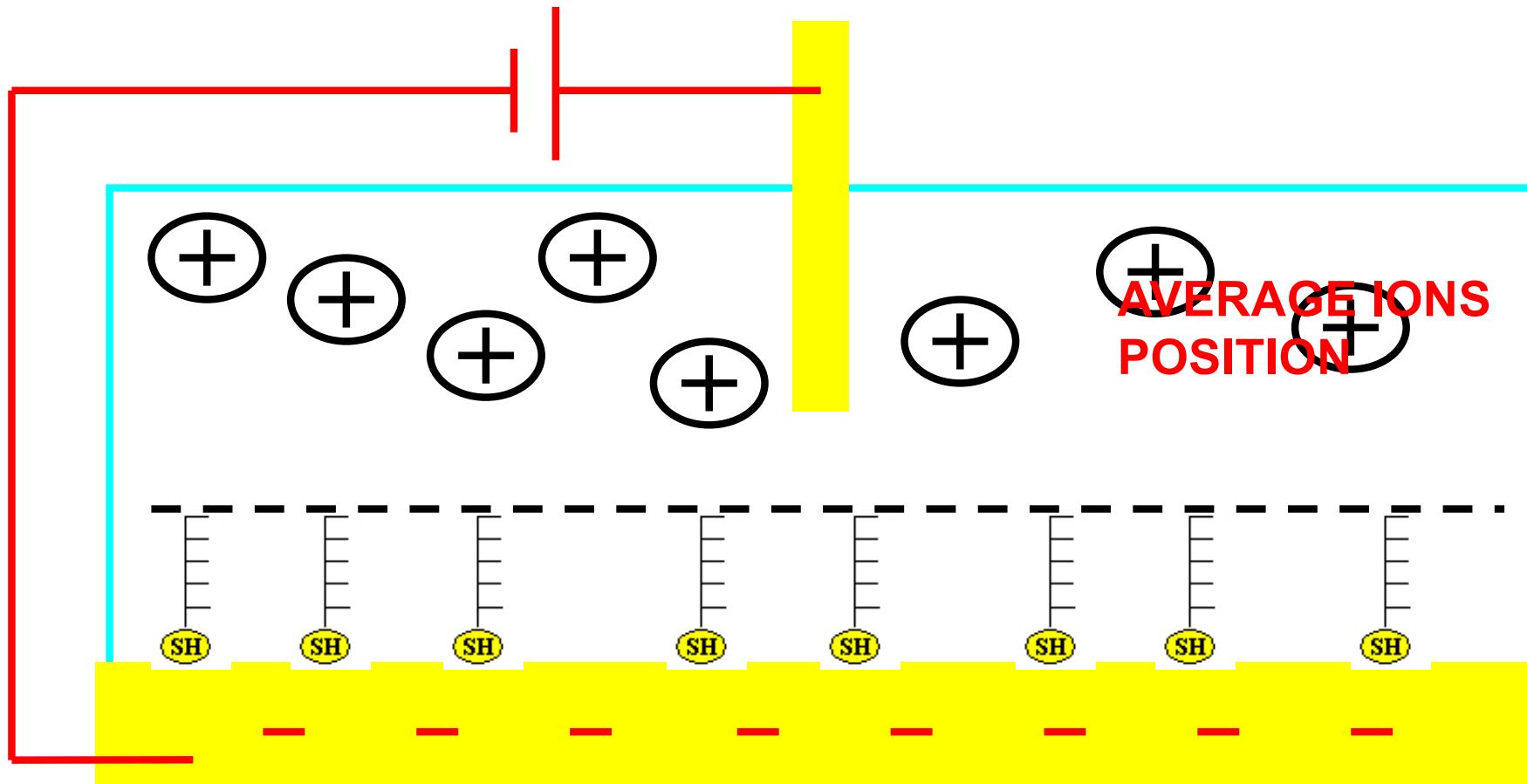

Ion planes are formed at the interface when electrodes immersed in solution are polarized

# Electrochemical Interface

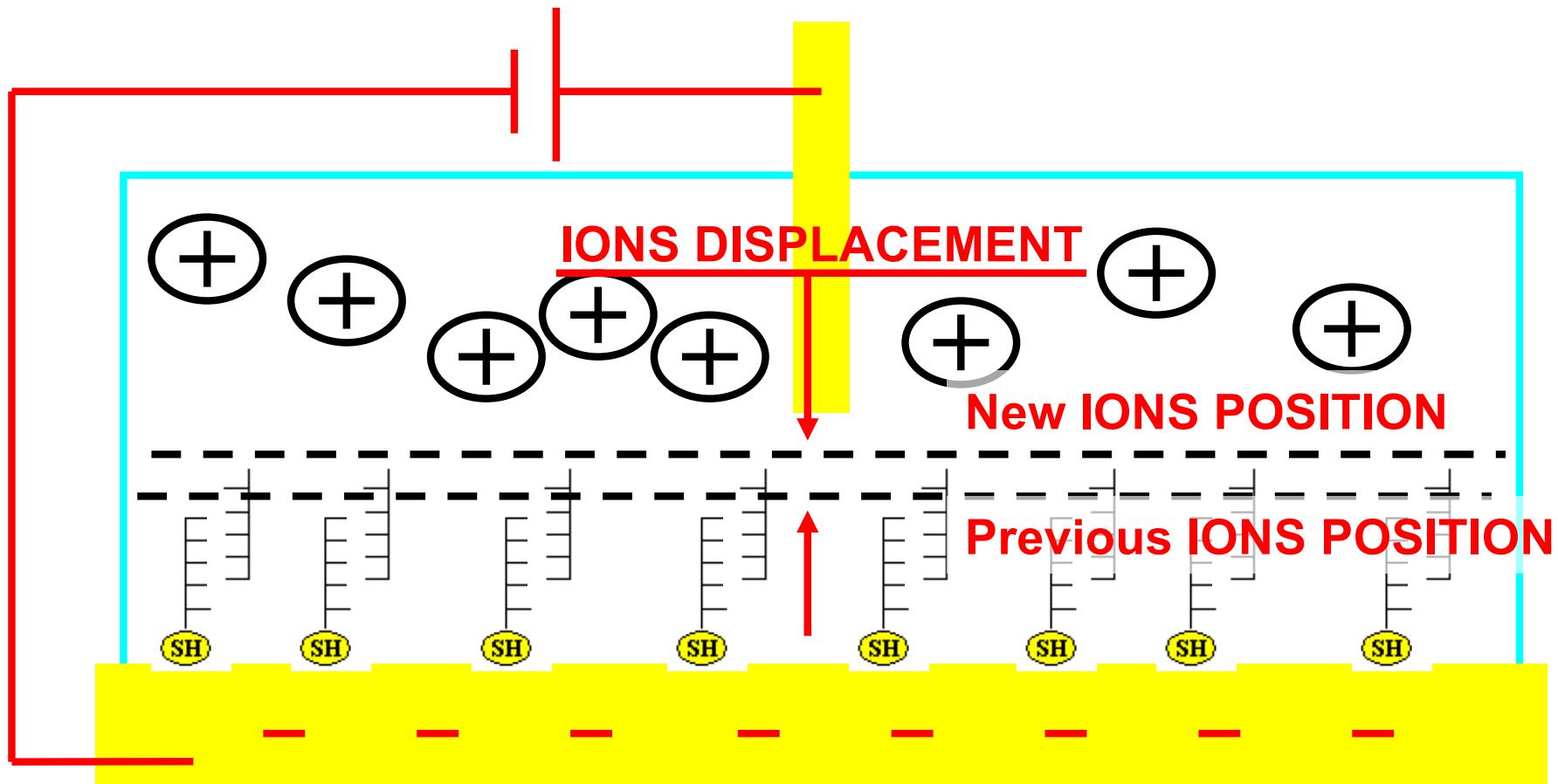

Ion planes are formed at the interface when electrodes immersed in solution are polarized




Q2

## Do we usually get only the fully matching sequences?


- A. No, we always have mismatches
- B.** Yes, but we might get few-bases mismatch
- C.** May be, since we might get non-specific adsorption on the surface
- D. On same probes, we may get a wrong sequence
- E. Yes, of course!

# The Capacitance DNA Detection

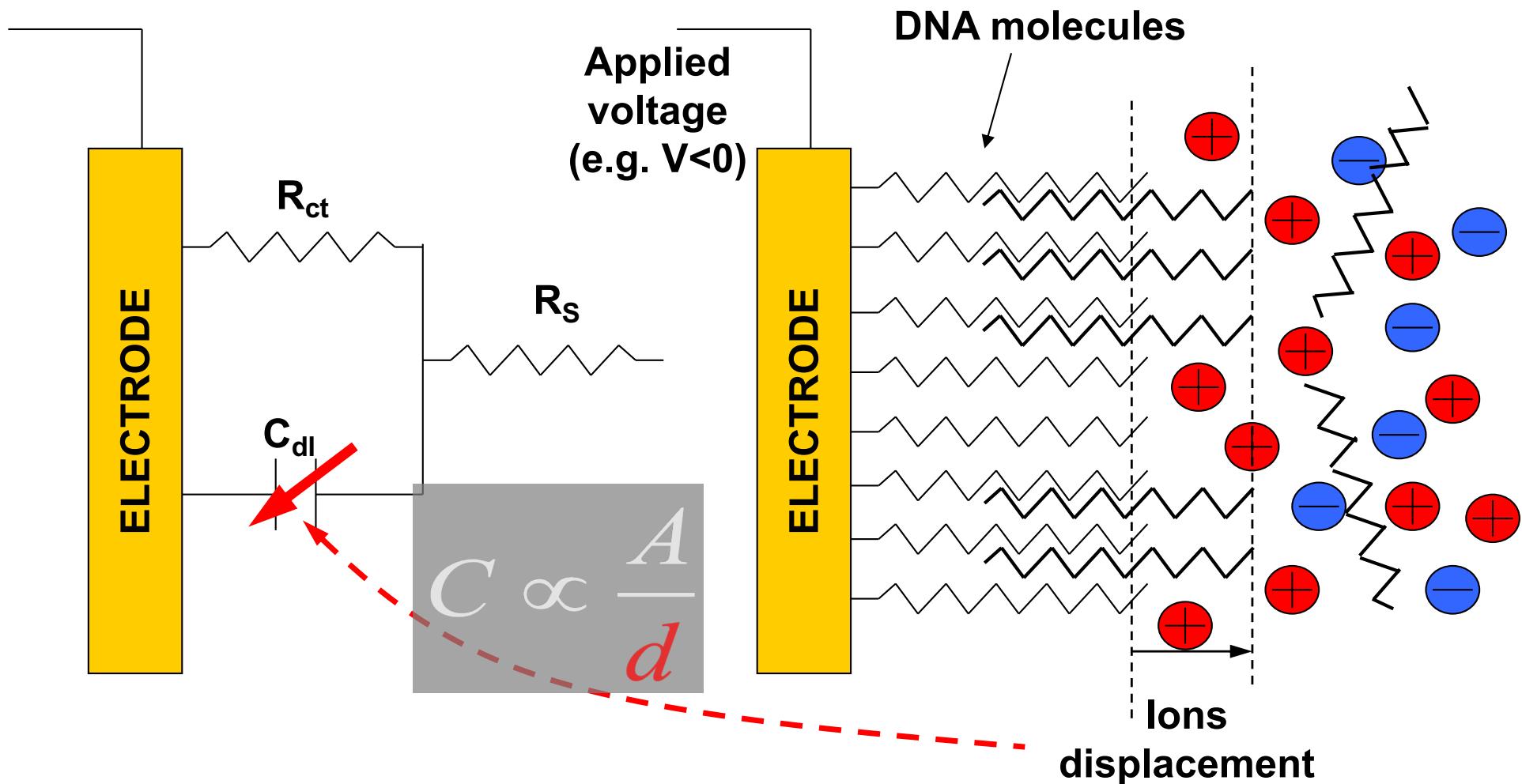

Unlabeled ssDNA may be detected with capacitance measurements as due to charge displacement
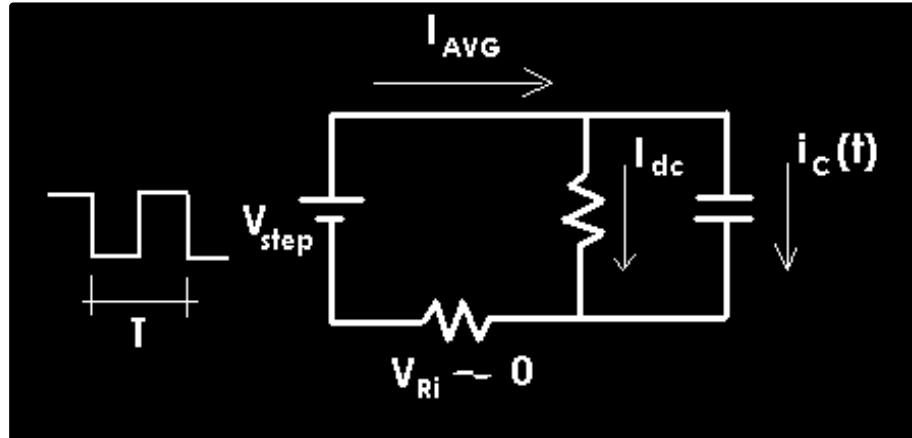
# Charge-Based Capacitance Measurement (CBCM)




$$i(t) = I_{dc} + i_C(t)$$

Frequency!

$$I_{AVG} = \frac{I_{dc}}{2} + \frac{1}{T} \int_0^{T/2} i_C(t) dt$$

$$I_{AVG} = \frac{I_{dc}}{2} + C V_{step} f$$

THE CAPACITANCE !

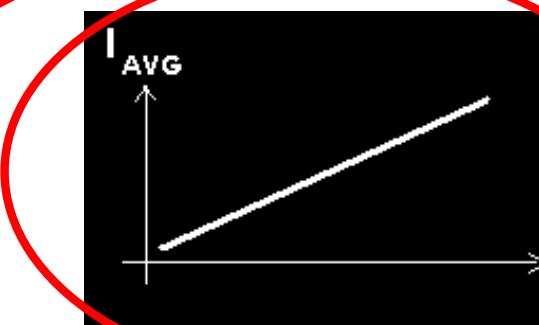

Method for a precise Capacitance measurement




Q3

# Is that correct to estimate the C-value in frequency?


- A. No, C always changes with the frequency
- B. Not always, since C might change with the frequency**
- C. May be, in case of some good interfaces**
- D. Some times, we got a totally wrong estimation
- E. Yes, of course!

# CMOS for CBCM detection

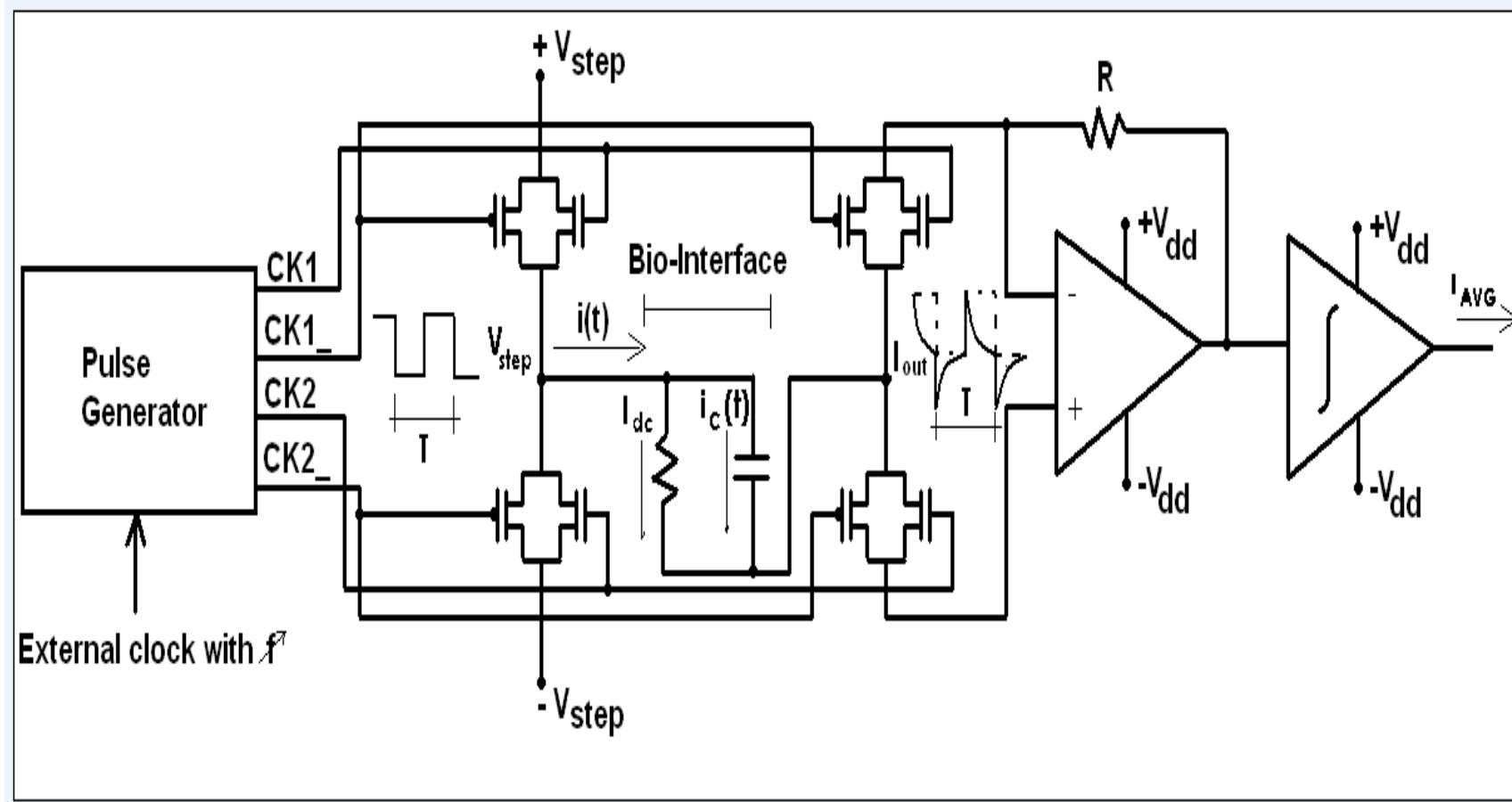


The circuit assures the square signal generator, an inverters, and an integrator to calculate the average current

# *The Chip Electrodes Layout*

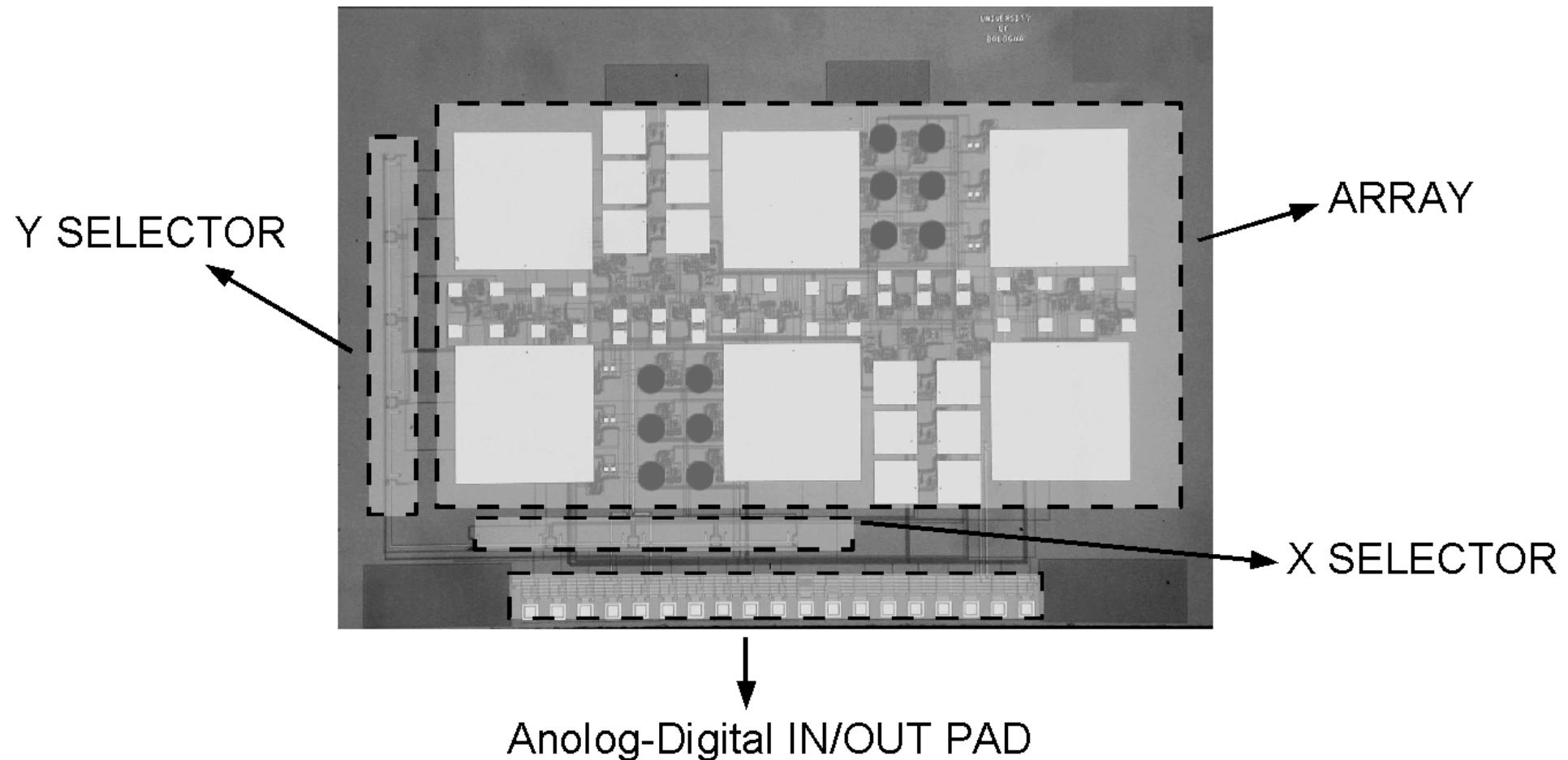

# *The VLSI Implementation of the Chip (CBCM method)*

*(CBCM = Charge Base Capacitance Mode)*

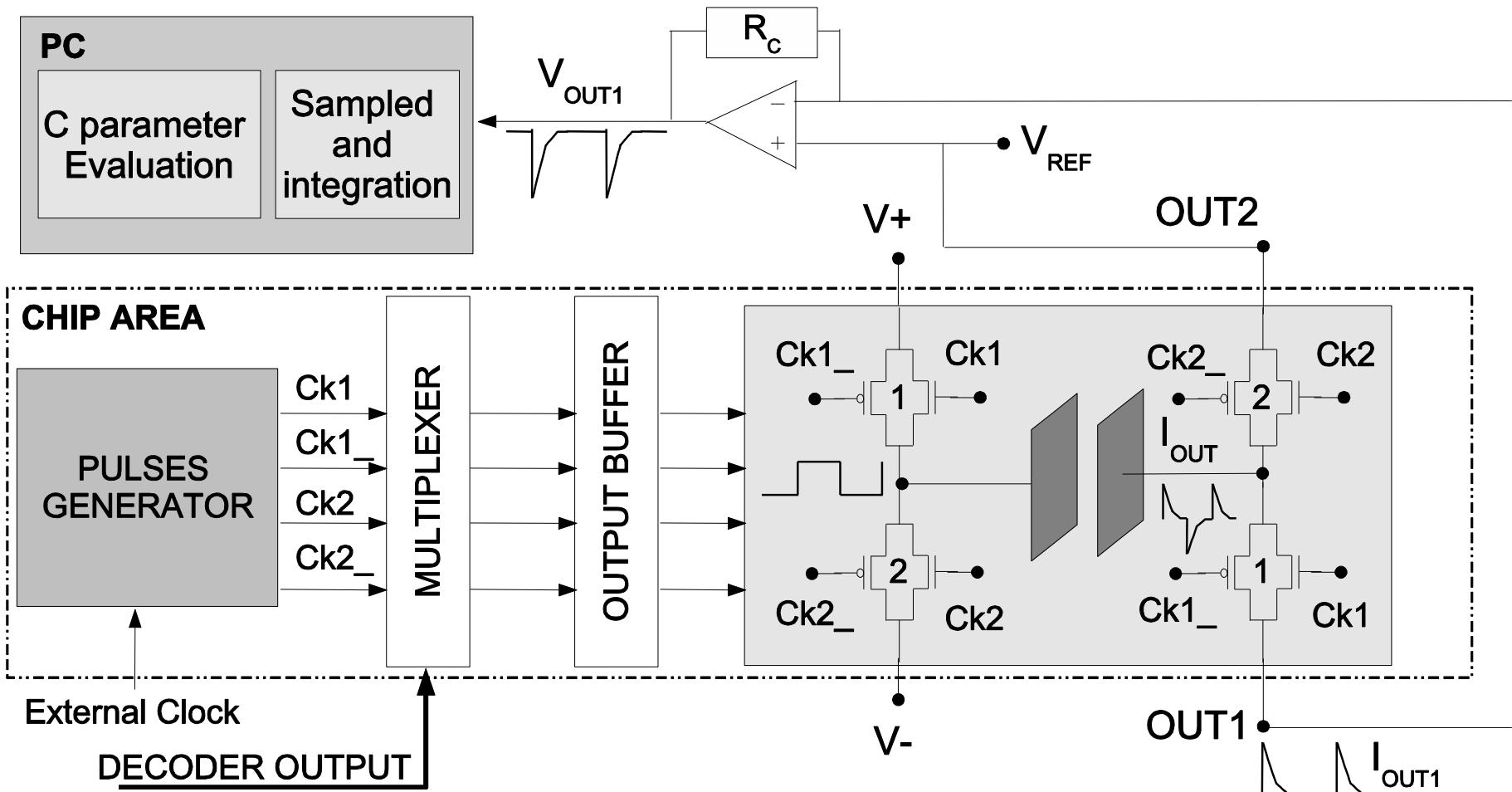

# The problem of overlapping signals

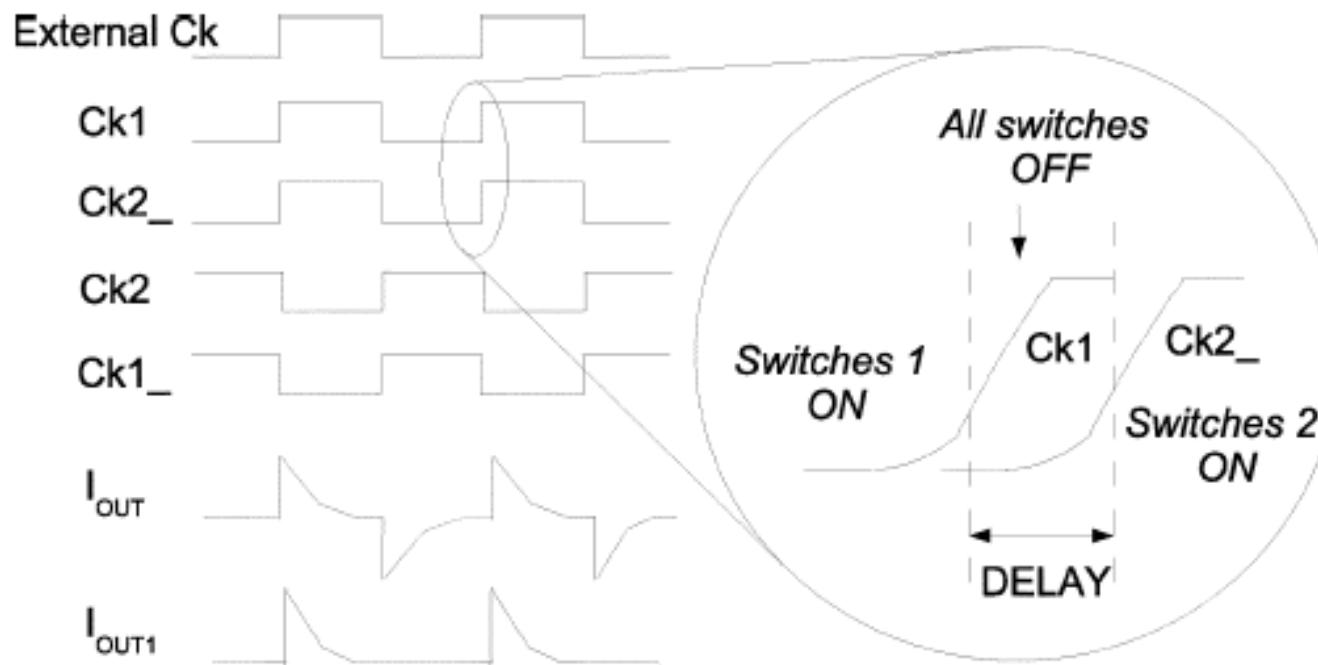


Fig. 4. Schematic representation of the signals flow used in the experiments.

$Ck$  and  $Ck_$  signals need to be not-overlapping in order to assure the correct square signal generation

# The circuit solution

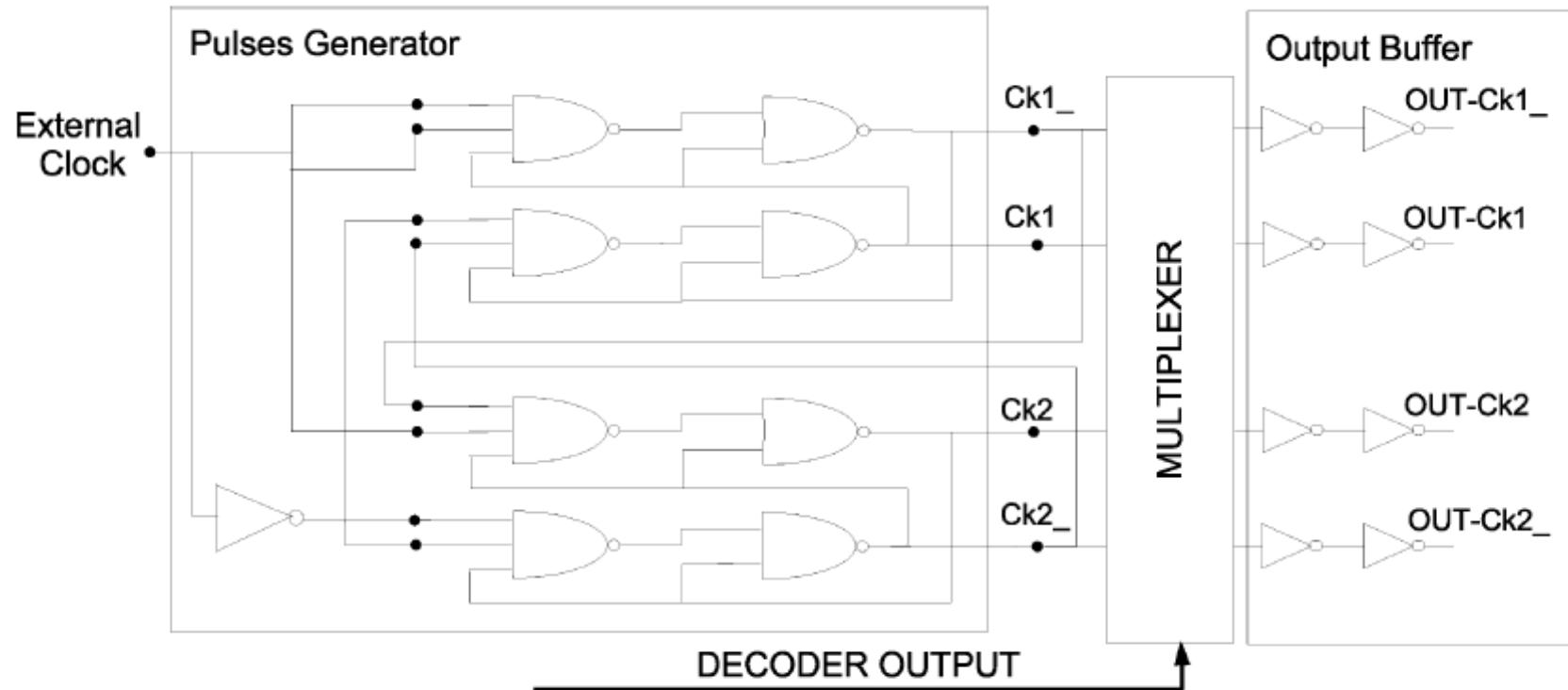


Fig. 5. Schematic plot of the block used to generate not overlapping clock signals.

A simple logical circuit and a digital multiplexer assures not-overlapping  $Ck$  and  $Ck_$  signals

# The Measurements Set-up

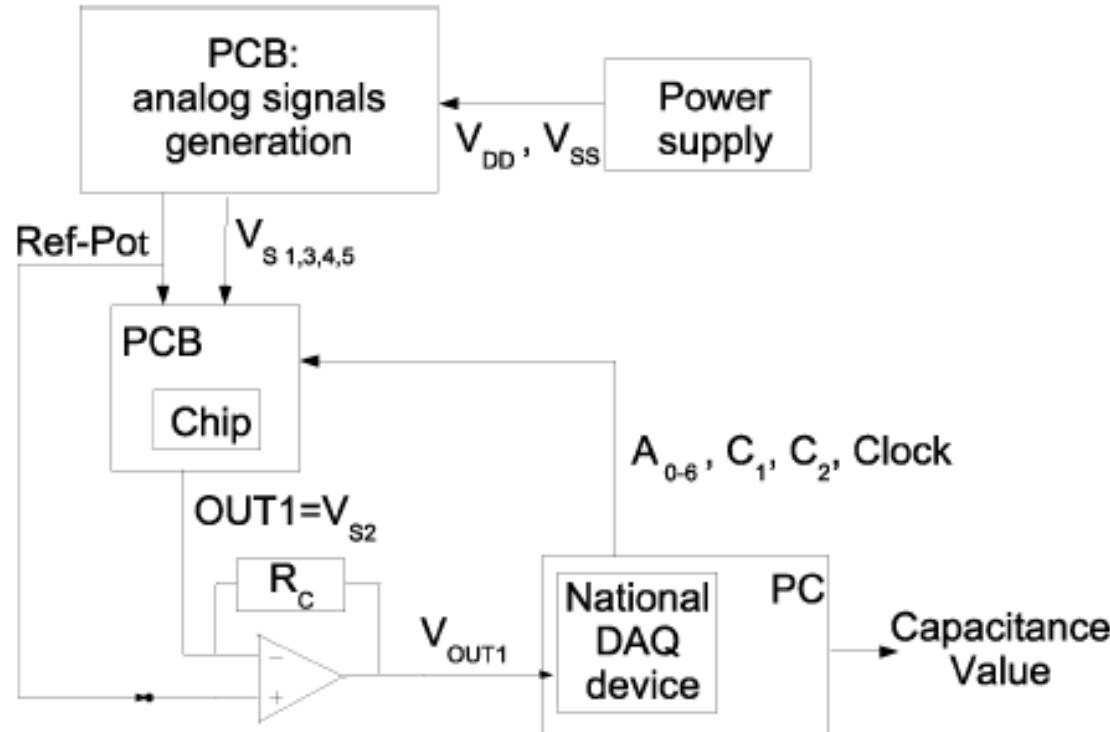


Fig. 8. Schematic representation of the measurement setup.

The Chip has been mounted onto a PCB for PC remote control and testing

# Liquid Measurement set-up




Output PCB pads

Bonding wires


Chip is glued on a PCB

Fluidic cell

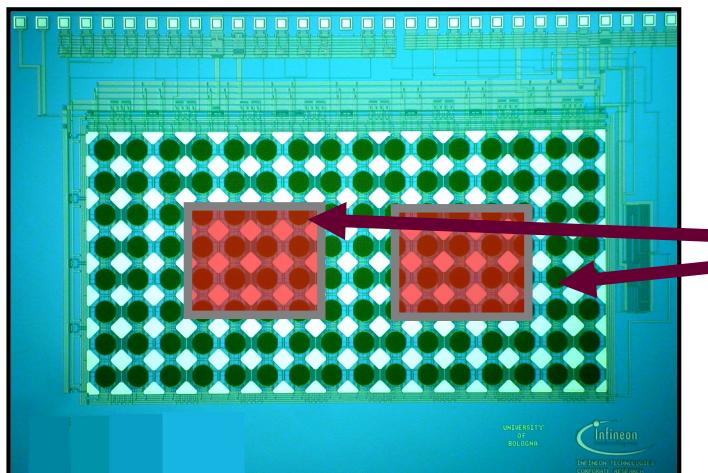

Two different  
Chambers  
1mmX1mm

(c) S.Carrara

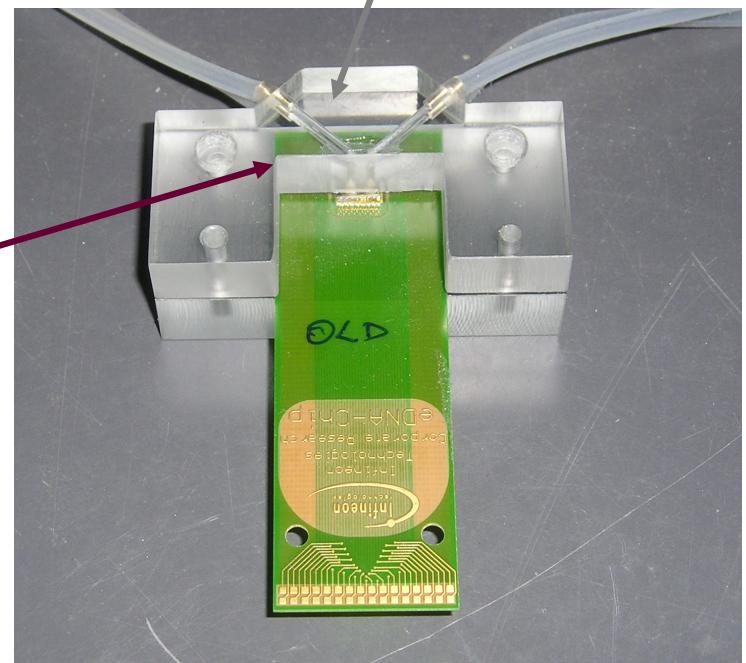

# DNA detection in CBCM mode

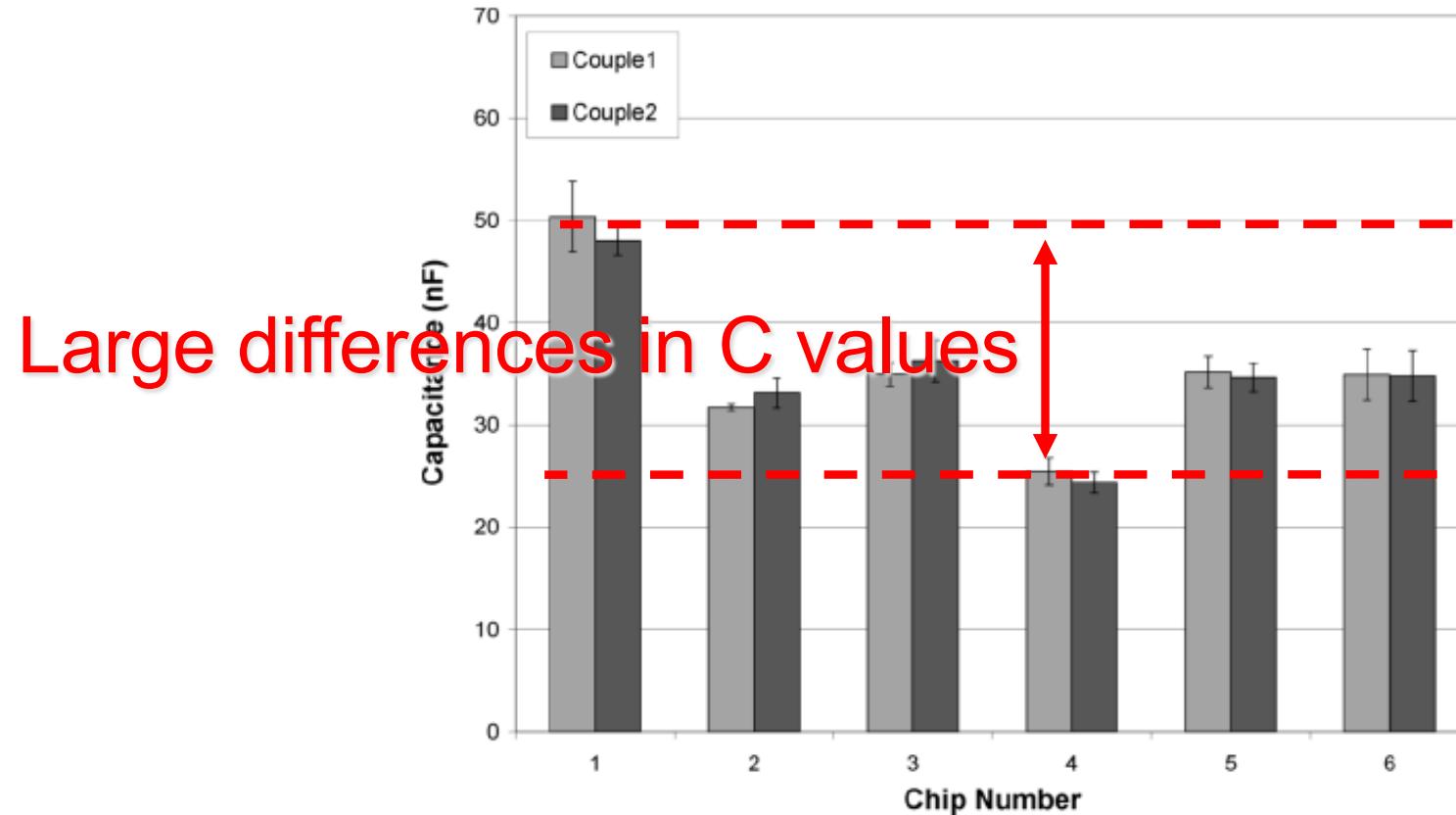


Fig. 10. Capacitance measurements of electrode couples on different chips.

The chip-by-chip reproducibility has been not so high:  
the problem is on the chip electrodes cleaning



Q4

## Is it correct to use CBCM for the C-value on bare electrodes?

- A. No, C always changes with the frequency
- B. Not always, since C might change with the frequency
- C. May be, in case of some good interfaces
- D. Some times, we got a totally wrong estimation
- E. Yes, of course!

# Capacitance vs Frequency

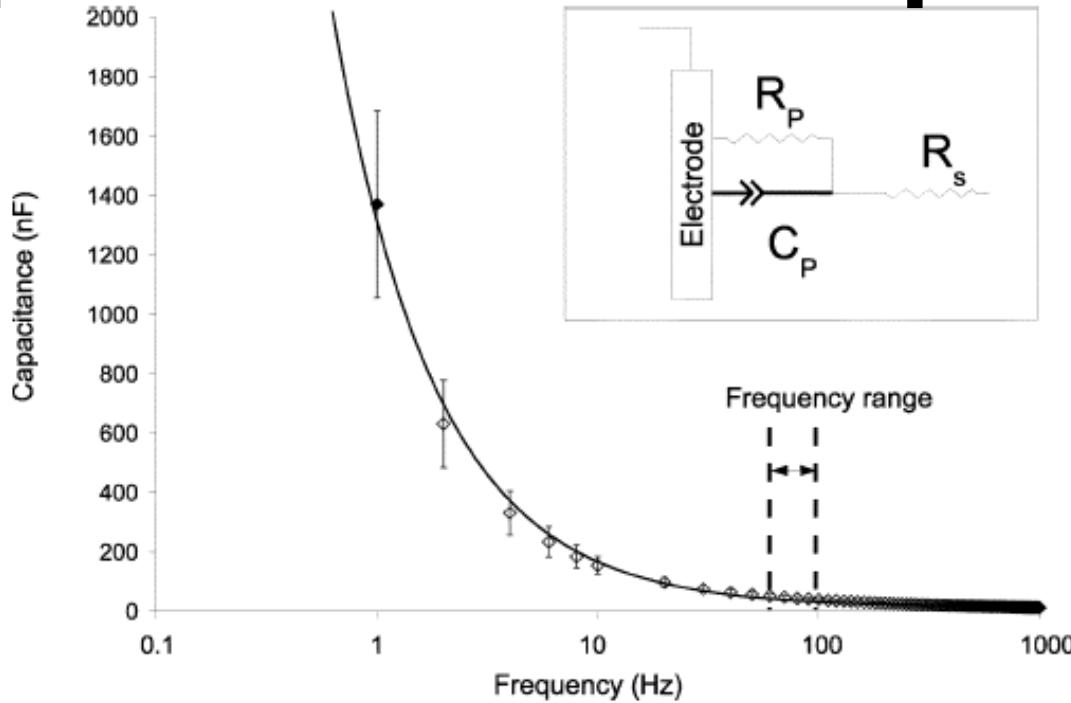


Fig. 9. Measured capacitance versus charge/discharge frequency on clean gold electrodes. The continuous line shows the fitting.

The trends of the measured capacitance vs frequency decrease the accuracy of the measurements in CBCM mode




Q5

## May we improve the ideality of C-behaviour of gold electrodes?


- A. Impossible, C always changes with the frequency
- B. Not easy, since C might change any way with the frequency
- C.** May be, in case of some good self-assembly
- D. Some times, we get the right behavior
- E.** Yes, by measuring at high frequency!

# Good DNA Layer

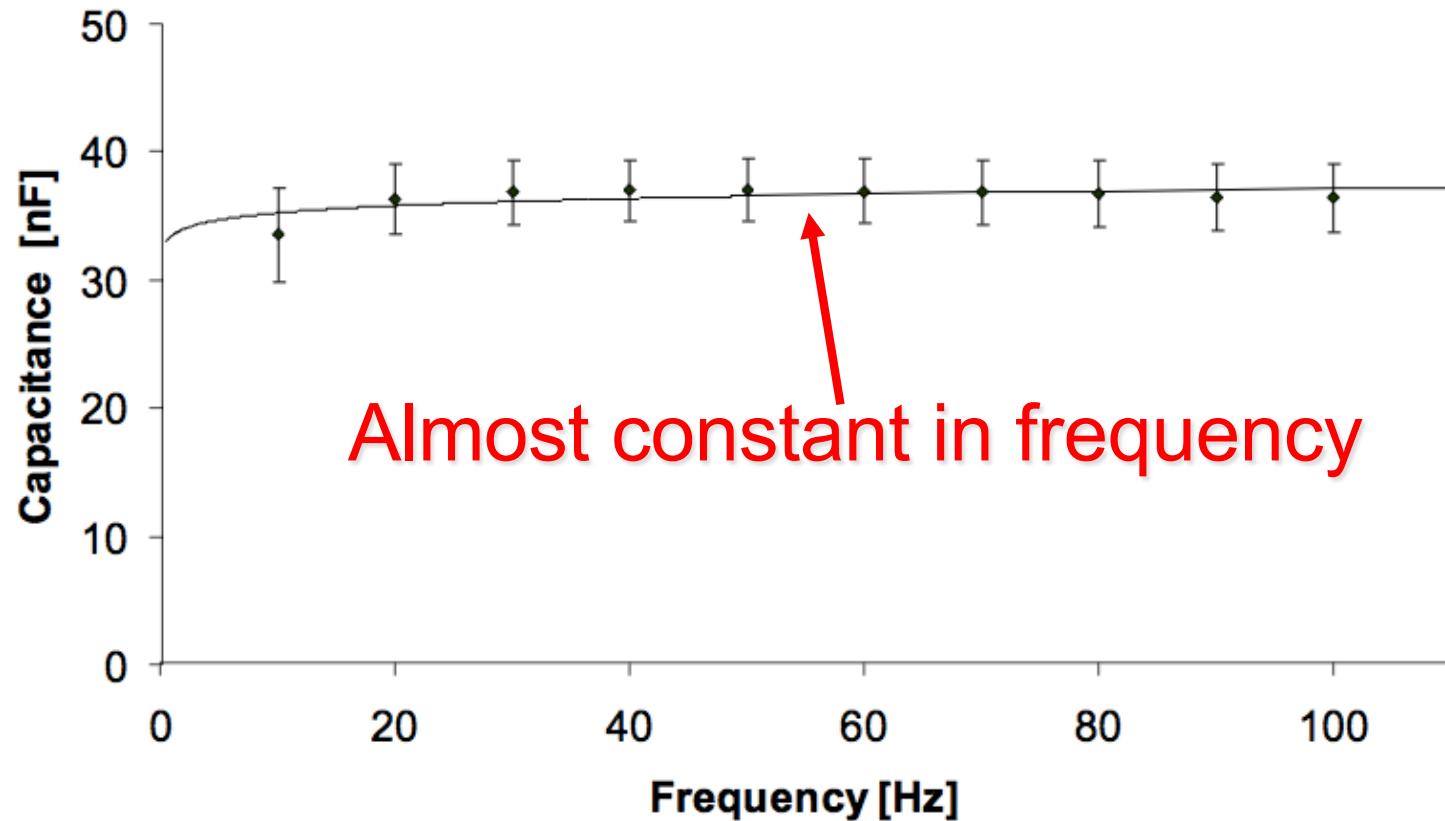


DNA Layer is independent by the frequency thanks to probes immobilized on Ethylene-Glycol Thiols

# CBCM on good DNA Layer

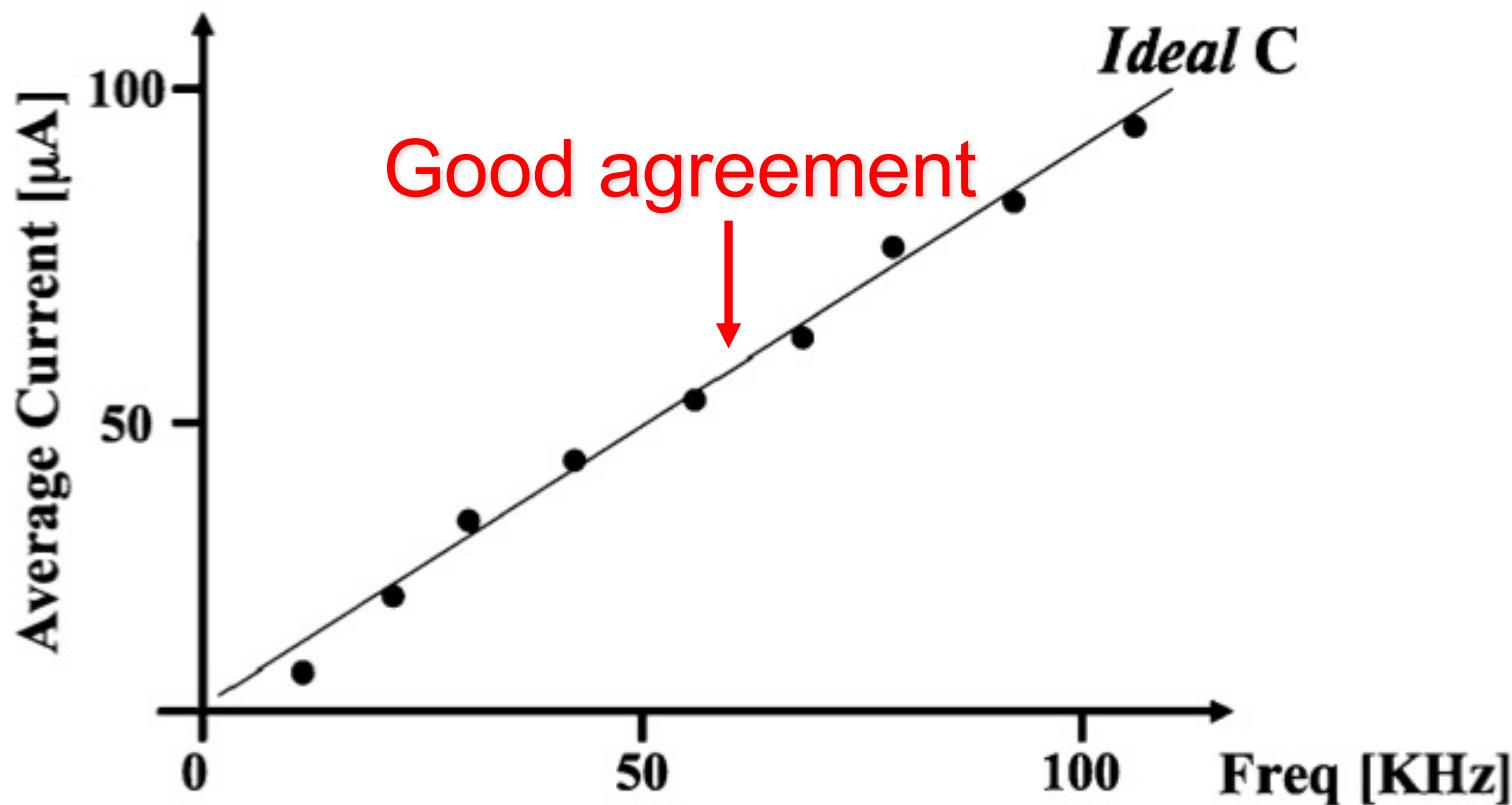

CBCM method on a DNA Layer that is  
independents by the frequency

# Bad DNA Layer

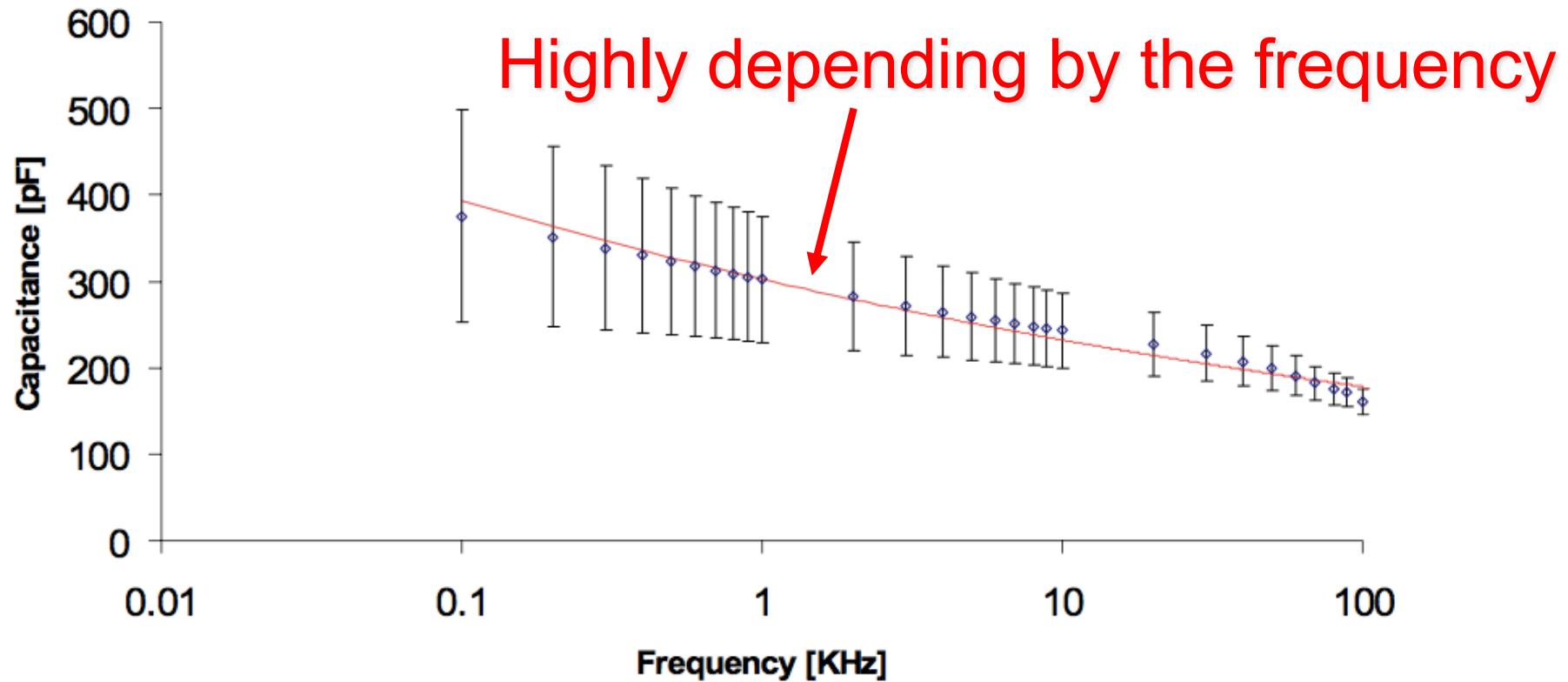

DNA Layer is dependent by the frequency since the monolayer is not extremely well formed




Q6

## How much wrong may be the C-value estimation by CBCM?

- A. Always really bad since C always changes in frequency
- B. Some times really wrong, when C changes in frequency**
- C. Almost always good, in case of DNA interfaces
- D. Always largely good
- E. Always largely wrong

# CBCM on bad DNA Layer

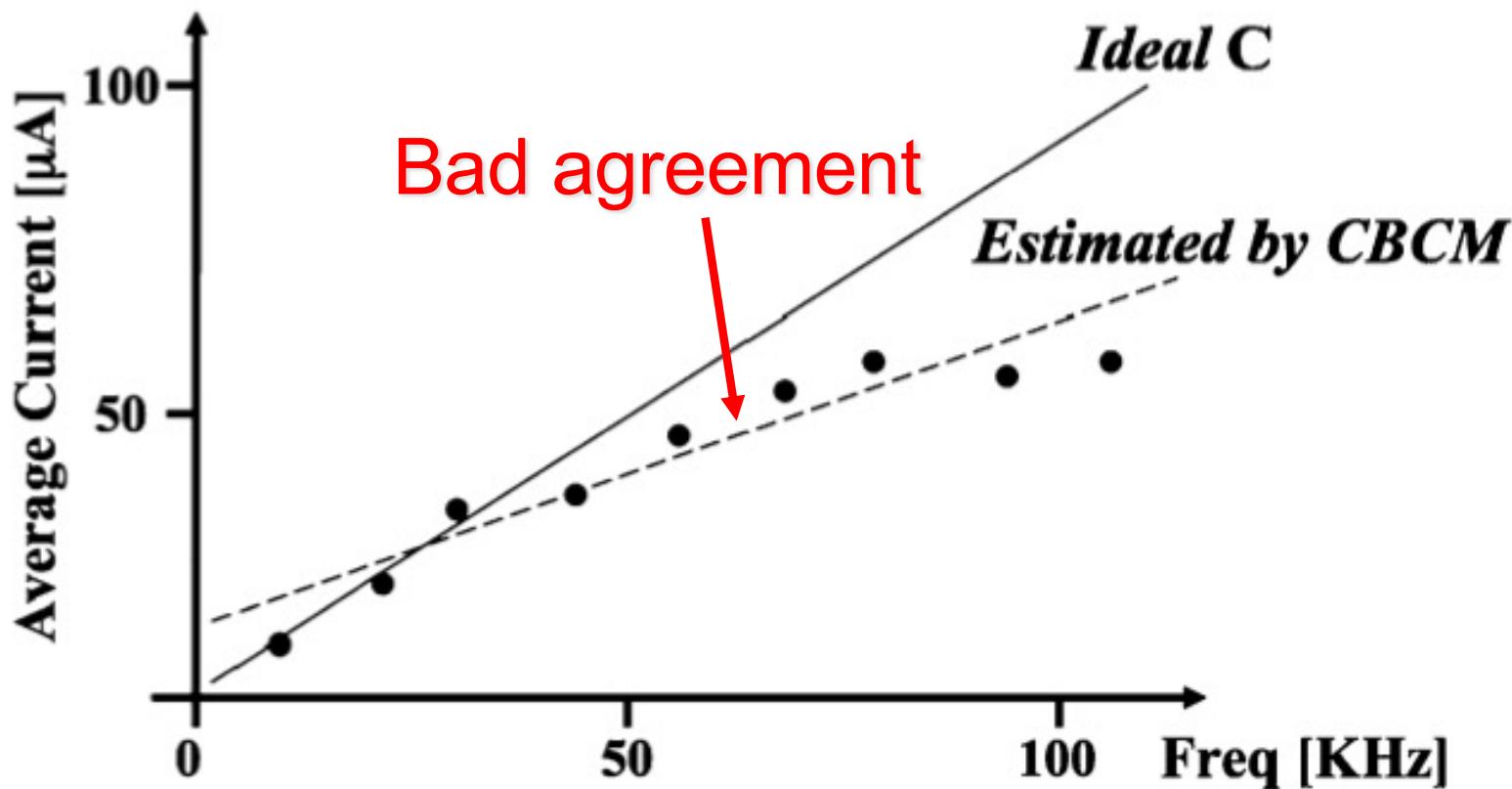

CBCM method on a DNA Layer that  
dependents by the frequency



Q7

# Bad interfaces impact only on the wrong estimation of C-values?

- A. Definitely yes: that's the only effect of bad interfaces
- B. Some times that's the only effect of bad interfaces
- C. Usually also impact the Sensitivity
- D. Usually also impact the LoD**
- E. Usually also impact the reproducibility**

# DNA detection in CBCM mode

Large Standard deviation


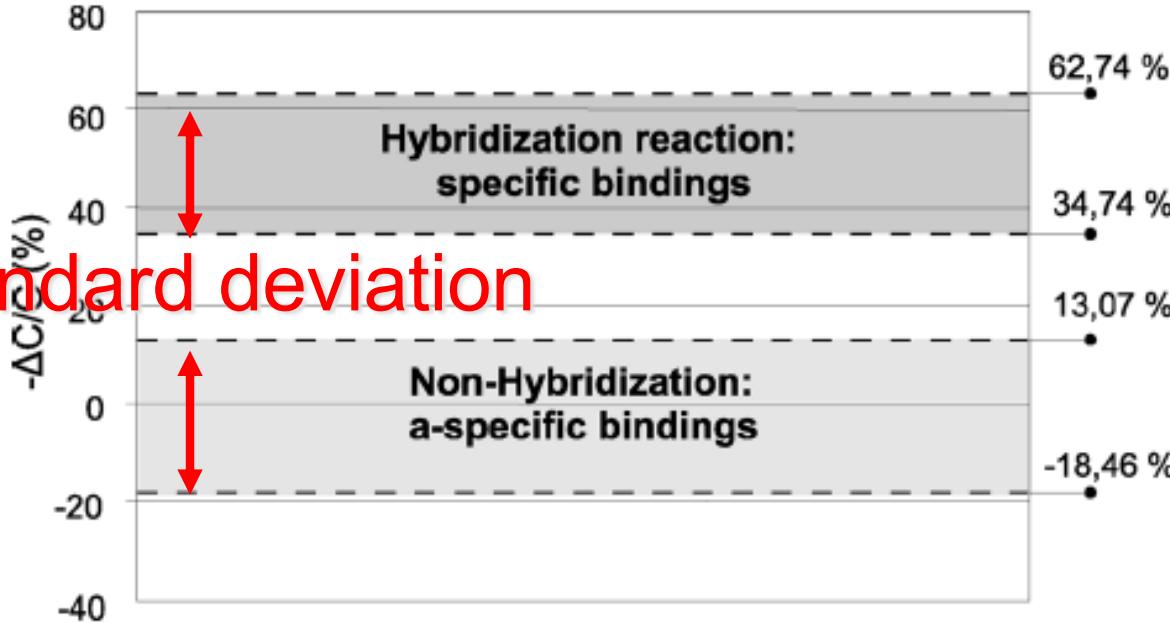


Fig. 12. Capacitance variations due to specific and a-specific bindings (upper and lower bands of measured capacitances, respectively). Positive values indicate capacitance decrease.

The reproducibility on the same chip-spot is not so high: here the problem is on the nano-scale aperture in the probes surfaces


# Current to frequency concept

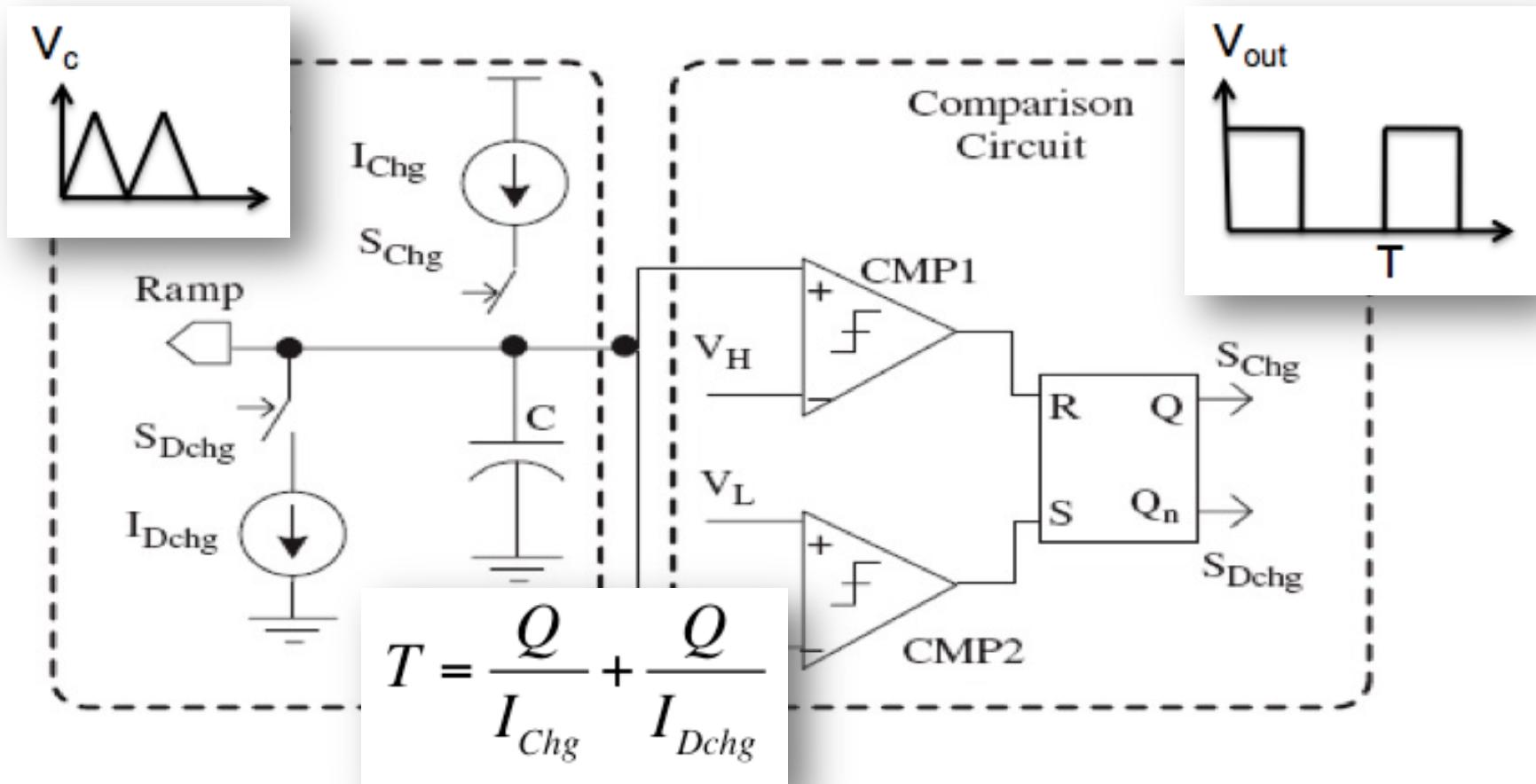


- Two current sources are used to charge and discharge the capacitor:
- The output period depends on both currents
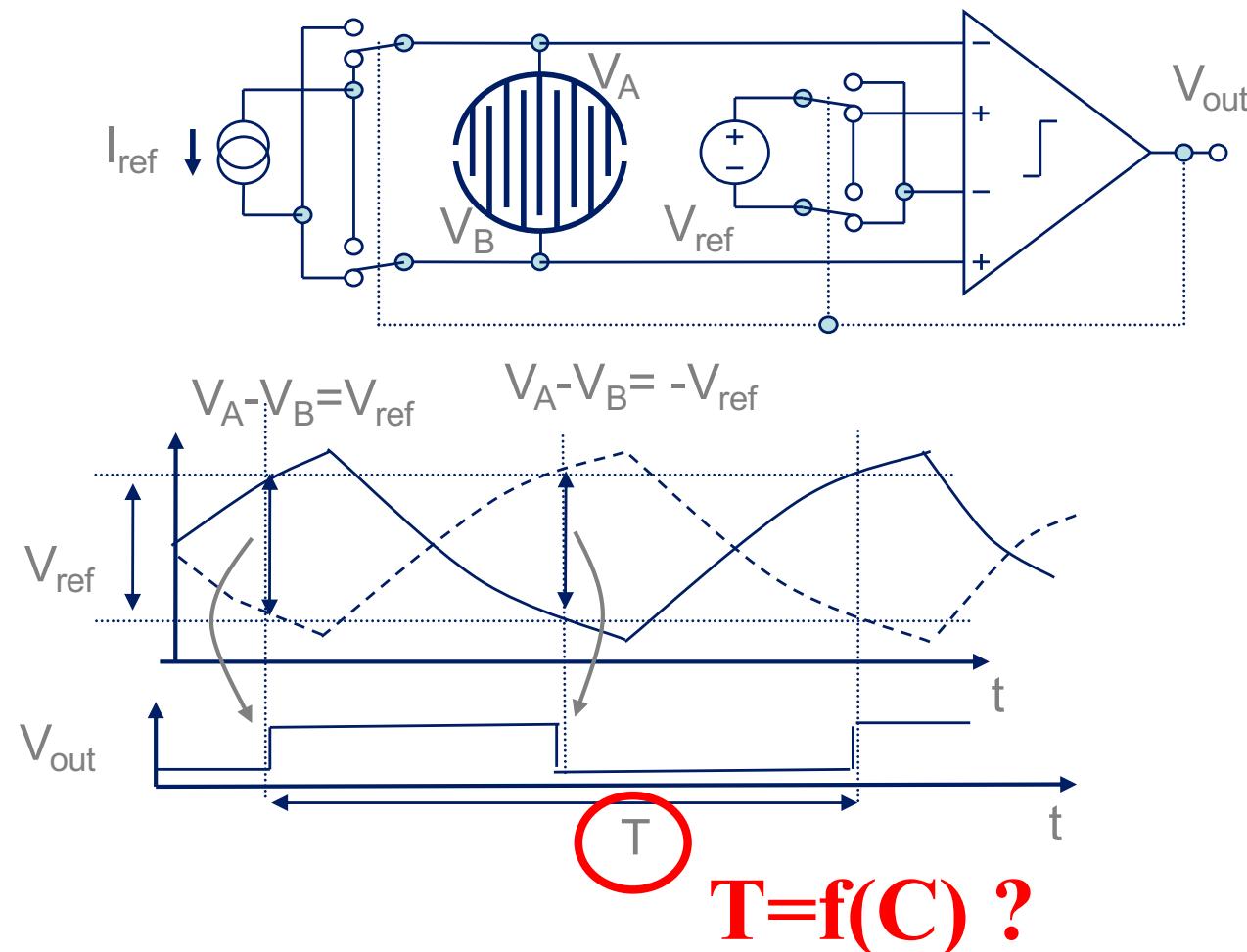
# Frequency to Capacitance Measurement (FTCM)

*Principle: Frequency To Capacitance Mode*


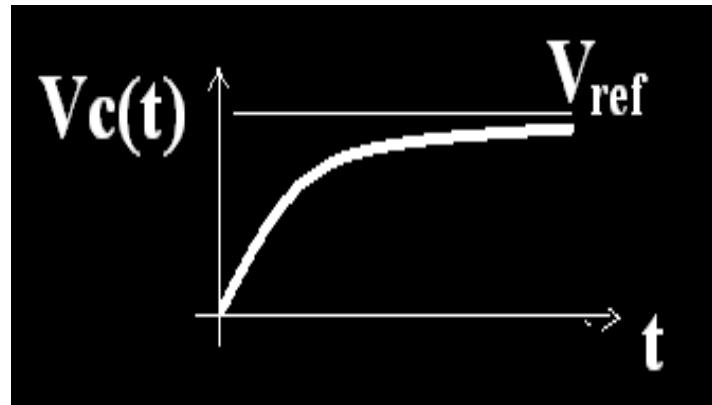
# Frequency to Capacitance Measurement (FTCM)



$$V_c(t) = V_{charge} \left[ 1 - e^{-\frac{t}{RC}} \right]$$

$$V_c\left(\frac{T}{2}\right) = V_{ref} = V_{charge} \left[ 1 - e^{-\frac{T}{2RC}} \right]$$

$$V_c\left(\frac{T}{2}\right) = V_{ref} = RI_{ref} \left[ 1 - e^{-\frac{T}{2RC}} \right]$$

$$\frac{T}{2RC} = -\ln \left[ 1 - \frac{V_{ref}}{RI_{ref}} \right] \quad \rightarrow T = 2RC \ln \left[ 1 - \frac{V_{ref}}{RI_{ref}} \right]^{-1}$$

# The Taylor Series


$$f(x) = f(0) + \left\{ \frac{\partial f(x)}{\partial x} \right\} x + \left\{ \frac{\partial^2 f(x)}{\partial x^2} \right\} x^2 + o(3)$$

$$\frac{1}{1-x} = 1 + \{-(-1)\}x + o(2) \cong 1 + x$$

$$\ln\left[\frac{1}{1-x}\right] = \ln[1 + x + o(2)] \cong \ln[1 + x] = 0 + x + o(2) \cong x$$

Linearity by approximation in the right range of values
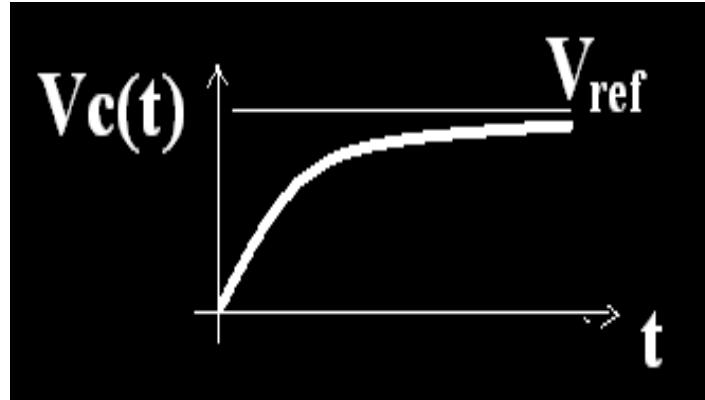
# Frequency to Capacitance Measurement (FTCM)





$$T = 2RC \ln \left[ 1 - \frac{V_{ref}}{RI_{ref}} \right]^{-1}$$

$$T = 2RC \ln \left[ \frac{1}{1 - \frac{V_{ref}}{RI_{ref}}} \right] \cong 2RC \ln \left[ 1 + \frac{V_{ref}}{RI_{ref}} \right] \cong \frac{2CV_{ref}}{I_{ref}}$$

Method for the estimation of the Capacitance

# Frequency to Capacitance Measurement (FTCM)

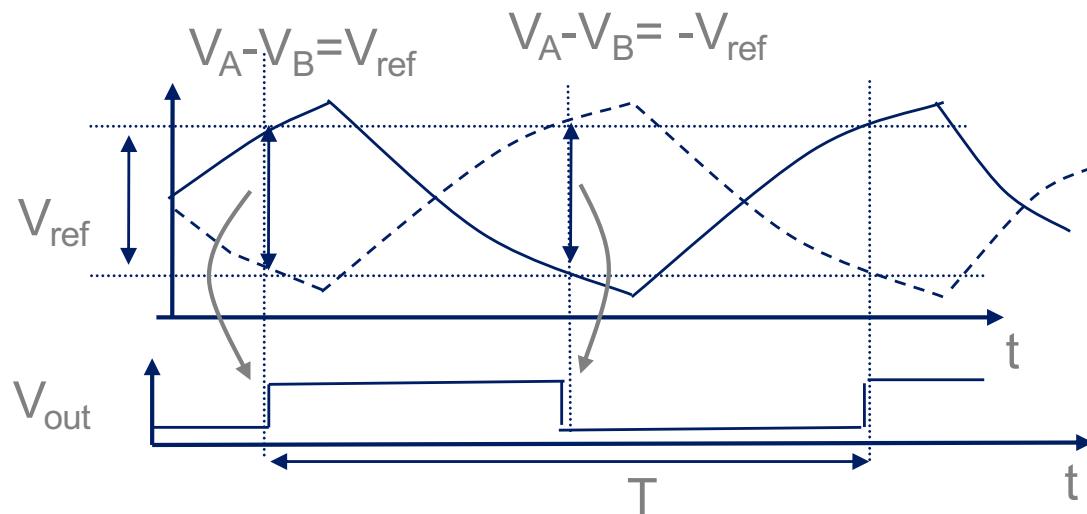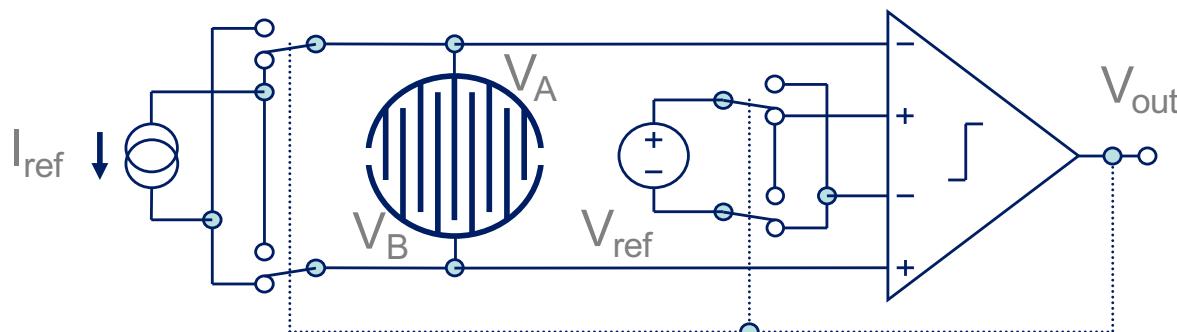**Principle: Frequency To Capacitance Mode**




$$T = 2RC \ln \frac{1}{1 - \frac{V_{REF}}{I_{REF}R}}$$

$V_{REF}/I_{REF}R \rightarrow 0$




$$T = \frac{2 \cdot V_{REF} \cdot C}{I_{REF}}$$

# Electrodes Layout

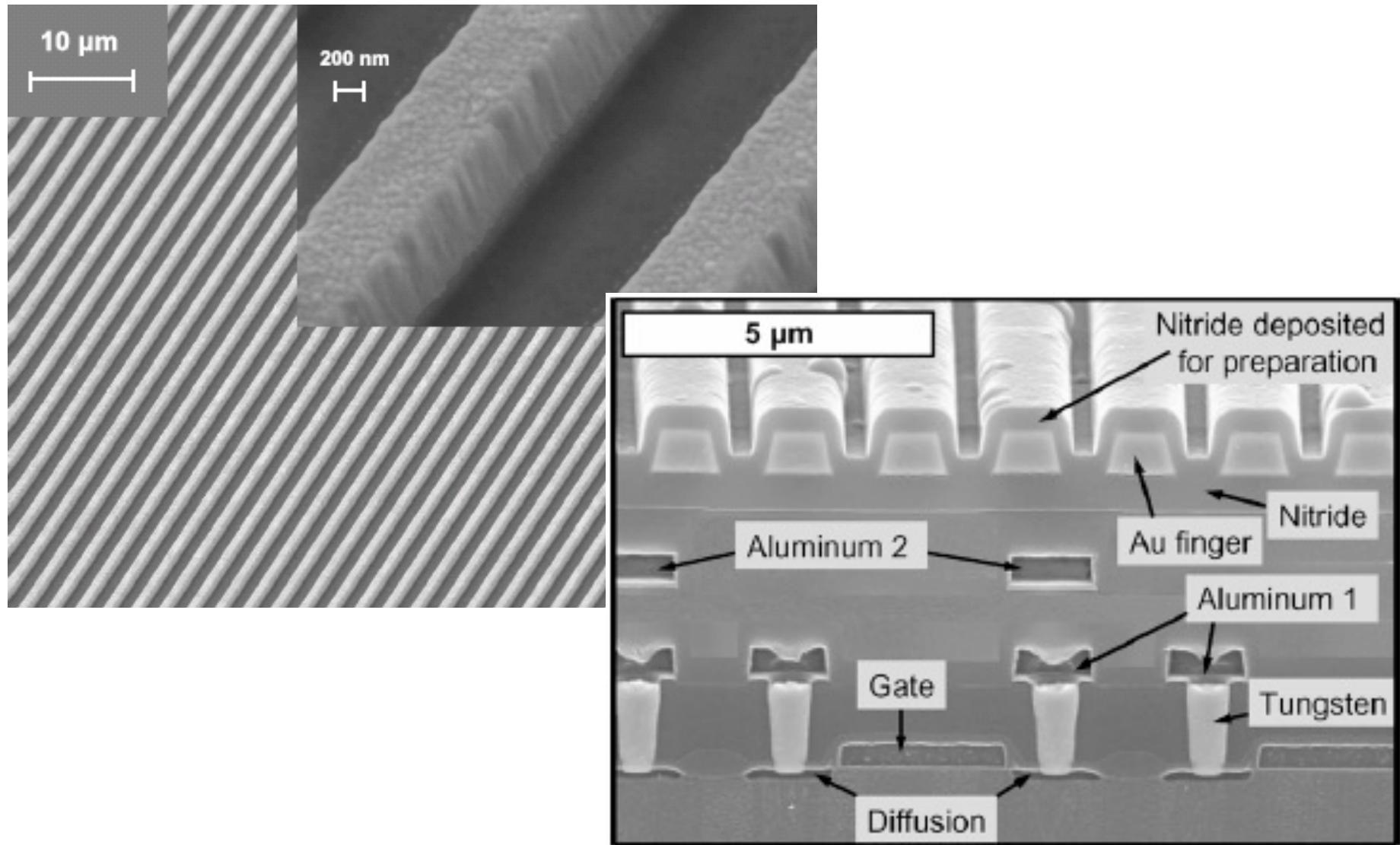

# Chip Architecture (FTCM)

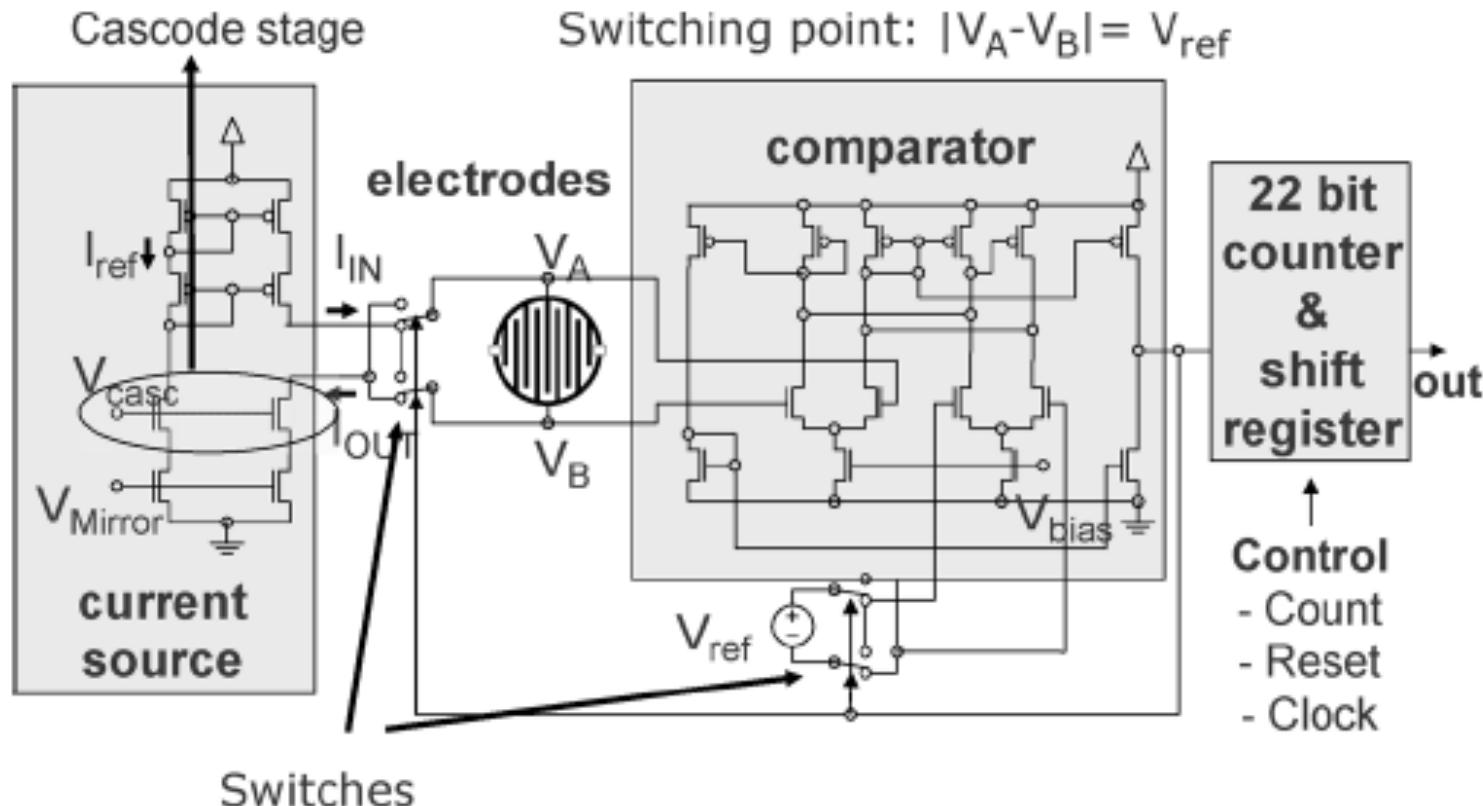

# Measurements Set-up


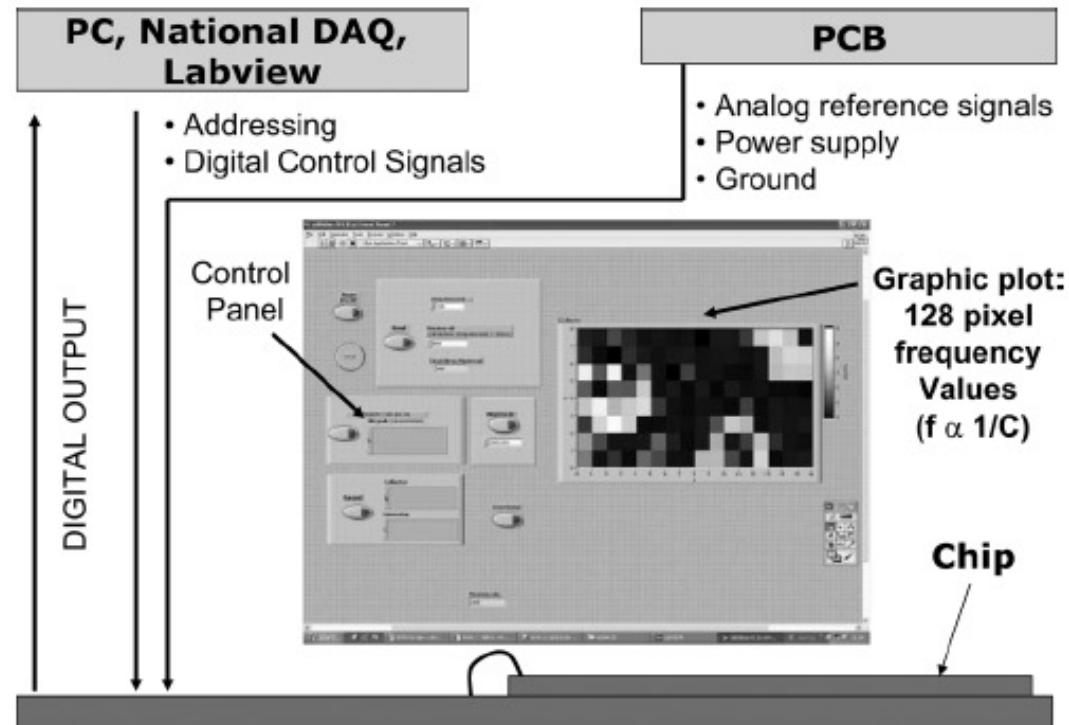


Fig. 9. Schematic representation of the measurement set-up. Voltage reference signals and power supply are generated by circuitry on the PCB. Digital control signals are provided by a PC. The LabView interface manages all the parameters involved in the measurements and shows directly on the screen the measurement results of the whole array.
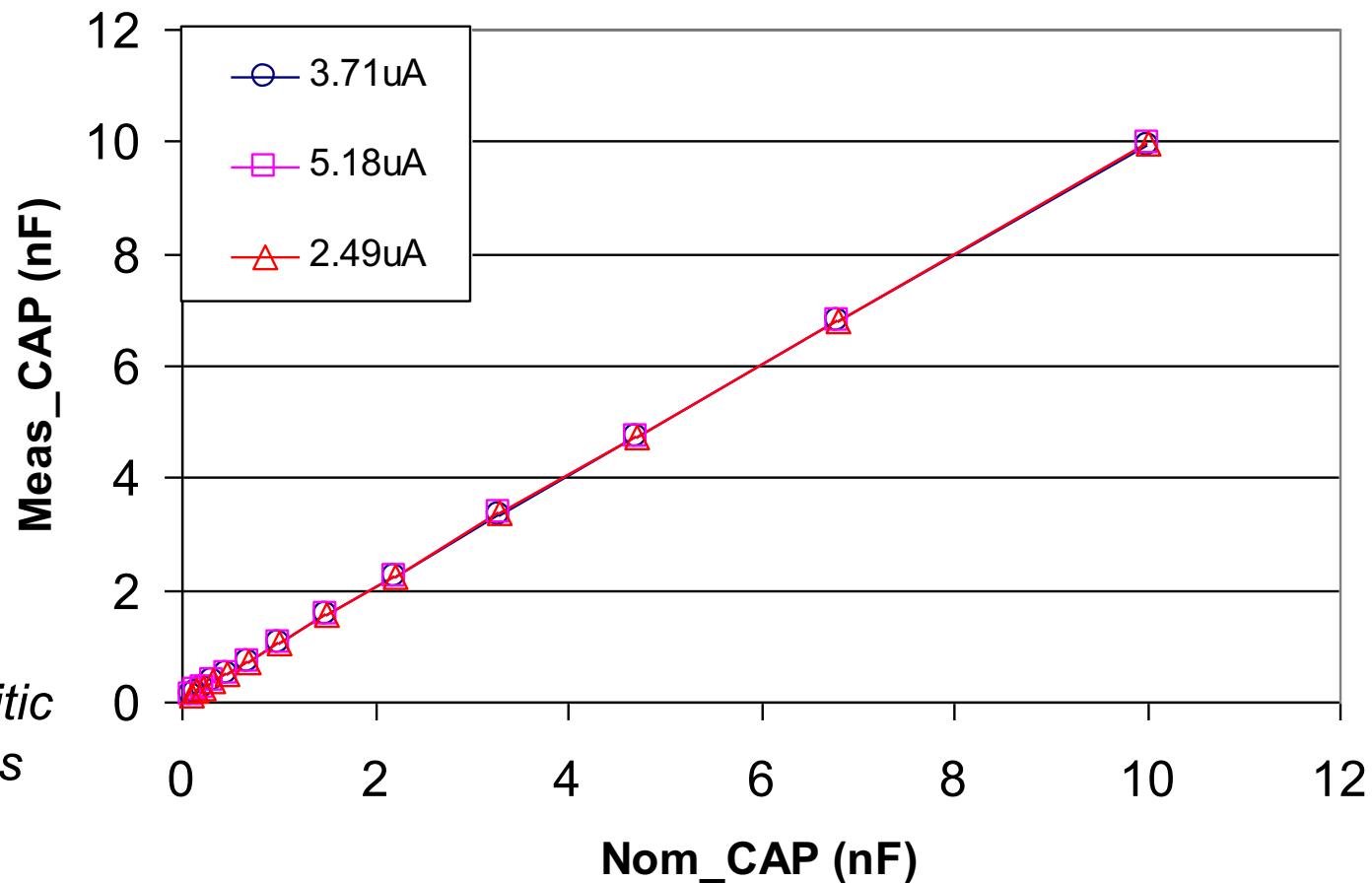
# Validation Test

**Slope = 0.9837**  
**Intercept = 62 pF**  
 $\sigma < 0.3 \%$

*Offset is due to parasitic capacitances of cables*



A test structure has been implemented on chip beside the array to characterize the measurement circuit with discrete test capacitances (10 pF - 10 nF)



Q8

## Does the FTCM returns good C-value estimations also on bad interfaces?

- A. Definitely not, if C changes with the frequency
- B. Not really, since C might change with the frequency
- C. Not always, since  $R_P$  might be extremely small**
- D. Some times, since  $R_P$  is usually extremely large
- E. Yes, of course!

# Probes property on FTCM mode

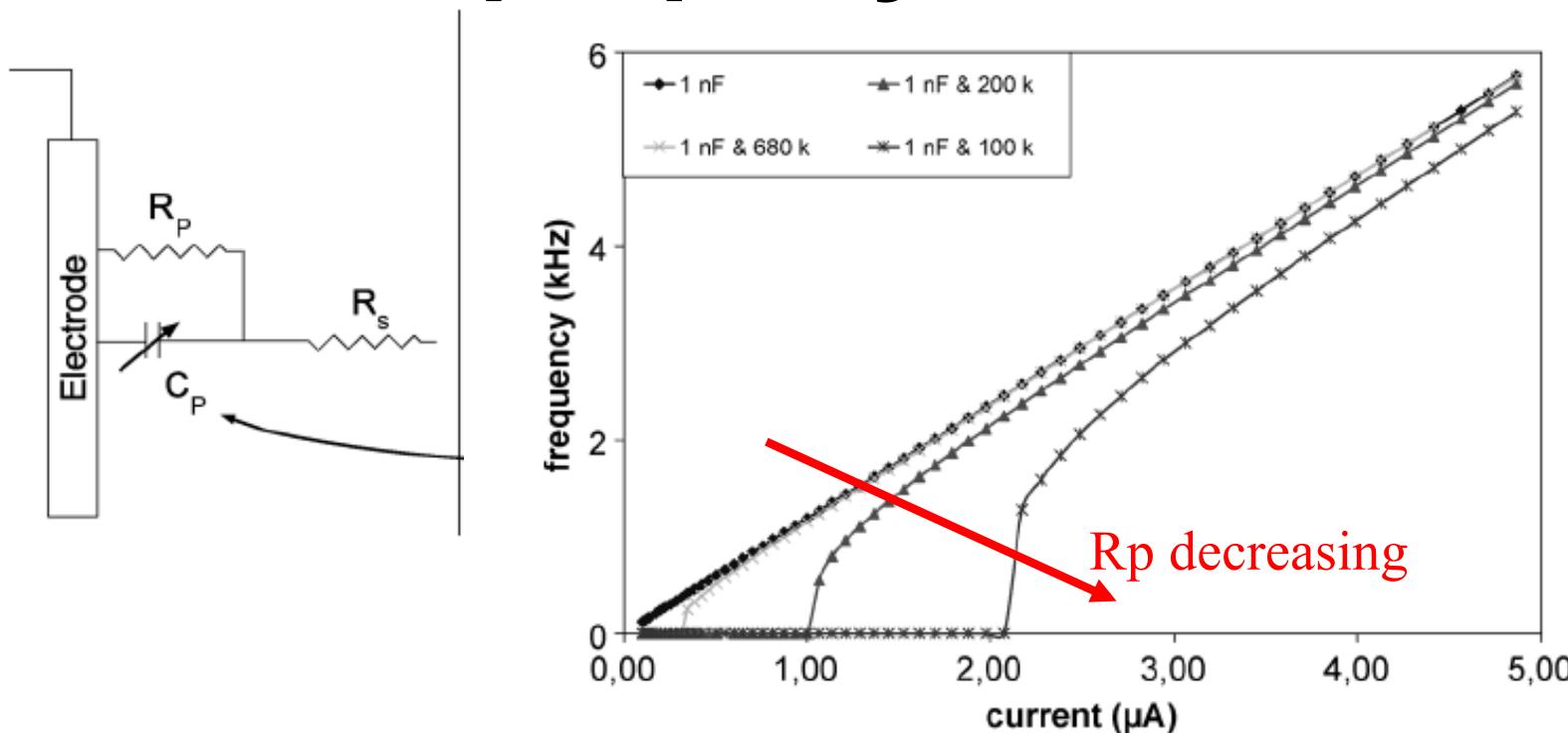


Fig. 12. Frequency versus reference current showing that a significant influence of the parallel resistance on the measurement result occurs only at low current values and at  $R_p$  values lower than  $680\text{ k}\Omega$ .

The linearity between the current and the measured frequency is lost at low current if the CMOS/Bio interface is not a perfect capacitor




Q9

# May we obtain ideal interfaces for FTCM estimations?

- A. Impossible,  $R_P$  always is too small
- B. Not easy, since  $R_P$  might change in frequency
- C.** May be, in case of some good self-assembly
- D.** Some times, by assuring large  $R_P$
- E. Some times, by assuring small  $R_P$

# Liquid Measurement set-up

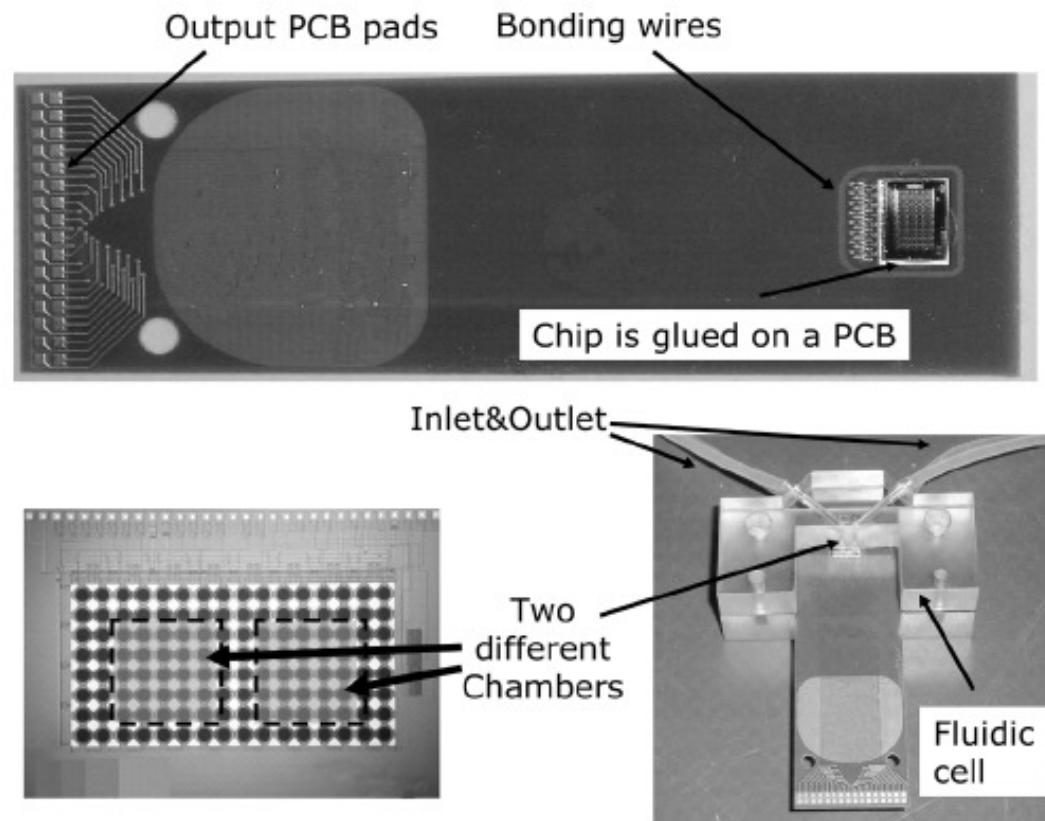

# DNA detection in FTCM mode

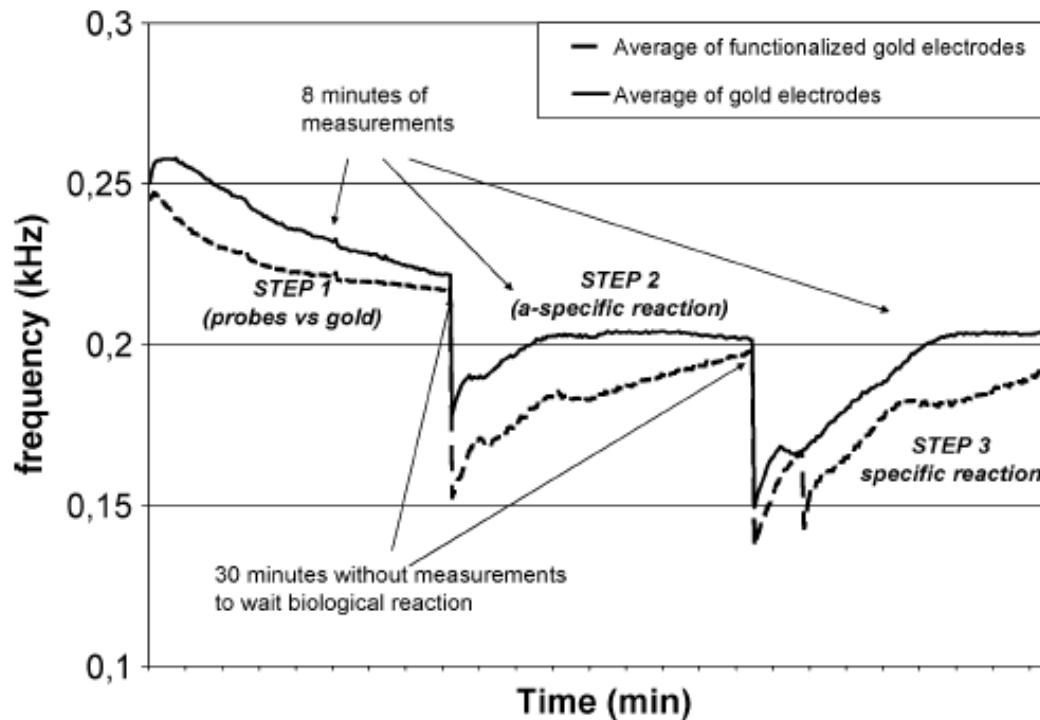


Fig. 13. Frequency changes of the average of reference electrodes (continuous line), and the average of functionalized electrodes (dashed line) show a larger gap after DNA hybridization step considering the stable value reached at the end of the transient.

Time stability on the single chip-spot is poor due to nano-scale aperture in the probes surfaces

# DNA detection in FTCM mode

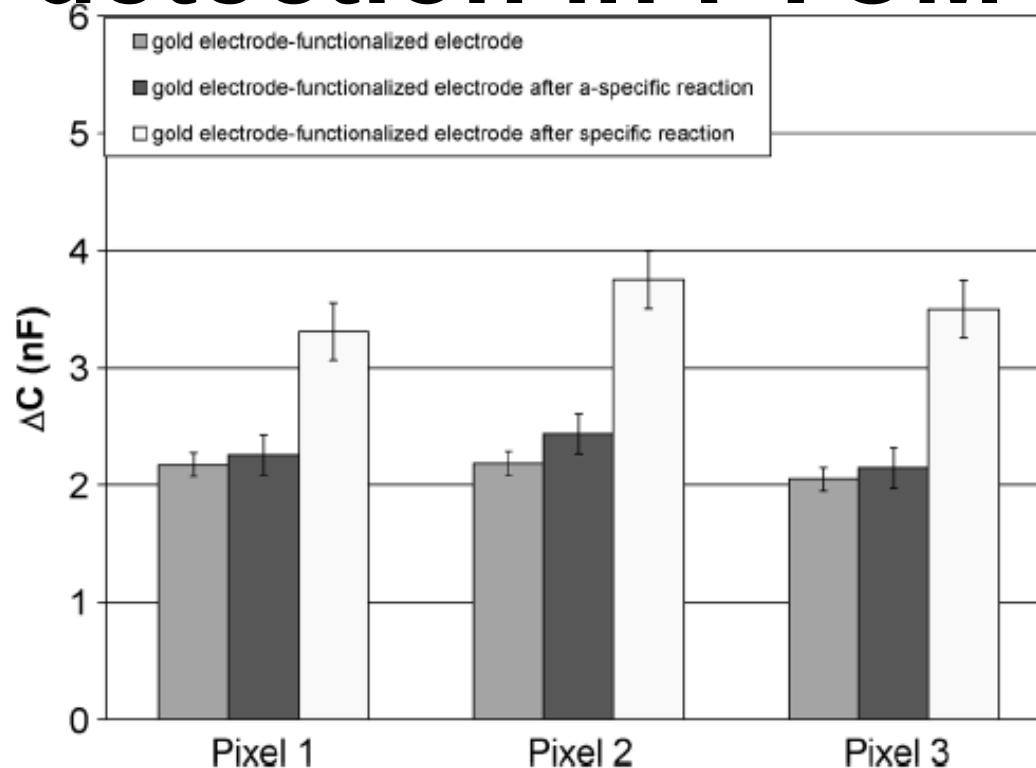


Fig. 14. Typical variations for several pixels among functionalized electrodes and the average value of reference gold electrodes. Capability to distinguish between specific and nonspecific binding is shown for each pixel.

In chip spot-by-spot reproducibility is improved also due to better cleaning of the spot gold electrodes




Q10

# How we may detect DNA with Amperometric Methods?

- A. Impossible,  
Amperometry works  
only with enzymes
- B. Not easy, since  
Amperometry works  
mainly with enzymes
- C. May be by using  
DNA-Polymerase
- D. May be by using  
electrochemical  
labels
- E. May be by using  
DNA-Helicase


# Amperometric Detection of DNA

Figure by Frey et al, IEEE ISCAS 2015

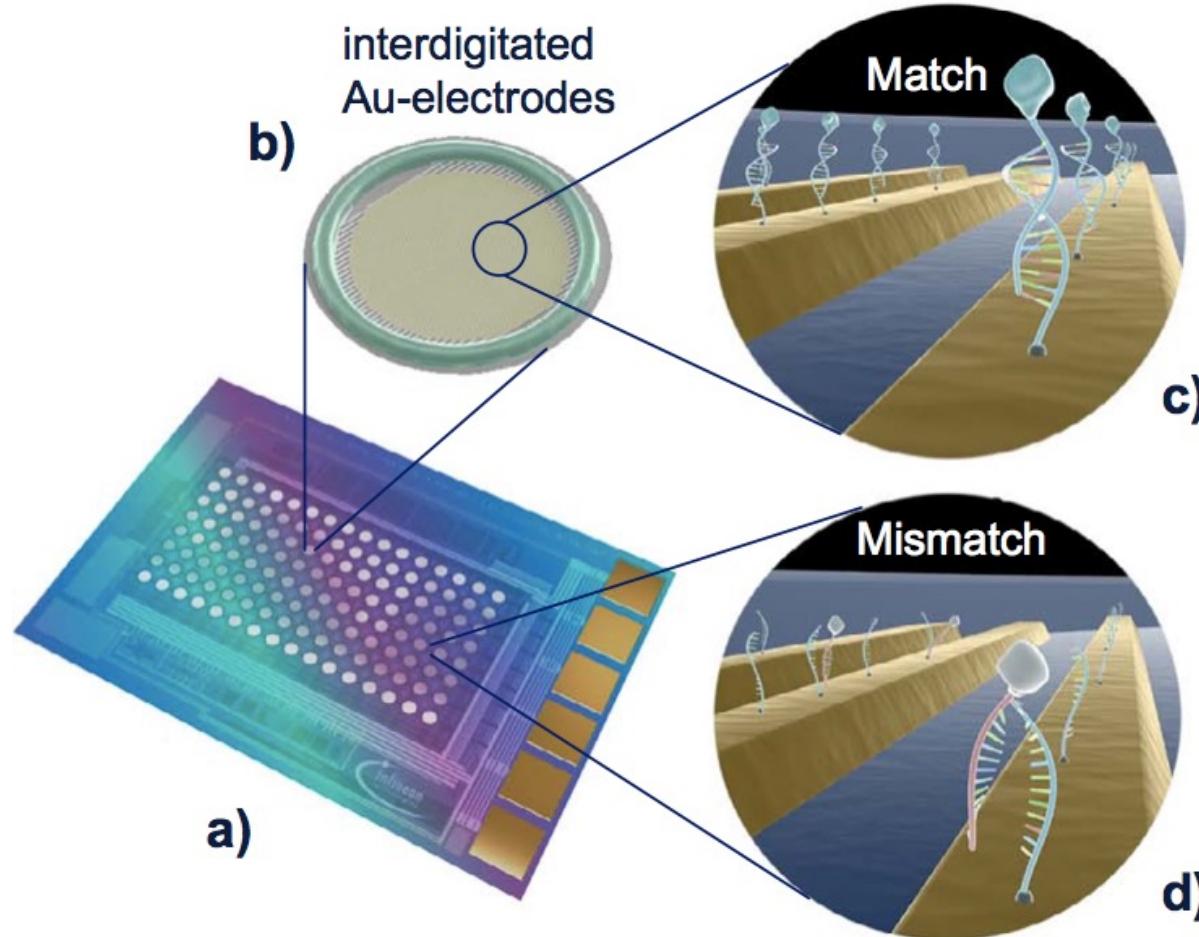



Electrochemical labels might be used to detect DNA

# Amperometric Detection of DNA

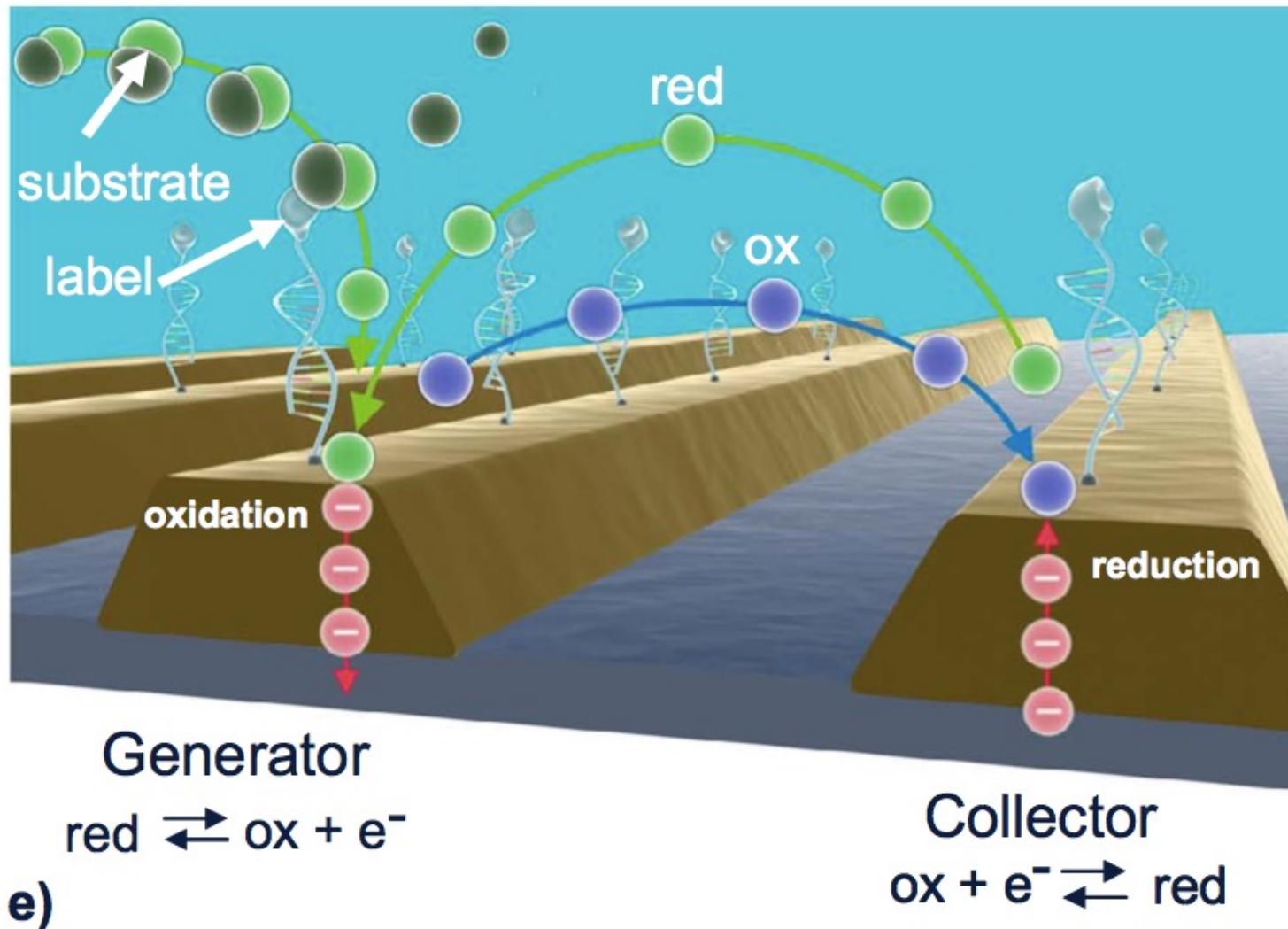

Redox species can be then measured at the electrodes

# Amperometric Detection Principle

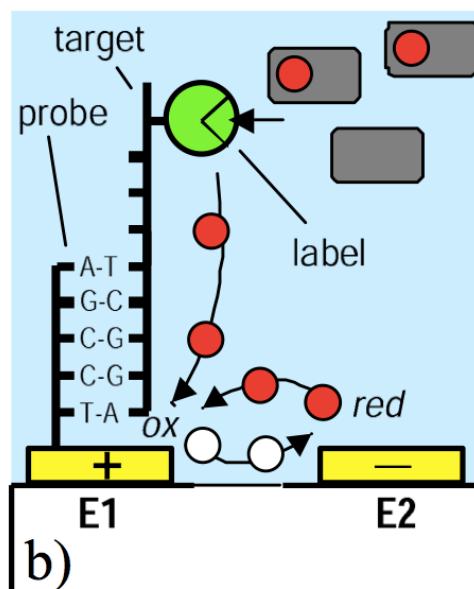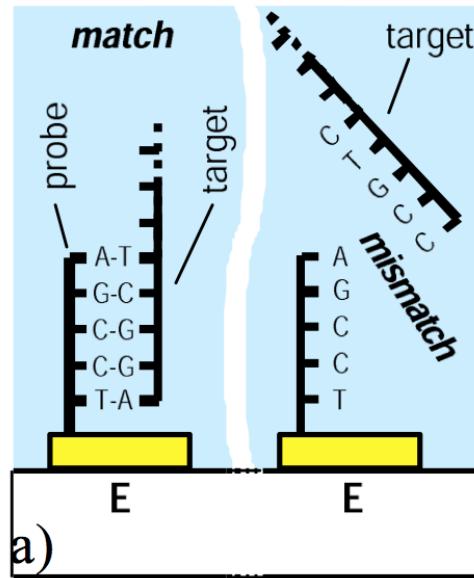


## How it works:

- ✓ First, single stranded DNA molecules (about 20 bases) are immobilized by using a spotting machine on top of the gold electrodes due to gold-thiol coupling.
- ✓ Then, the chip is flooded with an analyte containing labeled target DNA ss: hybridization takes place in case of matching.
- ✓ A suitable substrate is applied to the buffer solution and it is enzymatically cleaved by the label.
- ✓ Resulting species starts an electrochemical redox process at the electrodes.
- ✓ Faradaic currents generated by the related redox process is detected and transduces DNA hybridization


# Enzymatically cleavage & redox process

## a) Process at the label

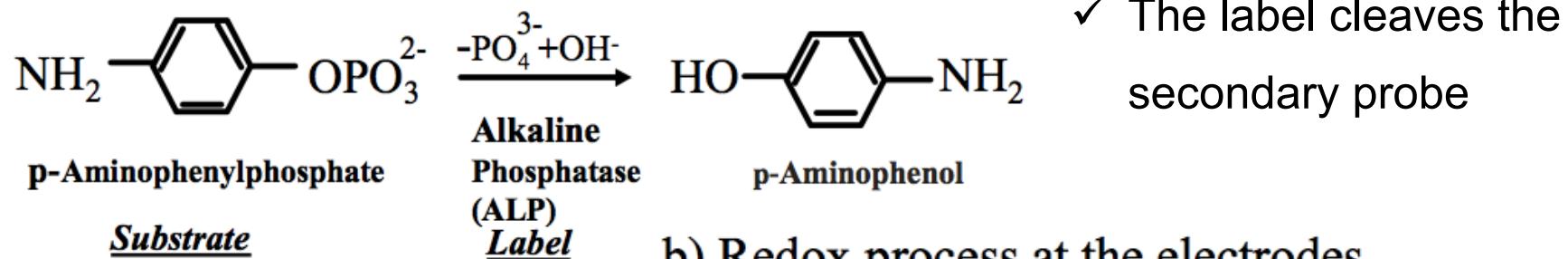


✓ The product of the cleavage is generating an oxidation process at the anode and, once oxidized, a reduction at the cathode

## b) Redox process at the electrodes


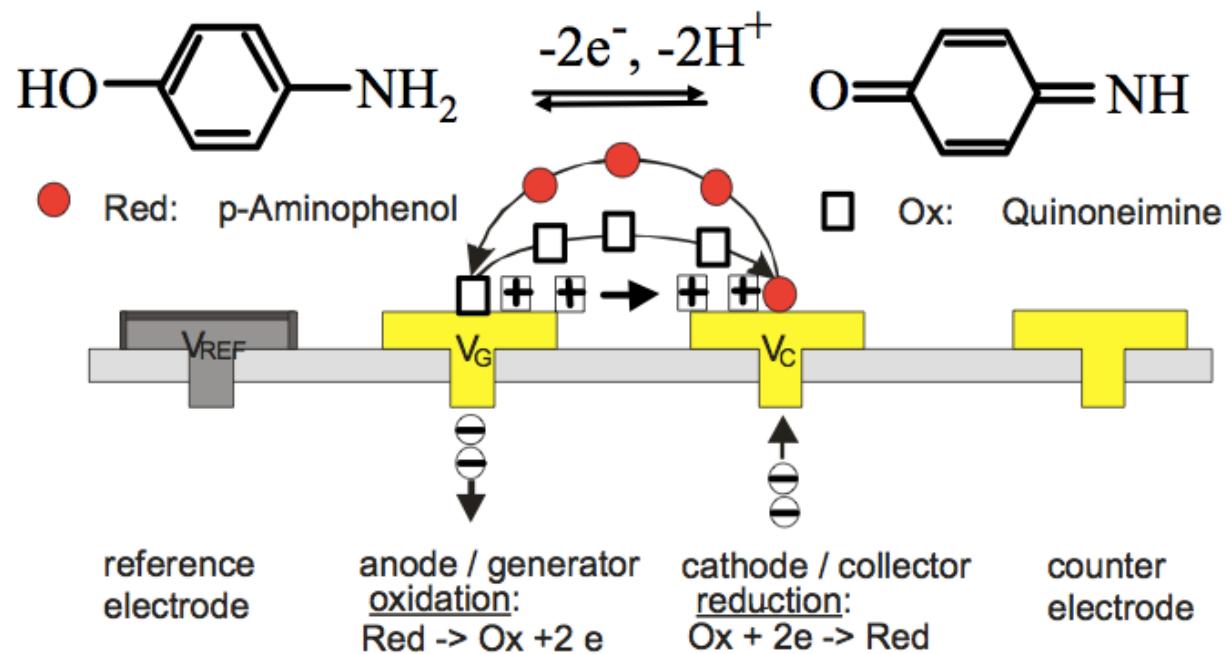


# The Electrochemical Cell

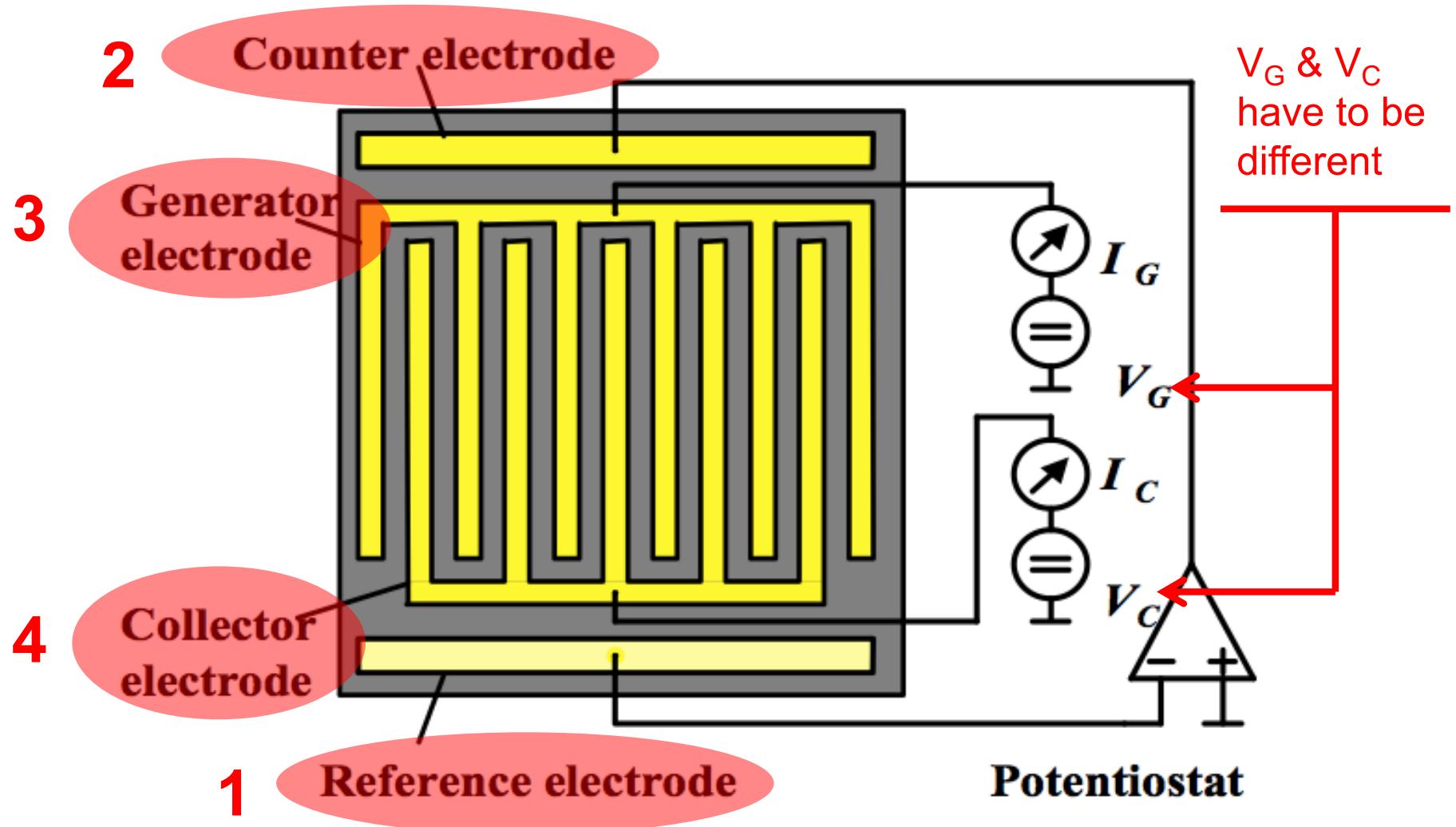

A 4-electrode Electrochemical Cell is here required

# Cyclic Voltammetry

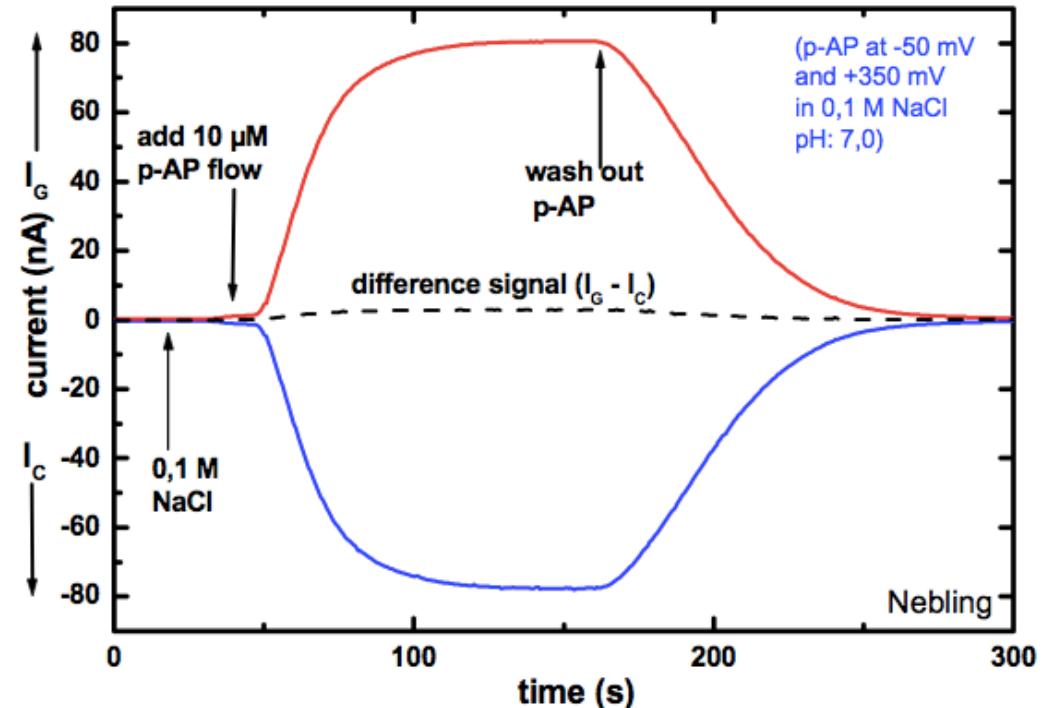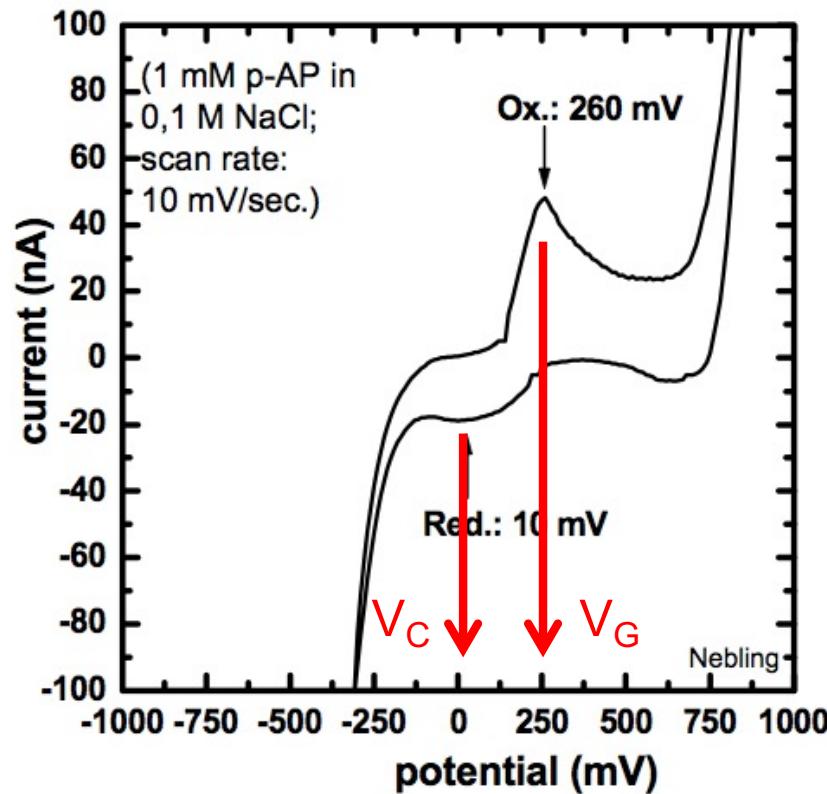


- ✓ Typical Cyclic Voltammetry acquired with 3-electrode cell

- ✓ Chronoamperometry acquired with 4-electrode cell

Simultaneous acquisition of Ox/Red current with 4-el

# Match/Mismatch DNA Hybridization

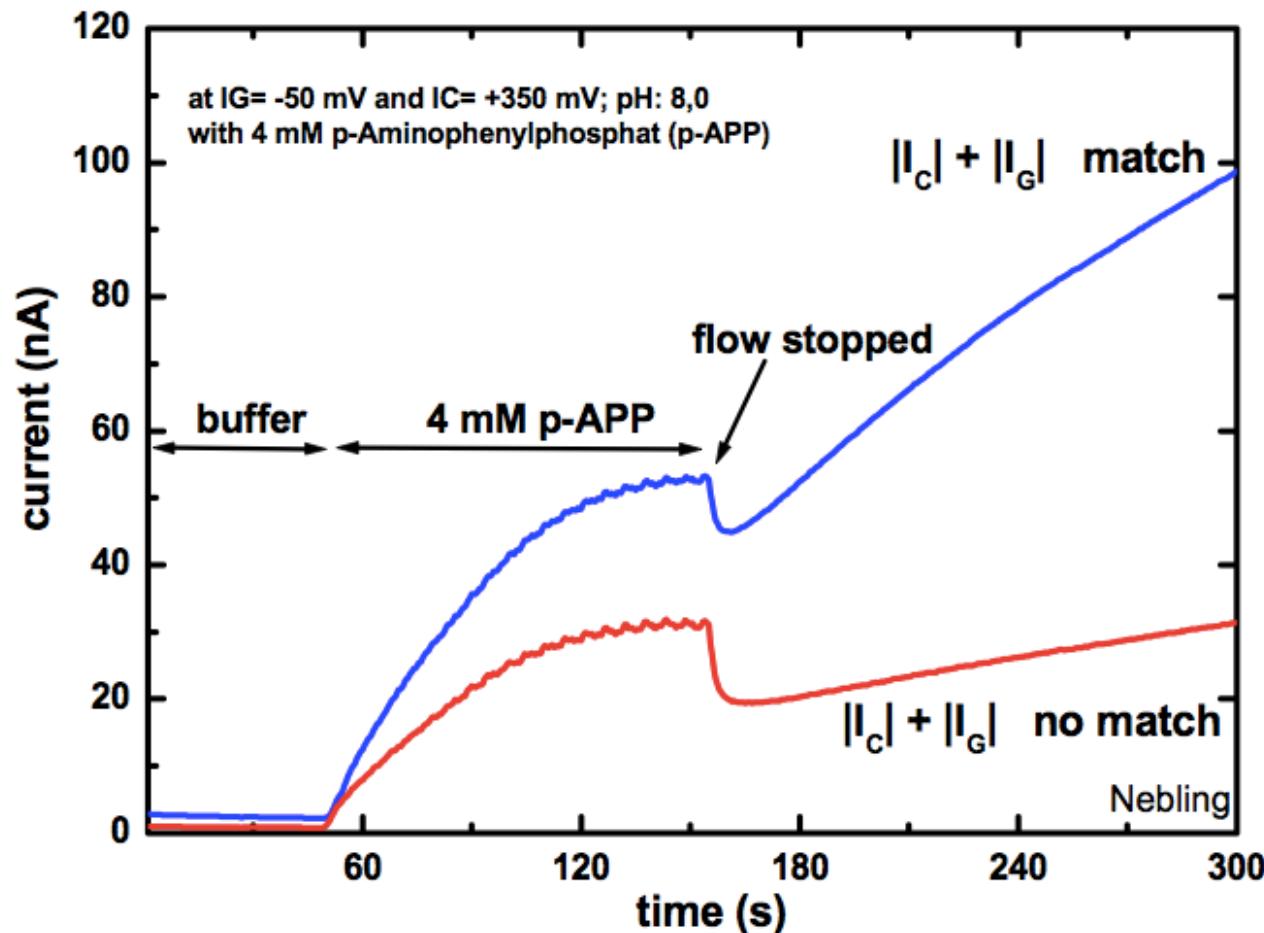


Successful detection of the matching sequence by significant signal by non-matching ones too

# Gibbs free energy for Match/Mismatch

duplex	<i>Experimental</i> $\Delta G$ [kJ/mol]
GGTTATTGG CCAATAACC	-26.8
GGTTCTTGG CCAAGAACCC	-31.4
GGTTTTGG CCAAAAACC	-29.5
GGTTATTGG CCAAAAACC	-12.0
GGTTCTTGG CCAATAACC	-12.4
GGTTTTGG CCAAGAACCC <small>(c) S. Carrara</small>	-17.5


Roughly  
50% less

# Match/Mismatch DNA Hybridization

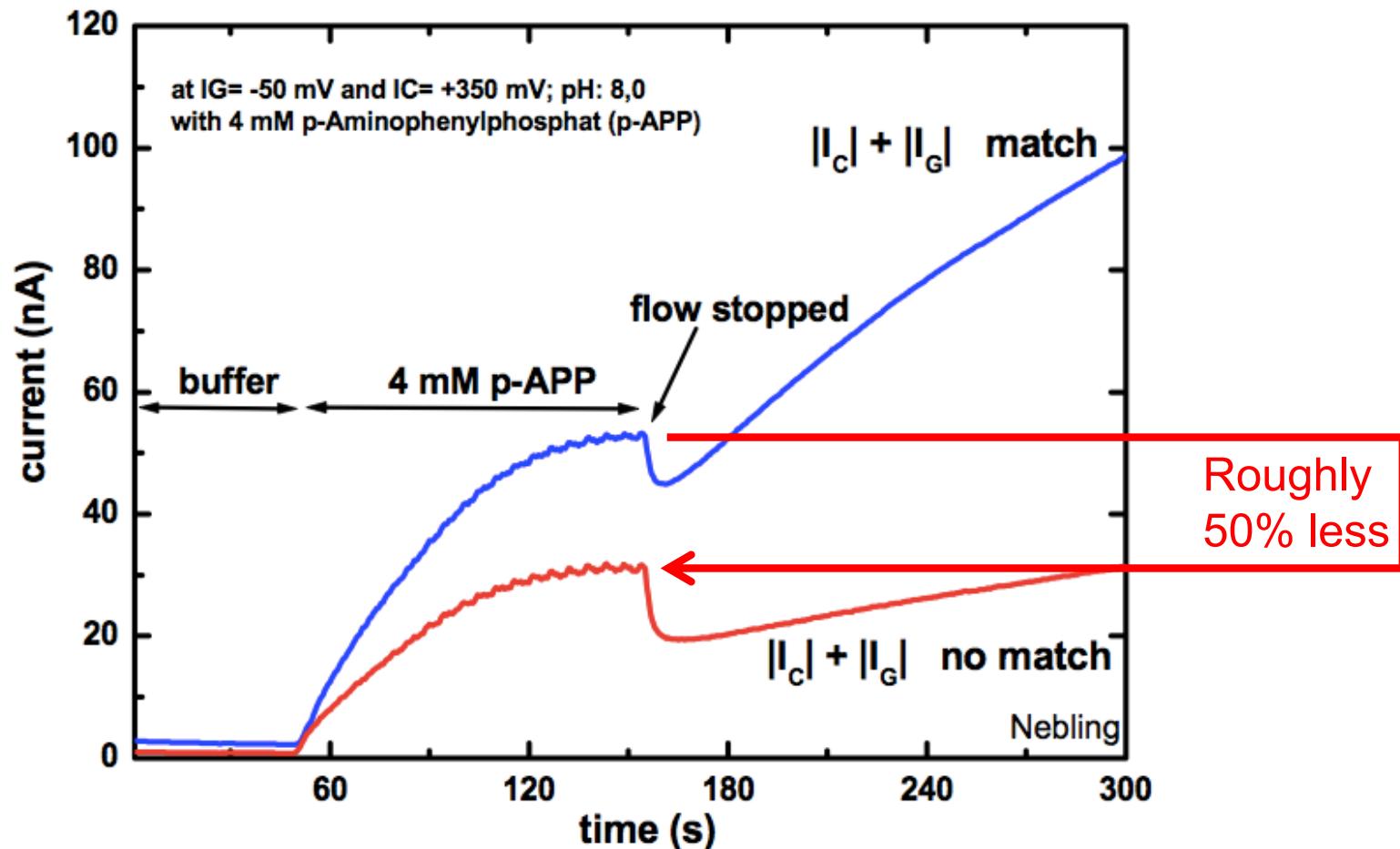


Successful detection of the matching sequences  
but significant signal by non-matching too

# Current CMOS Readout

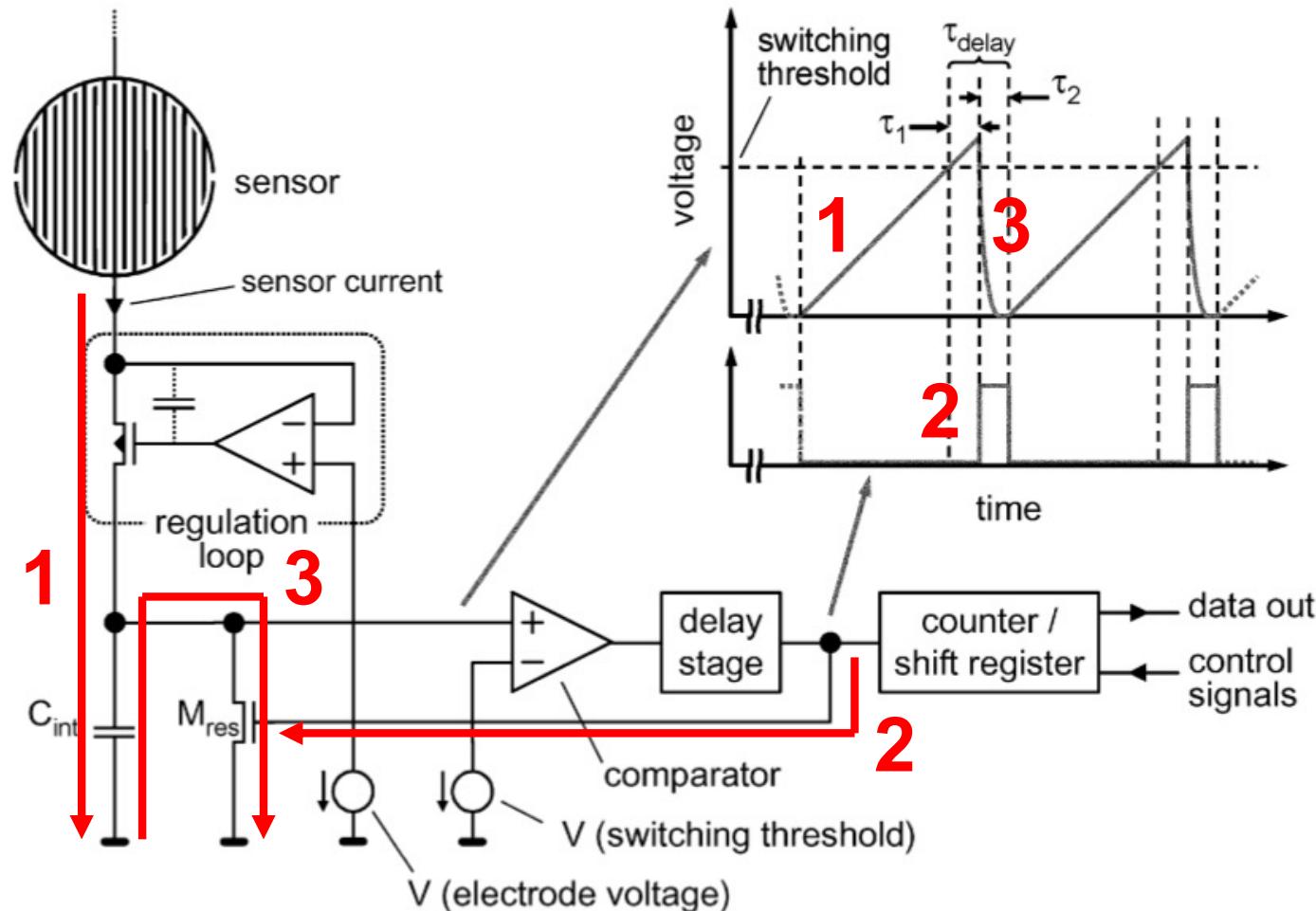


Frequency-To-Current Conversion (FTCC)  
method is used here too

# Current CMOS Readout

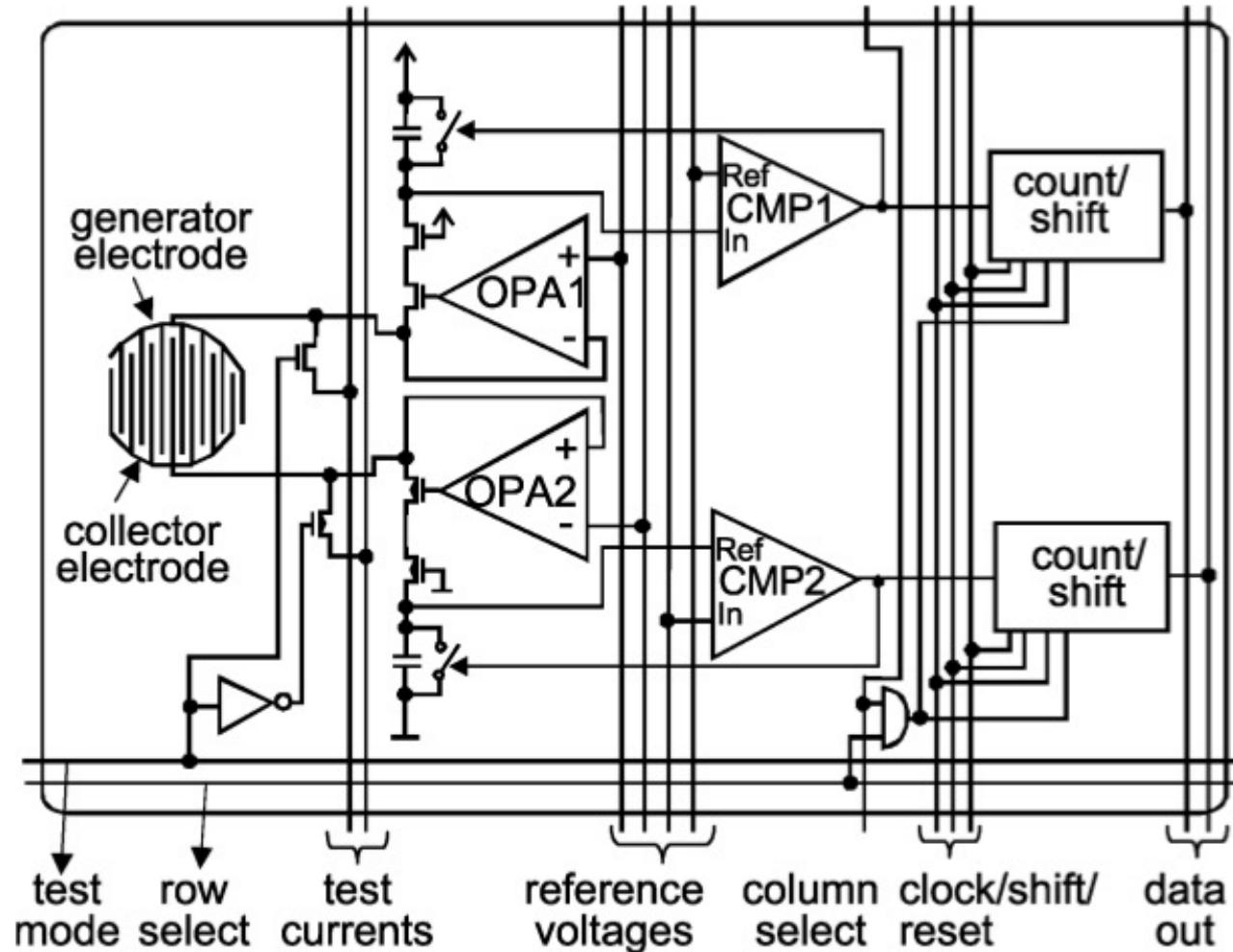


Sensor-site circuit architecture with digital output

# Array Architecture

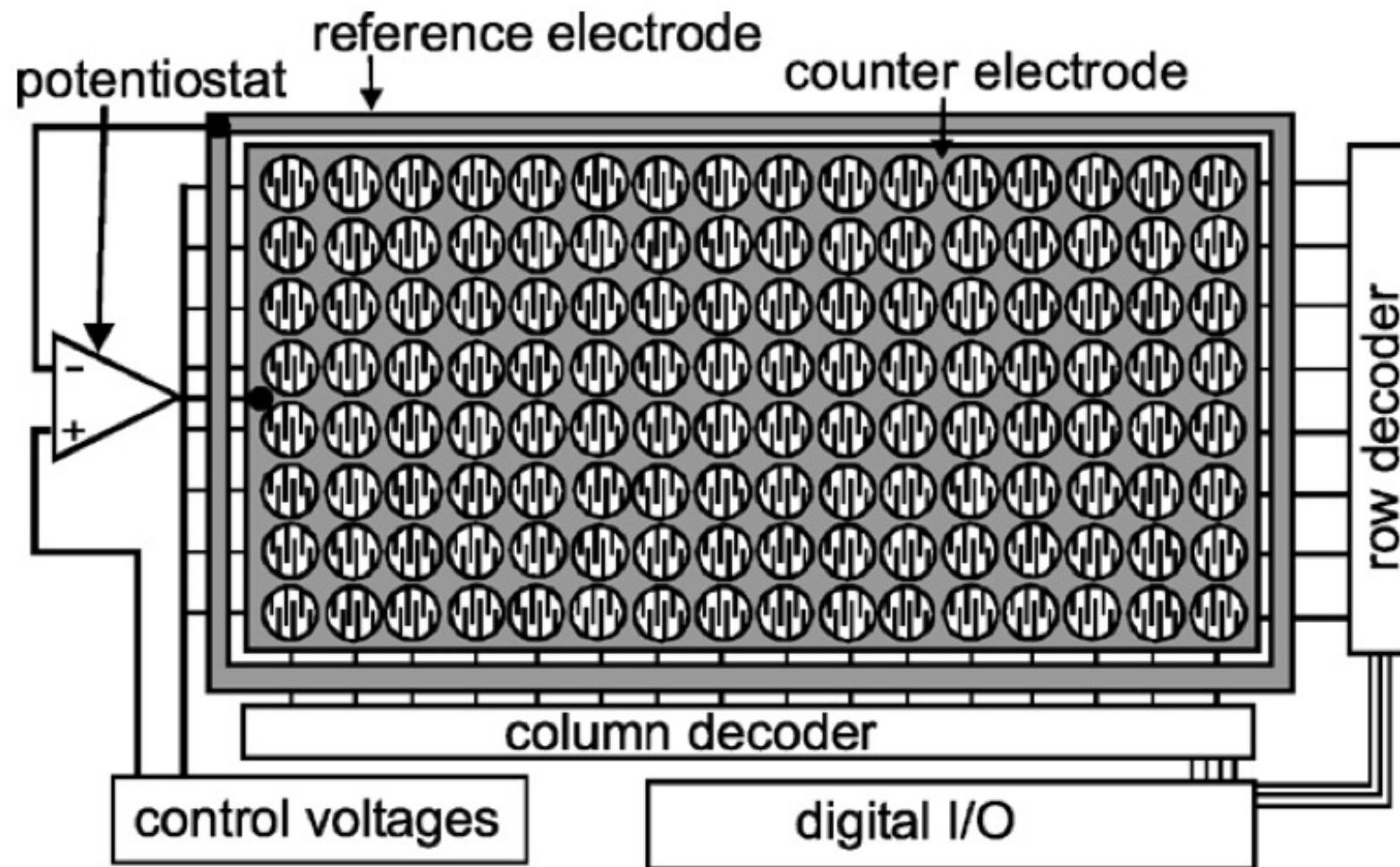

Whole Chip architecture including Row/Column decoders

# The realized IC

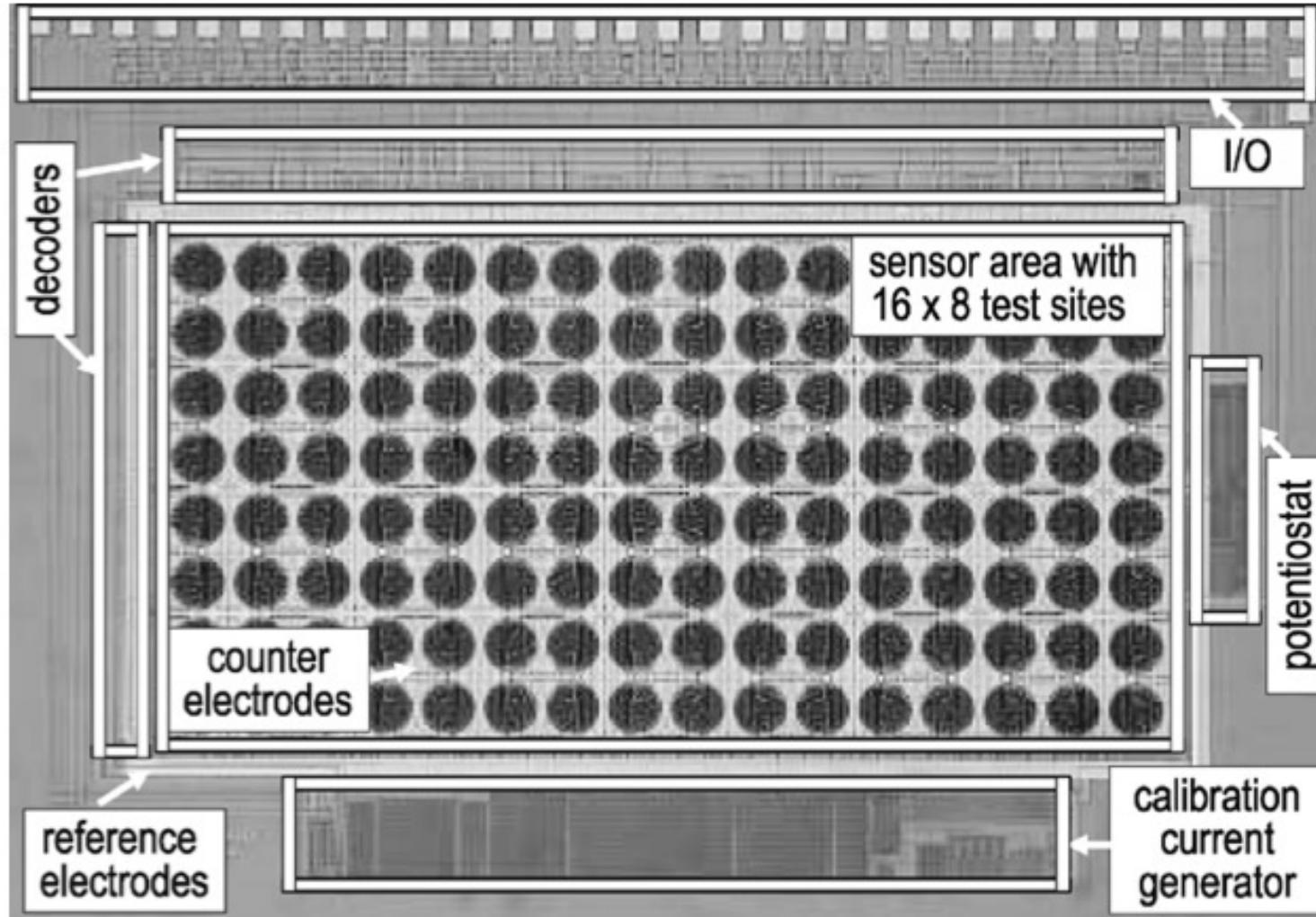

Chip microphotograph. Total dimensions are  $6.4 \times 4.5 \text{ mm}^2$ .

# Exposed IC-Die Electrodes



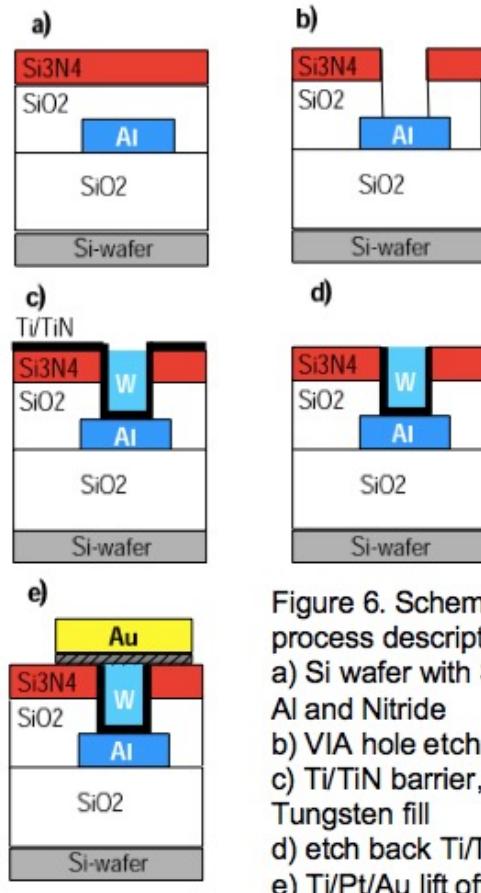


Figure 6. Schematic process description  
a) Si wafer with  $\text{SiO}_2$ , Al and Nitride  
b) VIA hole etch  
c) Ti/TiN barrier, Tungsten fill  
d) etch back Ti/TiN  
e) Ti/Pt/Au lift off

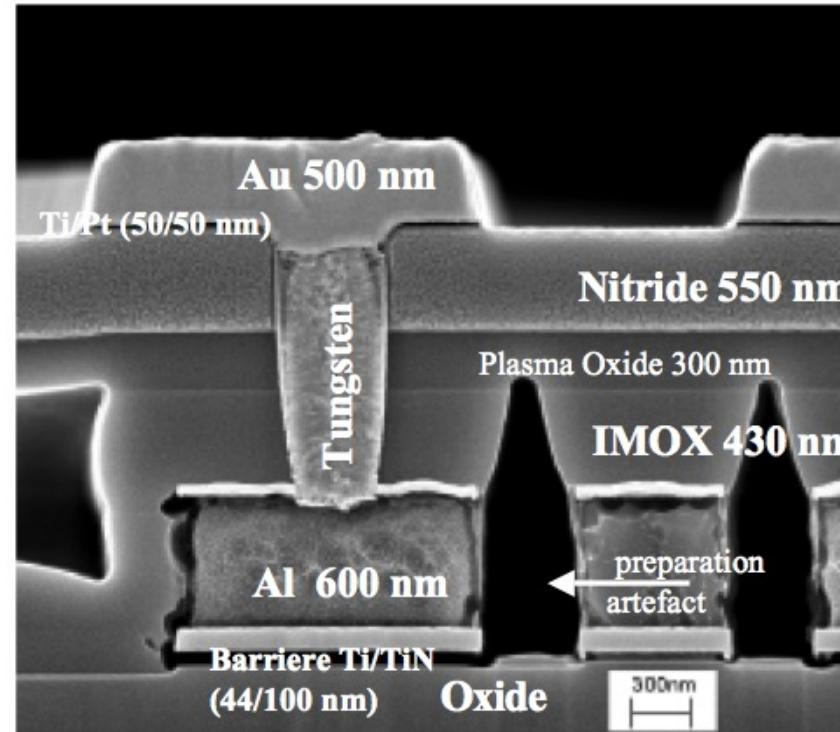


Electrochemical electrodes are created on top of the last CMOS metal Al layer

# Frequency Readout

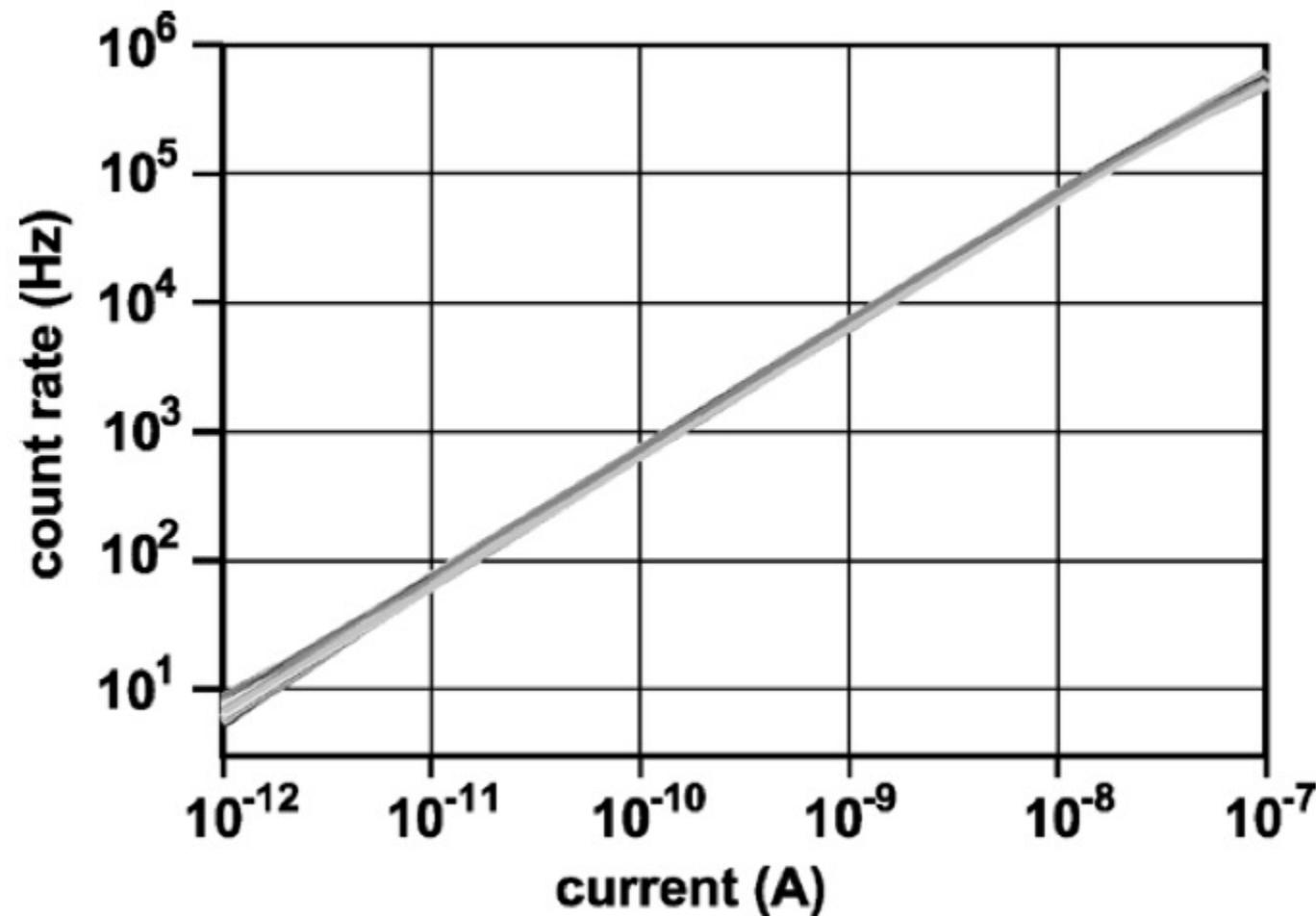

Measured count rate of all 128 DNA sensors


# Test Measures

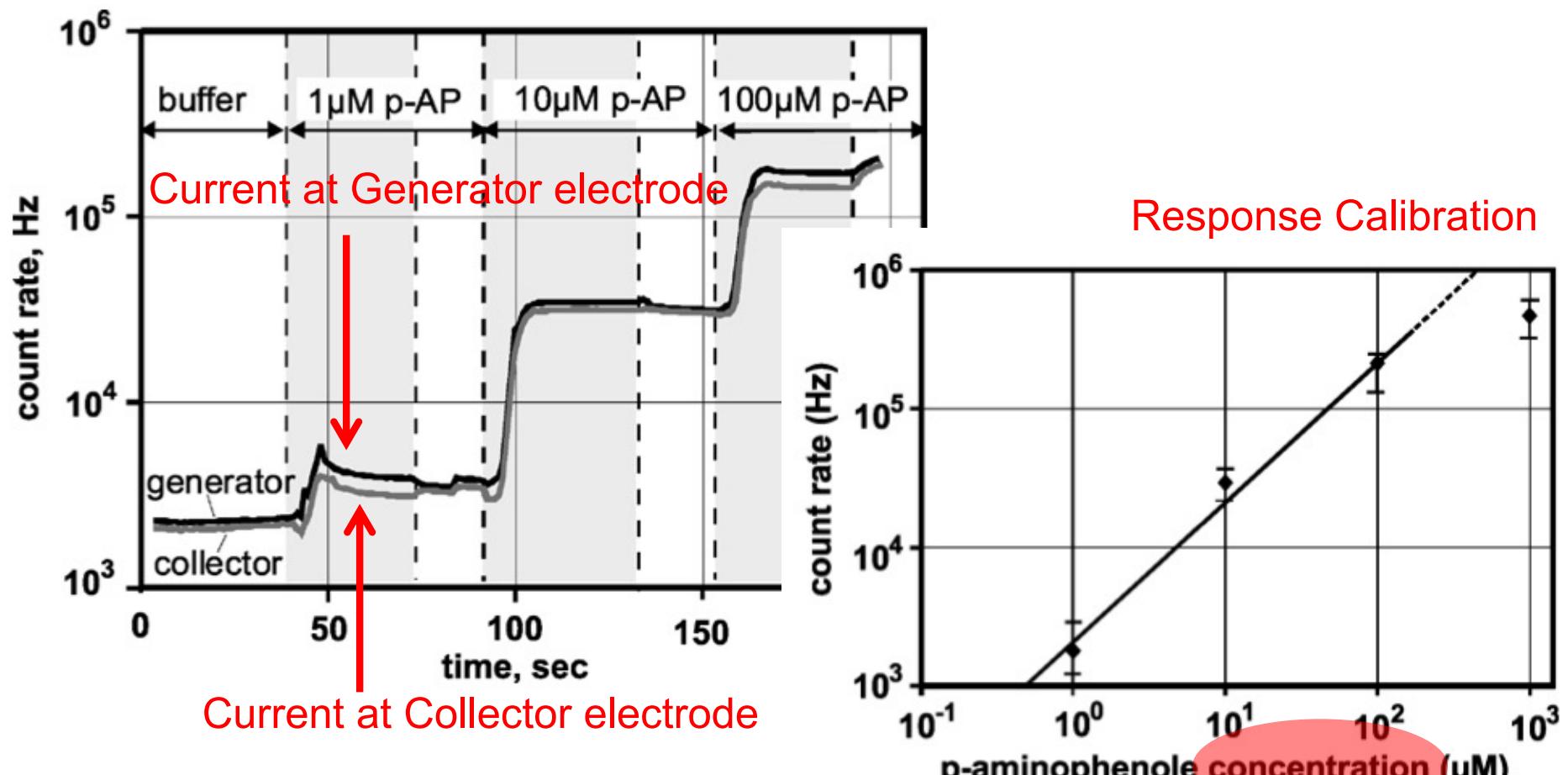

Concentration of the secondary probe, not of the DNA

Response of the sensor versus secondary probe

# DNA Detection

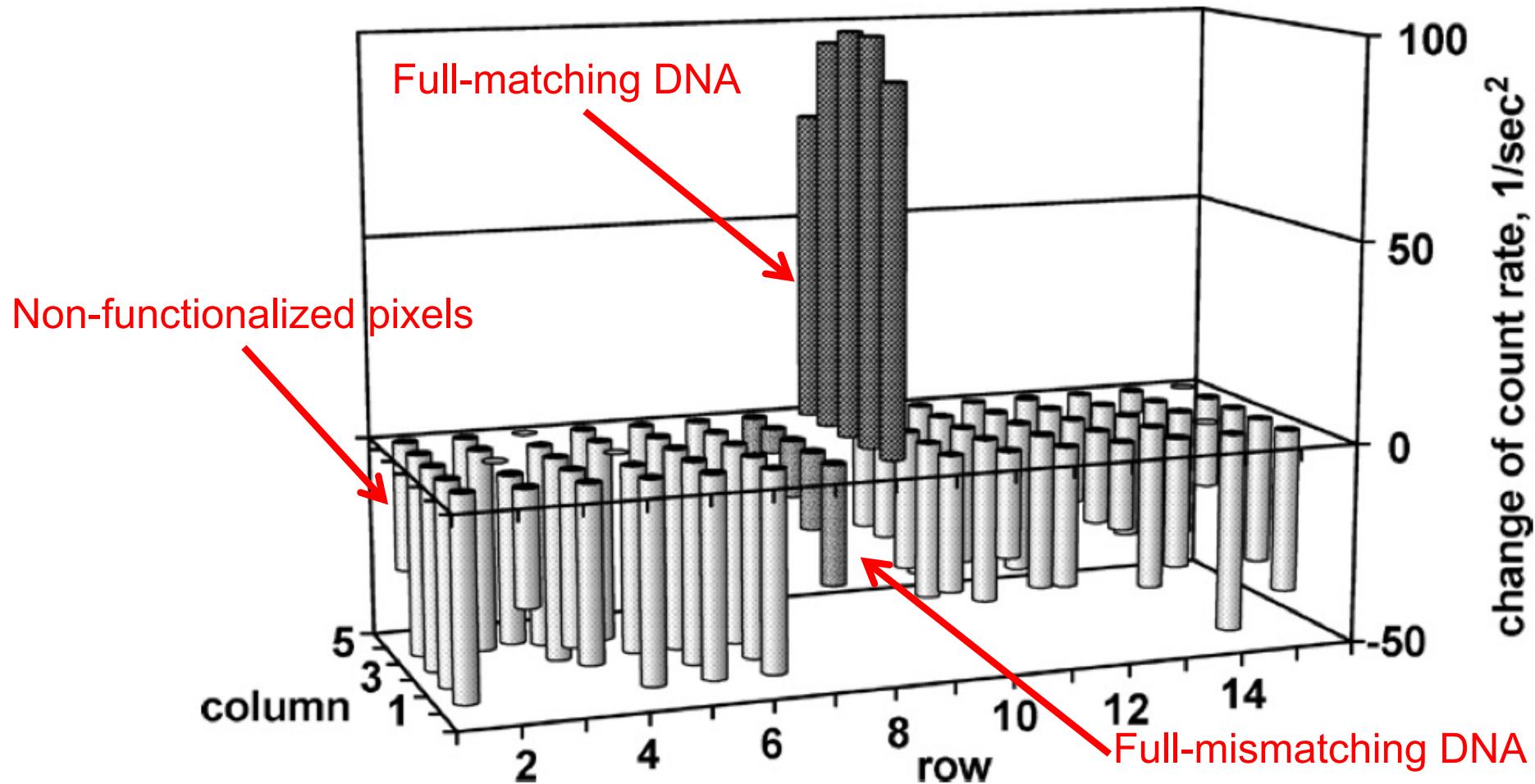

Row 8: full matching DNA, row 7: full mismatching DNA, all other positions not functionalized.