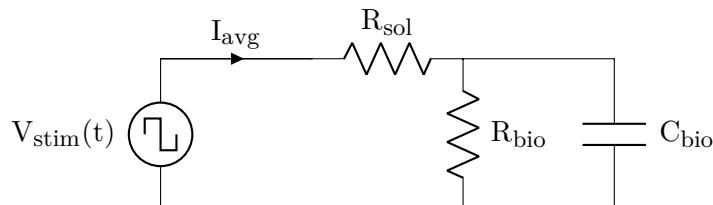


### Problem 1

With *Charge-Based Capacitance Measurement* (CBCM) method, the bio/nano interface is assumed to behave as an ideal capacitor  $C$ , independent of frequency. The CBCM front-end circuit is displayed hereunder,




where the voltage step generator (period  $T$  and step voltage  $V_{\text{step}}$ ) polarizes the bio/nano layer modeled as a resistance  $R_{\text{bio}}$  and a capacitor  $C_{\text{bio}}$ . The voltage drop across the solution resistance is neglected so that the average current through the bio/nano layer is

$$\begin{aligned} I_{\text{avg}} &= \frac{1}{T} \int_0^T \frac{V_{\text{stim}}(t)}{R_{\text{bio}}} dt + \frac{Q_{\text{tot}}}{T} \\ &= \frac{V_{\text{step}}}{2R_{\text{bio}}} + \frac{C_{\text{bio}} V_{\text{step}}}{T} \end{aligned} \quad (1)$$

Therefore,  $C_{\text{bio}} = \frac{1}{fV_{\text{step}}} \left( I_{\text{avg}} - \frac{V_{\text{step}}}{2R_{\text{bio}}} \right)$ . The upper and lower bounds are  $C_{\text{bio,min}} = 3.3 \text{ pF}$  and  $C_{\text{bio,max}} = 3.3 \text{ mF}$ , respectively.
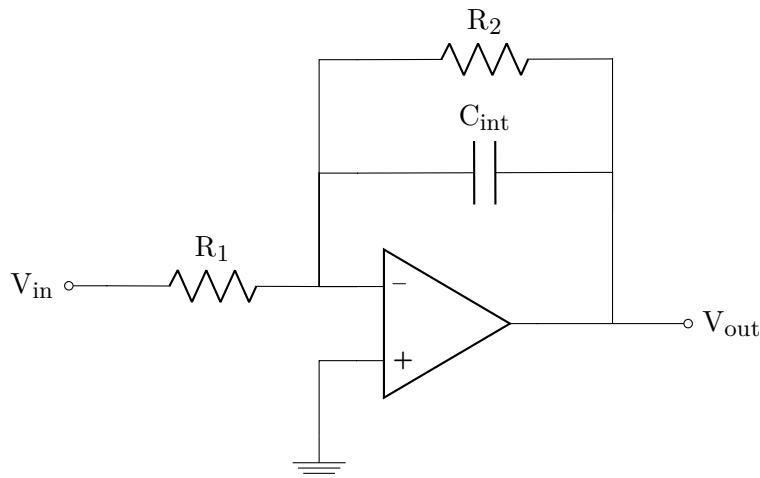
### Problem 2

The integration stage of the CBCM is implemented with the following circuit.




By applying nodal voltage analysis at the virtual ground of the opamp,

$$\frac{V_{\text{out}}(s)}{V_{\text{in}}(s)} = -\frac{R_2}{R_1} \frac{1}{1 + s R_2 C_{\text{int}}}$$

The integrator acts as a low-pass filter and the DC gain is set by the ratio of resistors. The integrator is sized such that the signal is not attenuated, and by applying Nyquist criterion,


$$\begin{aligned}
 2f_{\max} \leq \frac{1}{2\pi R_2 C_{\text{int}}} &\iff R_2 C_{\text{int}} \leq \frac{1}{4\pi f_{\max}} \\
 &\iff R_2 C_{\text{int}} \leq 0.796 \mu\text{s}.
 \end{aligned}$$

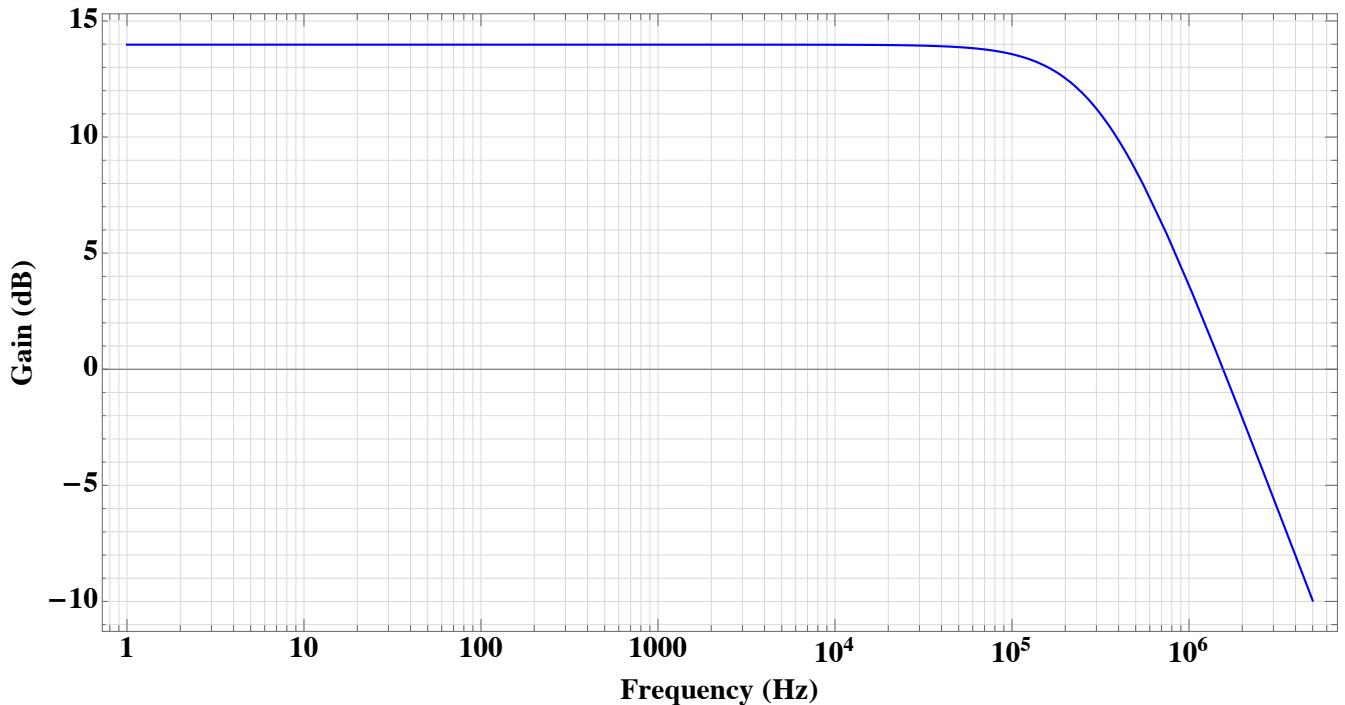Therefore,  $R_1 = 100\text{k}\Omega$ ,  $R_2 = 500\text{k}\Omega$ , and  $C_{\text{int}} = 1\text{pF}$  is a possible design choice. The corresponding Bode diagram is plotted below.



## Problem 3

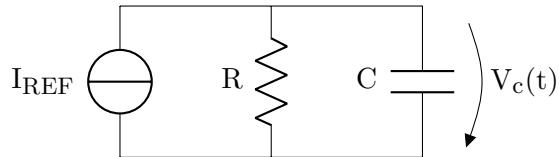(a) By neglecting the solution resistance and the geometrical two-plates capacitance formed by the two electrodes, the Randles circuit of the bio/CMOS interface is simply



where  $R$  and  $C$  represent the contributions of resistive and capacitive elements variations at the electrode/solution interface. By applying Kirchhoff current law,

$$I_{\text{REF}} = \frac{V_C(t)}{R} + C \frac{dV_C(t)}{dt}$$

The differential equation is solved with  $V_C(t=0) = 0$ , yielding

$$V_C(t) = R I_{\text{REF}} \left(1 - e^{-\frac{t}{RC}}\right)$$

The square signal  $V_{\text{OUT}}$  at the output of the comparator flips its state when a voltage  $V_{\text{REF}}$  is built across the electrodes. Thus,

$$\begin{aligned} V_C(t = \frac{T}{2}) = V_{\text{REF}} &\iff R I_{\text{REF}} \left(1 - e^{-\frac{T}{2RC}}\right) = V_{\text{REF}} \\ &\iff T = 2RC \ln \left( \frac{1}{1 - \frac{V_{\text{REF}}}{R I_{\text{REF}}}} \right) \end{aligned}$$

(b) The upper and lower bounds of the period of the output signal are  $T_{\text{min}} = 2.68 \text{ ms}$  and  $T_{\text{max}} = 5.34 \text{ ms}$ , respectively. In terms of frequency,  $f_{\text{min}} = 187 \text{ Hz}$  and  $f_{\text{max}} = 373 \text{ Hz}$ .

## Problem 4

If the assumption  $\frac{V_{\text{ref}}}{R I_{\text{ref}}} \rightarrow 0$  is made, the period of the output signal is simplified to  $T = 2C \frac{V_{\text{ref}}}{I_{\text{ref}}}$ , by applying the following approximations:

- $\frac{1}{1-\frac{1}{x}} \xrightarrow{x \rightarrow 0} 1+x$ .
- $\ln(1+x) \xrightarrow{x \rightarrow 0} x$ .

The upper bounds of the period of the output signal are  $T_{\text{min}} = 2.67 \text{ ms}$  and  $T_{\text{max}} = 5.33 \text{ ms}$ , respectively.

The relative error made by doing the assumption is

$$\epsilon = \max \frac{|T_{\text{approx}} - T_{\text{theo}}|}{T_{\text{theo}}} = 0.4\%$$