

EPFL

Electrical and Electronics Engineering

EE-518

Analog Circuits for Biochip

Master in Electrical and Electronics Engineering

EE-518: Analog Circuits for Biochip


	Subject of the week	Chapter' paragraphs
Week 1	Biochips & Related Applications (Sandro)	§1.1-1.4*
Week 2	Equivalent Circuits for Bio/CMOS interfaces (Sandro)	§2.2-3,8-9; §4.4.2-3; §5.5.4; §10.2*
Week 3	Brain/Machine interfaces: Circuit for Electrical Stimulation/Sensing (Sandro)	Course slides (**)
Week 4	Circuits for Amperometric Potentiometric Chemical Sensing (Sandro)	§5.2-3; §10.1-6, and §12.1*
Week 5	Circuits for Capacitive & Impedimetric Chemical Sensing (Sandro)	§5.5 & Chap. 13*
Week 6	Architecture of wireless implantable systems (Alexandre, 3 hours lecture)	Course slides (**)
Week 7	Inductive links TX (power, data) (Alexandre, 2 hours lecture, 1 hour exercise)	Course slides (**)
Week 8	Inductive links RX (Alexandre, 2 hours lecture, 1 hour exercise)	Course slides (**)
18-23/04	EASTER HOLIDAY	
Week 9	RF telemetry TX, RX (power, data) (Alexandre, 2 hours lecture, 1 hour exercise)	Course slides (**)
Week 10	RF telemetry (Alexandre, 1 hour lecture, 2 hours exercises)	Course slides (**)
Week 11	Introduction to antennas and radiation regulations (Anja)	Course slides
Week 12	WBAN Antennas (Anja)	Course slides
Week 13	WBAN Antennas (Anja)	Course slides
Week 14	Review for final exam	-

* S. Carrara, Bio/CMOS interfaces and Co-Design, 2nd edition, Springer, 2024 – ** Supporting reading references announced in the slide set

Glucometer on iPhone




The electrochemical Cell

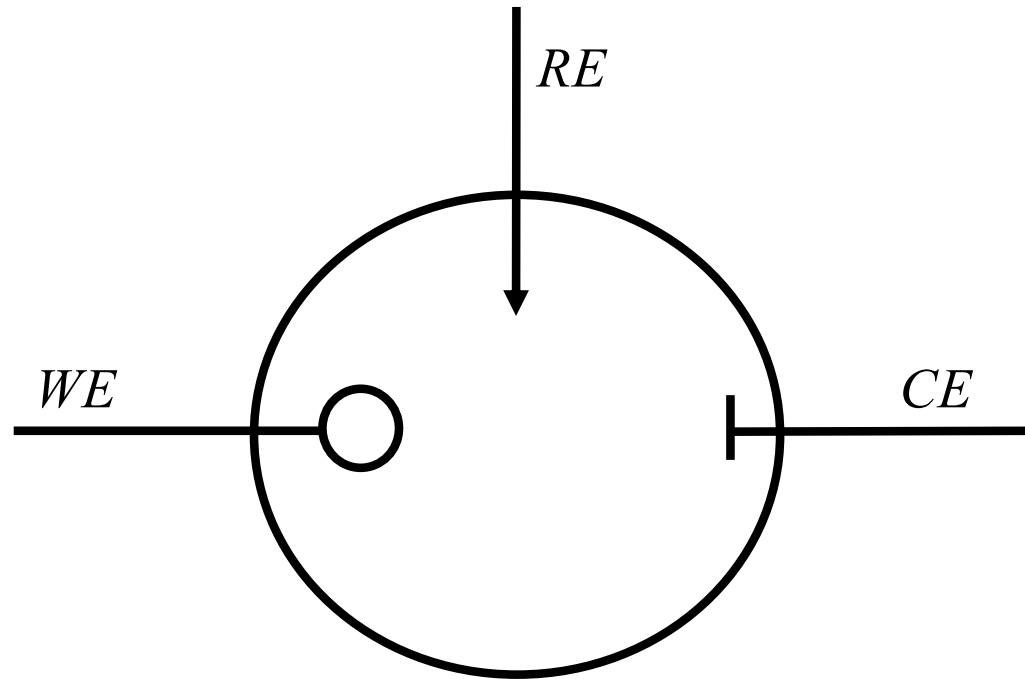


The typical electrochemical cell needs 3 electrodes: the working, the counter, and the reference

How to measure a redox reaction?

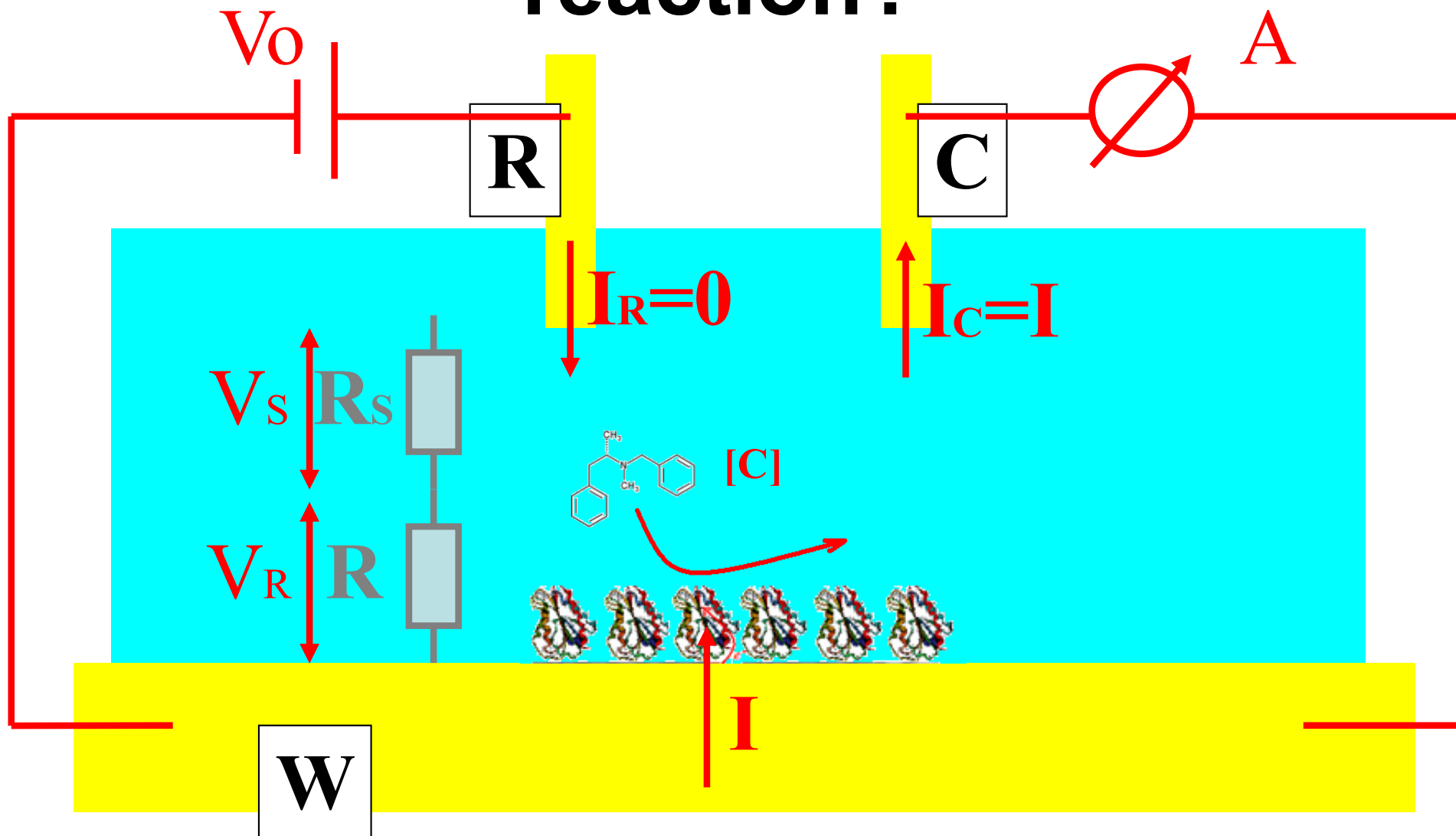


The 4e Electrochemical Cell

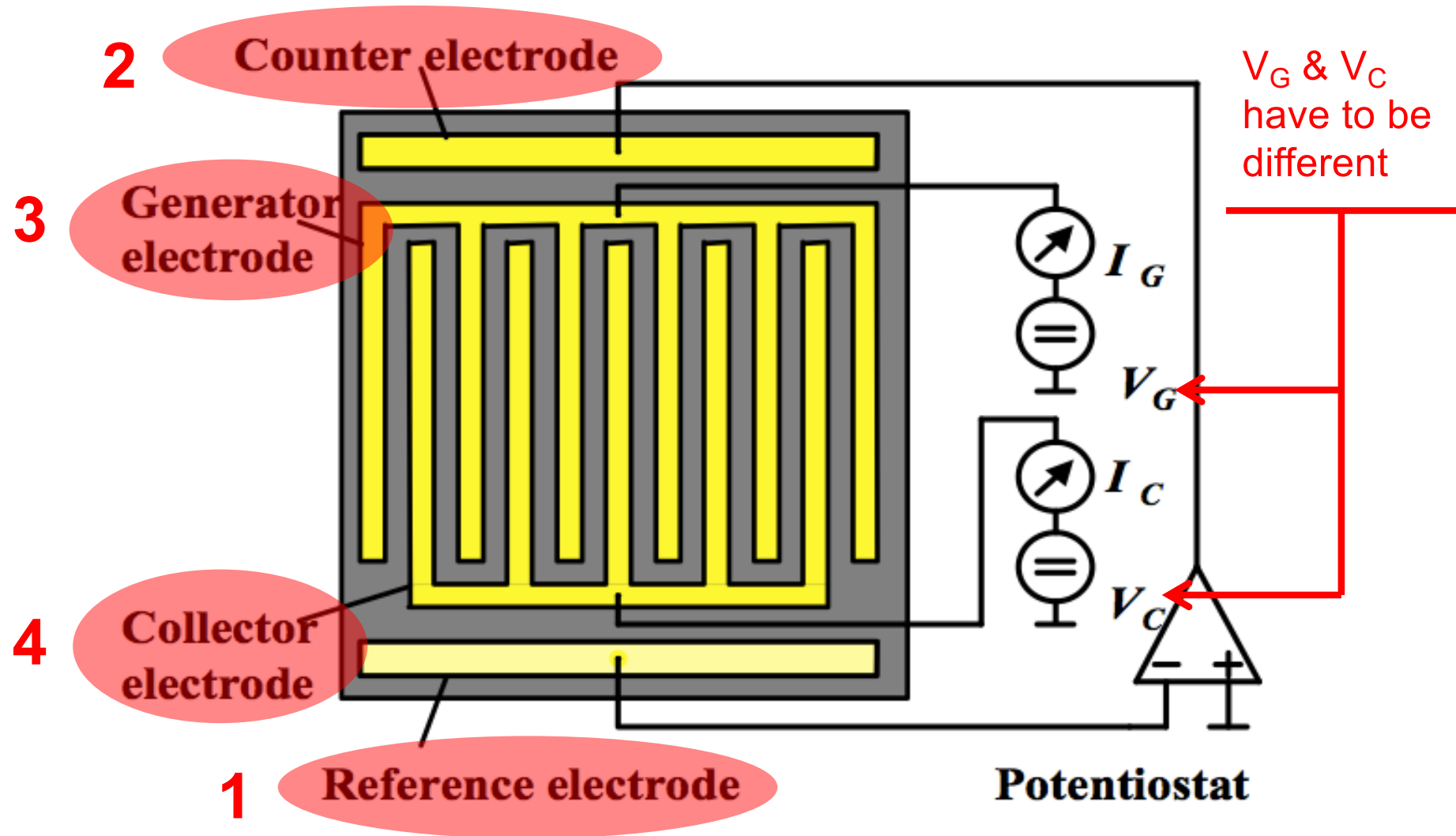


A 4-electrode Electrochemical Cell is here required

Control Amplifier @ RE

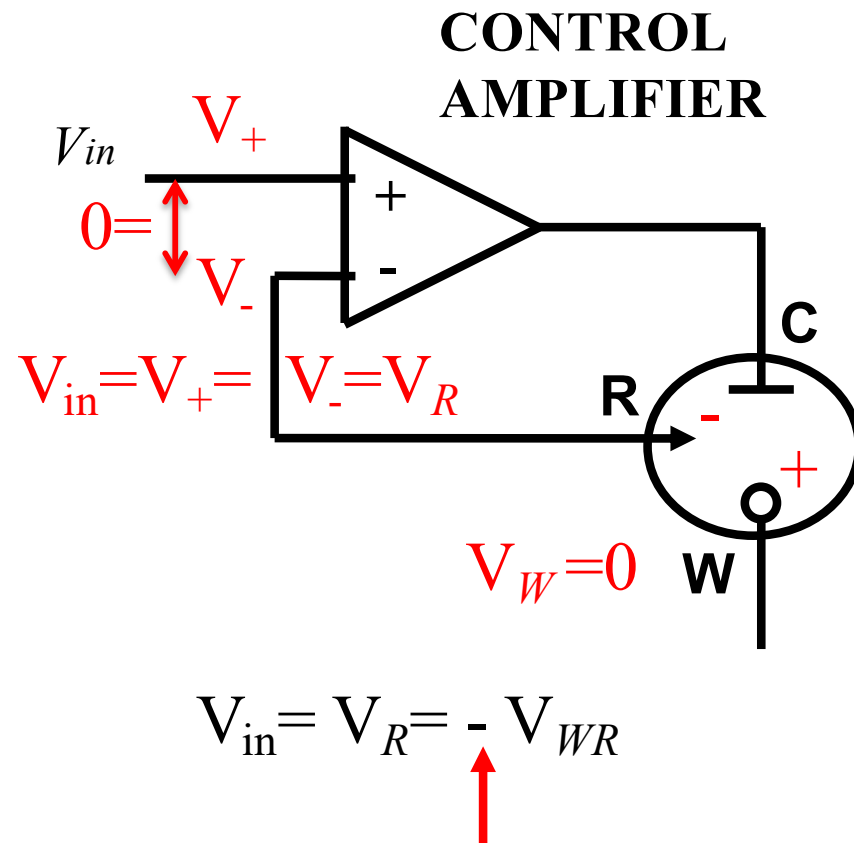


Risk of Saturation

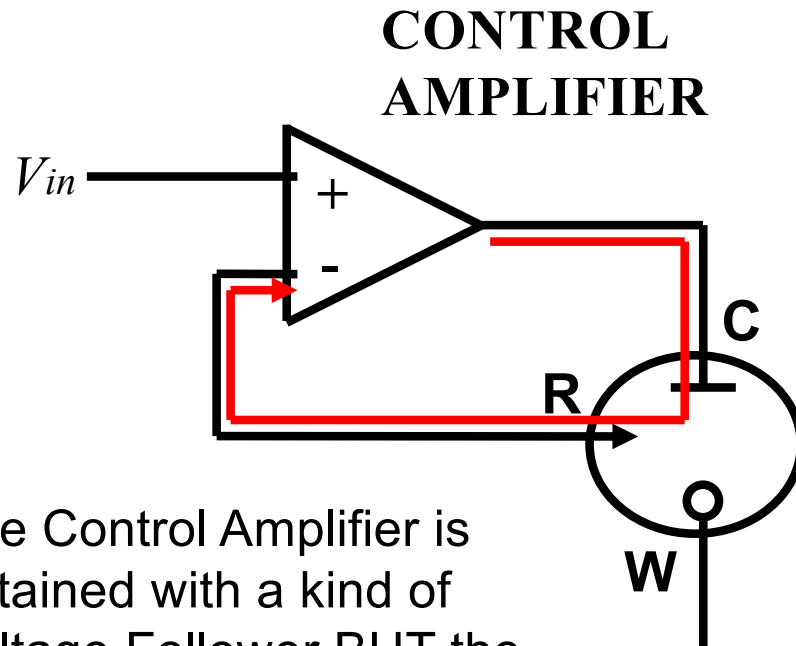

1. The Control Amplifier is obtained with a kind of Voltage Follower BUT the Cell is inserted in its feedback loop
2. Thus, the Voltage Follower might saturate if the design (both Cell & Follower) are not co-designed properly


Risk of Saturation

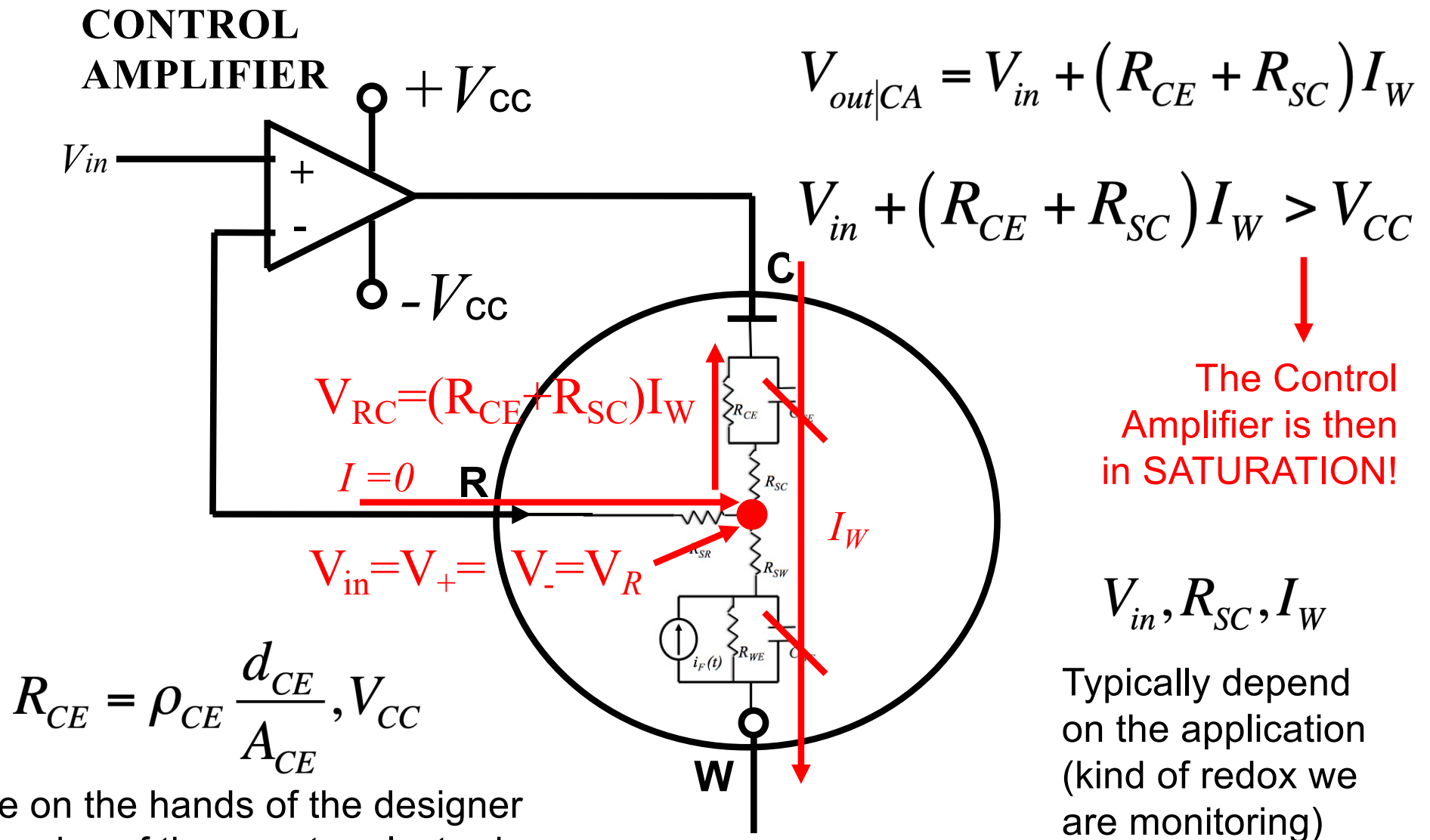

Are on the hands of the designer
(the size of the counter electrode
and/or the circuit powering)


(c) S.Carrara

Faradaic Current @ Fixed Bias

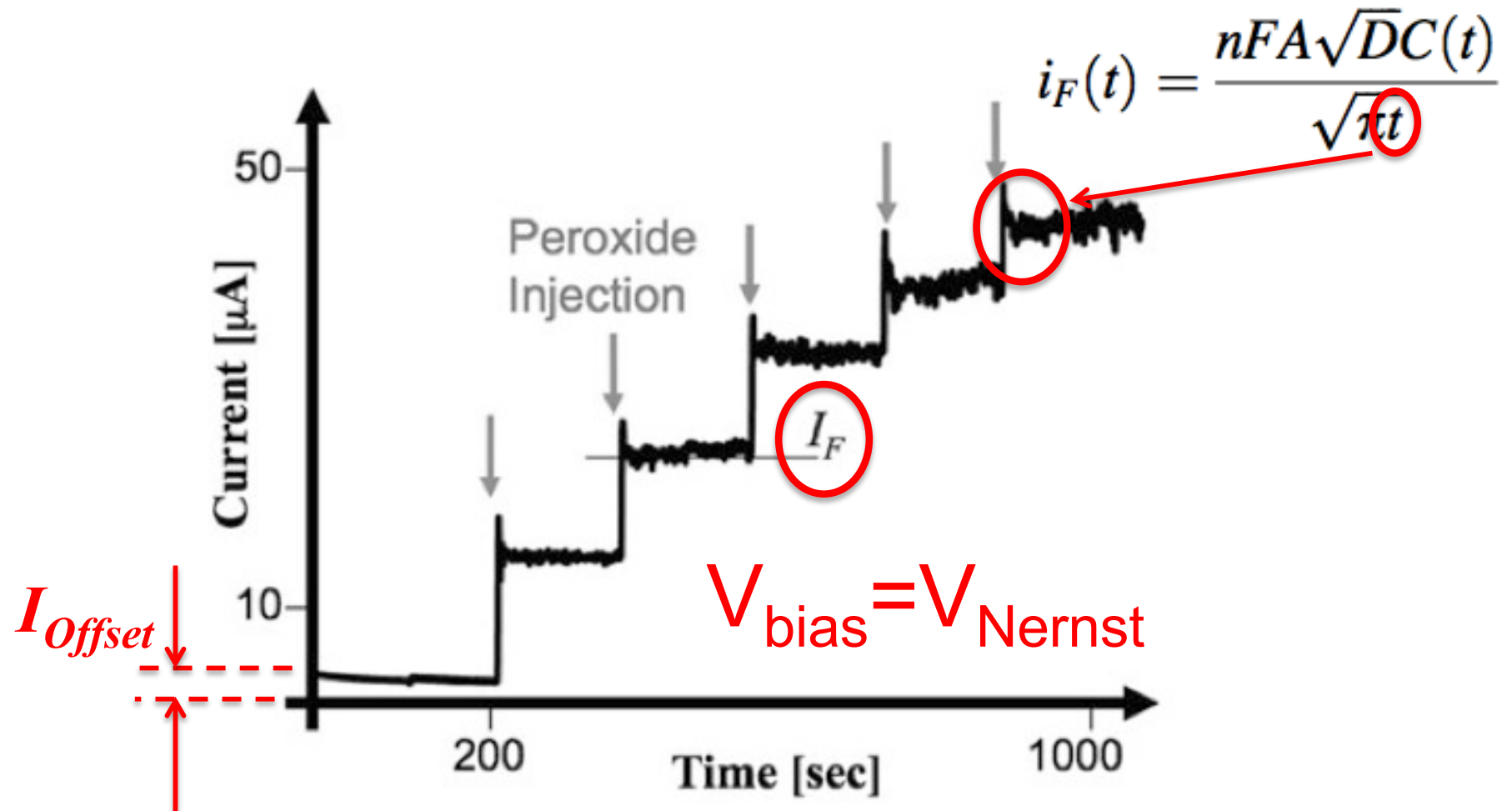


Typical curve in chronoamperometry

Faradaic Current in Voltage Scan

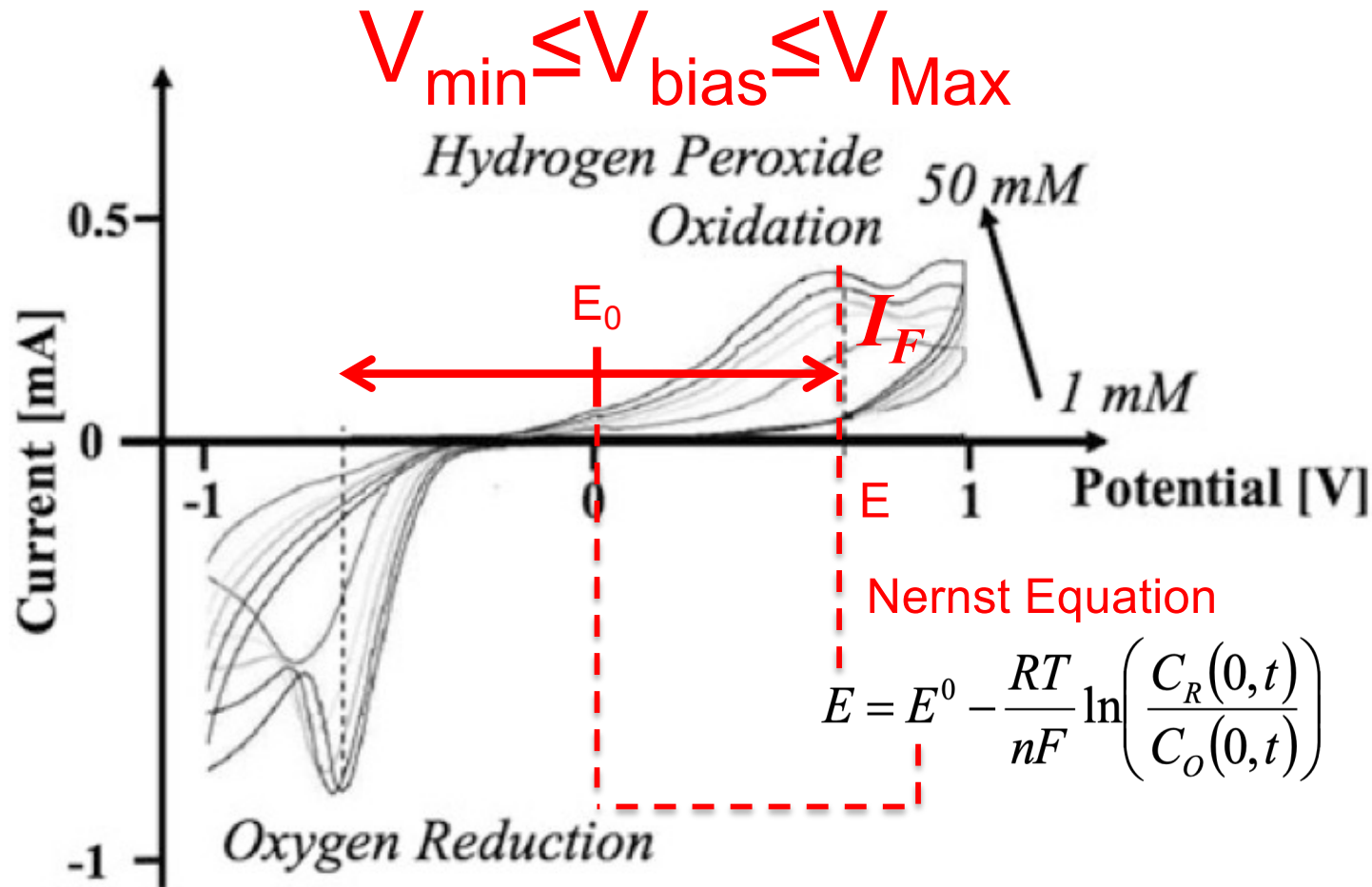


O⁺ reduction and H₂O₂ oxidation
observed in Cyclic Voltammetry (CV)


Transimpedance Amplifier @ WE

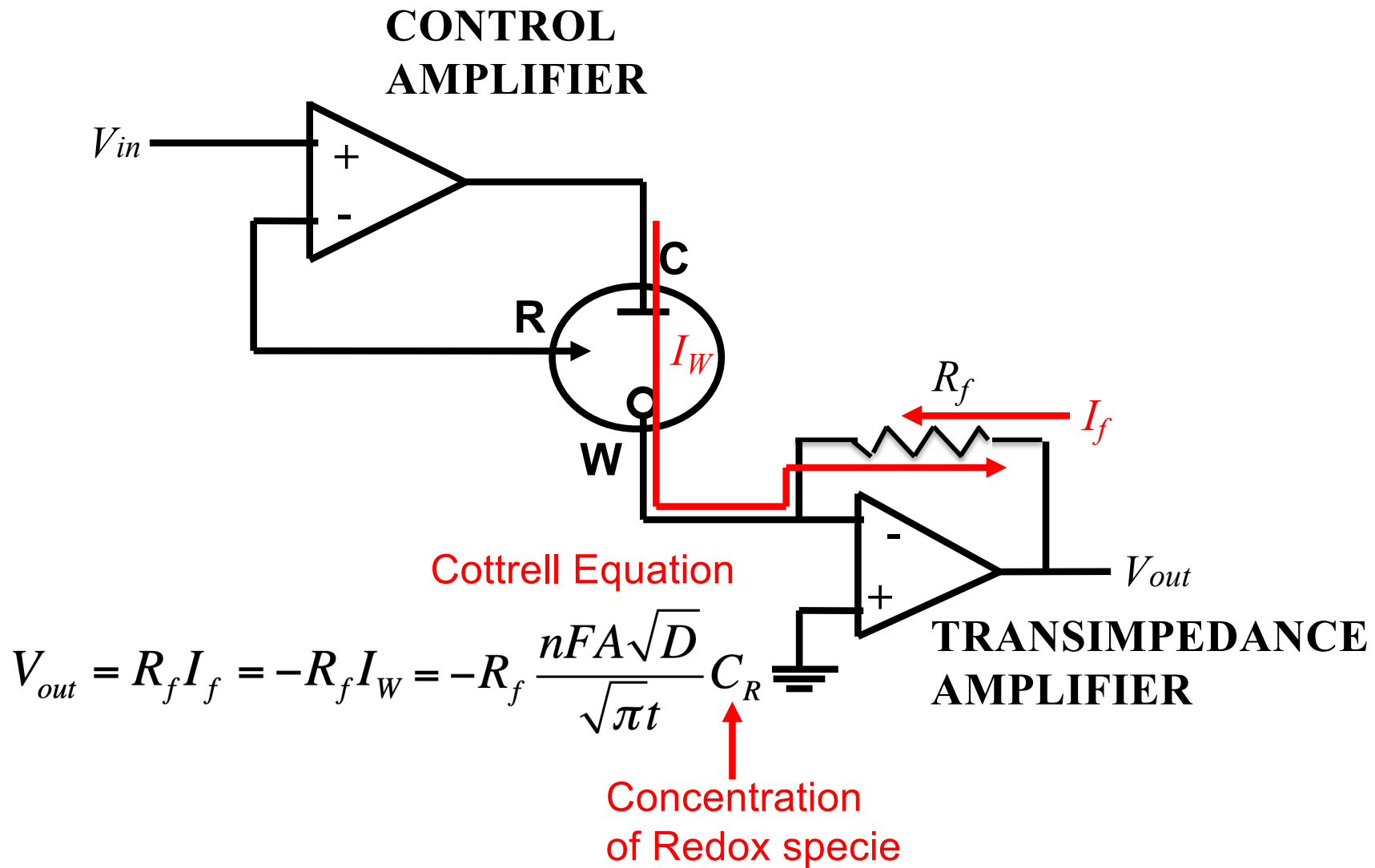


Grounded Working

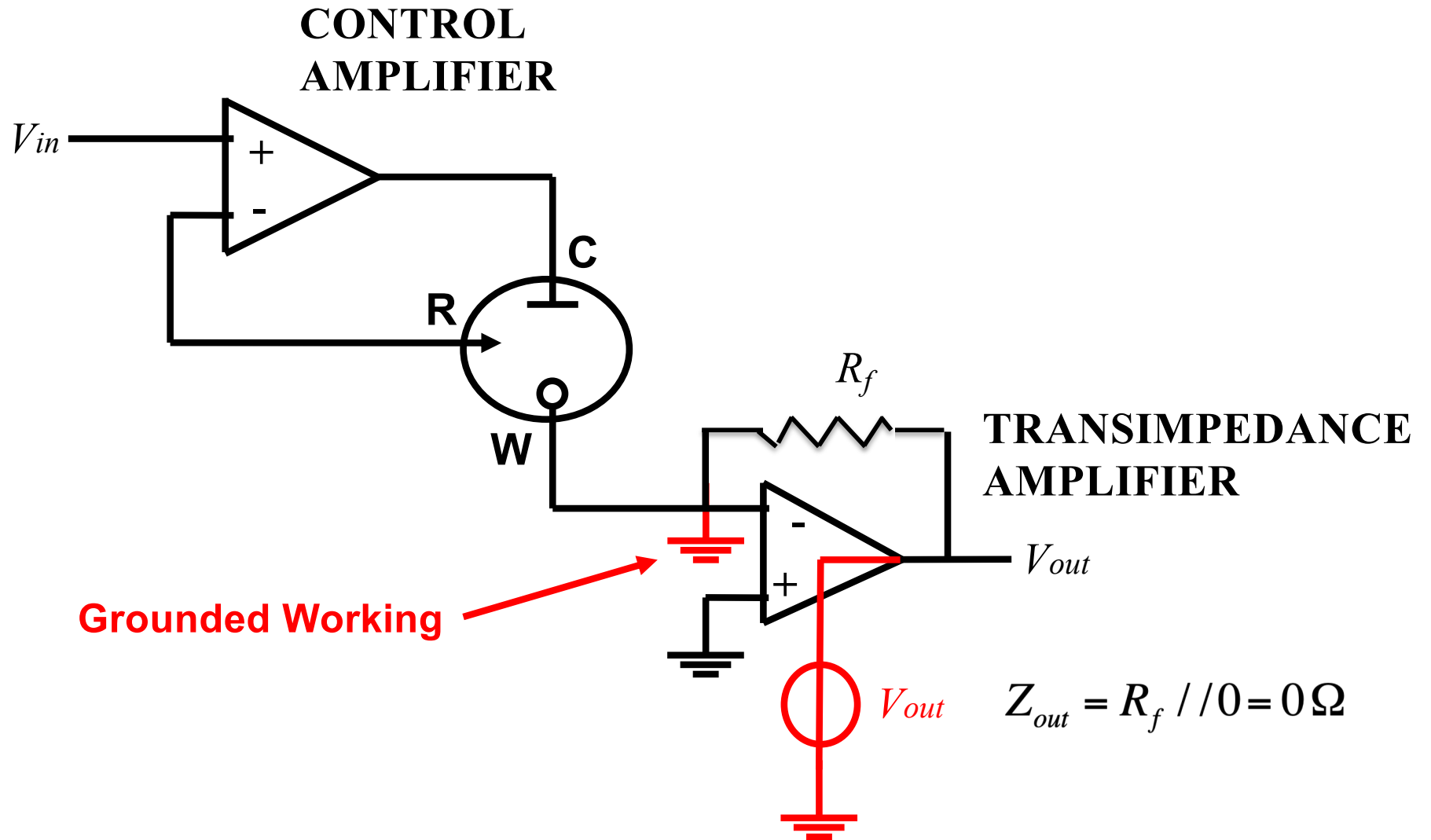


Current-to-Voltage Conversion

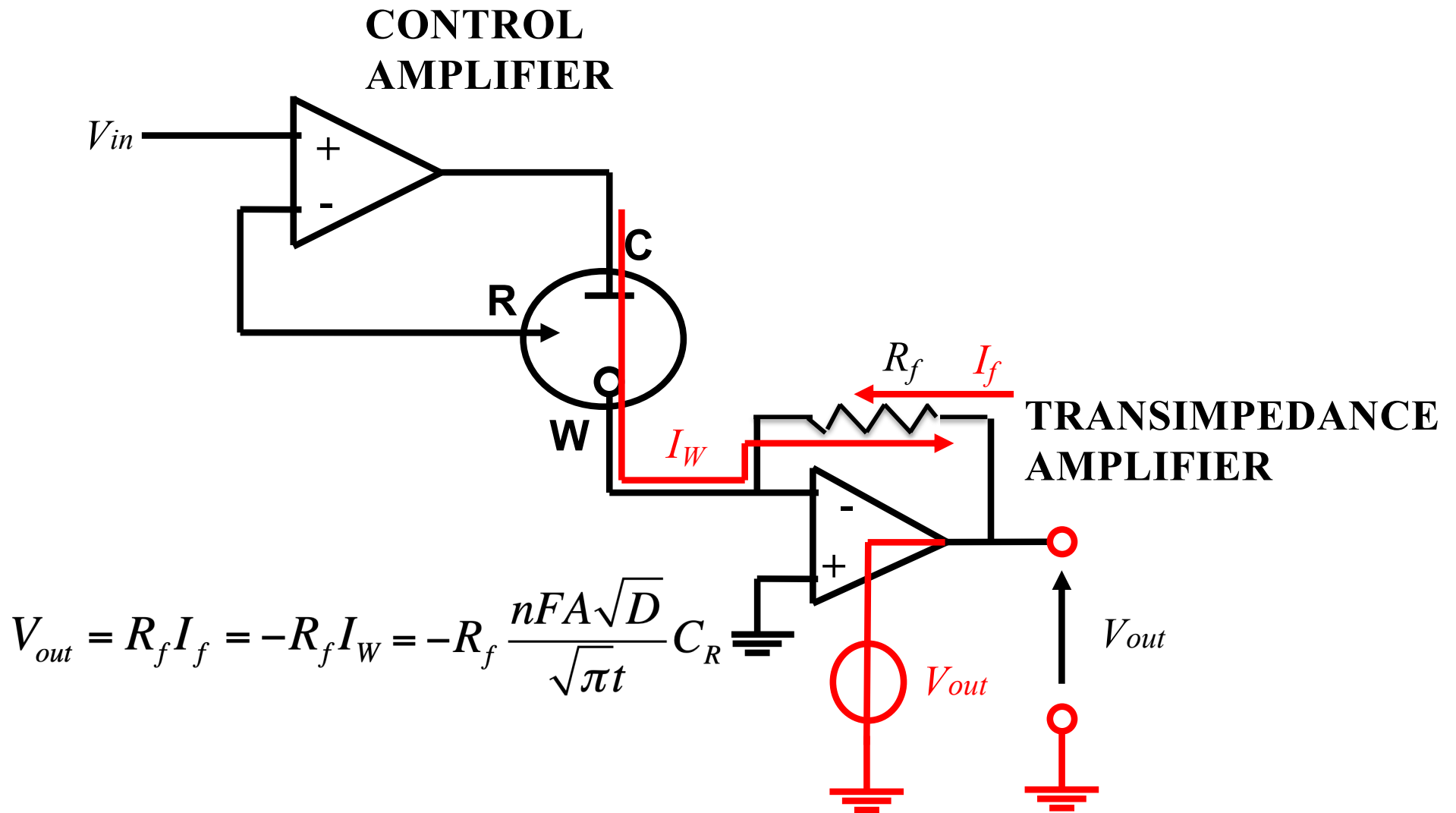


Inside the Cell: Faradaic Currents

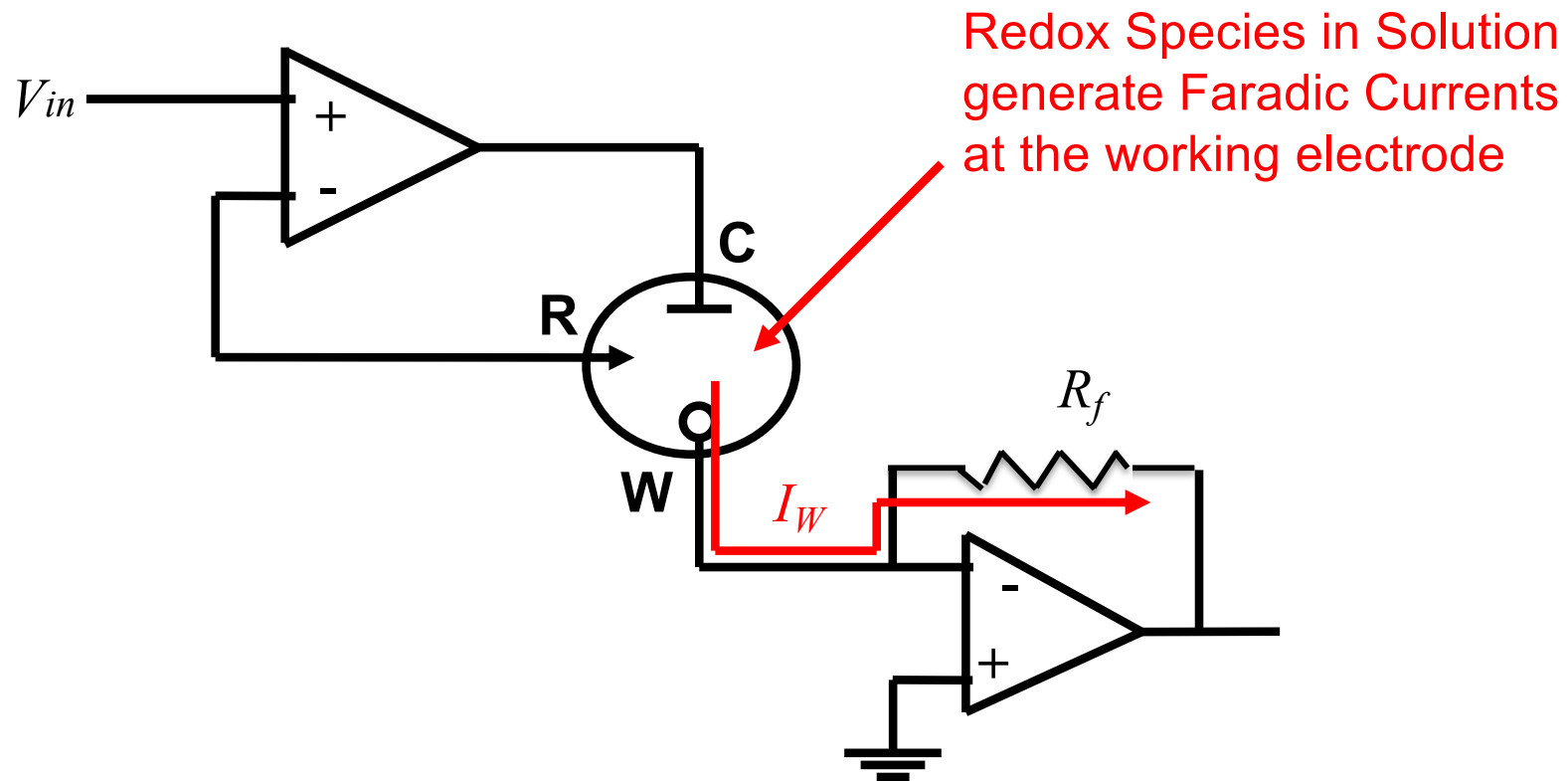


Oxidases based detection

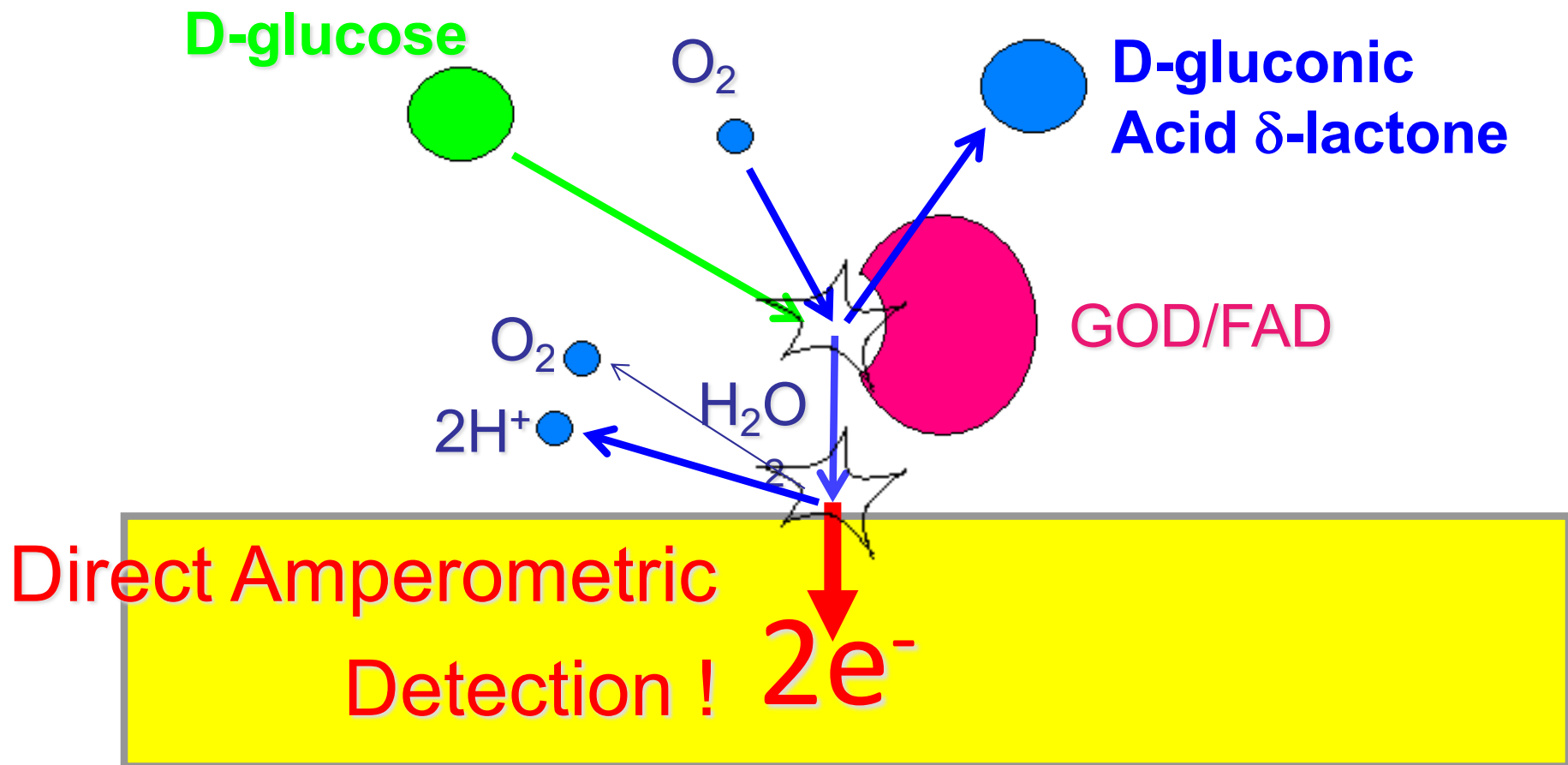

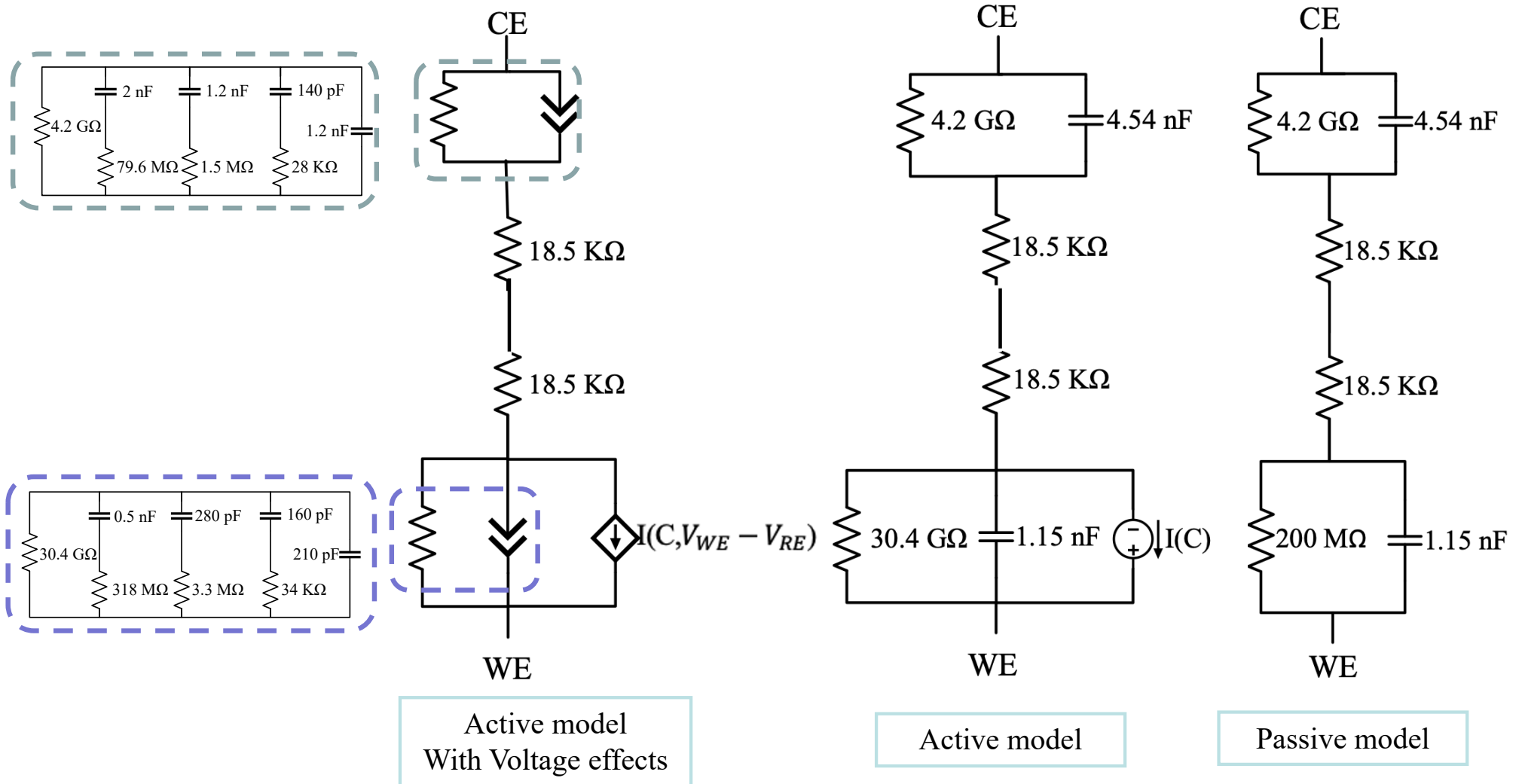Equivalent Circuit for Bio/CMOS interfaces




The Capacitance DNA Detection

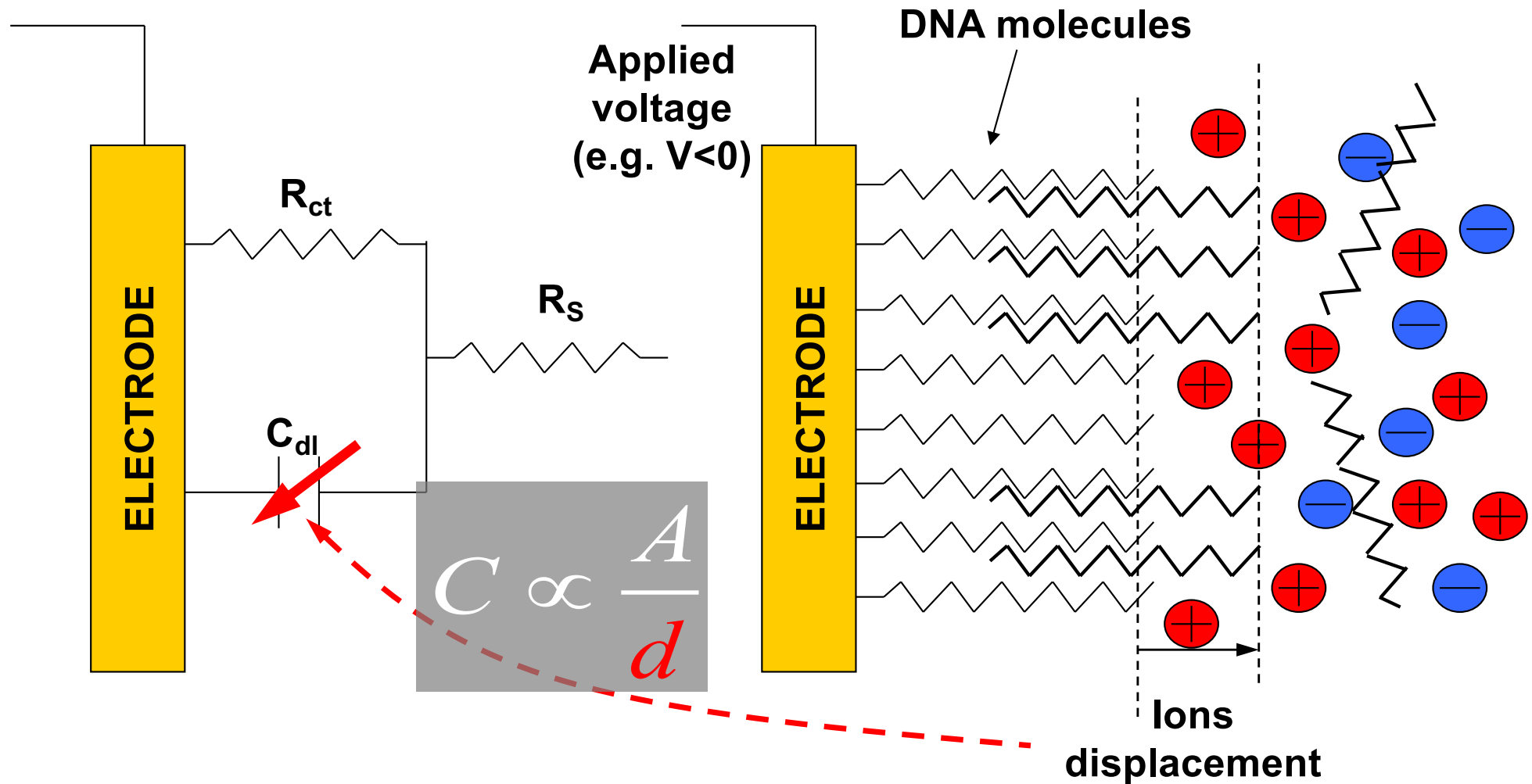

Unlabeled ssDNA may be detected with capacitance measurements as due to charge displacement

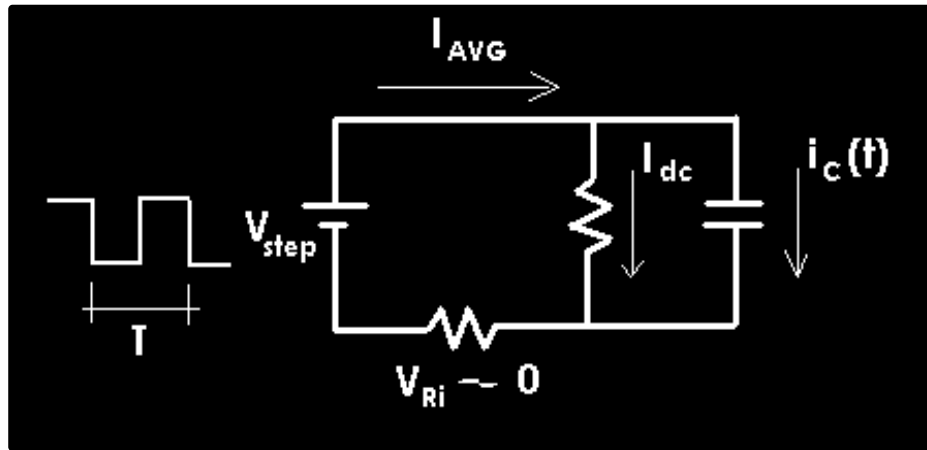Charge-Based Capacitance Measurement (CBCM)




$$i(t) = I_{dc} + i_C(t)$$

Frequency!

$$I_{AVG} = \frac{I_{dc}}{2} - \frac{1}{T} \int_0^{T/2} i_C(t) dt$$


$$I_{AVG} = \frac{I_{dc}}{2} - CV_{step}f$$

THE CAPACITANCE !

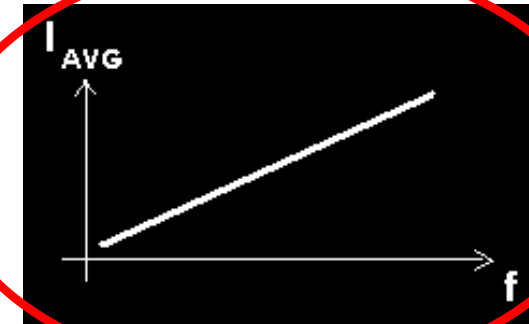

Method for a precise Capacitance measurement


CMOS for CBCM detection

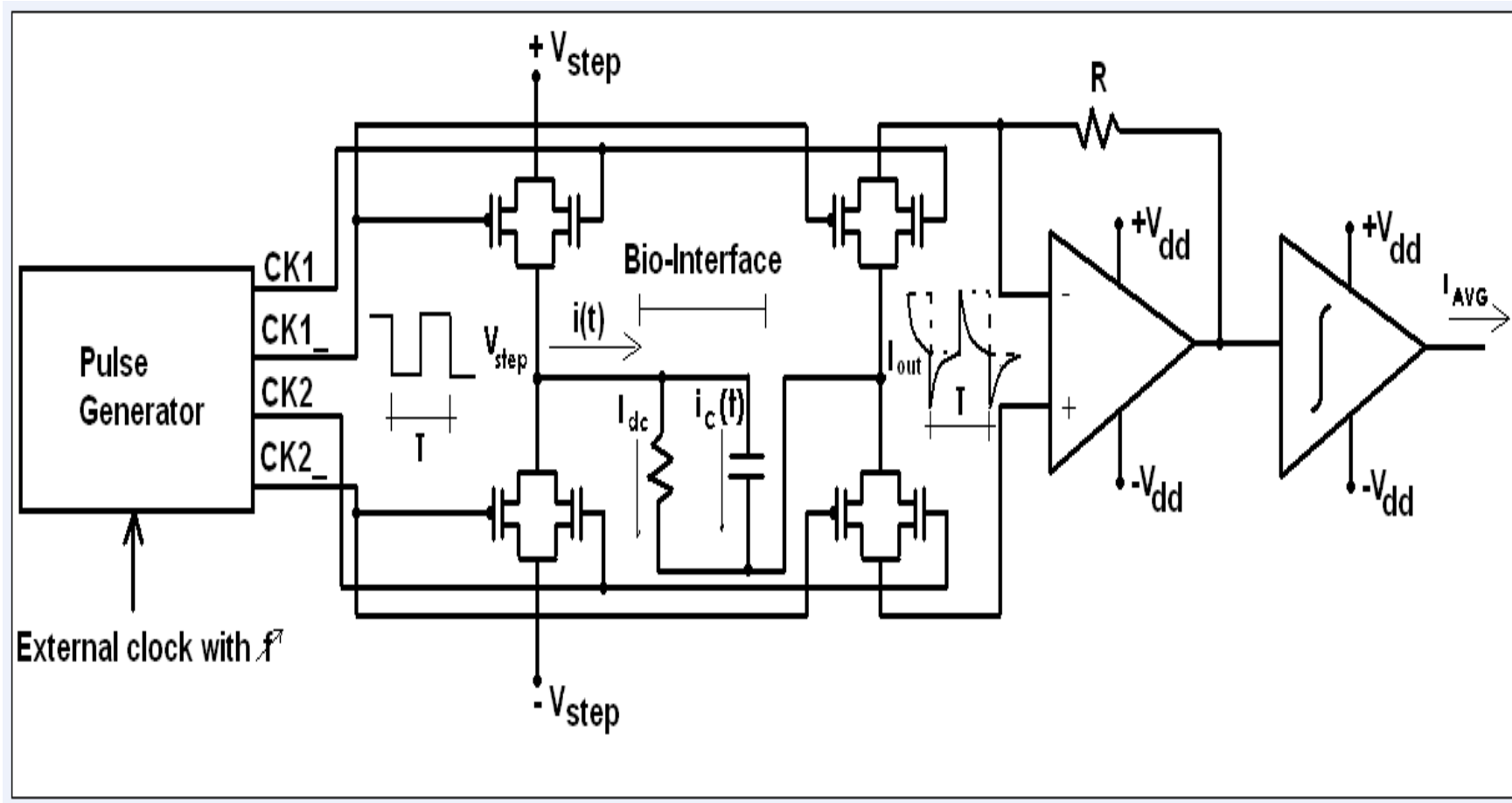


The circuit assures the square signal generator, an inverters, and an integrator to calculate the average current

Frequency to Capacitance Measurement (FTCM)


Principle: Frequency To Capacitance Mode

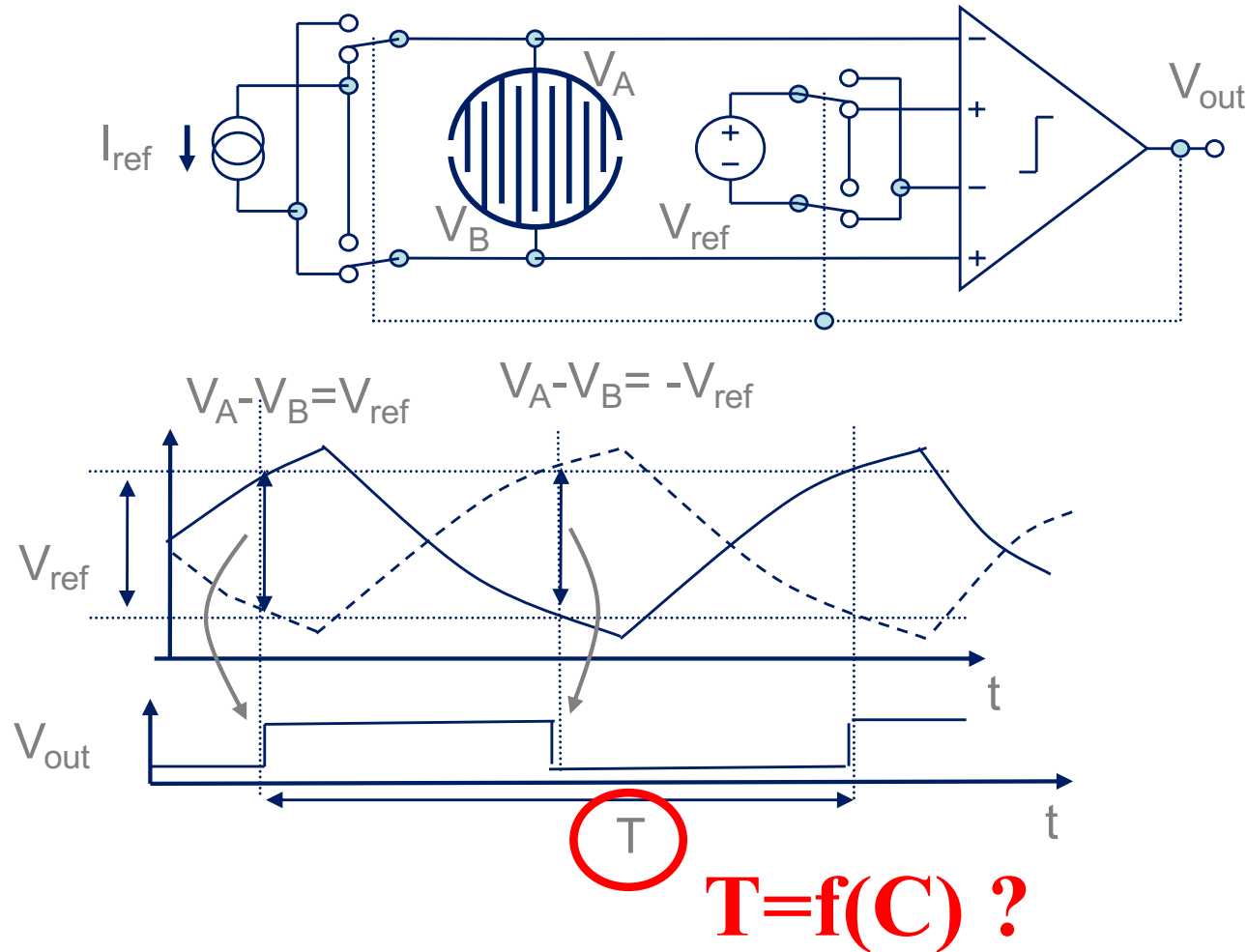

Chip Architecture (FTCM)

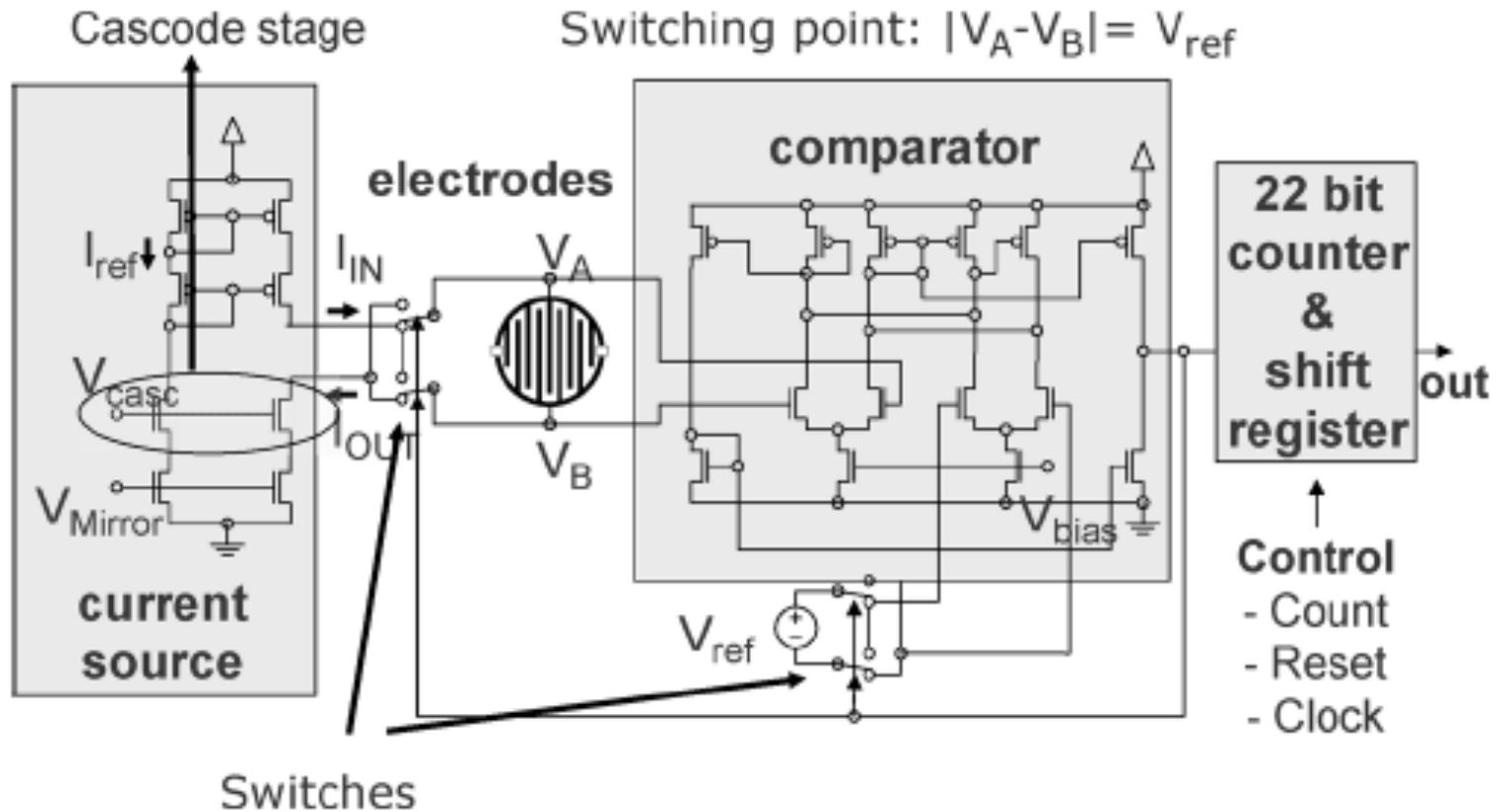


Impedimetric Sensing

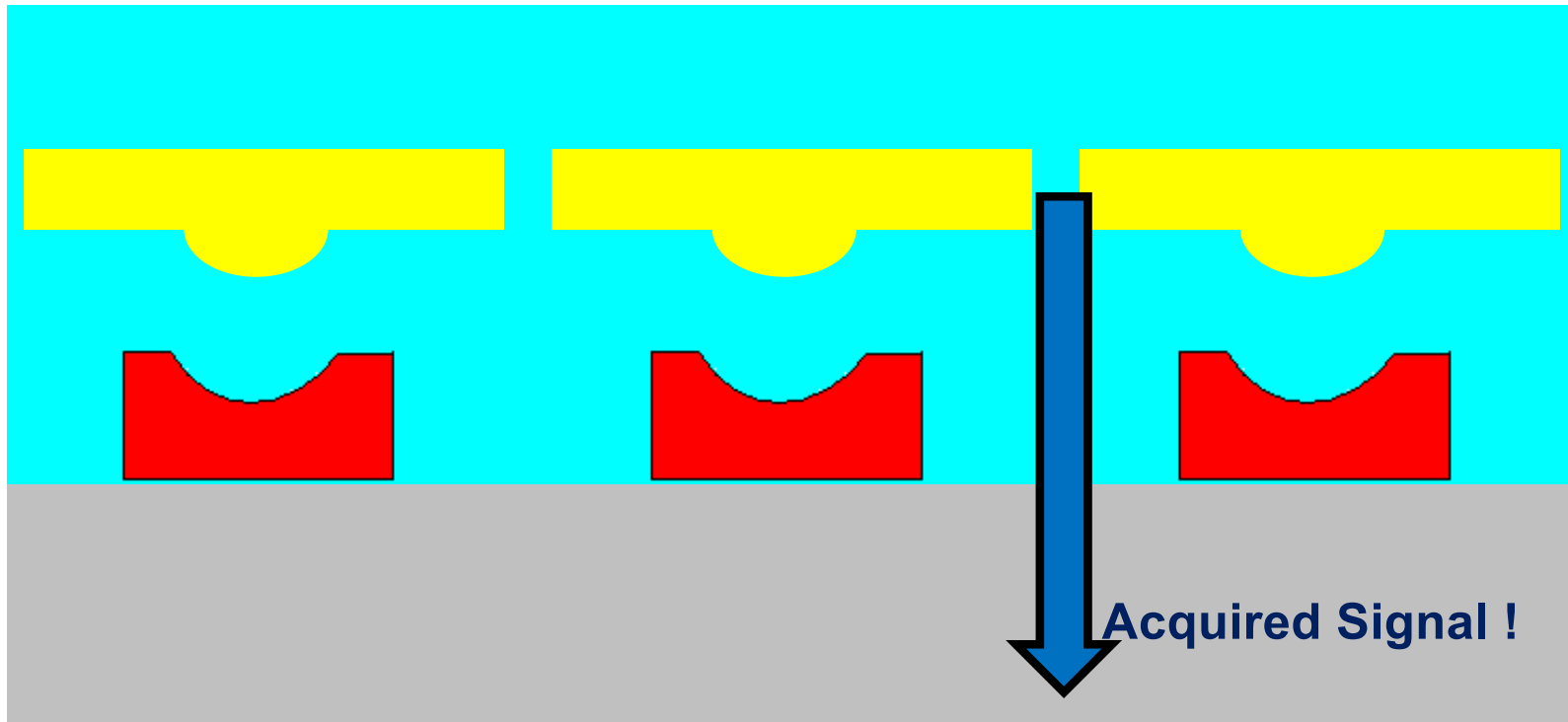


Clearly, the impedance of the Bio/CMOS interface changes accordingly to molecular steric hindrance

Impedimetric Sensing

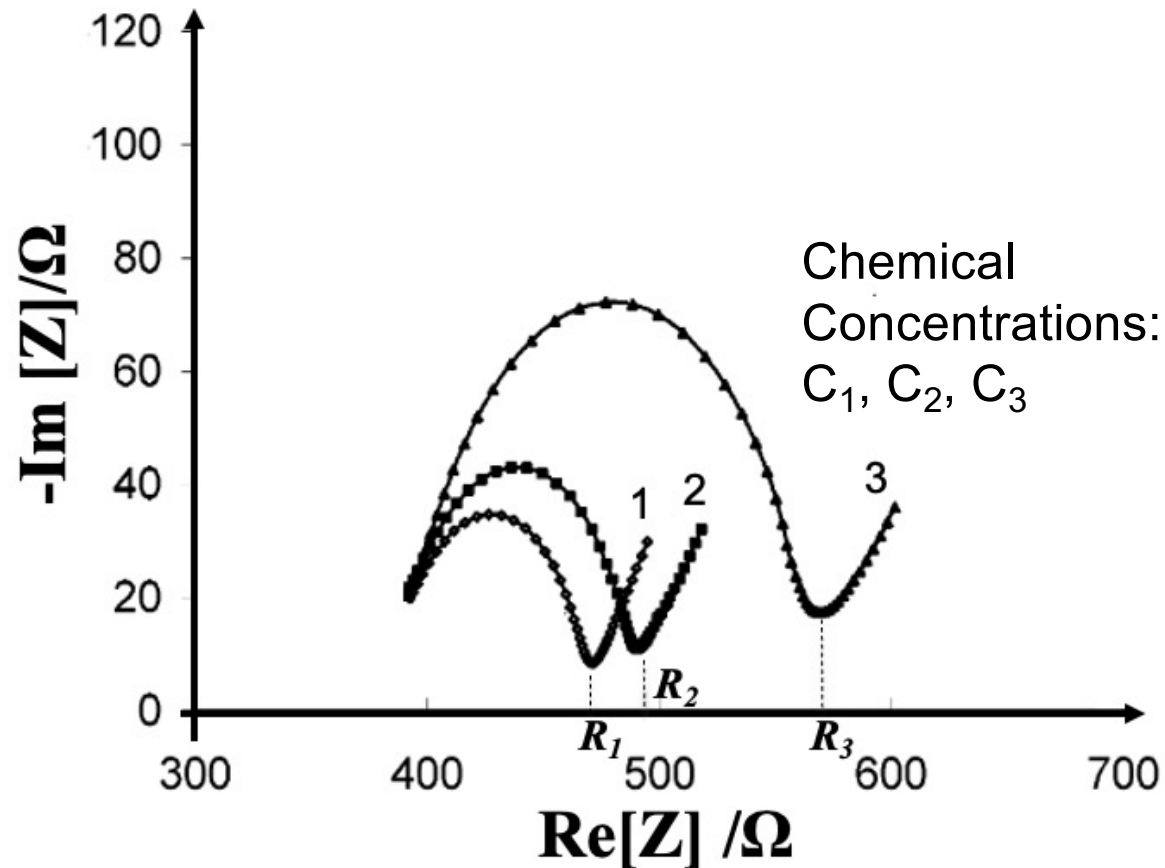

Nyquist Plots may be used for Molecular Detection by following changes in Z

Impedimetric Sensing

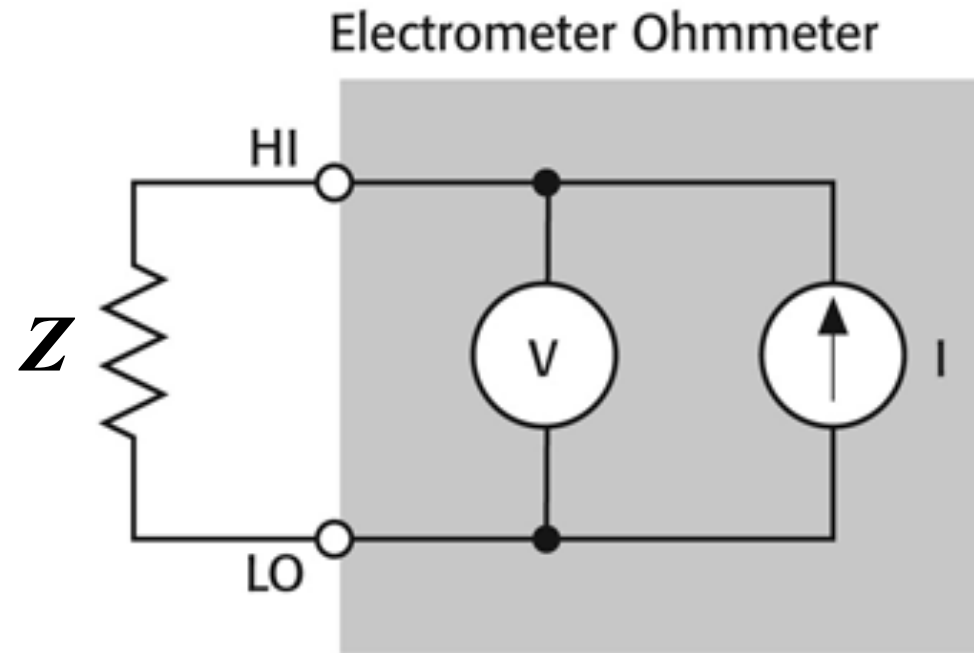


$$\underline{Z} = |\underline{Z}|e^{j\varphi} = Z[\cos(\varphi) + j\sin(\varphi)]$$


$$\underline{I}(t) = I_0 \sin(\omega t)$$

$$V_{\text{out}} = \underline{Z}\underline{I}(t) = ZI_0\sin(\omega t + \varphi)$$


Impedimetric Sensing

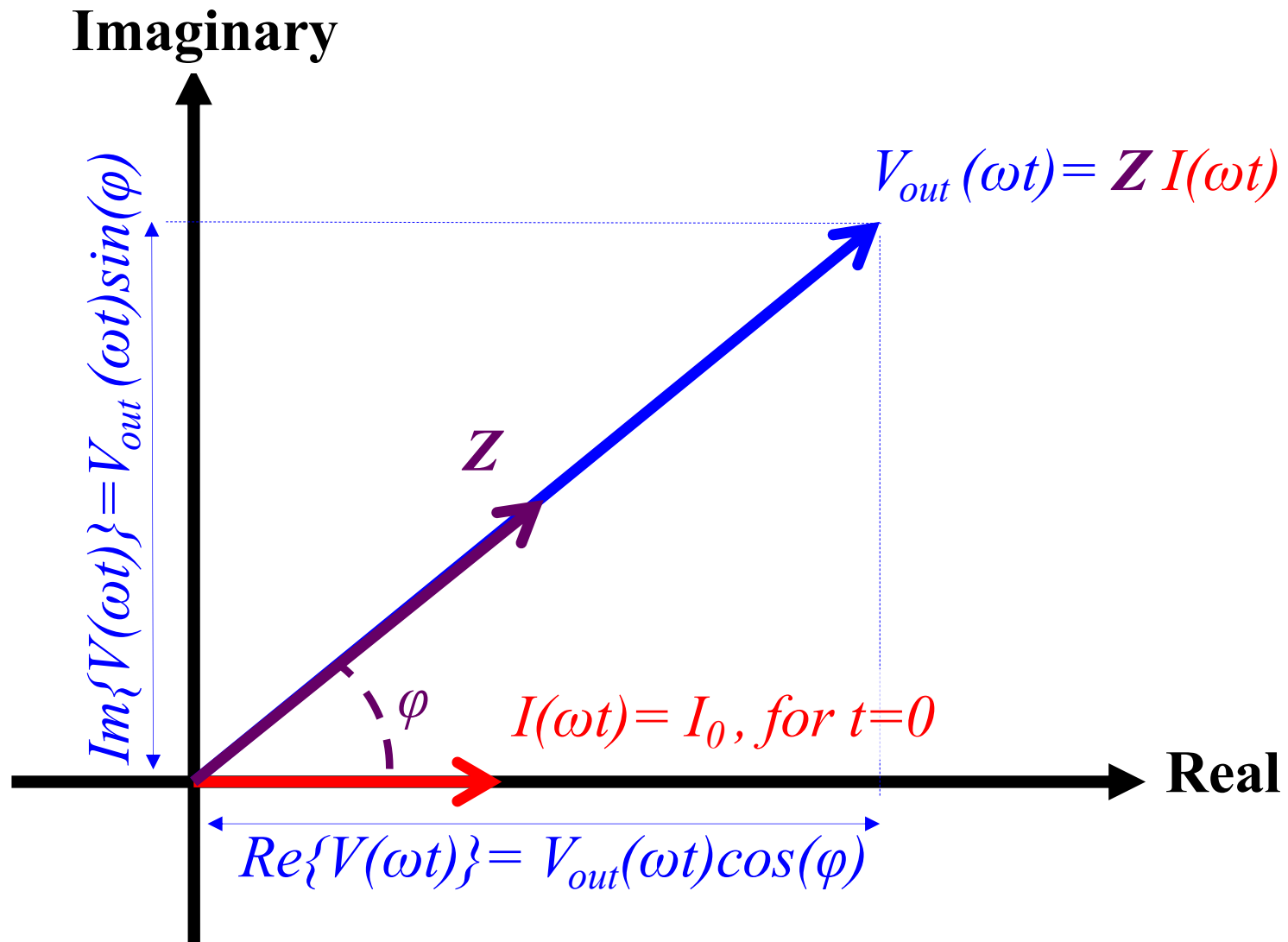

Impedimetric Sensing

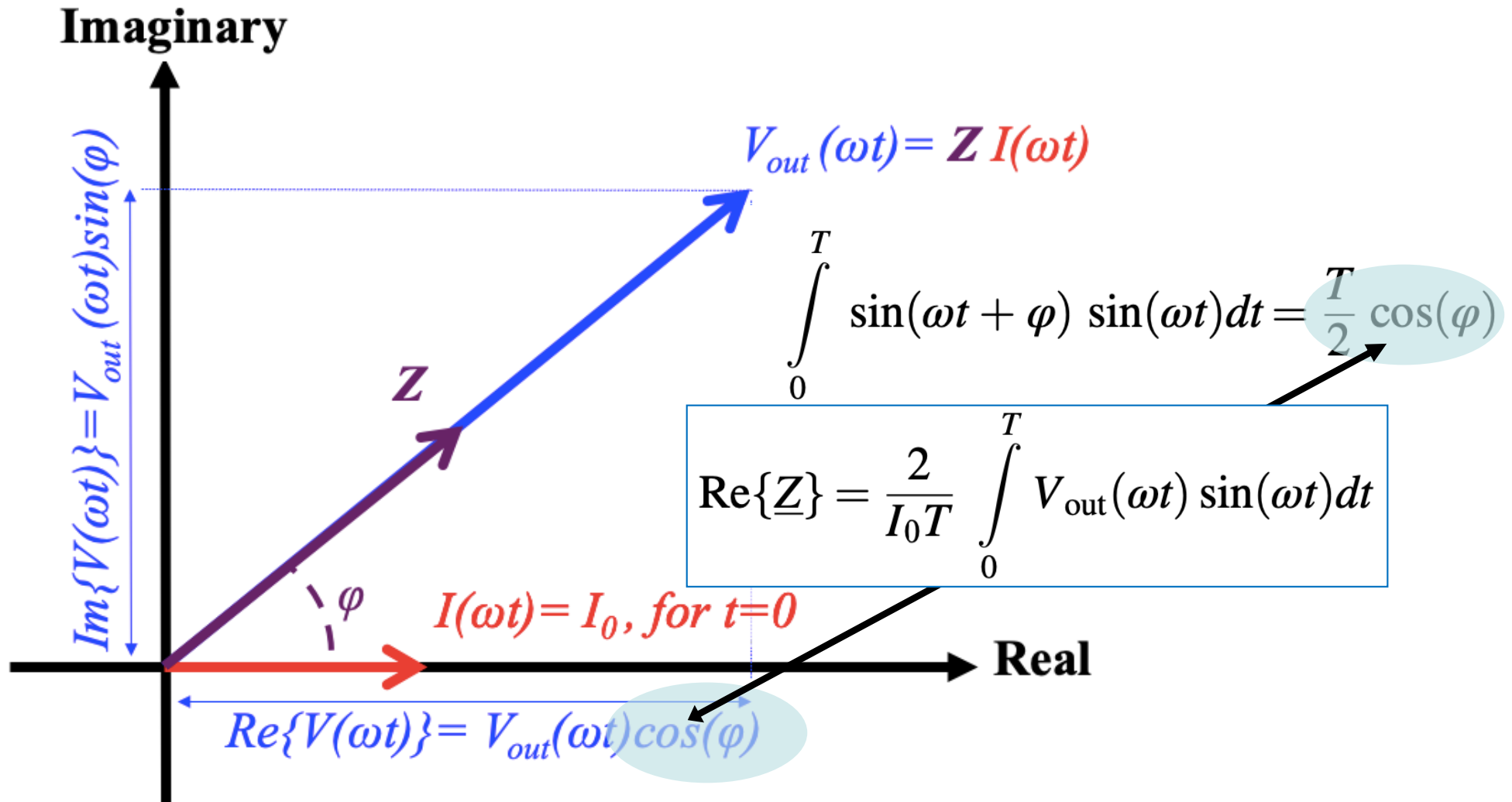

Impedimetric Sensing

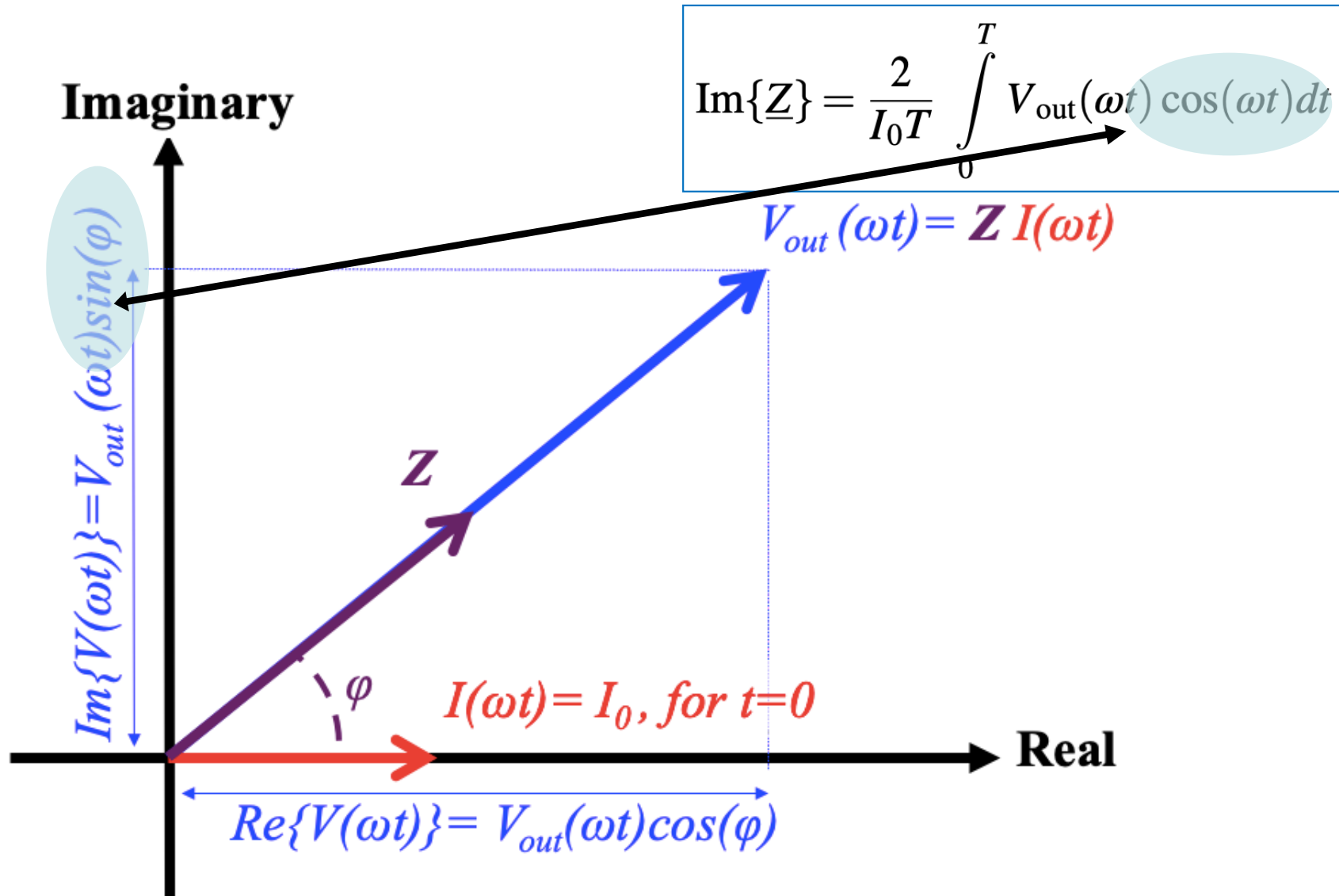

Impedimetric Sensing


$$\left\{ \begin{array}{l} \text{Re}\{\underline{Z}\} = \frac{2}{I_0 T} \int_0^T V_{\text{out}}(\omega t) \sin(\omega t) dt \\ \text{Im}\{\underline{Z}\} = \frac{2}{I_0 T} \int_0^T V_{\text{out}}(\omega t) \cos(\omega t) dt \end{array} \right.$$

Diagram illustrating the calculation of the real and imaginary parts of the impedance $\underline{Z}$ using the output voltage $V_{\text{out}}(\omega t)$ and the reference signals $\sin(\omega t)$ and $\cos(\omega t)$.


The real part $\text{Re}\{\underline{Z}\}$ is calculated by multiplying $V_{\text{out}}(\omega t)$ by $\sin(\omega t)$ (indicated by a circle with an 'X') and then integrating the result over the period T (indicated by a square with an integral symbol $\int$).

The imaginary part $\text{Im}\{\underline{Z}\}$ is calculated by multiplying $V_{\text{out}}(\omega t)$ by $\cos(\omega t)$ (indicated by a circle with an 'X') and then integrating the result over the period T (indicated by a square with an integral symbol $\int$). A phase shift of $+90^\circ$ is indicated for the cosine reference signal.


Impedimetric Sensing

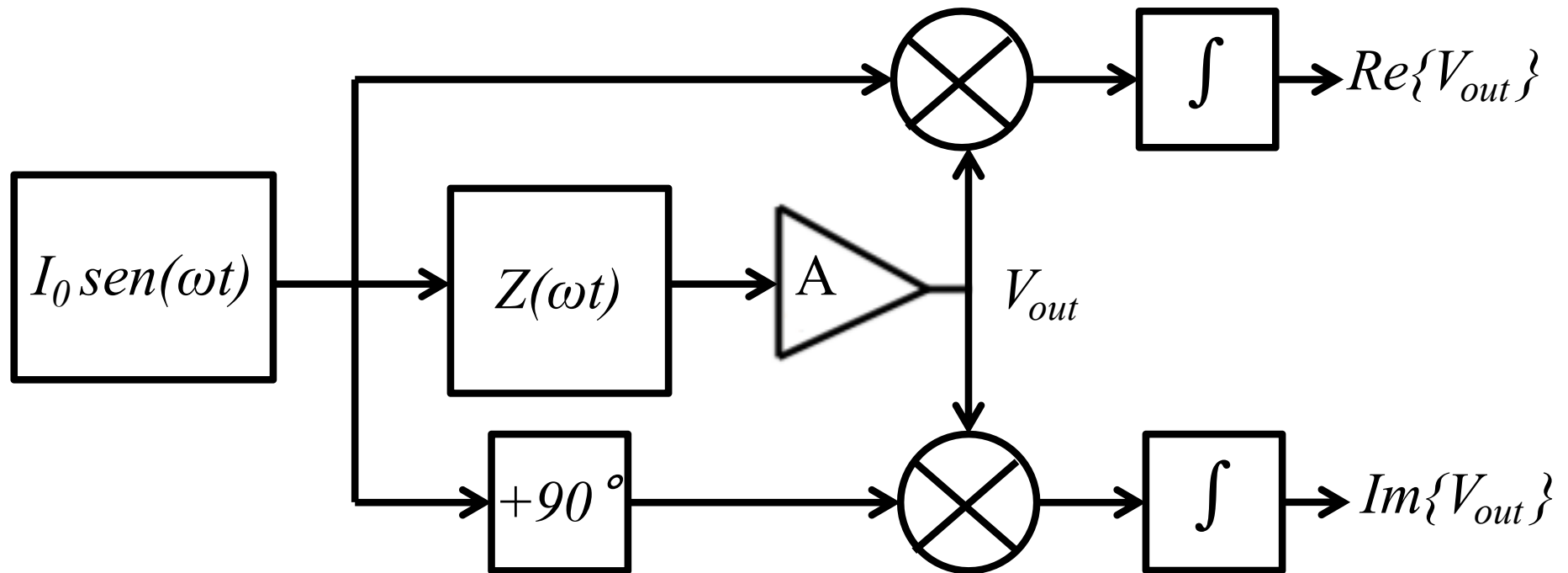

Brain/Machine interfaces

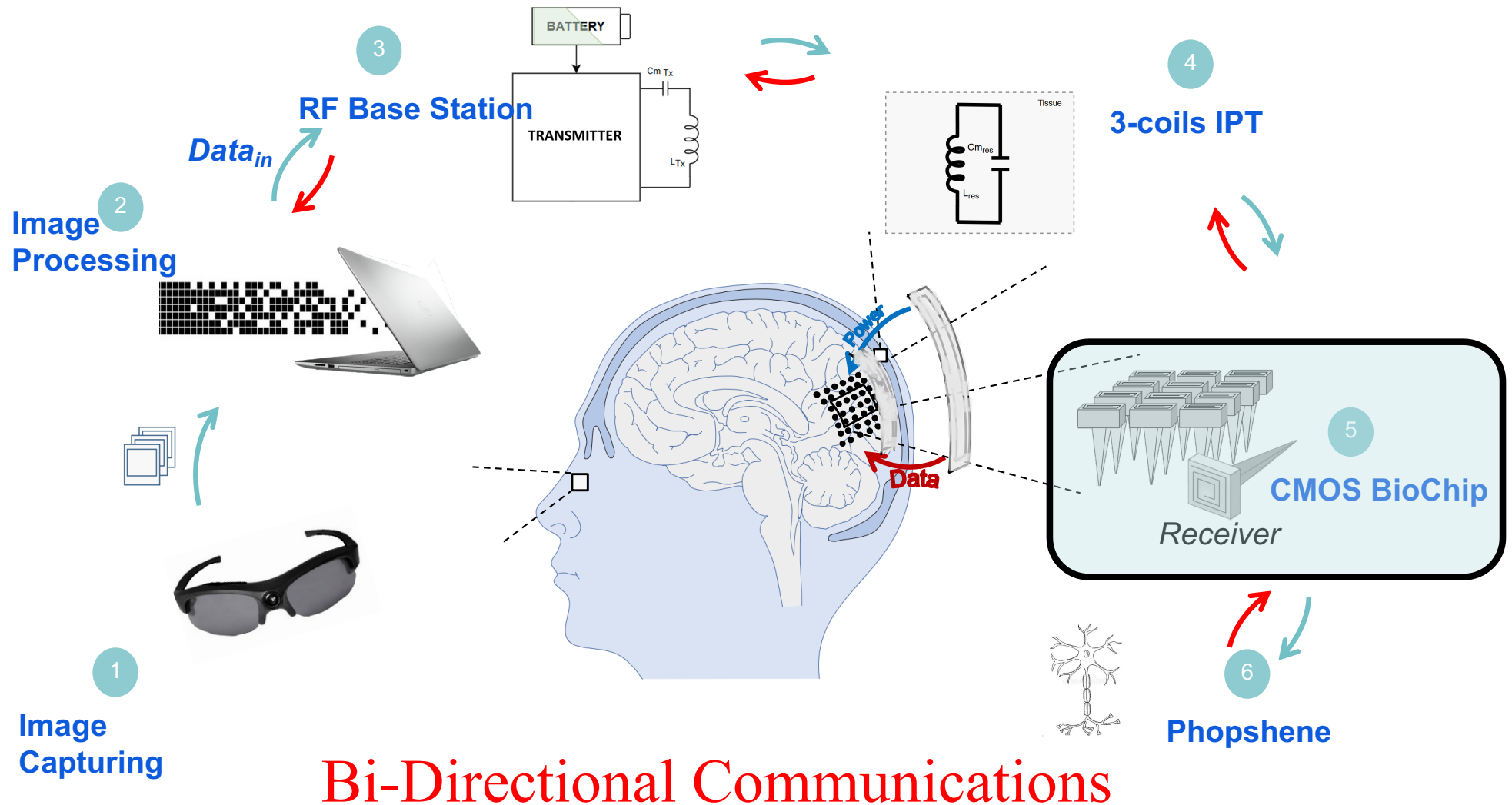

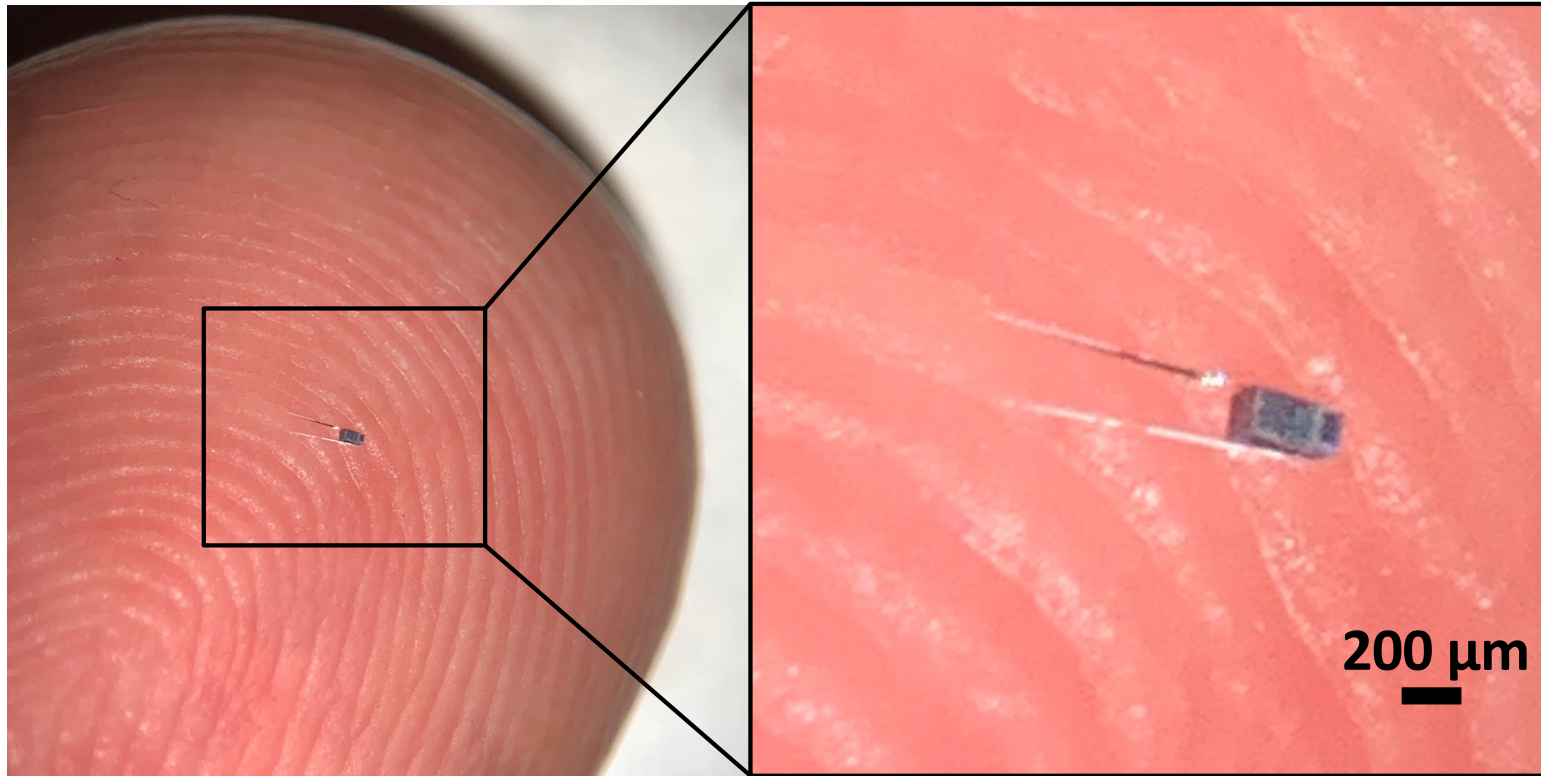CMOS BioChip for Intracortical Visual Stimulation




Barbruni et al., *PCT/IB2022/059944*, 2022

Intracortical BioChip to Vision Restoring in Blind Patients


Cortical Stimulation for Vision

400 μm pitch
1.5 mm deep

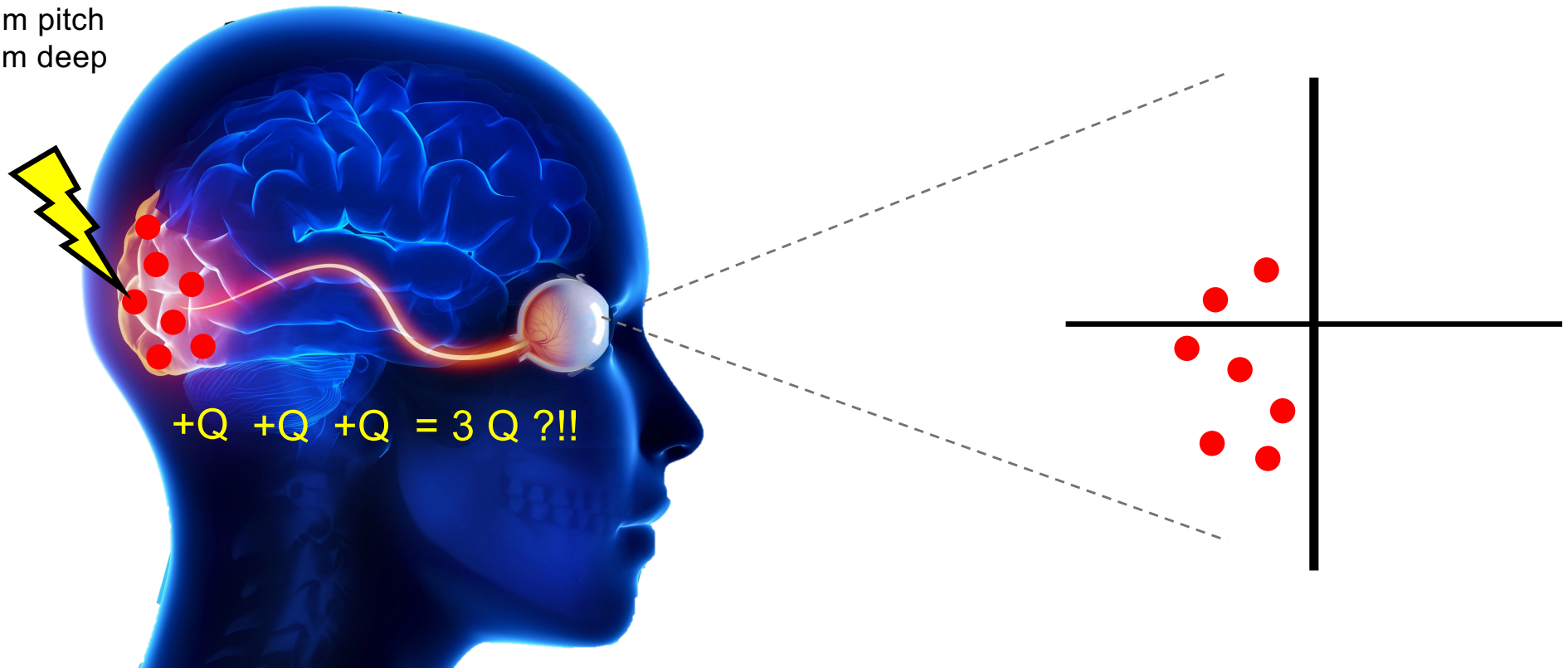


Charges sent to the Cortex need to be Compensated,
not Accumulated!

BioChip Stimulator

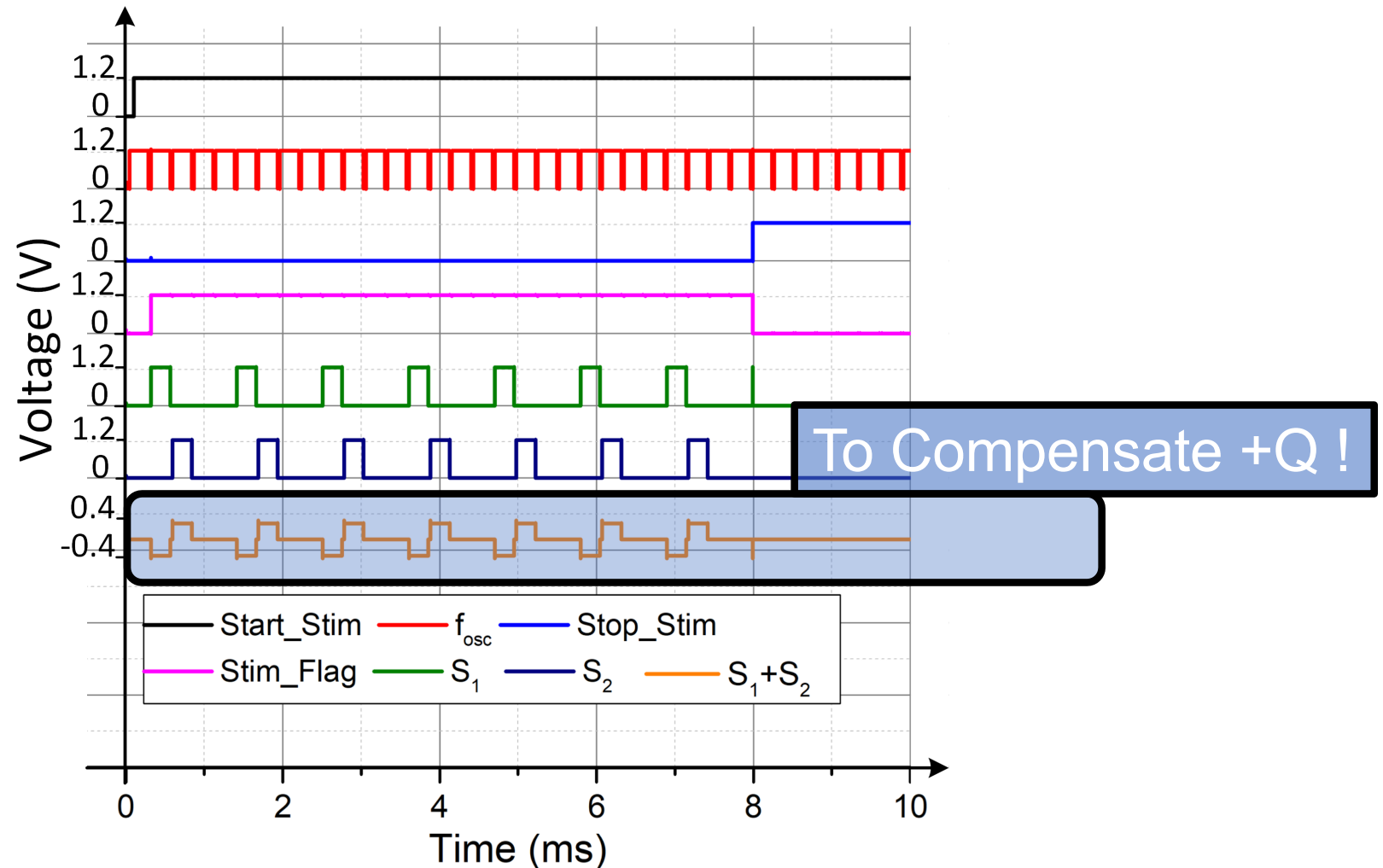


The Identified Logic Signal is now used to Stimulate

BioChip Stimulator

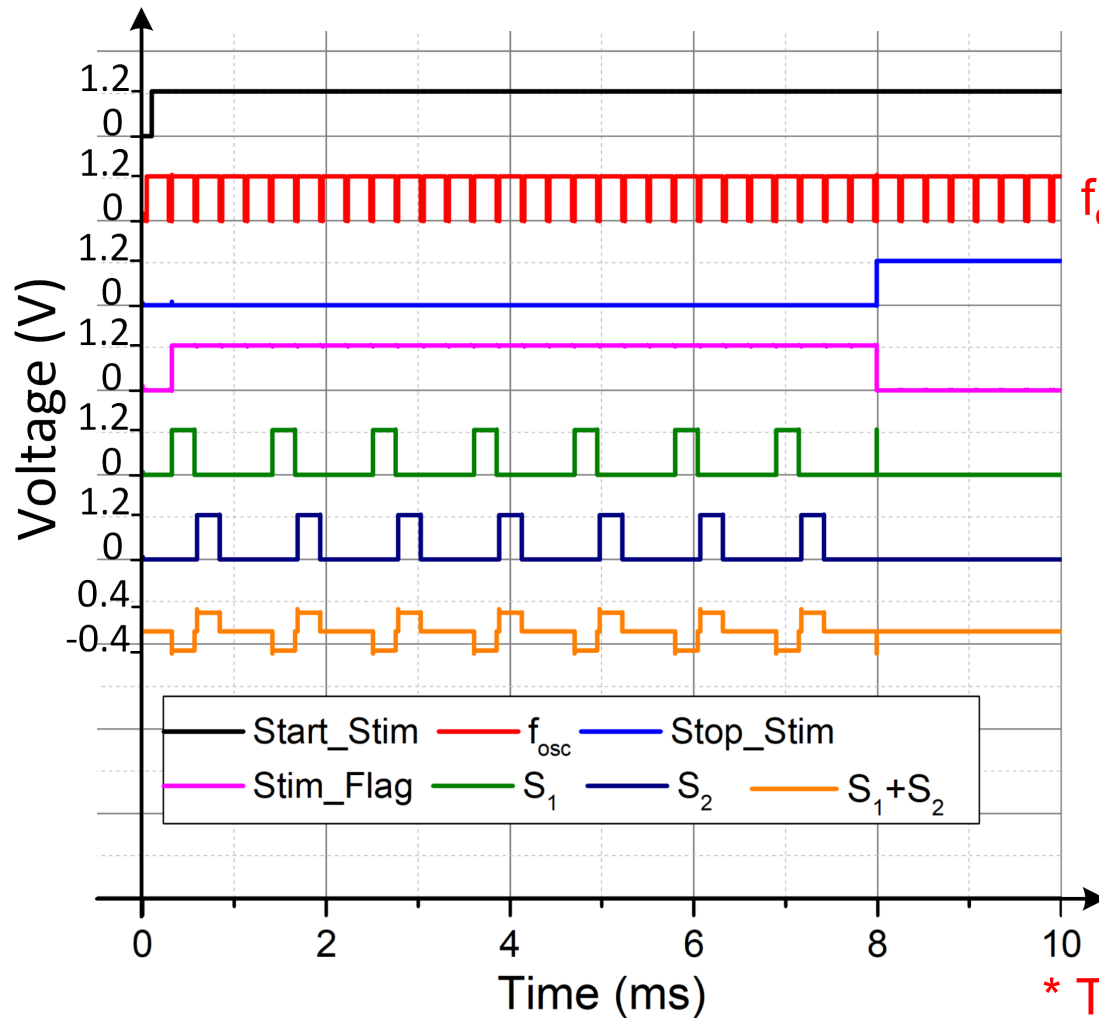


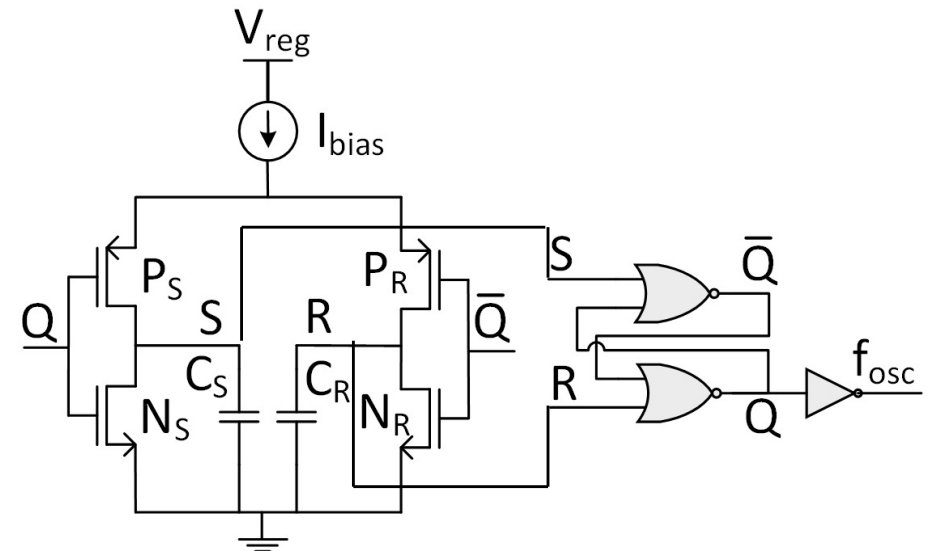I_{bias} is used to charge C_S and C_R in a relaxation* oscillator, while couple of NOR logic gates return the desired pulses for f_{osc}




* The Relaxation Oscillator is a nonlinear electronic oscillator circuit that produces a non-sinusoidal repetitive output signal

BioChip Stimulator


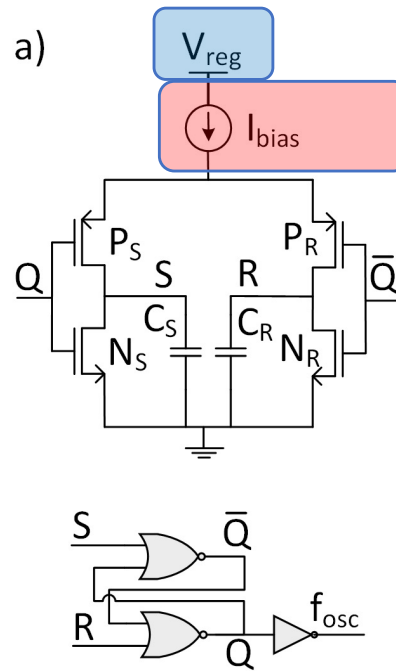


$$f_{osc} \propto \frac{I_{bias}}{(C_S + C_R) \cdot V_{reg}}$$

Current Mirror

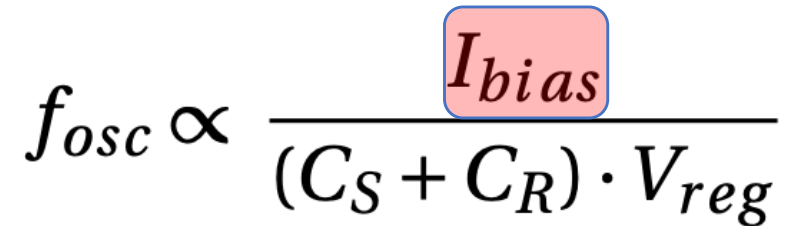



BioChip Stimulator

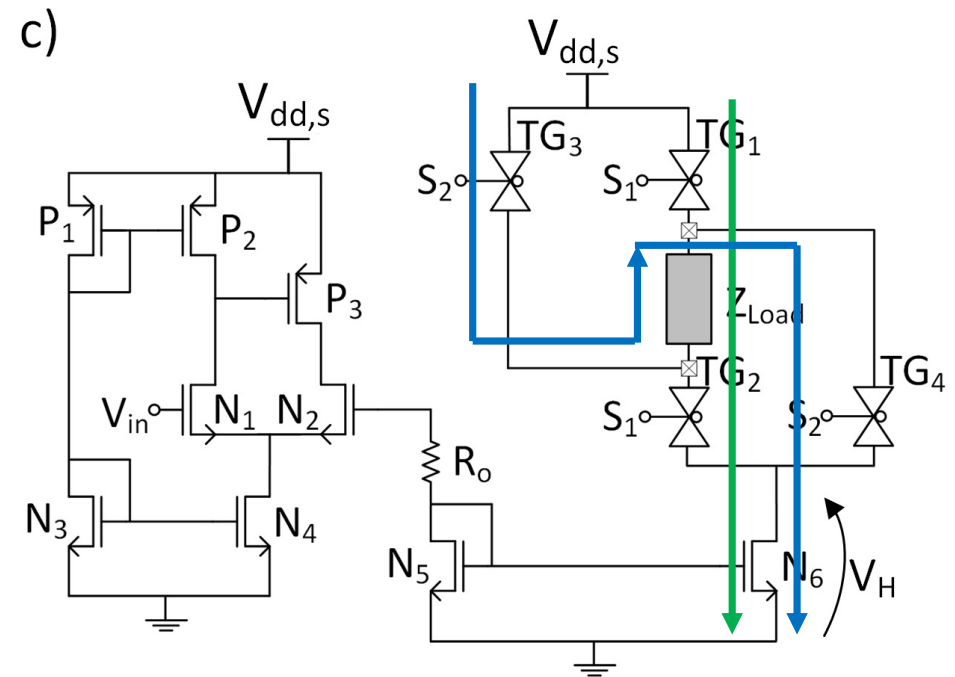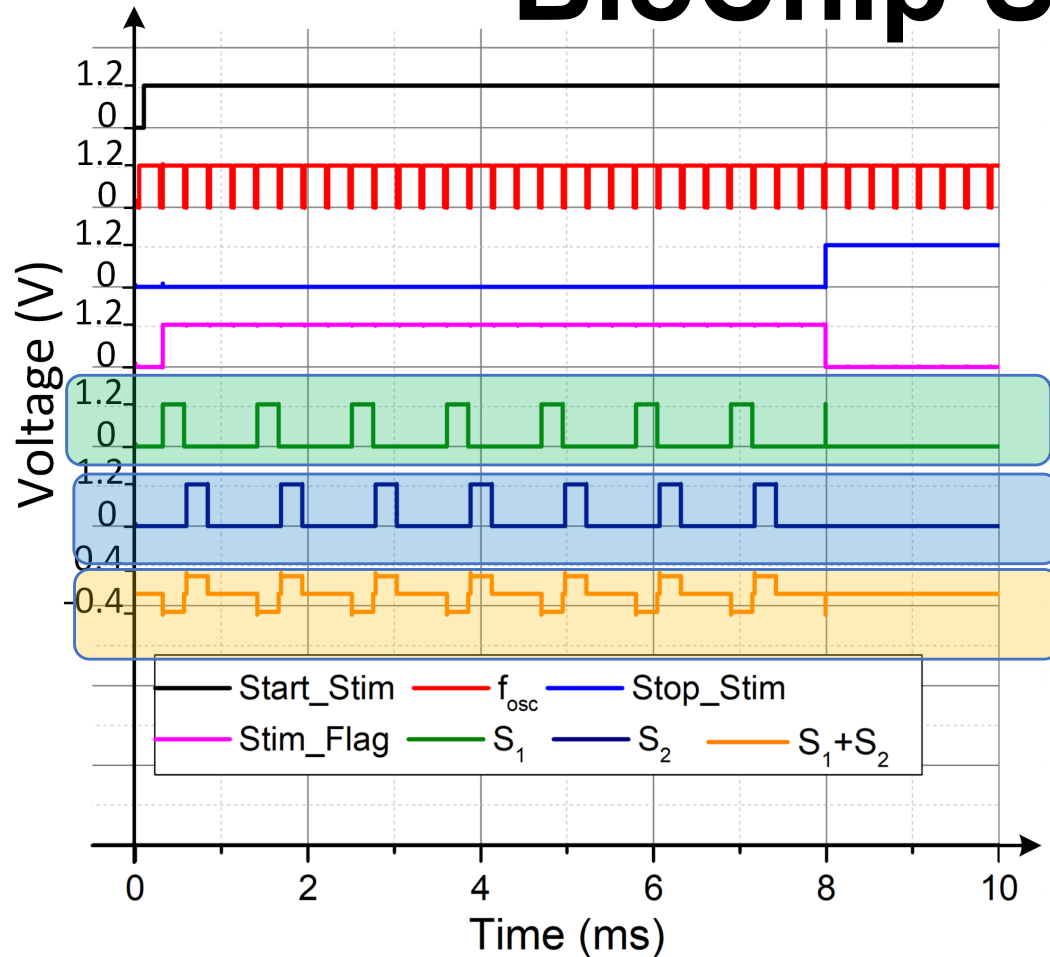

Barbruni et al., *IEEE MOCAST*, 2023

Finally, the H-Bridge provides
the Right Current with the mentioned Q-Compensation

BioChip Stimulator

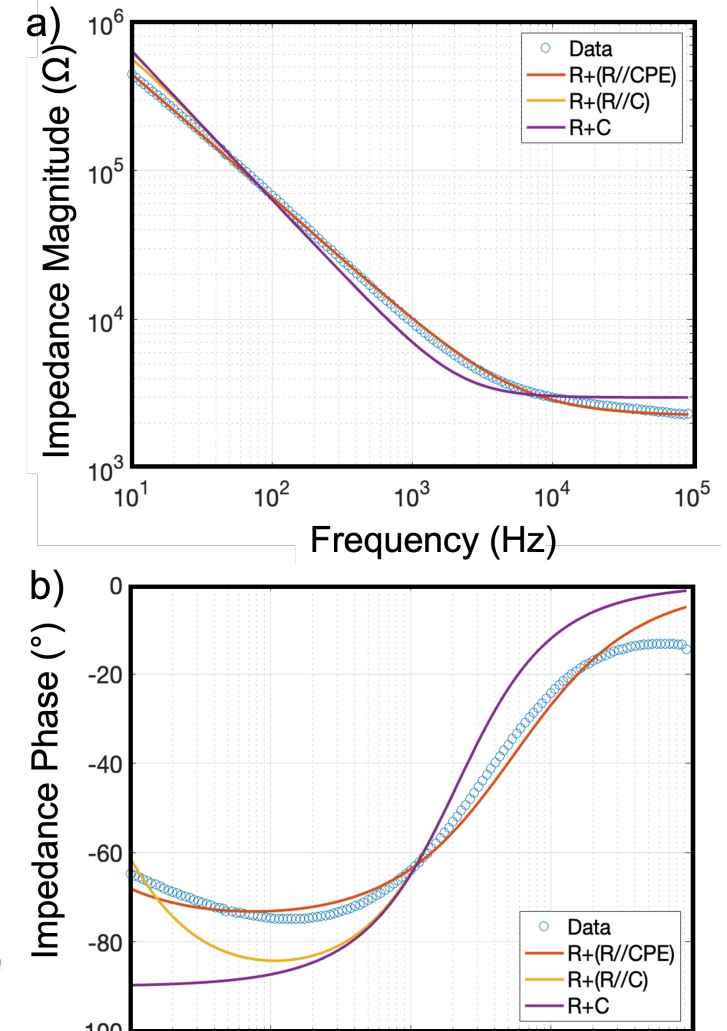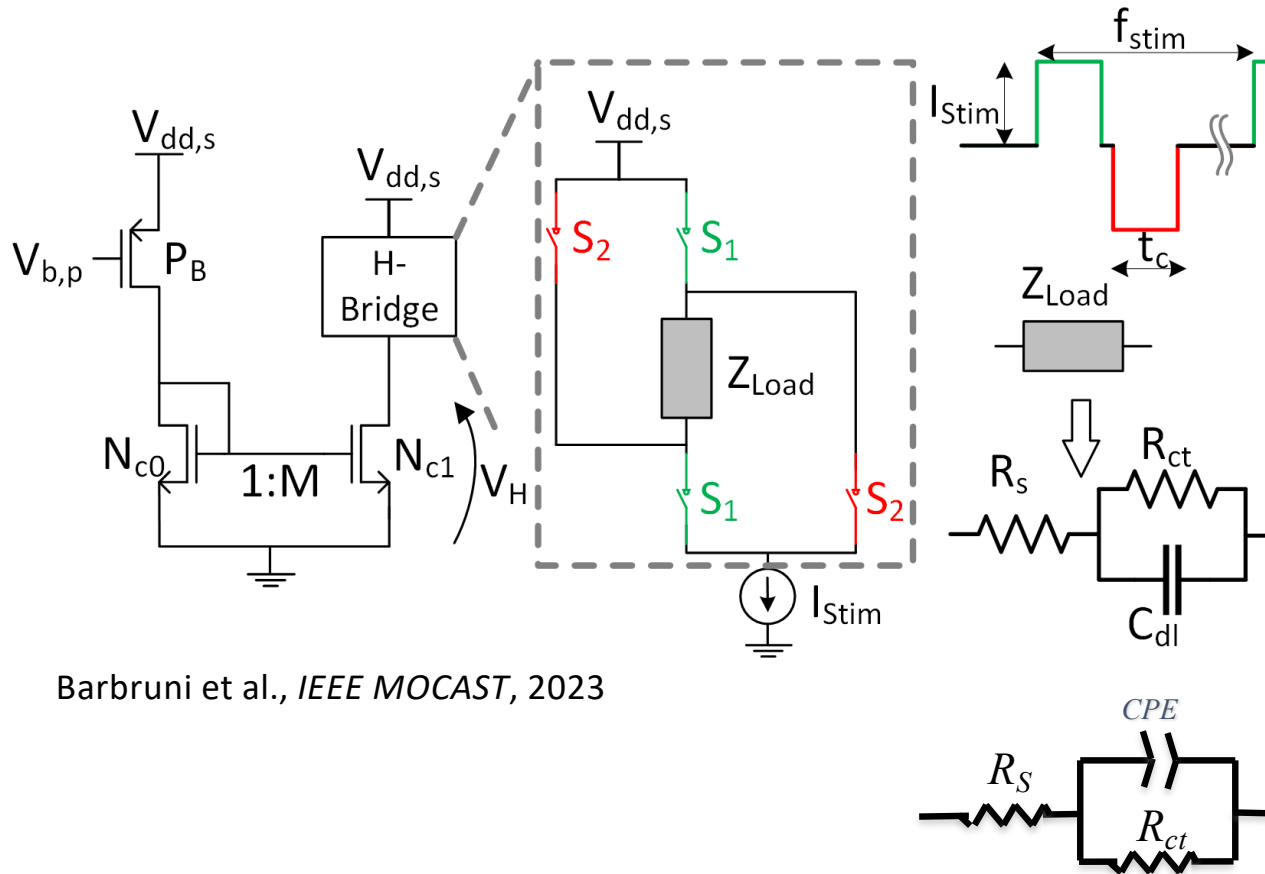

The Simulated Performance changes with Different Bio/CMOS interface models

Get you copy of the Textbooks

Bio/CMOS Interfaces and Co-Design – Springer

link.springer.com/book/10.1007/978-1-4614-4690-3

Sign up / Log in English Academic edition

EPFL ÉCOLE POLYTECHNIQUE FÉDÉRALE DE LAUSANNE

Sandro Carrara

Bio/CMOS Interfaces and Co-Design

Authors: Sandro Carrara

SBN: 978-1-4614-4689-7 (Print) 978-1-4614-4690-3 (Online)

Download Book (7,900 KB)

Search within this book

Table of contents (10 chapters)

Front Matter

» Download PDF (54KB) Pages i-xiv

Book Chapter

Introduction

MyCopy Softcover Edition

24.99 EUR/USD /GBP/CHF

Buy Now

Other actions

Master in Electrical and Electronics Engineering

EE-517: Bio-Nano-Chip Design

Subject of the week	Chapter' paragraphs*
Introduction to Bio-Nano-Chip design, and Conductive Solutions	§1.1-1.5, §2.1-2.7, §2.14-15
Biological molecules: Proteins and DNA building blocks	§3.5-9, §4.13 and §4.17-18
Biological molecules interactions (DNA, Antibodies, Oxidases and Cytochromes)	§4.4-17 and §4.19-23
Biosensors Principle with DNA, Antibodies, and Enzymes	§6.1-4 and §8.2
Biosensors Principle by Redox reactions and Faradaic processes	§8.4-8
Nanotechnology for molecular assembly on chip' surfaces (absorption models)	§5.1
Nanotechnology for checking molecular assembly on chip' surfaces (SPR+ AFM)	§5.2
Nanotechnology to prevent electron transfer	§6.3-7
Nanotechnology to enhance electron transfer in redox reactions	§8.4-8, and 8.3 and 8.9
Chip design for electrochemical sensing: basic configurations and equivalent circuits	§9.1-9.2
Amperometric biosensing in constant-bias (Current-to-Voltage & FTCC Methods)	§9.1.2 and 9.3-5
Amperometric biosensing in voltage-scan (VDCM & DDSM Methods)	§10.3-5
Label-free capacitance detection (CBCM & FTCM Methods)	§7.2-6
Review for final exam	

Bio

Nano

CMOS

* textbook : Sandro Carrara, Bio/CMOS interfaces and Co-Design, Springer publisher, New York, 2013

(c) S.Carrara

Master Projects

<https://www.epfl.ch/labs/iclab/index-html/bci-group/>




Body Dust: CMOS Design for Dopamine monitoring in the Brain

Collaboration with
Imperial Collage London

Master Projects

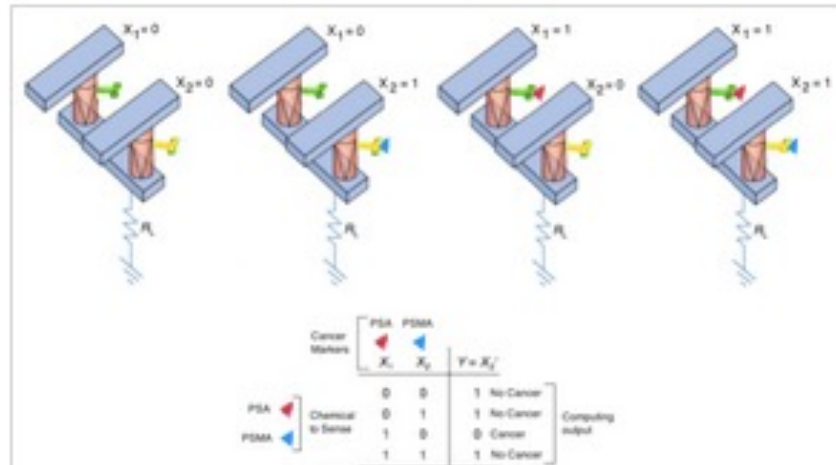
<https://www.epfl.ch/labs/iclab/index-html/bci-group/>



in-Memory
Sensing:
Computing done
in the sensors, not
close to the sensor

Master Projects
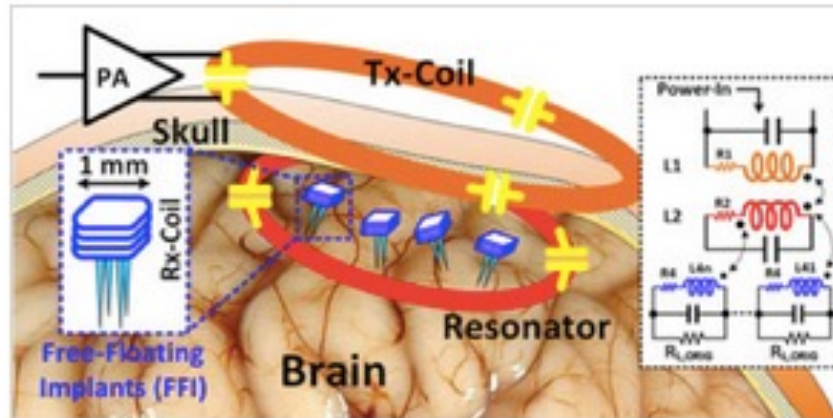
<https://www.epfl.ch/labs/iclab/index-html/bci-group/>




Challenges in sub-
millimetric
Neurostimulators
Wirelessly
Powered via highly
efficient Inductive
Links

Collaboration with
Politecnico di Torino

Master Projects
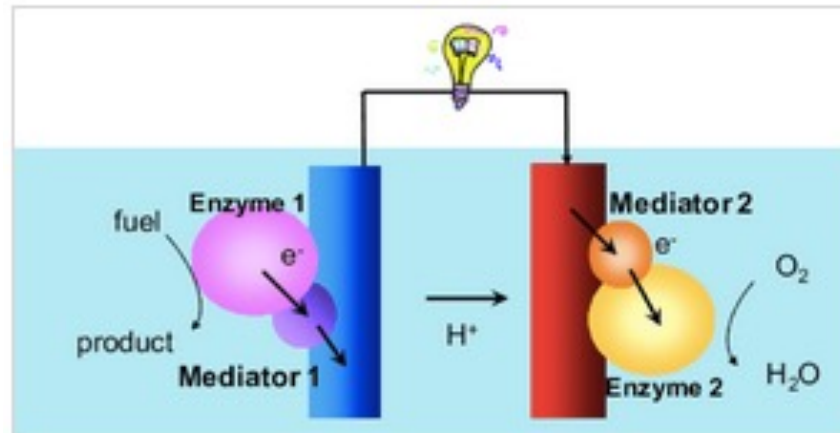
<https://www.epfl.ch/labs/iclab/index-html/bci-group/>



Self-Wake-Up
Device for
Therapeutic
Compounds on
Human Skin

Collaboration with
ST Microelectronics