
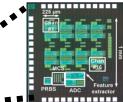


*Integrated Neurotechnologies
Laboratory*

EPFL

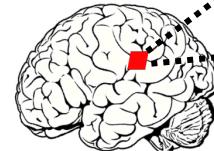



Advanced analog integrated circuit design (EE-523), Lecture 2

Prof. Mahsa Shoaran

Institutes of Electrical and Micro Engineering and Neuro-X, School of Engineering, EPFL

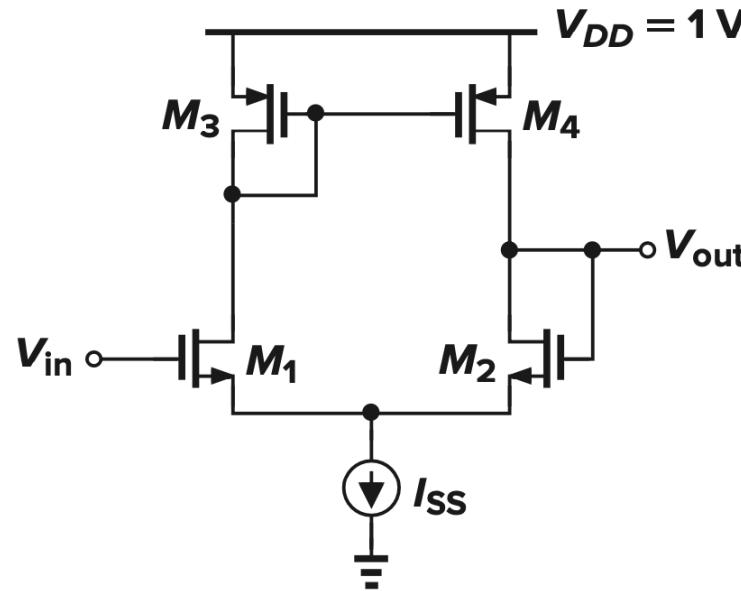
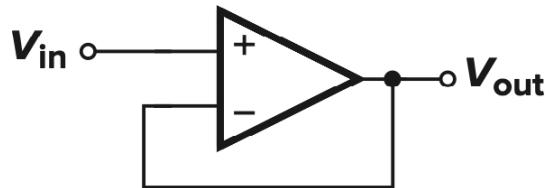
Example: Input CM Range and Output Impedance

- Find the input common-mode voltage range and closed-loop output impedance of the unity-gain buffer shown below. Assume $V_{th} = 0.3V$ and $V_{od} = 0.1V$.



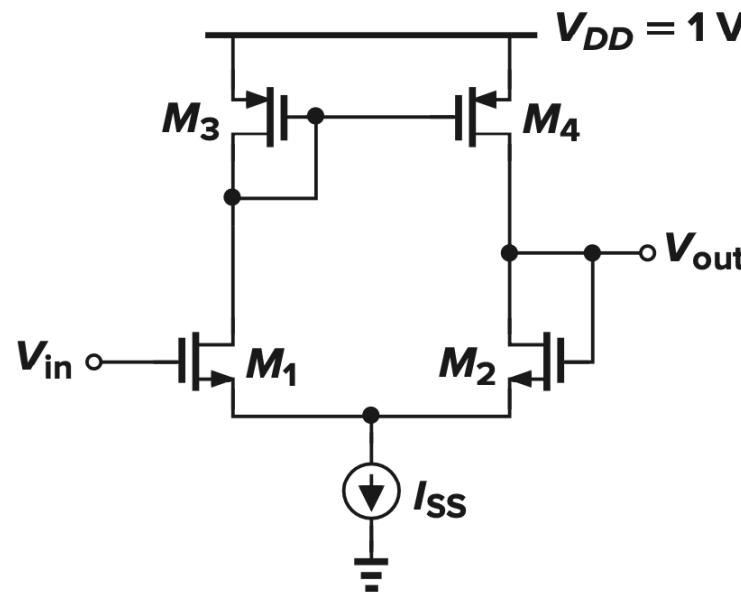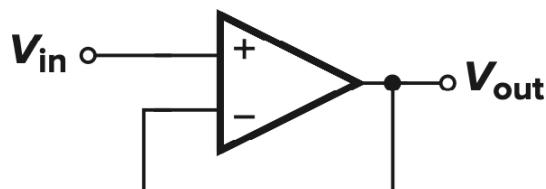Example: Input CM Range and Output Impedance

- Find the input common-mode voltage range and closed-loop output impedance of the unity-gain buffer shown below. Assume $V_{th} = 0.3V$ and $V_{od} = 0.1V$.





$$V_{ISS} + V_{GS1} \longrightarrow V_{DD} - |V_{GS3}| + V_{TH1}$$

$$(r_{OP} \| r_{ON})/[g_{mN}(r_{OP} \| r_{ON})] = 1/g_{mN}$$

One-Stage Op amps with Higher Gain: Cascode

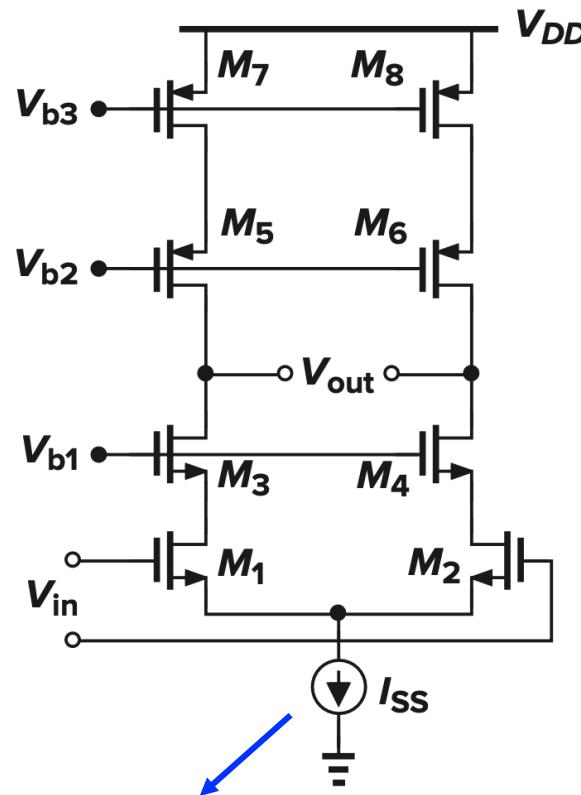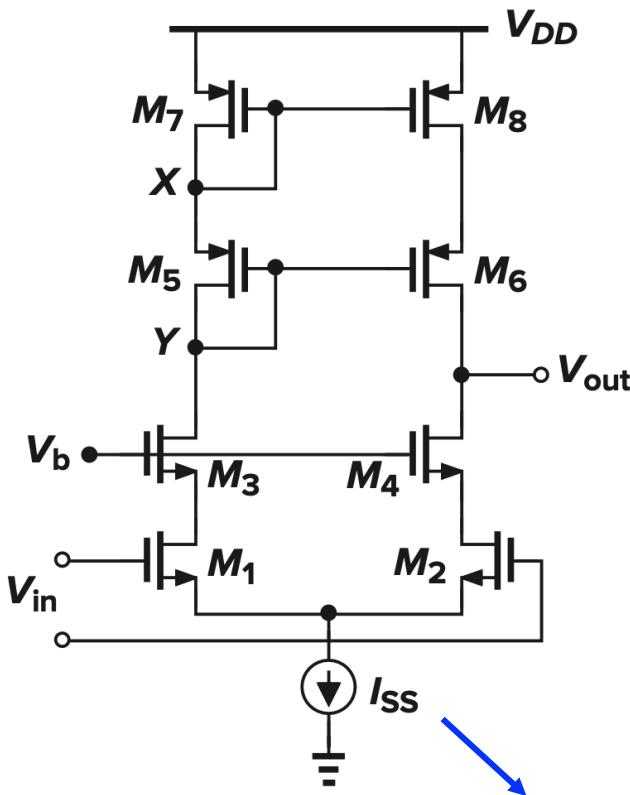
- Telescopic cascode with **single-ended** and **differential** outputs
- High gain at the cost of output swing and additional poles



$$g_{mN}[(g_{mN}r_{ON}^2) \parallel (g_{mP}r_{OP}^2)]$$



Cascode Op Amp

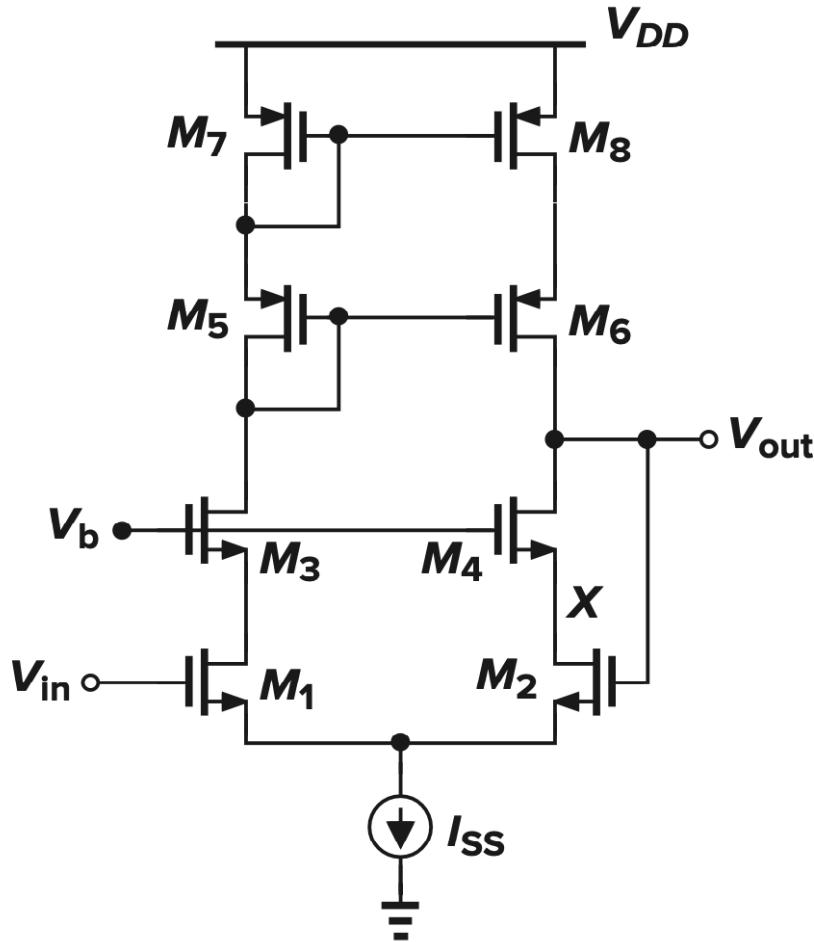- Difficult to use as a unity-gain buffer: limited output range
- **Op Amp design procedure** will be practiced during the TP sessions




Cascode Op Amp

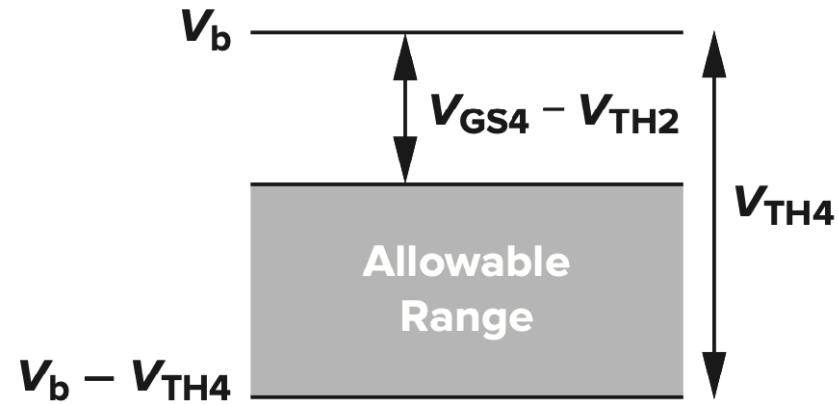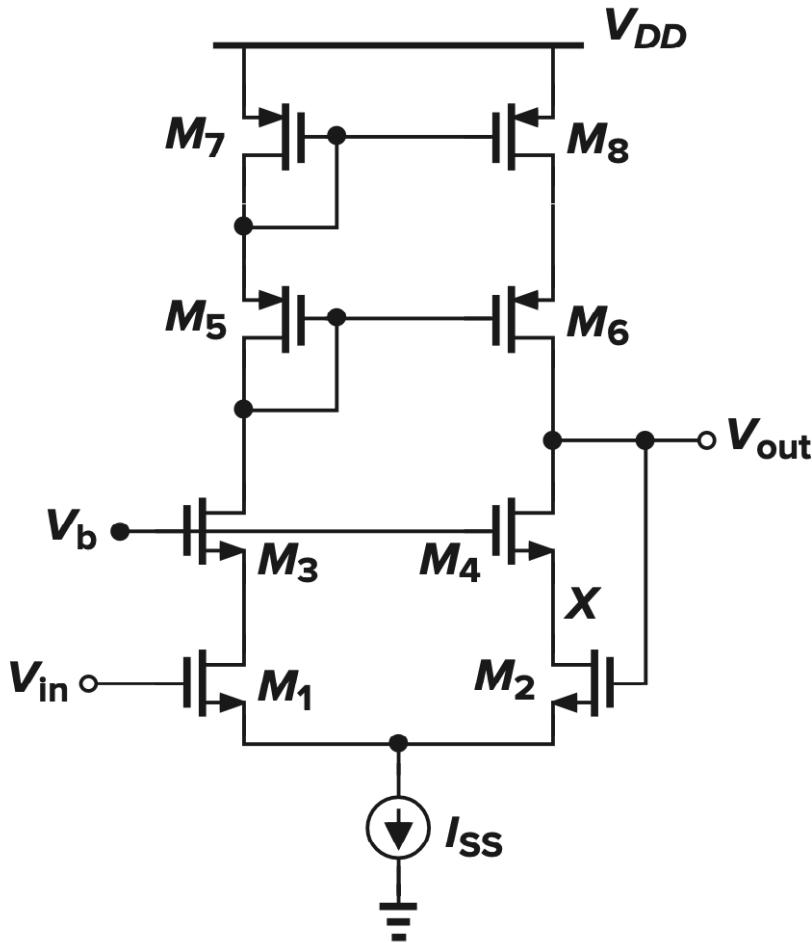- Difficult to use as a unity-gain buffer: limited output range
- Op Amp design procedure** will be practiced during the TP sessions




Folded-Cascode Op Amp

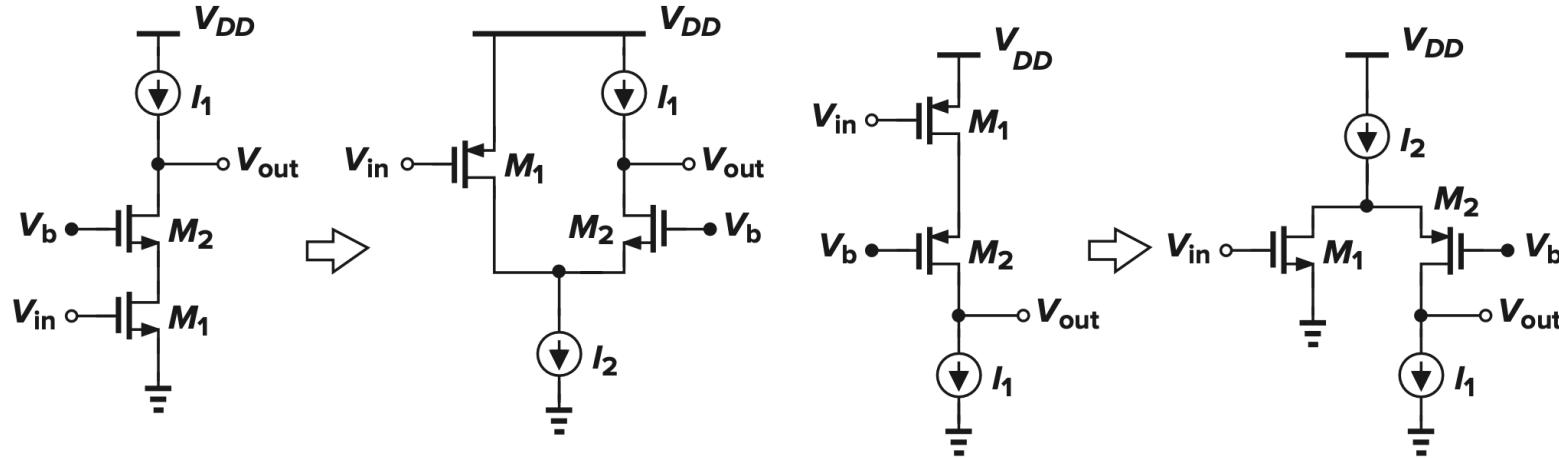- Folded structure: To address the limited output swing and difficulty in choosing equal input and output CM levels for the telescopic cascode




Folded-Cascode Op Amp

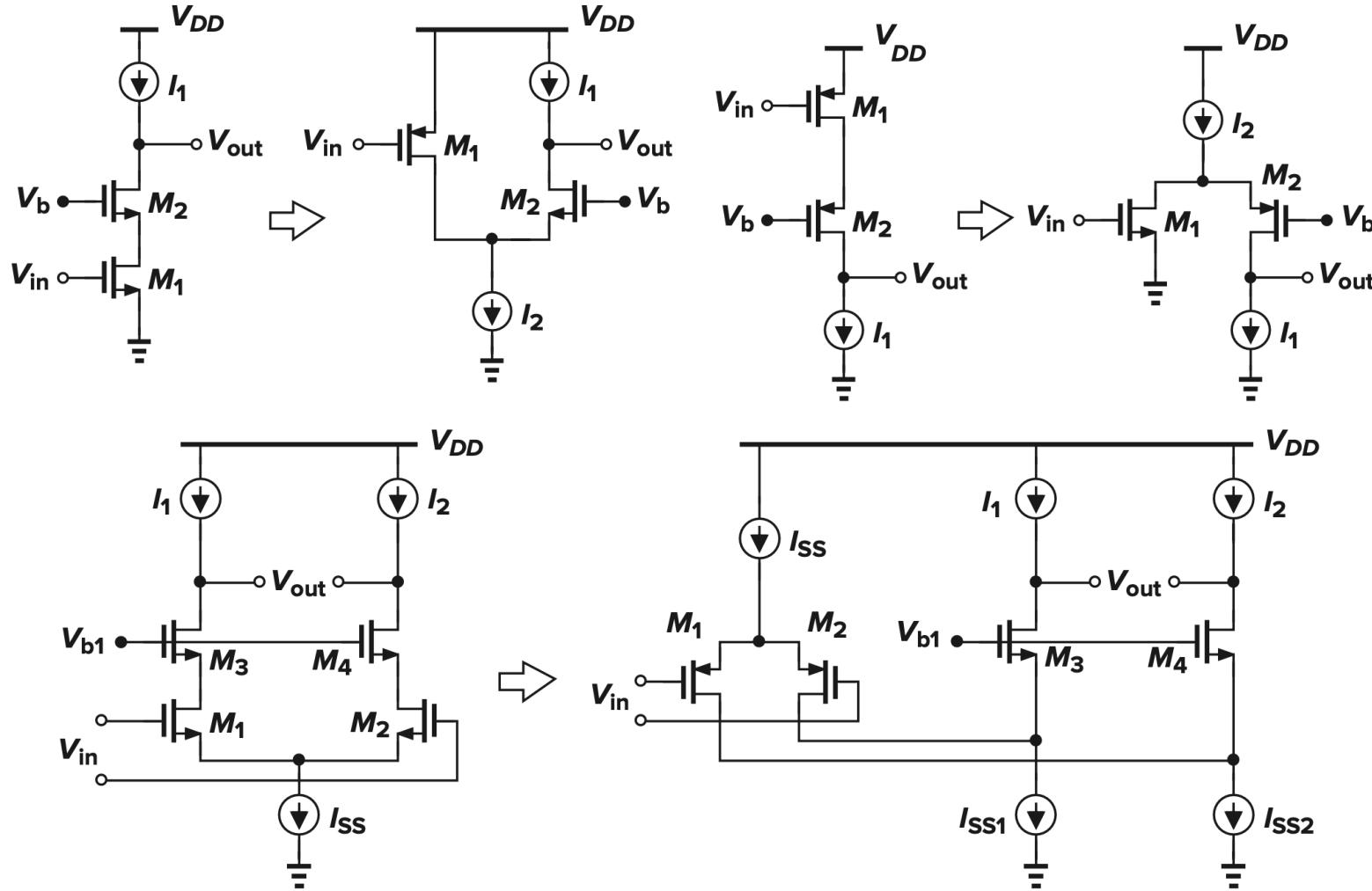- Folded structure: To address the limited output swing and difficulty in choosing equal input and output CM levels for the telescopic cascode



Folded-Cascode: Maximum output swing


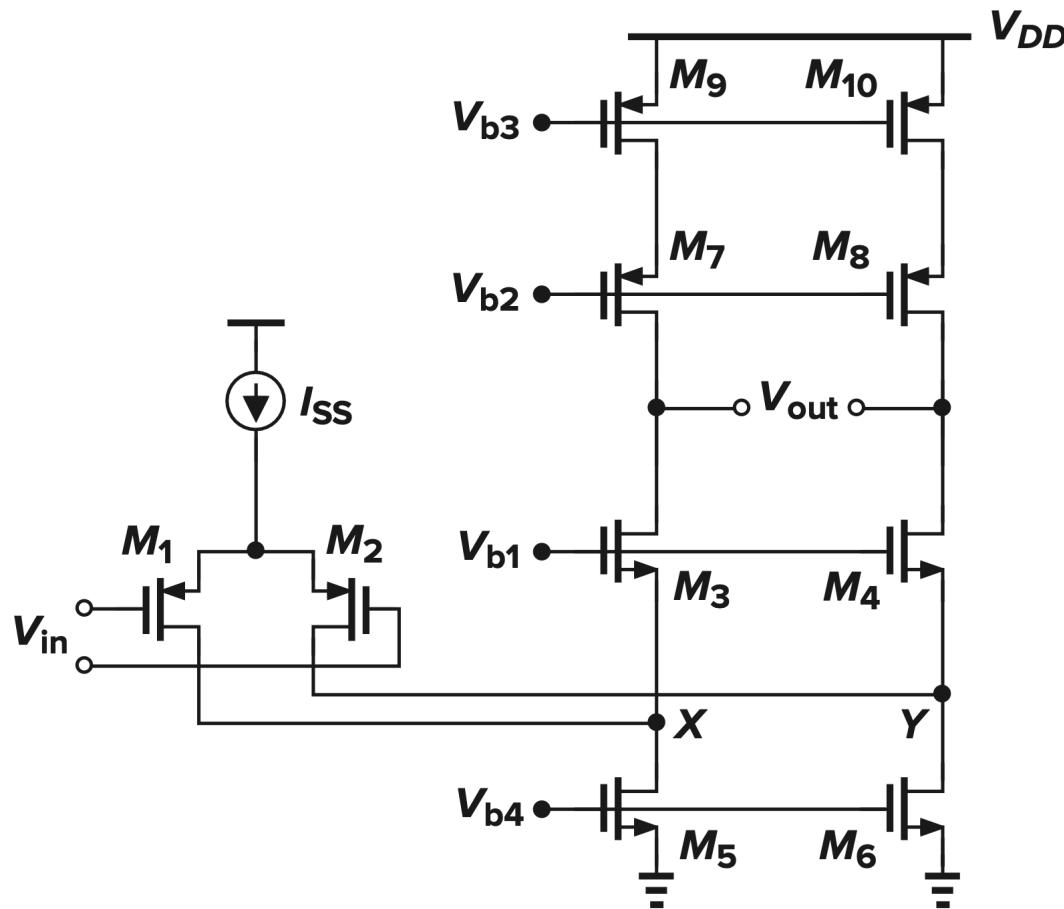


- Single-ended output swing:

$$V_{DD} - (V_{OD3} + V_{OD5} + |V_{OD7}| + |V_{OD9}|)$$





Folded-Cascode: Voltage gain

Half-circuit

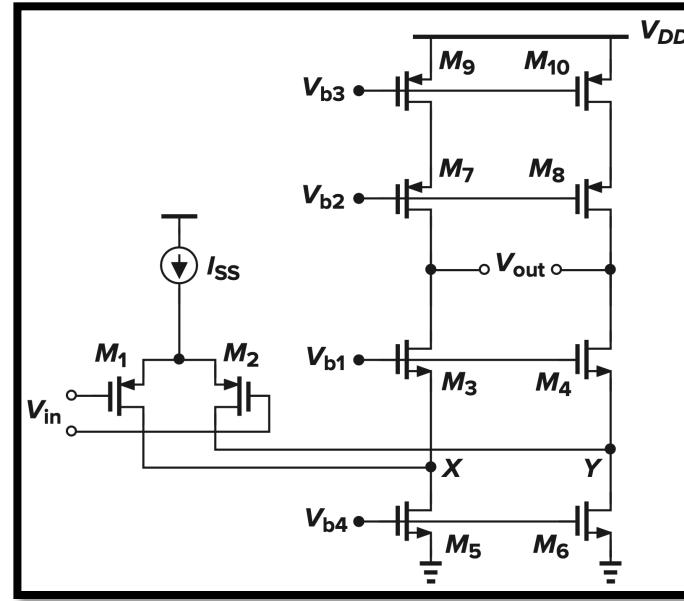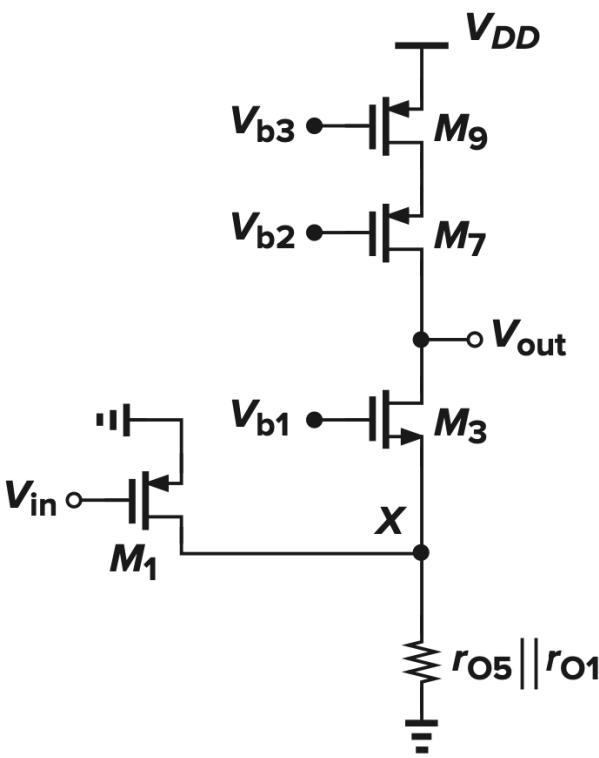

Folded-Cascode: Voltage gain





Half-circuit

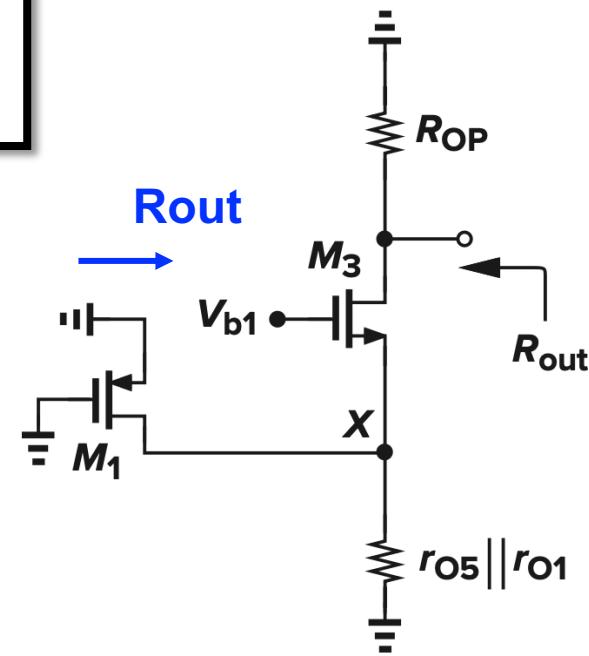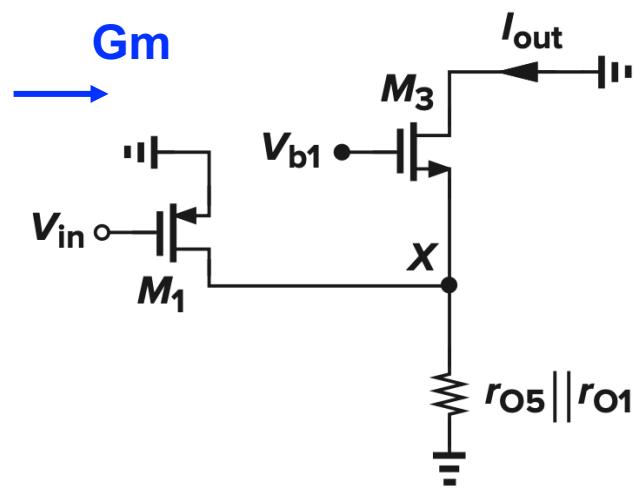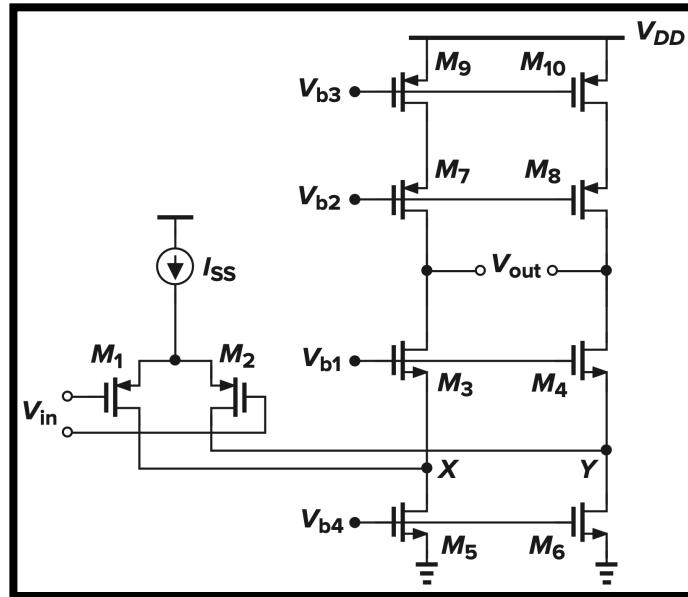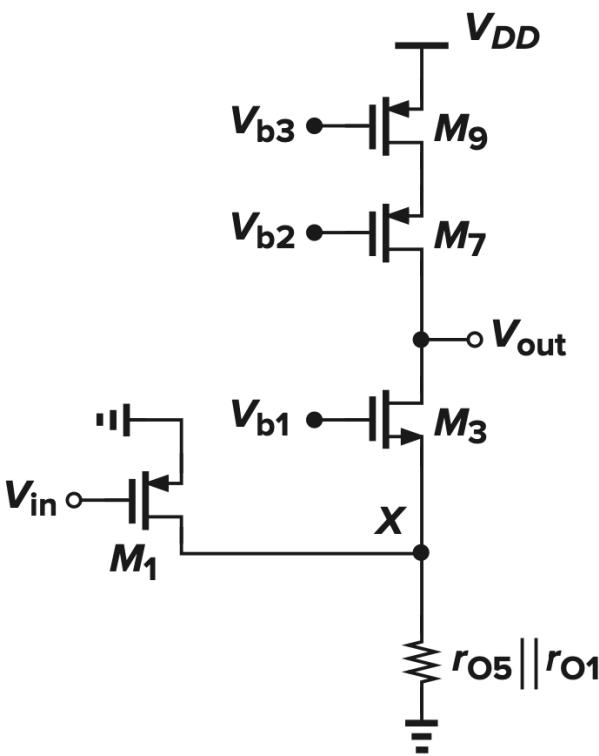

$$|A_v| = G_m R_{out}$$

Folded-Cascode: Voltage gain


Half-circuit

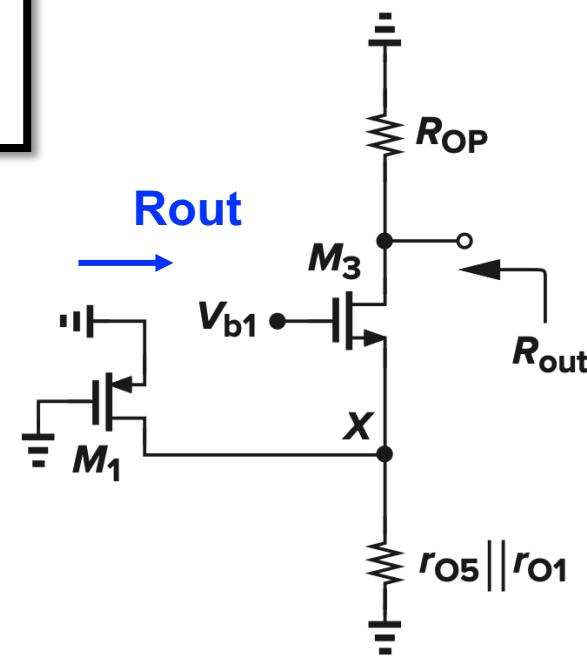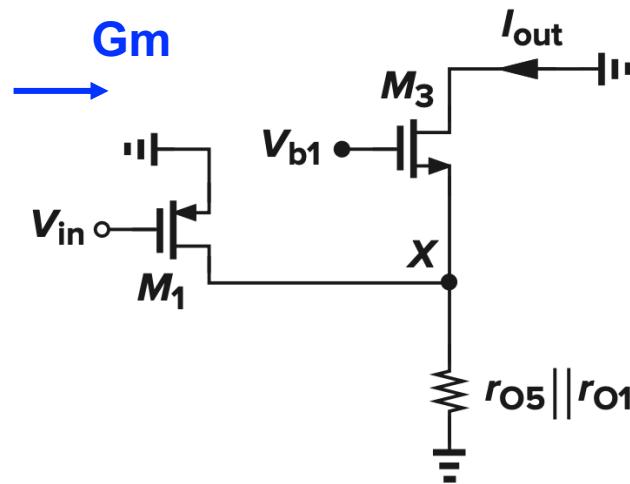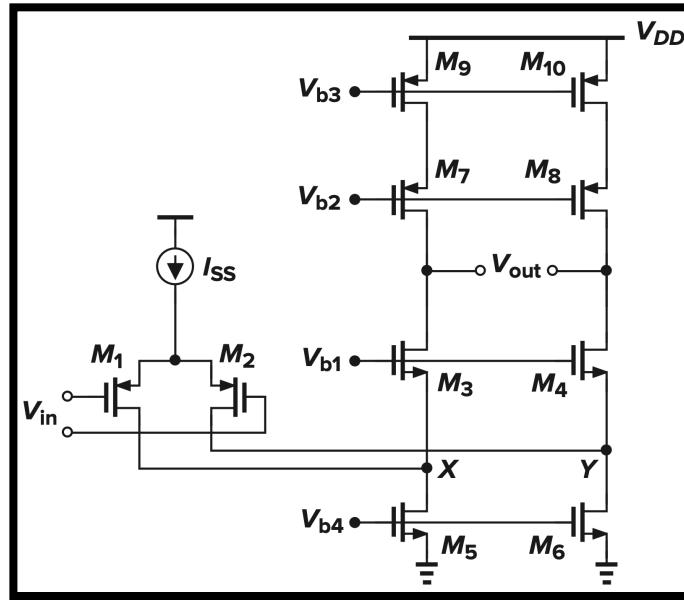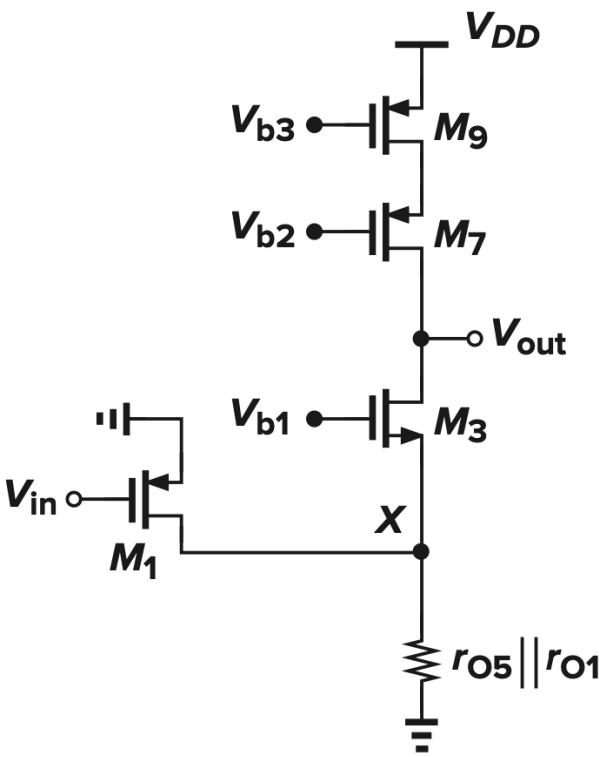


$$|A_v| \approx g_{m1}\{[(g_{m3} + g_{mb3})r_{O3}(r_{O1}\|r_{O5})]\|[(g_{m7} + g_{mb7})r_{O7}r_{O9}]\}$$

Folded-Cascode: Nondominant pole location

Telescopic Cadcode

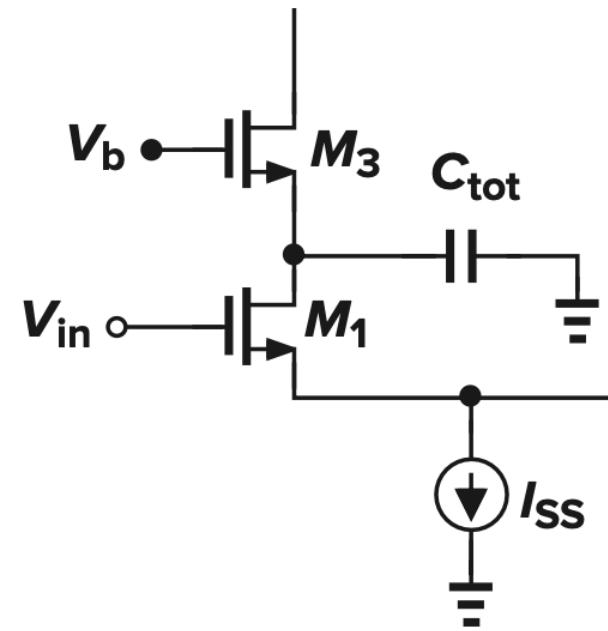


Folded Cadcode

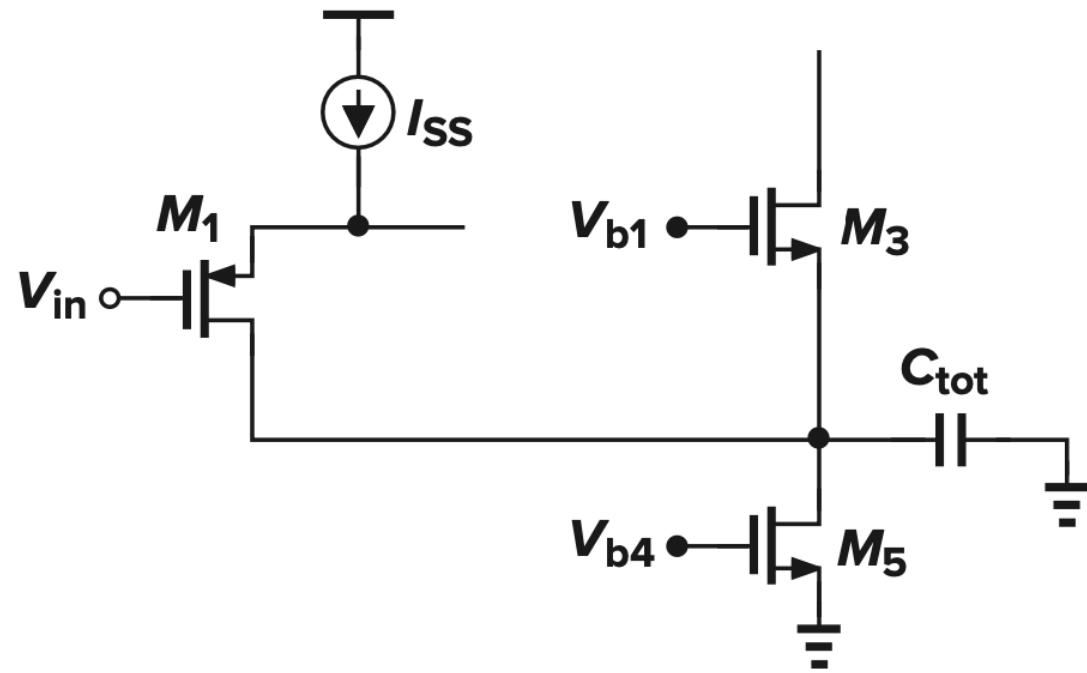


Folded-Cascode with NMOS input pair

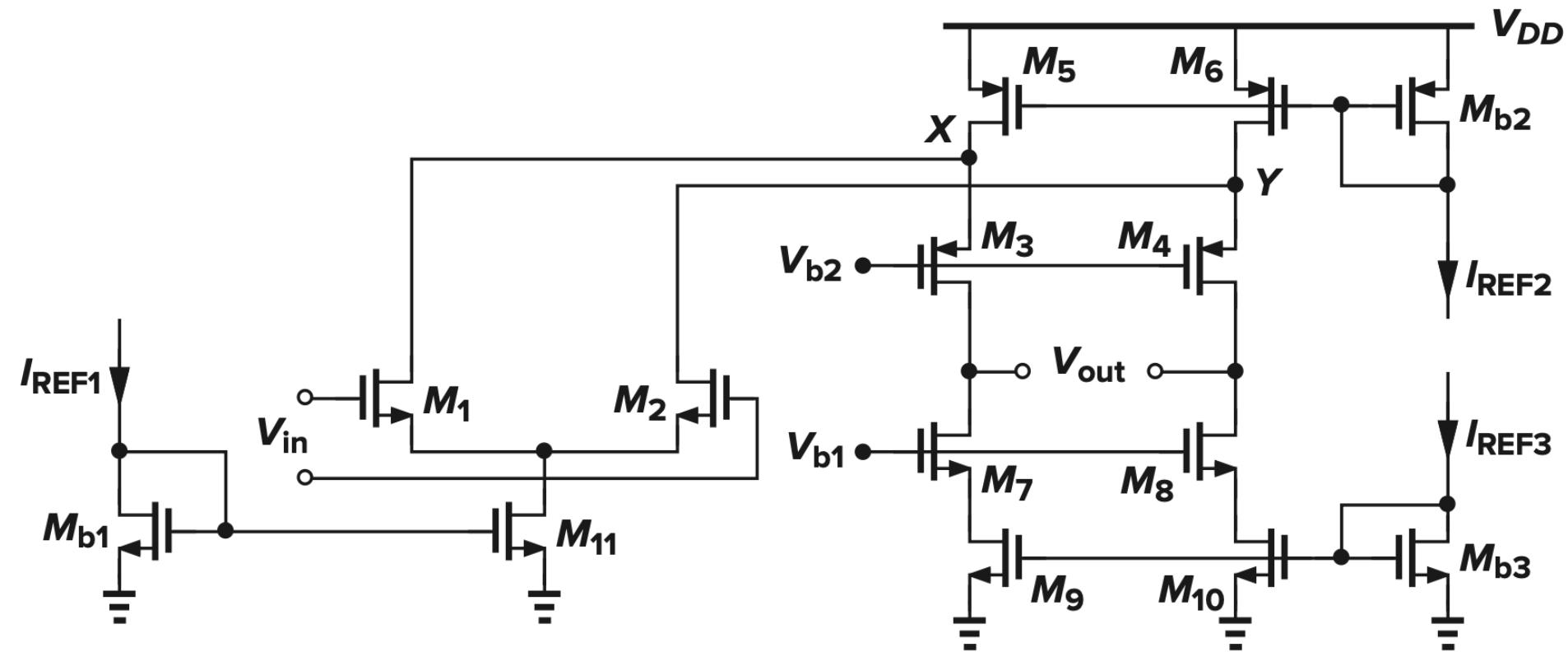- Folded cascode with **NMOS input devices**: Higher gain




Folded-Cascode Advantages

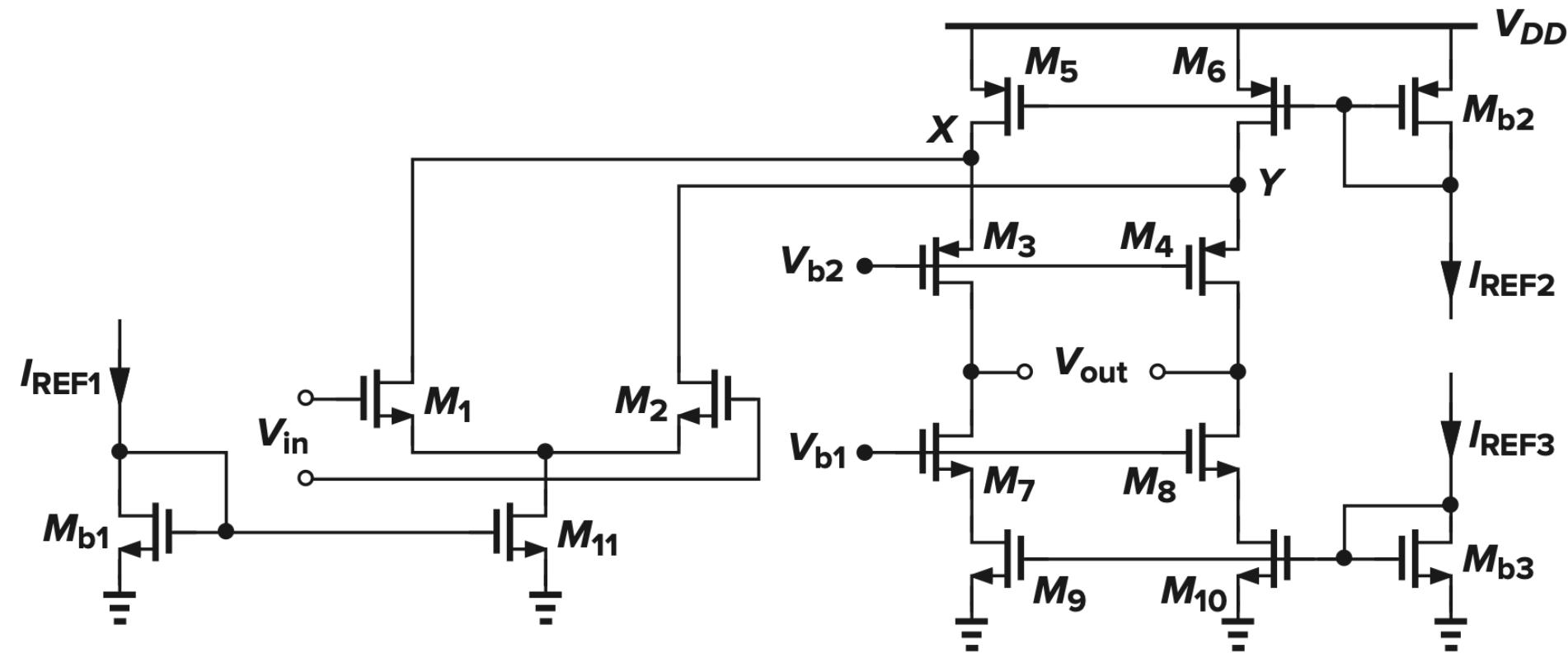- Folded-cascode op amps are used more widely than telescopic because:
(1) Input & output CM levels can be chosen equal without limiting output swing
(2) They can accommodate a wider input CM range



Two-Stage Op Amps

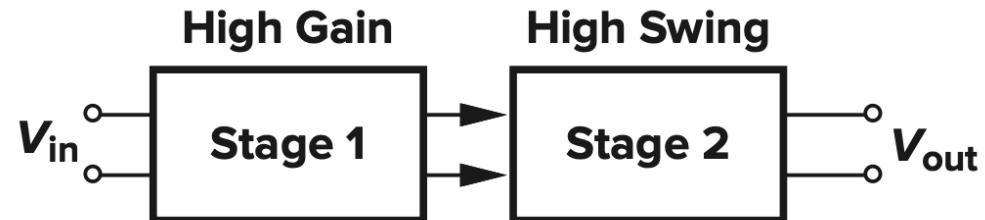- In contrast to cascode op amps, a two-stage configuration isolates the gain and swing requirements.




$$g_{m1,2}(r_{O1,2} \parallel r_{O3,4})$$


\times

$$g_{m5,6}(r_{O5,6} \parallel r_{O7,8})$$

$$V_{DD} - |V_{OD5,6}| - V_{OD7,8}$$

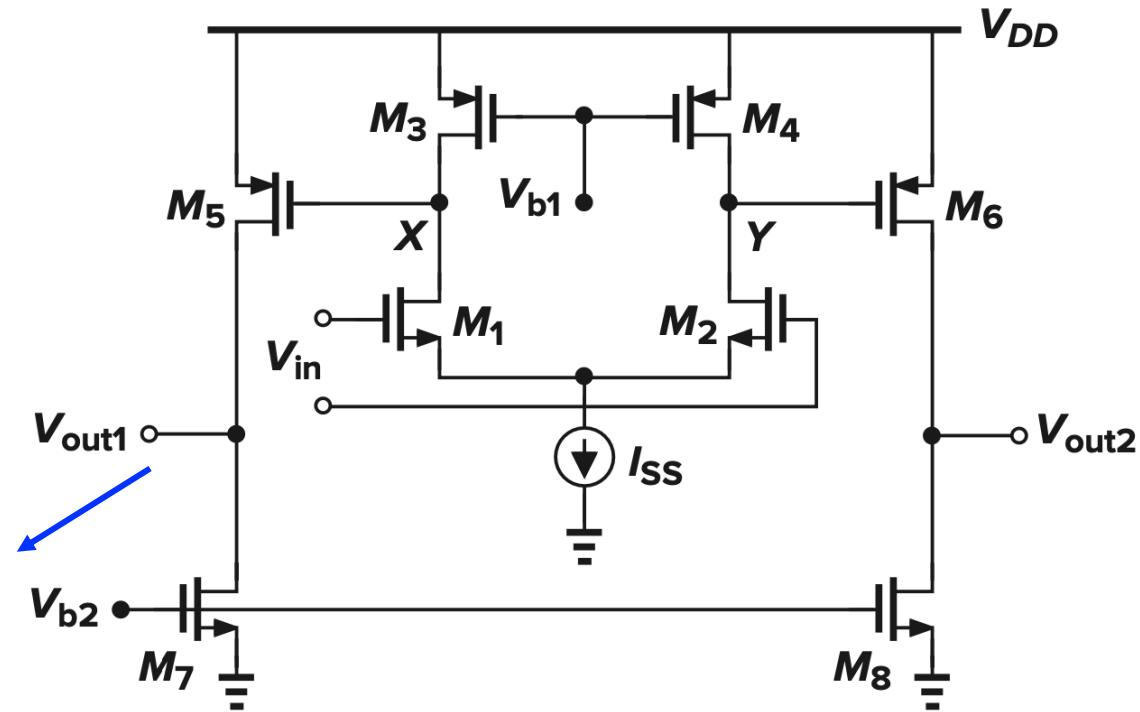


Two-Stage Op Amps

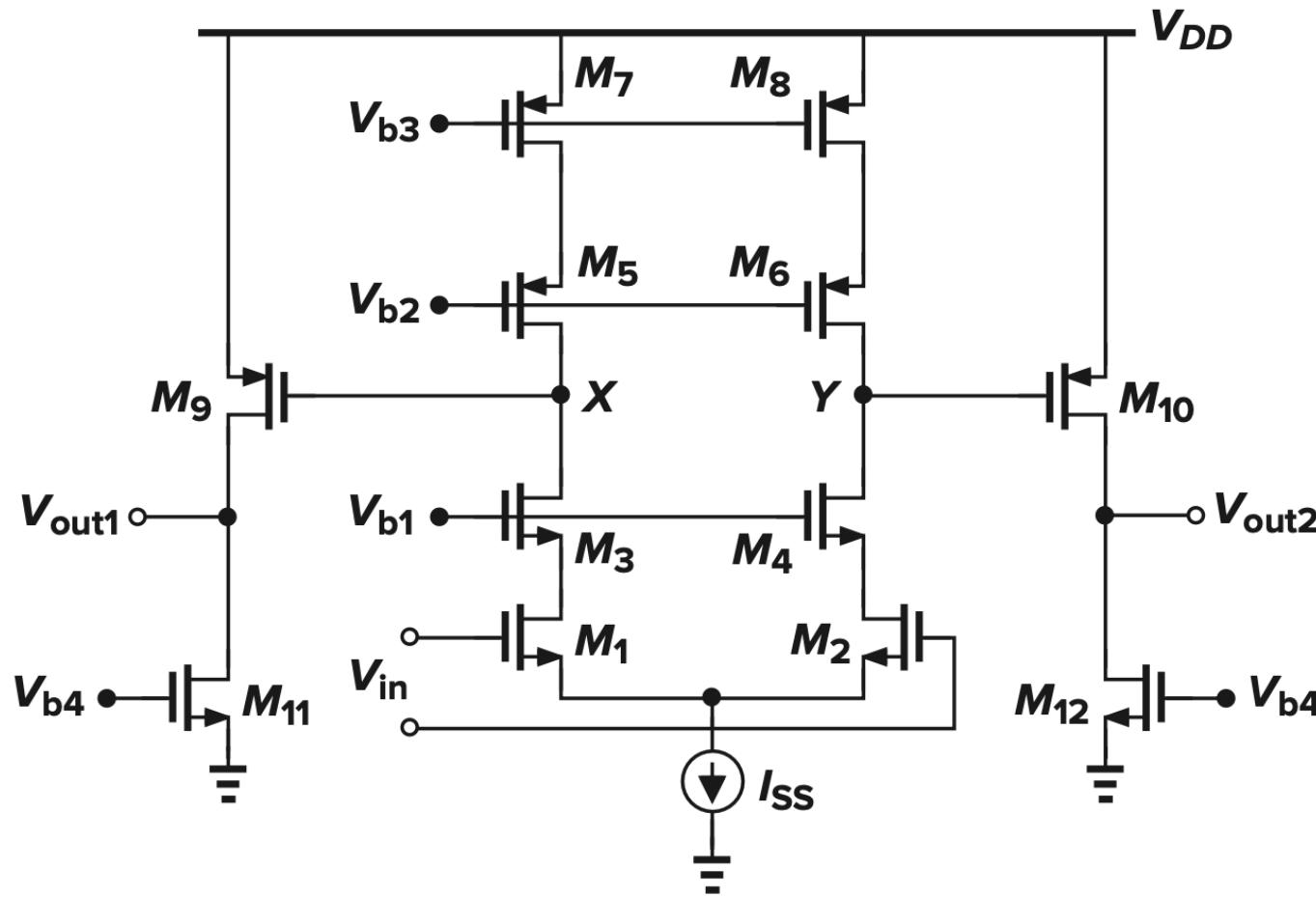

$$\begin{aligned}
 A_v \approx & \{g_{m1,2}[(g_{m3,4} + g_{mb3,4})r_{O3,4}r_{O1,2}]\|[(g_{m5,6} + g_{mb5,6})r_{O5,6}r_{O7,8}]\} \\
 & \times [g_{m9,10}(r_{O9,10}\|r_{O11,12})]
 \end{aligned}$$


Gain Boosting

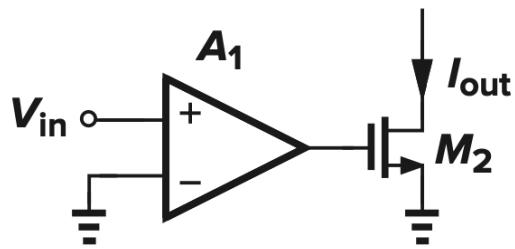- Motivation: The limited gain of the one-stage op amps and the difficulties in using two-stage op amps at high speeds necessitate new topologies
- The idea behind gain boosting is to increase the output impedance **without adding more cascode devices**




Gain Boosting

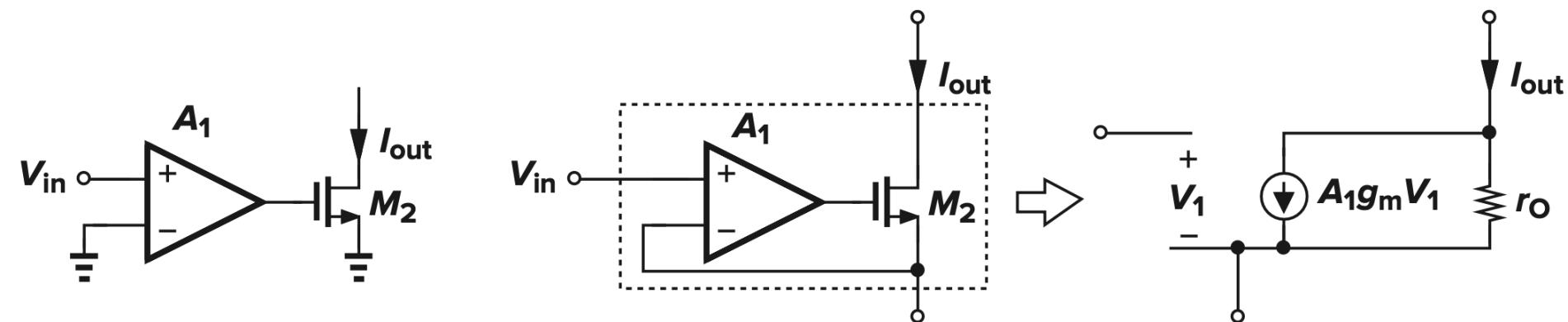- Motivation: The limited gain of the one-stage op amps and the difficulties in using two-stage op amps at high speeds necessitate new topologies
- The idea behind gain boosting is to increase the output impedance **without adding more cascode devices**




Gain Boosting: Gm

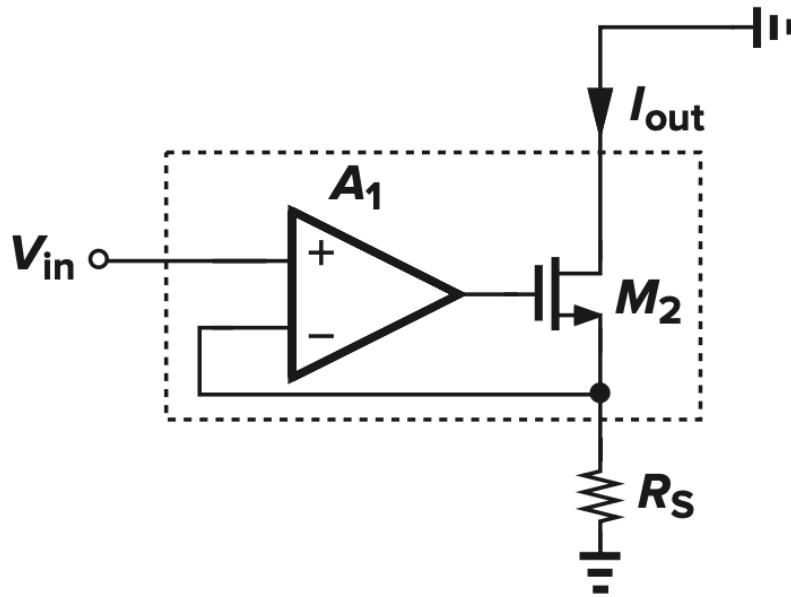


$$I_{out} = g_m [(V_{in} - R_S I_{out}) A_1 - R_S I_{out}]$$

$$\frac{I_{out}}{V_{in}} = \frac{A_1 g_m}{1 + (A_1 + 1) g_m R_S}$$

Gain Boosting: Rout

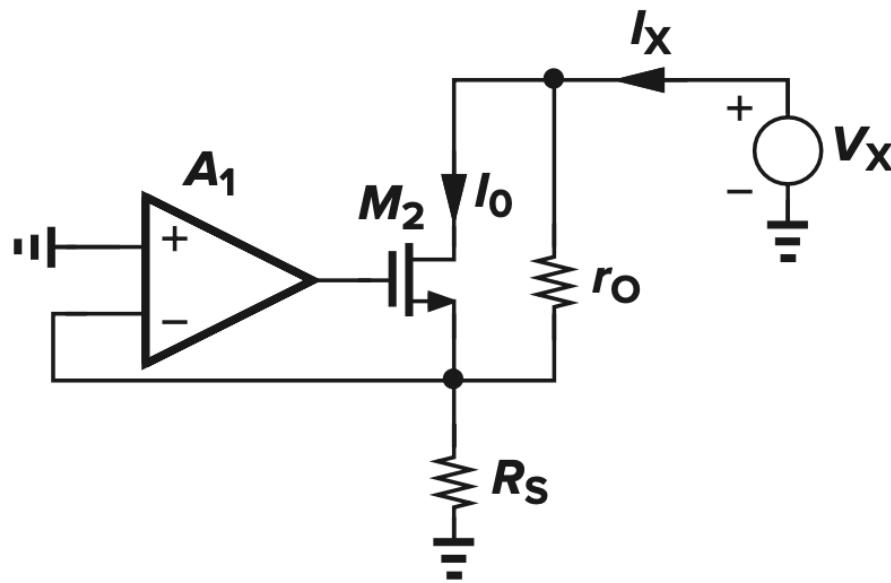


Gain Boosting: Rout

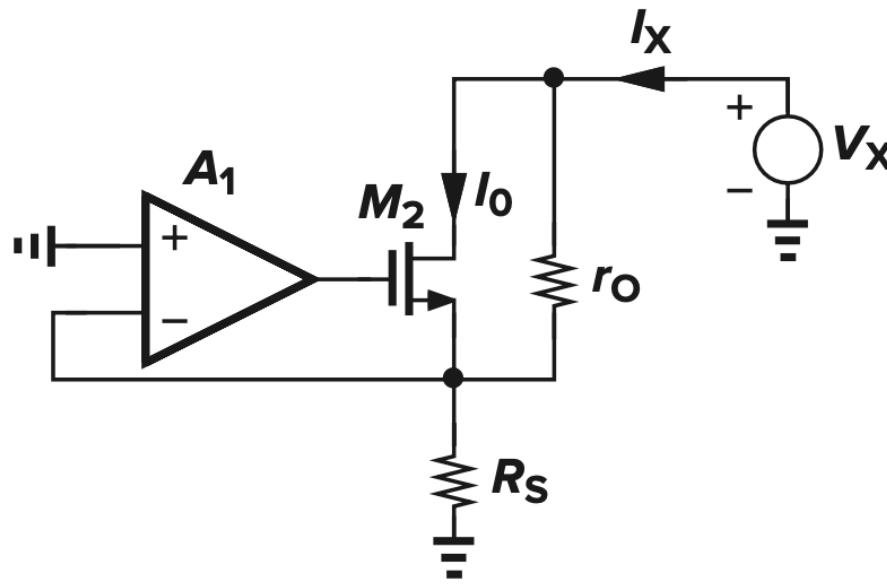

$$I_X = (-A_1 R_S - R_S) g_m I_X + \frac{V_X - R_S I_X}{r_O}$$

$$R_{out} = r_O + (A_1 + 1) g_m r_O R_S + R_S$$

Gain Boosting: Voltage Gain

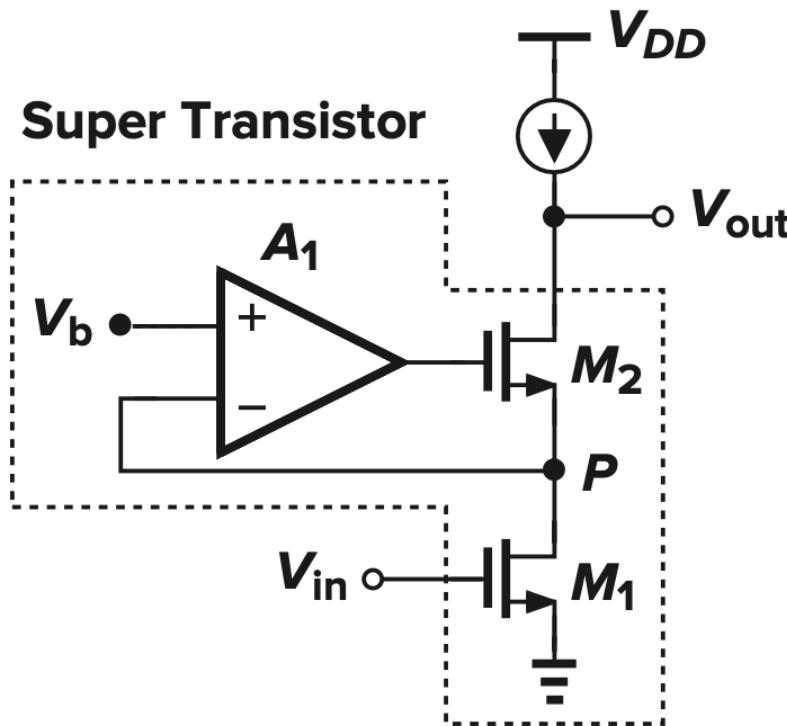


Output impedance:

$$r_{O2} + (A_1 + 1)g_{m2}r_{O2}r_{O1} + r_{O1}$$


$$G_m \approx g_{m1}$$

$$\begin{aligned}|A_v| &\approx g_{m1}[r_{O2} + (A_1 + 1)g_{m2}r_{O2}r_{O1} + r_{O1}] \\ &\approx g_{m1}g_{m2}r_{O1}r_{O2}(A_1 + 1)\end{aligned}$$

Gain Boosting: Circuit Implementation

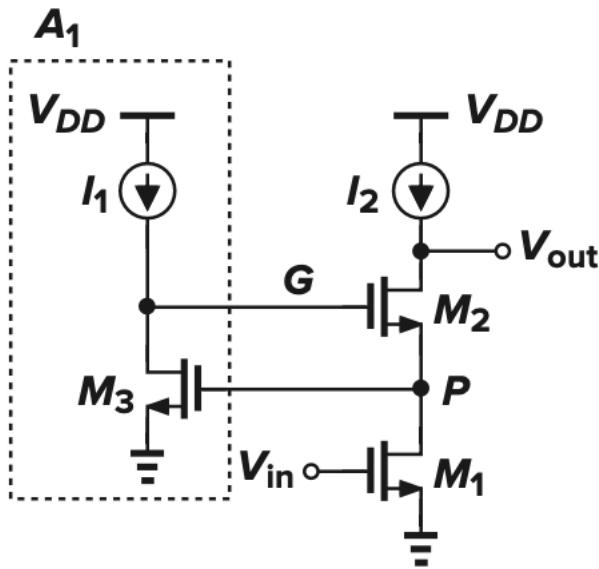


Gain Boosting: Circuit Implementation

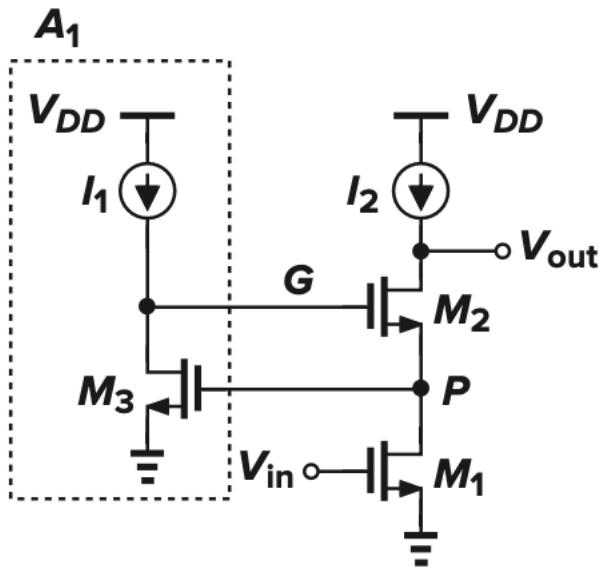


$$|A_1| = g_{m3}r_{O3}$$

$$|V_{out}/V_{in}| \approx g_{m1}r_{O1}g_{m2}r_{O2}(g_{m3}r_{O3}+1)$$




Gain Boosting: Circuit Implementation

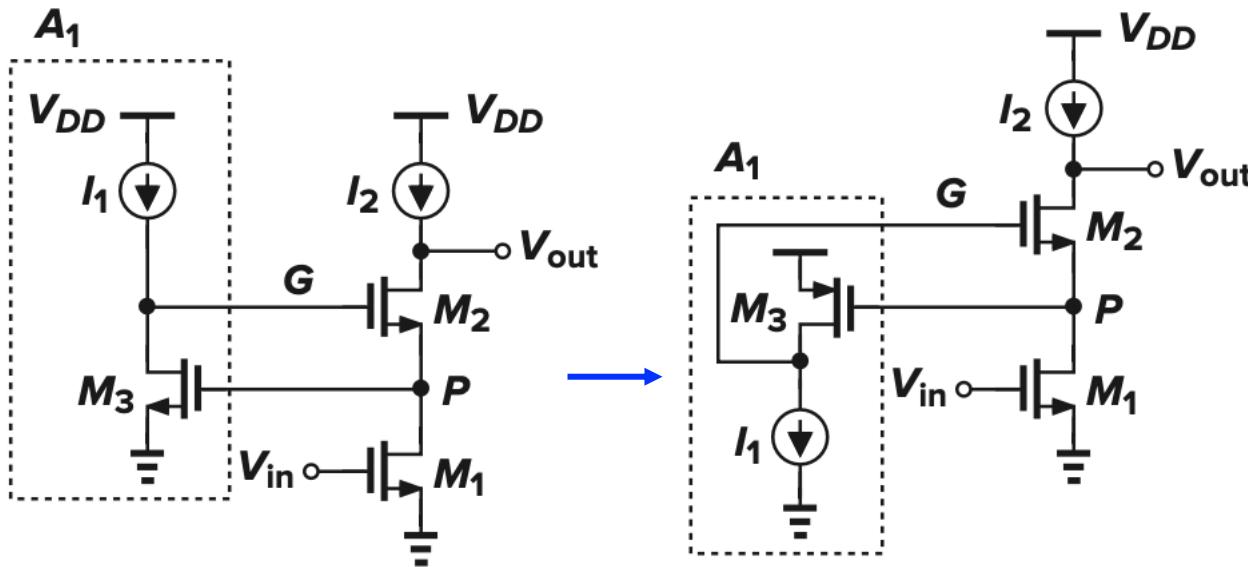


Gain Boosting: Circuit Implementation

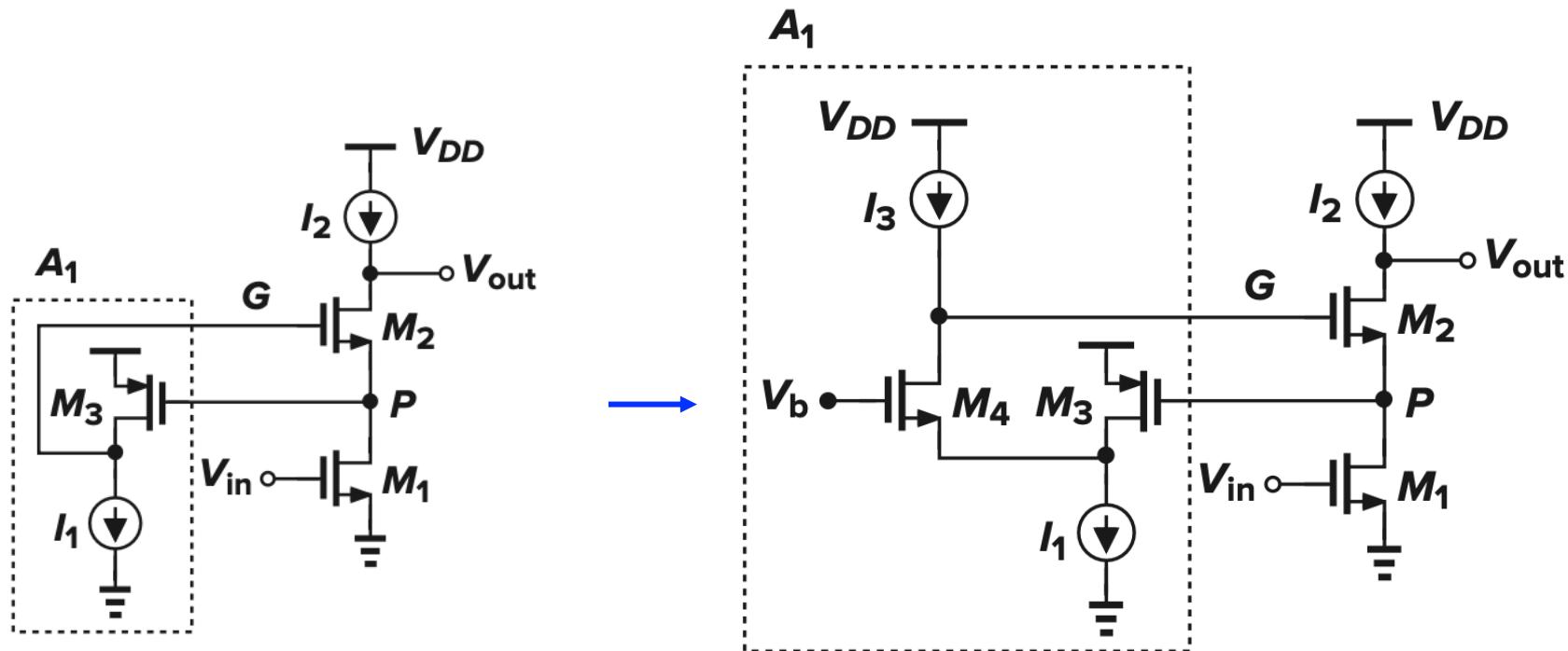



Gain Boosting: Differential

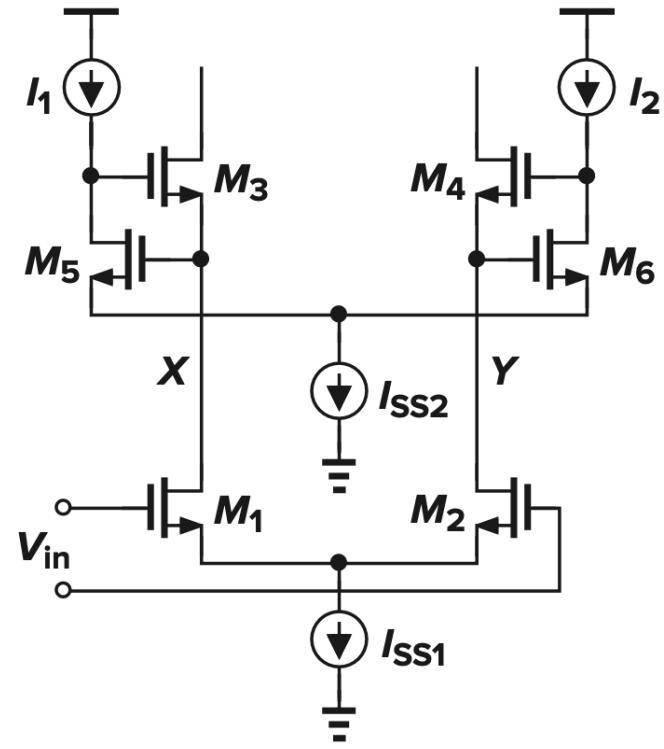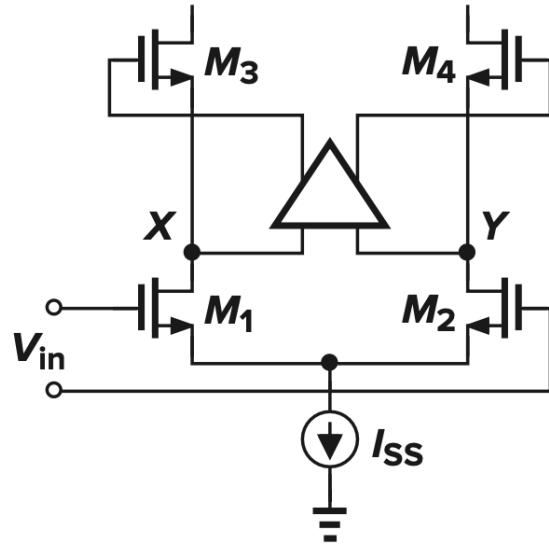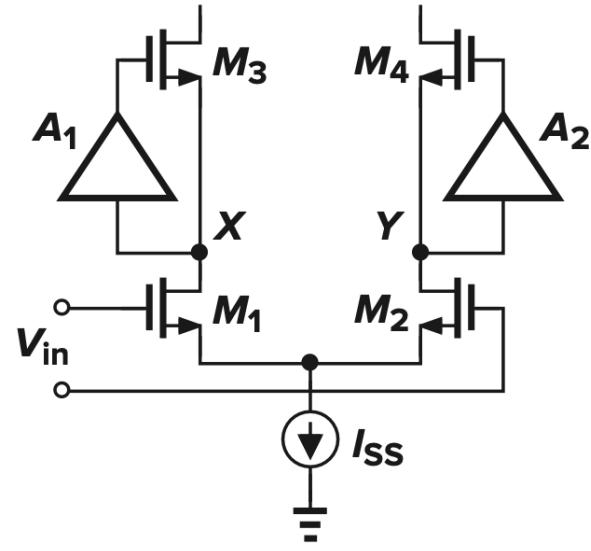


Gain Boosting: Differential

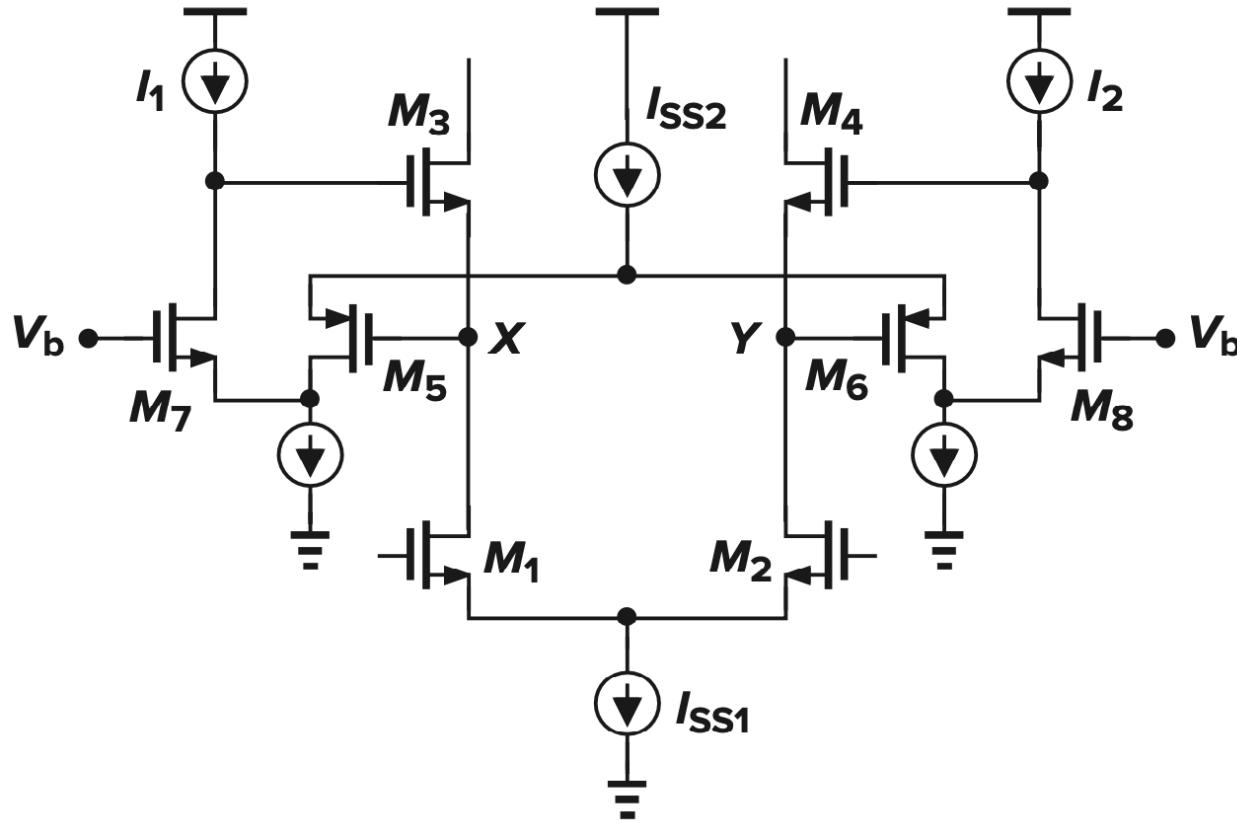

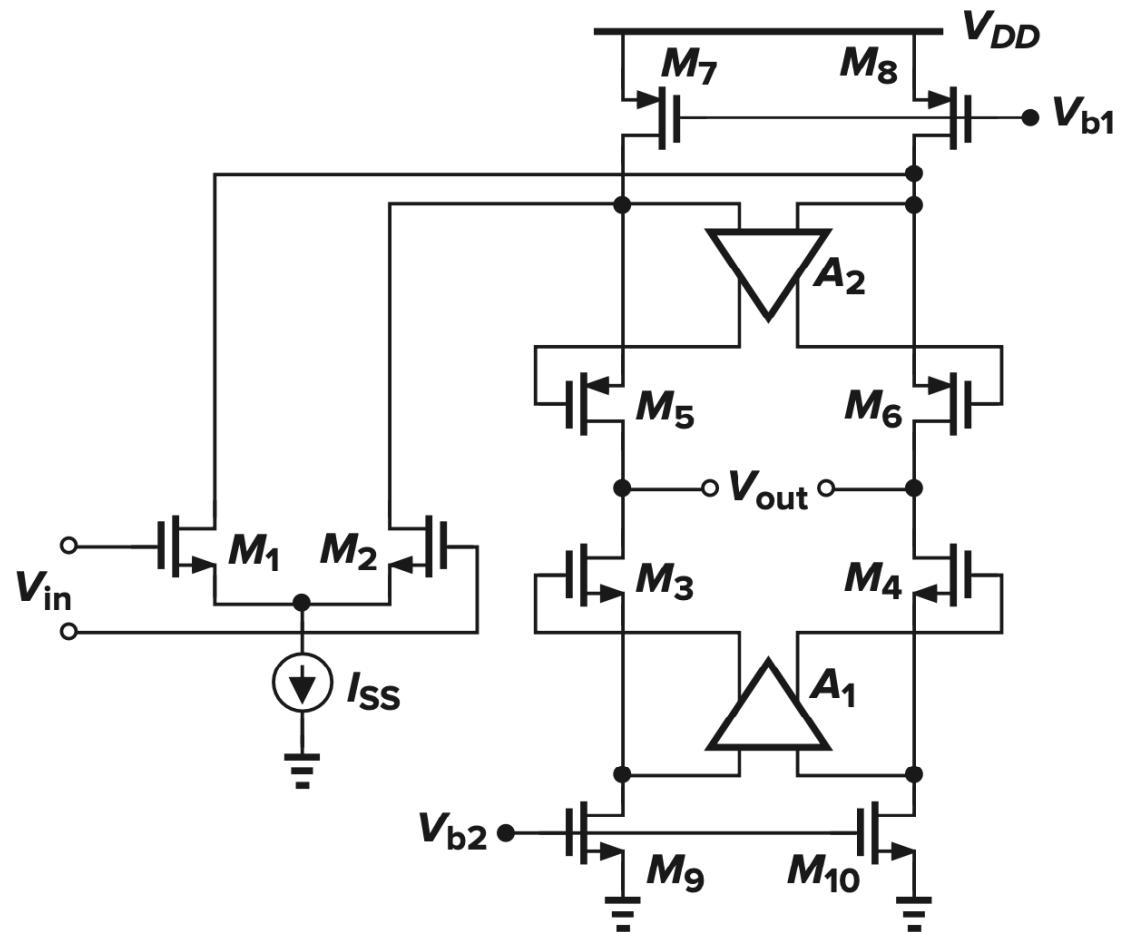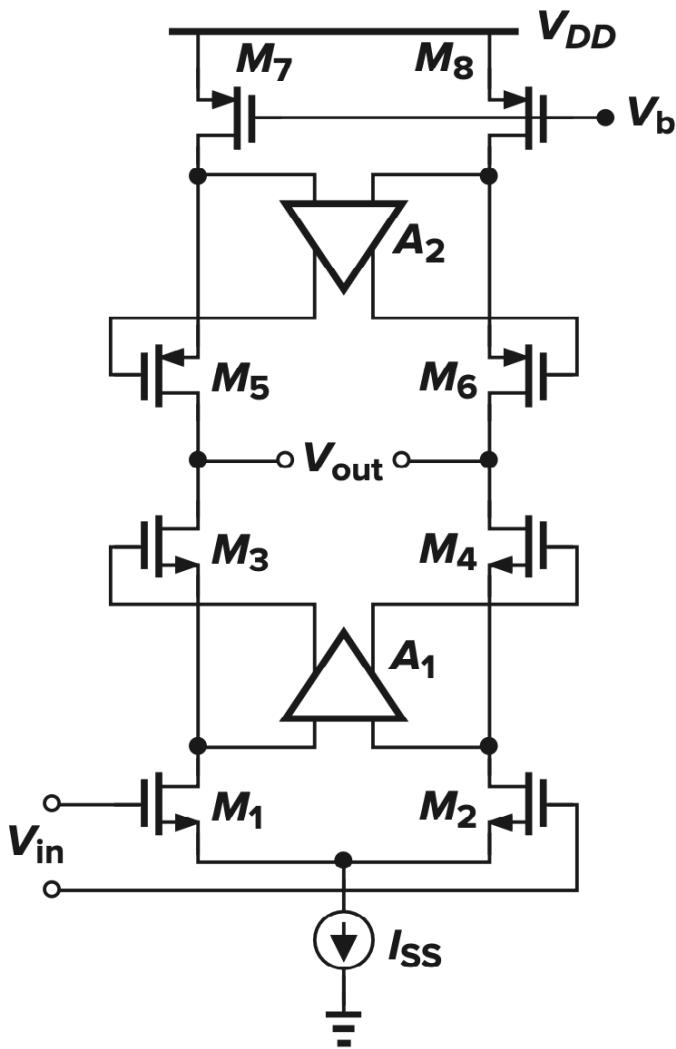
Gain Boosting in both Signal Path and Load Devices



Gain Boosting: Frequency Response

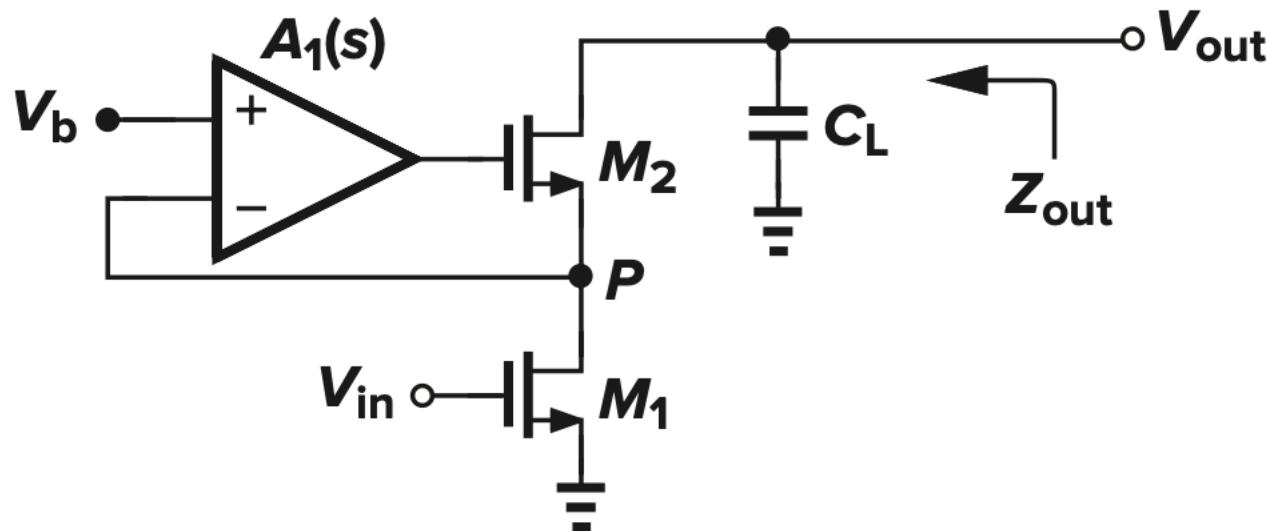

Gain Boosting: Frequency Response

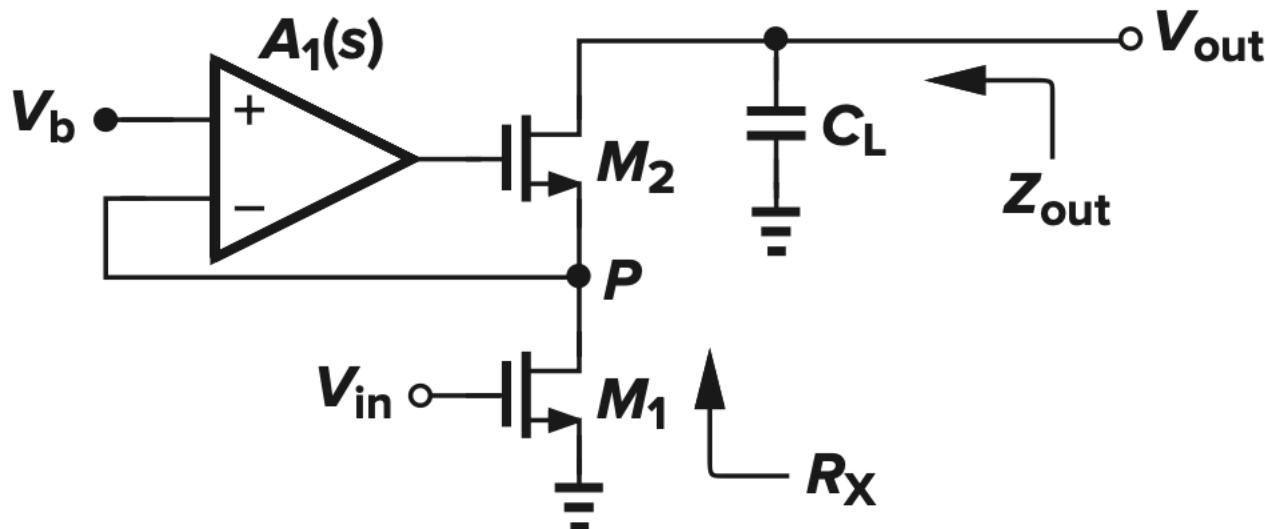


$$G_m(s) = g_{m1} \frac{r_{O1}}{r_{O1} + \frac{r_{O2}}{1 + (A_1 + 1)g_{m2}r_{O2}}} \quad r_{O2}/[1 + (A_1 + 1)g_{m2}r_{O2}]$$

$$= \frac{g_{m1}r_{O1}[1 + (A_1 + 1)g_{m2}r_{O2}]}{r_{O1} + (A_1 + 1)g_{m2}r_{O2}r_{O1} + r_{O2}}$$


$$Z_{out} = [r_{O1} + (A_1 + 1)g_{m2}r_{O2}r_{O1} + r_{O2}]||\frac{1}{C_Ls}$$

Gain Boosting: Frequency Response

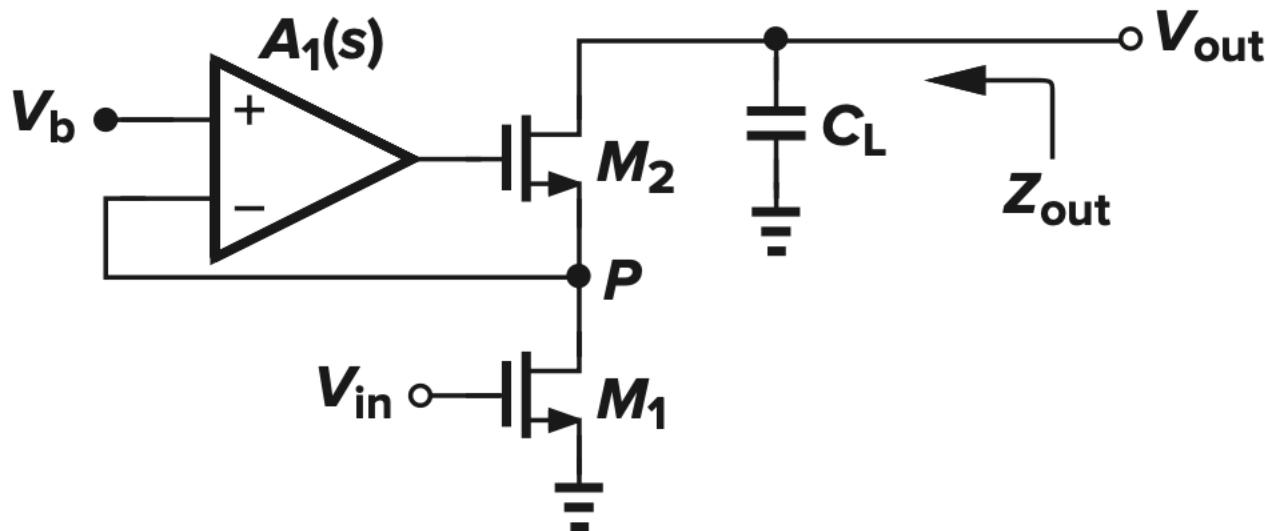


$$\begin{aligned}\frac{V_{out}}{V_{in}}(s) &= -G_m(s)Z_{out}(s) \\ &= \frac{-g_{m1}r_{O1}[1 + (A_1 + 1)g_{m2}r_{O2}]}{(r_{O1} + r_{O2})C_Ls + (A_1 + 1)g_{m2}r_{O2}r_{O1}C_Ls + 1}\end{aligned}$$

Gain Boosting: Frequency Response

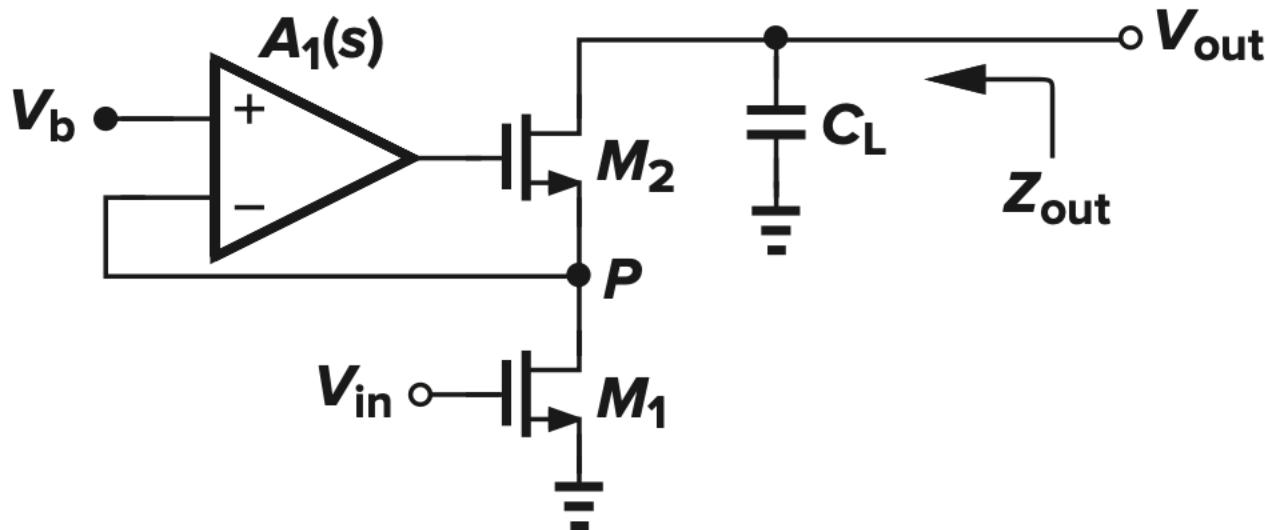

$$\frac{V_{out}}{V_{in}}(s) = \frac{-g_{m1}r_{O1}[(1 + g_{m2}r_{O2})\frac{s}{\omega_0} + (A_0 + 1)g_{m2}r_{O2} + 1]}{\frac{(r_{O1} + r_{O2})C_L}{\omega_0}[1 + g_{m2}(r_{O2}/r_{O1})]s^2 + [(r_{O1} + r_{O2})C_L + (A_0 + 1)g_{m2}r_{O2}r_{O1}C_L + \frac{1}{\omega_0}]s + 1}$$

Gain Boosting: Frequency Response

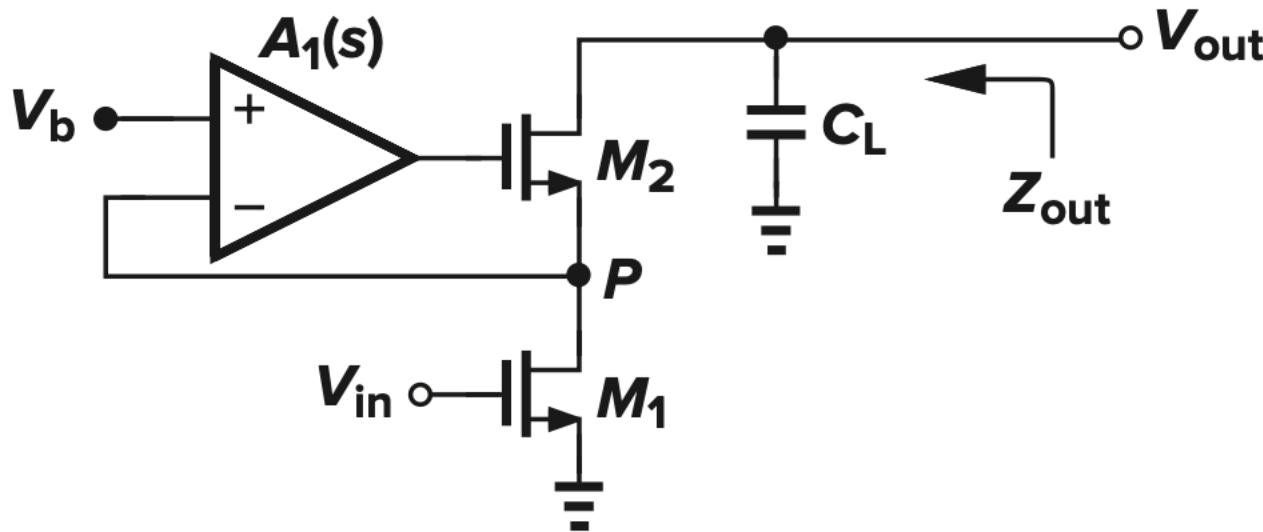

$$\frac{V_{out}}{V_{in}}(s) = \frac{-g_{m1}r_{o1}[(1 + g_{m2}r_{o2})\frac{s}{\omega_0} + (A_0 + 1)g_{m2}r_{o2} + 1]}{\frac{(r_{o1} + r_{o2})C_L}{\omega_0}[1 + g_{m2}(r_{o2}||r_{o1})]s^2 + [(r_{o1} + r_{o2})C_L + (A_0 + 1)g_{m2}r_{o2}r_{o1}C_L + \frac{1}{\omega_0}]s + 1}$$

$$|\omega_{p1}| = \frac{1}{[r_{o1} + (A_0 + 1)g_{m2}r_{o2}r_{o1} + r_{o2}]C_L + \frac{1}{\omega_0}}$$

$$\approx \frac{1}{A_0g_{m2}r_{o2}r_{o1}C_L}$$

$$|\omega_{p2}| = \frac{[r_{o1} + (A_0 + 1)g_{m2}r_{o2}r_{o1} + r_{o2}]C_L + \frac{1}{\omega_0}}{\frac{(r_{o1} + r_{o2})C_L}{\omega_0}[1 + g_{m2}(r_{o1}||r_{o2})]}$$

$$\approx (A_0 + 1)\omega_0 + \frac{1}{g_{m2}r_{o2}r_{o1}C_L}$$

Gain Boosting: Frequency Response

