
 


*Integrated Neurotechnologies
Laboratory*

EPFL

 


Advanced analog integrated circuit design (EE-523), Lecture 4

Prof. Mahsa Shoaran

Institutes of Electrical and Micro Engineering and Neuro-X, School of Engineering, EPFL





Recap: CMFB

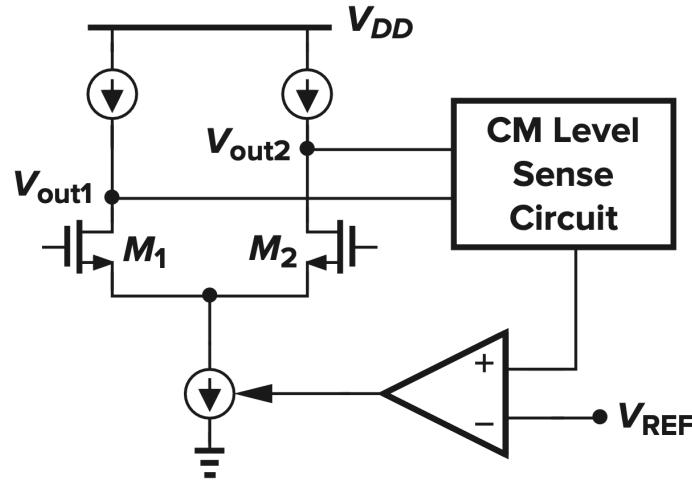- High-gain differential circuits require “common-mode feedback” (CMFB)





Recap: CMFB

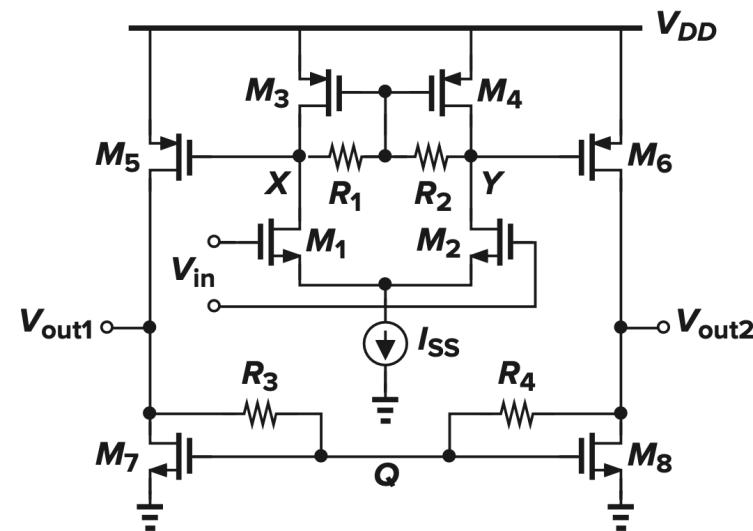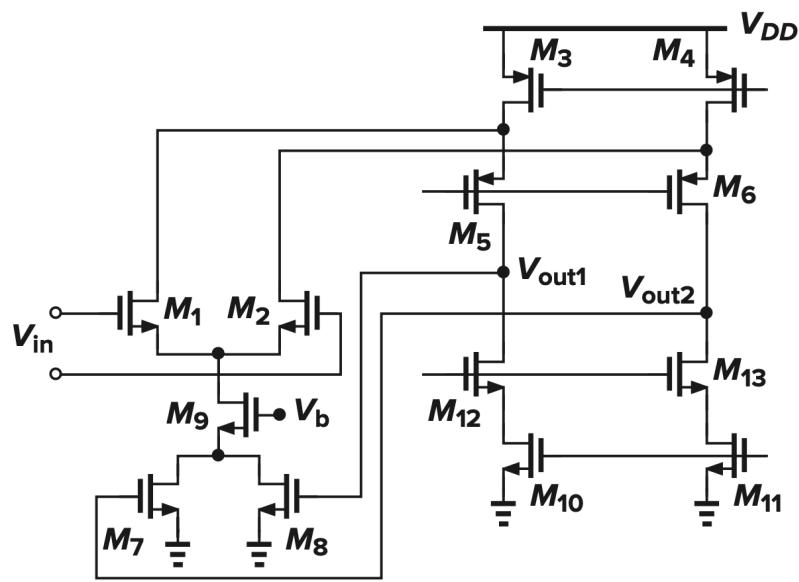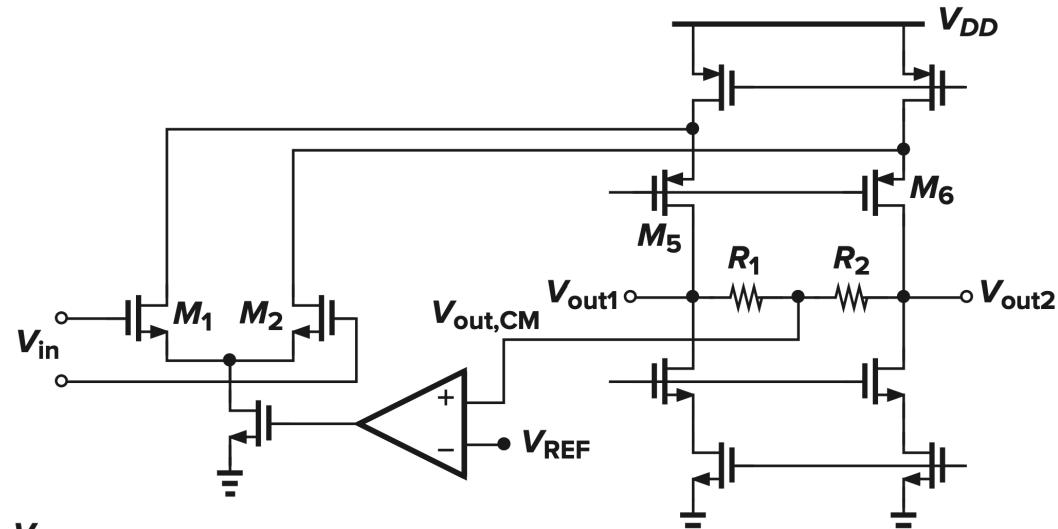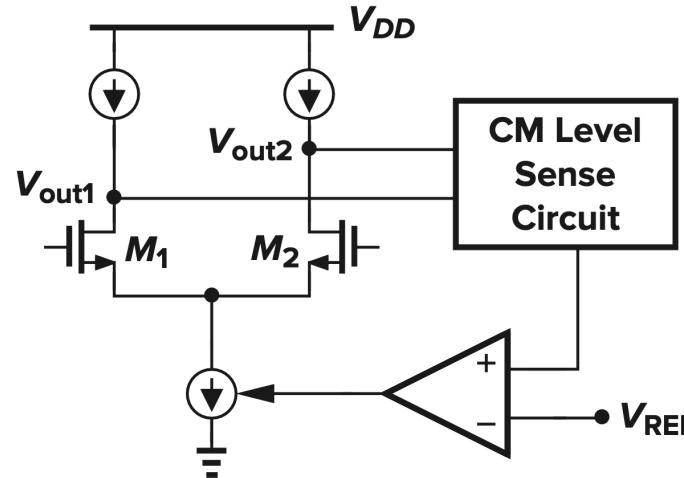- High-gain differential circuits require “common-mode feedback” (CMFB)




Input Range

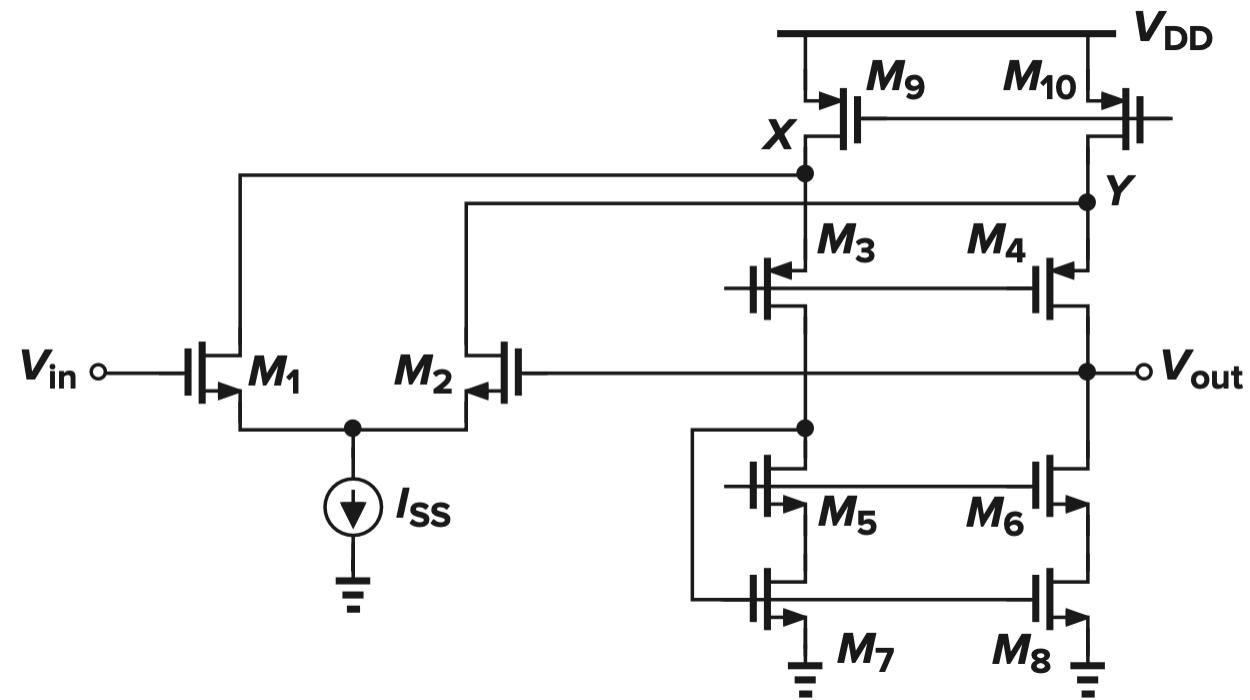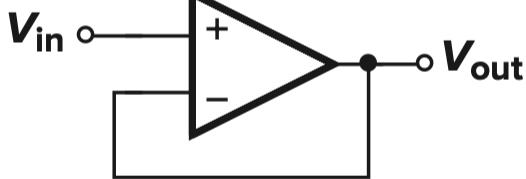

$$V_{in,min} \approx V_{out,min} = V_{GS1,2} + V_{ISS}$$

Input Range Extension

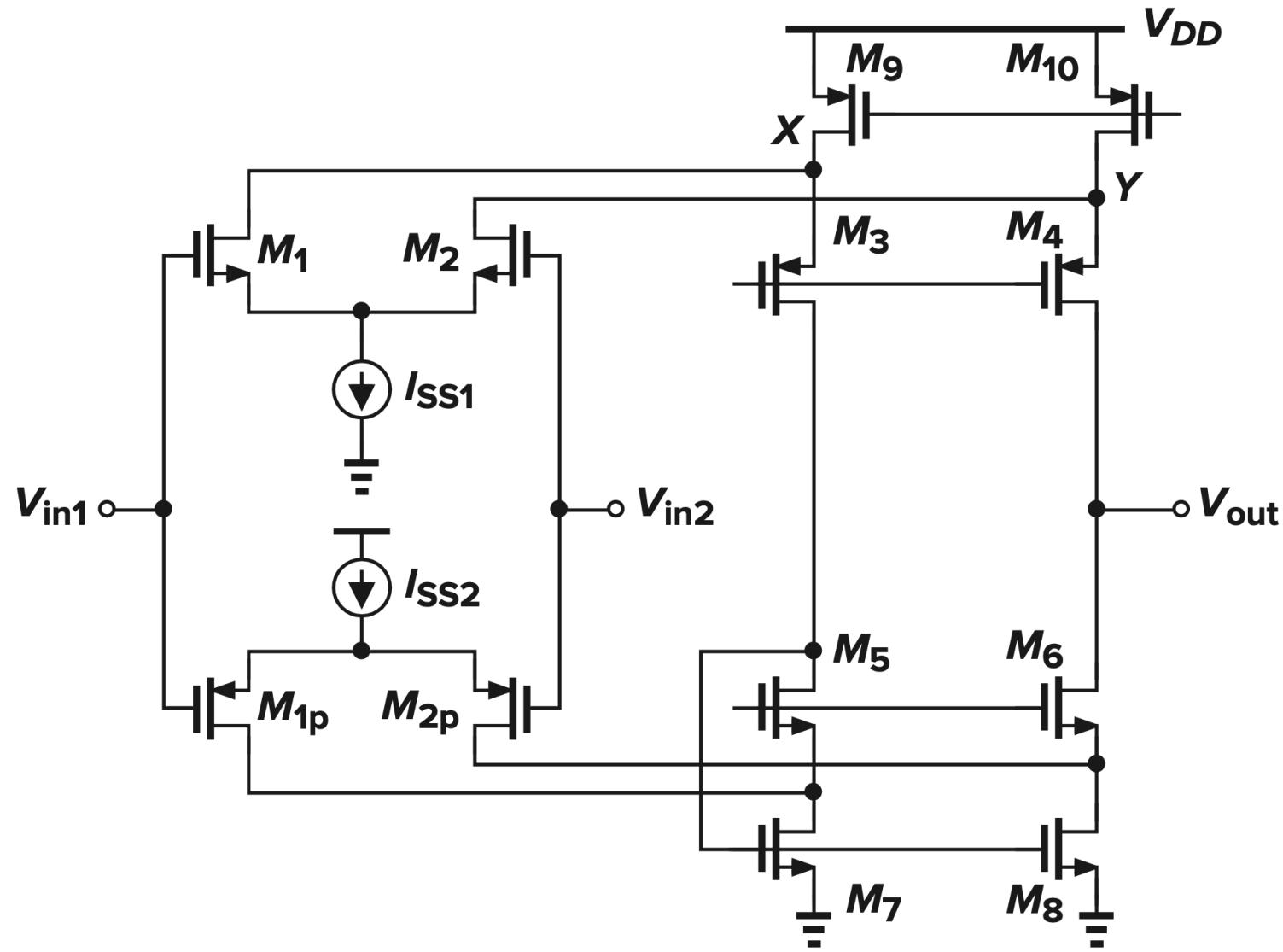



Why Switched-Capacitor Circuits?

- **Continuous-time circuits:** Input and output are continuous signals
- **Discrete-time circuits:** Process input “at periodic instants of time and generates output at the end of each period. Example: **switched-capacitor (SC) circuits**

Why Switched-Capacitor Circuits?

- **Continuous-time circuits:** Input and output are continuous signals
- **Discrete-time circuits:** Process input “at periodic instants of time and generates output at the end of each period. Example: **switched-capacitor (SC) circuits**


Continuous-time feedback amplifier

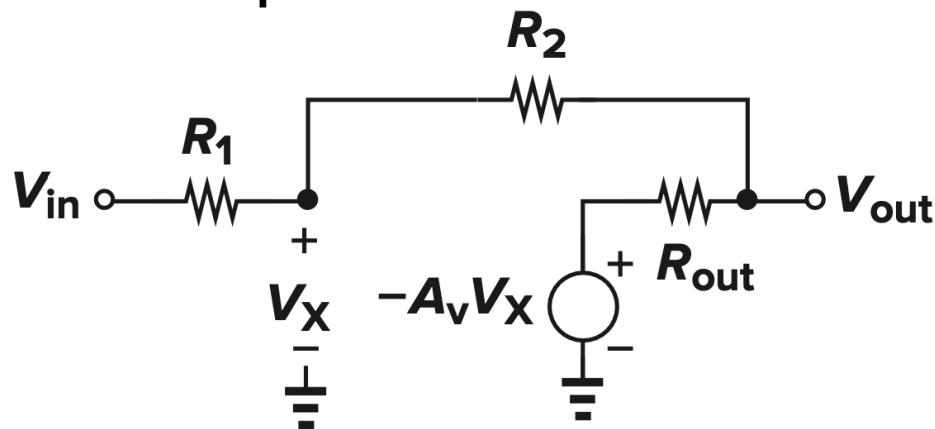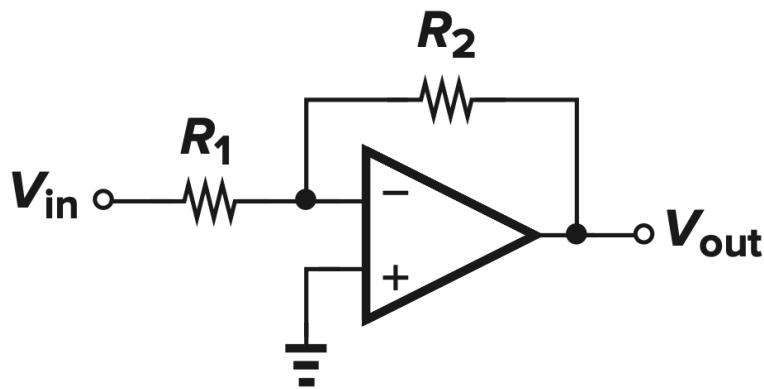

$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1} \cdot \frac{A_v - \frac{R_{out}}{R_2}}{1 + \frac{R_{out}}{R_1} + A_v + \frac{R_2}{R_1}}$$


Continuous-time Feedback Amplifier with Capacitors

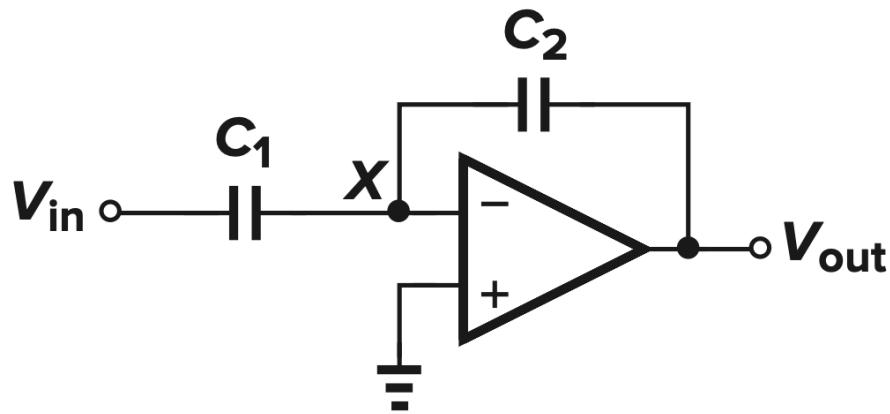- To avoid reducing the open-loop gain of the op amp, perhaps we can replace the resistors by capacitors:




Continuous-time Feedback Amplifier with Capacitors

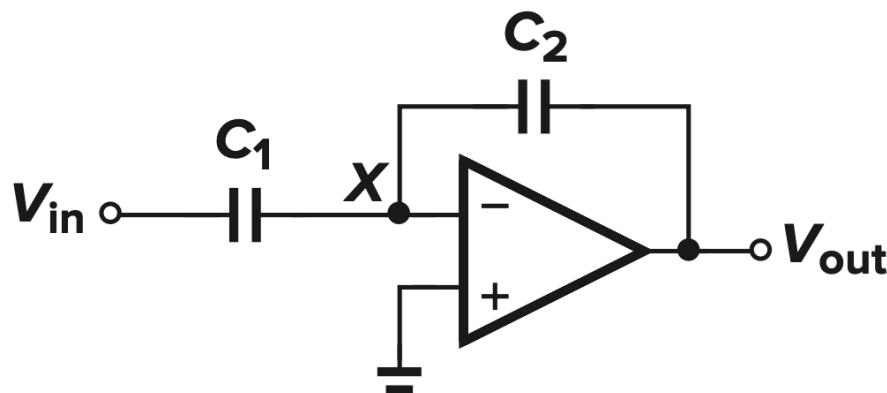- To avoid reducing the open-loop gain of the op amp, perhaps we can replace the resistors by capacitors:



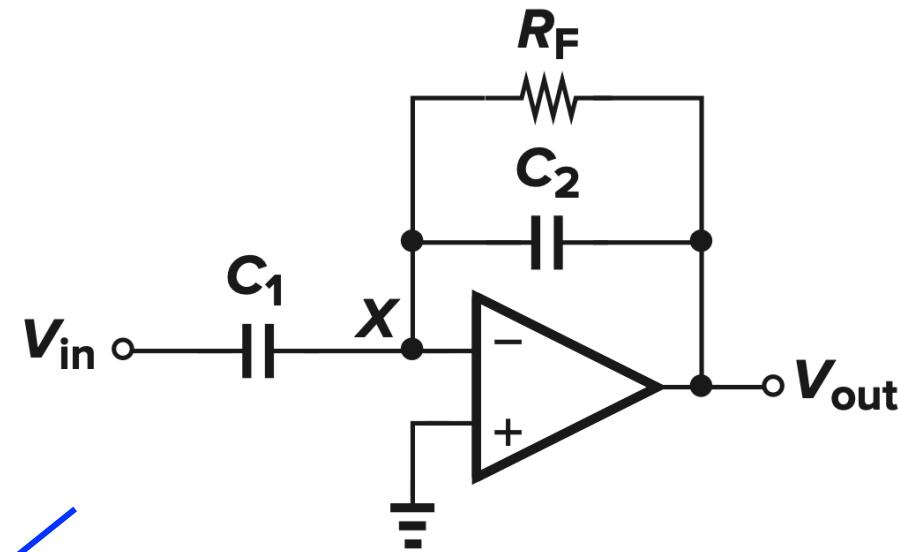
$$\begin{aligned}\frac{V_{out}}{V_{in}}(s) &\approx -\frac{R_F \frac{1}{C_2 s}}{R_F + \frac{1}{C_2 s}} \div \frac{1}{C_1 s} \\ &= -\frac{R_F C_1 s}{R_F C_2 s + 1}\end{aligned}$$




$$V_{out}/V_{in} \approx -C_1/C_2 \text{ only if } \omega \gg (R_F C_2)^{-1}$$

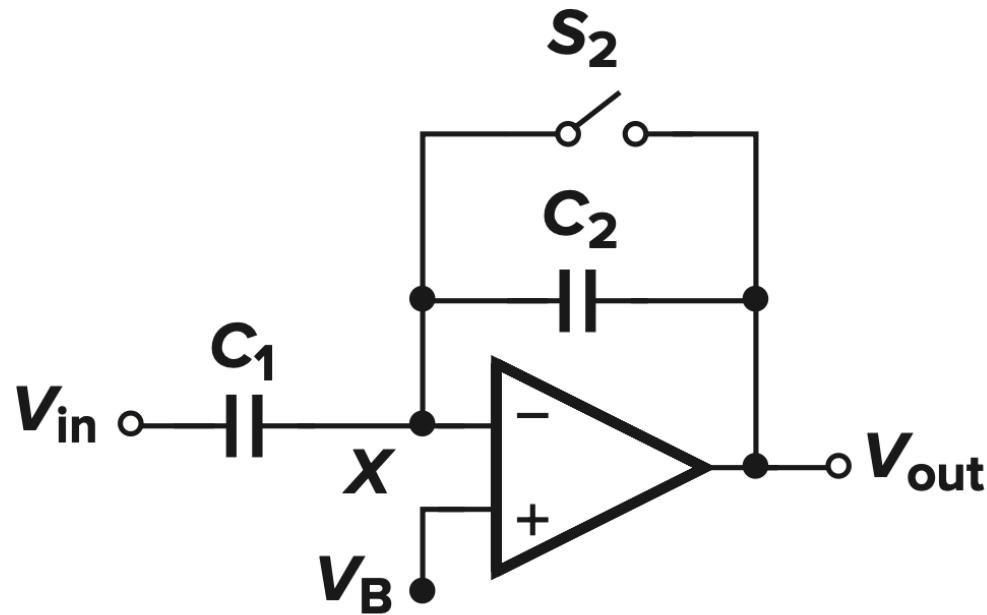
Use of Feedback Switch to Define DC Input Level





Switched-Capacitor Amplifier

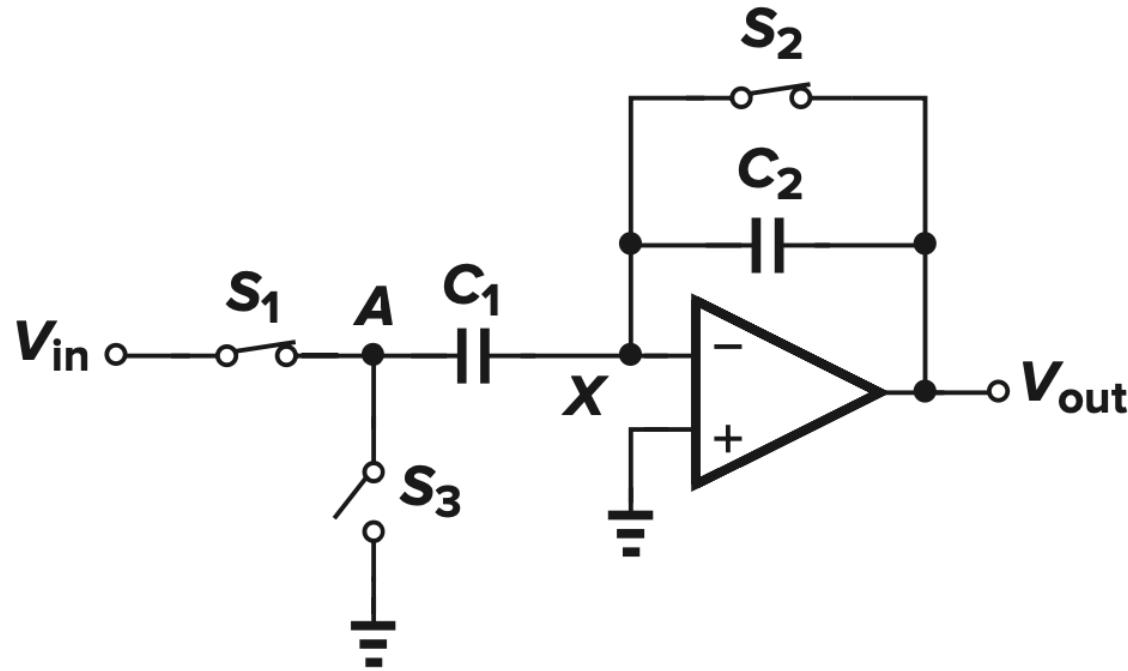


Switched-Capacitor Amplifier

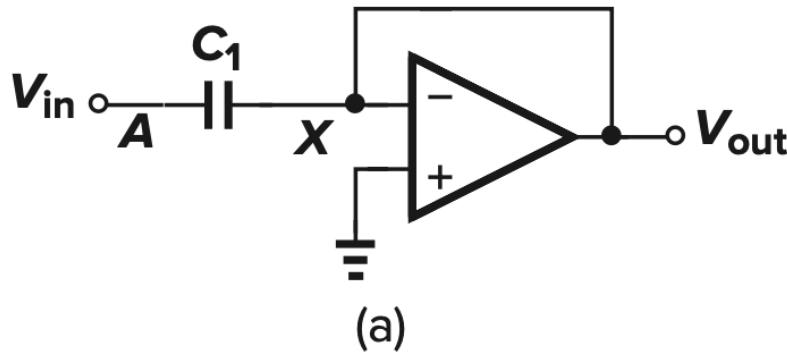


Switched-Capacitor Amplifier

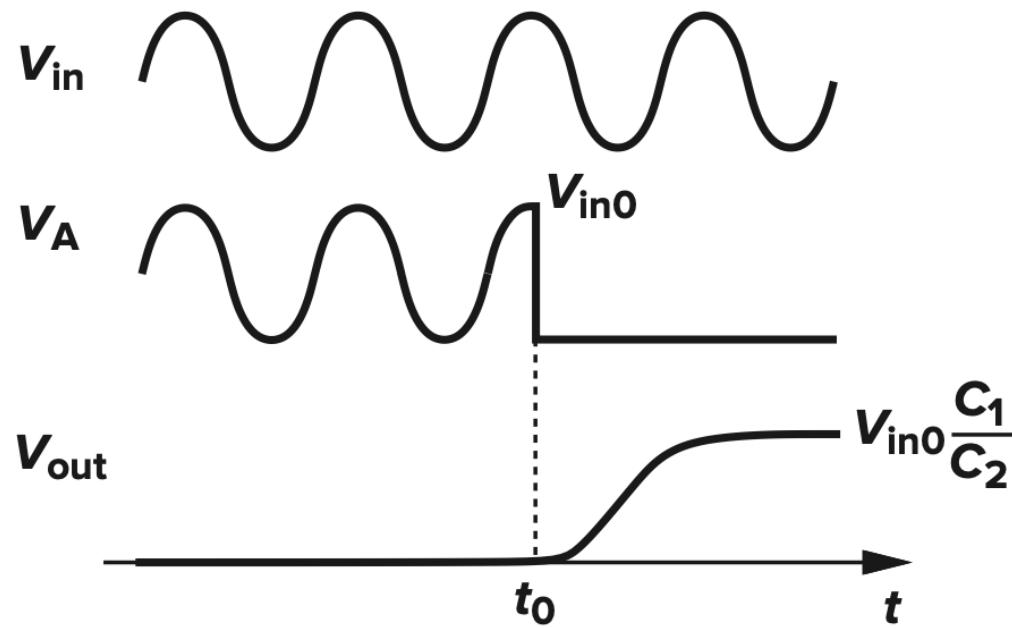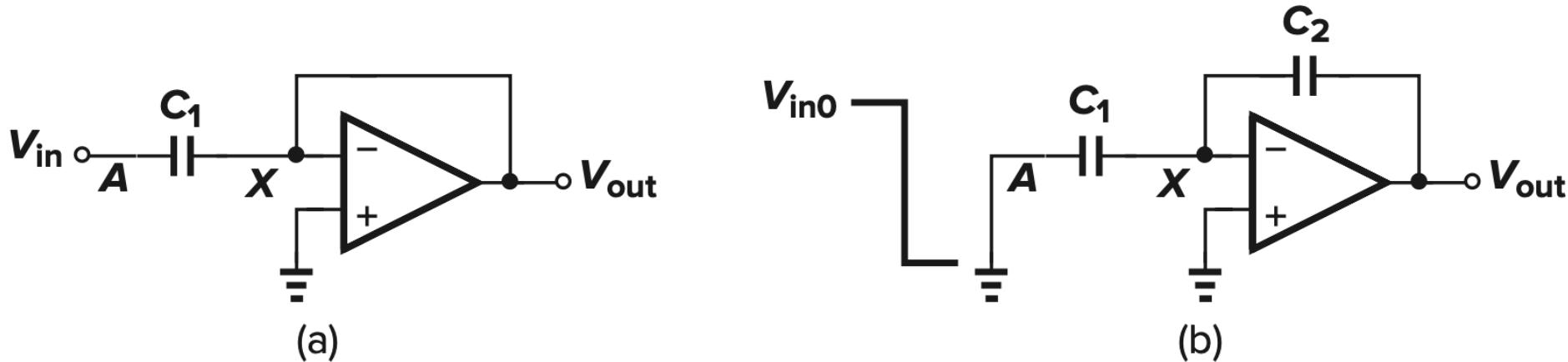


Switched-Capacitor Amplifier

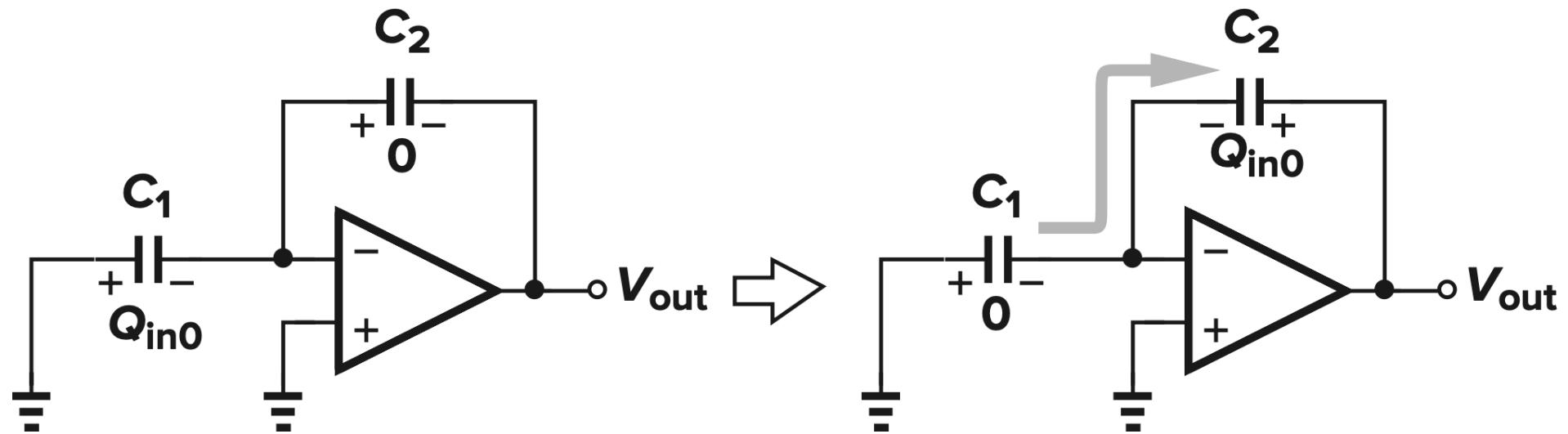



Discrete-time vs. Continuous-time

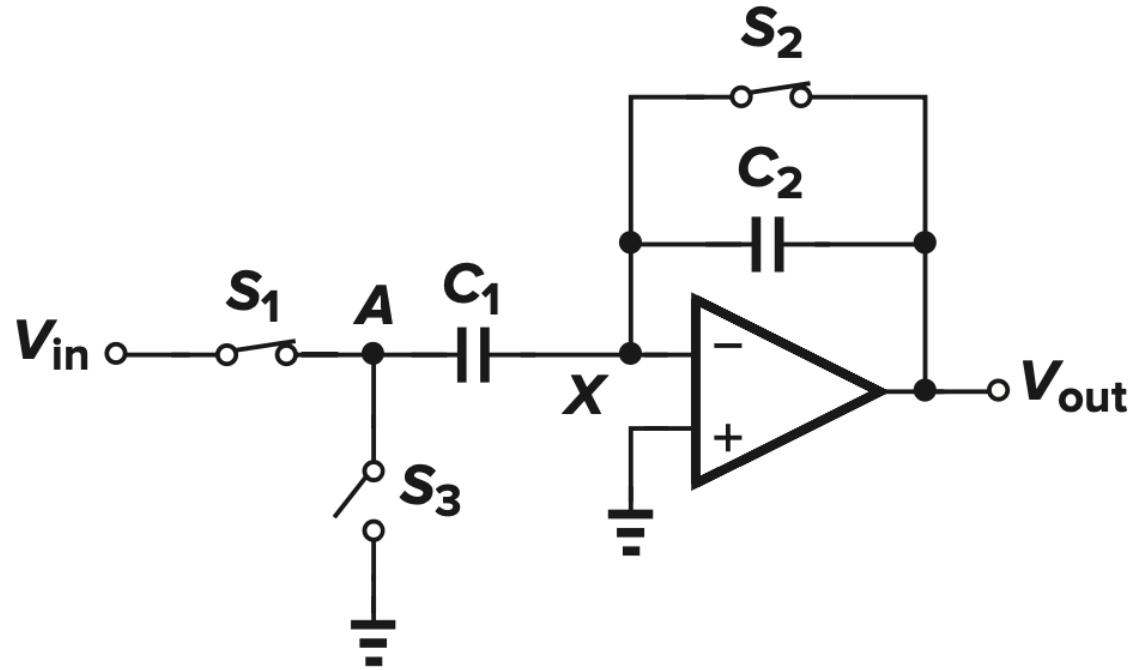




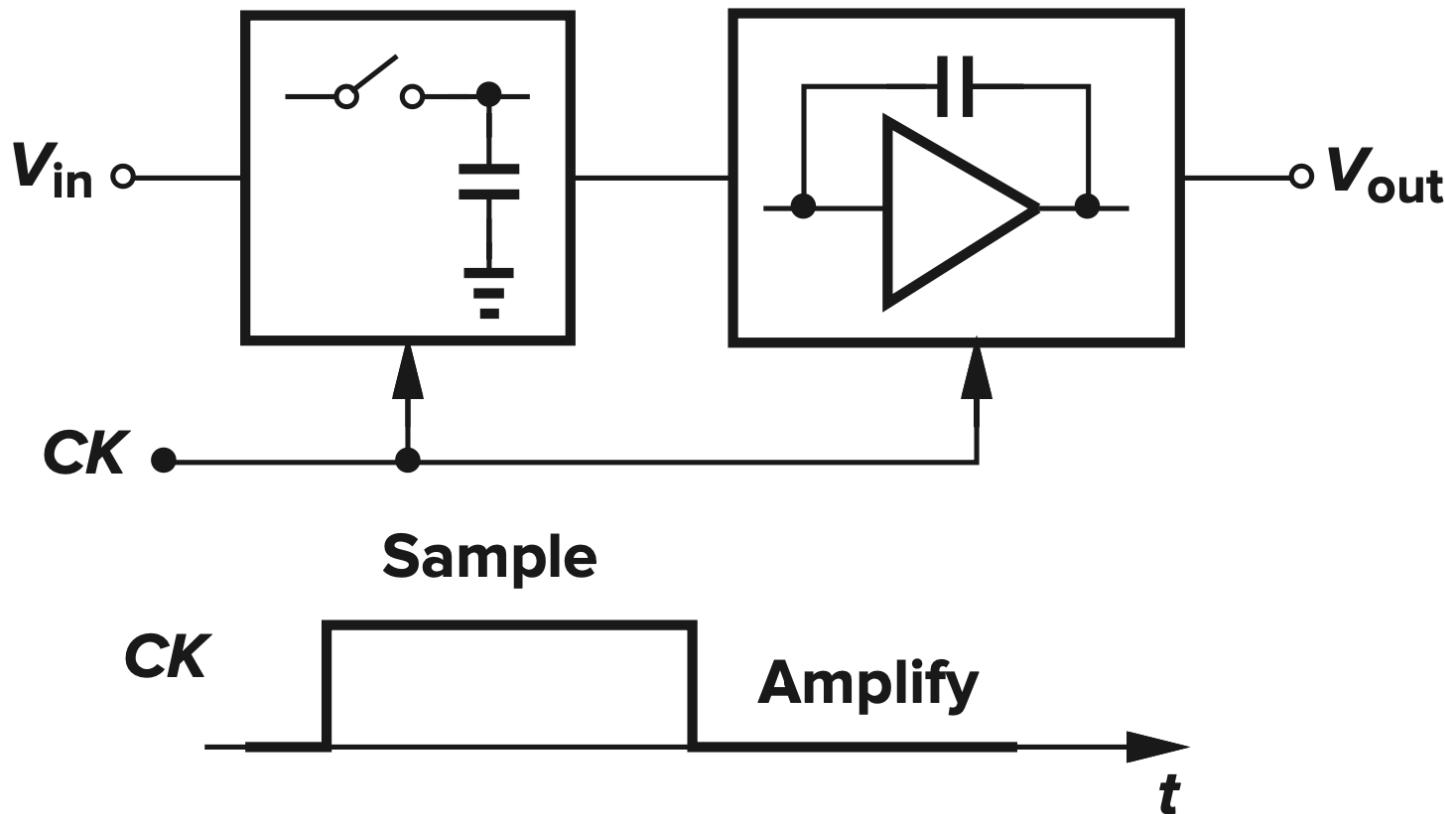
Switched-Capacitor Amplifier: General View








Simple sampling circuit

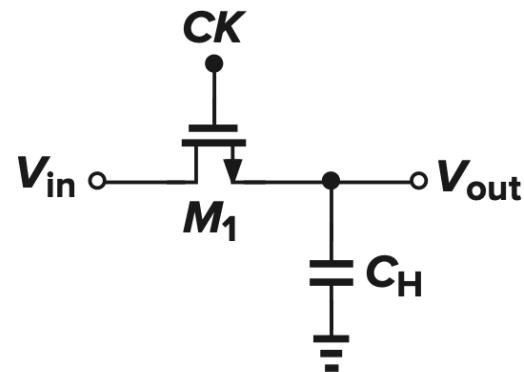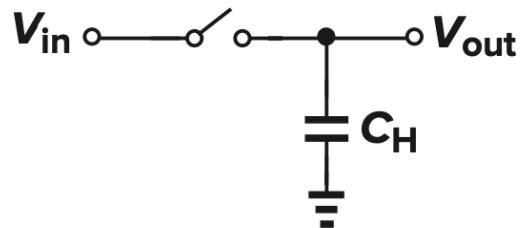


Simple sampling circuit

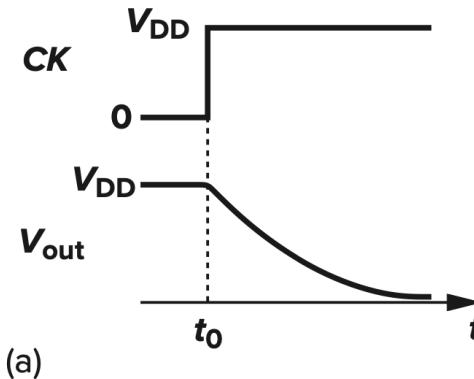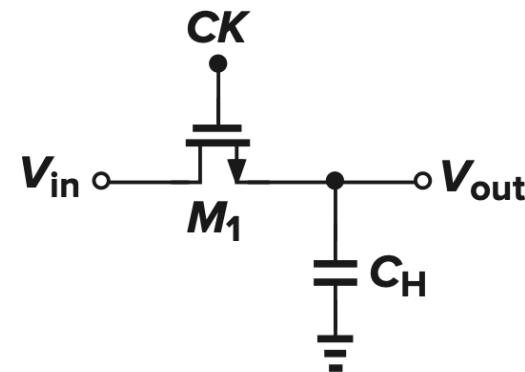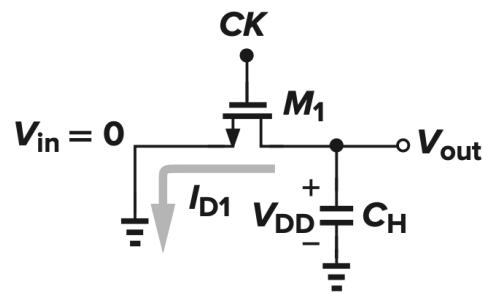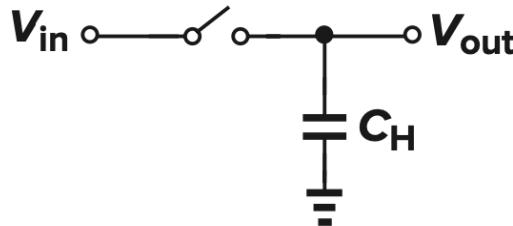

Simple sampling circuit

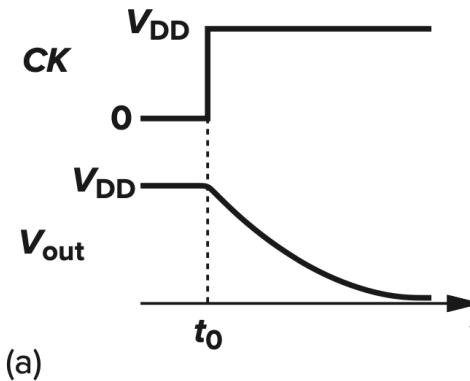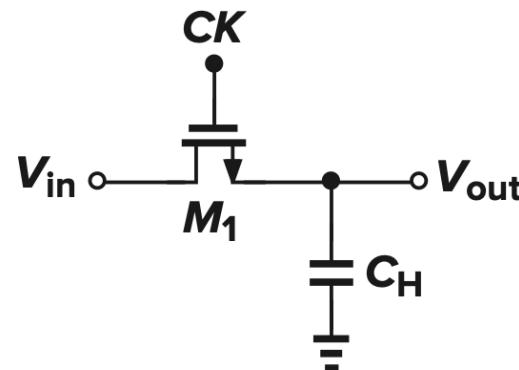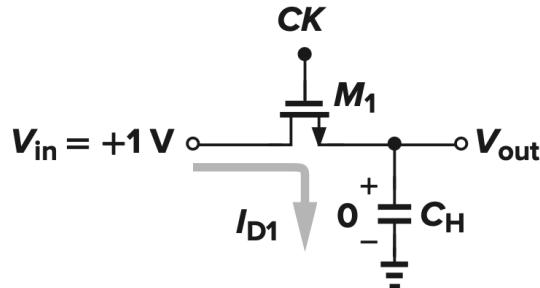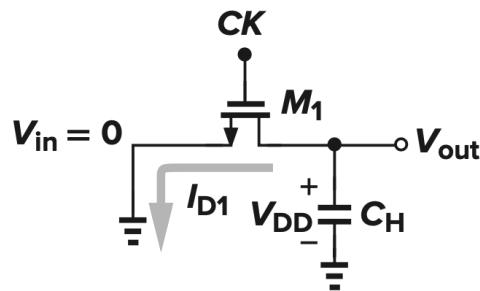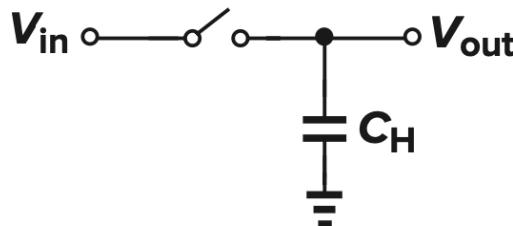


(a)

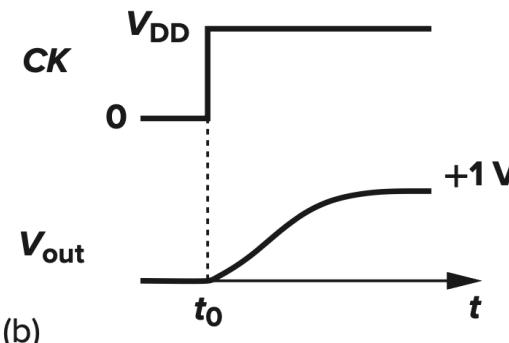


(b)

Track and hold


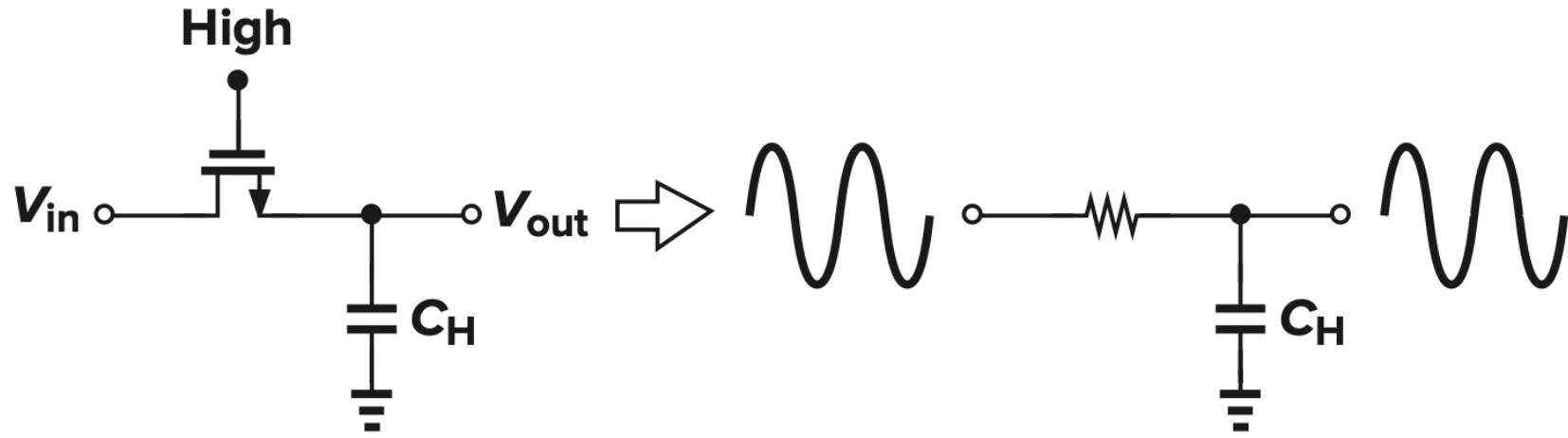


(a)

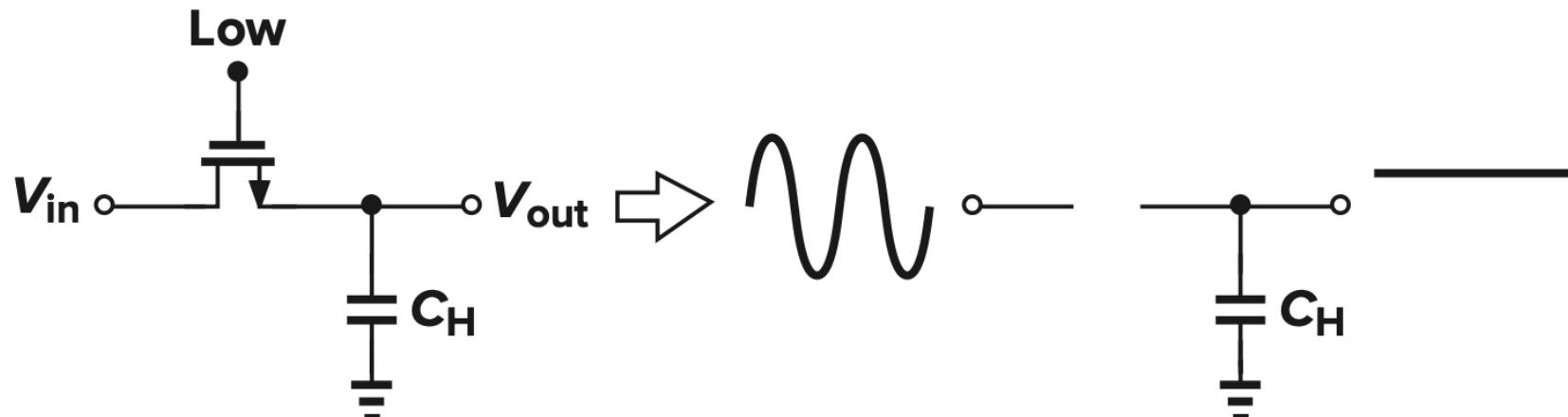

(b)

Maximum output level in an NMOS sampler

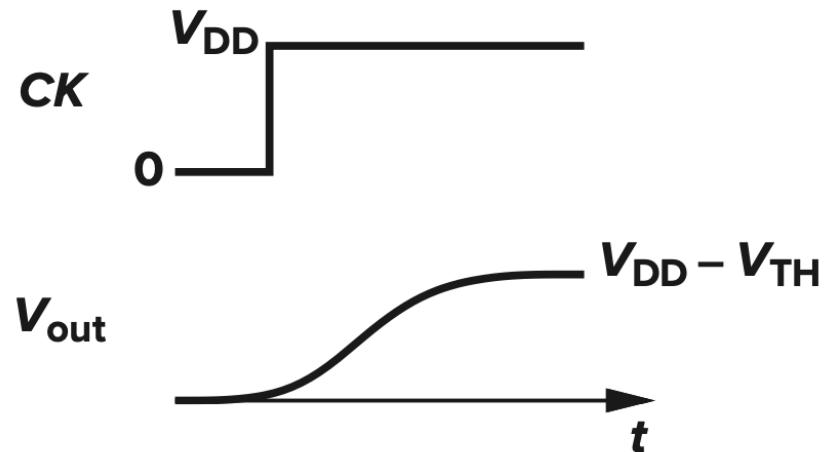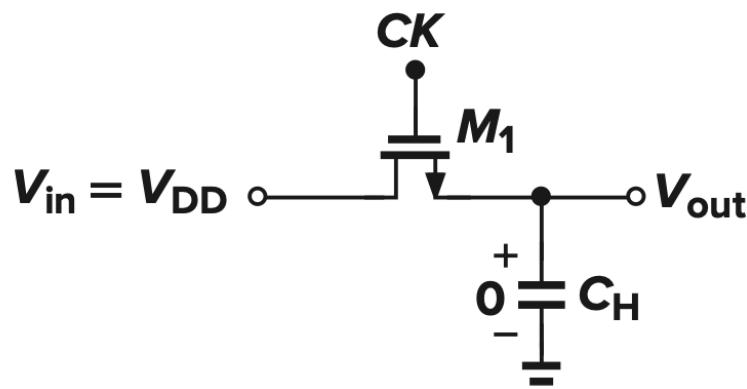

$$C_H \frac{dV_{out}}{dt} = I_{D1}$$





$$= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{DD} - V_{out} - V_{TH})^2$$

$$\frac{dV_{out}}{(V_{DD} - V_{out} - V_{TH})^2} = \frac{1}{2} \mu_n \frac{C_{ox}}{C_H} \frac{W}{L} dt$$

$$\frac{1}{V_{DD} - V_{out} - V_{TH}} \bigg|_0^{V_{out}} = \frac{1}{2} \mu_n \frac{C_{ox}}{C_H} \frac{W}{L} t \bigg|_0^t$$

Maximum output level in an NMOS sampler

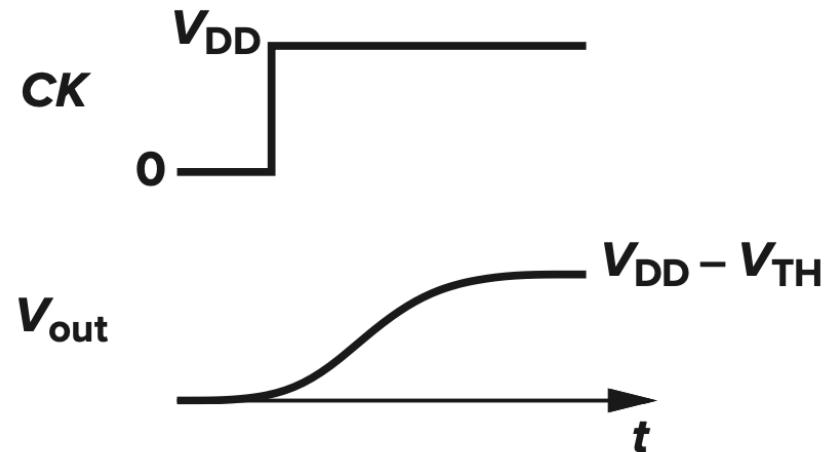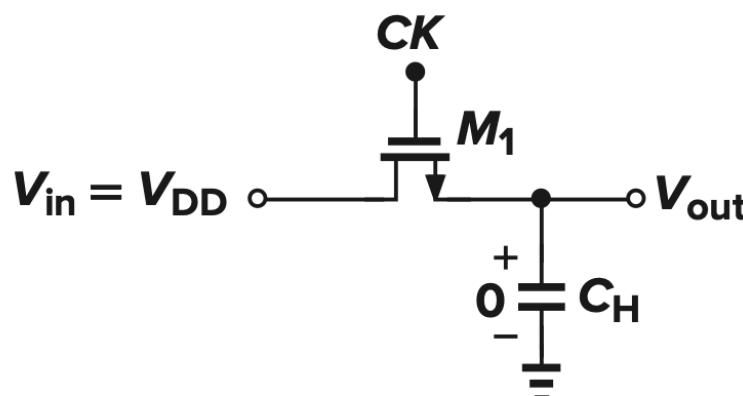

$$\frac{dV_{out}}{(V_{DD} - V_{out} - V_{TH})^2} = \frac{1}{2} \mu_n \frac{C_{ox}}{C_H} \frac{W}{L} dt$$

$$C_H \frac{dV_{out}}{dt} = I_{D1}$$





$$= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{DD} - V_{out} - V_{TH})^2$$





$$\frac{1}{V_{DD} - V_{out} - V_{TH}} \bigg|_0^{V_{out}} = \frac{1}{2} \mu_n \frac{C_{ox}}{C_H} \frac{W}{L} t \bigg|_0^t$$

$$V_{out} = V_{DD} - V_{TH} - \frac{1}{\frac{1}{2} \mu_n \frac{C_{ox}}{C_H} \frac{W}{L} t + \frac{1}{V_{DD} - V_{TH}}}$$



NMOS and PMOS Switches

 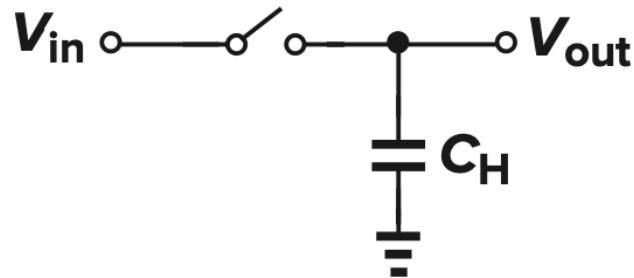



NMOS and PMOS Switches

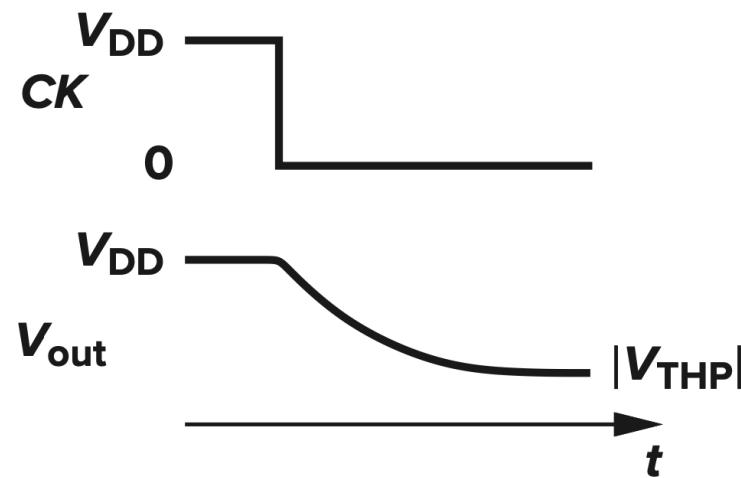  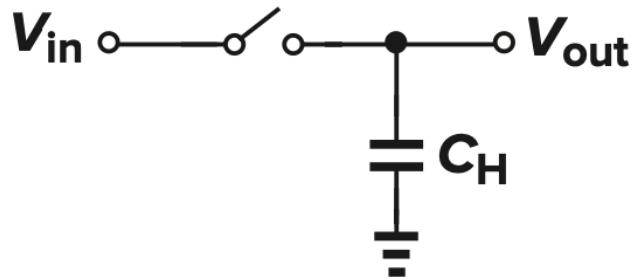



Speed Considerations

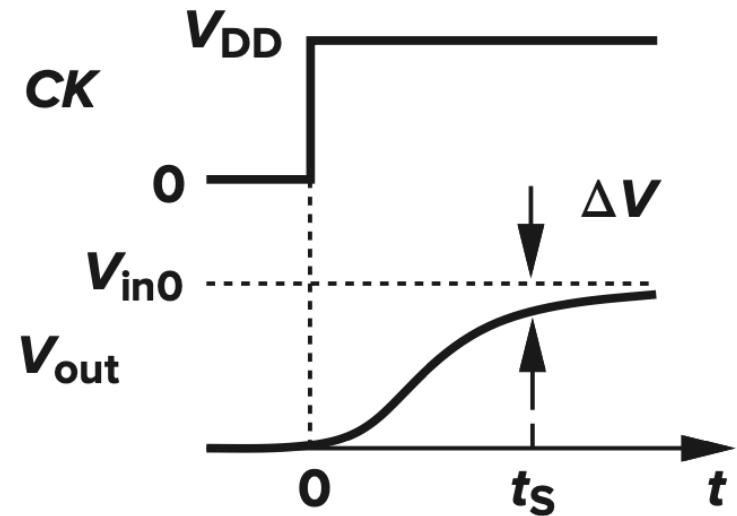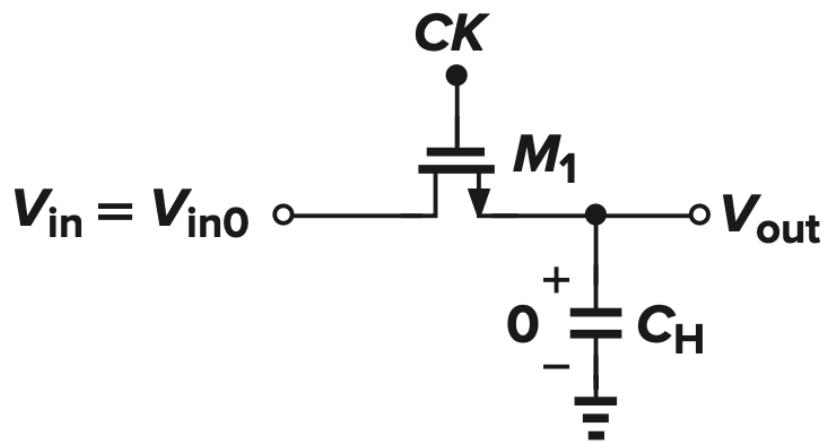

Speed Considerations

 
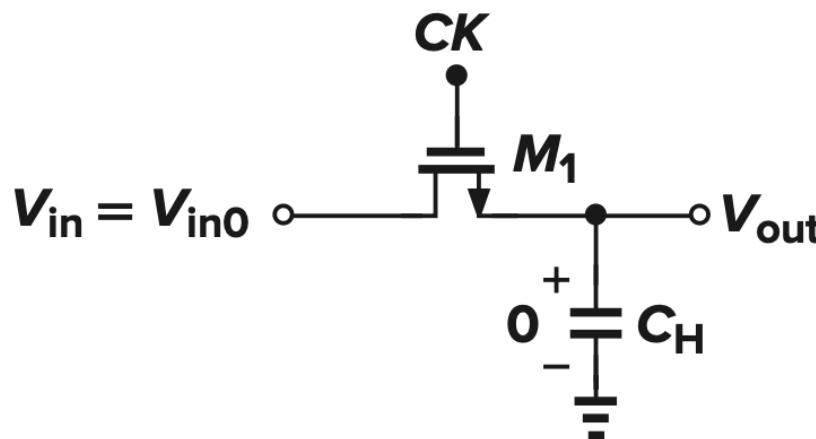


  On-resistance of NMOS and PMOS devices as a function of input voltage



Speed Considerations: Complementary Switch

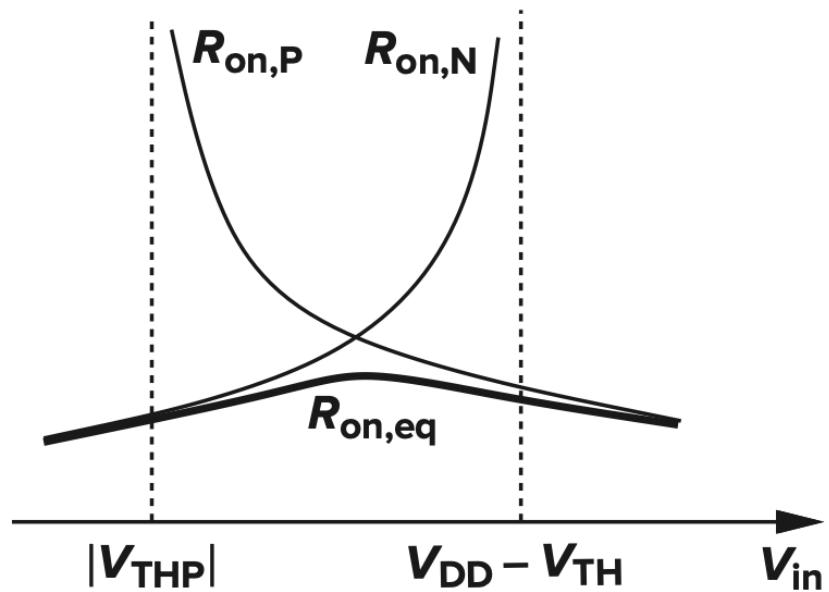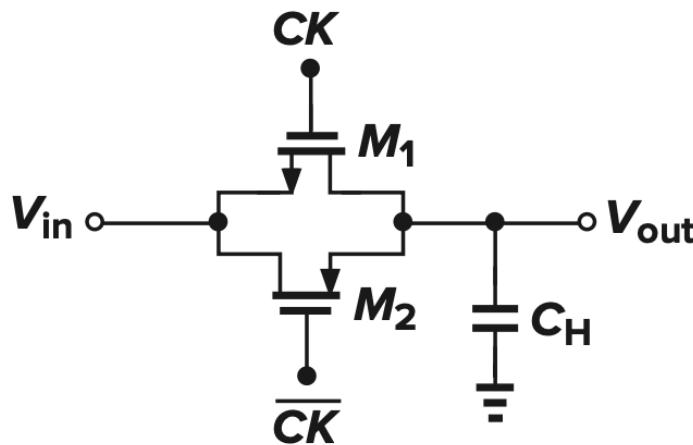
On-resistance of the complementary switch



Precision Considerations

- A larger W/L or a smaller sampling capacitor in MOS switches results in a higher speed.
- However, these methods of increasing the speed degrade the precision with which the signal is sampled
- Three mechanisms in MOS transistor operation introduce error at the instant the switch turns off:
 - Channel Charge Injection
 - Clock Feedthrough
 - kT/C Noise


Channel Charge Injection

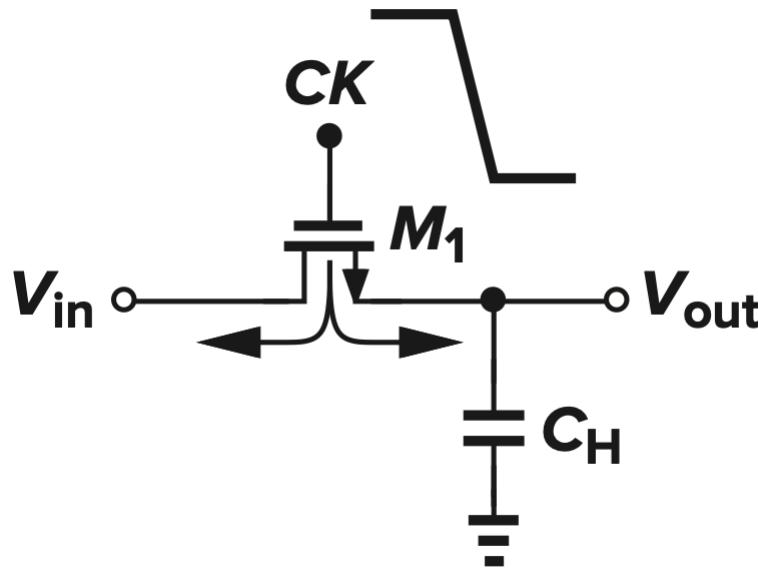

$$Q_{ch} = WLC_{ox}(V_{DD} - V_{in} - V_{TH})$$



 
$$\Delta V = \frac{WLC_{ox}(V_{DD} - V_{in} - V_{TH})}{2C_H}$$



Channel Charge Injection

$$V_{out} \approx V_{in} - \frac{WLC_{ox}(V_{DD} - V_{in} - V_{TH})}{C_H}$$

 
$$V_{out} = V_{in} \left(1 + \frac{WLC_{ox}}{C_H} \right) - \frac{WLC_{ox}}{C_H} (V_{DD} - V_{TH})$$



Channel Charge Injection

$$V_{out} \approx V_{in} - \frac{WLC_{ox}(V_{DD} - V_{in} - V_{TH})}{C_H}$$
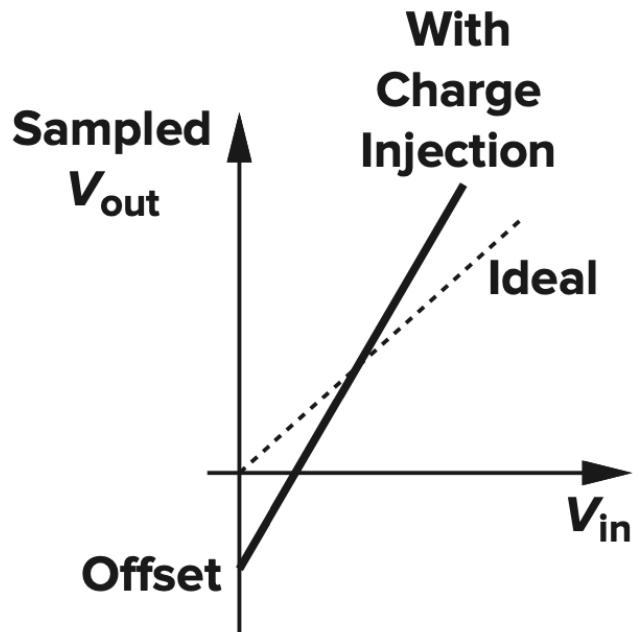
$$V_{out} = V_{in} \left(1 + \frac{WLC_{ox}}{C_H} \right) - \frac{WLC_{ox}}{C_H} (V_{DD} - V_{TH})$$



$$V_{TH} = V_{TH0} + \gamma (\sqrt{2\phi_B + V_{SB}} - \sqrt{2\phi_B})$$

Speed-Precision Trade-off due to Charge Injection

$$F = (\tau \Delta V)^{-1}$$


$$\tau = R_{on} C_H$$

$$= \frac{1}{\mu_n C_{ox} (W/L) (V_{DD} - V_{in} - V_{TH})} C_H$$

$$\Delta V = \frac{WLC_{ox}}{C_H} (V_{DD} - V_{in} - V_{TH})$$

$$F = \frac{\mu_n}{L^2}$$


Clock Feedthrough

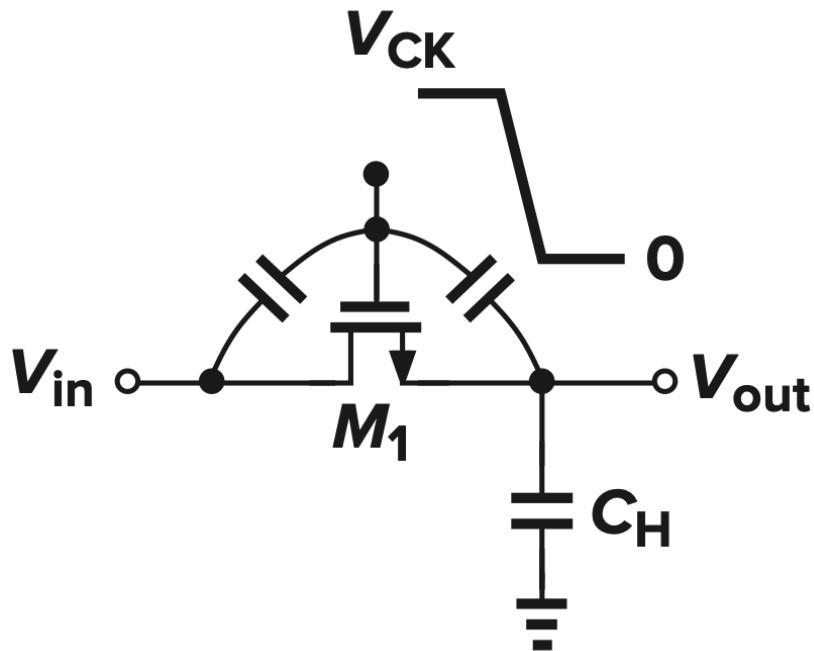

$$\Delta V = V_{CK} \frac{W C_{ov}}{W C_{ov} + C_H}$$


kT/C Noise

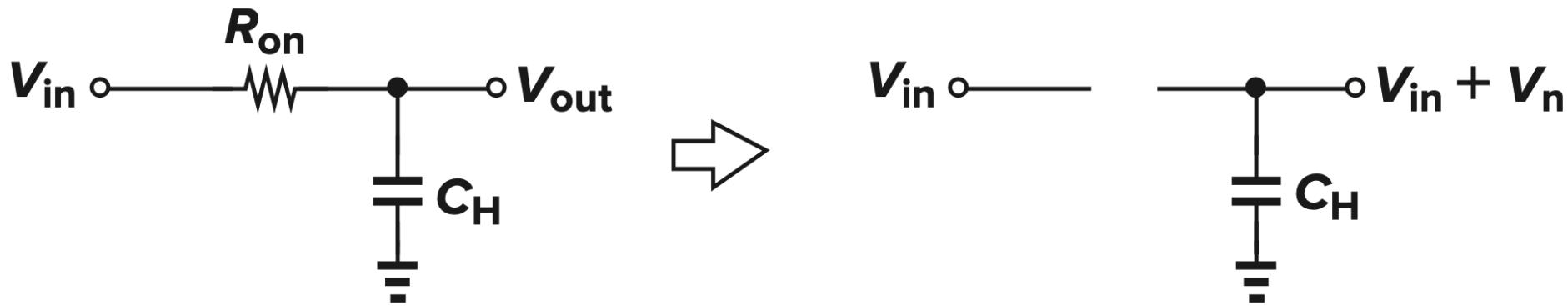- The on-resistance of the switch introduces thermal noise at the output
- When the switch turns off, this noise is stored on the capacitor along with the instantaneous value of the input voltage
- The rms voltage of the sampled noise is $\sim \sqrt{kT/C}$




Charge Injection Cancellation

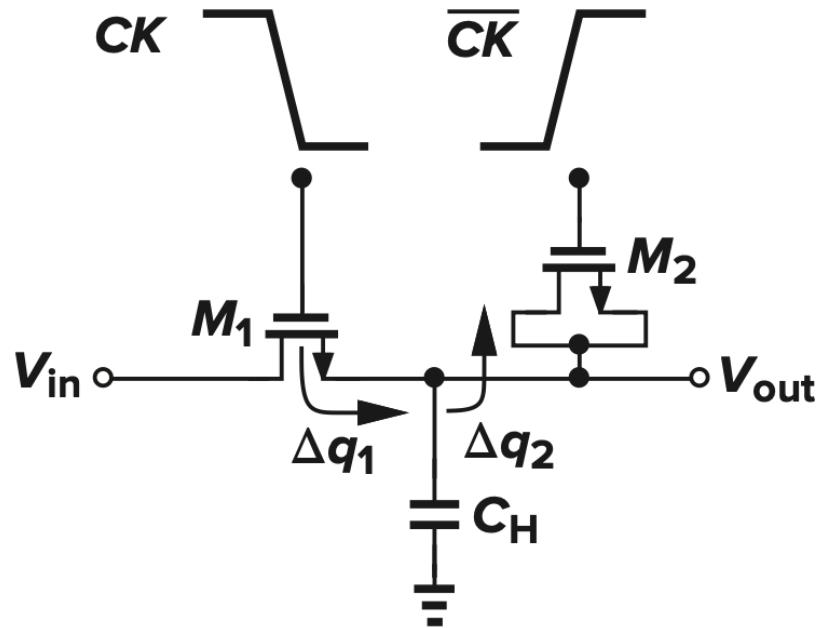- The charge injected by the main transistor can be removed by means of a second “dummy” transistor



Charge Injection Cancellation

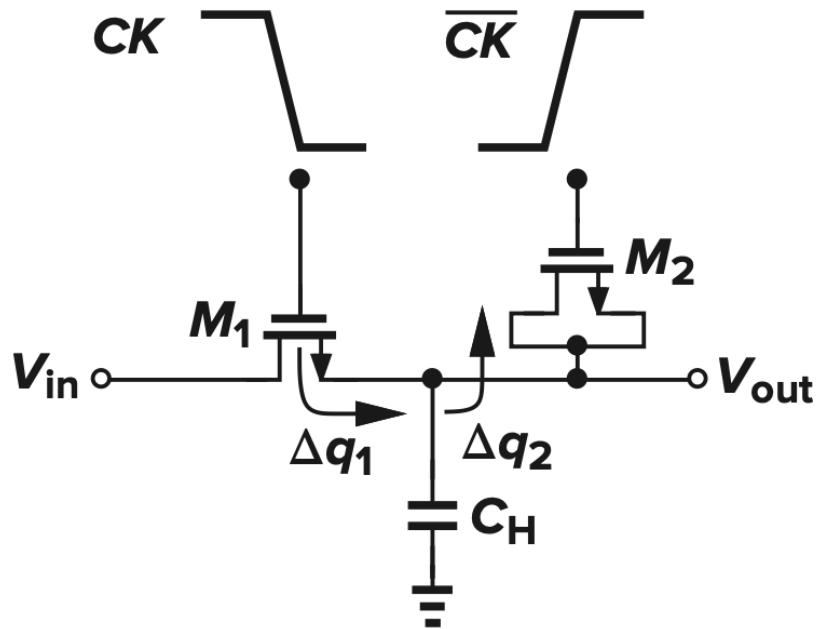- The charge injected by the main transistor can be removed by means of a second “dummy” transistor




$$\Delta q_1 = \frac{W_1 L_1 C_{ox}}{2} (V_{CK} - V_{in} - V_{TH1})$$

$$\Delta q_2 = W_2 L_2 C_{ox} (V_{CK} - V_{in} - V_{TH2})$$



$W_2 = 0.5W_1$ and $L_2 = L_1$, then $\Delta q_2 = \Delta q_1$ X


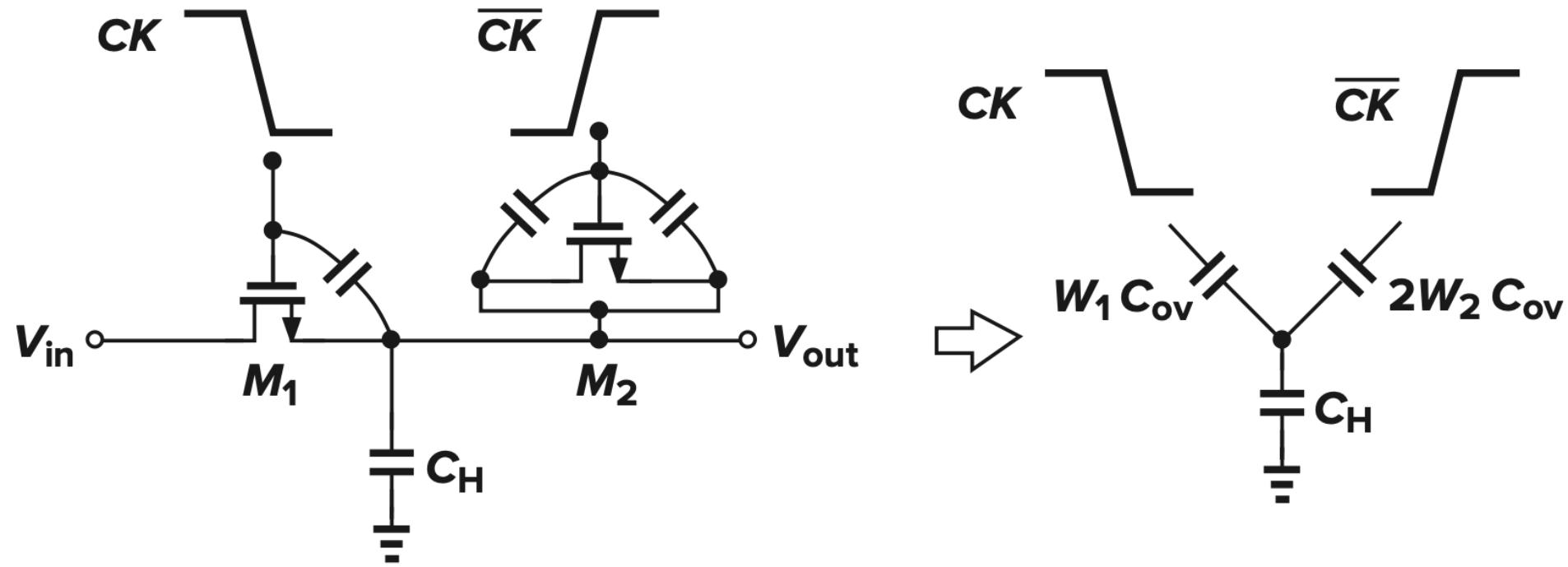
Clock feedthrough suppression by dummy switch




$$-V_{CK} \frac{W_1 C_{ov}}{W_1 C_{ov} + C_H + 2W_2 C_{ov}} + V_{CK} \frac{2W_2 C_{ov}}{W_1 C_{ov} + C_H + 2W_2 C_{ov}} = 0$$

Capacitors in CMOS technology


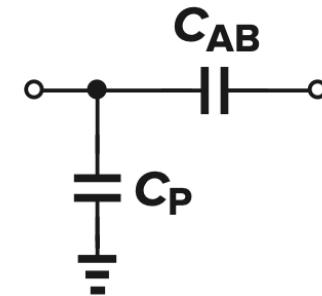
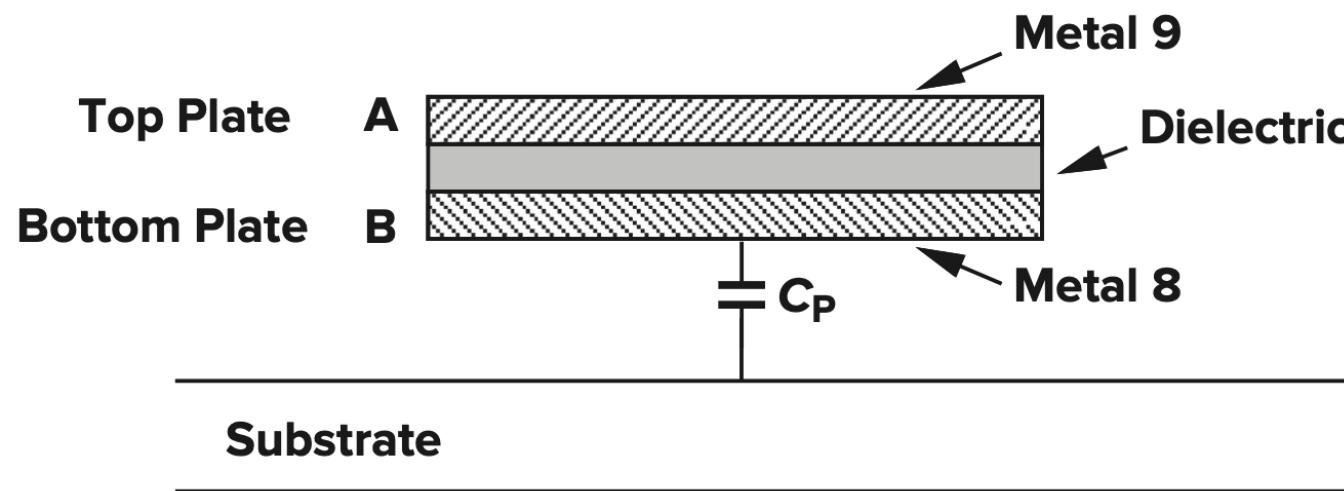
- Capacitors in CMOS technology: The “top plate” and the “bottom plate” are realized by metal layers
- The bottom plate suffers from capacitance C_p to the underlying substrate: a value typically 5 to 10% of the main capacitance





Switched-Capacitor Amplifiers

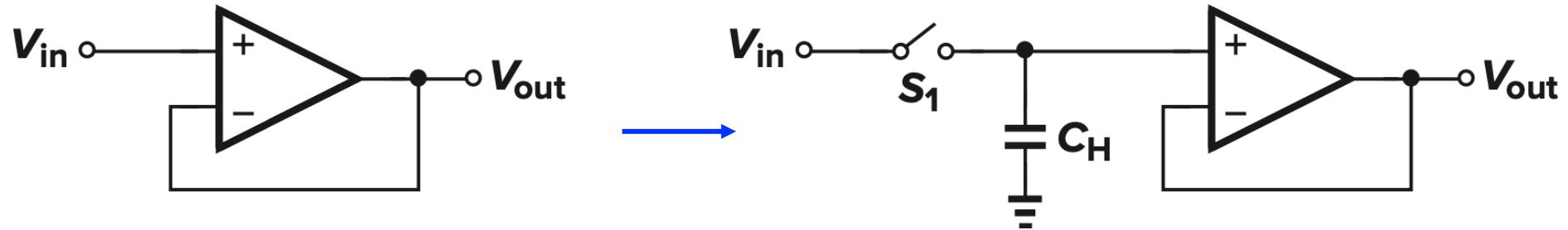




Switched-Capacitor Amplifiers

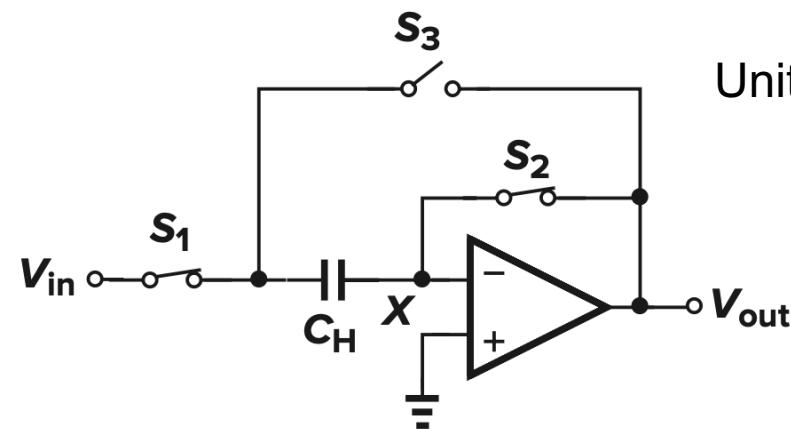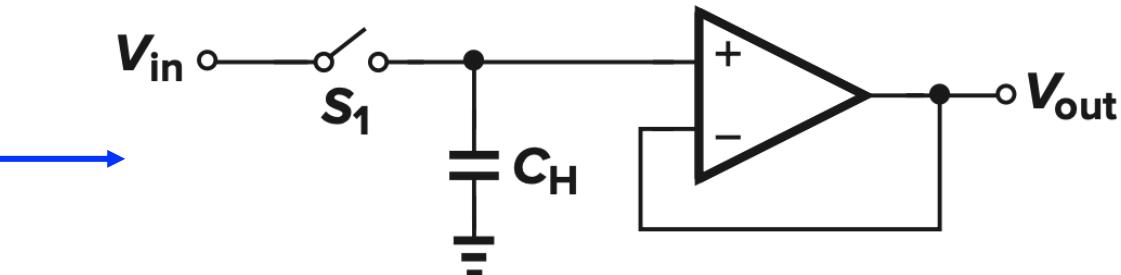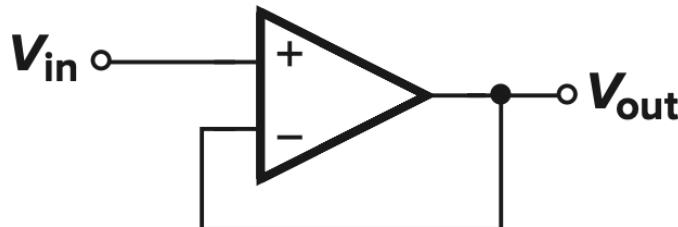






Unity-gain sampler

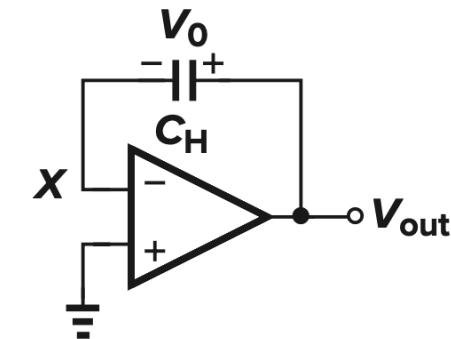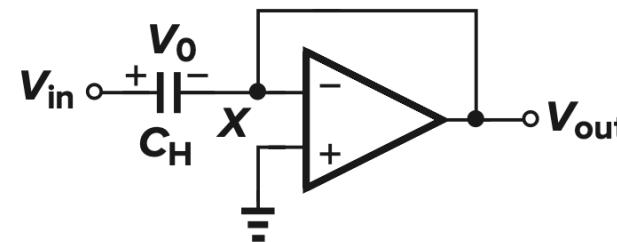

Switched-Capacitor Amplifiers

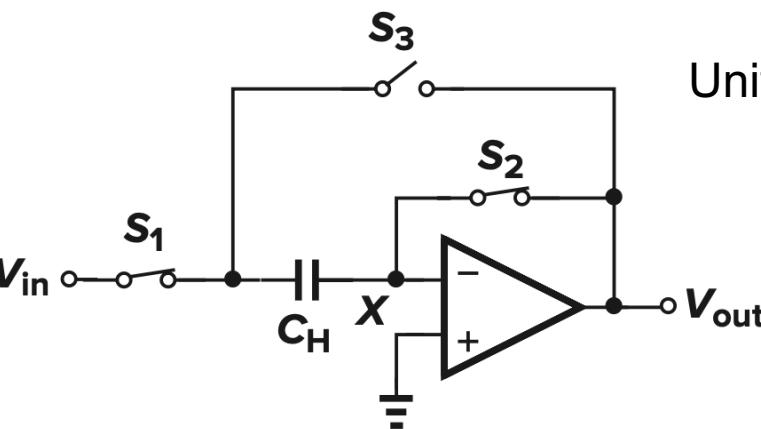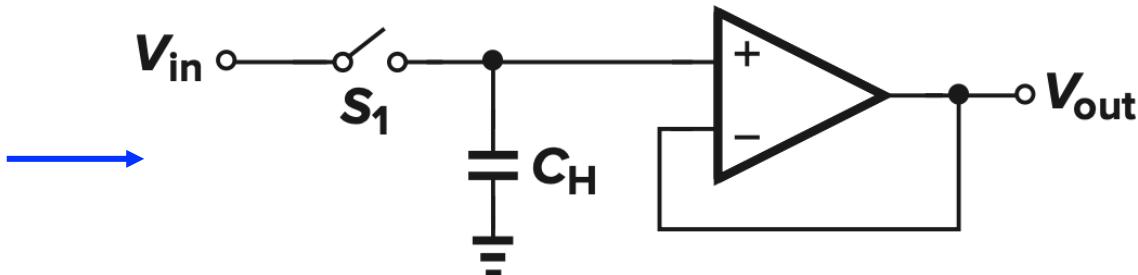
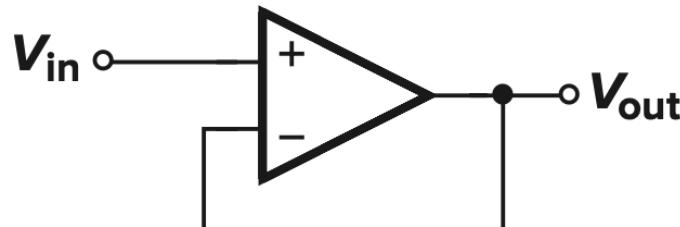


Unity-gain sampler

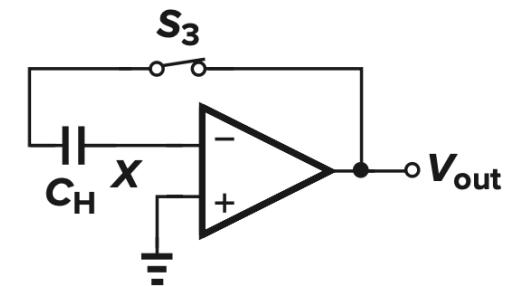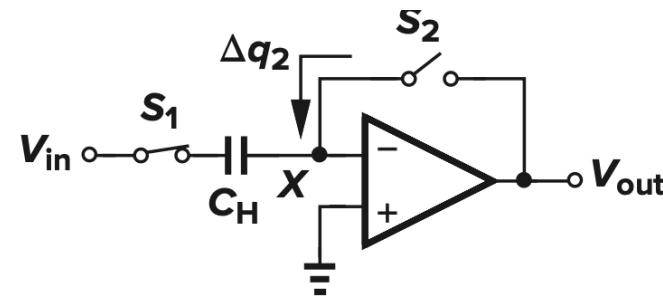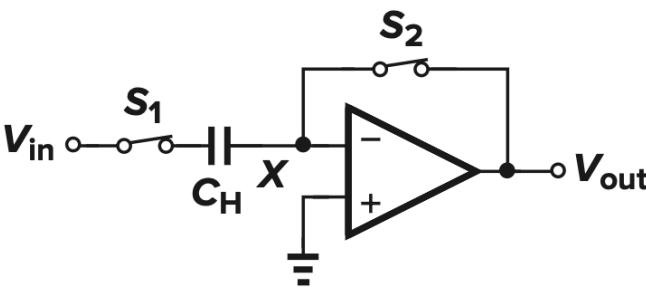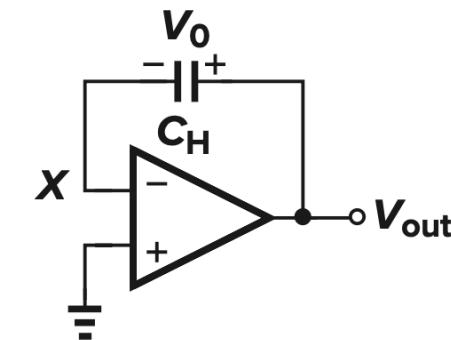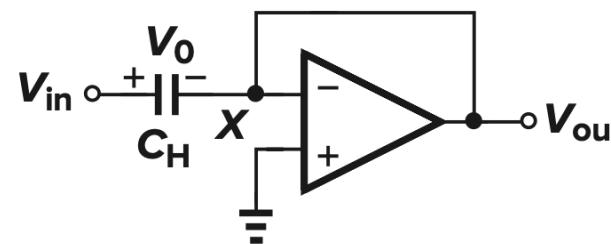


Unity-gain sampler

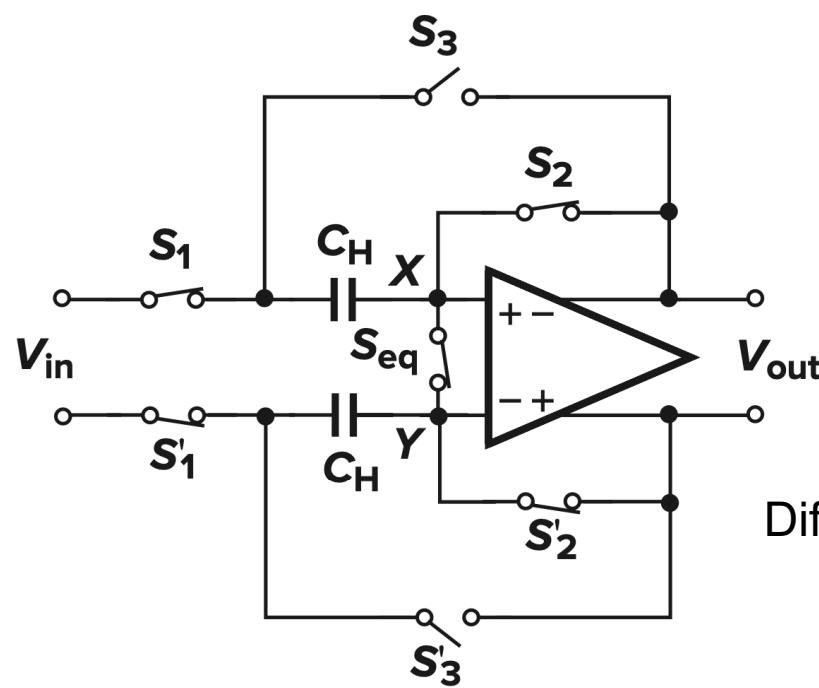 Generation of proper clock edges for unity-gain sampler




Differential realization of unity-gain sampler


Bottom-plate sampling

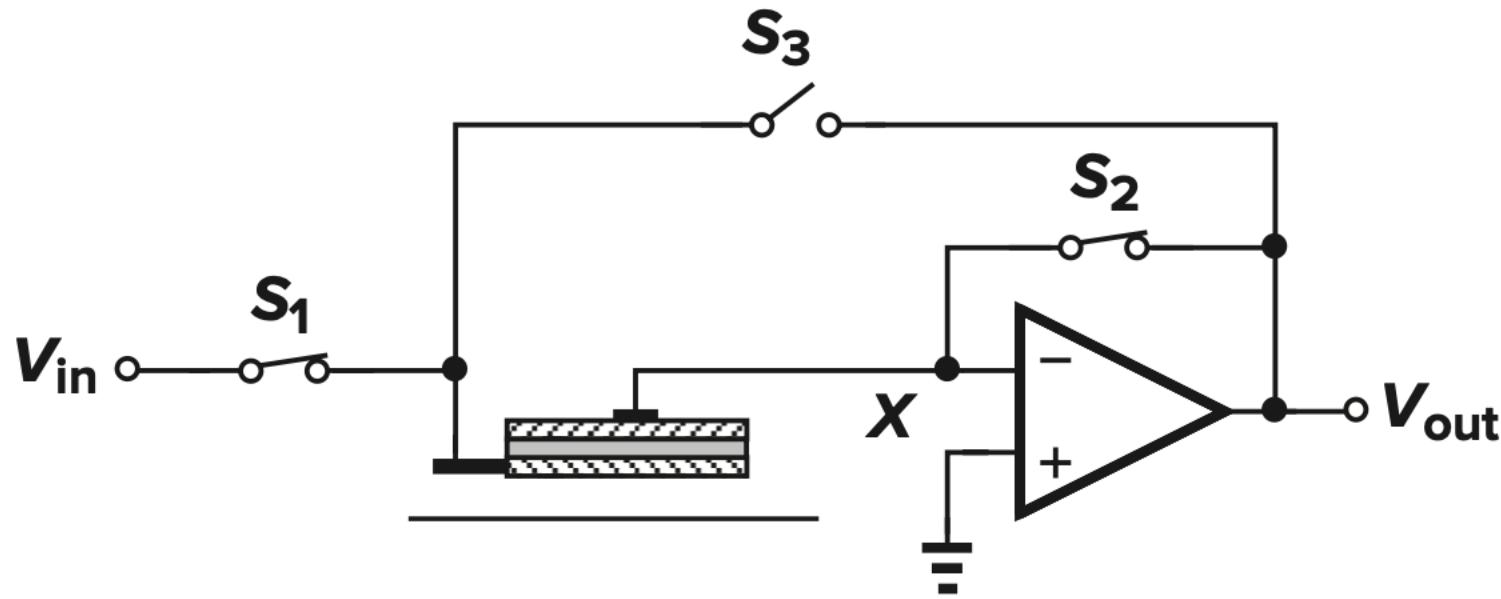


Noninverting Amplifier

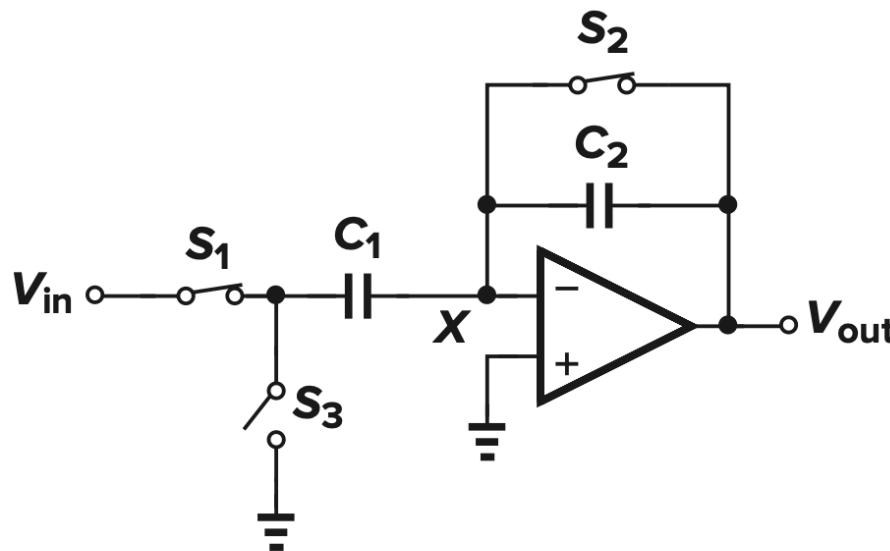

(a)

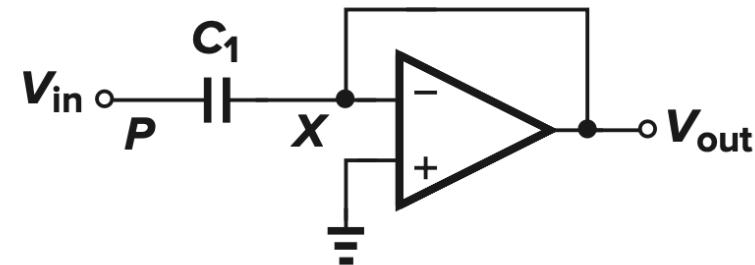

(b)

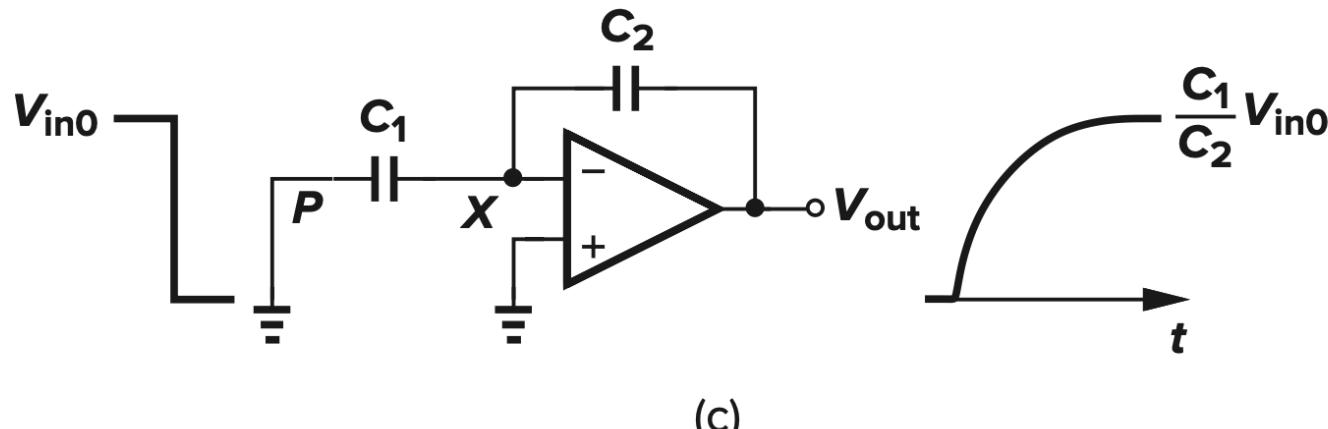

(c)

Differential realization of noninverting amplifier

