
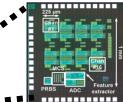


***Integrated Neurotechnologies
Laboratory***

EPFL

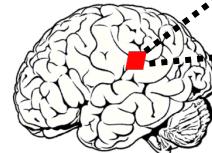

Advanced analog integrated circuit design (EE-523), Lecture 5

Prof. Mahsa Shoaran


Institutes of Electrical and Micro Engineering and Neuro-X, School of Engineering, EPFL

Recap: Switched-Capacitor Circuits



- **Continuous-time circuits:** Input and output are continuous signals
- **Discrete-time circuits:** Process input at periodic instants of time

Recap: Switched-Capacitor Circuits


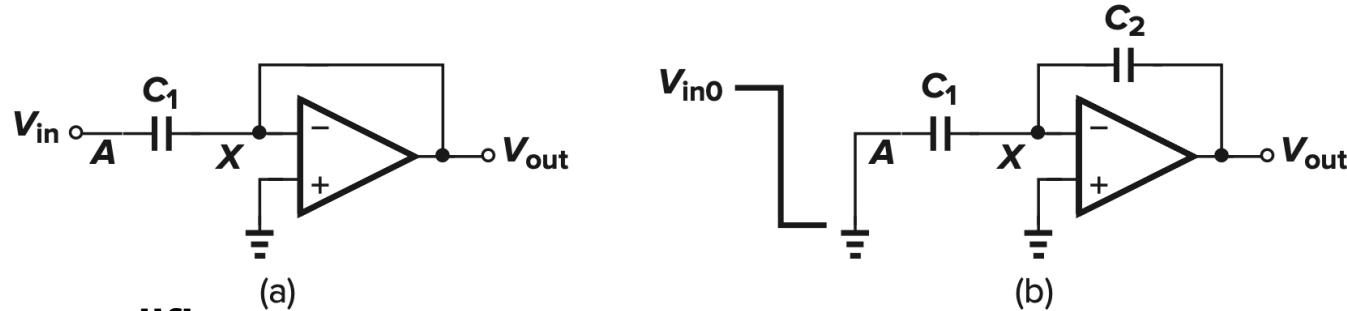
- **Continuous-time circuits:** Input and output are continuous signals
- **Discrete-time circuits:** Process input at periodic instants of time





Switched-capacitor amplifier

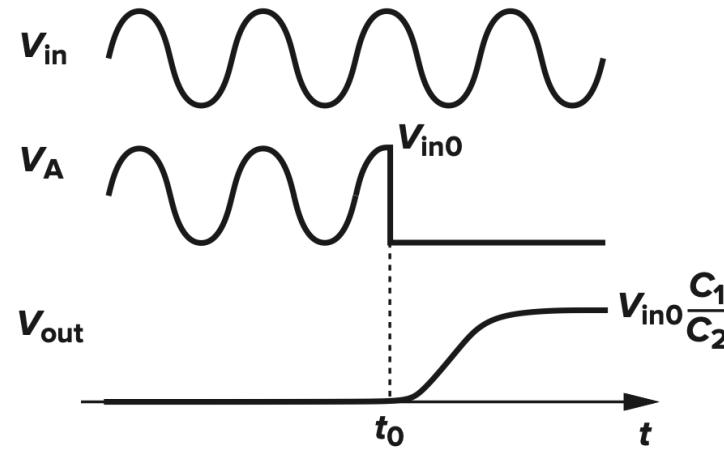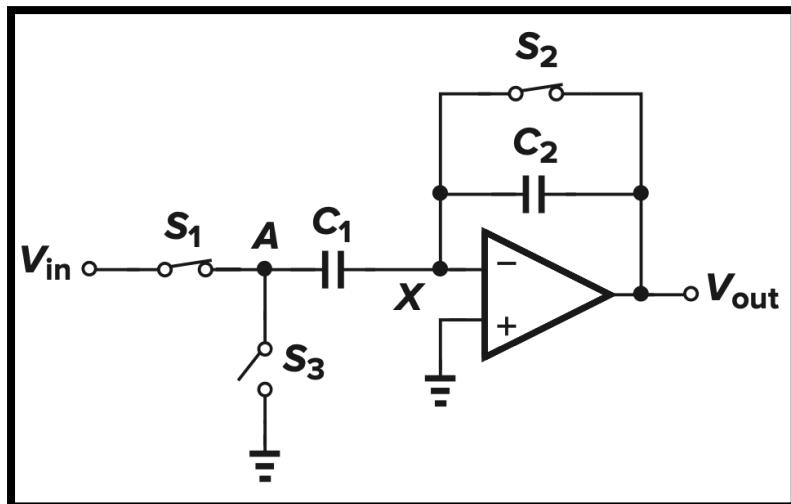

Recap: SC Circuits – Speed and Precision

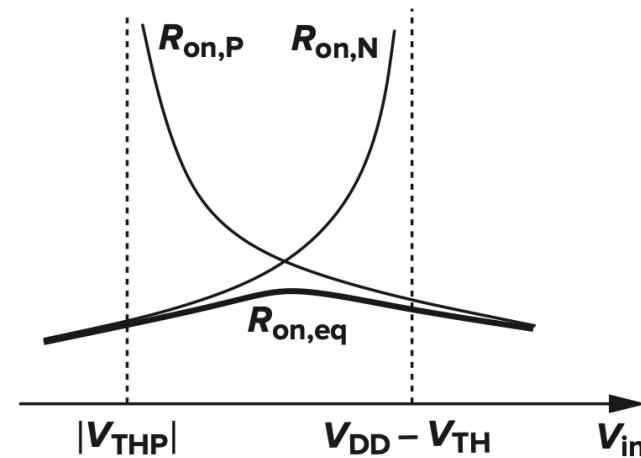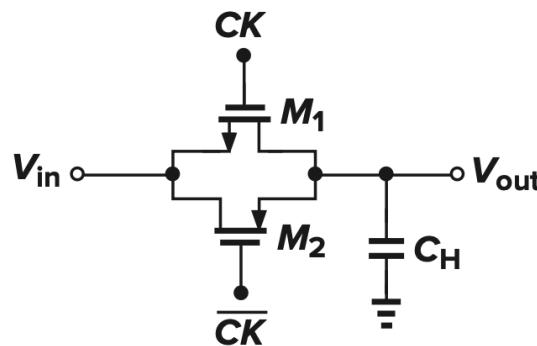


Recap: SC Circuits – Speed and Precision

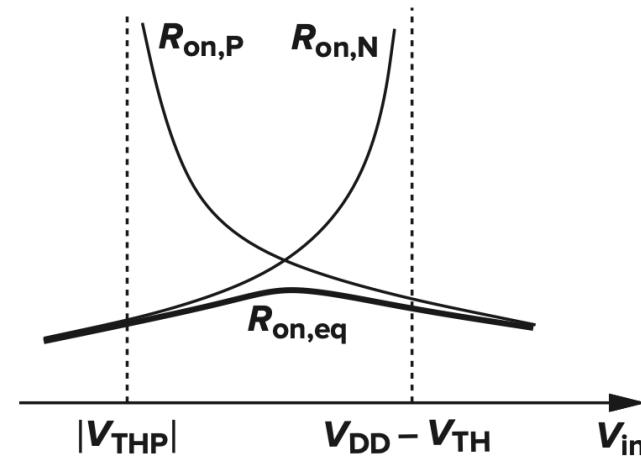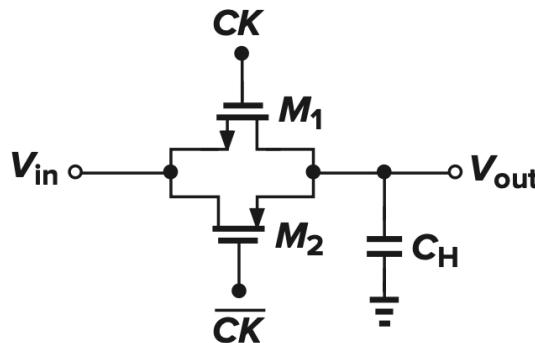


- Three mechanisms introduce error at the instant the MOS switch turns off:
 - Channel Charge Injection
 - Clock Feedthrough
 - kT/C Noise

Clock Feedthrough

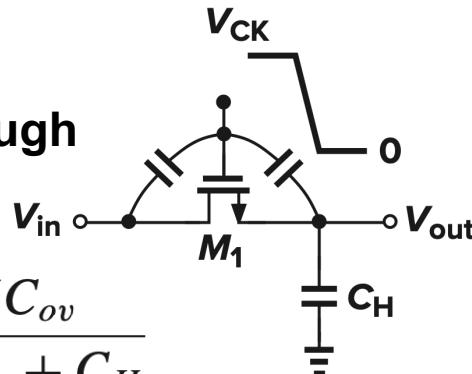


$$\Delta V = V_{CK} \frac{W C_{ov}}{W C_{ov} + C_H}$$

Channel Charge Injection



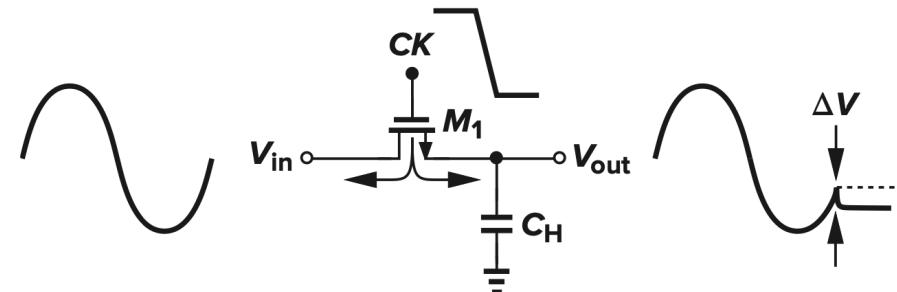


$$\Delta V = \frac{W L C_{ox} (V_{DD} - V_{in} - V_{TH})}{2 C_H}$$



Switched-Capacitor Amplifiers

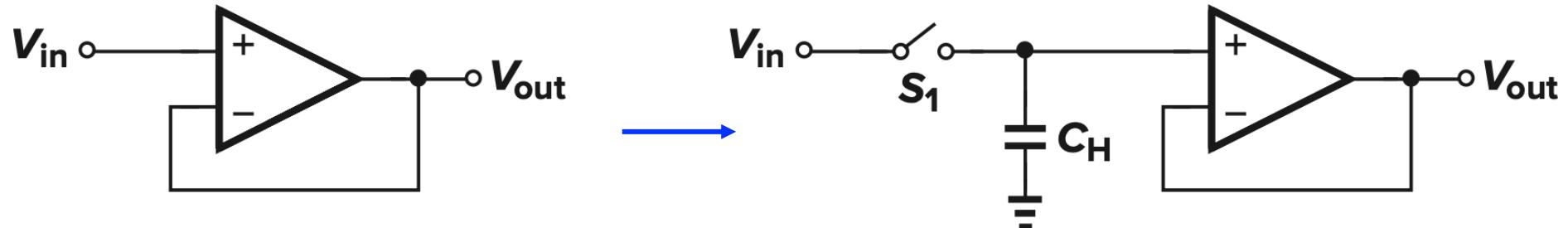




Switched-Capacitor Amplifiers

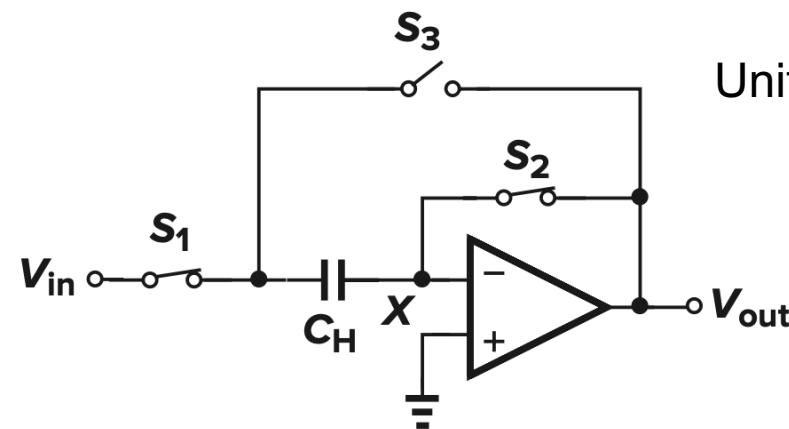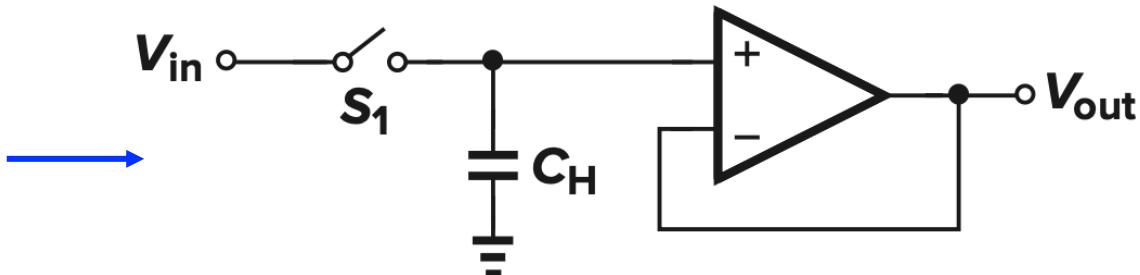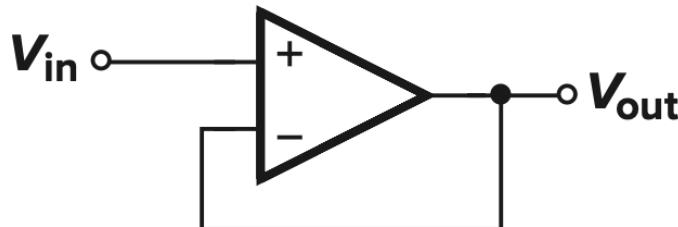






Unity-gain sampler

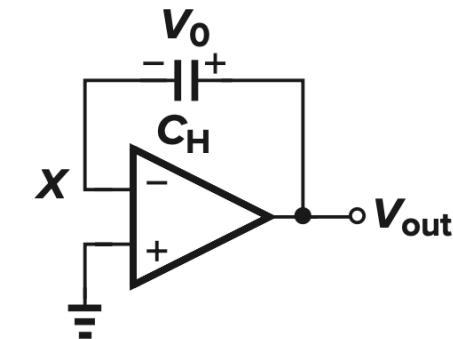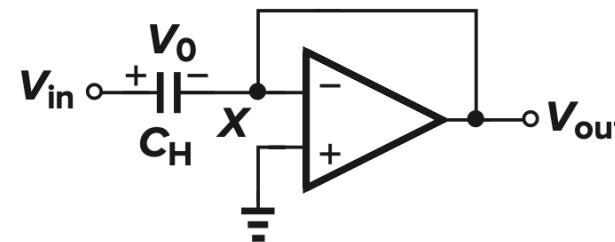

Switched-Capacitor Amplifiers

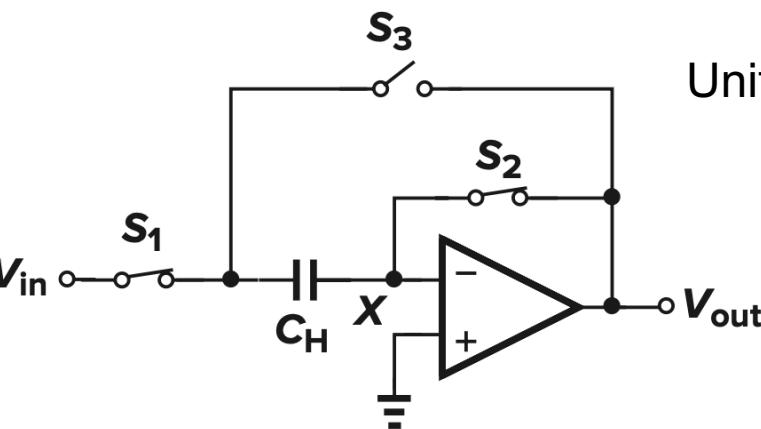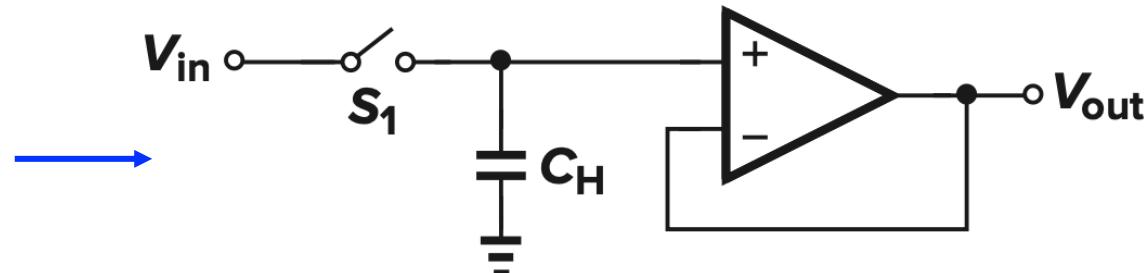
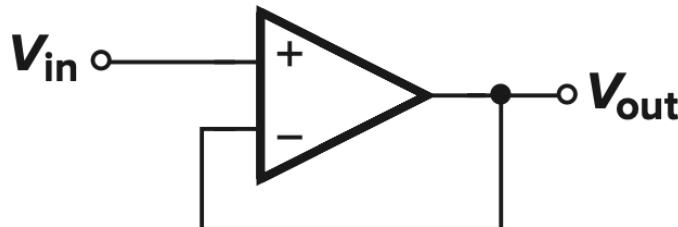


Unity-gain sampler

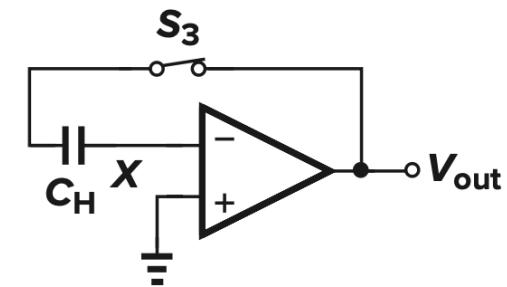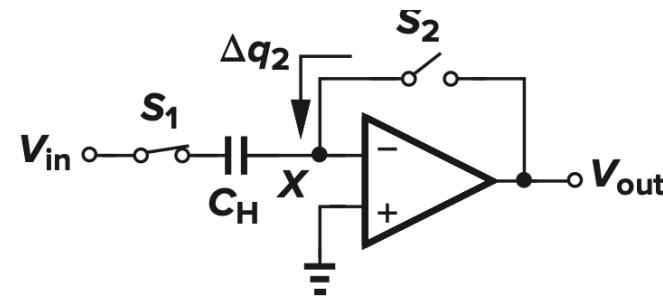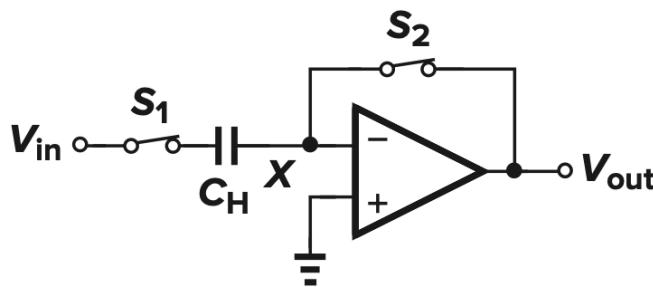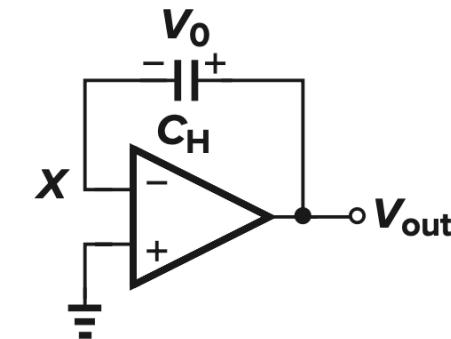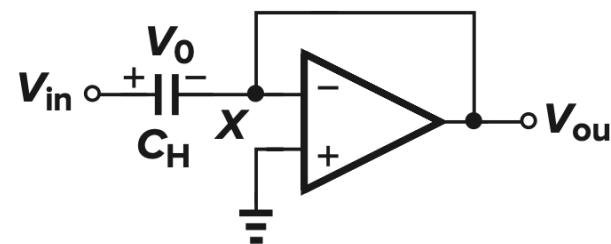


Unity-gain sampler

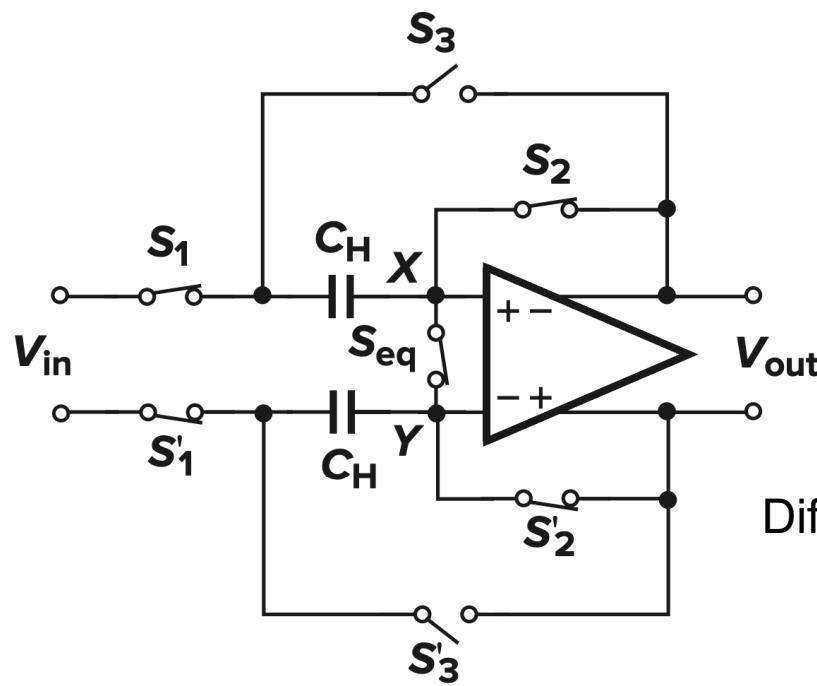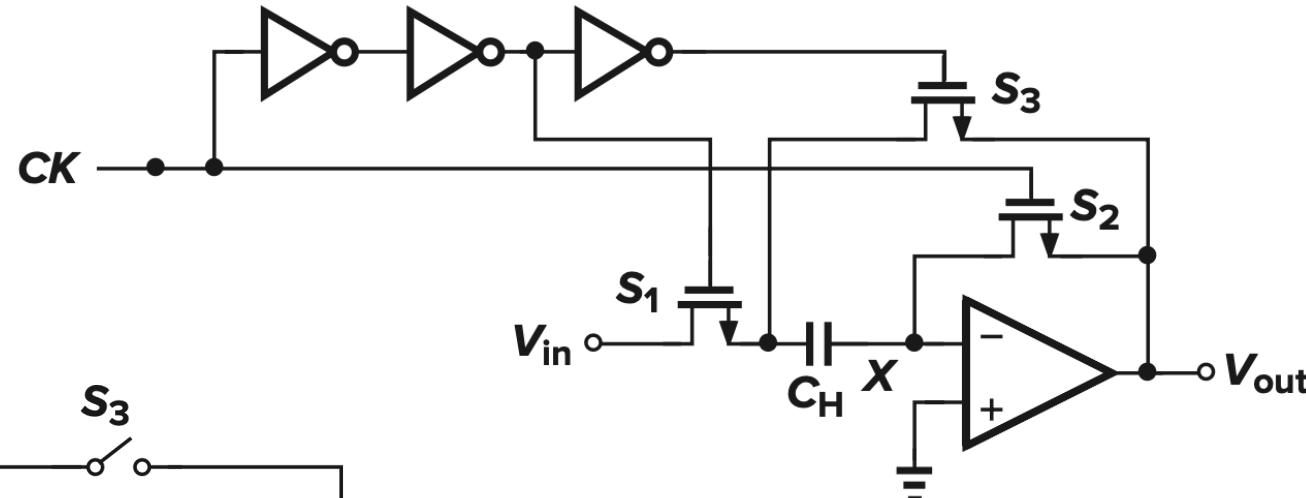Generation of proper clock edges for unity-gain sampler




Differential realization of unity-gain sampler


Bottom-plate sampling

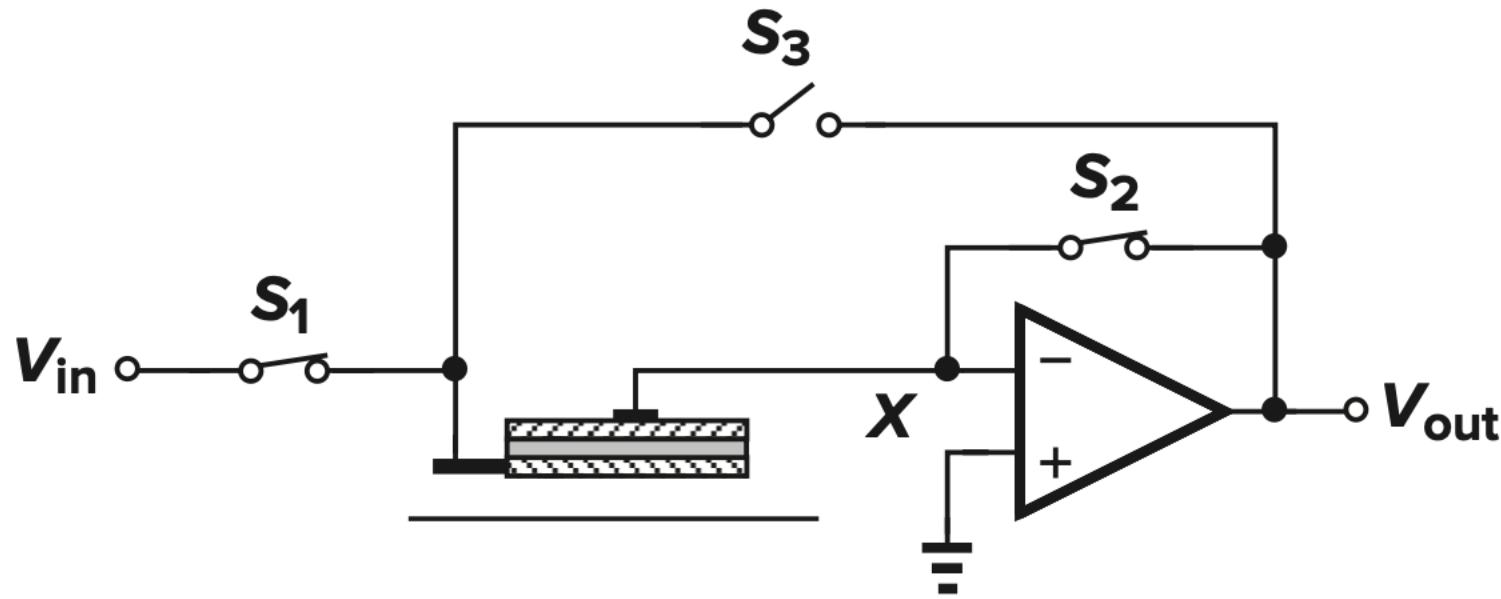


Noninverting Amplifier

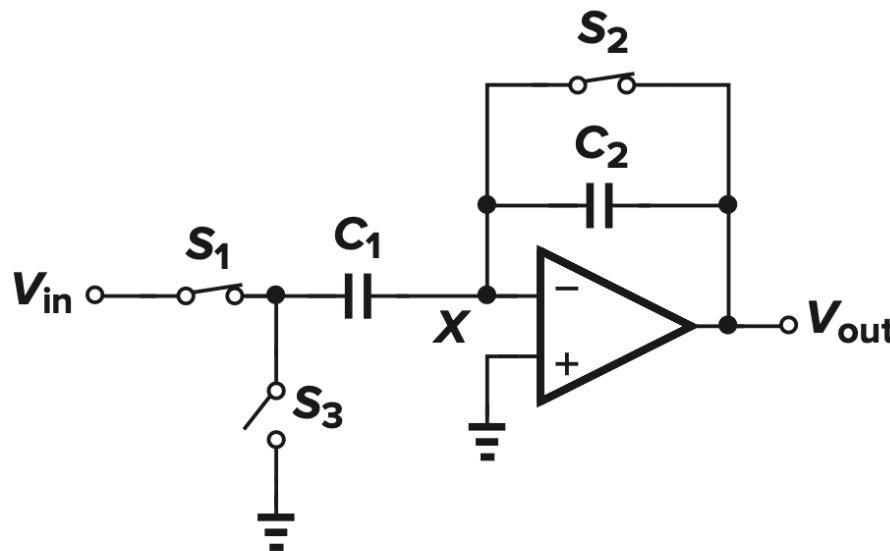

(a)

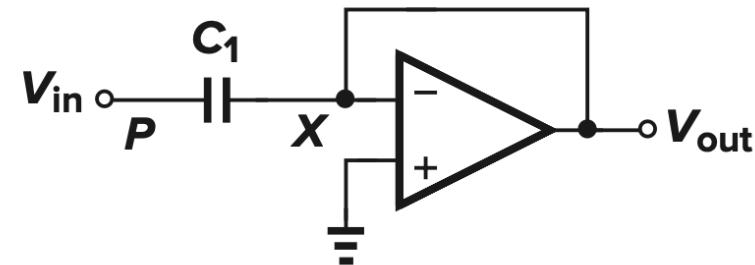


(b)

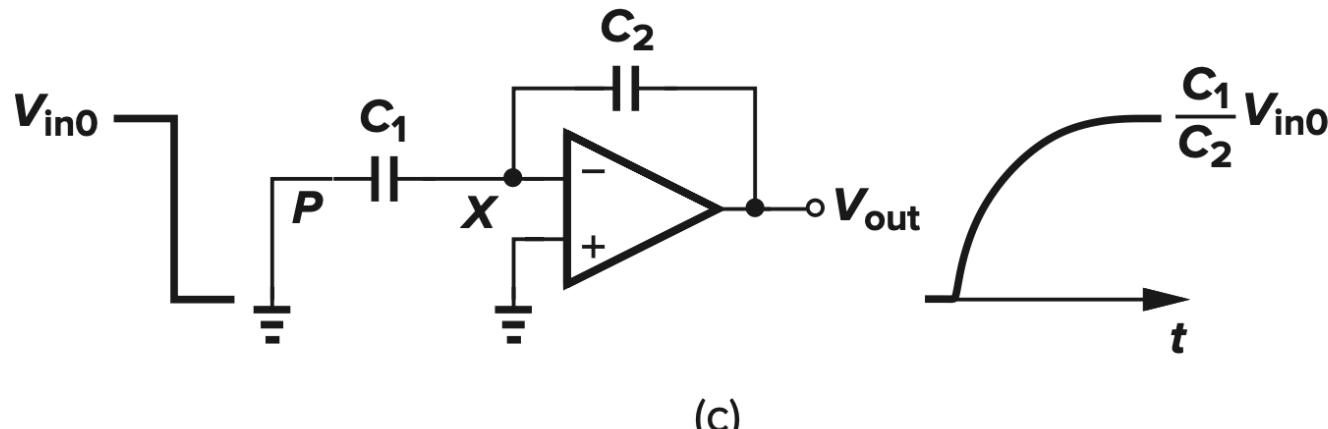

(c)

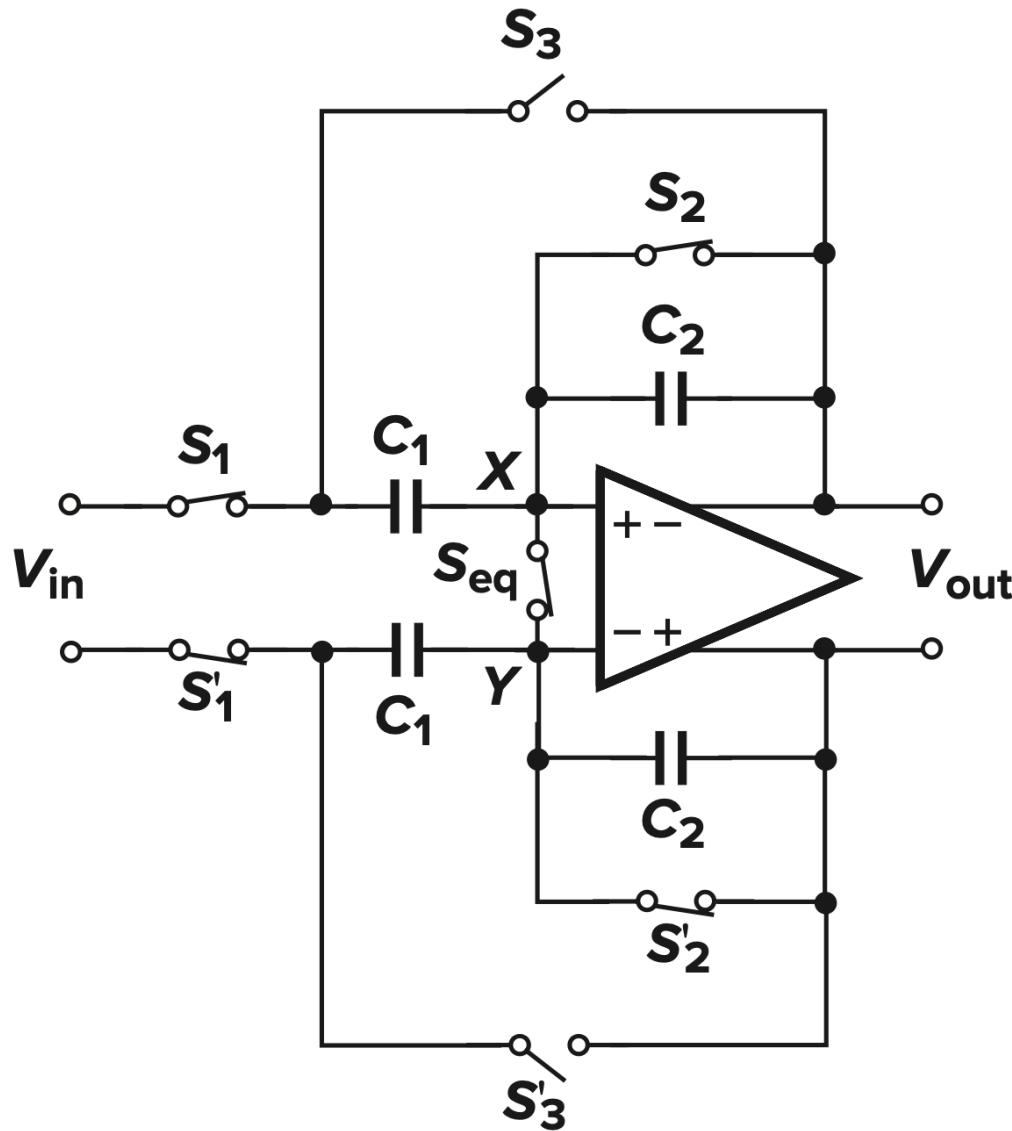Differential realization of noninverting amplifier




Nonlinearity

- Two types of nonidealities: **nonlinearity and mismatch**



Nonlinearity

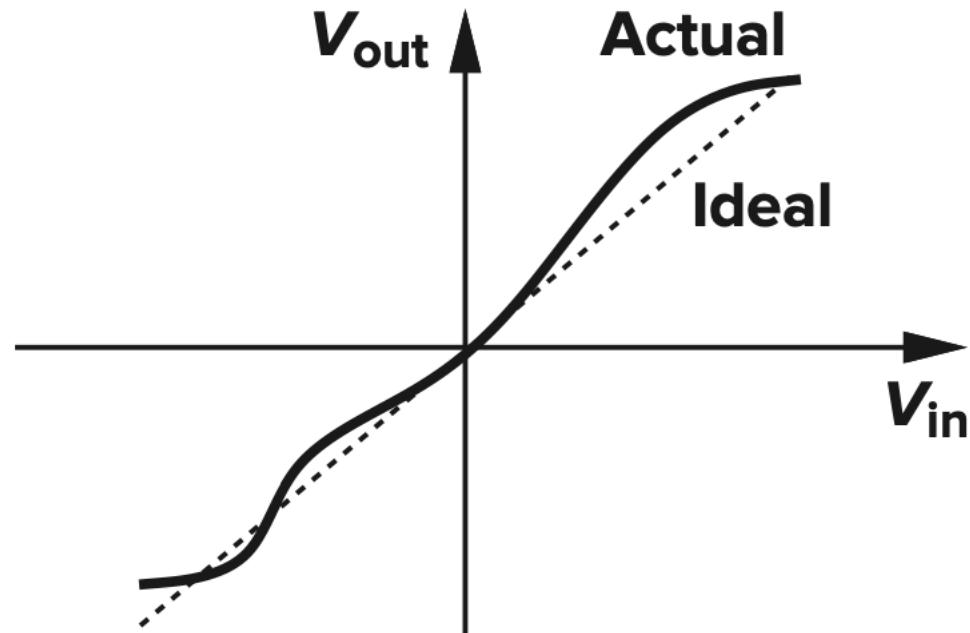- Two types of nonidealities: **nonlinearity** and mismatch




Nonlinearity Examples

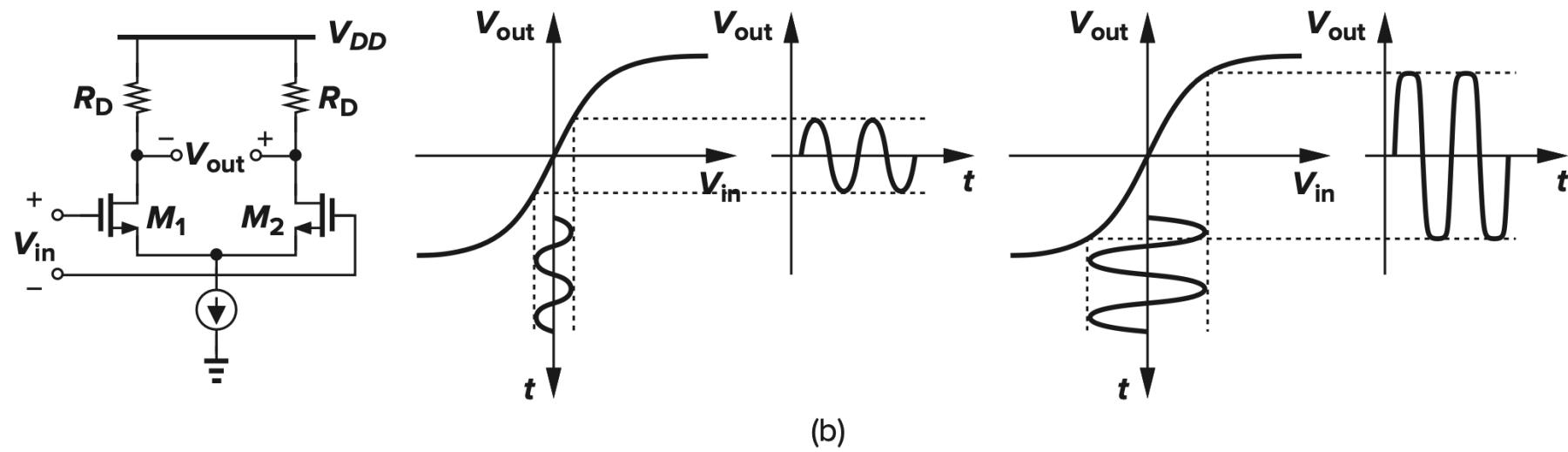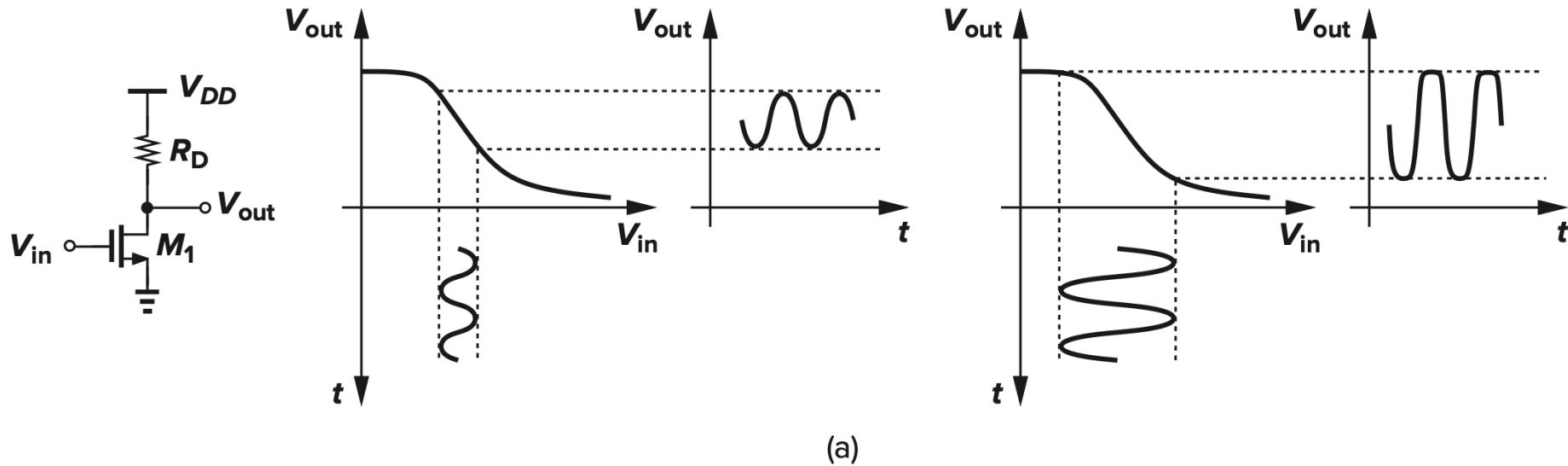Distortion in (a) a common-source stage and (b) a differential pair




Nonlinearity Behavior

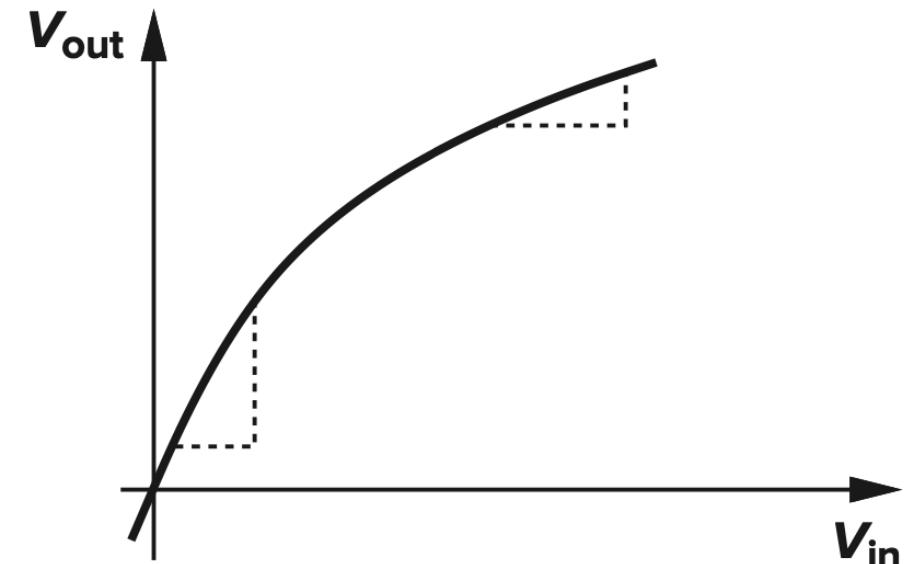Variation of small-signal gain in a nonlinear amplifier



(a)

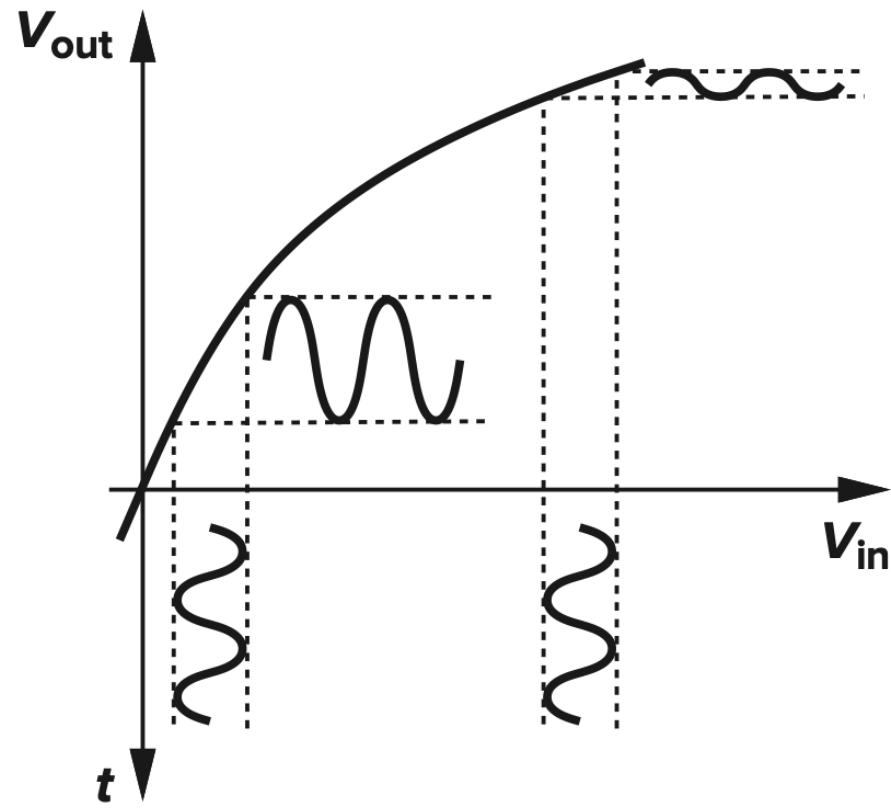


(b)

Nonlinearity Definition

$$y(t) = \alpha_1 x(t) + \alpha_2 x^2(t) + \alpha_3 x^3(t) + \dots$$

Nonlinearity Definition
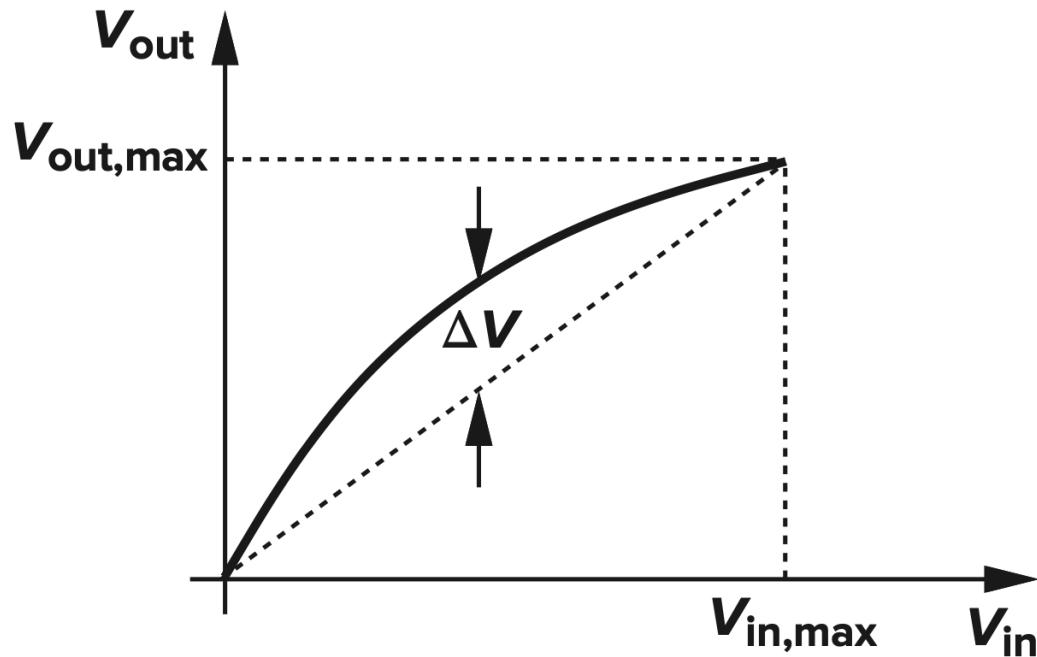
$$y(t) = \alpha_1 x(t) + \alpha_2 x^2(t) + \alpha_3 x^3(t) + \dots$$



1% nonlinearity ($\Delta V / V_{out,max} = 0.01$)

Nonlinearity Definition

$$\begin{aligned}y(t) &= \alpha_1 A \cos \omega t + \alpha_2 A^2 \cos^2 \omega t + \alpha_3 \cos^3 \omega t + \dots \\&= \alpha_1 A \cos \omega t + \frac{\alpha_2 A^2}{2} [1 + \cos(2\omega t)] + \frac{\alpha_3 A^3}{4} [3 \cos \omega t + \cos(3\omega t)] + \dots\end{aligned}$$

Total Harmonic Distortion

$$\text{THD} = \frac{(\alpha_2 A^2/2)^2 + (\alpha_3 A^3/4)^2}{(\alpha_1 A + 3\alpha_3 A^3/4)^2}$$

Nonlinearity Definition

$$y(t) = \alpha_1 A \cos \omega t + \alpha_2 A^2 \cos^2 \omega t + \alpha_3 \cos^3 \omega t + \dots$$

$$= \alpha_1 A \cos \omega t + \frac{\alpha_2 A^2}{2} [1 + \cos(2\omega t)] + \frac{\alpha_3 A^3}{4} [3 \cos \omega t + \cos(3\omega t)] + \dots$$


Total Harmonic Distortion

$$\text{THD} = \frac{(\alpha_2 A^2/2)^2 + (\alpha_3 A^3/4)^2}{(\alpha_1 A + 3\alpha_3 A^3/4)^2}$$

Nonlinearity of Differential Circuits:

$$y(t) = \alpha_1 x(t) + \alpha_3 x^3(t) + \alpha_5 x^5(t) + \dots$$

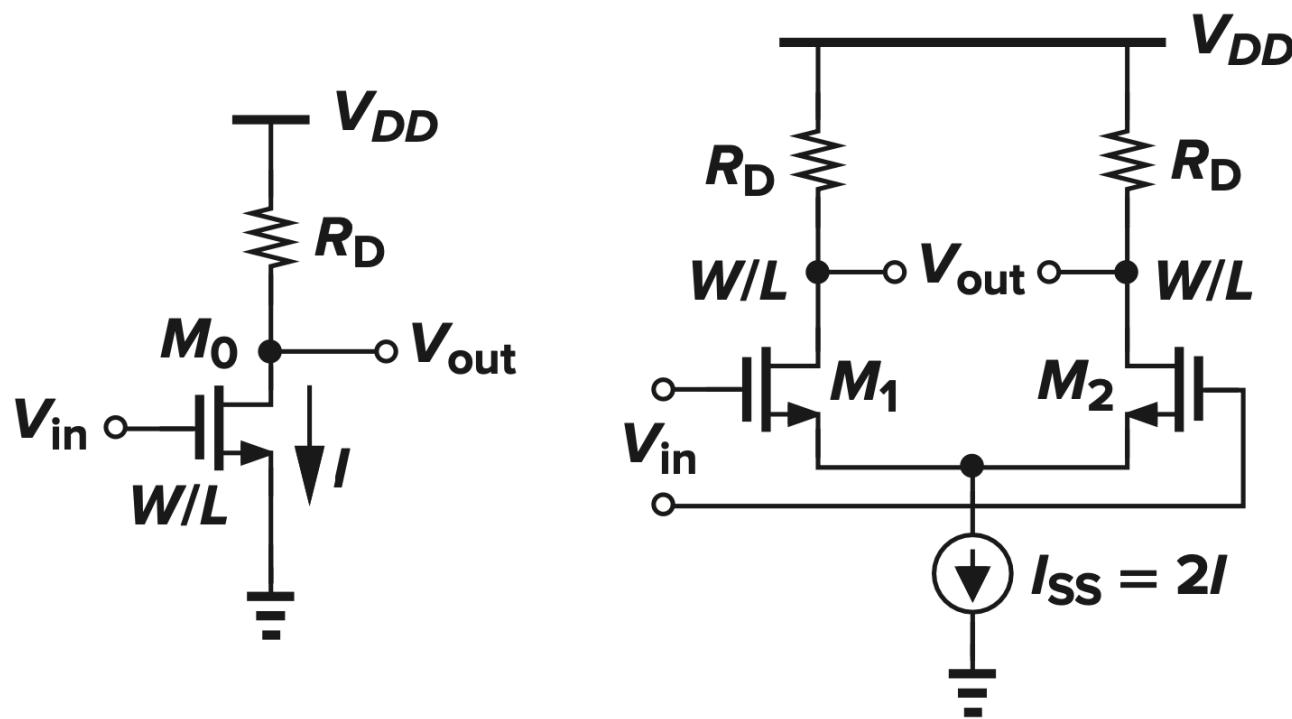Nonlinearity: Single-ended and differential amplifiers



$$|A_v| \approx g_m R_D$$

$$= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) R_D$$

Nonlinearity: Single-ended amplifiers

$$\begin{aligned} I_{D0} &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH} + V_m \cos \omega t)^2 \\ &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 + \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) V_m \cos \omega t \\ &\quad + \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_m^2 \cos^2 \omega t \\ &= I + \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) V_m \cos \omega t + \frac{1}{4} \mu_n C_{ox} \frac{W}{L} V_m^2 [1 + \cos(2\omega t)] \end{aligned}$$

input signal

$$\boxed{\frac{A_{HD2}}{A_F} = \frac{V_m}{4(V_{GS} - V_{TH})}}$$

Nonlinearity: Differential amplifiers

$$\begin{aligned} I_{D1} - I_{D2} &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{in} \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - V_{in}^2} \\ &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{in} \sqrt{4(V_{GS} - V_{TH})^2 - V_{in}^2} \end{aligned}$$

Nonlinearity: Differential amplifiers

$$\begin{aligned} I_{D1} - I_{D2} &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{in} \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - V_{in}^2} \\ &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{in} \sqrt{4(V_{GS} - V_{TH})^2 - V_{in}^2} \end{aligned}$$

$$|V_{in}| \ll V_{GS} - V_{TH}$$



$$\begin{aligned} I_{D1} - I_{D2} &= \mu_n C_{ox} \frac{W}{L} V_{in} (V_{GS} - V_{TH}) \sqrt{1 - \frac{V_{in}^2}{4(V_{GS} - V_{TH})^2}} \\ &\approx \mu_n C_{ox} \frac{W}{L} V_{in} (V_{GS} - V_{TH}) \left[1 - \frac{V_{in}^2}{8(V_{GS} - V_{TH})^2} \right] \\ &= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \left[V_m \cos \omega t - \frac{V_m^3 \cos^3 \omega t}{8(V_{GS} - V_{TH})^2} \right] \end{aligned}$$

Nonlinearity: Differential amplifiers

$$I_{D1} - I_{D2} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \left[V_m \cos \omega t - \frac{V_m^3 \cos^3 \omega t}{8(V_{GS} - V_{TH})^2} \right]$$

$$\cos^3 \omega t = [3 \cos \omega t + \cos(3\omega t)]/4$$



$$I_{D1} - I_{D2} = g_m \left[V_m - \frac{3V_m^3}{32(V_{GS} - V_{TH})^2} \right] \cos \omega t - g_m \frac{V_m^3 \cos(3\omega t)}{32(V_{GS} - V_{TH})^2}$$



Single-ended (for comparison)

$$\frac{A_{HD3}}{A_F} \approx \frac{V_m^2}{32(V_{GS} - V_{TH})^2}$$

$$\frac{A_{HD2}}{A_F} = \frac{V_m}{4(V_{GS} - V_{TH})}$$

Capacitor Nonlinearity

- In switched-capacitor circuits, the voltage dependence of capacitors may introduce substantial distortion
- While for a linear capacitor we have $Q = C \cdot V$, for a **voltage-dependent capacitor** $dQ = C \cdot dV$. Thus, the total charge on a capacitor sustaining a voltage V_1 is:


$$Q(V_1) = \int_0^{V_1} C \, dV$$

Capacitor Nonlinearity

- In switched-capacitor circuits, the voltage dependence of capacitors may introduce substantial distortion
- While for a linear capacitor we have $Q = C \cdot V$, for a **voltage-dependent capacitor** $dQ = C \cdot dV$. Thus, the total charge on a capacitor sustaining a voltage V_1 is:

$$Q(V_1) = \int_0^{V_1} C \, dV$$
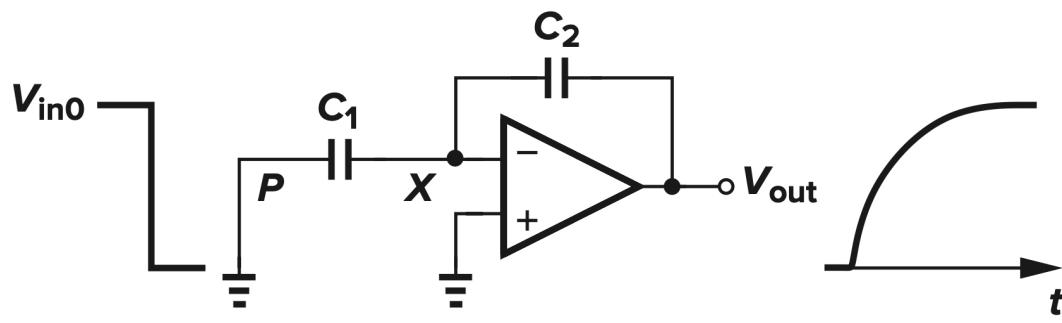
$$C = C_0(1 + \alpha_1 V + \alpha_2 V^2 + \dots)$$



$$\begin{aligned} Q_1 &= \int_0^{V_{in0}} C_1 \, dV \\ &= \int_0^{V_{in0}} M C_0 (1 + \alpha_1 V) \, dV \\ &= M C_0 V_{in0} + M C_0 \frac{\alpha_1}{2} V_{in0}^2 \end{aligned}$$

$$\begin{aligned} Q_2 &= \int_0^{V_{out}} C_2 \, dV \\ &= C_0 V_{out} + C_0 \frac{\alpha_1}{2} V_{out}^2 \end{aligned}$$

Capacitor Nonlinearity



$$V_{out} = \frac{1}{\alpha_1} \left(-1 + \sqrt{1 + M\alpha_1^2 V_{in0}^2 + 2M\alpha_1 V_{in0}} \right)$$

$$\epsilon \ll 1, \sqrt{1 + \epsilon} \approx 1 + \epsilon/2 - \epsilon^2/8$$




$$V_{out} \approx M V_{in0} + (1 - M) \frac{M\alpha_1}{2} V_{in0}^2$$

Linearization Techniques

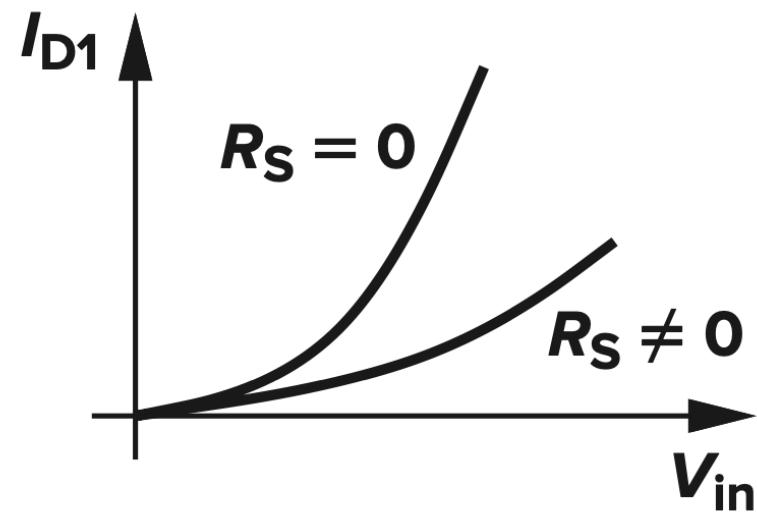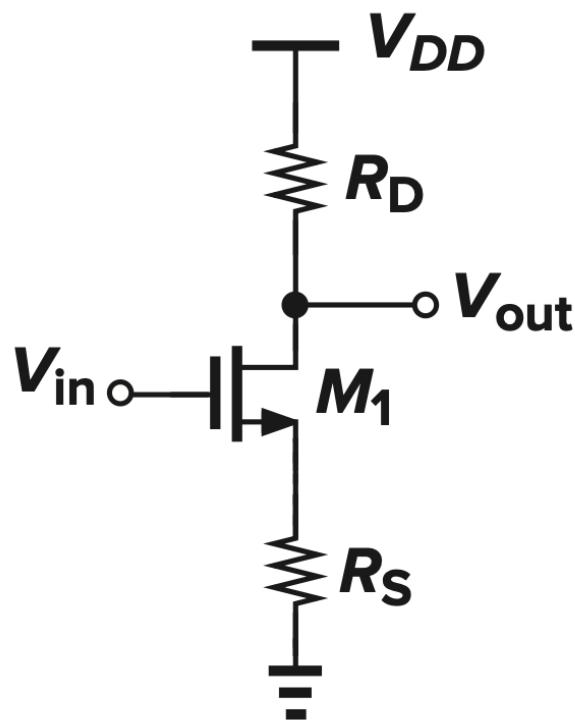


$$G_m = \frac{g_m}{1 + g_m R_S}$$

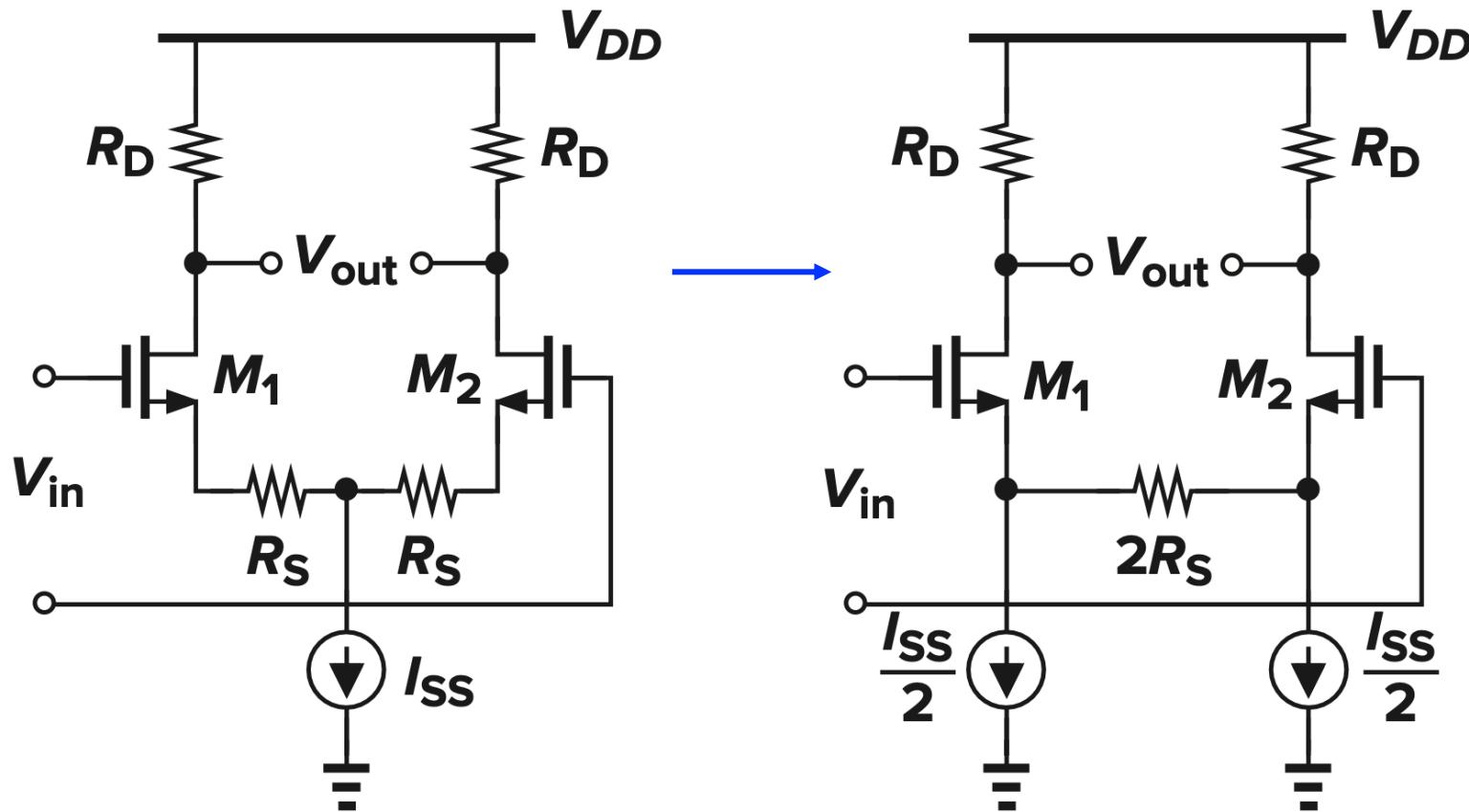Source degeneration applied to a differential pair



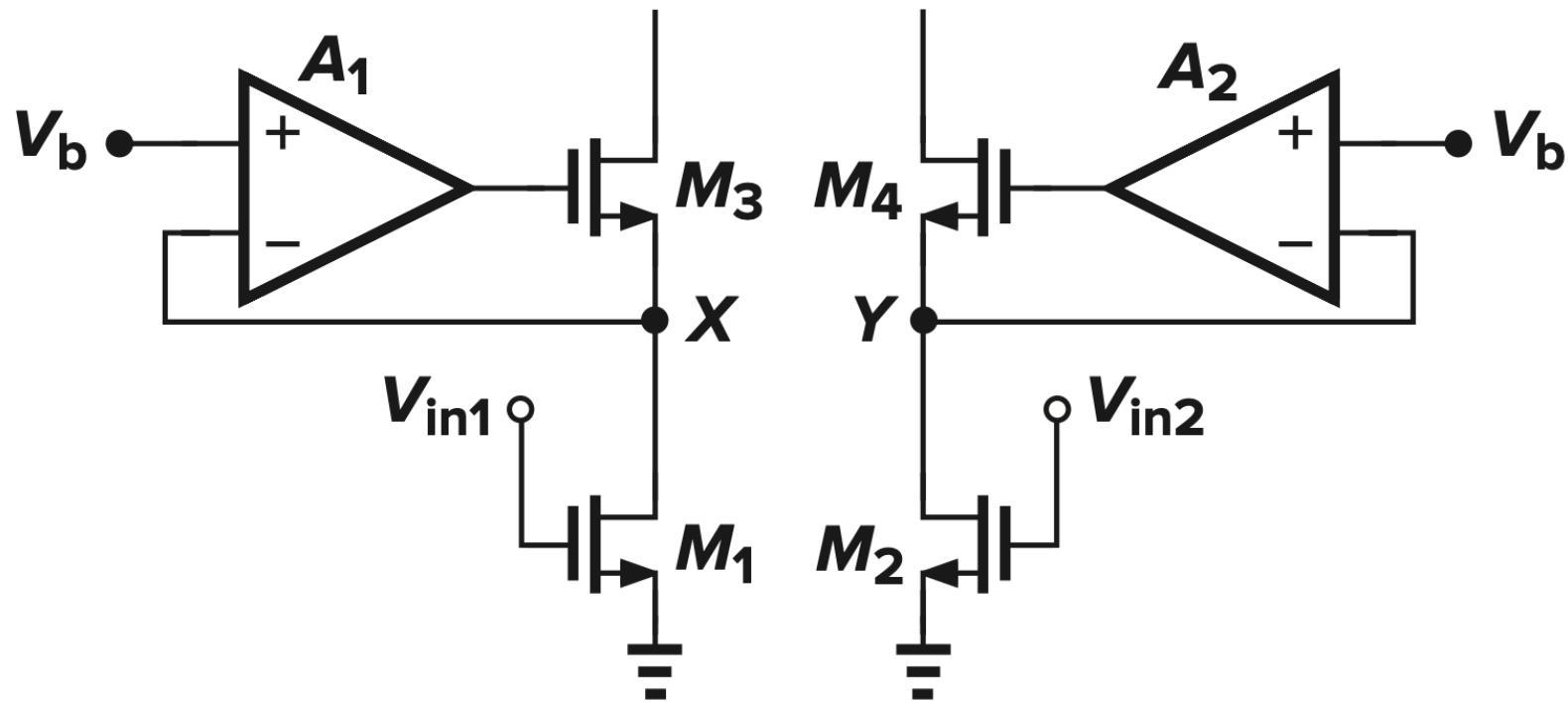
Linearization: Differential pair with input devices in triode



$$I_D = (1/2)\mu C_{ox} (W/L) [2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2]$$


Mismatch

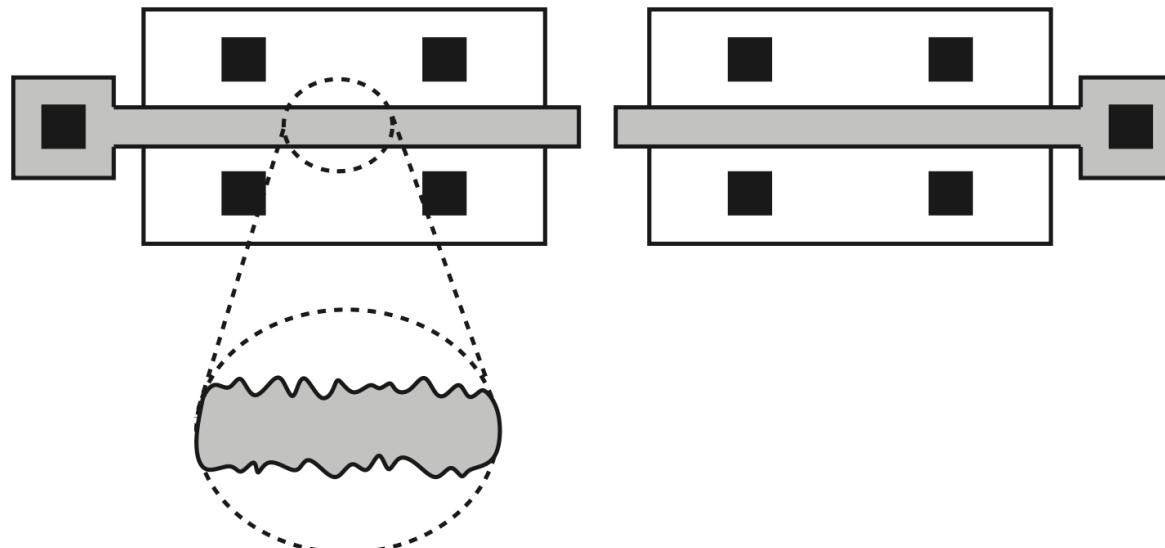Random mismatches due to microscopic variations in device dimensions



Mismatch

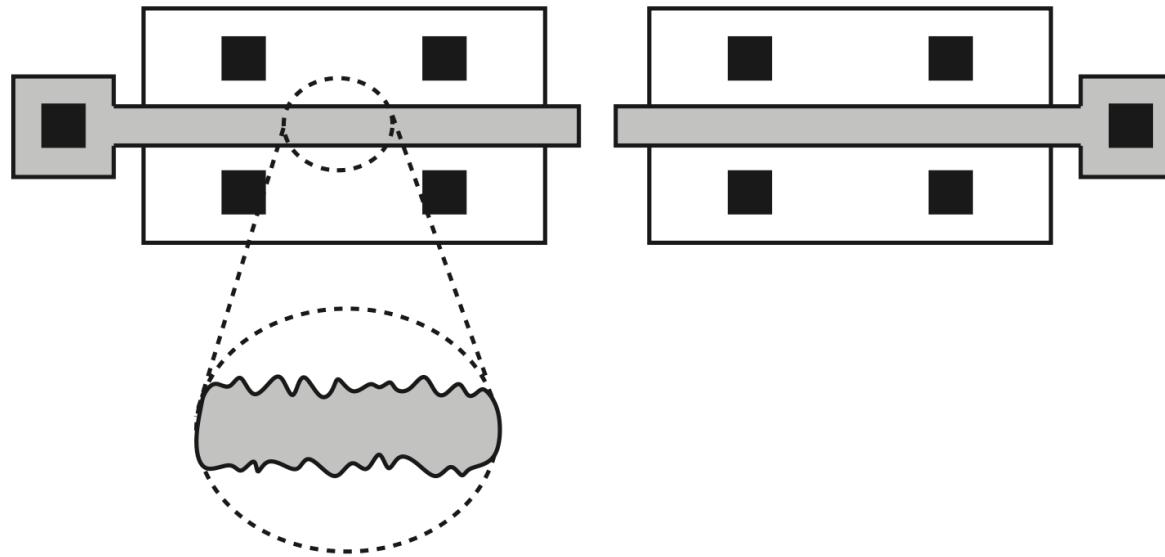Random mismatches due to microscopic variations in device dimensions





- (1) Identify and formulate the mechanisms that lead to mismatch between devices
- (2) Analyze the effect of device mismatches on the performance of circuits

$$I_D = (1/2)\mu C_{ox} (W/L)(V_{GS} - V_{TH})^2$$

Mismatch

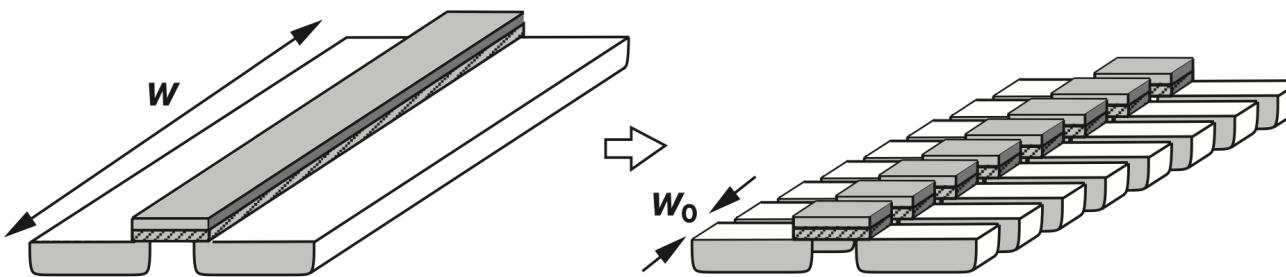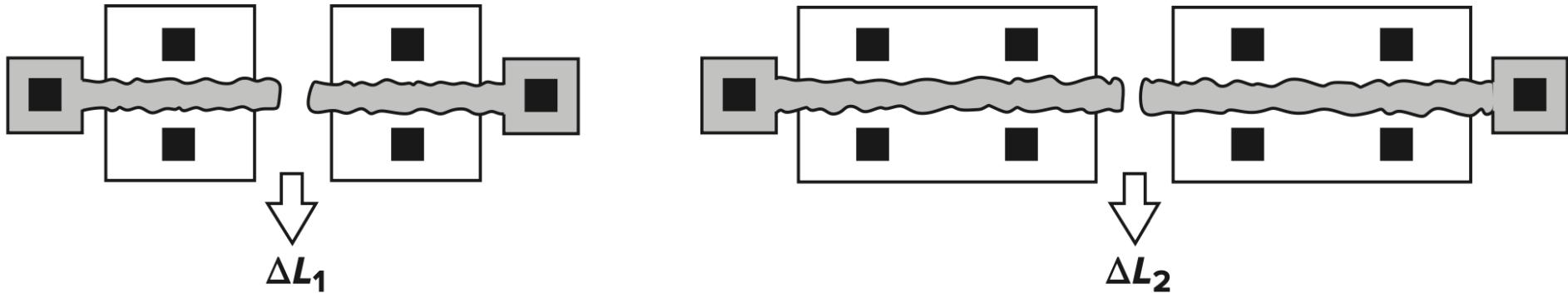Reduction of length mismatch as a result of increasing the width





$$\Delta L_{eq} \approx (\Delta L_1^2 + \Delta L_2^2 + \dots + \Delta L_n^2)^{1/2} / n$$

$$L_{eq} \approx (L_1 + L_2 + \dots + L_n) / n \quad \xrightarrow{\hspace{1cm}} \quad = \frac{(n \Delta L_0^2)^{1/2}}{n}$$
$$= \frac{\Delta L_0}{\sqrt{n}}$$


Effect of Mismatch: Offset

Offset voltage referred to the input

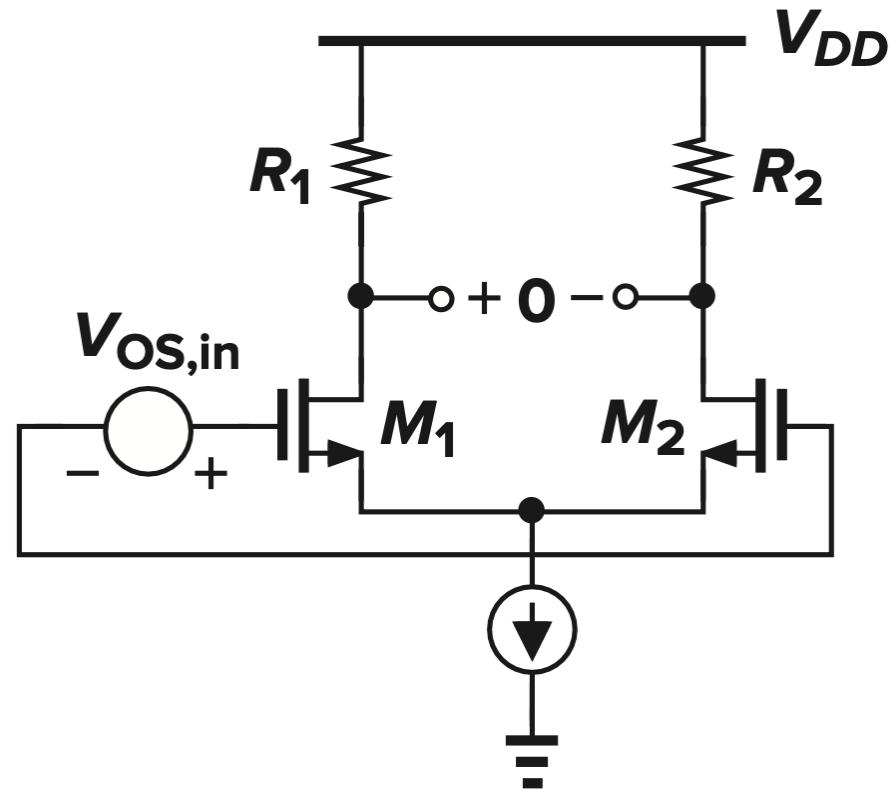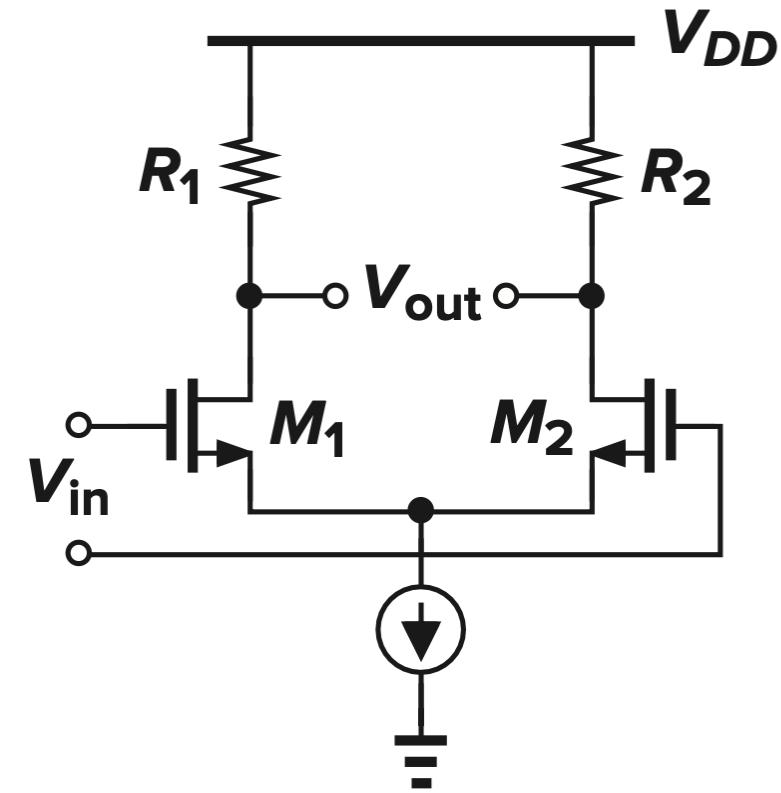

$$|V_{OS,in}| = |V_{OS,out}|/A_v$$

Effect of offset in an amplifier.

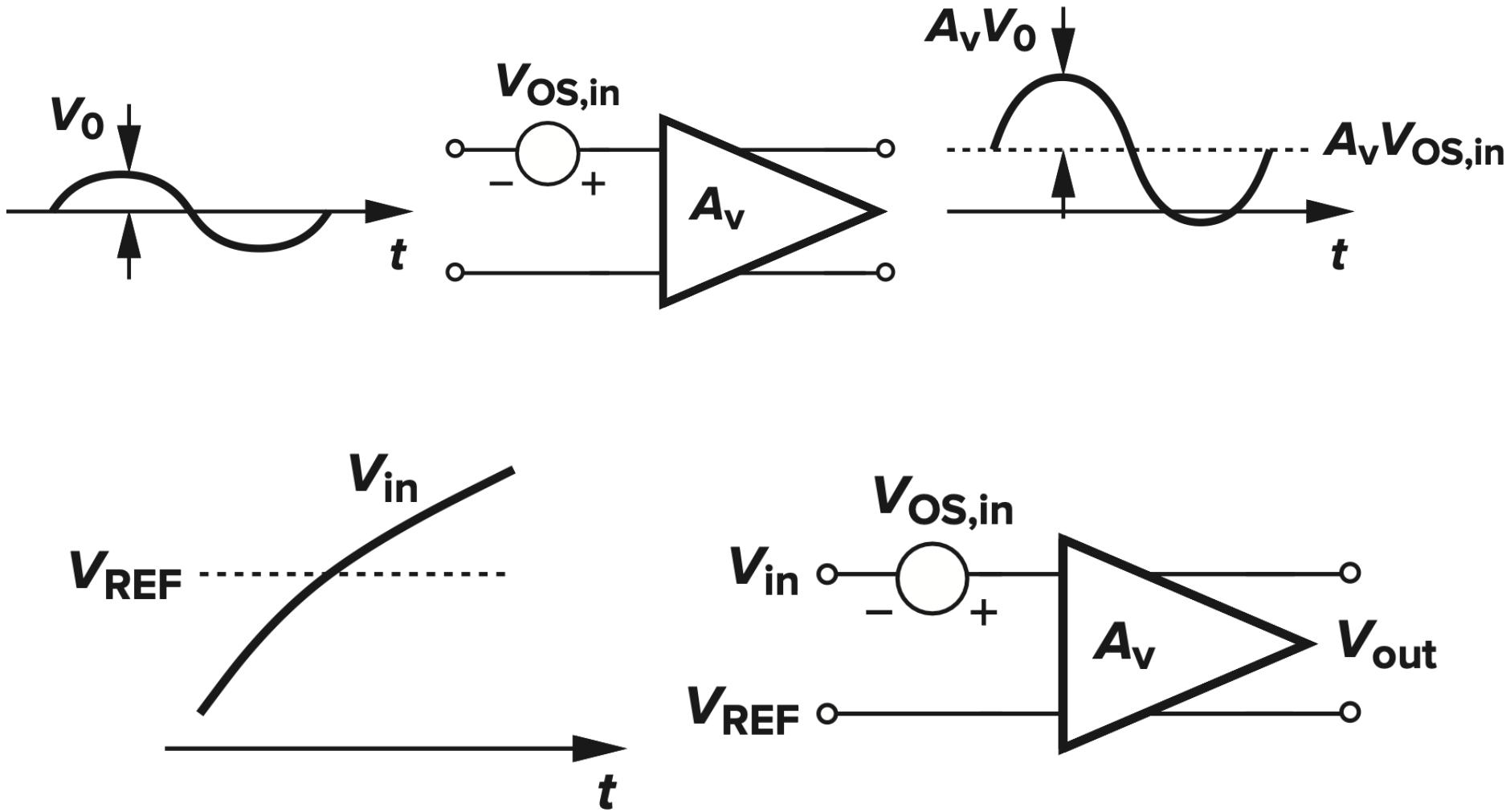

Input offset of a differential pair

$$V_{TH1} = V_{TH}, V_{TH2} = V_{TH} + \Delta V_{TH}$$

$$(W/L)_1 = W/L, (W/L)_2 = W/L + \Delta(W/L)$$


$$R_1 = R_D, R_2 = R_D + \Delta R$$

$$I_{D1} = I_D, I_{D2} = I_D + \Delta I_D$$

$$V_{OS,in} = V_{GS1} - V_{GS2}$$

$$V_{OS,in} = \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} + V_{TH1} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2}} - V_{TH2}$$
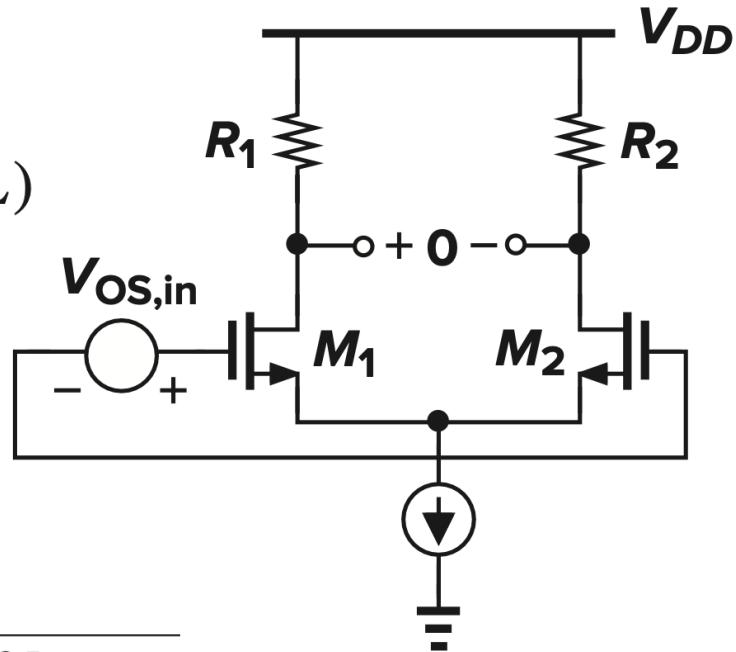
$$= \sqrt{\frac{2}{\mu_n C_{ox}}} \left[\sqrt{\frac{I_D}{\frac{W}{L}}} - \sqrt{\frac{I_D + \Delta I_D}{\frac{W}{L} + \Delta \left(\frac{W}{L}\right)}} \right] - \Delta V_{TH}$$



Input offset of a differential pair

$$= \sqrt{\frac{2}{\mu_n C_{ox}}} \sqrt{\frac{I_D}{W/L}} \left[1 - \sqrt{\frac{1 + \frac{\Delta I_D}{I_D}}{1 + \Delta \left(\frac{W}{L} \right) / \left(\frac{W}{L} \right)}} \right] - \Delta V_{TH}$$

$$\sqrt{1 + \epsilon} \approx 1 + \epsilon/2 \text{ and } (\sqrt{1 + \epsilon})^{-1} \approx 1 - \epsilon/2$$



$$V_{OS,in} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L} \right)}} \left\{ 1 - \left(1 + \frac{\Delta I_D}{2I_D} \right) \left[1 - \frac{\Delta(W/L)}{2(W/L)} \right] \right\} - \Delta V_{TH}$$

$$= \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L} \right)}} \left[\frac{-\Delta I_D}{2I_D} + \frac{\Delta(W/L)}{2(W/L)} \right] - \Delta V_{TH}$$

Input offset of a differential pair

$$I_{D1}R_1 = I_{D2}R_2$$

$$I_D R_D = (I_D + \Delta I_D)(R_D + \Delta R_D) \approx I_D R_D + R_D \Delta I_D + I_D \Delta R_D$$



$$\Delta I_D / I_D \approx -\Delta R_D / R_D$$

$$V_{OS,in} = \frac{1}{2} \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} \left[\frac{\Delta R_D}{R_D} + \frac{\Delta(W/L)}{(W/L)} \right] - \Delta V_{TH}$$


$$V_{OS,in} = \frac{V_{GS} - V_{TH}}{2} \left[\frac{\Delta R_D}{R_D} + \frac{\Delta(W/L)}{(W/L)} \right] - \Delta V_{TH}$$

Mismatch between current sources

$$y = f(x_1, x_2, \dots)$$

$$\Delta y = \frac{\partial f}{\partial x_1} \Delta x_1 + \frac{\partial f}{\partial x_2} \Delta x_2 + \dots$$
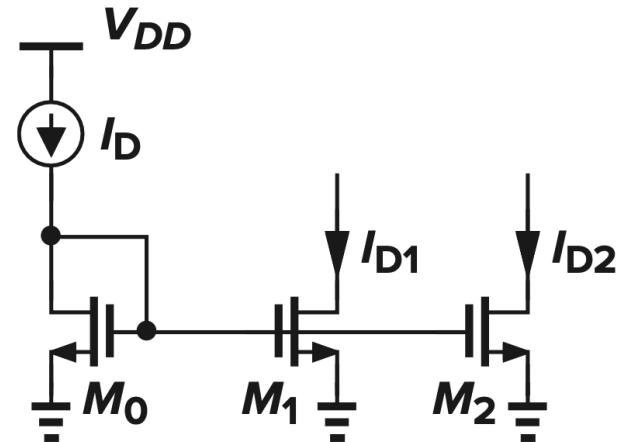
$$I_D = (1/2)\mu_n C_{ox} (W/L)(V_{GS} - V_{TH})^2$$



Mismatch between current sources

$$y = f(x_1, x_2, \dots)$$


$$\Delta y = \frac{\partial f}{\partial x_1} \Delta x_1 + \frac{\partial f}{\partial x_2} \Delta x_2 + \dots$$

$$I_D = (1/2)\mu_n C_{ox} (W/L) (V_{GS} - V_{TH})^2$$

$$\Delta I_D = \frac{\partial I_D}{\partial (W/L)} \Delta \left(\frac{W}{L} \right) + \frac{\partial I_D}{\partial (V_{GS} - V_{TH})} \Delta (V_{GS} - V_{TH})$$

$$\Delta I_D = \frac{1}{2} \mu_n C_{ox} (V_{GS} - V_{TH})^2 \Delta \left(\frac{W}{L} \right) - \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \Delta V_{TH}$$
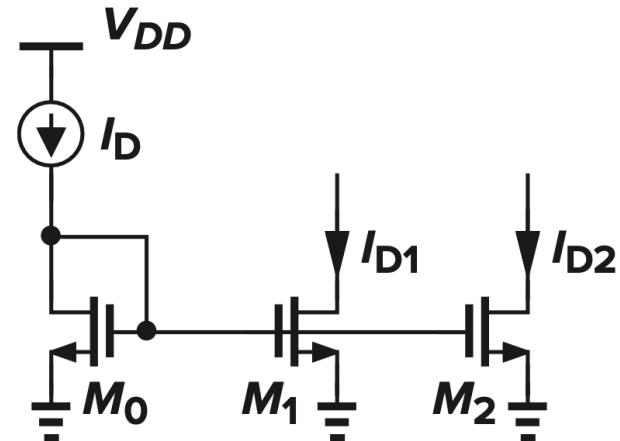
$$\frac{\Delta I_D}{I_D} = \frac{\Delta (W/L)}{W/L} - 2 \frac{\Delta V_{TH}}{V_{GS} - V_{TH}}$$



Even-Order Distortion

$$y_1 \approx \alpha_1 x_1 + \alpha_2 x_1^2 + \alpha_3 x_1^3 \text{ and } y_2 \approx \beta_1 x_2 + \beta_2 x_2^2 + \beta_3 x_2^3$$

$$y_1 - y_2 = (\alpha_1 x_1 - \beta_2 x_2) + (\alpha_2 x_1^2 - \beta_2 x_2^2) + (\alpha_3 x_1^3 - \beta_3 x_2^3)$$

$$y_1 - y_2 = (\alpha_1 + \beta_1) x_1 + (\alpha_2 - \beta_2) x_1^2 + (\alpha_3 + \beta_3) x_1^3$$

