
 


*Integrated Neurotechnologies
Laboratory*

EPFL

 

Advanced analog integrated circuit design (EE-523), Lecture 6

Prof. Mahsa Shoaran

Institutes of Electrical and Micro Engineering and Neuro-X, School of Engineering, EPFL

Recap: Nonlinearity

- Two types of nonidealities: **nonlinearity and mismatch**

$$y(t) = \alpha_1 x(t) + \alpha_2 x^2(t) + \alpha_3 x^3(t) + \dots$$

$$y(t) = \alpha_1 A \cos \omega t + \alpha_2 A^2 \cos^2 \omega t + \alpha_3 \cos^3 \omega t + \dots$$

$$= \alpha_1 A \cos \omega t + \frac{\alpha_2 A^2}{2} [1 + \cos(2\omega t)] + \frac{\alpha_3 A^3}{4} [3 \cos \omega t + \cos(3\omega t)] + \dots$$

$$\boxed{\text{THD} = \frac{(\alpha_2 A^2/2)^2 + (\alpha_3 A^3/4)^2}{(\alpha_1 A + 3\alpha_3 A^3/4)^2}}$$

Recap: Nonlinearity


- Two types of nonidealities: **nonlinearity and mismatch**

$$y(t) = \alpha_1 x(t) + \alpha_2 x^2(t) + \alpha_3 x^3(t) + \dots$$


$$y(t) = \alpha_1 A \cos \omega t + \alpha_2 A^2 \cos^2 \omega t + \alpha_3 \cos^3 \omega t + \dots$$

$$= \alpha_1 A \cos \omega t + \frac{\alpha_2 A^2}{2} [1 + \cos(2\omega t)] + \frac{\alpha_3 A^3}{4} [3 \cos \omega t + \cos(3\omega t)] + \dots$$
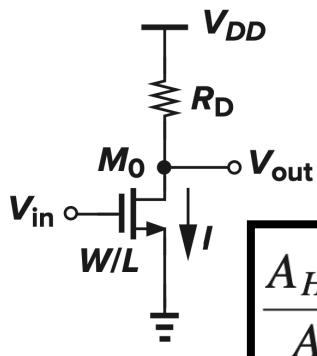
$$\text{THD} = \frac{(\alpha_2 A^2/2)^2 + (\alpha_3 A^3/4)^2}{(\alpha_1 A + 3\alpha_3 A^3/4)^2}$$



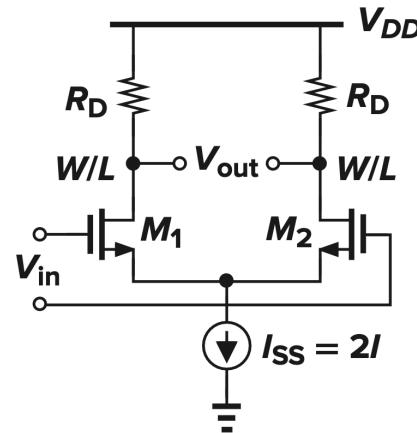
$$\frac{A_{HD2}}{A_F} = \frac{V_m}{4(V_{GS} - V_{TH})}$$



$$\frac{A_{HD3}}{A_F} \approx \frac{V_m^2}{32(V_{GS} - V_{TH})^2}$$

Recap: Mismatch

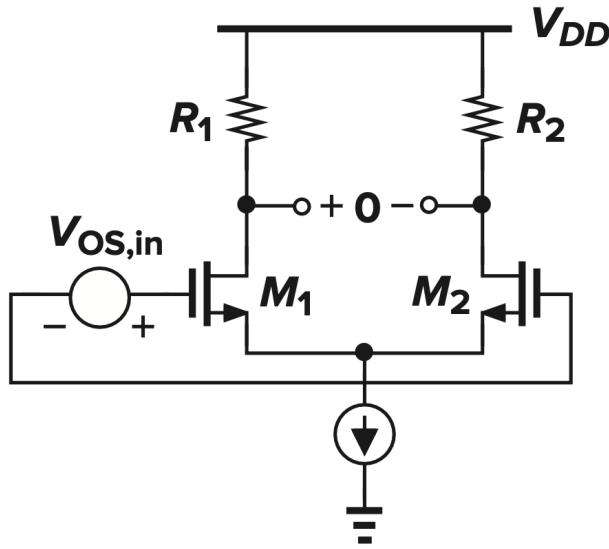- Mismatch typically leads to 3 important effects: **dc offsets, even-order distortion, and lower common-mode rejection.**



$$V_{TH1} = V_{TH}, V_{TH2} = V_{TH} + \Delta V_{TH}$$


$$(W/L)_1 = W/L, (W/L)_2 = W/L + \Delta(W/L)$$

$$R_1 = R_D, R_2 = R_D + \Delta R$$

$$V_{OS,in} = \frac{V_{GS} - V_{TH}}{2} \left[\frac{\Delta R_D}{R_D} + \frac{\Delta(W/L)}{(W/L)} \right] - \Delta V_{TH}$$

Recap: Mismatch

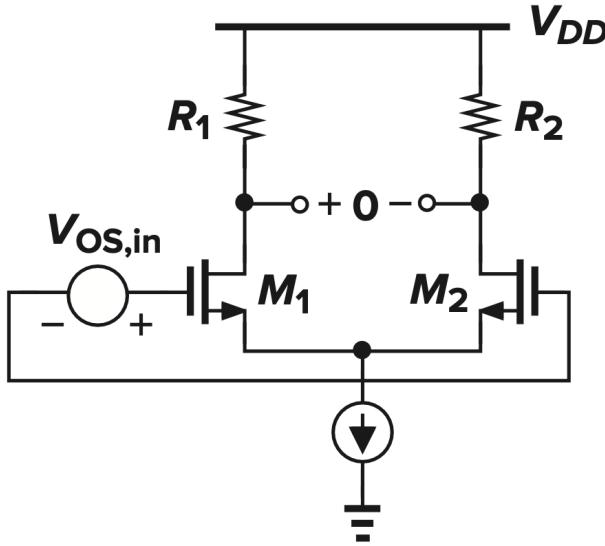- Mismatch typically leads to 3 important effects: **dc offsets, even-order distortion, and lower common-mode rejection.**




$$V_{TH1} = V_{TH}, V_{TH2} = V_{TH} + \Delta V_{TH}$$

$$(W/L)_1 = W/L, (W/L)_2 = W/L + \Delta(W/L)$$

$$R_1 = R_D, R_2 = R_D + \Delta R$$
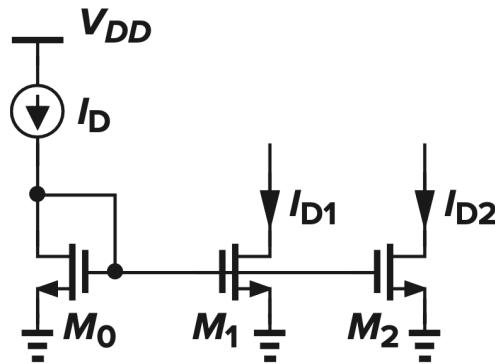
$$V_{OS,in} = \frac{V_{GS} - V_{TH}}{2} \left[\frac{\Delta R_D}{R_D} + \frac{\Delta(W/L)}{(W/L)} \right] - \Delta V_{TH}$$




$$\frac{\Delta I_D}{I_D} = \frac{\Delta(W/L)}{W/L} - 2 \frac{\Delta V_{TH}}{V_{GS} - V_{TH}}$$

Even-Order Distortion


$$y_1 \approx \alpha_1 x_1 + \alpha_2 x_1^2 + \alpha_3 x_1^3 \text{ and } y_2 \approx \beta_1 x_2 + \beta_2 x_2^2 + \beta_3 x_2^3$$

$$y_1 - y_2 = (\alpha_1 x_1 - \beta_1 x_2) + (\alpha_2 x_1^2 - \beta_2 x_2^2) + (\alpha_3 x_1^3 - \beta_3 x_2^3)$$
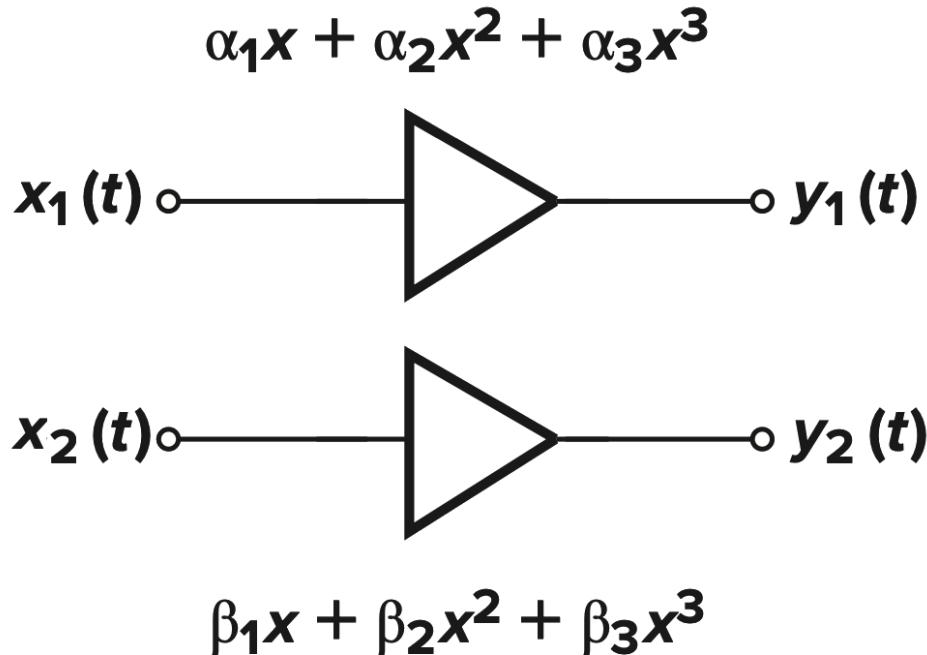
$$y_1 - y_2 = (\alpha_1 + \beta_1)x_1 + (\alpha_2 - \beta_2)x_1^2 + (\alpha_3 + \beta_3)x_1^3$$




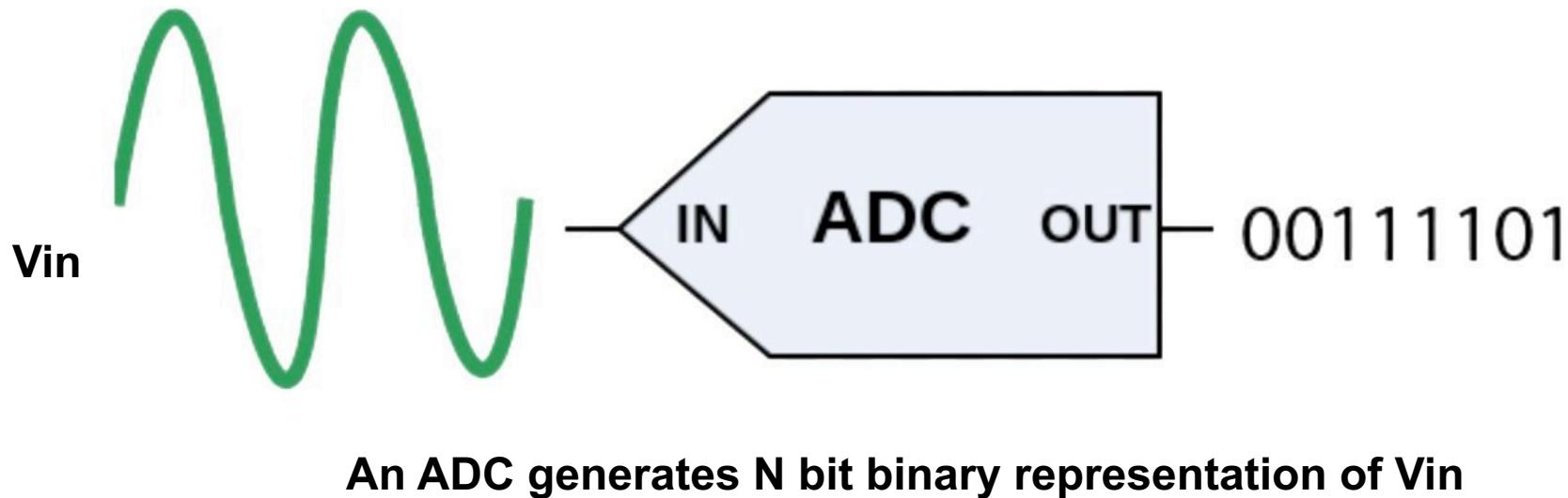Analog-to-digital Converter (ADC): Introduction





- In most cases, a reference voltage is supplied to the ADC (for example a bandgap reference)
- The analog input, V_{in} , is “quantized” in the voltage range

ADC Introduction: LSB

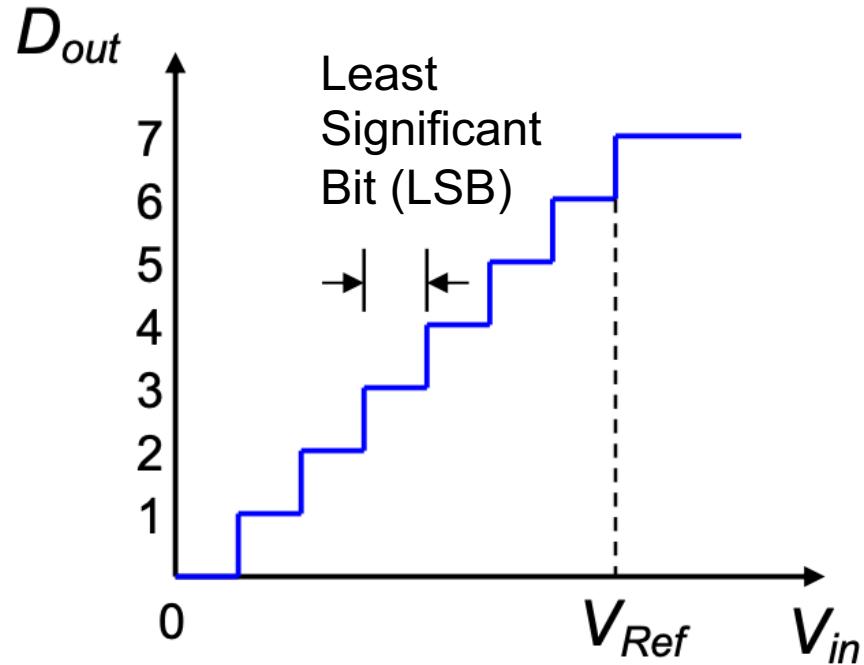


- The voltage change associated with an LSB change in the digital output

ADC Introduction: Clock

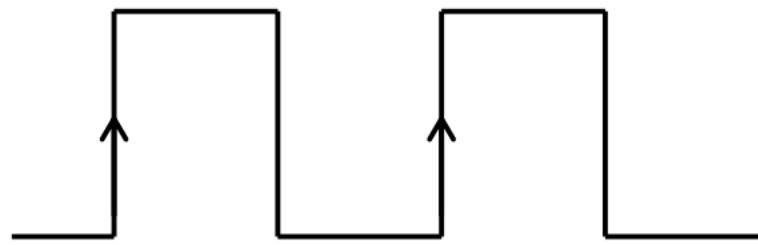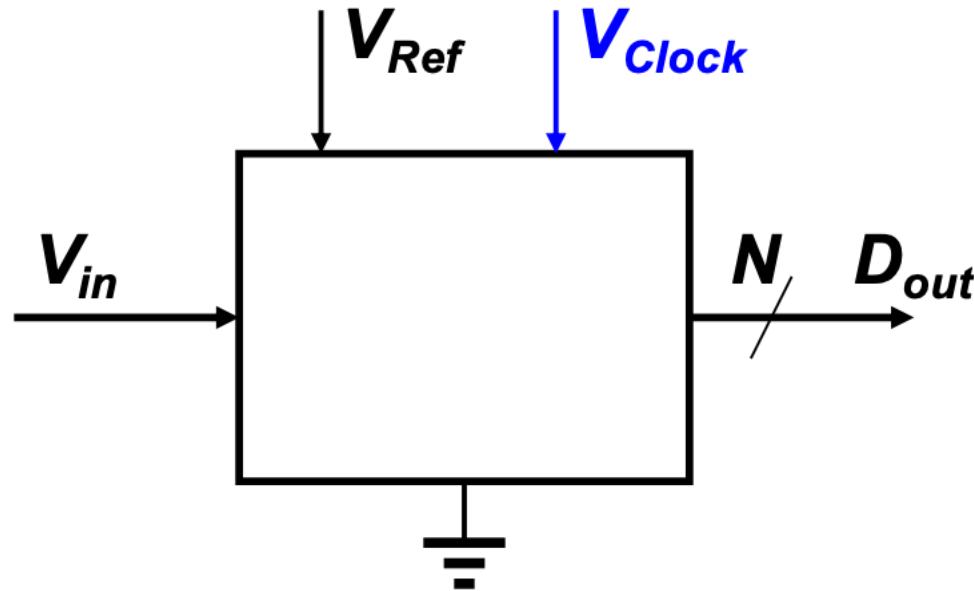


Uniform and Nonuniform Sampling


Uniform
Analog

 



Nonuniform
Analog

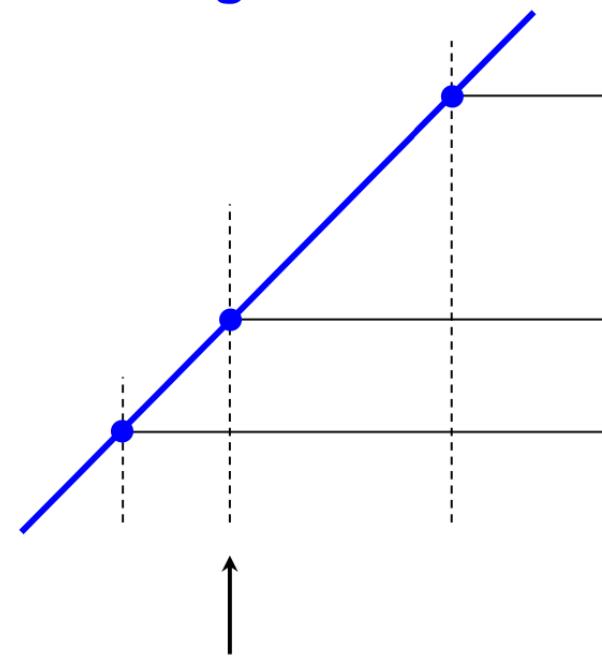



Various Types of Data Converters

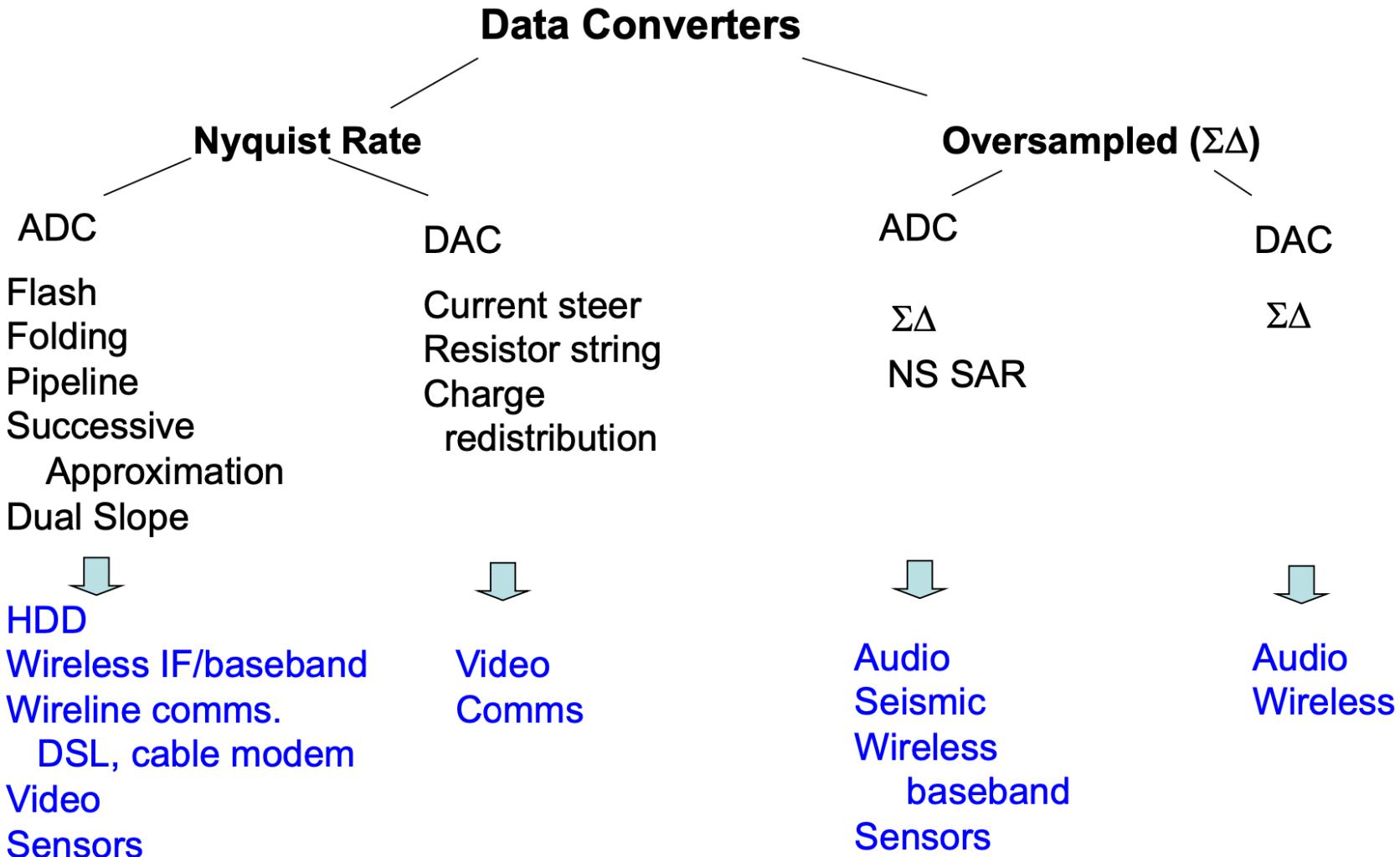


Nyquist rate sampling, aliasing

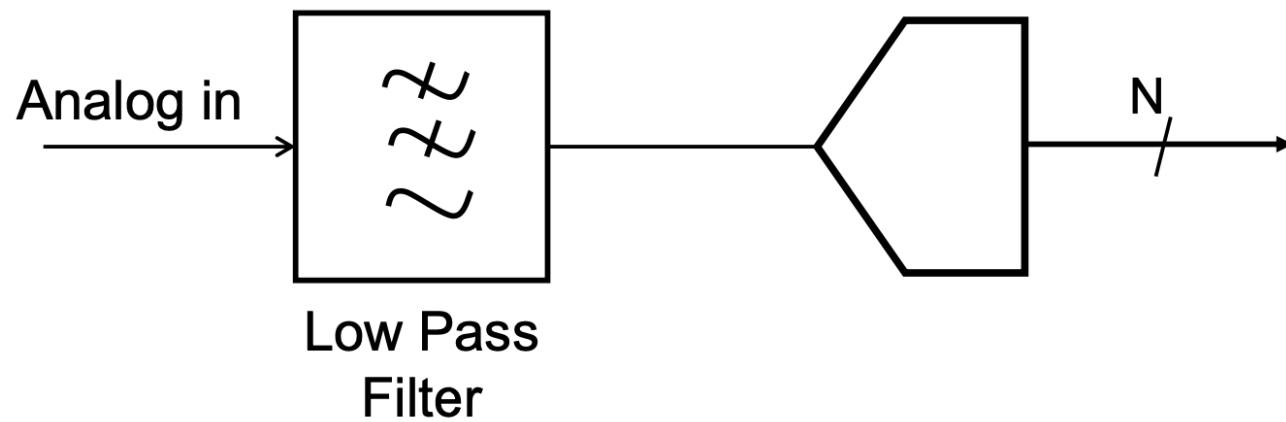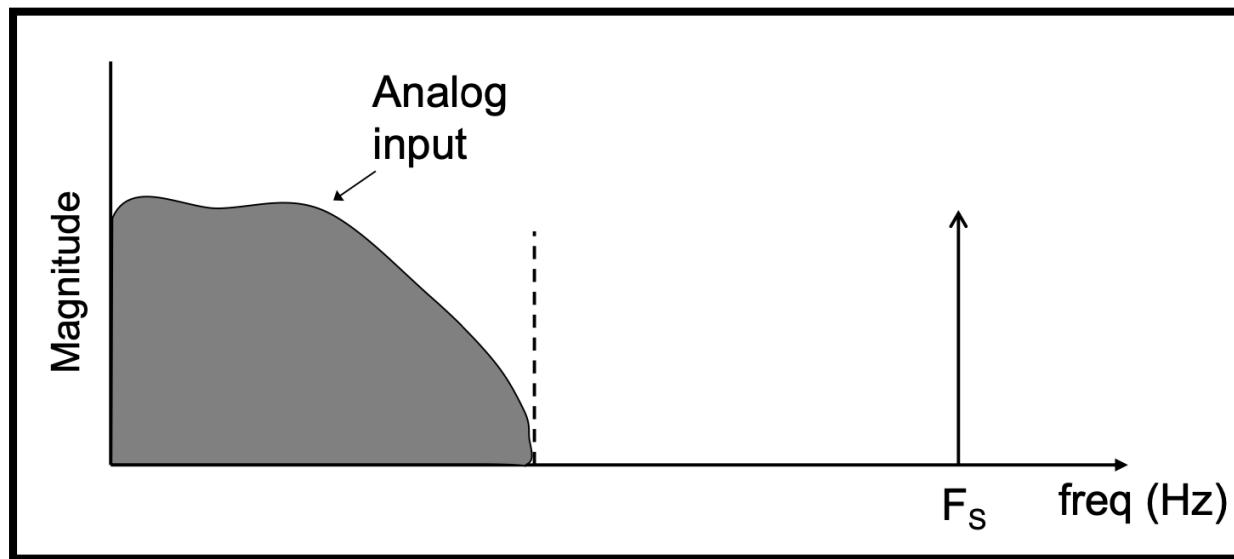

Sample and Hold

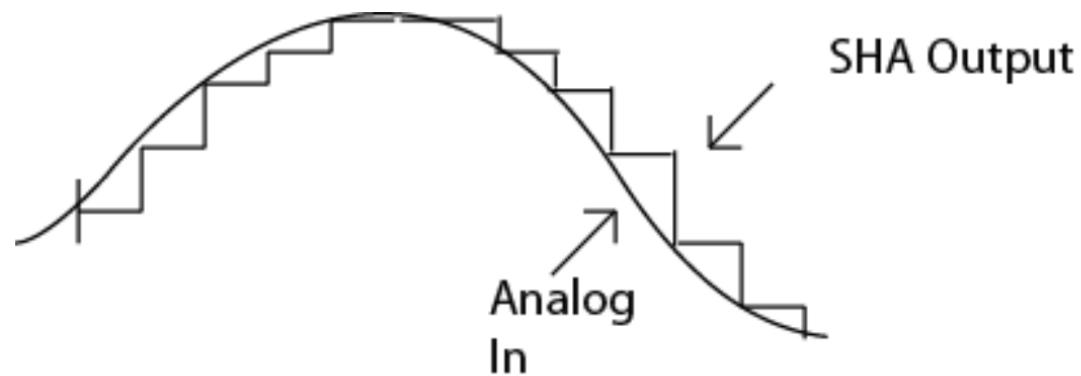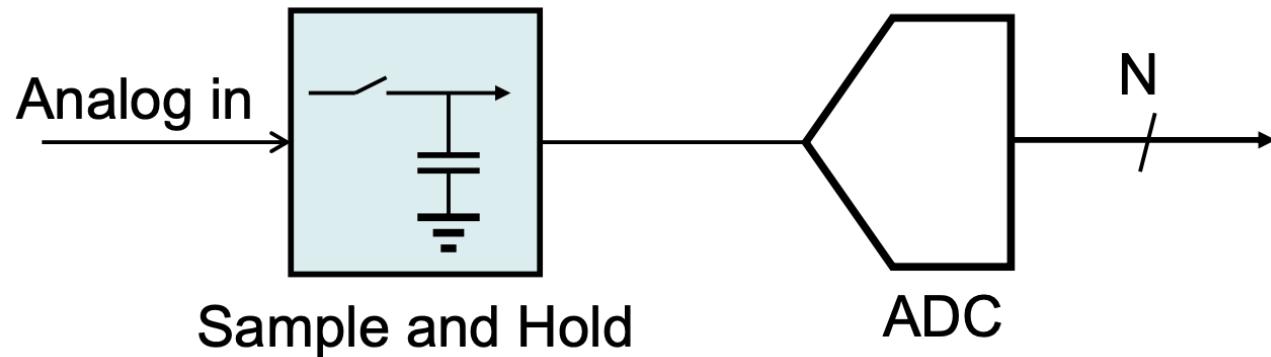



Sample and Hold

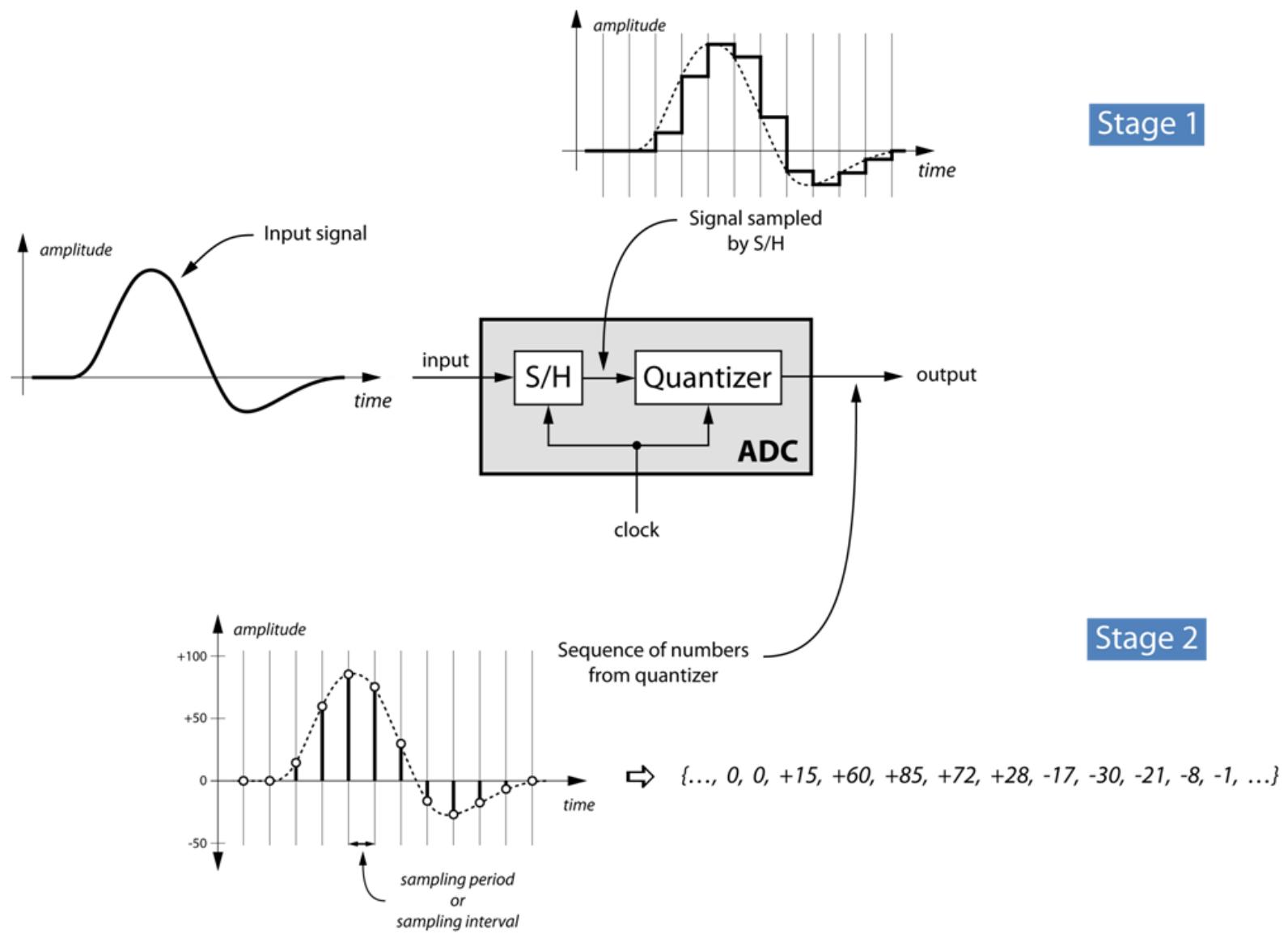

DC Characteristics – Monotonicity



- Monotonicity is usually required in ADCs
- Output code should increase with increasing input voltage

Monotonic

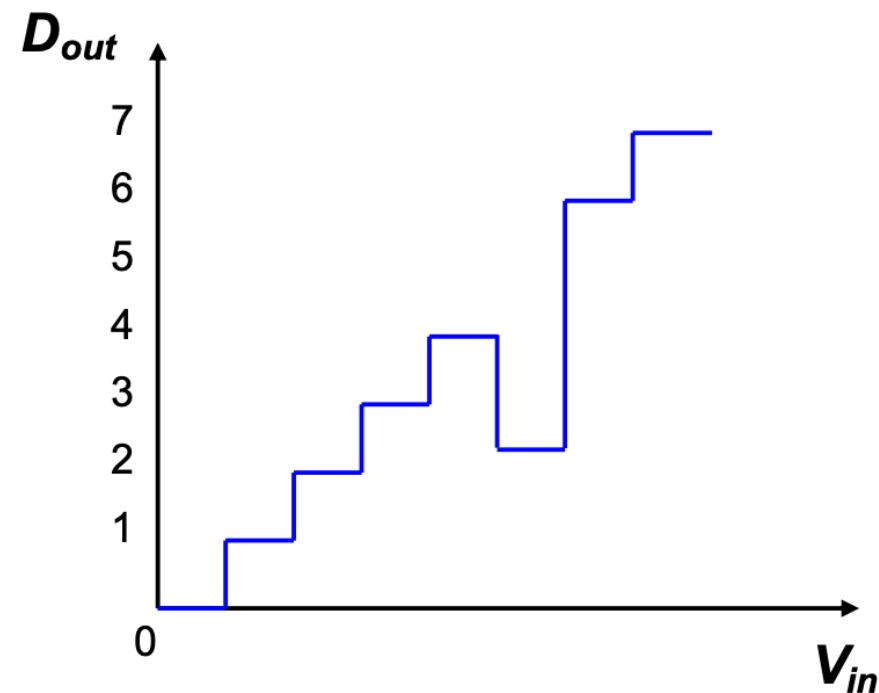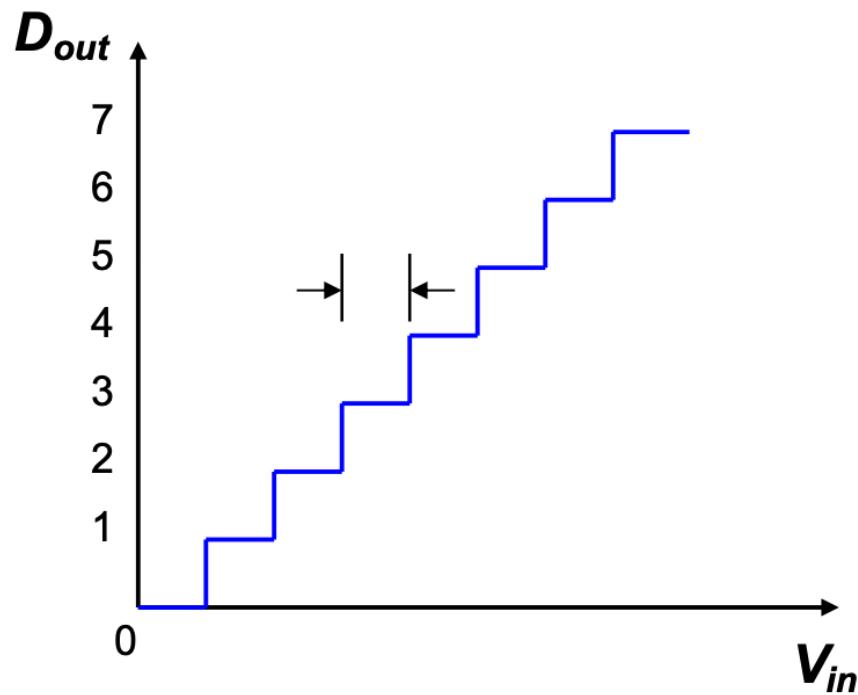



DC Test Setup

Test Setup

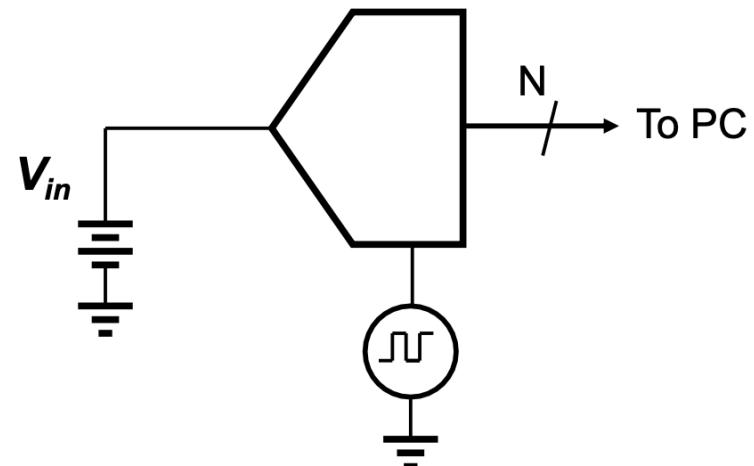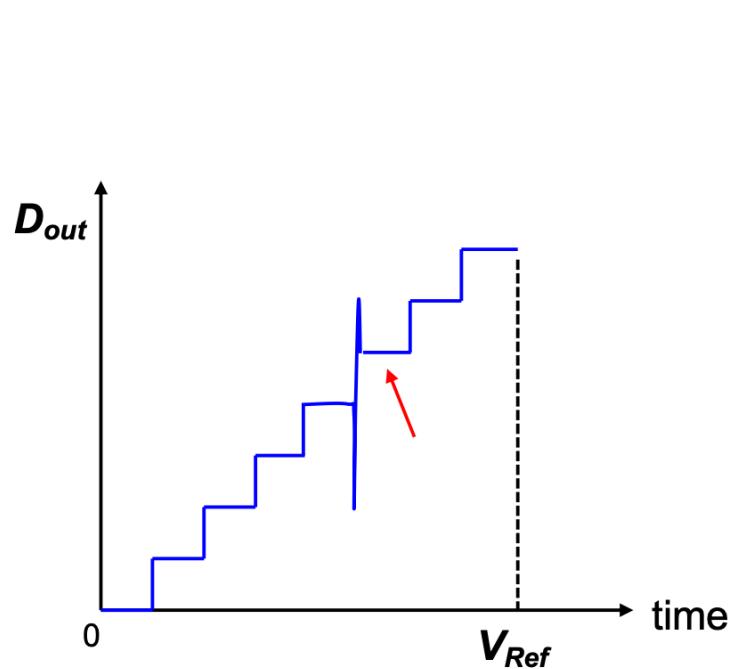


Missing Codes

Code 3 missing

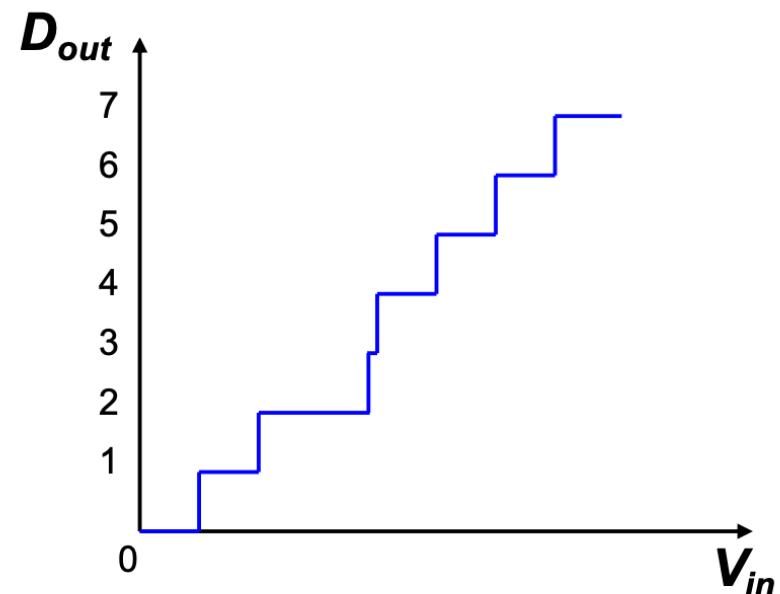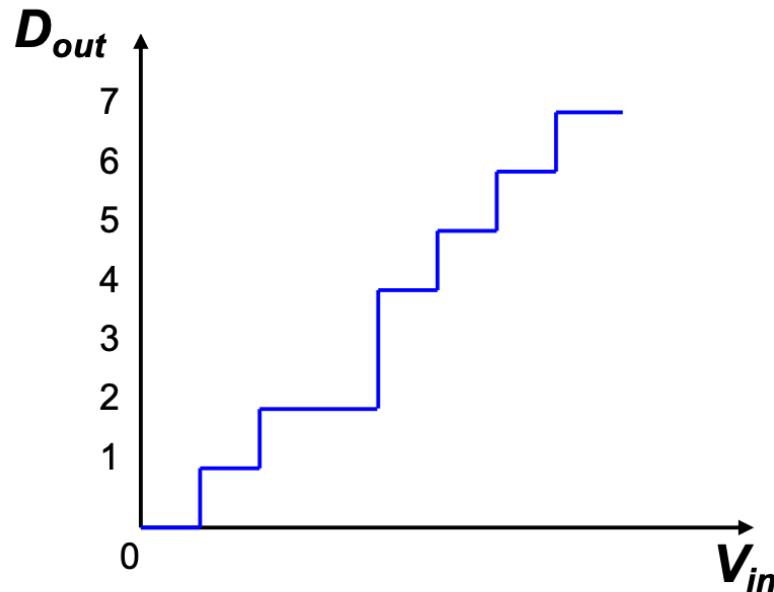


Differential Non-Linearity (DNL)

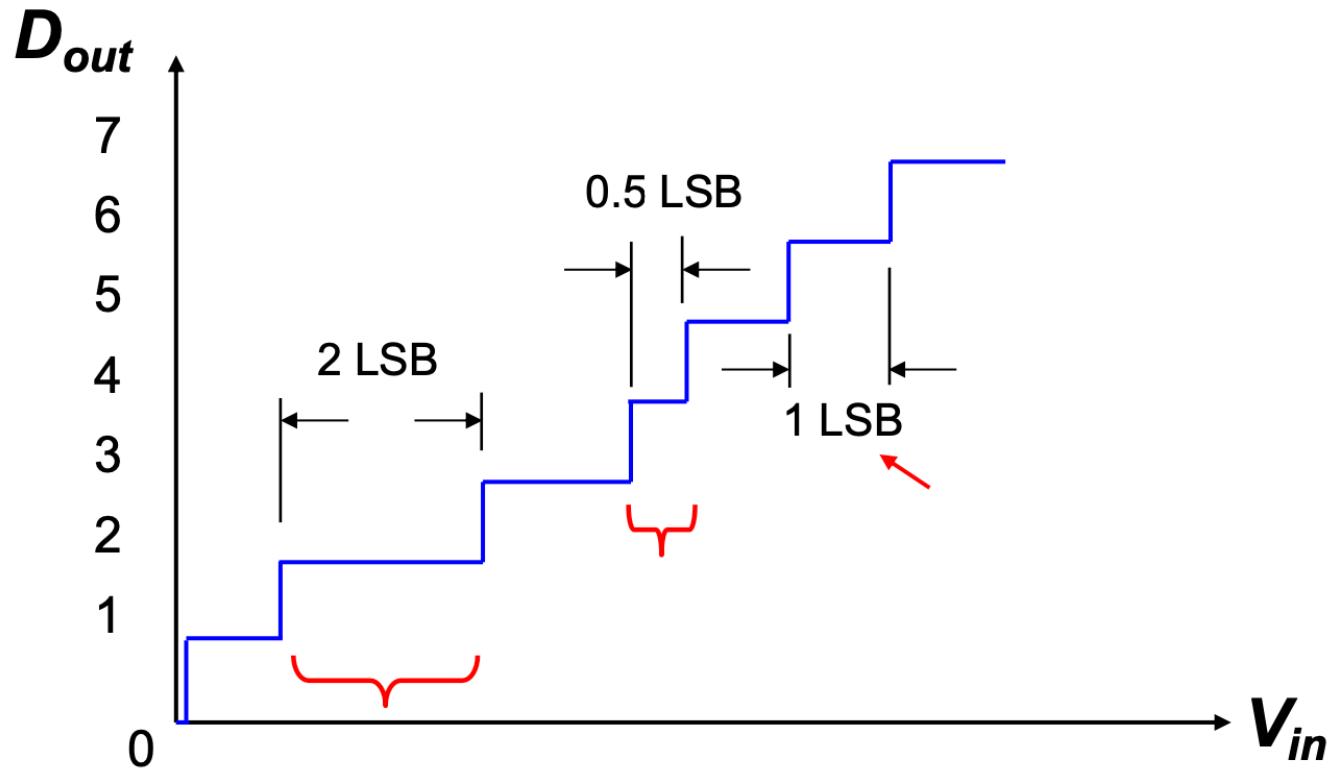

DNL = Actual width (in LSB) – Ideal width (i.e. 1 LSB)


Integral Non-Linearity (INL)

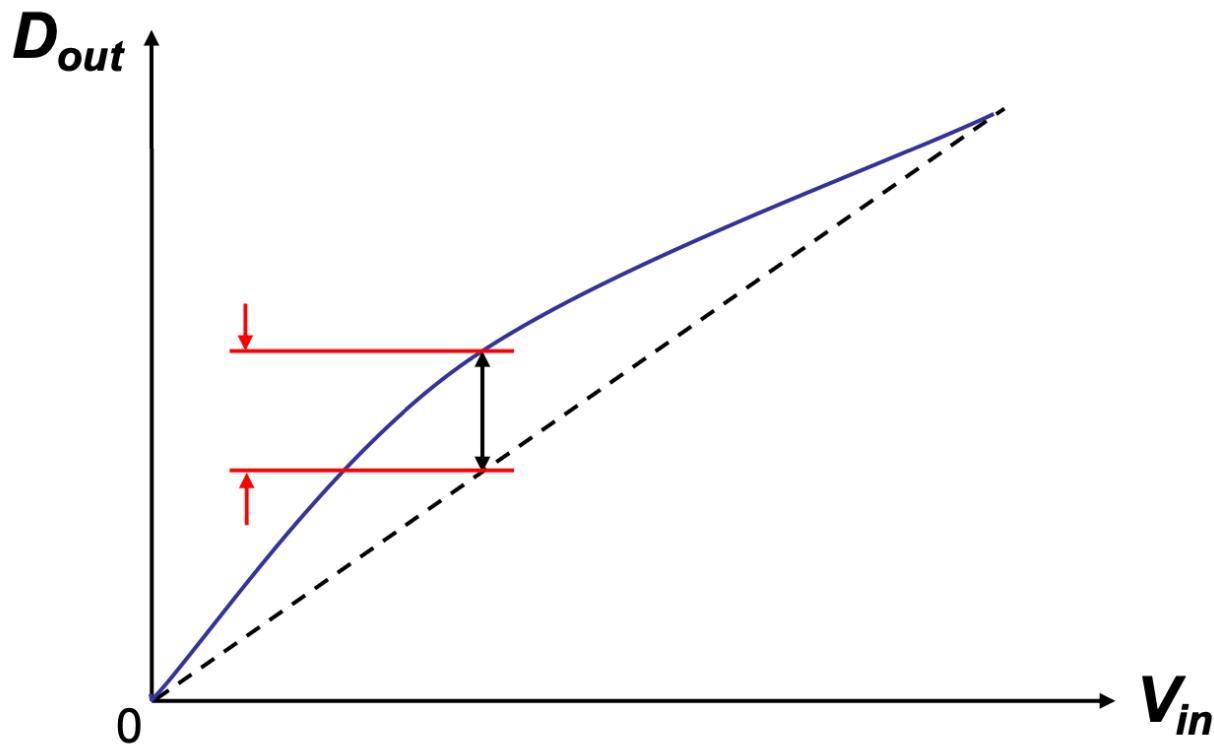

- Just like DNL, INL can be specified at each code
- INL is often derived from DNL information


INL and DNL Plots

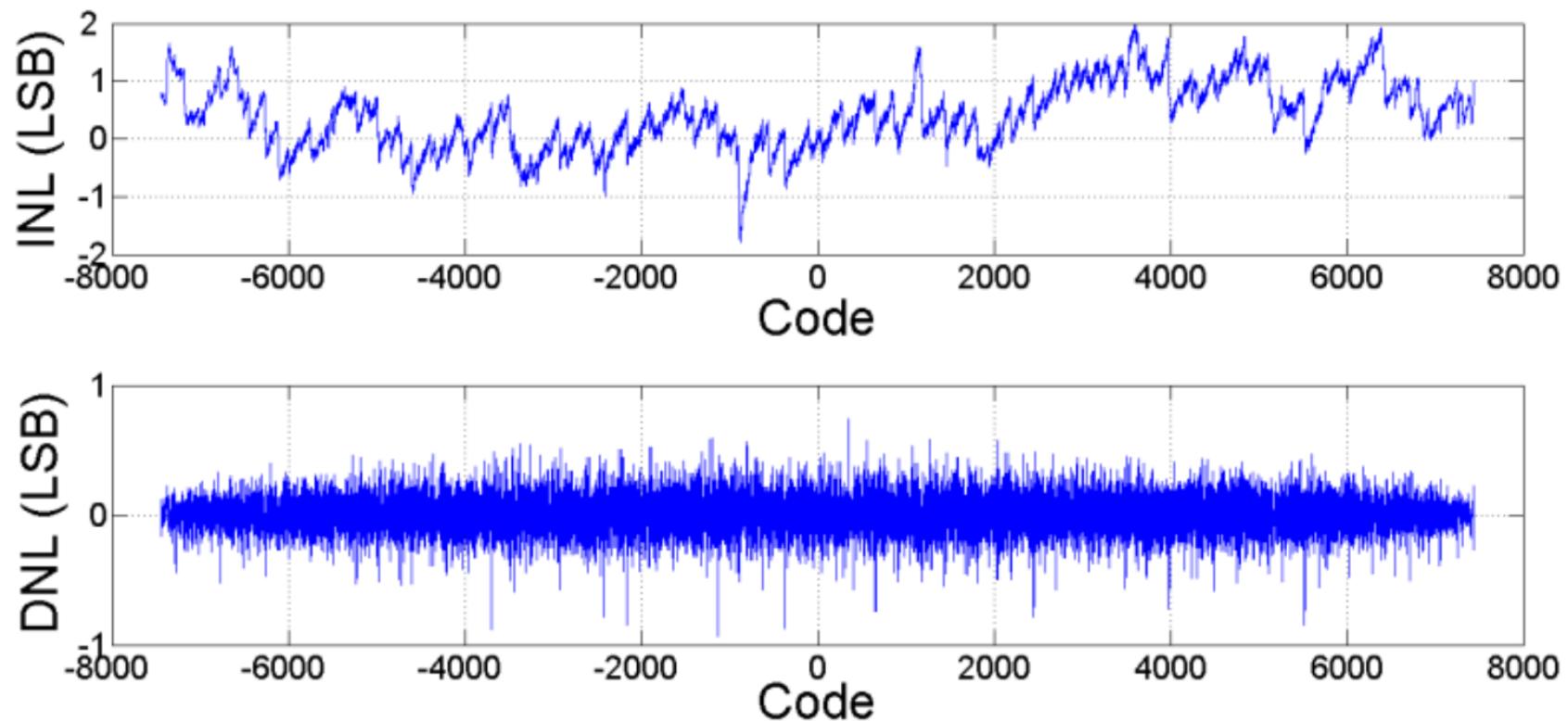- **INL and DNL for an experimental 14b ADC**



SNR, Quantization Noise


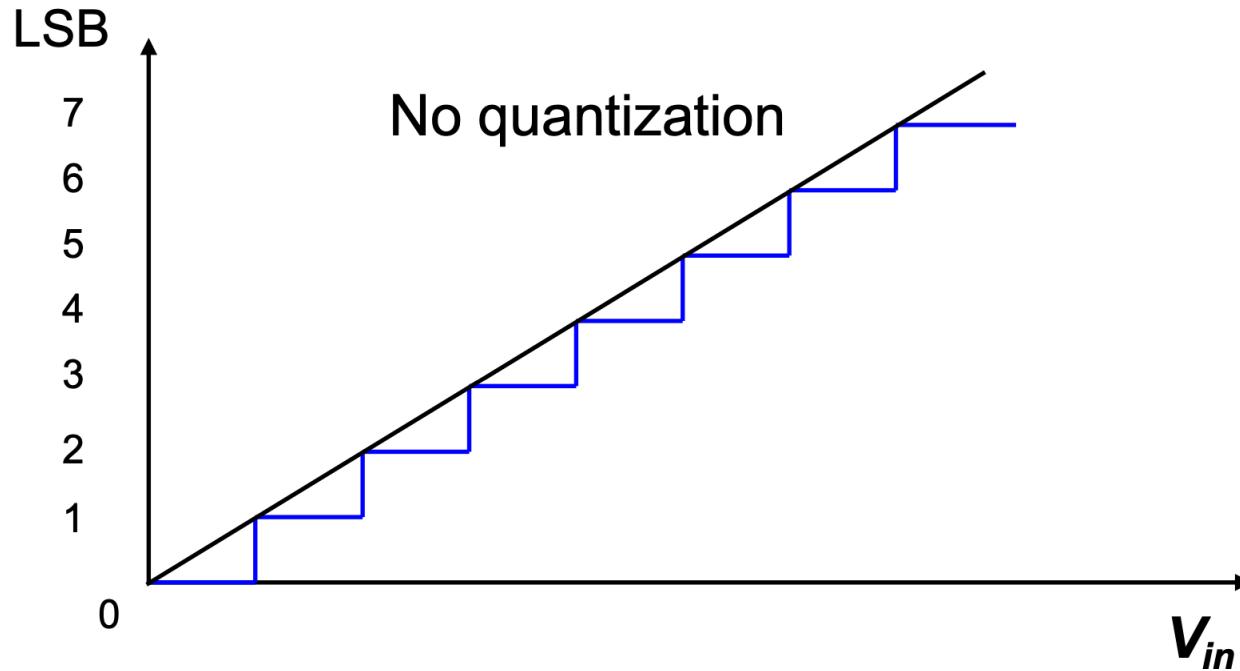
- **SNR or Signal-to-Noise ratio:** Signal power, and noise power (**quantization noise/error** and the circuit noise)
- We consider **quantization noise** as a white noise that is uncorrelated with the signal, with a uniform probability distribution
- **ENOB:** Effective Number of Bits, calculated from **SNDR**





SNR, Quantization Noise

- We want to determine the mean squared value of the quantization noise

Quantization noise

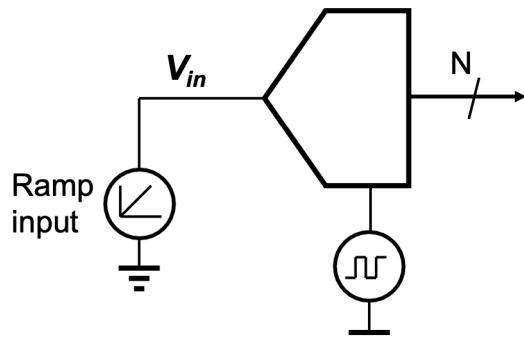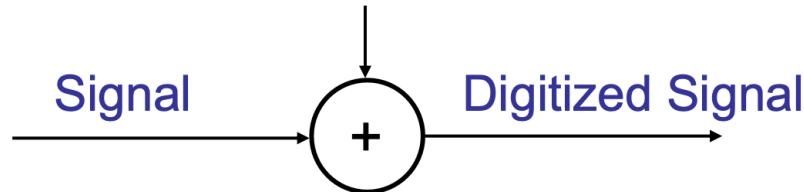


Test Setup

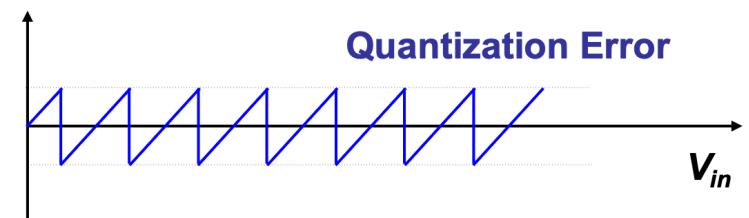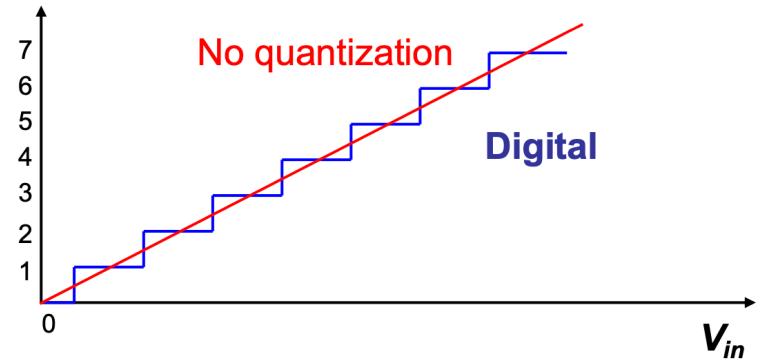



Quantization Noise for Ramp Input

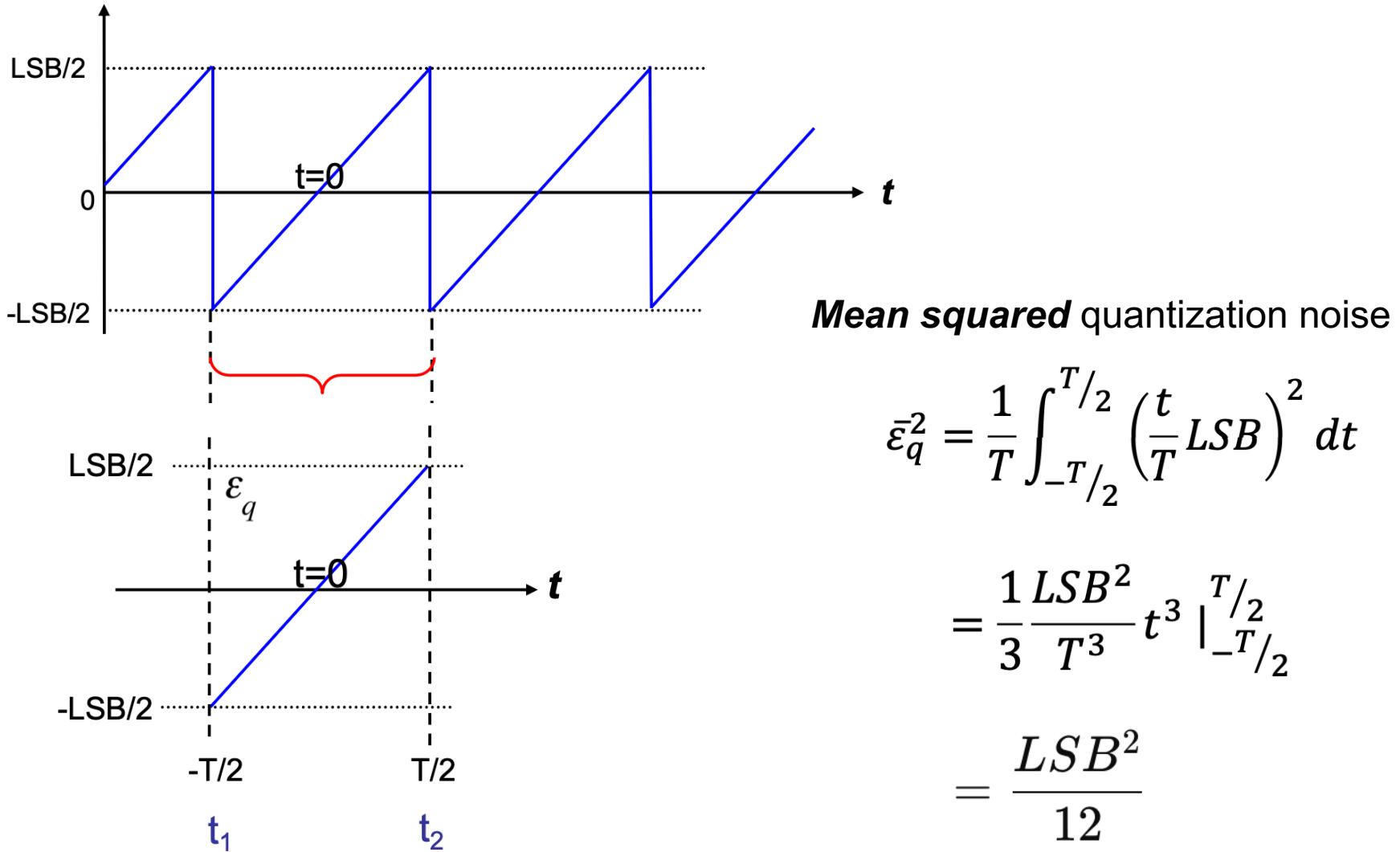- Concentrating on region from $-T/2$ to $T/2$



SNR for Ideal ADC

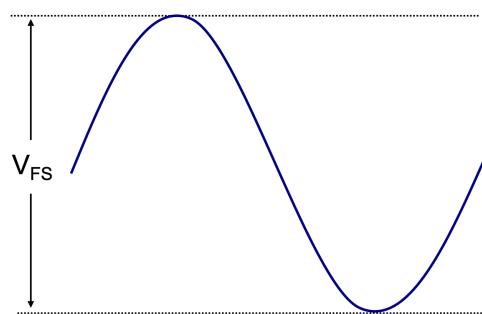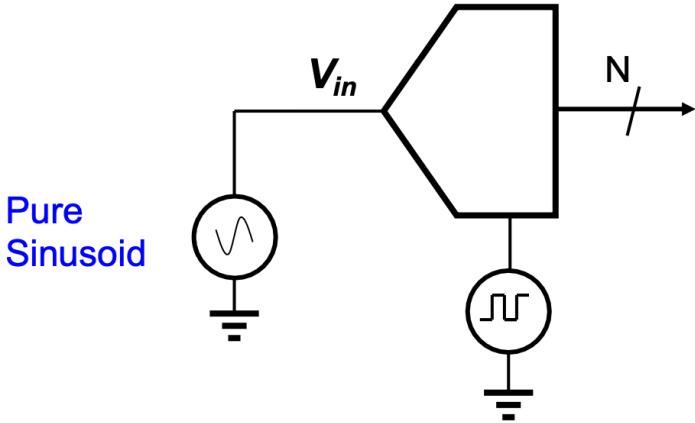- Pure sine wave has only one frequency component, easier to generate



$$\text{Signal to Noise Ratio (SNR)} = \frac{\text{Signal Power}}{\text{Noise Power}}$$

$$\text{SNR} = 10 \log_{10} \left(\frac{\text{signal power}}{\text{noise power}} \right)$$


$$= 20 \log_{10} \left(\frac{\frac{2^N}{2\sqrt{2}} \text{ LSB}}{\frac{1}{\sqrt{12}} \text{ LSB}} \right)$$

$$\text{SNR} = (6.02N + 1.76) \text{ dB}$$

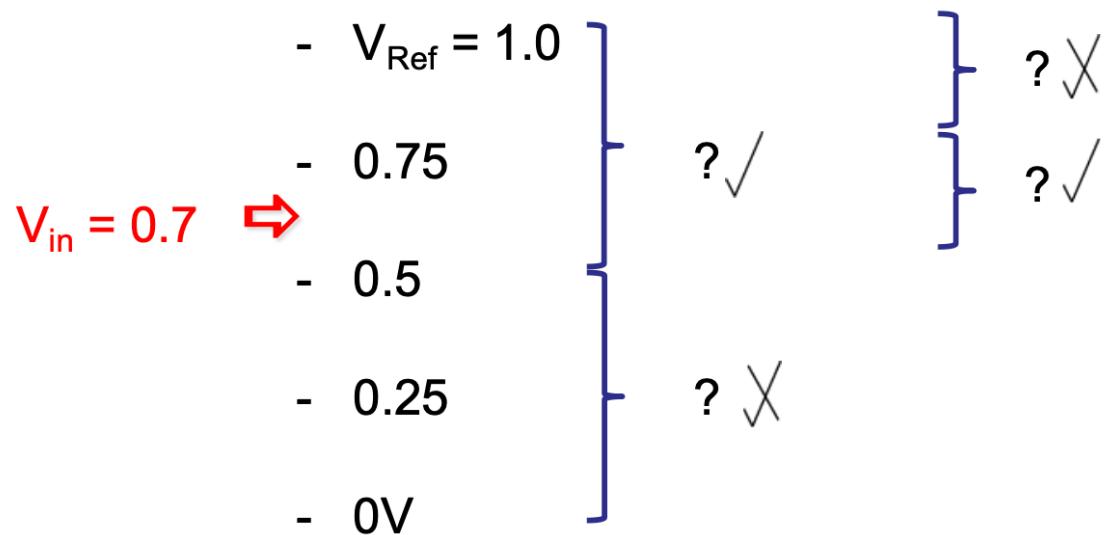- Example: For an 8-bit ADC (N=8), the maximum SNR is 49.76 dB


Successive Approximation

- **Key idea:** Performing a binary search, and finding 1 bit from each cycle, starting with the MSB





Successive Approximation Register (SAR)


- Binary search for input voltage

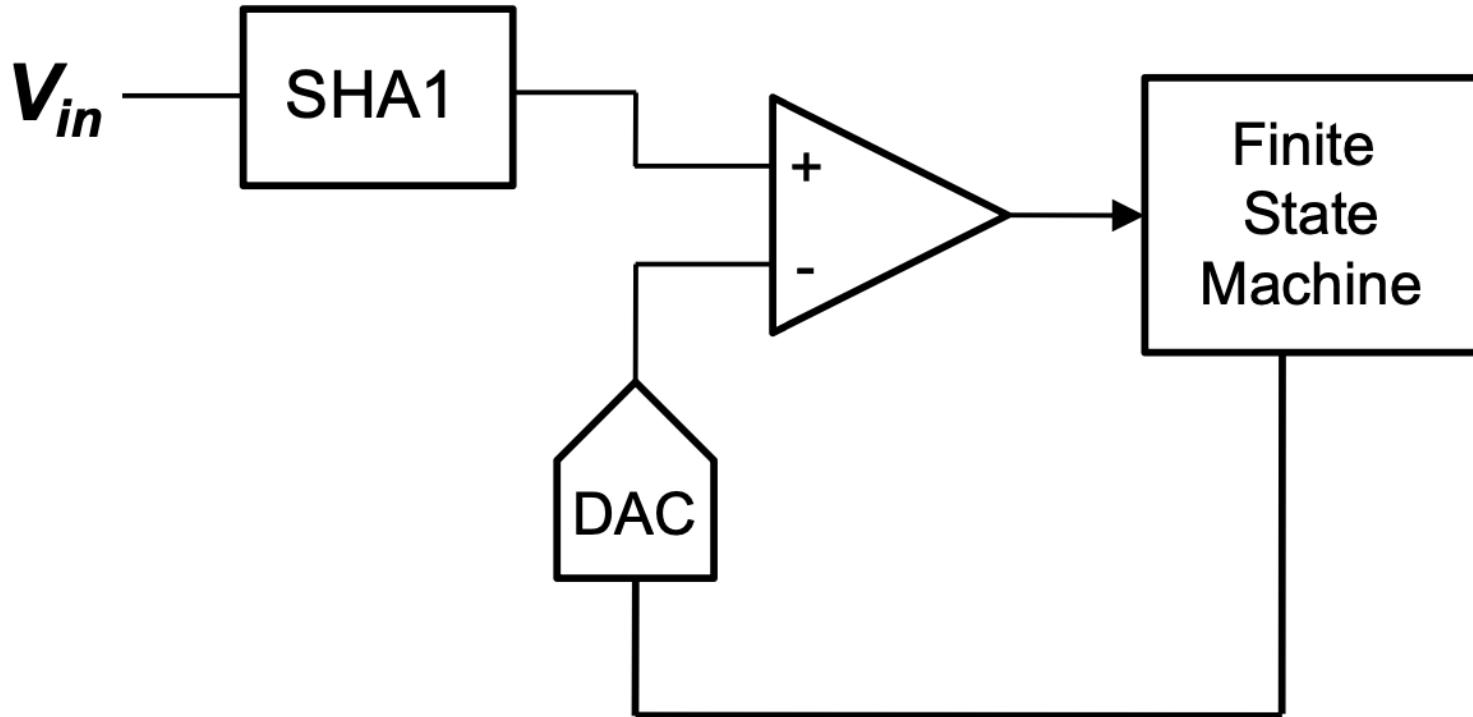

SAR Operation

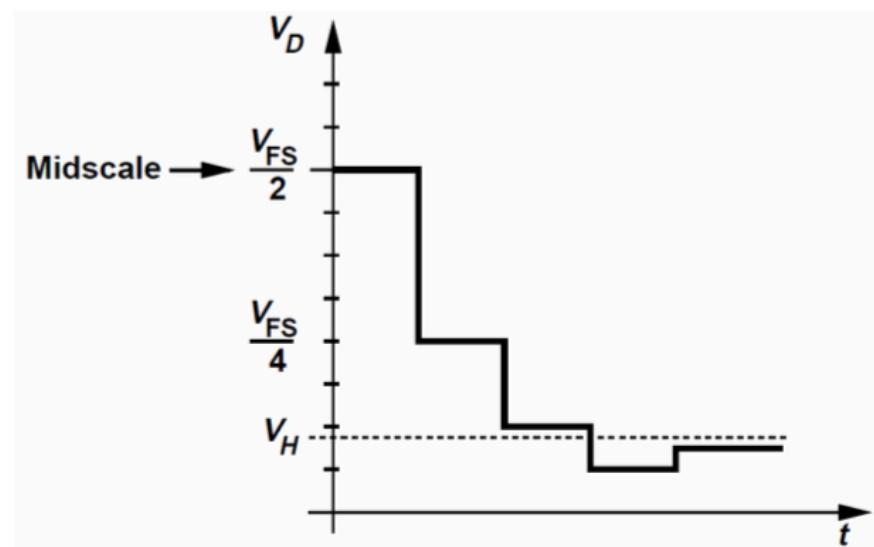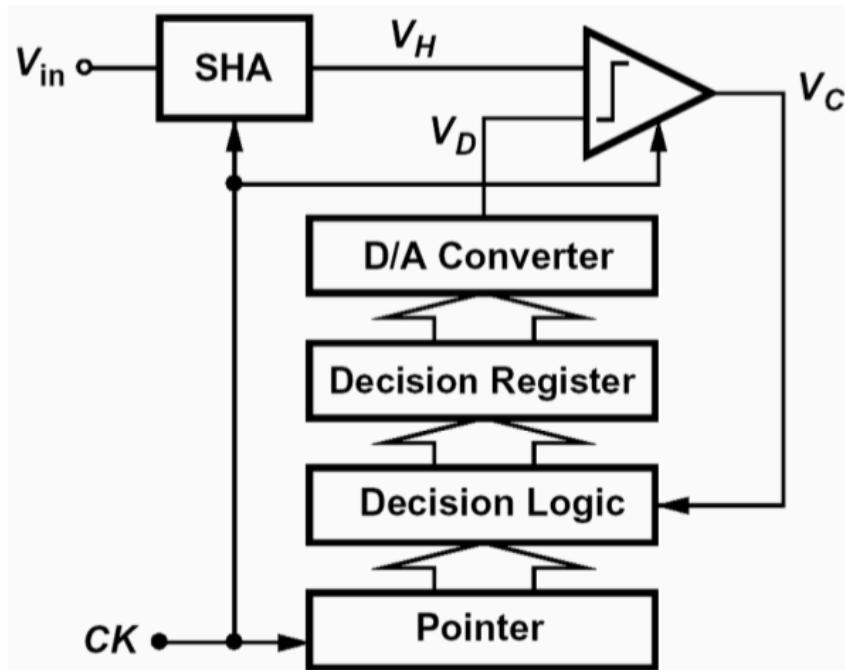


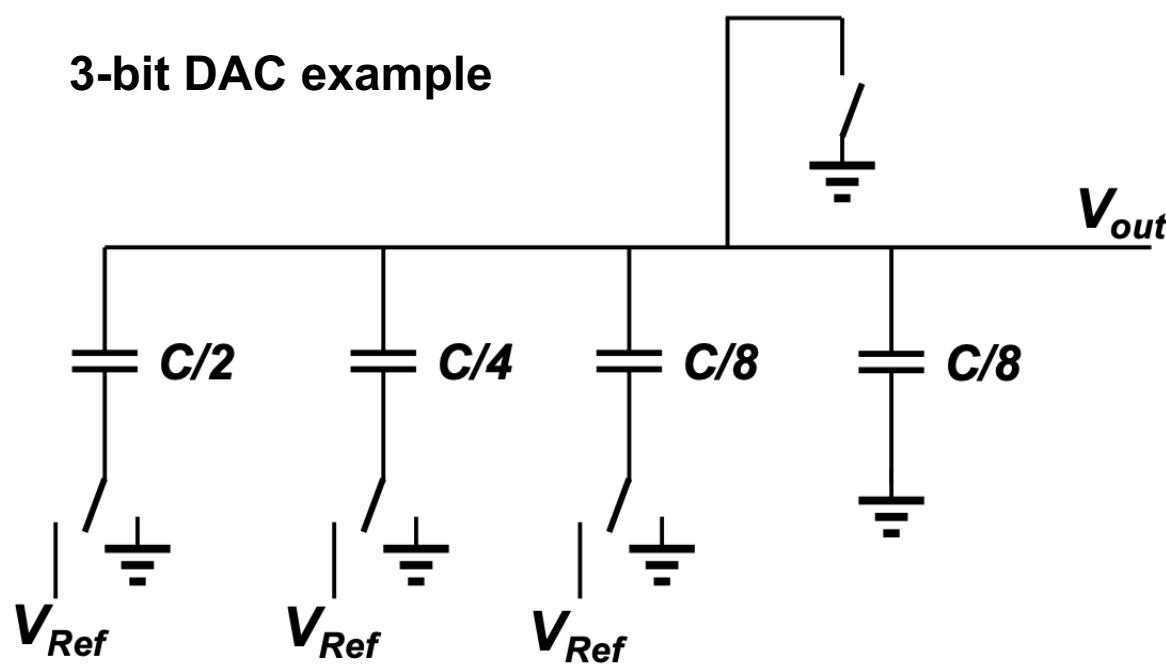- Capacitive DACs are common in SAR ADC
- Most common: Charge Redistribution DAC
- Switches individually connect to V_{Ref} or ground




CDAC Operation (1) - Reset

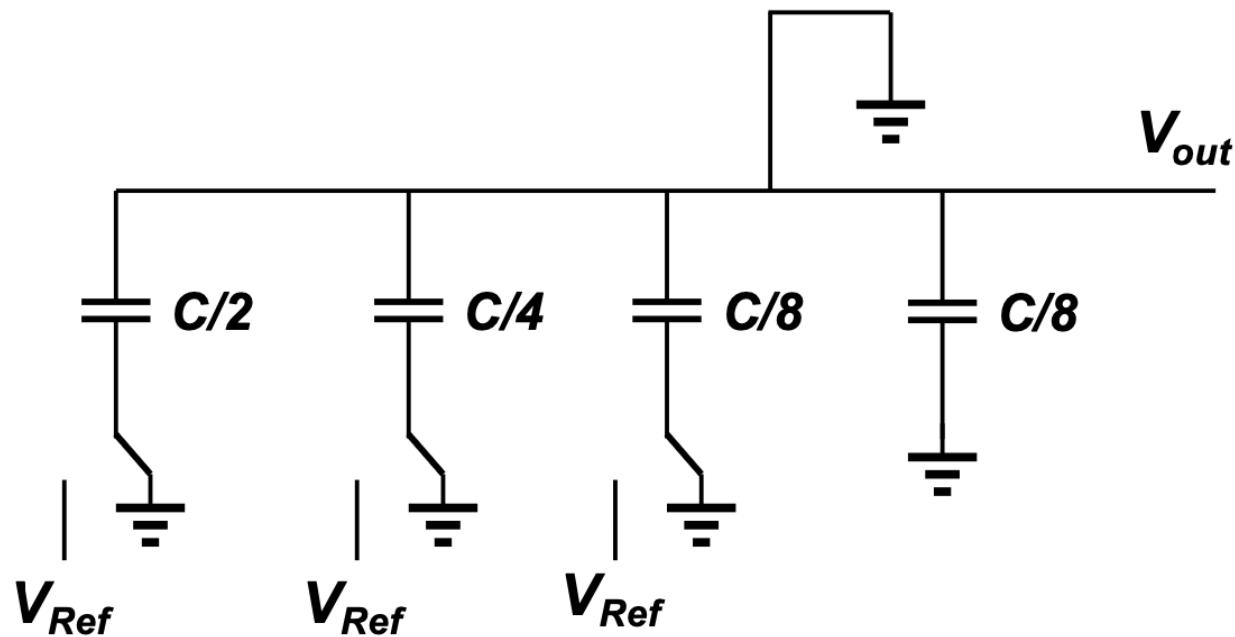- Reset charge on all caps
- Shorting top and bottom connections to GND




CDAC Operation (2) – Charge Redistribution

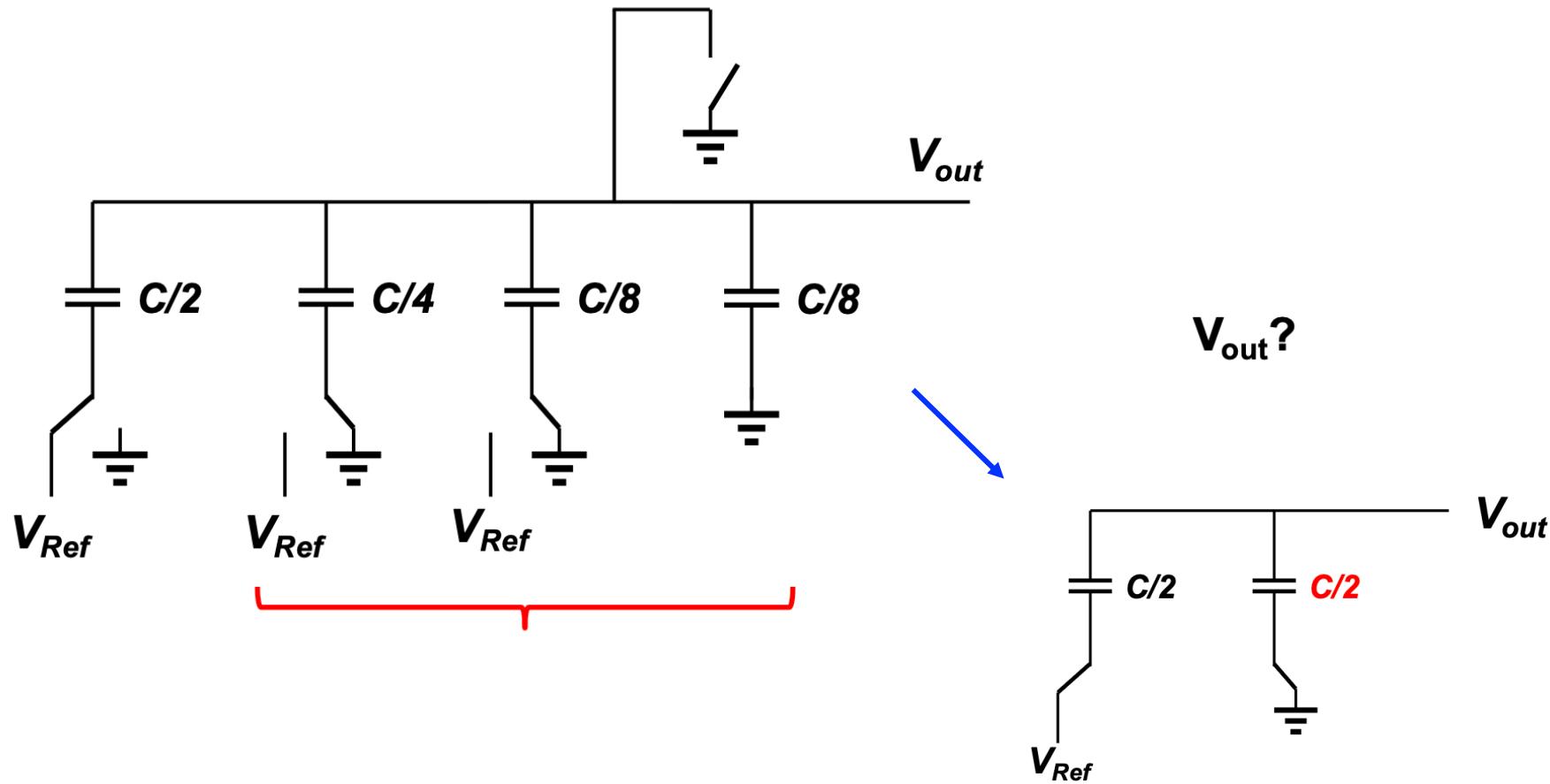- Dial up a voltage by connecting the switches in a binary fashion to V_{Ref}
- Let's say we want code 100:




SHA combined with CDAC – Sample Phase

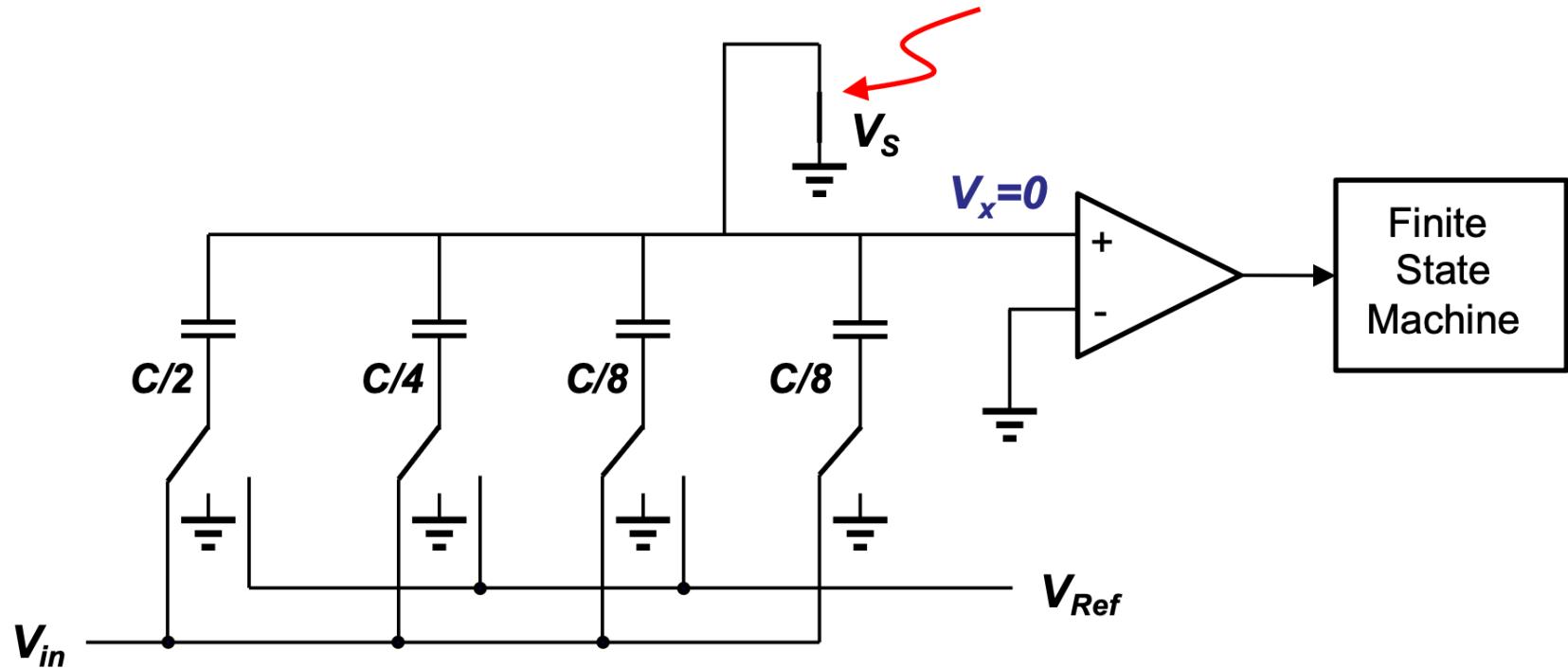- It is possible to combine S/H capacitance with CDAC
- Use the same cap for sampling and DAC




Redistribution Phase

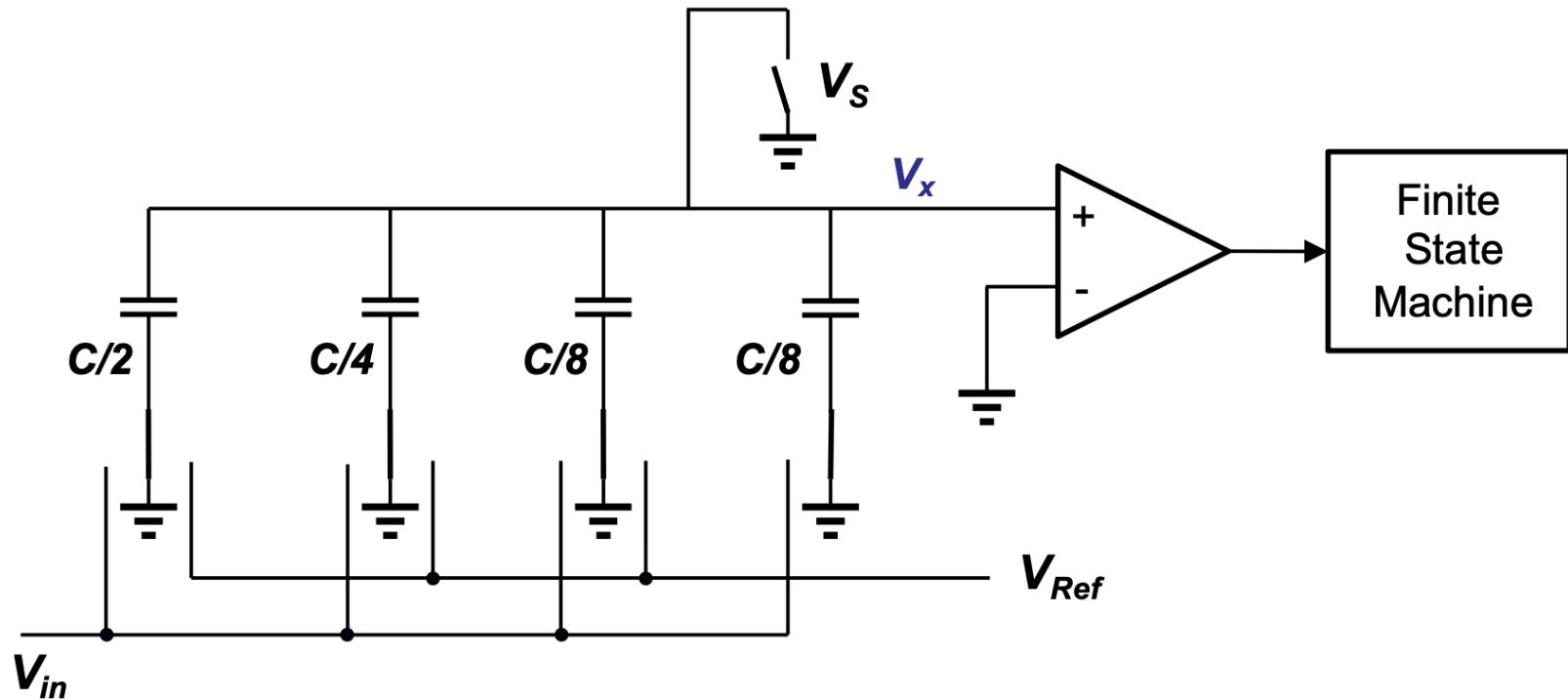- Sampling switches are connected to ground
- $V_x = -V_{in}$



3-bit ADC Example: MSB Trial

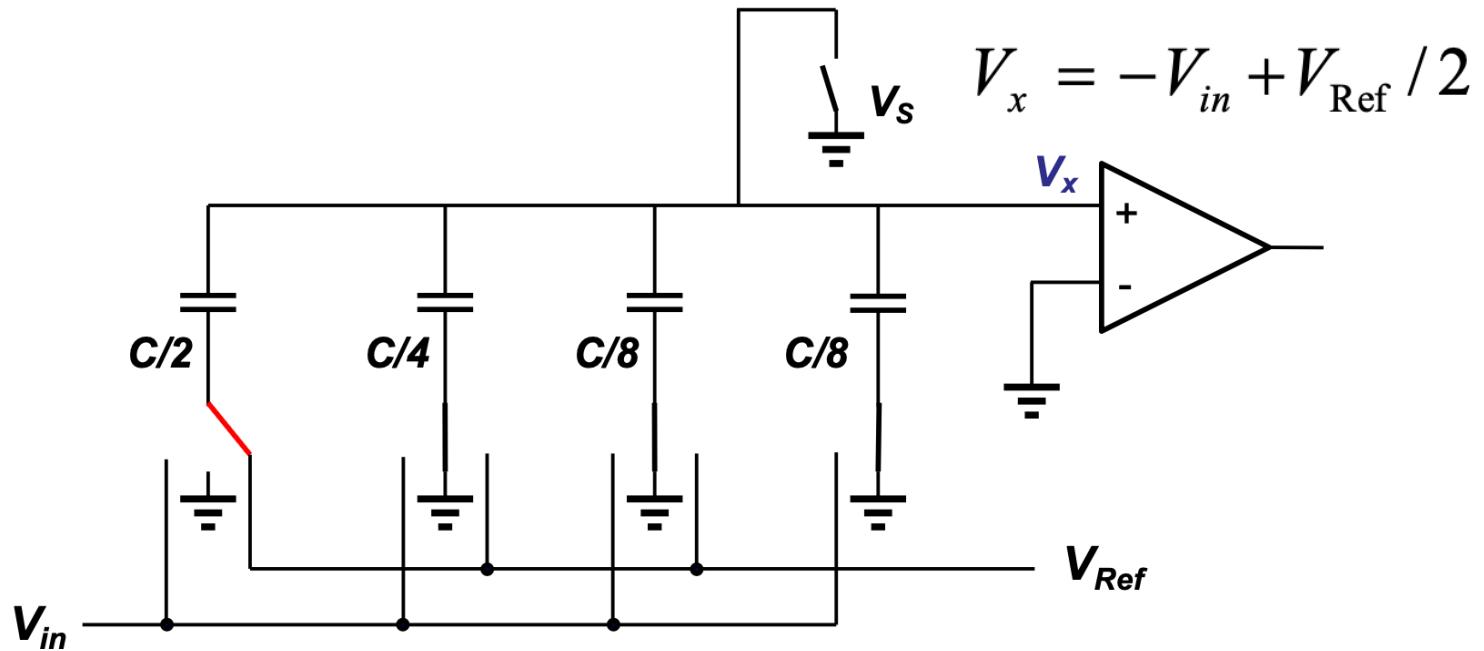- Next test if $V_{in} > V_{ref}/2$, or is MSB (b_0) = 1?




If $V_x > 0 \Rightarrow$

If $V_x < 0 \Rightarrow$

- Then proceed to next most significant bit (i.e., b_1) and so on...

3-bit ADC Example

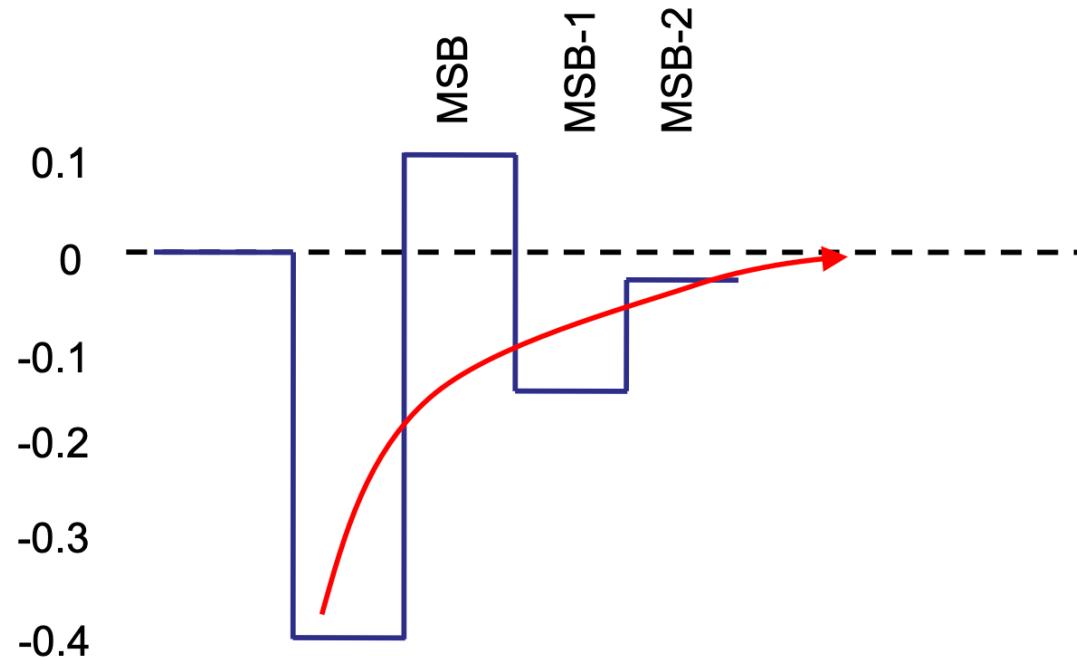
- Waveform at V_x (the comparator input) during conversion
- $V_{ref} = 1V$, $V_{in} = 0.4V_{ref}$



- V_x gets closer and closer to the ground

SAR Logic

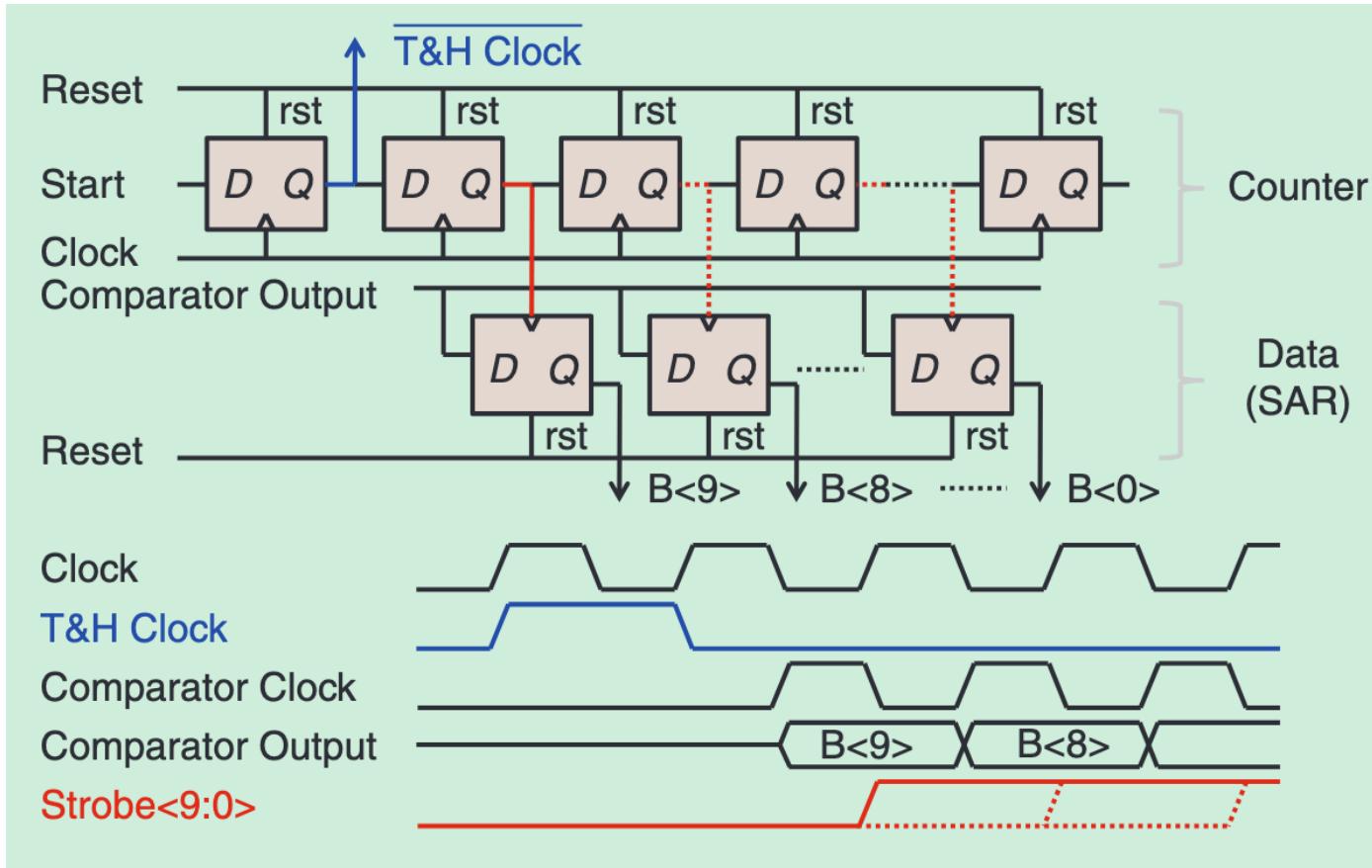
- The logic controls the operation of ADC and generates the digital output code




P. Harpe, *IEEE Solid-State Circuits Magazine*, 2016

Fully Differential SAR ADC

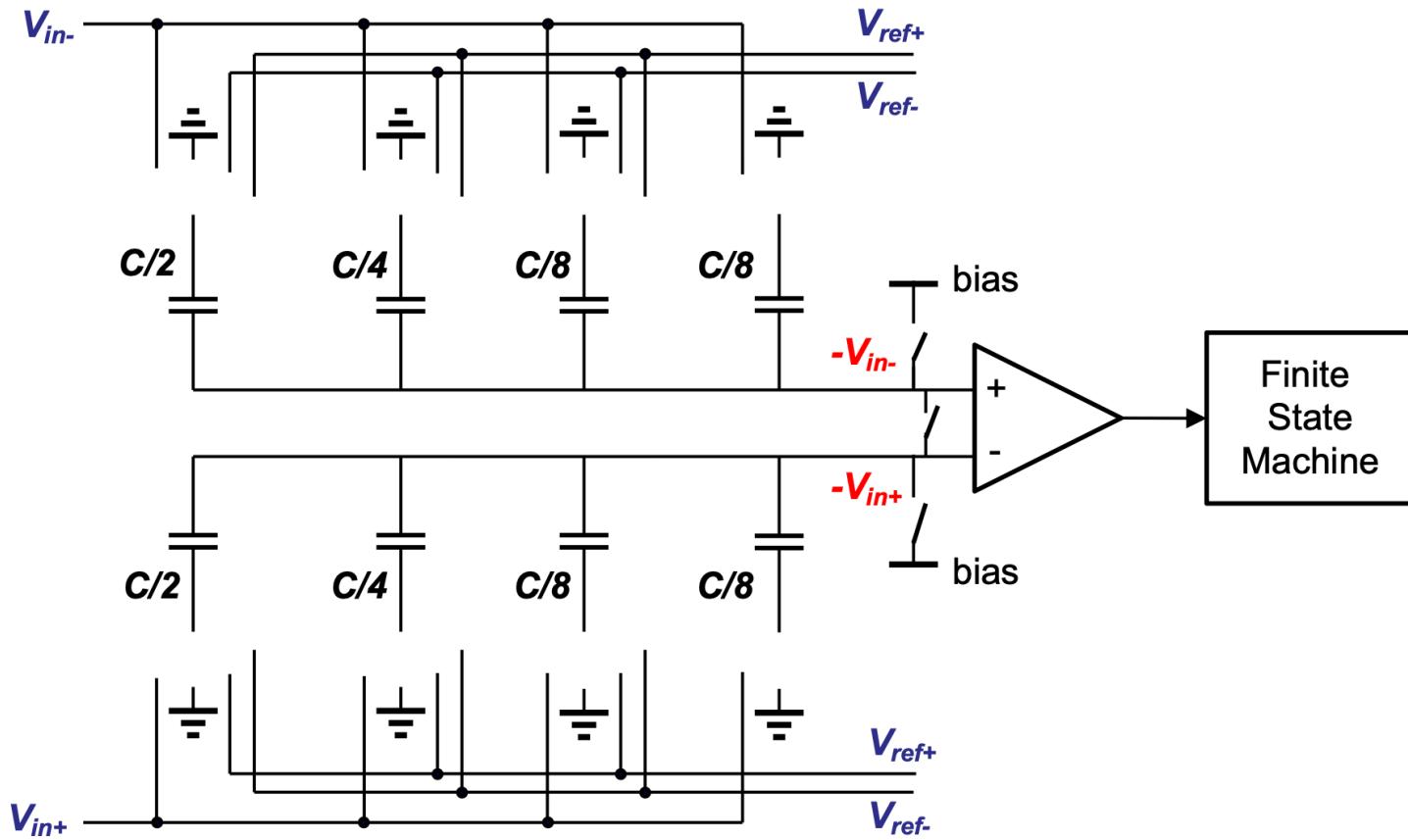
- N-bit differential SAR has 2^{N-1} unit caps on each side
- Comparator decides the sign (i.e., MSB) and 3 bits
- Connect to V_{ref+} , V_{ref-} depending on MSB decision, continue with other bits



CDAC Topologies

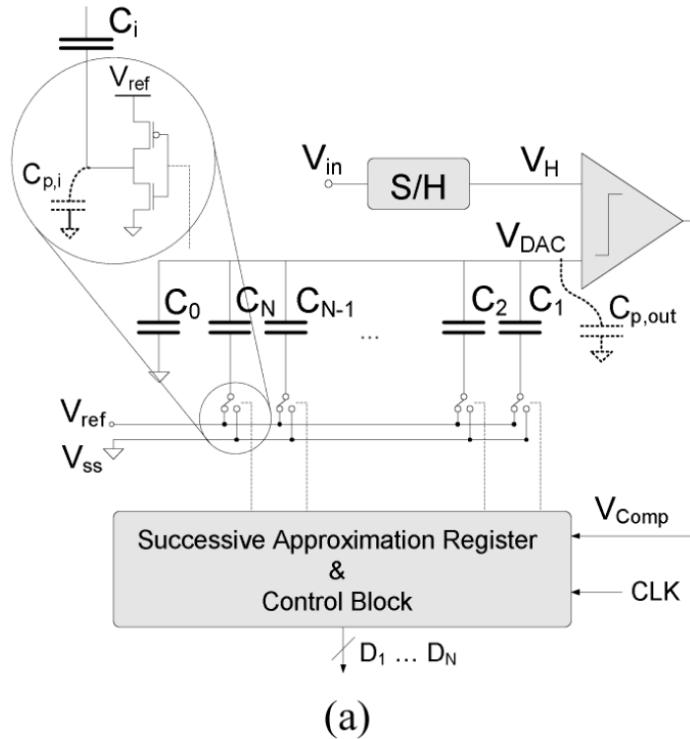

Conventional Binary Weighted (CBW)

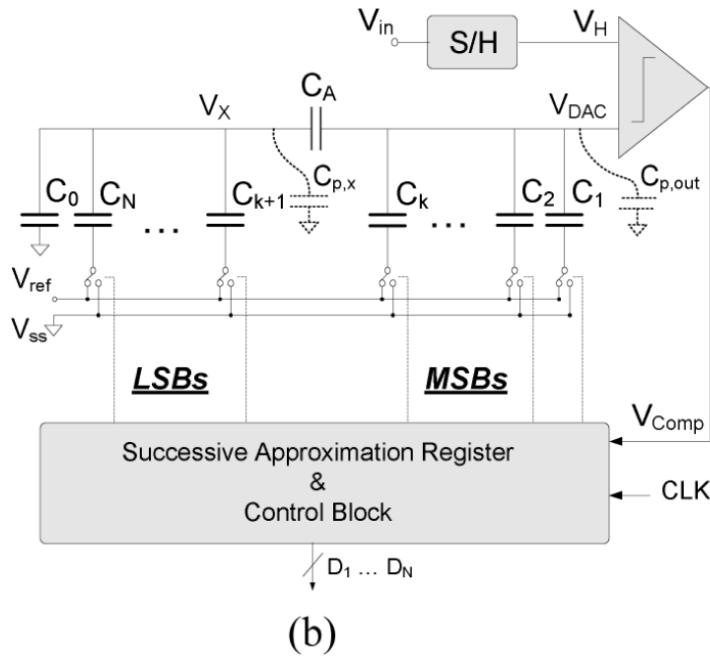

Binary Weighted w/ Attenuator Cap (BWC)

M. Saberi, et al., TCAS-I, 2011

StrongARM Latch Comparator

The StrongARM latch has become popular for three reasons:

- it consumes zero static power
- it directly produces rail-to-rail outputs
- its input-referred offset arises from primarily one differential pair



T. Kobayashi, et al., *VLSI Circuits Symp.*, 1992

StrongARM Latch Comparator

The StrongARM latch has become popular for three reasons:


- it consumes zero static power
- it directly produces rail-to-rail outputs
- its input-referred offset arises from primarily one differential pair

 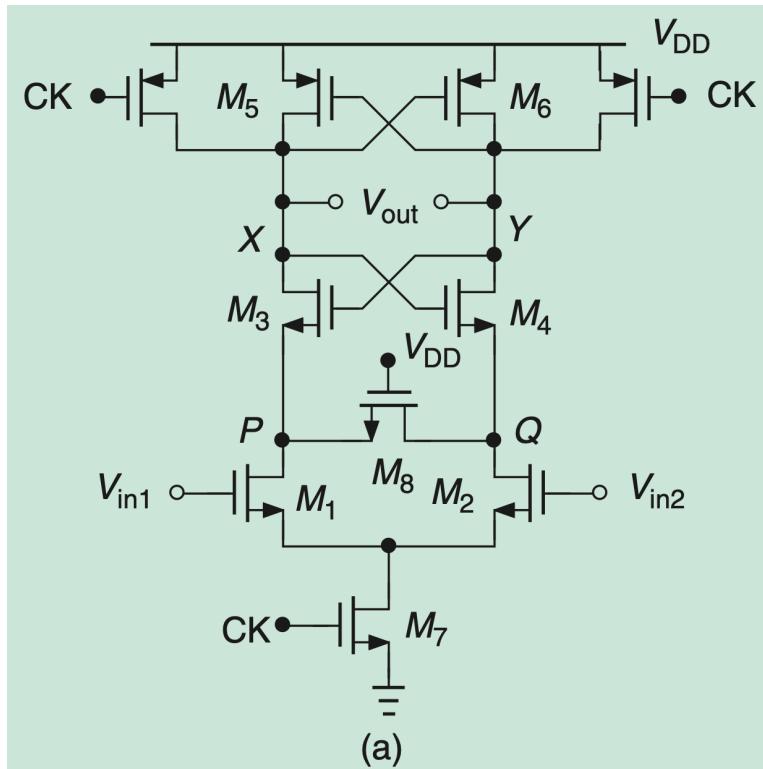(a) The original and (b) modified StrongARM latch topologies




Y. T. Wang and B. Razavi, JSSC, 2000

StrongARM Latch Comparator: Phase 1

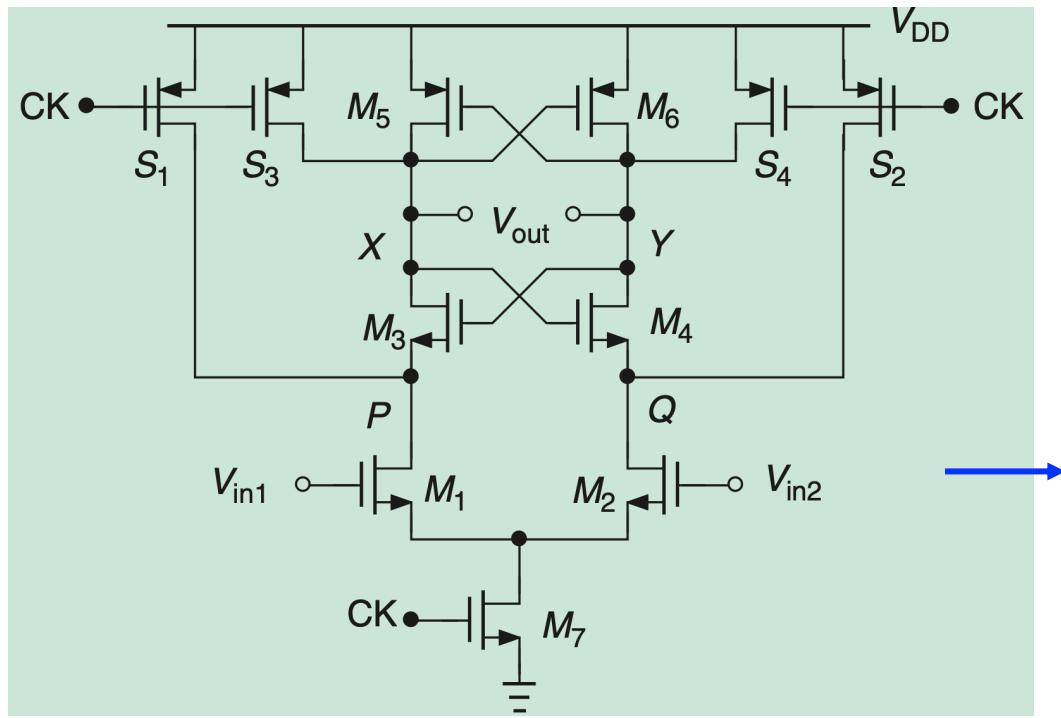


(1) Precharge

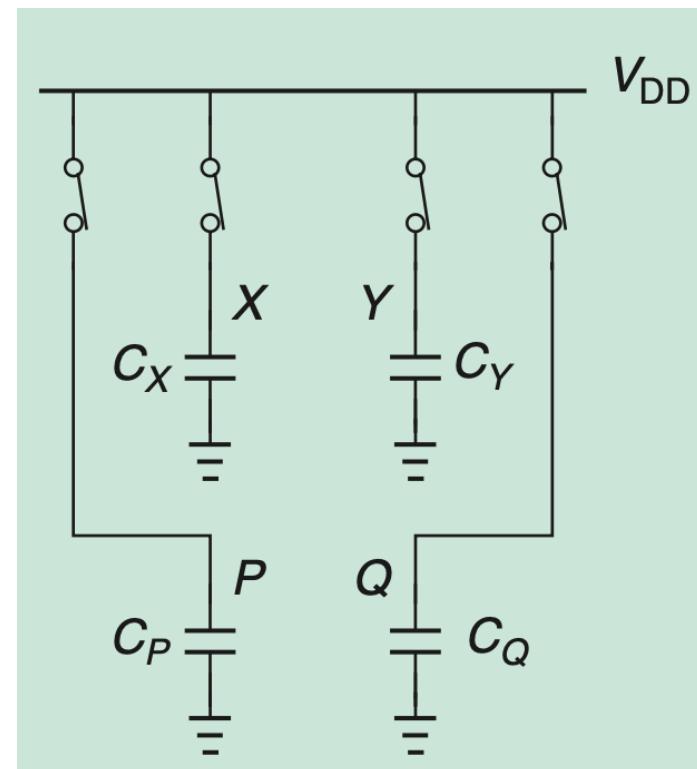

StrongARM Latch Comparator: Phase 2


(2) Amplification

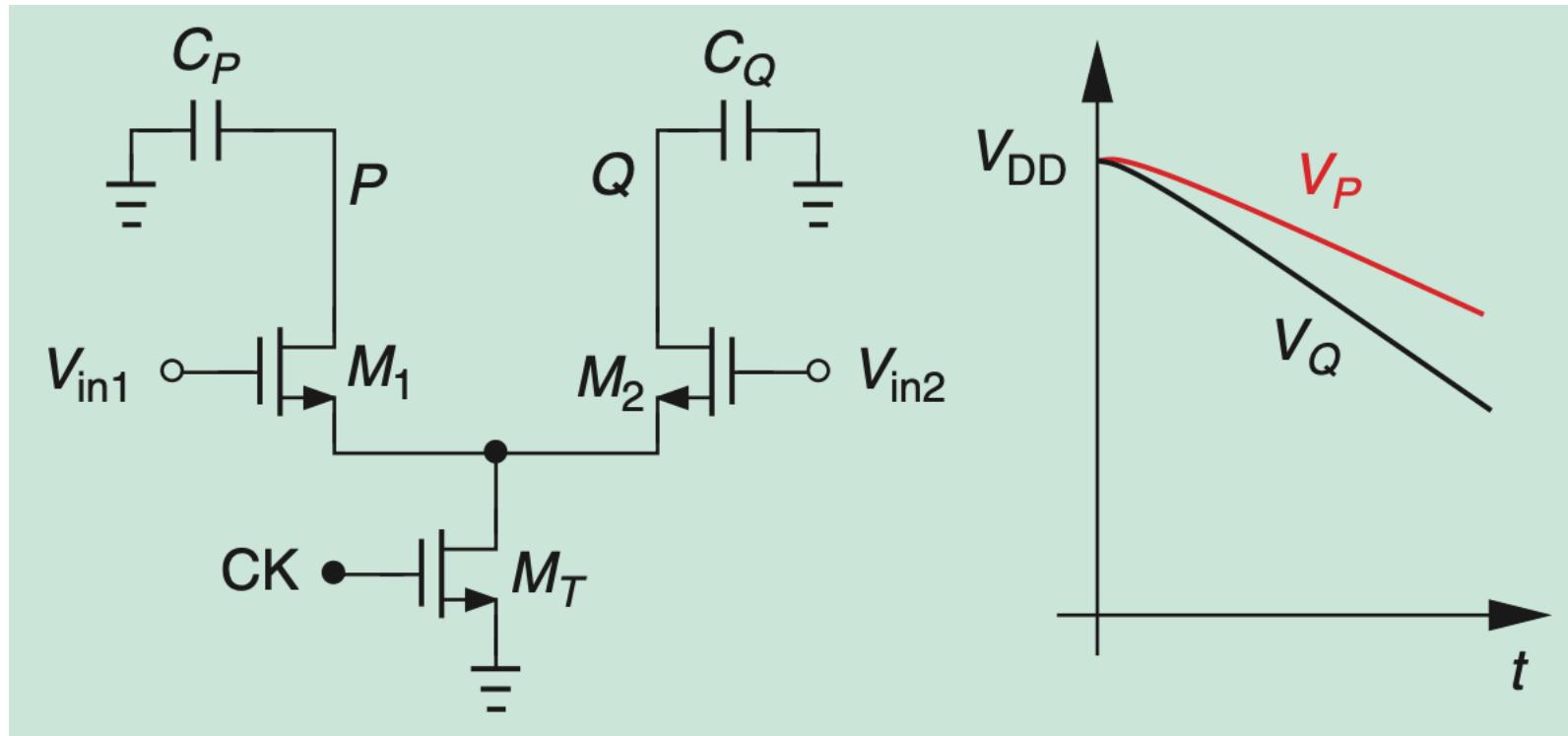

$$|V_P - V_Q| \approx (g_{m1,2} |V_{in1} - V_{in2}| / C_{P,Q}) t$$


StrongARM Latch Comparator: Phase 3

(3) Turn-on of cross-coupled NMOS pair

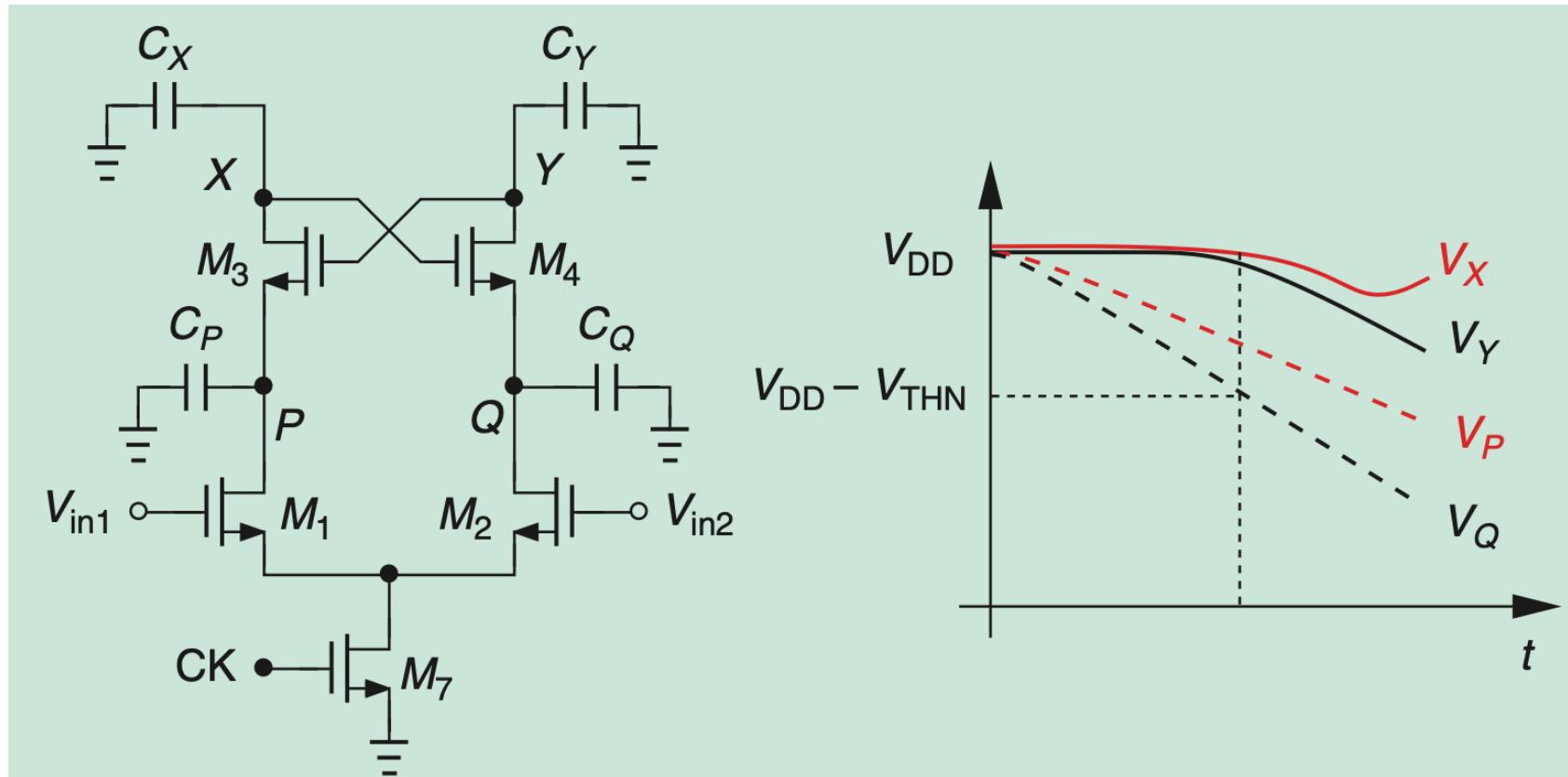

StrongARM Latch Comparator: Phase 3


Equivalent circuit

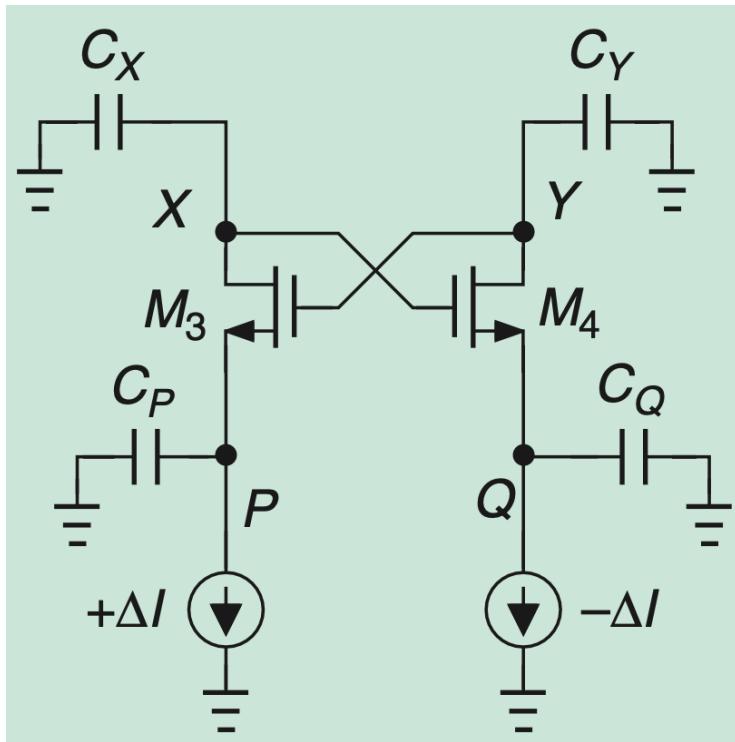

$$\begin{aligned}-C_X \frac{dV_X}{dt} &= g_{m3}(V_Y - V_P) \\-C_Y \frac{dV_Y}{dt} &= g_{m4}(V_X - V_Q) \\-C_P \frac{dV_P}{dt} &= C_X \frac{dV_X}{dt} + \Delta I \\-C_Q \frac{dV_Q}{dt} &= C_Y \frac{dV_Y}{dt} - \Delta I.\end{aligned}$$

StrongARM Latch Comparator: Phase 3

Equivalent circuit

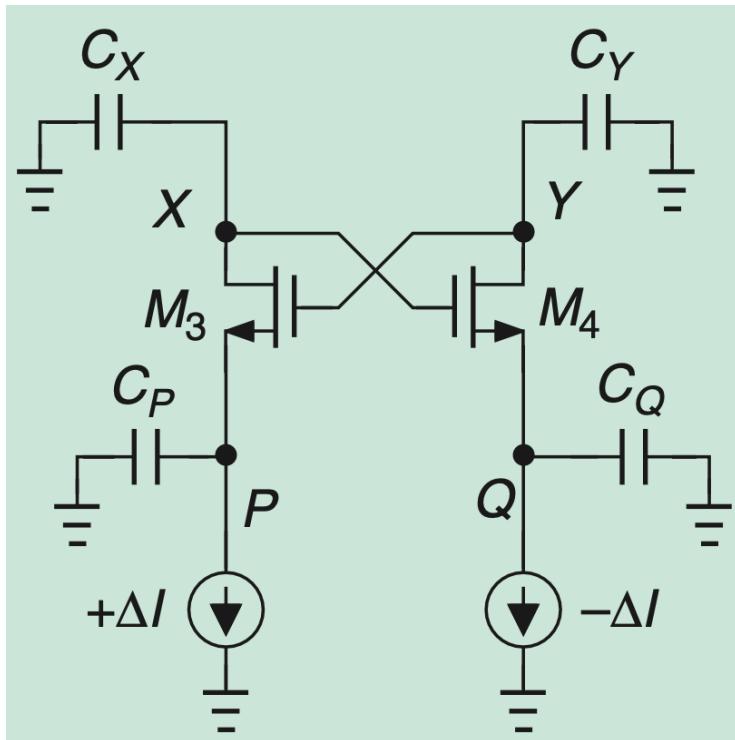

$$-C_X \frac{dV_X}{dt} = g_{m3}(V_Y - V_P)$$

$$-C_Y \frac{dV_Y}{dt} = g_{m4}(V_X - V_Q)$$

$$-C_P \frac{dV_P}{dt} = C_X \frac{dV_X}{dt} + \Delta I$$

$$-C_Q \frac{dV_Q}{dt} = C_Y \frac{dV_Y}{dt} - \Delta I.$$

$$-C_{X,Y} \frac{d(V_X - V_Y)}{dT} = g_{m3,4}(-V_X + V_Y - V_P + V_Q)$$

$$C_{X,Y} \frac{d(V_X - V_Y)}{dt}$$

$$-g_{m3,4} \left(1 - \frac{C_{X,Y}}{C_{P,Q}} \right) (V_X - V_Y)$$


$$= -2g_{m3,4} \frac{\Delta I}{C_{P,Q}} t.$$

$$C_{P,Q}(V_Q - V_P) = C_{X,Y}(V_X - V_Y) + 2\Delta I t$$


$$\tau_{\text{reg}} = \frac{C_{X,Y}}{g_{m3,4} (1 - C_{X,Y}/C_{P,Q})}$$

StrongARM Latch Comparator: Phase 4


(4) Turn-on of cross-coupled PMOS pair

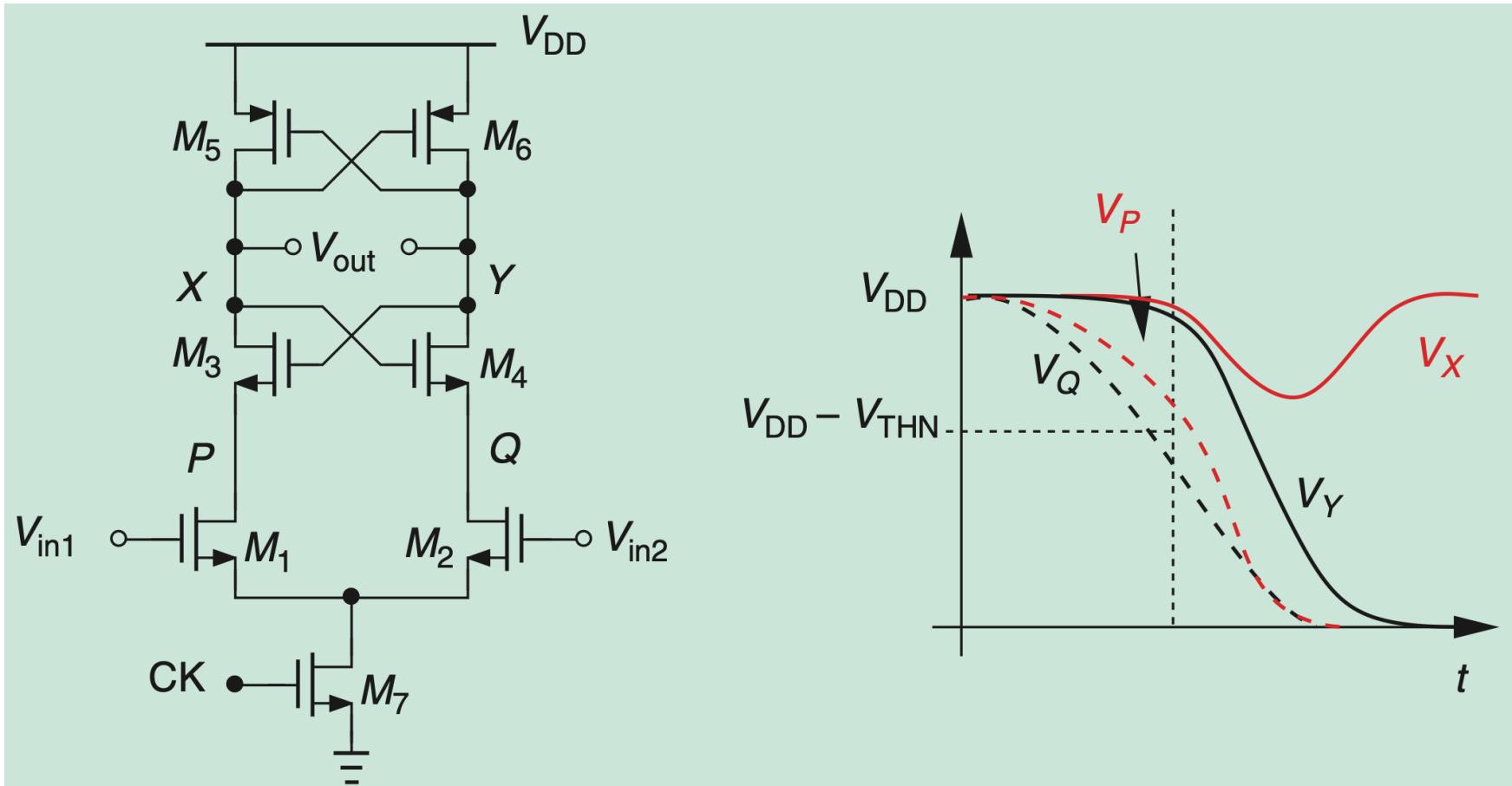


StrongARM Latch Comparator

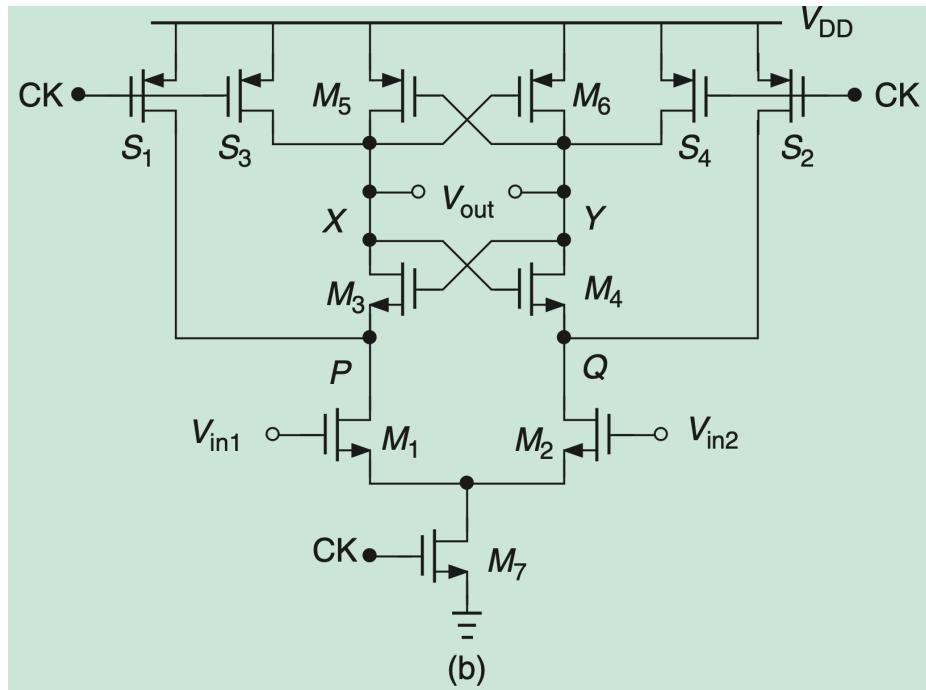


StrongARM Latch Comparator

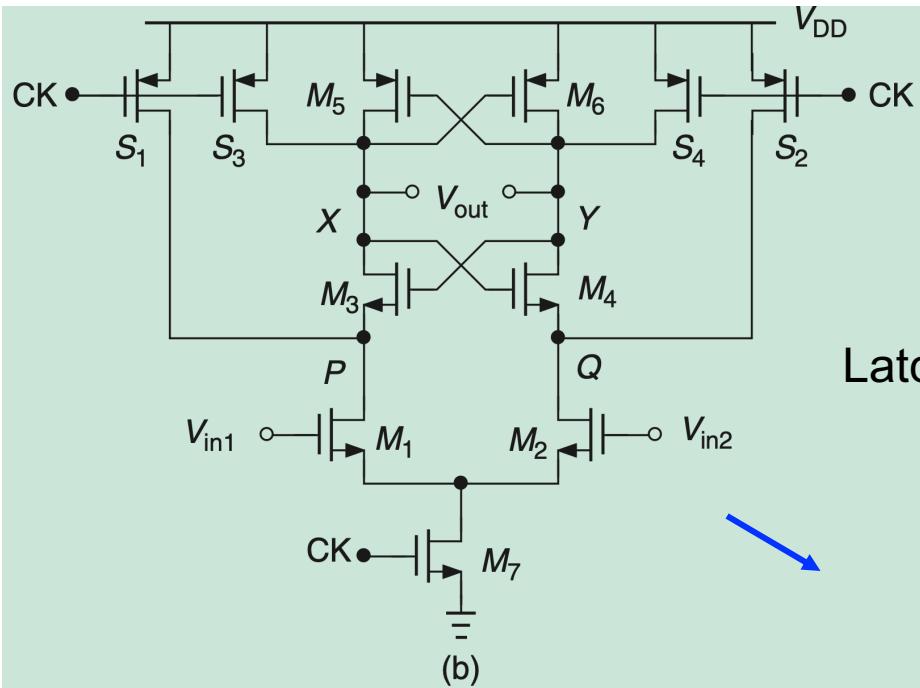

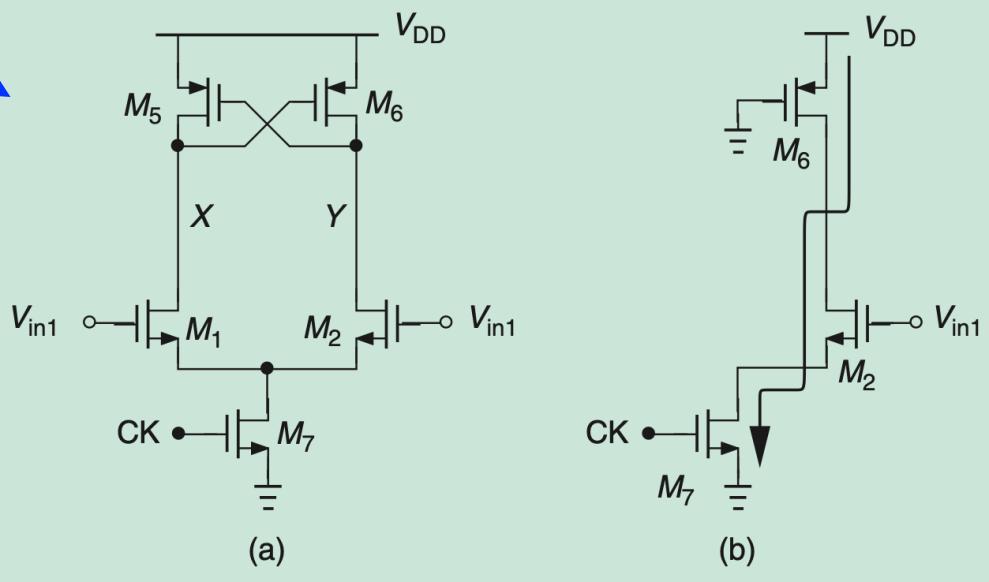
Latch without cross-coupled NMOS pair and the resulting static current



StrongARM latch followed by the RS latch

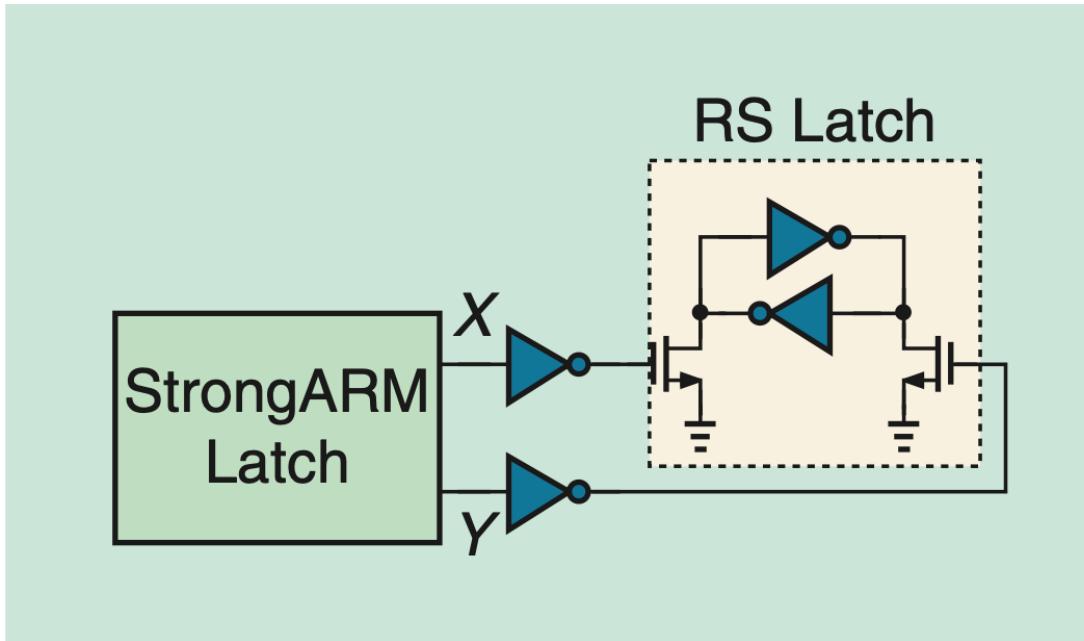

StrongARM Latch: Offset

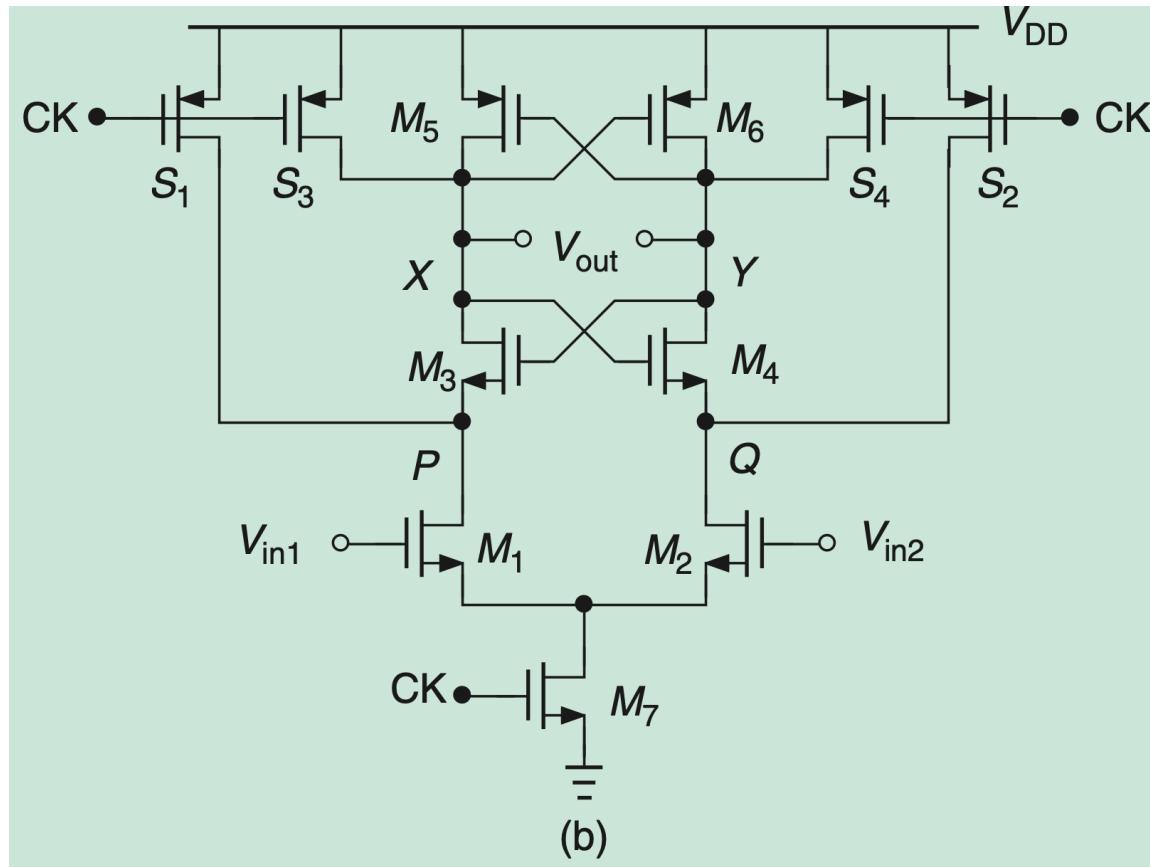

References

- M. J. M. Pelgrom, "Analog-to-Digital Conversion", 3rd ed., Springer, 2017.
- B. Razavi, "The StrongARM Latch [A Circuit for All Seasons]," in *IEEE Solid-State Circuits Magazine*, vol. 7, no. 2, pp. 12-17, Spring 2015, doi: 10.1109/MSSC.2015.2418155.
- M. Saberi, R. Lotfi, K. Mafinezhad, W. A. Serdijn, "Analysis of Power Consumption and Linearity in Capacitive Digital-to-Analog Converters Used in Successive Approximation ADCs," in *IEEE Transactions on Circuits and Systems I: Regular Papers*, vol. 58, no. 8, pp. 1736-1748, Aug. 2011, doi: 10.1109/TCSI.2011.2107214.
- Data converter slides by Prof Flynn, University of Michigan
- Data converter slides by Prof Tajalli, University of Utah
- P. Harpe, "Successive Approximation Analog-to-Digital Converters: Improving Power Efficiency and Conversion Speed," in *IEEE Solid-State Circuits Magazine*, vol. 8, no. 4, pp. 64-73, Fall 2016.
- T. Kobayashi, et al., "A current-mode latch sense amplifier and a static power saving input buffer for low-power architecture," in *Proc. VLSI Circuits Symp. Dig. Technical Papers*, June 1992, pp. 28–29.
- Y. T. Wang and B. Razavi, "An 8-bit 150-MHz CMOS A/D converter," *IEEE J. Solid-State Circuits*, vol. 35, pp. 308–317, Mar. 2000.