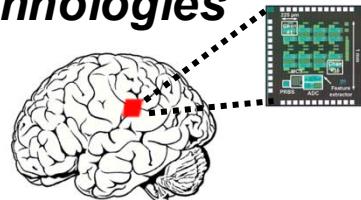


*Integrated Neurotechnologies  
Laboratory*

**EPFL**



## Advanced analog integrated circuit design (EE-523), Lecture 7

Armin Tajalli (invited speaker, visiting Professor)

Institutes of Electrical and Micro Engineering and Neuro-X, School of Engineering, EPFL

# Advanced Analog Integrated Circuit Design (EE-523), Lecture 7

# Sigma-Delta ADC

Prof. Armin Tajalli, University of Utah  
Spring 2025



- Basic Concept
- Background
- Oversampling Process
- Noise shaping
- Implementation
- Non-ideal effects
- More complex topologies
- Summary

# Basics of Sigma-Delta ADCs

# Introduction Overall Specifications

- SD architecture offers a very high level of precision (12 to 24 bits)
- Key concept: oversampling and noise shaping
- Slower than SAR and pipeline ADCs, but offers higher resolution
- Resolution range: 13 to 24b
- Frequency range: kS/s to MS/s

# Background


# Background Challenges to Improve Resolution



- There is a growing demand for implementing high-resolution data converters.
- Traditionally, audio systems require 16b or more resolution for providing a proper sound quality.
- Internet-of-Thing (IoT) is a new field, where high resolution data converters are essential (high-precision sensor interface).

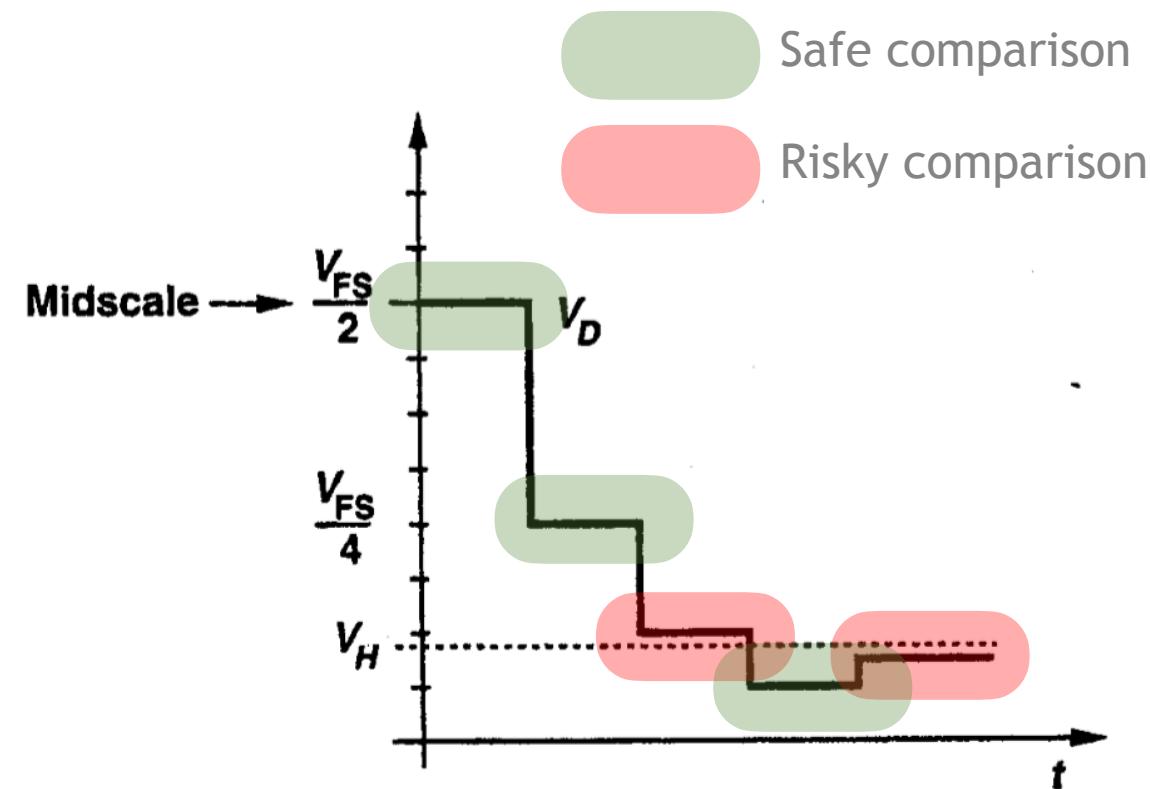
# Background Challenges to Improve Resolution

- SAR ADCs are energy-efficient and fast, however their resolution can not be extended beyond 12b
- There are some reports where resolution is above 12b, however employ heavy calibrations.
- What indeed is limiting the resolution of SAR ADCs?



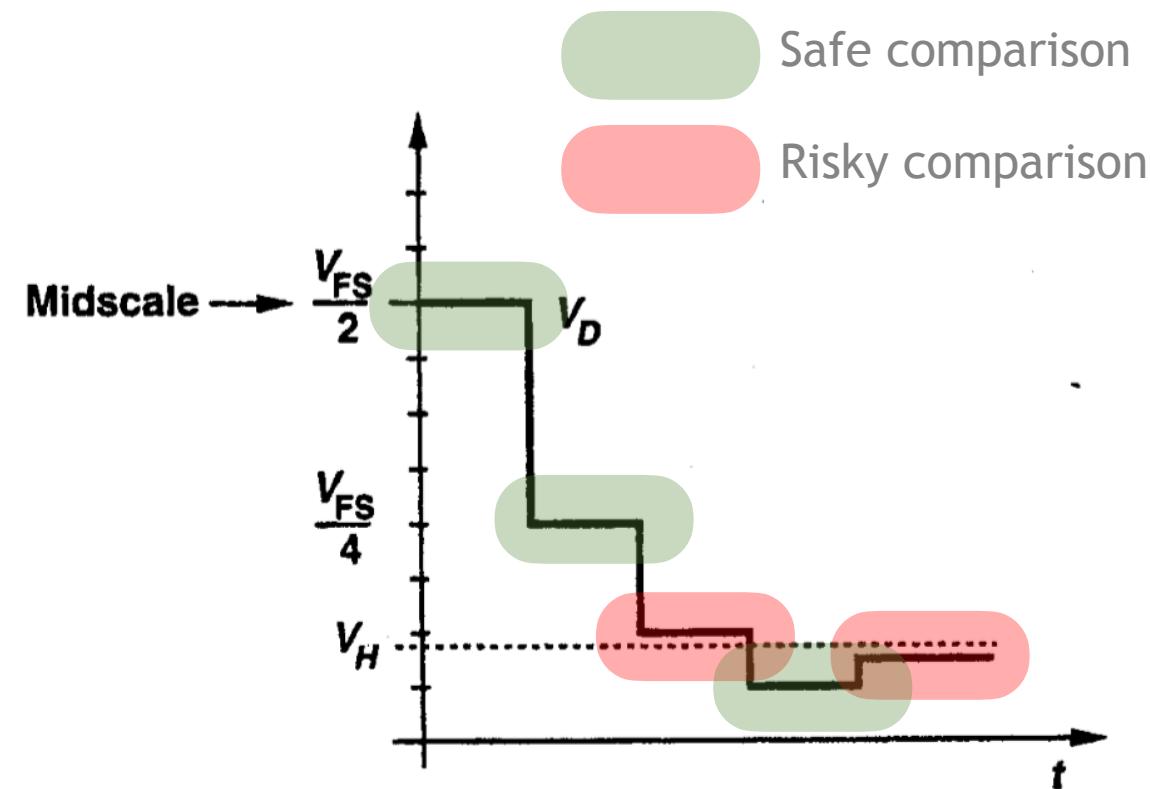
# Background Challenges to Improve Resolution

- There are at least two comparisons during the SAR process that suffer from noise and also device mismatch.
- SAR does not employ any correction mechanism to mitigate these issues (noise and device and mismatch).
- The other issue, that cannot be addressed easily, is meta-stability.
- **Conclusion:** resolution of SAR will be limited to  $\sim 12b$ .


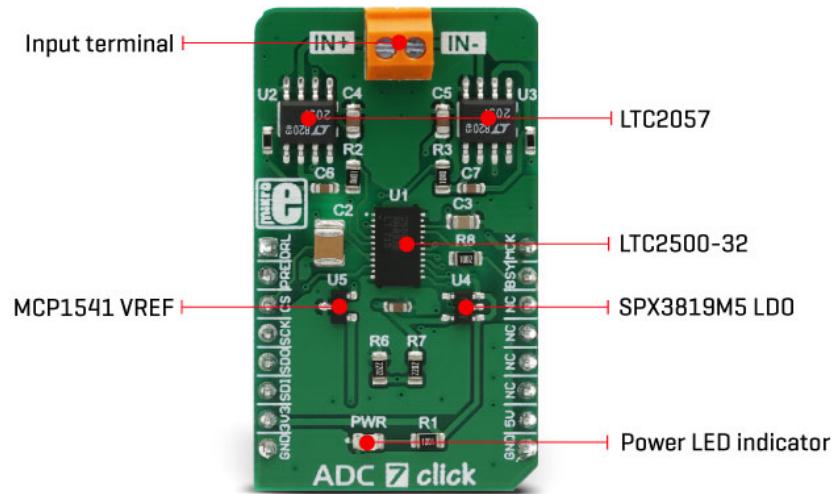
# Background Challenges to Improve Resolution


- Having said that, there are examples of oversampled-SAR, where resolution is high.
- **Example:** oversampled-SAR with 32b resolution, operating at 61 Samples per second.



# Oversampling Process

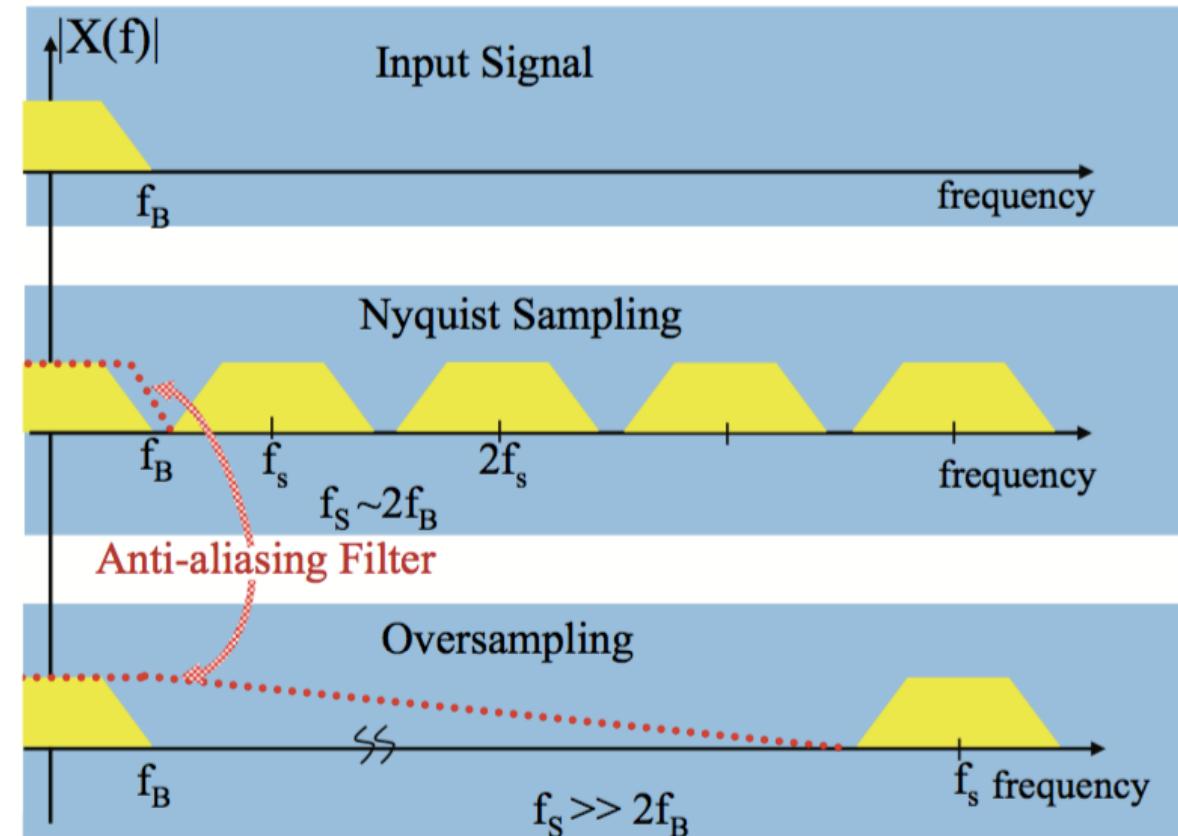
# Introduction Oversampling Concept

- **Main goal:** do some extra signal processing in order to improve precision of data converters.
- **Concept:** could we use averaging to improve precision ?
- **Example,** take few extra samples, consider the average value of those samples, thus remove random and quantization noise.


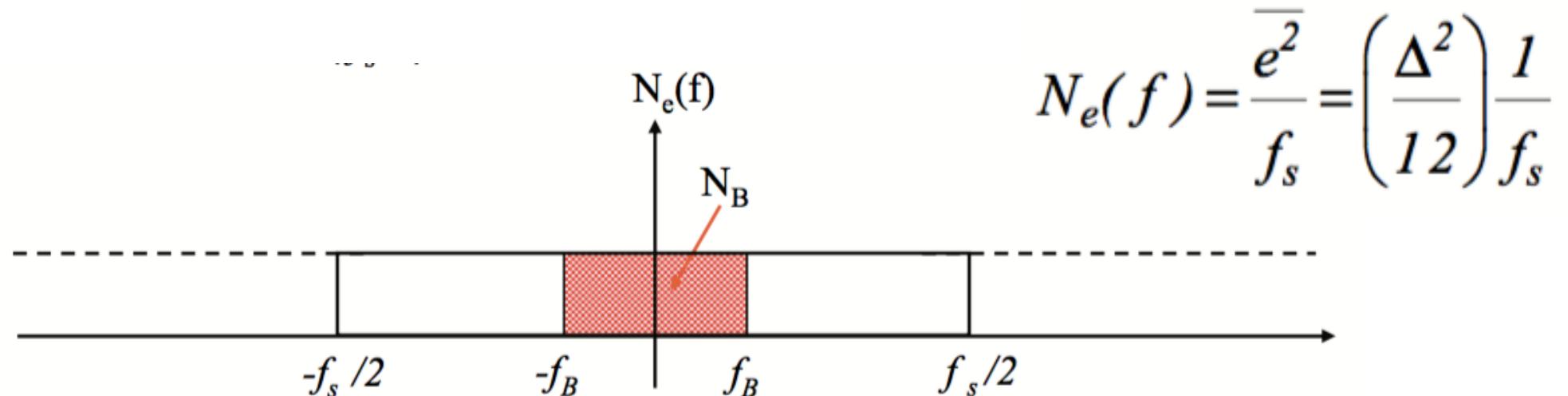
# Introduction Oversampling Concept

- **Key Concept:** reduce the effective quantization noise with reducing the integration BW:
  - Quantization noise power is indeed inversely proportional to the sampling frequency.



# Introduction Oversampling Concept

- Integrating the noise over a smaller BW, results in lower RMS quantization noise.
- **Note:** to reduce the noise power using averaging technique, the noise source needs to be random.

$$\begin{aligned} S_B &= \int_{-f_B}^{f_B} N_e(f) df = \int_{-f_B}^{f_B} \left( \frac{\Delta^2}{12} \right) \frac{1}{f_s} df \\ &= \frac{\Delta^2}{12} \left( \frac{2f_B}{f_s} \right) \end{aligned}$$

# Introduction Oversampling Concept

- Equivalently, SNR of ADC can be improved by increasing the number of samples per unit interval:
  - Increase the oversampling ratio (OSR) to enhance SNR.
  - Example: Multiplying OSR by four, results in one bit more resolution


$$\text{OSR} = \frac{f_s}{f_{s,ny}} = \frac{f_s}{2f_b}$$

$$Q_b^2 = \frac{V_{\text{LSB}}^2 f_b}{6f_s} = \frac{V_{\text{LSB}}^2}{12} \frac{1}{\text{OSR}}$$

# Noise Shaping

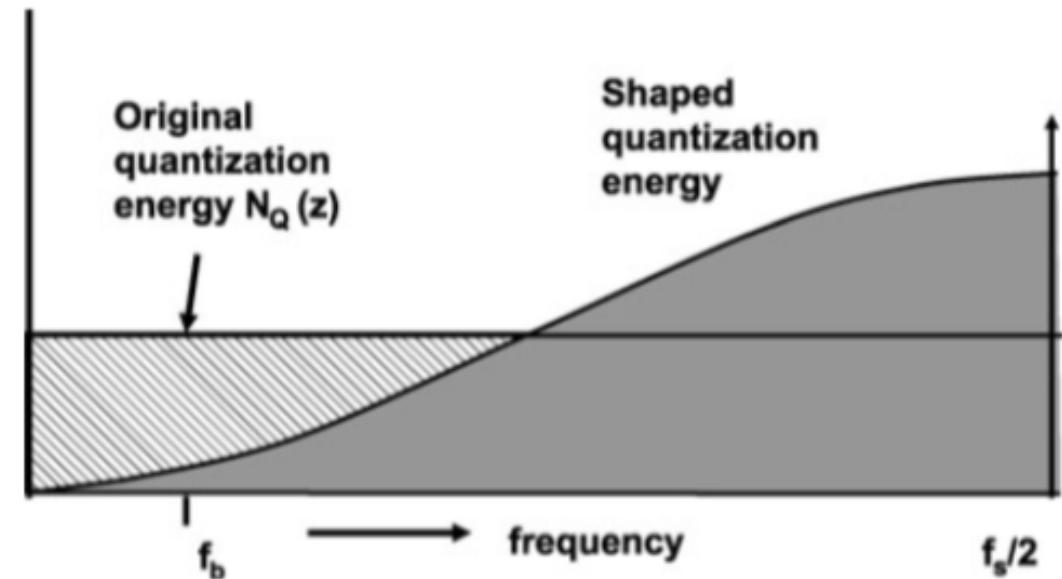
# Introduction Noise Shaping

- **Main goal:** filter out quantization noise by proper choice of the system Noise Transfer Function (NTF).
- High-pass filters can push out the quantisation noise from the band of interest.


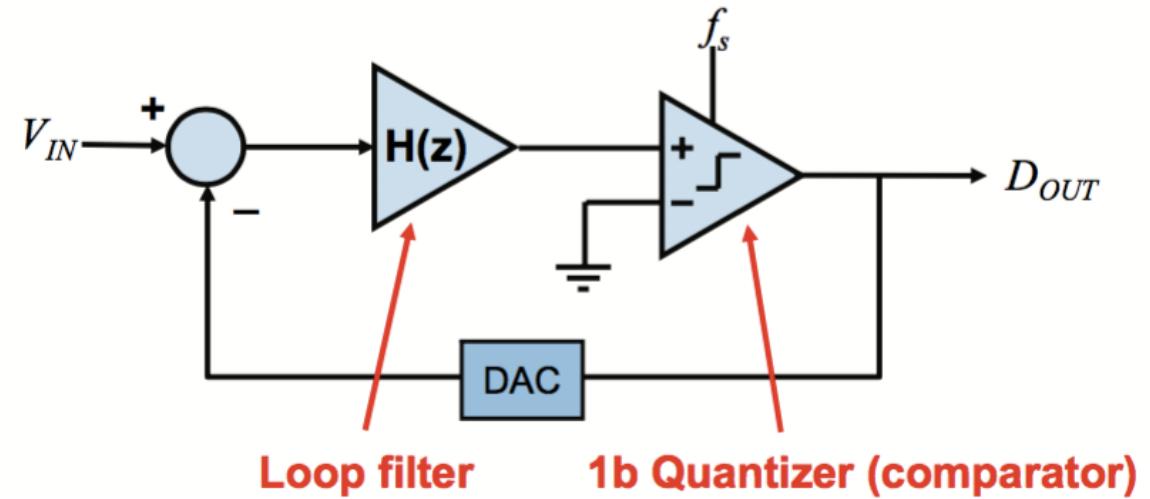
# Introduction Noise Shaping

- **Fundamental Concept:** Use a feedback structure, in which the Signal Transfer Function (STF) is low pass, while the NTF is high-pass.
- **Example:** A first order SDM
  - SDM: Sigma-Delta Modulator
  - $H(z)$ : an integrator or a low-pass filter.
- **Question:** any similarity to the SAR architecture?




# Introduction

## Noise Shaping: Analysis

- Small signal model of a first order SDM is shown:
  - $G(z)$ : integrator
  - $N_Q$ : low-resolution ADC. For example, this low-resolution ADC can be a single bit converter.
  - Quantization noise is modeled at the output of the comparator (or: 1b /ADC)

$$Y(z) = X(z) + [1 - z^{-1}]N_Q(z)$$

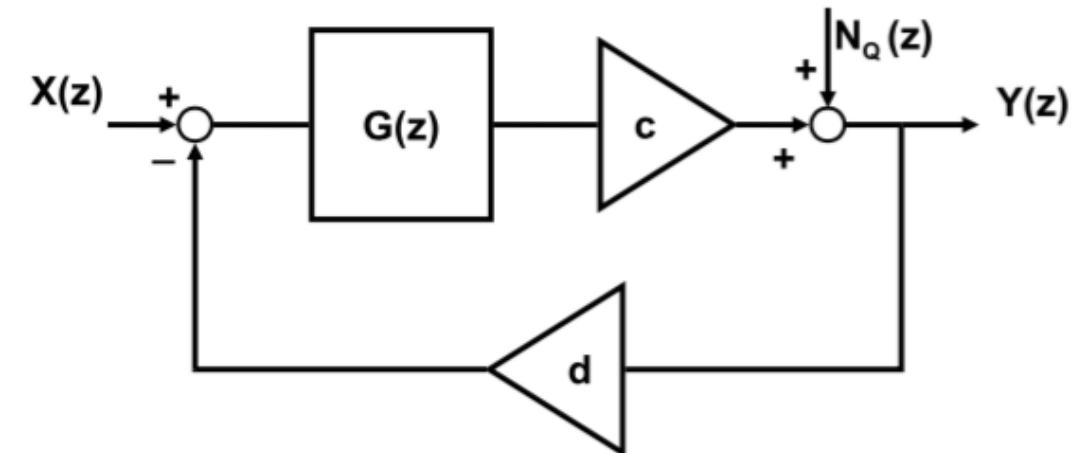

# Introduction

## Noise Shaping: Analysis

- The  $z^{-1}$  operator represents a unit delay in time domain.
- The unit delay can be represented in frequency domain (Laplace Transform):

$$Y(z) = X(z) + [1 - z^{-1}]N_Q(z)$$

$$z = e^{j\omega T_s}$$

# Introduction

## Noise Shaping: Analysis

- Frequency domain transfer function can be estimated using z-domain formulation.
- The noise transfer function is high-pass, while the signal transfer function is low pass.

$$Y(z) = X(z) + [1 - z^{-1}]N_Q(z)$$

$$Y(\omega) = X(\omega) + (1 - e^{-j\omega T_s})N_Q(\omega)$$

$$|\text{NTF}(\omega)|^2 = \left| \frac{Y(\omega)}{N_Q(\omega)} \right|^2 = |1 - e^{-j\omega T_s}|^2 = 2 - 2\cos(\omega T_s)$$

# Introduction


## Noise Shaping: Analysis

- Noise shaping helps to improve the achievable SNR furthermore.
- Noise power can be calculated by:

$$\frac{V_{\text{LSB}}^2}{12} \frac{\pi^2}{3\text{OSR}^3}$$

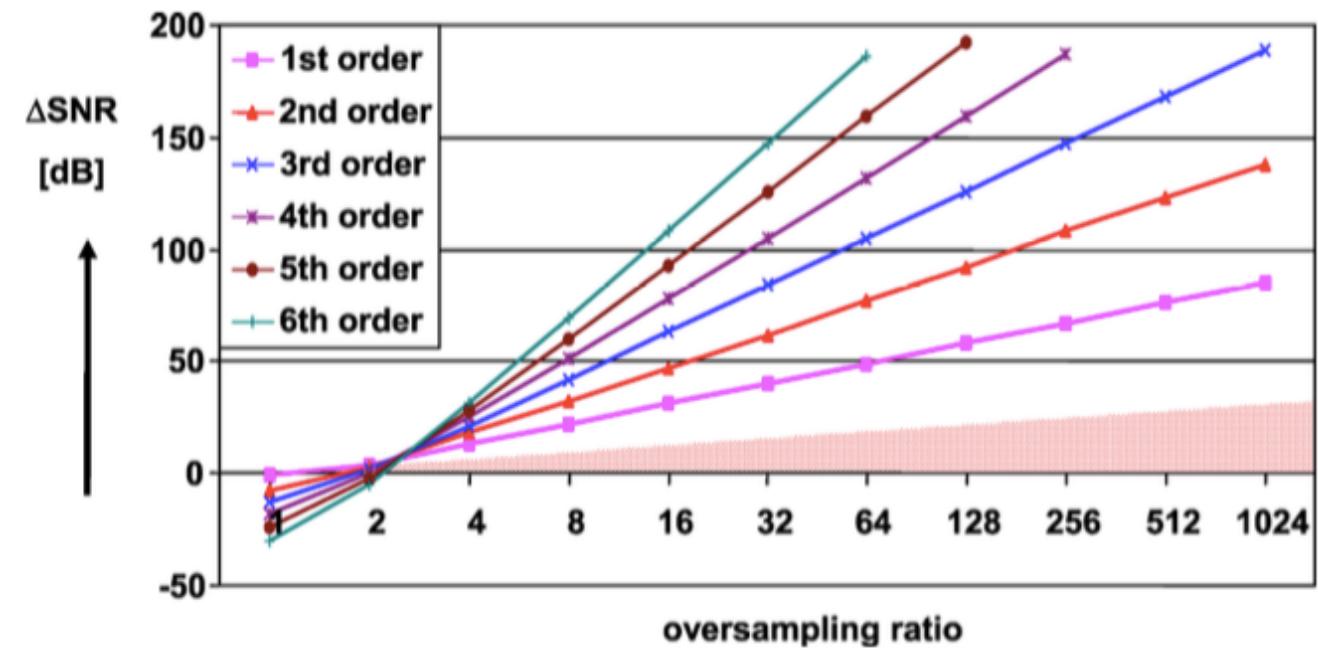
# Introduction Noise Shaping

- Higher order noise shaping can be achieved using higher order filters.


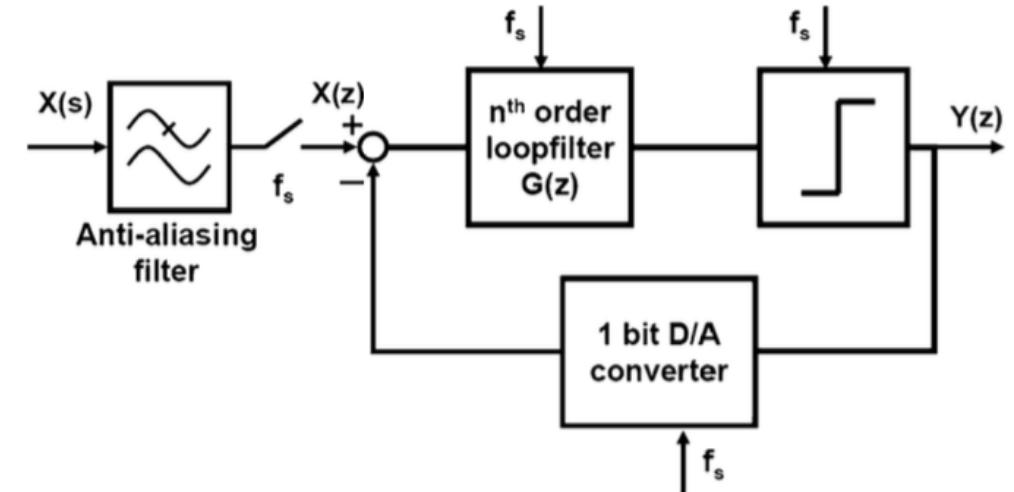
# Introduction Noise Shaping

- Further noise shaping using higher-order filter in the loop.
- This example shows a single-loop including a high-order filter
- The resolution of ADC used inside the loop can be as low as 1b.



$$Y(\omega) = X(\omega) + (1 - e^{-j\omega T_s})^n Q(\omega)$$

$$\left(\frac{V_{\text{LSB}}^2}{12}\right) \times \left(\frac{1}{\text{OSR}}\right) \times \left(\frac{\pi^{2n}}{(2n+1)\text{OSR}^{2n}}\right)$$

# Introduction Noise Shaping

## Overall Quantization Noise of a SDM

Quantization  
Noise of the  
in-loop ADC



$$\left( \frac{V_{\text{LSB}}^2}{12} \right) \times \left( \frac{1}{\text{OSR}} \right) \times \left( \frac{\pi^{2n}}{(2n+1)\text{OSR}^{2n}} \right)$$

Quantization Noise  
improvement due to  
OSR

Quantization Noise  
filtering effect thanks  
to SDM

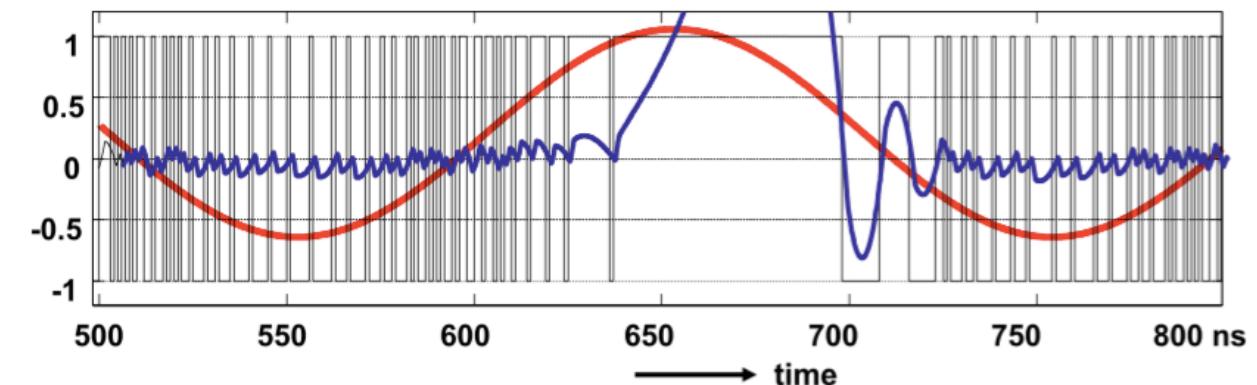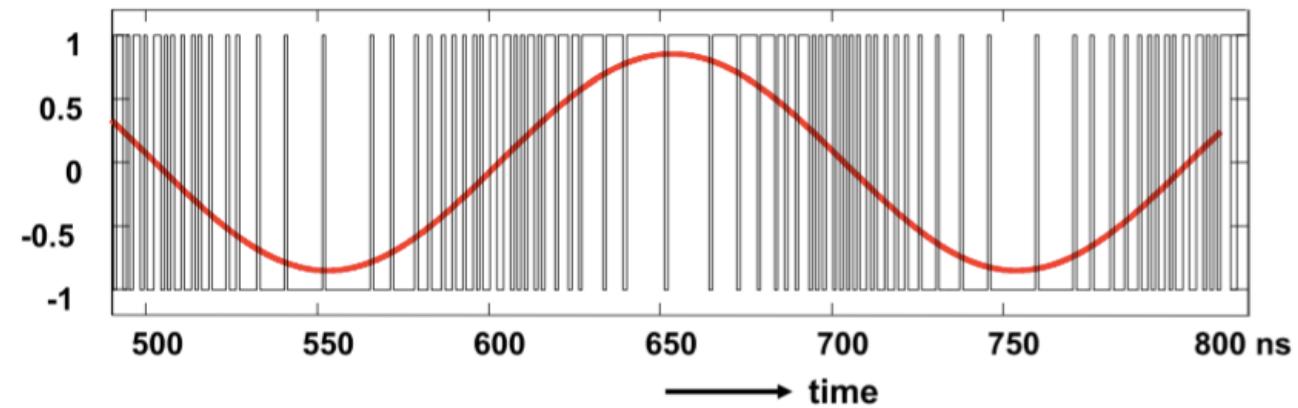
# Introduction Noise Shaping

- Time domain waveform:
  - Top plot shows the output of a SDM system.
  - Red: input sine wave
  - Gray: output of SDM
- When the input signal is out of the expected signal range, it causes instability, saturation.
  - Also it takes a bit of time to comeback to the normal mode of operation




# Introduction Noise Shaping

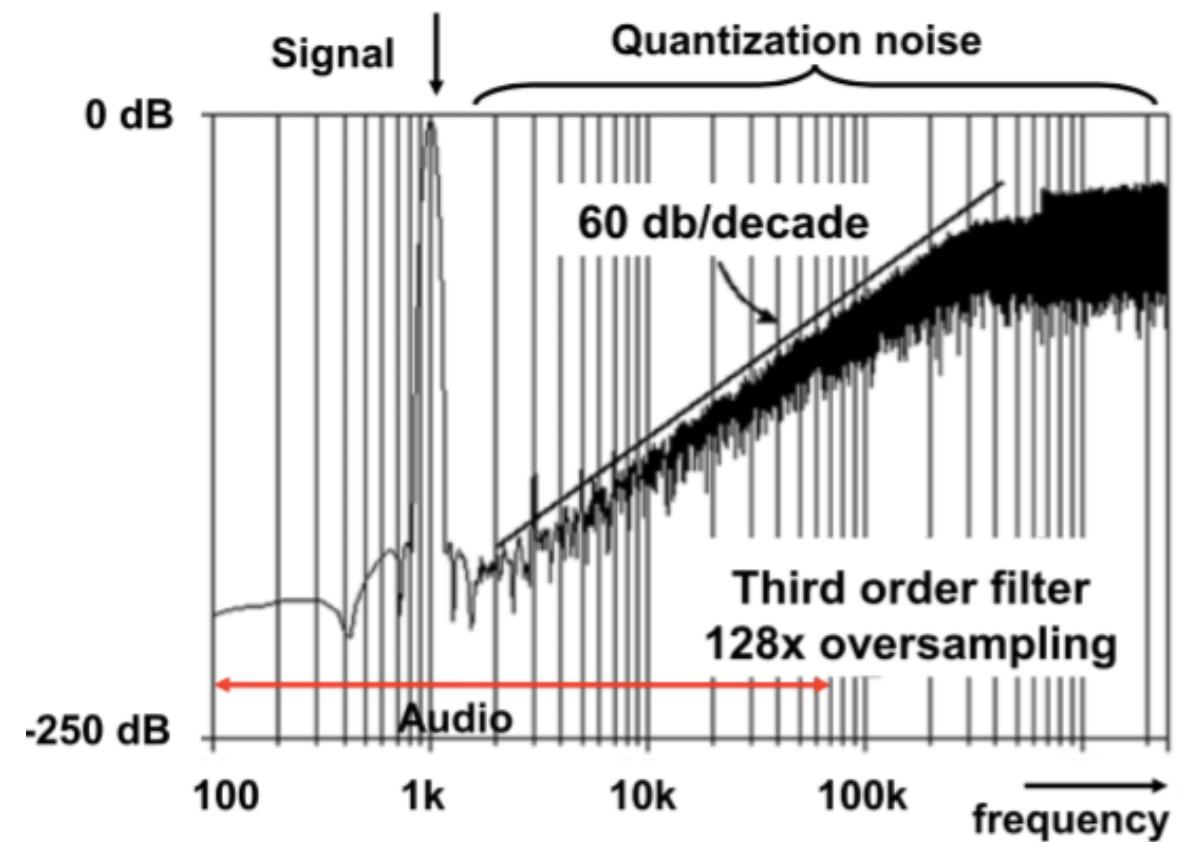- **Example:** a 3rd order filter has been used to enhance the noise filtering.
  - Signal is at 1 kHz
  - Noise shaping shows a third order transfer function (60 dB/dec).
  - Oversampling ratio (OSR) = 128


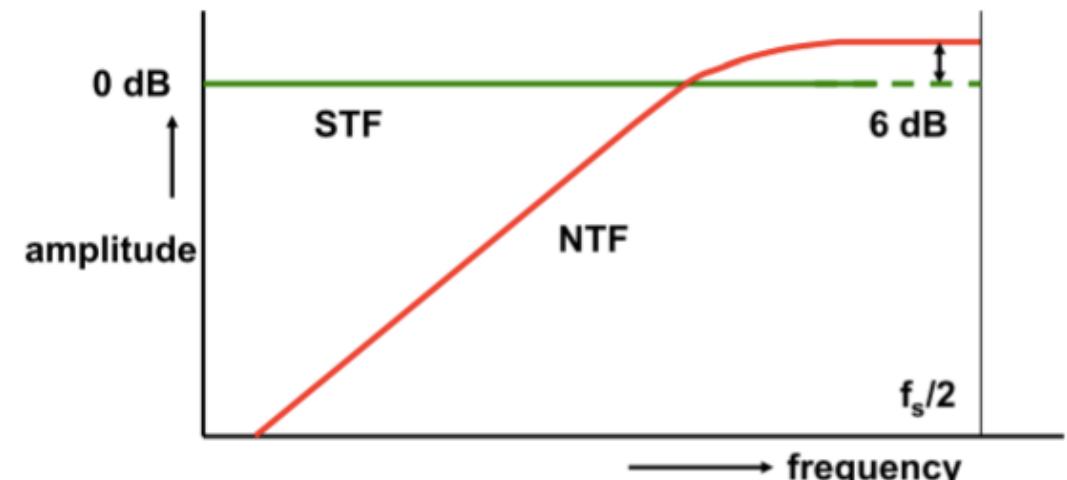
# Introduction Noise Shaping

- In a SDM structure, the NTF and the STF are different (noise and signal transfer functions):
  - STF is preferably an all-pass signal
  - NTF generally has a high pass transfer function.





$$Y(\omega) = \text{STF}(\omega)X(\omega) + \text{NTF}(\omega)N_Q(\omega)$$

$$\text{STF}(\omega) = \frac{cG(\omega)}{1 + cG(\omega)}$$
$$\text{NTF}(\omega) = \frac{1}{1 + cG(\omega)}$$

# Implementation

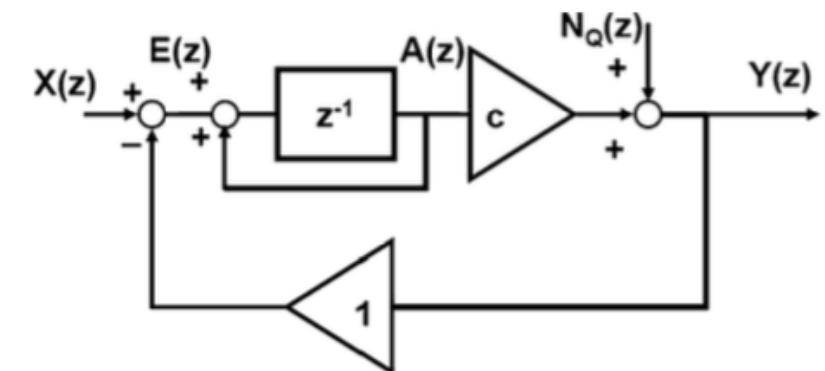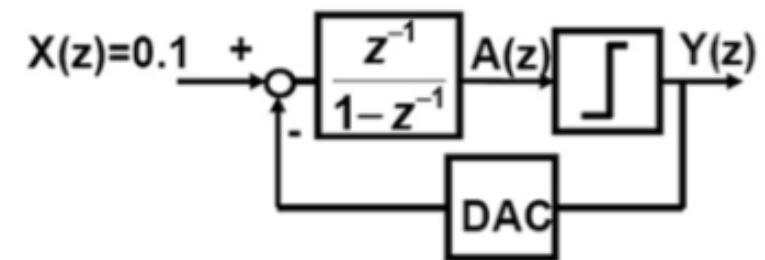
# Implementation Switched-Cap Filter

- **SDM order:** 1st order
- **Type of filter:** discrete-time (e.g., switched cap)
- **Resolution of loop ADC:** 1b
- **Integrator transfer function:**
  - $H(z) = 1+z^{-1} = z^{-1}/(1-z^{-1})$
  - Sum up every input with the previous value (integrator)


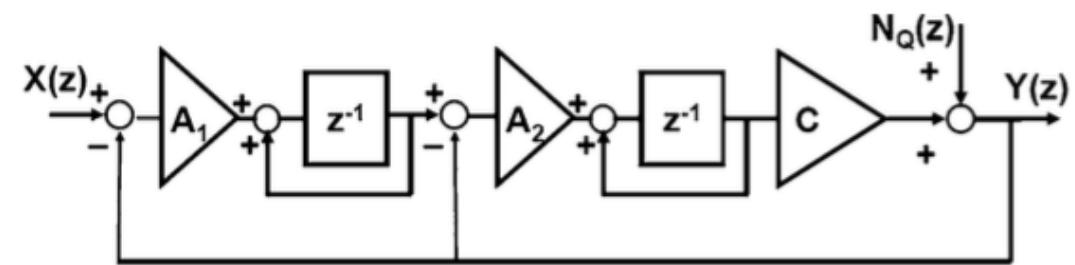
# Implementation Switched-Cap Filter


- SDM order: 2nd
  - STF =  $z^{-1}$  (an all-pass filter, with one unit delay).
  - NTF =  $(1-z^{-1})$ , which is a differentiator, or high-pass filter.





$$Y(z) = \underbrace{z^{-1}}_{\text{LPF}} X(z) + \underbrace{(1 - z^{-1})^2}_{\text{HPF}} E(z)$$
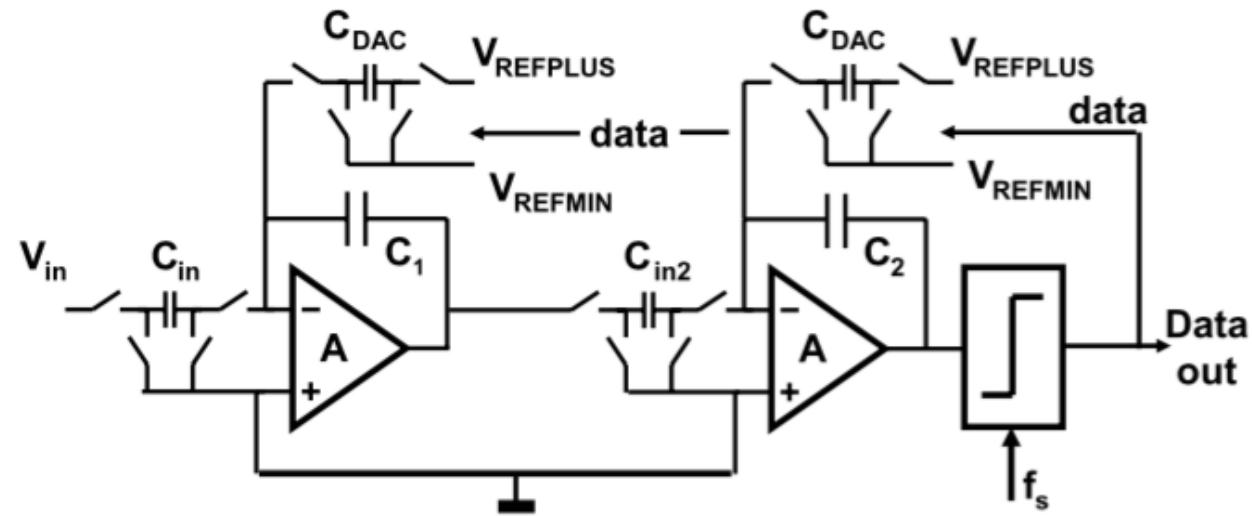
# Implementation Switched-Cap Filter

- Single-ended circuit diagram of a switched-cap SDM:
  - Generally a differential circuits are used
  - $C_1$  and  $C_2$ , combined with the amplifiers (A) implement the two integrators.
  - CDACs are used to implement the DAC.


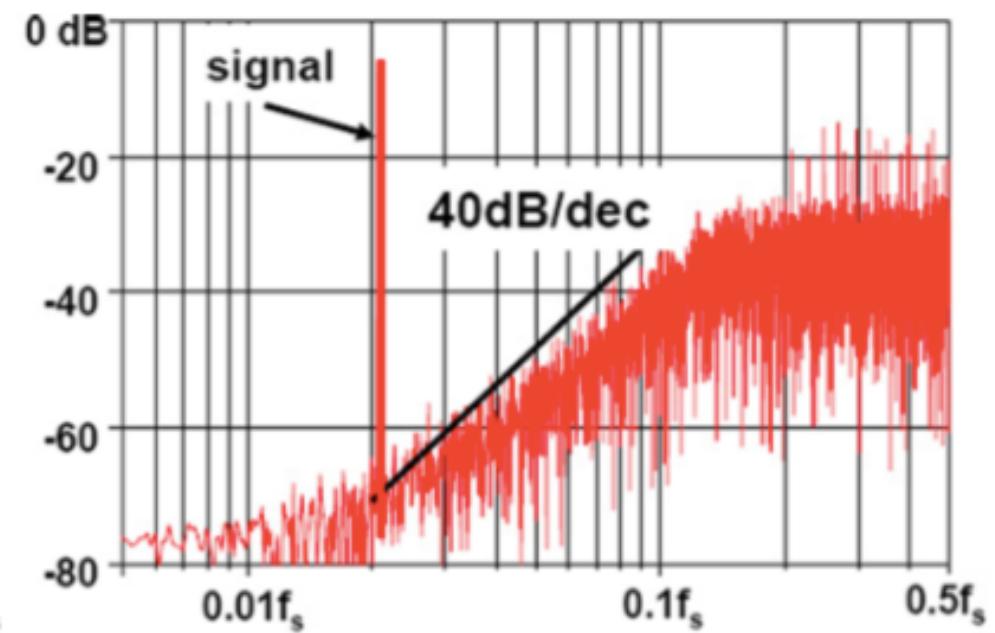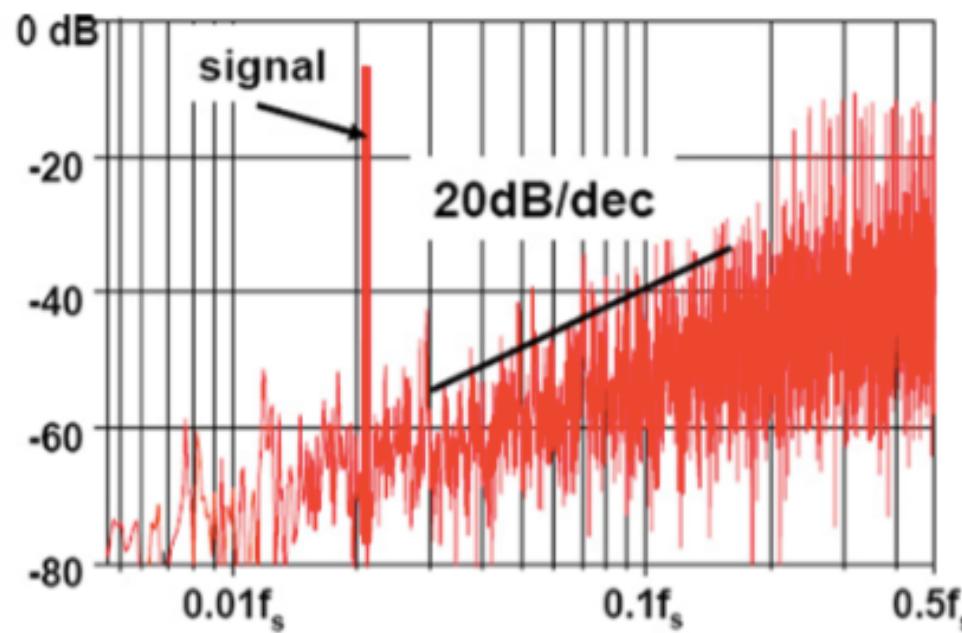
# Implementation Switched-Cap Filter: Response



- Frequency domain response of a 1st order and a 2nd order SDM.


# Non-Ideal Effects

# Non Idealities

- Circuit non-idealities degrade performance of the SD ADC.
- Examples are:
  - Bandwidth limitation
  - Slew rate
  - Circuit noise
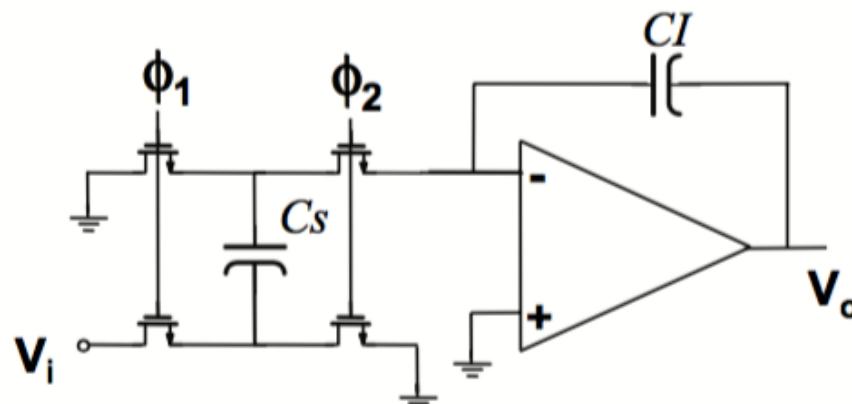
# Non Idealities Sampling Noise

- Sampling noise power of a switched-capacitor circuit is proportional to  $kT/C$ .
- Due to oversampling, the effective sampling noise will be  $M = OSR$  times smaller than  $kT/C$ , i.e.:  $kT/MC$ .



$$\overline{v_n^2} = \frac{2kT}{Cs}$$

$$\overline{v_n^2} / f = 2 \frac{kT}{Cs} \times \frac{1}{fs/2} = 4 \frac{kT}{Cs \times fs}$$



Total in-band noise:

$$\overline{v_n^2}_{input-referred} = 4 \frac{kT}{Cs \times fs} \times f_B$$

$$= \frac{2kT}{Cs \times M}$$

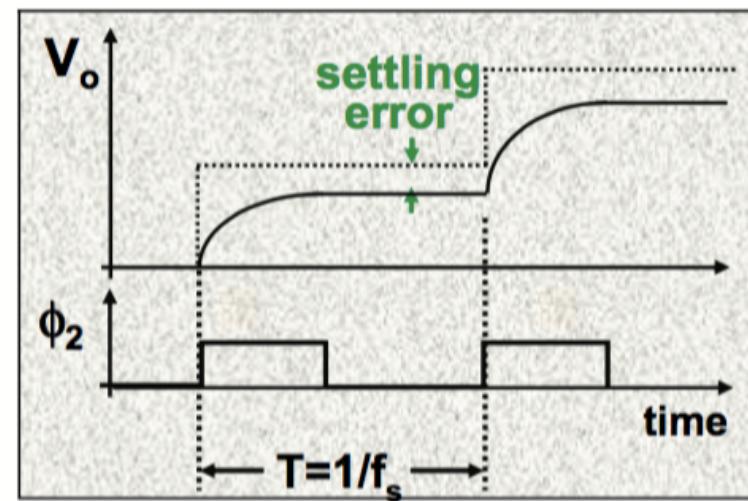
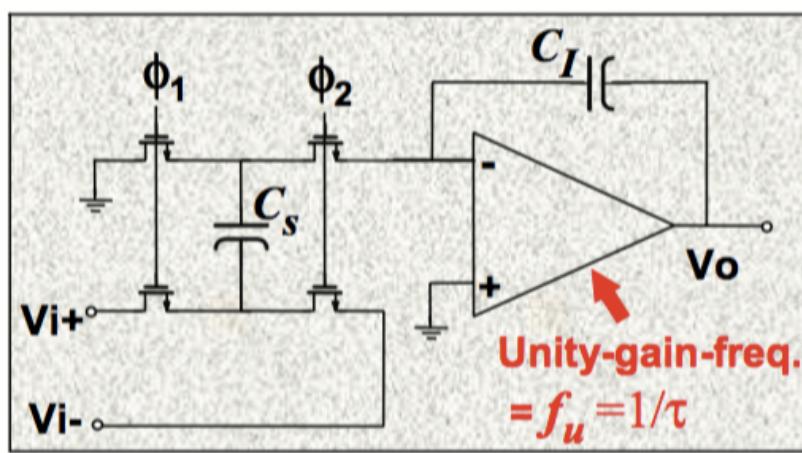
# Non Idealities Bandwidth

- In switched-cap circuits, generally, the GBW of amplifiers need to be at least 5x more than the switching frequency.
- In SDM systems, the amplifier GBW generally needs to be only two times more than the sampling clock frequency.
  - This is mainly because of noise and error shaping of the SDM loop.



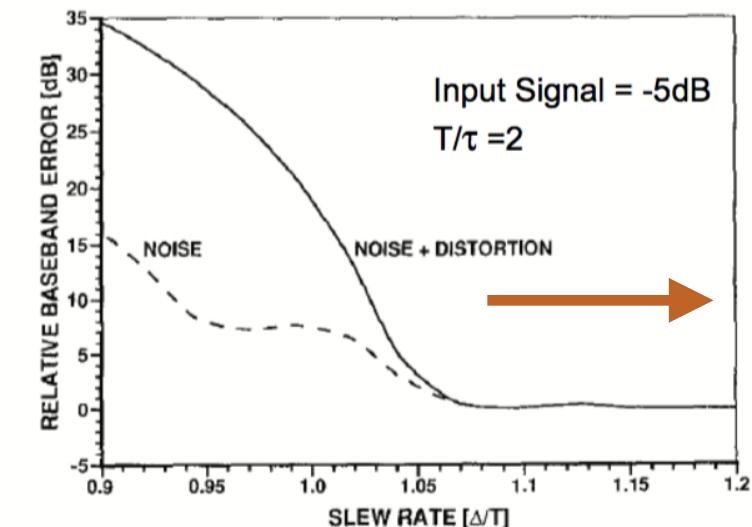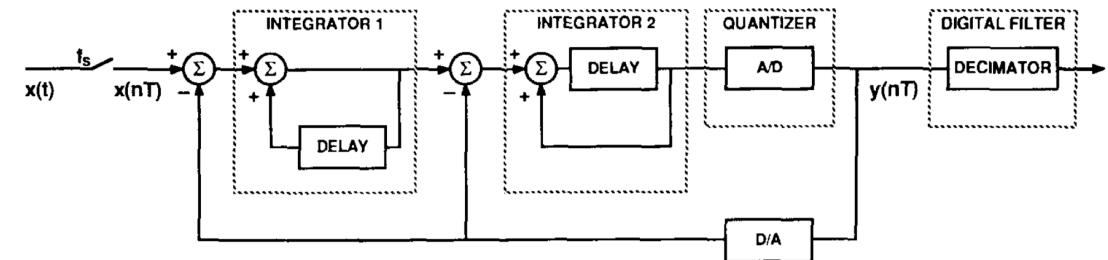
# Non Idealities Slew Rate

- Slew rate of amplifier adds some more error to the system.
- **Example:** in a 2nd order SDM, the amplifier SR (slew rate) needs to be 10% more than quantization noise, times the sampling frequency.


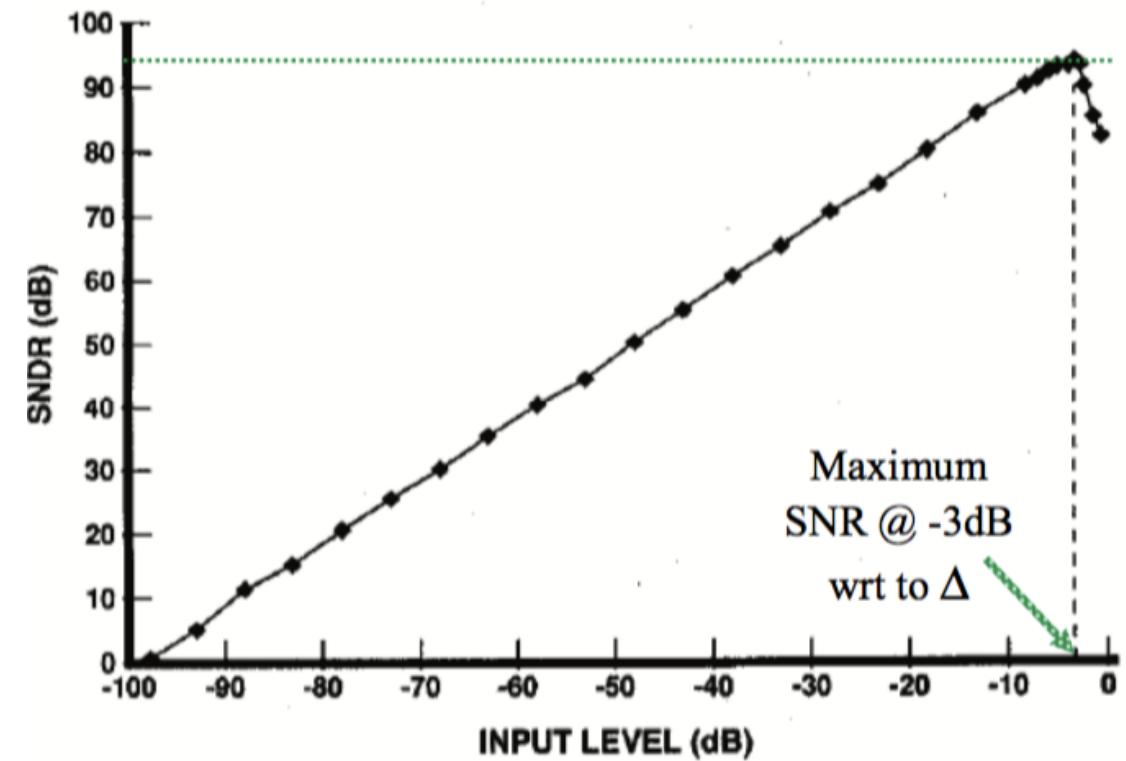
# Non Idealities Voltage Swing

- The input full range for a SDM circuit is generally limited.
- For example, a 0dB input will cause saturation and even instability.
- The acceptable input full range is generally 3dB lower than the reference voltage level.




# More Complex Topologies

Cascade and Mesh Topologies

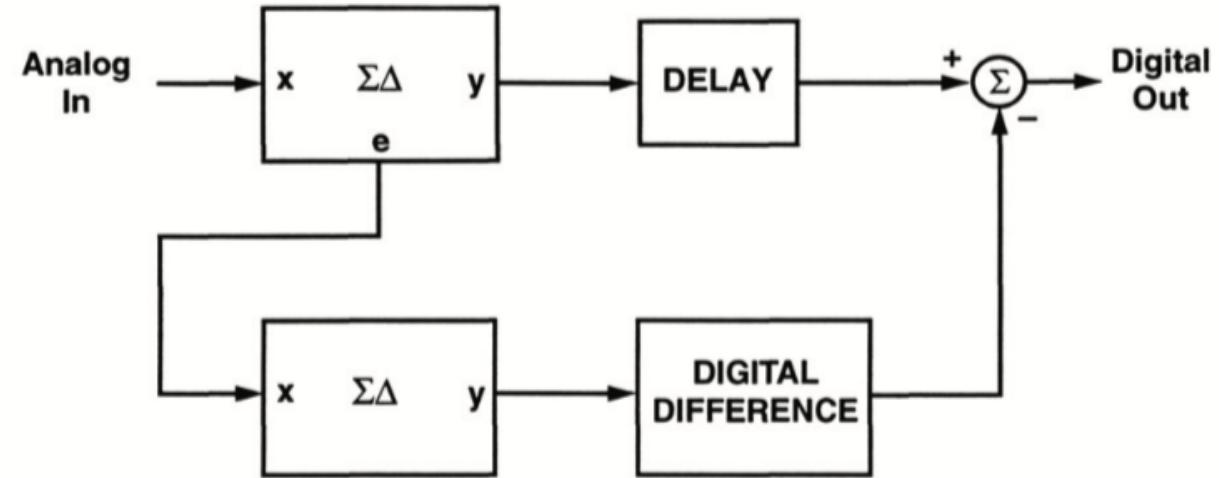
# Cascade Architecture

- Generally, it is very difficult to stabilize higher order modulators ( $n > 3$ )
- In order to further suppress the low-frequency quantization noise is to use cascade topologies.
- **Example:** 1-1 cascade structure.


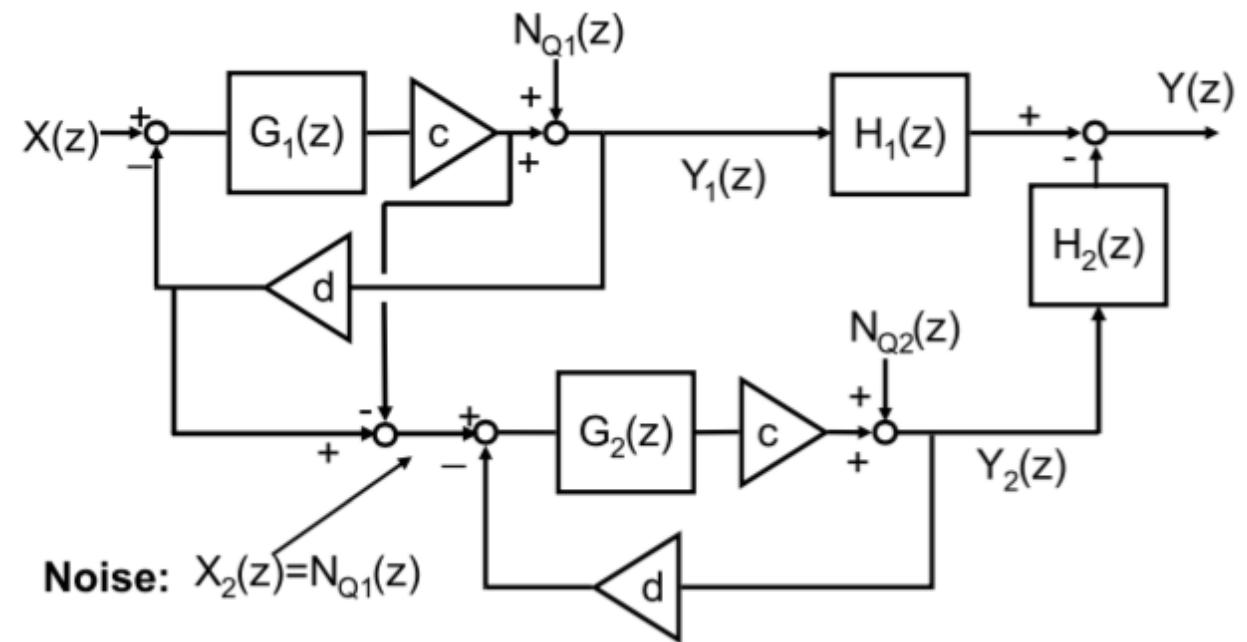
# Cascade Architecture

- Detailed block diagram of a 1-1 cascade architecture.



# Cascade Architecture Analysis

$$Y_1(z) = \frac{G_1(z)}{1+G_1(z)}X(z) + \frac{1}{1+G_1(z)}N_{Q1}(z)$$

$$Y_2(z) = \frac{G_2(z)}{1+G_2(z)}N_{Q1}(z) + \frac{1}{1+G_2(z)}N_{Q2}(z)$$

$$Y(z) = \frac{H_1(z)G_1(z)}{1+G_1(z)}X(z) + \left( \frac{H_1(z)}{1+G_1(z)} - \frac{H_2(z)G_2(z)}{1+G_2(z)} \right)N_{Q1}(z) - \frac{H_2(z)}{1+G_2(z)}N_{Q2}(z)$$

$$H_2(z)G_1(z) = H_1(z) = z^{-k}$$

$$Y(z) = X(z) + \frac{1}{G_1(z)G_2(z)}N_{Q2}(z)$$

Step 1:

Find the system transfer function

Step 2:

STF should be all pass (with some delay)

Step 3:

NTF should be high-pass

# Cascade Architecture Example 1-1

$$Y_1(z) = z^{-1}X(z) + (1 - z^{-1})E_1(z)$$


$$Y_2(z) = z^{-1}E_1(z) + (1 - z^{-1})E_2(z)$$

$$Y(z) = z^{-1}Y_1(z) - (1 - z^{-1})Y_2(z)$$

$$= z^{-2}X(z) + z^{-1}(1 - z^{-1})E_1(z) - z^{-1}(1 - z^{-1})E_1(z) \\ - (1 - z^{-1})^2E_2(z)$$

$$Y(z) = z^{-2}X(z) - (1 - z^{-1})^2E_2(z)$$


2<sup>nd</sup> order noise shaping

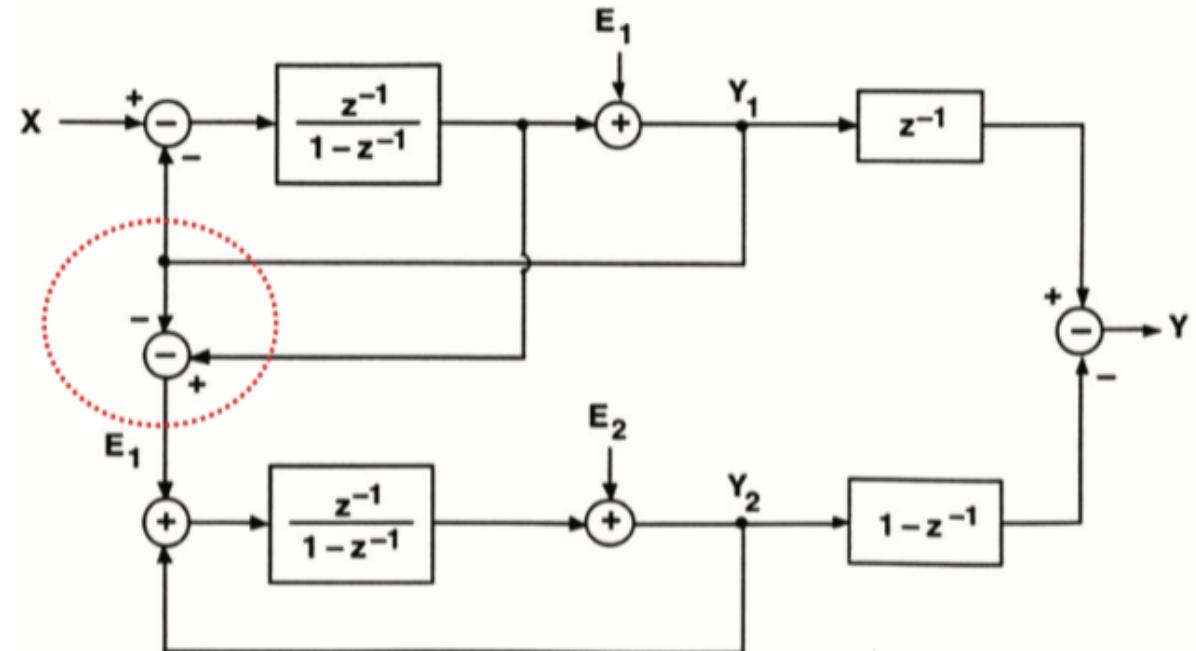

# Cascade Architecture

## Cascade 1-1-1

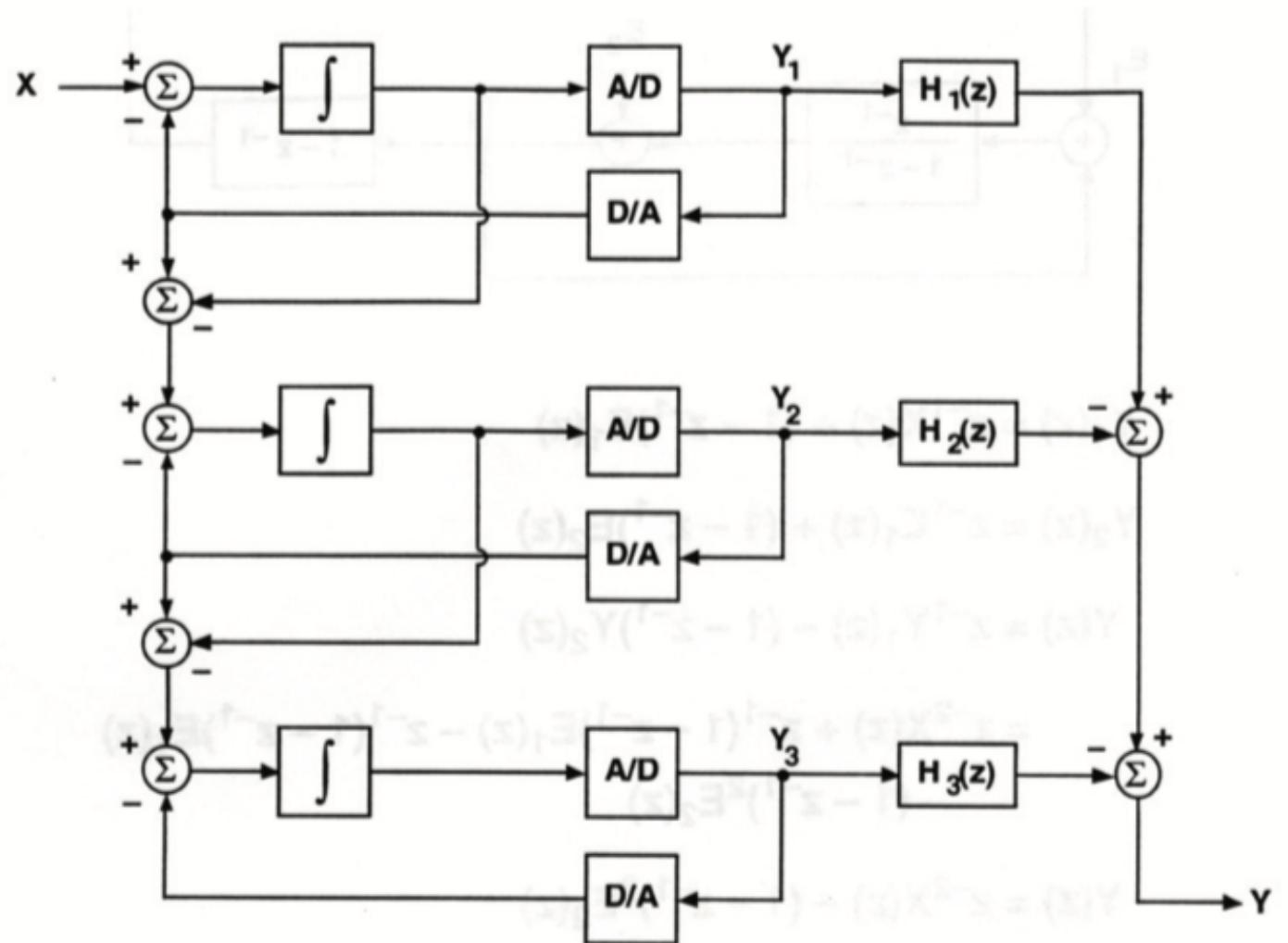- Example: cascade 1-1-1
- STF/NTF: third order (60 dB/dec)



# Cascade Architecture

## Cascade 2-1


$$Y_1(z) = z^{-2}X(z) + (1 - z^{-1})^2E_1(z)$$

$$Y_2(z) = z^{-1}E_1(z) + (1 - z^{-1})E_2(z)$$

$$Y(z) = z^{-1}Y_1(z) - (1 - z^{-1})^2Y_2(z)$$


$$\begin{aligned} &= z^{-3}X(z) + z^{-1}(1 - z^{-1})^2E_1(z) - z^{-1}(1 - z^{-1})^2E_1(z) \\ &\quad - (1 - z^{-1})^3E_2(z) \end{aligned}$$
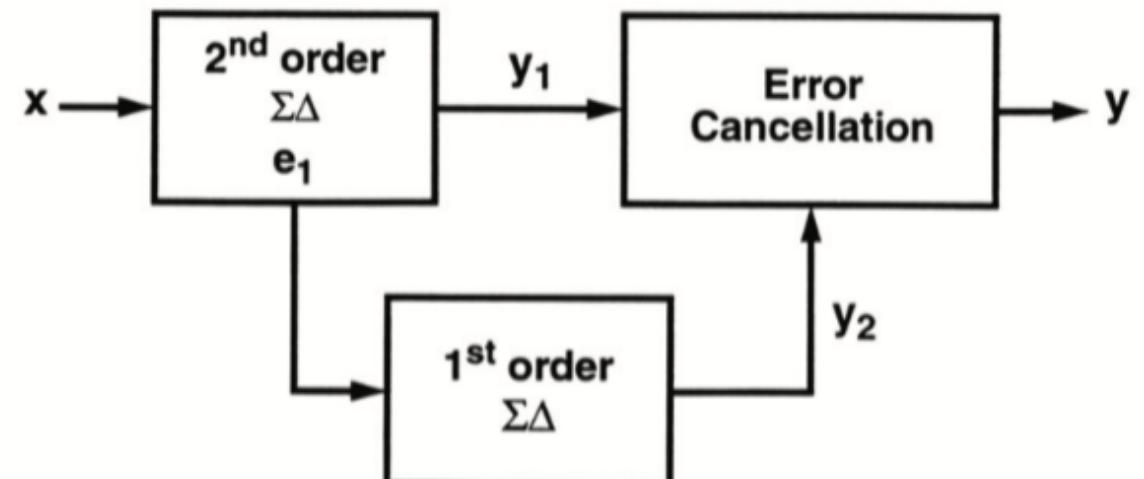
$$Y(z) = z^{-3}X(z) - (1 - z^{-1})^3E_2(z)$$



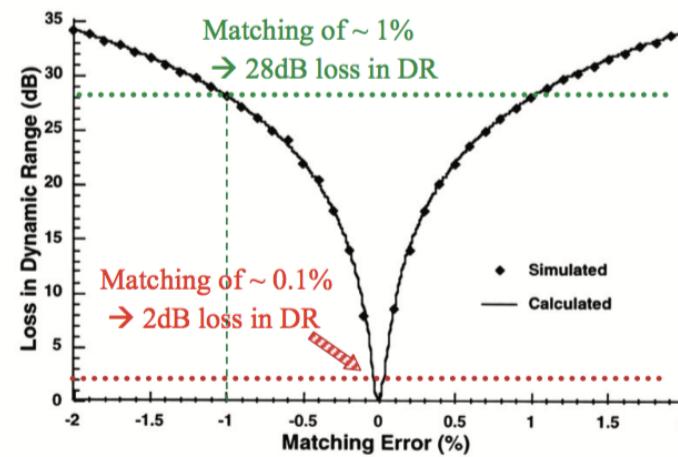
# Cascade Architecture Robustness

Sensitivity of Cascade of (1-1-1)  $\Sigma\Delta$  Modulators to Matching of Analog & Digital Paths





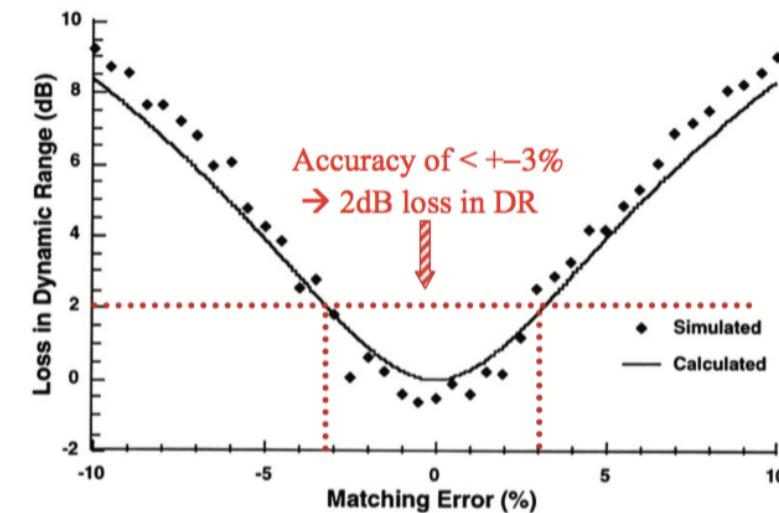Sensitivity of Cascade of (2-1)  $\Sigma\Delta$  Modulators to Matching Error


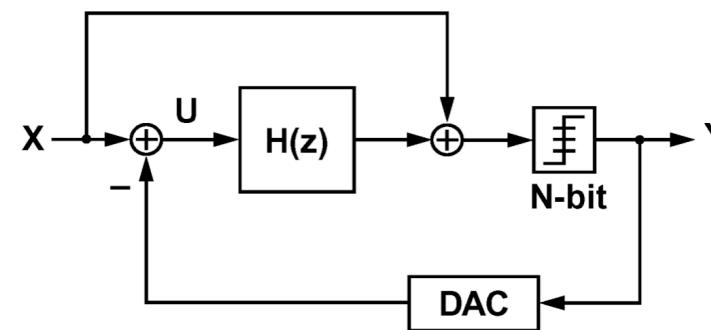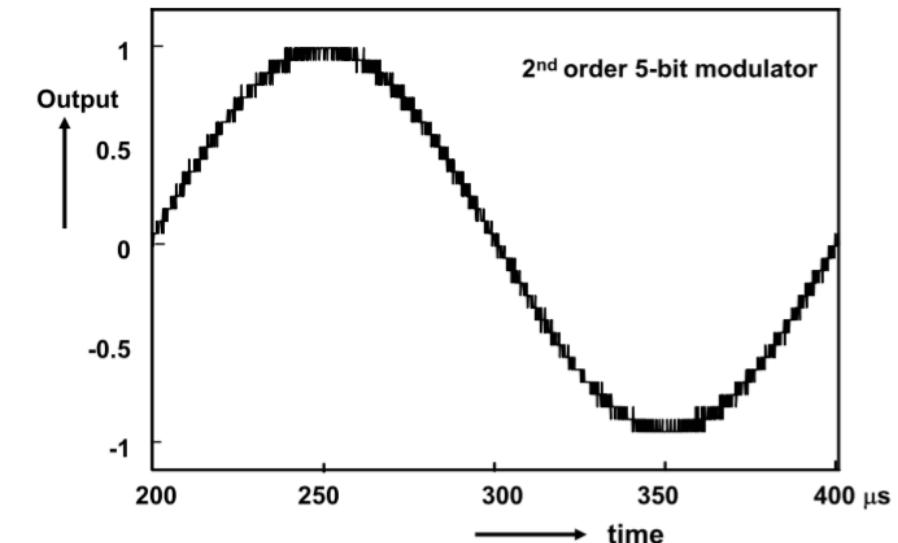
# High Resolution ADC/DAC


- The other possibility to increase the overall SDM resolution is to employ loop ADC/DAC with more than 1b resolution.



Resolution	$\Delta$ SNR
$1 \rightarrow 2$	7.0 dB
$2 \rightarrow 3$	6.2 dB
$3 \rightarrow 4$	6.1 dB
$4 \rightarrow 5$ , etc.	6.0 dB
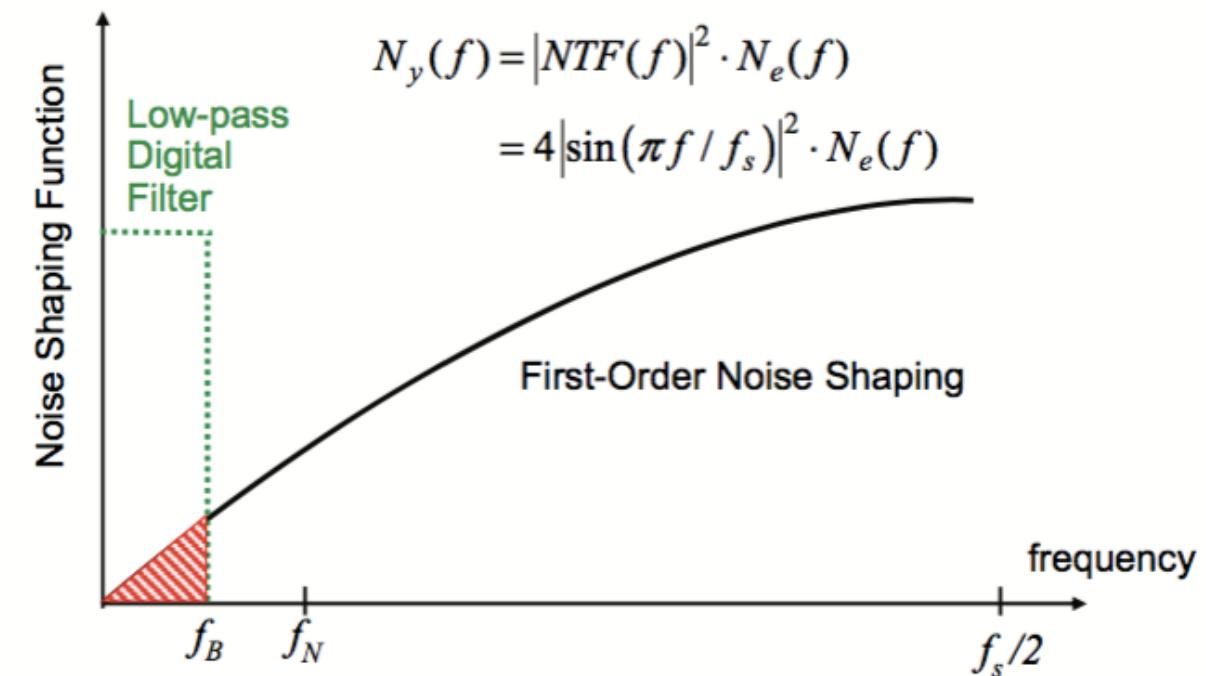
# Decimation Filter

- How the noise bandwidth can be limited ?
- If no limitation, then noise should be integrated from DC to half the sampling frequency
- **Solution:** use digital low-pass filter
- In addition to rejecting the high frequency noise, the digital filter will reduce the rate of data (decimation filter)



# Summary

# Summary

- SD architecture is based on noise shaping and oversampling.
- SD ADCs are very popular in applications such as audio systems, wireless transceivers, and sensor interface.
- The energy-efficiency of SD ADCs is not as good as SAR architecture, however they offer much higher resolution.
- There are continuous-time and discrete-time SD implementations, the former is mostly being used in wireless applications, where speed is important, while the latter is used in sensor interfaces and audio.
- Mesh and cascade SD architectures can be utilized to enhance the resolution of the ADC.

# References

## References |

- [1] B. Boser, and Bruce A. Wooley, “The design of sigma-delta modulation analog-to-digital converters,” IEEE JSSC, 1988.
- [2] B. P. Brandt, B. A. Wooley, “A 50-MHz multibit sigma-delta modulator for 12-b 2-MHz A/D conversion,” IEEE JSSC 1991.
- [3] A. Tabatabaei, B. A. Wooley, “A two-path bandpass sigma-delta modulator with extended noise shaping,” IEEE JSSC 2002.
- [4] R. Schreiner and G. C. Temes, Understanding delta-sigma data converters, Wiley 2005.