

**Note:** For students connecting virtually, the details of the Zoom Meeting for this TP session are given below

**Topic:** Advanced Analog IC Design Zoom Meeting

**Time:** March 14, 2025 01:00 PM Amsterdam, Berlin, Rome, Stockholm, Vienna

**Join Zoom Meeting:**

<https://epfl.zoom.us/j/66887254608?pwd=MBLOAjyTb7PaR02tNUeDaHDb1q5WID.1>

**Meeting ID:** 668 8725 4608

**Passcode:** 191600

### Objectives of this Practical Exercise Session

1. Design and simulate a cascode op amp:
  - a) Following the design procedures, design a cascode op amp that meets the given set of specifications.
  - b) Perform DC Analysis for DC operating point.
  - c) Perform AC Analysis for frequency response.
  - d) Perform Transient Analysis with the unity-gain buffer configuration.
2. Design and simulate a two-stage op amp:
  - a) Following the design procedures, design a two-stage op amp that meets the given set of specifications.
  - b) Perform DC Analysis for DC operating point.
  - c) Perform AC Analysis for frequency response.
  - d) Perform Transient Analysis for output swing observation

**TIP OF THE DAY:** Save your work frequently




## 1. Design and Simulate a Cascode op amp

## Design Specification

- DC Gain ( $A_V$ ) > 65 dB  $\approx$  1800 V/V
- Unity Gain Bandwidth (UGB) > 20MHz
- Output Load Capacitance ( $C_L$ ) = 2pF
- $V_{OUT, DC} \approx 1.15$  V
- $V_{IN, DC} = 0.9$  V
- $V_{DD} = 1.8$  V

## Hand Calculation

 

**Fig. 1. Schematic of the Cascode op amp**

The circuit schematic is shown in Fig. 1. For simplicity, please connect the body terminals of transistors to their source terminals. We also suggest to group M0-M1, M2-M5, as well as M6-M9. Transistors in the same group have the same Finger Width, Length, and Finger Number (Note that the current mirror M0 and M1 have Finger Number of 1 and FTAIL, respectively), as shown in Fig. 1



Work out the sizes for each transistor, and the biasing current/voltages by writing out the square-law equations or if you are familiar with any of the design methodologies like  $gm/ID$  or Inversion Coefficient (IC), please feel free to use them.

For hand calculations,  $\mu_n C_{ox} = 278 \mu\text{A/V}^2$ ,  $V_{TH, N} = 0.4 \text{ V}$ ,  $\mu p C_{ox} = 61 \mu\text{A/V}^2$ ,  $|V_{TH, P}| = 0.54 \text{ V}$ .

Overall, we have the following parameters to achieve the required specifications. Here  $I_x$  denotes the current,  $L_x$  the channel length,  $W_x$  the width,  $F_x$  the number of fingers,  $V_{b1}$  and  $V_{b2}$  the biasing voltages.

We use  $g_m/I_D$  methodology to determine the sizing of transistors. Based on the specifications, we have:

$$UGB = \frac{g_{mn}}{2\pi C_L} > 20 \text{ MHz} \rightarrow g_{mn} > 251.2 \text{ } \mu\text{S} \quad (1)$$

$$A_v = g_{mn}(g_{mn}r_{oN}^2 // g_{mp}r_{oP}^2) \approx \frac{1}{2}g_{mn}^2r_{oN}^2 > 1800 \Rightarrow g_{mn}r_{oN} > 60 \text{ (assume } g_{mn}r_{oN}^2 \approx g_{mp}r_{oP}^2\text{)} \quad (2)$$

$$V_{ov6} = V_{OUT,DC} - V_{DD} - V_{TH,P} = 1.15 - 1.80 - (-0.54) = -0.11 \text{ V} \quad (3)$$

The first step is to choose the length of transistor. We plot the  $g_{mn}r_{ON}$  as a function of  $V_{ov}$  for different values of  $L_n$ , as shown in Fig. 2. Considering some margins (65~75 for  $g_{mn}r_{ON}$ ) and moderate inversion operations ( **$g_m/I_D$  in the range of 12-16, and  $V_{ov} \sim 0.1$  V for the amplifying transistors in this technology**),  $L_n = 720$  nm was chosen for our initial trial.

 


Fig. 2.  $g_m r_{on}$  as a function of  $V_{ov}$  under different  $L_n$

In the Excel sheet of  $L_n = 720 \text{ nm}$ , we identify the following point, where  $g_{mro} = 72.2$ ,  $g_m/I_D = 13.7$ , and  $V_{ov} \approx 0.1 \text{ V}$ . That seems a nice point to start with.

1	L	720nm	Vov	720nm	gm	720nm	ID	720nm	gm	ID	720nm	gm	720nm	ID/W	720nm	gm	W	720nm	rgm	Cgg	720n	1/(ID,ro)	720nm	VDSAT	720nm	W	720nm	rrro	720nm	Cgg	720nm	mgds	720nm
30	7.20E-07	1.01E-01	3.91E-05	2.85E-06	1.37E+01	7.22E+01	2.85E+00	3.91E+01	7.73E-09	1.90E-01	1.22E-01	1.00E-06	1.85E+06	5.06E-15	5.41E-07																		

Let's further calculate the required  $I_D$  and tail current  $I_{TAIL}$ . According to the identified  $g_m/I_D$  and (1), we have:  $I_D > 251.2/13.7 = 18.3 \mu\text{A}$  (rounding up to  $19 \mu\text{A}$ ),  $I_{TAIL} = 2 * I_D = 38 \mu\text{A}$ . How about the width? Since  $I_D/W = 2.85$ , the total width of NMOS is derived as  $19/2.85 = 6.7 \mu\text{m}$  ( $W_n = 1\mu\text{m}$ ,  $F_n = 7$ ).

Now we move to the sizing of PMOS transistors.  $L_p = 360 \text{ nm}$  is chosen because it generally provides higher  $g_m r_o$  (up to 100+). According to (3), we identify the following point in the Excel sheet of  $L_p = 360 \text{ nm}$ , where  $V_{ov} \approx -0.11 \text{ V}$ ,  $g_m/I_D = 12.7$ . Since  $I_D/W = 1.55$ , the total width of PMOS is derived as  $19/1.55 = 12.3 \mu\text{m}$  ( $W_p = 1 \mu\text{m}$ ,  $F_p = 12$ ).

1 L 360nm Vov 360nm gm 360nm ID 360nm gm/ID 360nm gmro 360nm ID/W 360nm gm/W 360nm Cgg 360nm 1/(ID.ro) 360nm VDSAT 360nm W 360nm ro 360nm Cgg 360nm gds 360nm  
17 3.60E-07 -1.05E-01 1.97E-05 1.55E-06 1.27E+01 9.82E+01 1.55E+00 1.97E+01 7.73E+00 1.29E-01 1.46E-01 1.00E-06 1.99E+06 2.54E-15 2.00E-07

As for the current mirror transistors M0-M1, the length could be the same as  $L_n$ , while we choose  $W_{TAIL}$  based on the  $V_{ov}$ . Typically, for current mirror, the  $g_m/I_D$  does not need to be high for reduced noise, which limits  $V_{ov}$  to be a bit less than 300 mV. We identify the following point, where  $V_{ov} \approx 0.29$  V and  $g_m/I_D = 6.1$ .  $I_{TAIL}/W = 16.5$ . Therefore, the total width of the tail transistor is derived as  $38/16.5 = 2.3 \mu\text{m}$  ( $W_{TAIL} = 1 \mu\text{m}$ ,  $F_{TAIL} = 2$ ), and  $I_{BIAS} = I_{TAIL}/F_{TAIL} = 19 \mu\text{A}$ .

1 L 720nm Vov 720nm gm 720nm ID 720nm gmro 720nm ID/W 720nm gm/Cgg 720nm 1/(ID,ro) 720nm VDSAT 720nm W 720nm ro 720nm Cgg 720nm gds 720nm  
166 7.20E-07 2.92E-01 1.00E-04 1.65E-05 6.09E+00 5.92E+01 1.65E+01 1.00E+02 1.95E+10 1.03E-01 2.58E-01 1.00E-06 5.91E+05 5.13E-15 1.69E-06

There are allowable ranges for the biasing voltage  $V_{b1}$  and  $V_{b2}$ . In this case,  $V_{ov1} + V_{ov3} + V_{ov5} + V_{THN} < V_{b1} < V_{OUT,DC} + V_{THN} \rightarrow 0.9 \text{ V} < V_{b1} < 1.55 \text{ V}$ , and  $V_{OUT,DC} - |V_{THP}| < V_{b2} < V_{DD} - |V_{ov6}| - |V_{ov8}| - |V_{THP}| \rightarrow 0.61 \text{ V} < V_{b2} < 1.04 \text{ V}$ . We may set  $V_{b1} = 1.2 \text{ V}$  and  $V_{b2} = 0.8 \text{ V}$  for our first trial. With DC analysis, we can revisit the biasing voltages to ensure similar  $V_{DS}$  across the cascode transistors, which helps maximize the gain.



$I_{BIAS}$	$L_{TAIL}$	$W_{TAIL}$	$F_{TAIL}$	$L_n$	$W_n$	$F_n$	$L_p$	$W_p$	$F_p$	$V_{b1}$	$V_{b2}$
19 $\mu\text{A}$	720 nm	1 $\mu\text{m}$	2	720 nm	1 $\mu\text{m}$	7	360 nm	1 $\mu\text{m}$	12	1.2	0.8

## Building the Schematic

The way of building the schematic is the same as the FIVE\_PACK\_OTA example demonstrated in TP1. Here are a few points to help you quickly create the schematic shown in Fig. 1.

- Create new cellview in the library manager and select “Schematic”.
- Choose “N\_18\_MM” and “P\_18\_MM” in the UMC\_18\_CMOS library for transistors.
- Choose “vsin” in the analogLib library for vip/vin input sources. The DC voltage should be 900 mV.
- Press “i” to add instances.
- Press “q” to bring the “Properties” dialogue.
- Press “w” for wiring connection of all components.
- Press “l” (the lowercase L) to label the nets.
- Press “Shift+x” to check and save your schematic.

## DC Operating Point using DC Analysis

The way of creating the simulation window is the same as the FIVE\_PACK\_OTA example demonstrated in TP1. Here are a few points to help you start the simulation.

- On your schematic window, click **Launch>ADE Explorer**. Select **Create New View**. Keep the View as **maestro**, select **Open in new tab**, and press OK.
- Click on “**Click to add analysis**”. Choose dc analysis, and don’t forget to check the “**Save DC Operating Point**” box.



- Below the Design Variables, click on Click to add variable. Select “**Copy from Cellview**”. Then fill in the variables derived from the hand calculation above.
- Click on the **green play button** (▶) to run the simulation.

After running the simulation, click **Results>Annotate>DC node voltages / DC operating points**. This will annotate DC node voltages / DC operating points on your schematic. Check the voltage and currents. Make sure they are close to the desired values. You can also click **Results>Print>DC Operating point** to check the small-signal variables of each transistor.

 


Fig. 3. Annotation of DC node voltages / DC operating points



#### Verify the DC operating point for all the transistors in the design.

**Tip:** Here, we introduce a new way of saving the small signal variables by clicking **Outputs>Add>Expression**. Type the expressions listed in Fig. 4 so that you can quickly verify the small-signal variables (such as  $g_m$  and  $r_o$ ) and DC gain after each simulation run.

Name	Type	Details	Value	Plot	Save	Spec
gm3	expr	OP("M3" "gm")	255.8u	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
ro3	expr	OP("M3" "rout")	252.8K	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
gm5	expr	OP("M5" "gm")	255.5u	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
ro5	expr	OP("M5" "rout")	245K	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
gm8	expr	OP("M8" "gm")	227.1u	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
ro8	expr	OP("M8" "rout")	272.7K	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
gm6	expr	OP("M6" "gm")	226.6u	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
ro6	expr	OP("M6" "rout")	252.8K	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
rn	expr	(gm5 * ro5 * ro3)	15.83M	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
rp	expr	(gm8 * ro8 * ro6)	15.66M	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
gain	expr	((gm3 * rn * rp) / (rn + rp))	2.013K	<input checked="" type="checkbox"/>	<input type="checkbox"/>	

Fig. 4. Expressions of small-signal variables and DC-gain calculation

## Frequency Response using AC Analysis

In order to verify the Unity Gain Bandwidth (UGB) specification, we perform the AC analysis. Similar to TP1, we click on “**Click to add analysis**”, choose ac, and setup the form as shown in Fig. 5.

 


Fig. 5. AC Analysis setup

**Tip:** To view the simulation results, as introduced in TP1, click **Results>Direct Plot>Main Form** and select **vout** in your schematic. You can also use **Outputs>Add>Expression** and type the expression as follows, which will plot the AC magnitude (in dB) frequency response after each simulation run, as shown in Fig. 6.

expr db(vfreq('ac "/vout"))

**Tip:** To create the marker as shown in Fig. 6, press “m”, and move the marker to where you want. To identify the UGB point, double click the marker, choose “by YMode” and type “0 dB” in the “Position”, so that the frequency point with 0 dB magnitude (UGB) is identified.



 


Fig. 6. Frequency response of  $v_{out}$  AC magnitude



Verify if the DC gain and UGB meet design specifications in the design. Little deviations from the required specifications are acceptable, as long as you understand how to fix it 😊

### Unity-gain buffer configuration with Transient Analysis

A high-gain op amp is commonly used as a unity-gain buffer. To do that, please short the  $v_{out}$  and  $v_{in}$  terminals, as shown in Fig. 7. However, as mentioned in Lecture-2-Slide page-6, it is difficult to use a cascode op amp as a unity-gain buffer due to the limited output swing. In our case,  $(V_{b1} - V_{TH,N}) < V_{OUT} < (V_{b1} - V_{ov5})$ ,  $V_{b1} = 1.3$  V, thereby  $0.9 \text{ V} < V_{OUT} < 1.2 \text{ V}$

To visually check it, we will perform a Transient Analysis. Click on “**Click to Add Analysis**” and fill in the transient simulation form as shown in Fig. 7. Also modify the swing of  $v_{ip}$  to a bit out of the boundary. For example, change the DC voltage as 1.1 V and Amplitude as 0.3 V, so that we get 0.8 ~ 1.4 V of  $v_{ip}$ .

 


Fig. 7. Transient Analysis setup and unity-gain buffer configuration

To plot the waveforms, select **Results>Direct Plot>Main Form**, and select “**Differential Nets**” and “**Net**” for plotting (**vip-vin**) and **vout**, respectively. Again, you can also click **Outputs>Add>Signal** to bring out the waveforms after each simulation run.

 


Fig. 8. Transient waveforms as a unity-gain buffer



It is not quite obvious to check if **vout** closely follows **vip** from the transient waveforms. You can perform DC simulation at  $V_{IN,DC} = 0.8$  V, 1.1 V, and 1.4 V, respectively, and check if the cascode transistors are all in the saturation region. An example is shown in Fig. 9.

expr	OP("M3" "region")	1	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
expr	OP("M5" "region")	2	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
expr	OP("M6" "region")	2	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
expr	OP("M8" "region")	1	<input checked="" type="checkbox"/>	<input type="checkbox"/>	

Fig. 9. M3 and M8 are in linear region when  $V_{IN,DC} = 1.4$  V (0: Cut-off region, 1: Linear region, 2: Saturation region).

## 2. Design and Simulate a Two-Stage op amp

### Design Specifications

- DC Gain ( $A_V$ )  $> 61$  dB  $\approx 1200$  V/V
- Output Load Capacitance ( $C_L$ ) = 2pF
- $V_{DD} = 1.8$  V
- $V_{IN, DC} = 1.0$  V
- Output Swing  $> 1.2$  V
- Unity Gain Bandwidth (UGB)  $> 20$ MHz

### Hand Calculation

The circuit schematic is shown in Fig. 10. For stability considerations, we put an additional compensation capacitance ( $C_c$ ) of 2 pF, which leads to  $UGB = g_{m3} / (2\pi C_c)$ . Besides, it is suggested that  $g_{m6} / C_L \approx 3$  \*

$g_{mn3} / C_c$  (also for stability). Since the topics of stability and frequency compensation are not covered in the lectures, feel free to check Chapter 10.2-10.3, 10.5 of Razavi, "Design of Analog CMOS Integrated Circuits" if you are interested. It is fine to simply use the conclusions above in this TP. 😊

 


Fig. 10. Schematic of the two-stage op amp

For simplicity, we will directly re-use the FIVE\_PACK\_OTA of TP1 as the first stage, with the circuit parameters and specifications listed below. Firstly, the FIVE\_PACK\_OTA provides  $>40$  V/V DC gain, leaving  $\sim 30$  V/V DC gain for the second stage. Secondly, to achieve the output swing requirements, we allocate an overdrive voltage of  $\sim 0.3$  V to M6 and M7 each, and luckily,  $|V_{ov6}| = |V_{MID,DC} - V_{DD} - V_{TH,P}| = 0.26$  V  $< 0.3$  V.

I <sub>BIAS</sub>	L <sub>TAIL</sub>	W <sub>TAIL</sub>	F <sub>TAIL</sub>	L <sub>n1</sub>	W <sub>n1</sub>	F <sub>n1</sub>	L <sub>p1</sub>	W <sub>p1</sub>	F <sub>p1</sub>
14 $\mu$ A	720 nm	1 $\mu$ m	3	720 nm	1 $\mu$ m	6	360 nm	1 $\mu$ m	3

Design specifications of FIVE\_PACK\_OTA:

- $V_{IN, DC} = 0.9$  V
- $V_{OUT, DC} = 1.0$  V
- DC gain  $\approx 45$
- Load  $C_L = 2$  pF
- UGB = 20 MHz



Work out the sizes for the second stage by writing out the square-law equations or if you are familiar with any of the design methodologies like  $gm/ID$  or Inversion Coefficient (IC), please feel free to use them.

For hand calculations,  $\mu_n C_{ox} = 278 \mu\text{A/V}^2$ ,  $V_{TH, N} = 0.4$  V,  $\mu_p C_{ox} = 61 \mu\text{A/V}^2$ ,  $|V_{TH, P}| = 0.54$  V.

Here we briefly demonstrate again how to use the  $g_m/I_D$  methodology to facilitate the sizing.

As mentioned before,  $g_{mp6}/C_L \approx 3 * g_{mn3}/C_c$ , thereby  $g_{mp6} \approx 3 \times g_{mn3} = 3 \times 251.2 \mu\text{S} = 753.6 \mu\text{S}$ .

According to  $V_{ov6} = -0.26$  V, we identify the following point in the Excel sheet of  $L_p = 360$  nm, where  $g_m r_o = 59.4$ , which should be sufficient to provide  $\sim 30$  V/V DC gain.


1	L 360nm	V <sub>ov</sub> 360nm	gm 360nm	ID 360nm	gm/ID 360nm	gmro 360nm	ID/W 360nm	gm/W 360nm	gm/C <sub>gg</sub> 360nm	1/(ID.ro) 360nm	VDSAT 360nm	W 360nm	ro 360nm	C <sub>gg</sub> 360nm	gds 360nm
67	3.60E-07	-2.60E-01	4.28E-05	6.55E-06	6.54E+00	5.94E+01	6.55E+00	4.28E+01	1.64E+10	1.10E-01	-2.76E-01	1.00E-06	1.39E+06	2.62E-15	7.21E-07

$$g_m/I_D = 6.54 \rightarrow I_{D6} = 115 \mu A.$$

$I_D/W = 6.55 \rightarrow$  Total width of M6 = 17.6  $\mu\text{m}$  ( $W_{p2} = 1 \mu\text{m}$ ,  $F_{p2} = 18$ ).

$$F_{n2} = I_{D6}/I_{BIAS} = 8.$$

$L_{p2}$	$W_{p2}$	$F_{p2}$	$F_{n2}$
360 nm	1 $\mu$ m	18	8

 

## DC Operating Point using DC Analysis



 Repeat the DC Analysis steps of cascode op amp. Run the simulation. Annotate the DC node voltages / DC operating points and check if they match the desired values. You can also use **Outputs>Add>Expression** to save small-signal variables and calculate the DC gain and the output swing.

gm3	expr	OP("M3" "gm")	259.3u	<input checked="" type="checkbox"/>	<input type="checkbox"/>
ro3	expr	OP("M3" "rout")	292.5K	<input checked="" type="checkbox"/>	<input type="checkbox"/>
ro5	expr	OP("M5" "rout")	455.5K	<input checked="" type="checkbox"/>	<input type="checkbox"/>
gm6	expr	OP("M6" "gm")	758.2u	<input checked="" type="checkbox"/>	<input type="checkbox"/>
ro6	expr	OP("M6" "rout")	61.66K	<input checked="" type="checkbox"/>	<input type="checkbox"/>
ro7	expr	OP("M7" "rout")	100.9K	<input checked="" type="checkbox"/>	<input type="checkbox"/>
ro0	expr	OP("M0" "rout")	653.1K	<input checked="" type="checkbox"/>	<input type="checkbox"/>
gain_1st	expr	$((gm3 * ro3 * ro5) / (r...$	46.19	<input checked="" type="checkbox"/>	<input type="checkbox"/>
gain_2nd	expr	$((gm6 * ro6 * ro7) / (r...$	29.02	<input checked="" type="checkbox"/>	<input type="checkbox"/>
gain	expr	$(gain\_1st * gain\_2nd)$	1.34K	<input checked="" type="checkbox"/>	<input type="checkbox"/>
vdsat7	expr	OP("M7" "vdsat")	243.3m	<input checked="" type="checkbox"/>	<input type="checkbox"/>
vdsat6	expr	OP("M6" "vdsat")	-278.3m	<input checked="" type="checkbox"/>	<input type="checkbox"/>
vout_swing	expr	$((1.8 - vdsat7) + vdsat6)$	1.278	<input checked="" type="checkbox"/>	<input type="checkbox"/>

 


Fig. 11. DC Analysis of two-stage op amp

## Frequency Response using AC Analysis



Repeat the AC Analysis steps. Run the simulation. Plot the frequency response of AC magnitude. Verify the DC gain and UGB.

 


Fig. 12. AC Analysis of two-stage op amp (To improve UGB, you can reduce  $C_c$  a bit)

### Output Swing Check using Transient Analysis



Verify if the output swing is greater than 1.2 V by performing Transient Analysis. How will you set the input DC voltage and Amplitude?